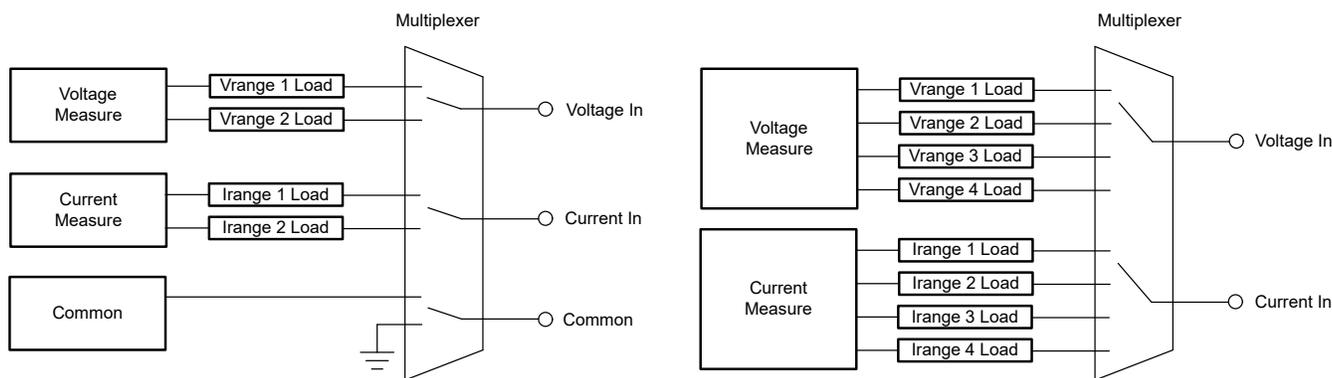


How to Multiplex Multiple Loads to Scale Voltage and Current Measurement Ranges



To enable measurement capability and accuracy across a wide voltage or current range, different resistive and/or capacitive loads are used to scale input signals. A multiplexer is used in between the input signal and the analog to digital converter to switch in and out the different loads that scale the inputs in order to take advantage of the entire dynamic range of the analog to digital converter.



Design Considerations

- Match the input signal range greater than or equal to the supply voltage of the multiplexer. Most multiplexers will only support signals up to the supply voltage provided to the mux.
- Select relatively low on-state resistance multiplexers with respect to the Vrange attenuation resistors to reduce errors and increase system measurement accuracy
- For battery powered systems, select multiplexers with low supply current to maximize battery life
- Learn about multiplexer parameters with [TI precision lab video](#)
- Ask a question on our [TI E2E™ forum](#)

Recommended Parts

Part Number	V _{CC} Range (V)	Configuration	R _{ON} (Ω)	Supply current (uA)	Features
TMUX4052	3 to +/-12	4:1 2-channel	60	20	1.8-V compatible control inputs
TMUX4052-Q1					
TMUX4053		2:1 3-channel			
TMUX1109	1.08 to +/-2.75	4:1 2-channel	1.8	0.008	1.8-V compatible control inputs, Break-before-make, Fail-safe logic
TMUX6209	4.5 to +/-18	4:1 2-channel	4	35	1.8-V compatible control inputs, Break-before-make, Fail-safe logic

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, on-state resistance and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated