

# TAS2120 and TAS2320 Shared Boost Feature and Configuration

---



Ivan Salazar

## ABSTRACT

This document provides an overview of the Shared Boost feature, including the device configuration, performance results, and a reference shared boost system. The document also includes recommendations for stereo and woofer-tweeter implementations, as well as a reference schematic and PCB layout.

Key points mentioned in the document include:

- The TAS2120 has an integrated boost that can be used to power the TAS2320.
  - The shared boost feature simplifies system implementation and reduces cost.
  - The feature is designed for stereo and woofer-tweeter applications, among other multiple speaker applications.
- 

## Table of Contents

|  |           |
|--|-----------|
| <b>1 Introduction</b>                  | <b>2</b>  |
| <b>2 Feature Description</b>           | <b>2</b>  |
| 2.1 EVM Setup for PPC3 Configuration   | 3         |
| 2.2 Device Configuration               | 4         |
| <b>3 Performance Results</b>           | <b>6</b>  |
| <b>4 Reference Shared Boost System</b> | <b>7</b>  |
| 4.1 Reference Schematic                | 8         |
| 4.2 Reference PCB Layout               | 11        |
| <b>5 Summary</b>                       | <b>13</b> |
| <b>6 References</b>                    | <b>13</b> |

## Trademarks


All trademarks are the property of their respective owners.



## 2.1 EVM Setup for PPC3 Configuration

The shared boost configuration can be tested using TAS2120EVM, TAS2320EVM and the AC-MB controller board provided in either of the EVM kits. With this EVM connection, PPC3 can be used to generate the required command script that is used on the end application for testing and final configuration.

The necessary connections between the boards are described in [Figure 2-2](#).

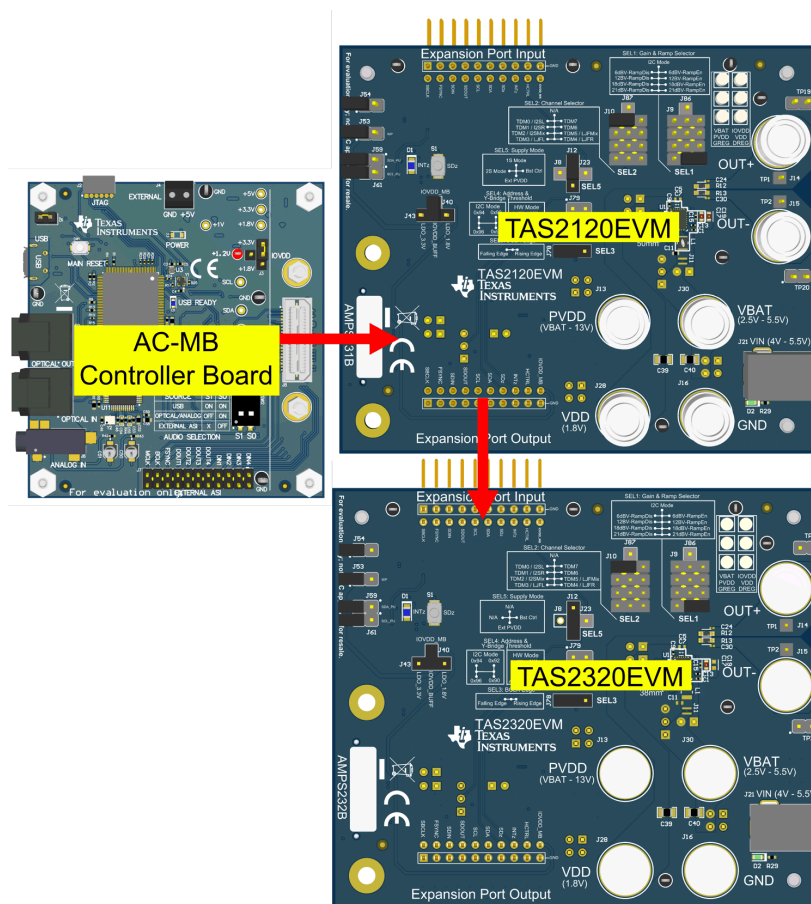

**Figure 2-2. TAS2120 and TAS2320 EVM Setup**


The hardware settings on EVM must be modified as described in [Table 2-1](#).

**Table 2-1. EVM Jumper Configuration for Shared Boost Mode**

|  | TAS2120EVM                    | TAS2320EVM                    |
|--|-------------------------------|-------------------------------|
| J54 (Top)  | Open                          | Short                         |
| SEL1 (Top)   | I2C Mode                      | I2C Mode                      |
| SEL2 (Top)   | Open                          | Open                          |
| SEL3 (Top)   | Open / 00 / SDA               | Open / 00 / SDA               |
| SEL4 (Top)   | 0x90 / 0001                   | 0x92 / 0010                   |
| SEL5 (Top)   | Bst Ctrl / 0001               | Bst Ctrl / 0001               |
| PVDD (J13) (Top)                                     | Connect to PVDD on TAS2320EVM | Connect to PVDD on TAS2120EVM |
| VBAT (J30) (Top)                                     | Connect to VBAT on TAS2320EVM | Connect to VBAT on TAS2120EVM |
| External Boost Jumpers (Bottom)<br>J1, J17, J24, J20 | Open                          | Open                          |

## 2.2 Device Configuration

PPC3 software has all the required controls to enable the shared boost feature. TAS2120EVM must be connected to a TAS2320EVM so that PPC3 detects the hardware combination.

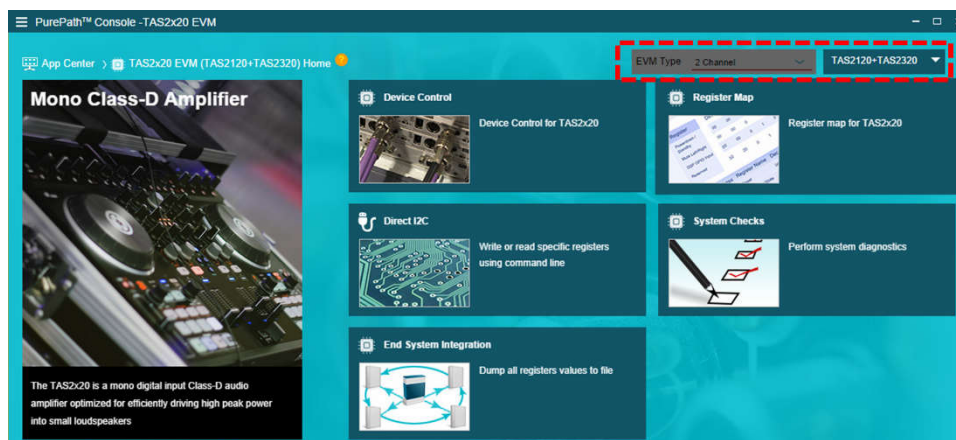


**Figure 2-3. TAS2120+TAS2320 PPC3 Mode**

### 2.2.1 Stereo Implementation Recommendations

Given that the total 8W of power from TAS2120 boost is shared across TAS2120 and TAS2320, the analog gain of both amplifiers must be reduced such that the total output power is not overloading the boost. For example, when using 8Ω load on both amplifiers, the analog gain (AMP\_LVL on register 0x07 at page 0) needs to be set to 15dBV or lower. Similarly, for 4Ω loads the analog gain need to be set to 12dBV or lower.

The gain allocation explained above is considering the worst case where both channels are playing the same signal at full volume, which is not very common for most audio content being music or dialog tracks. This means the gain can be increased in most cases.

For best results, gain needs to be fine-tuned based on the application requirements, speaker sensitivity and intended playback content.

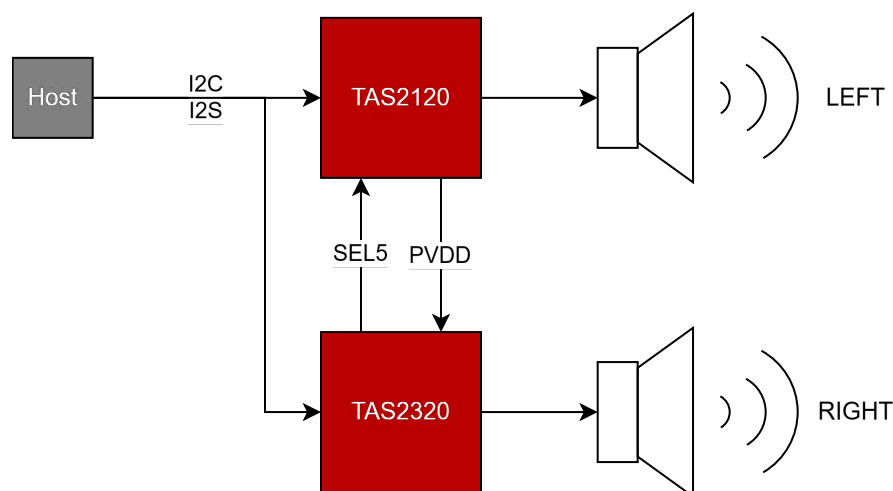

**Figure 2-4. Stereo Application**

## 2.2.2 Woofer-Tweeter Implementation Recommendations

On a Woofer-Tweeter application the power and frequency content can be differentiated between TAS2120 and TAS2320.

For example, TAS2120 is used to drive the Tweeter, using PPC3 the digital high-pass filter can be set to 1kHz and the gain to the maximum 21dBV. TAS2320 is used to drive the Woofer, the high-pass filter can be set to default 2Hz and the gain is also set to maximum 21dBV.

The gain for each amplifier can be fine tuned based on the sensitivity of each speaker.

### Playback

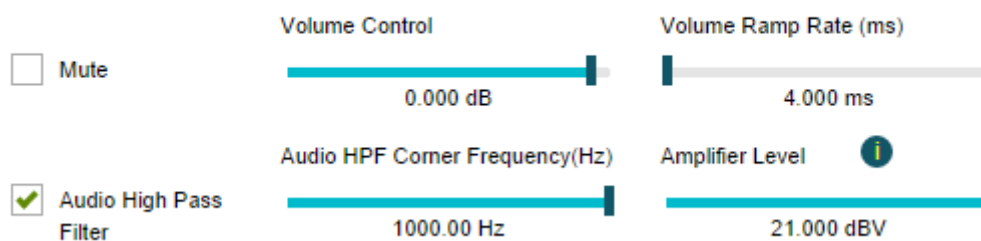


Figure 2-5. HPF Configuration TAS2120

### Playback

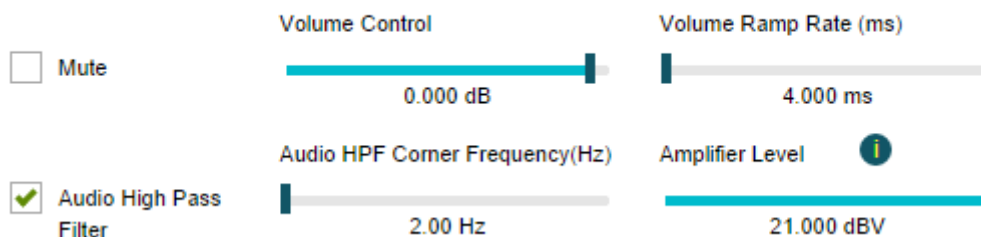


Figure 2-6. HPF Configuration TAS2320


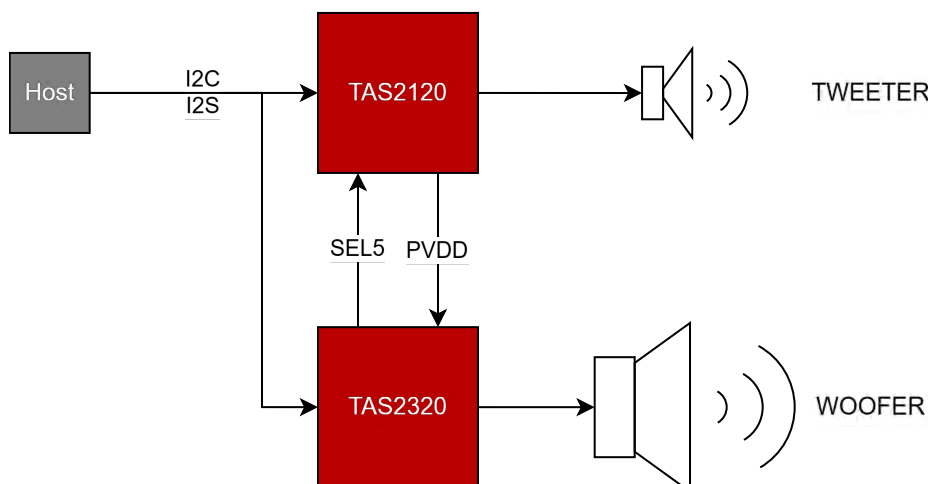


Figure 2-7. Woofer-Tweeter Application

### 3 Performance Results

A reference shared boost system was configured for an analog gain of 18dBV on both TAS2120 and TAS2320. The schematic and PCB design information for this hardware implementation is available in [Reference Shared Boost System](#).

Figure 3-1 shows the distortion and output power performance obtained using this setup. This shows that when only one of the amplifiers is driving the speaker, the undistorted output is higher, whereas driving both speakers equally at the same time can split the total power for each channel.

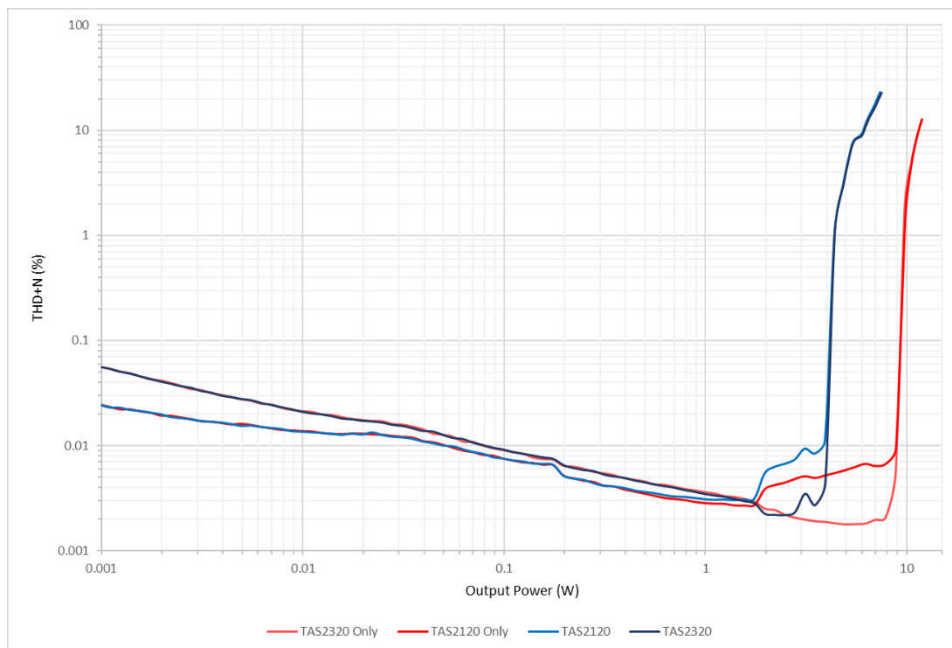

**Figure 3-1. THD+N vs Pout Shared Boost Performance (4Ω)**

## 4 Reference Shared Boost System

This section provides a reference design for a shared boost application. The performance curves included in [Section 3](#) were tested on this reference evaluation platform.

This reference platform is powered from a >45W USB-C adapter. The TPS25730 resistors for ADCINx can be adjusted for different power setups.

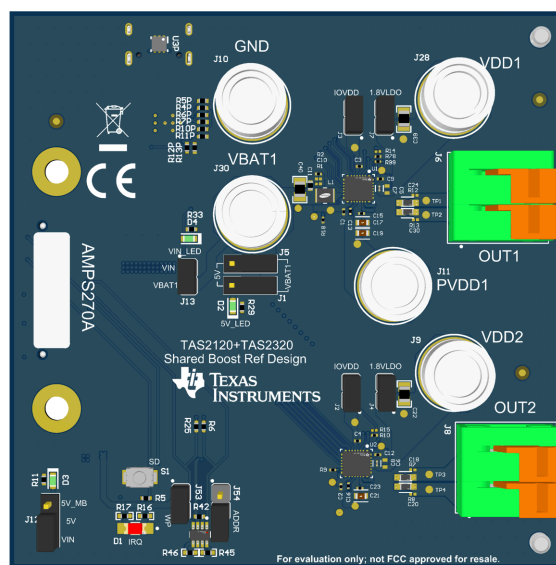


Figure 4-1. Reference Shared Boost Platform Top View



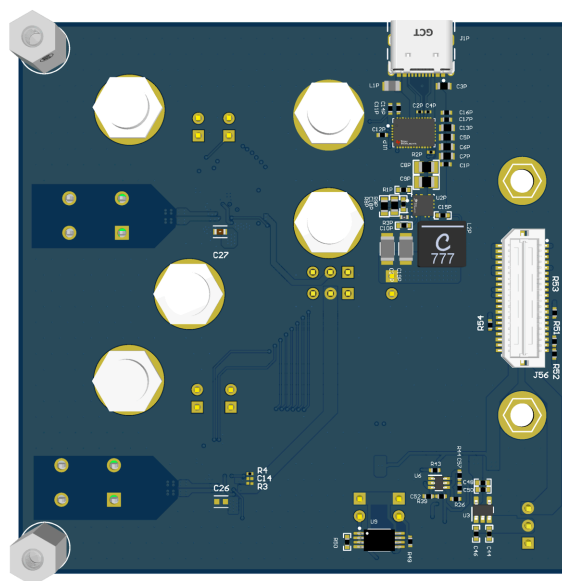


Figure 4-2. Reference Shared Boost Platform Bottom View

### 4.1 Reference Schematic

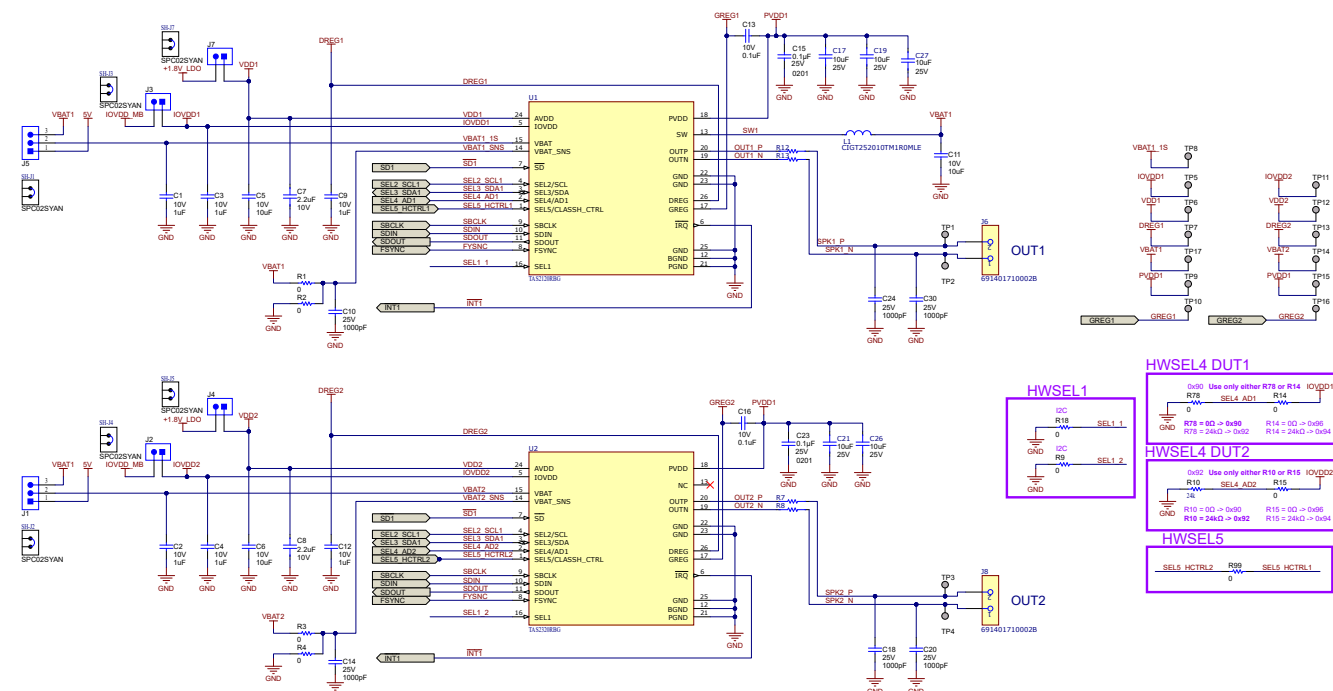
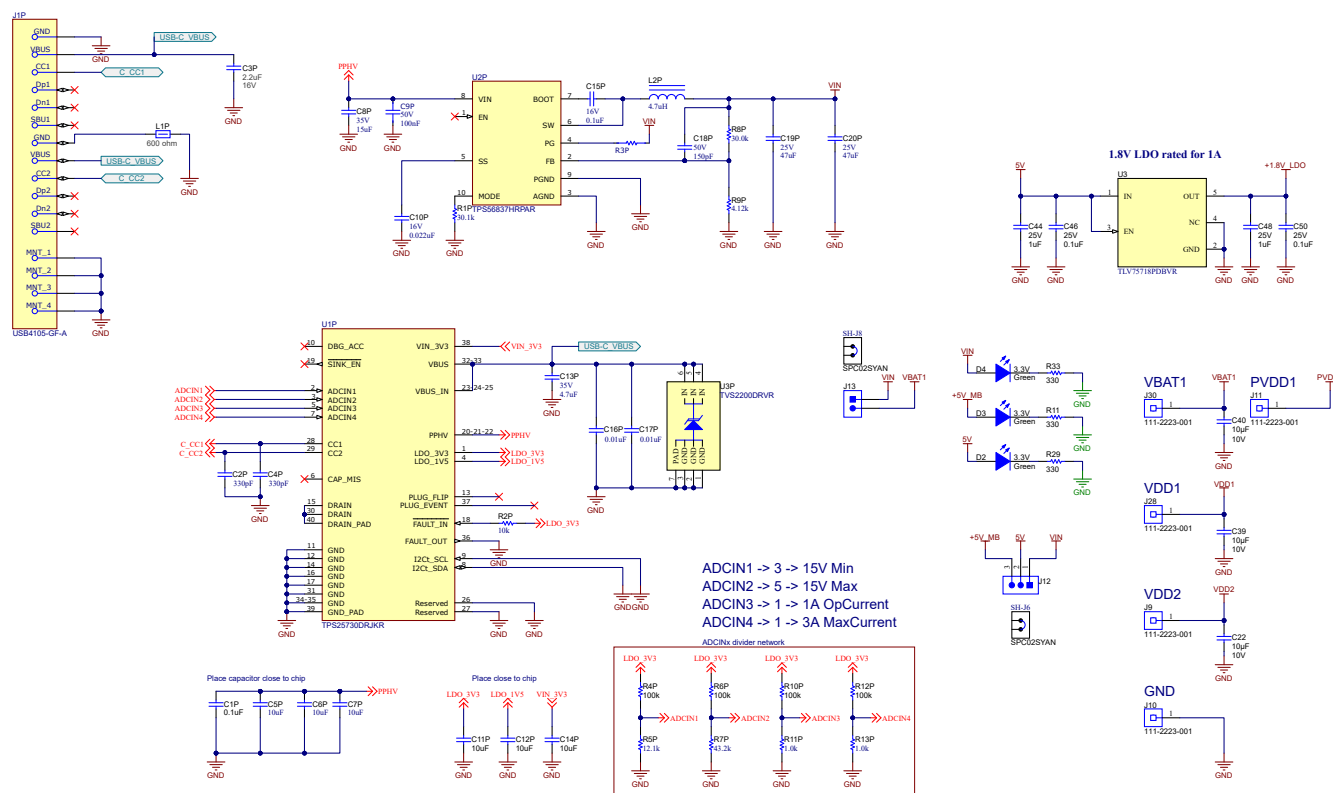
### Figure 4-3. TAS2120 and TAS2320 Schematic



### Figure 4-4. Power Supply Schematic




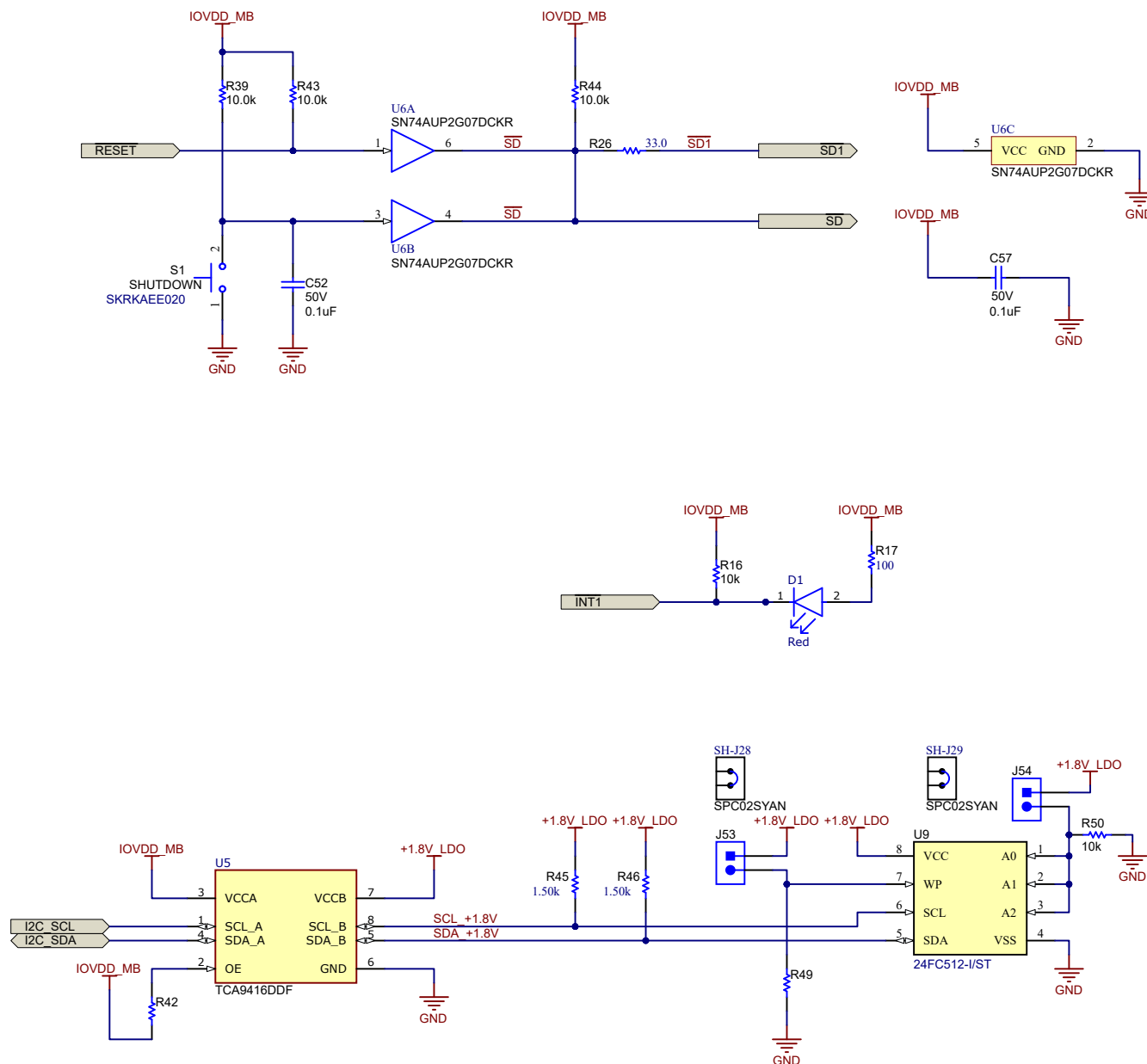


Figure 4-5. IRQ, SD and EEPROM Schematic

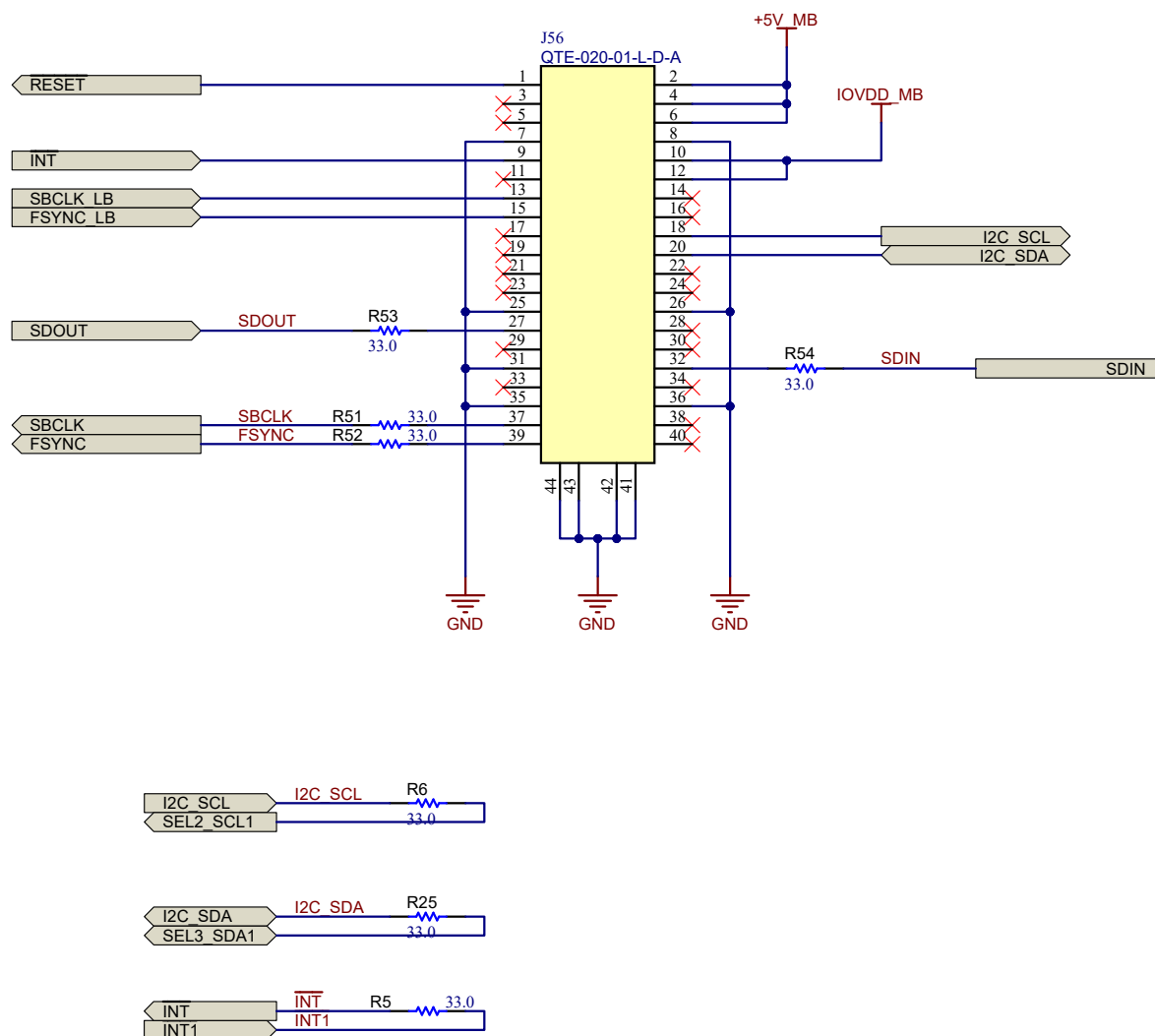

**Figure 4-6. IO Connector Schematic**

## 4.2 Reference PCB Layout

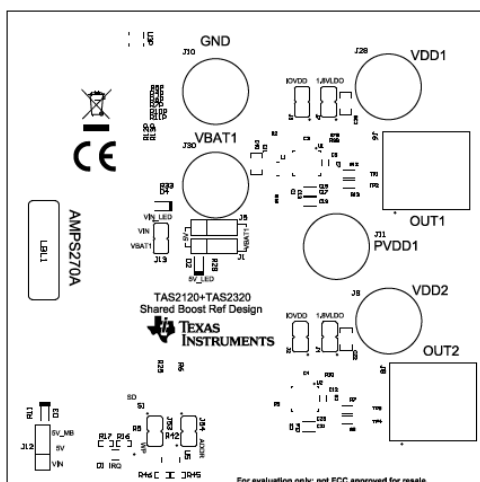


Figure 4-7. Top Overlay

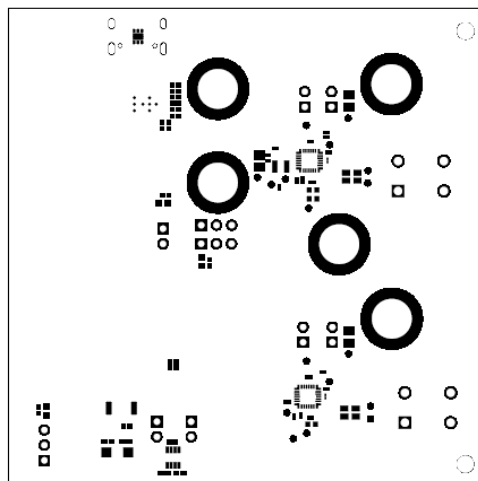


Figure 4-8. Top Solder Mask

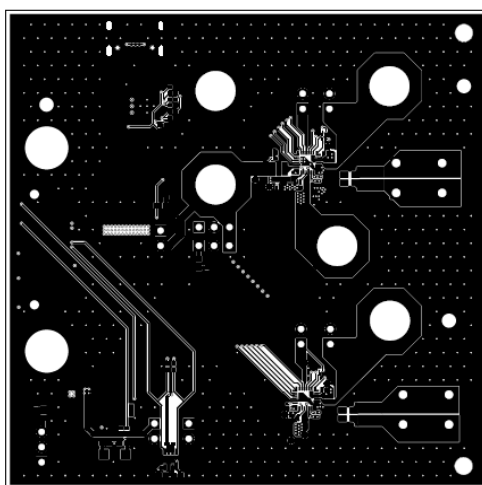


Figure 4-9. Layer 1

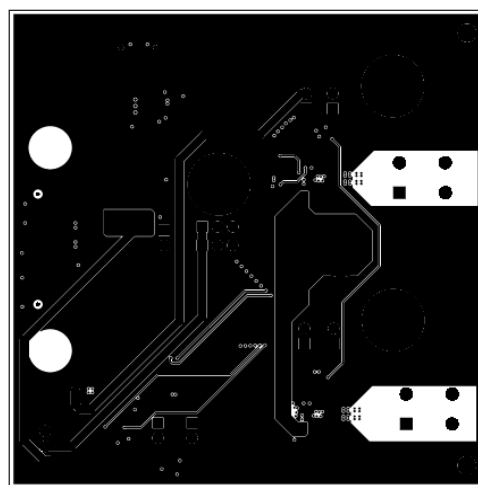


Figure 4-10. Layer 2

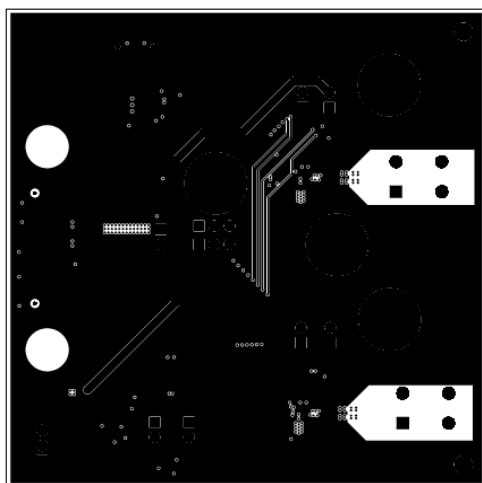


Figure 4-11. Layer 3



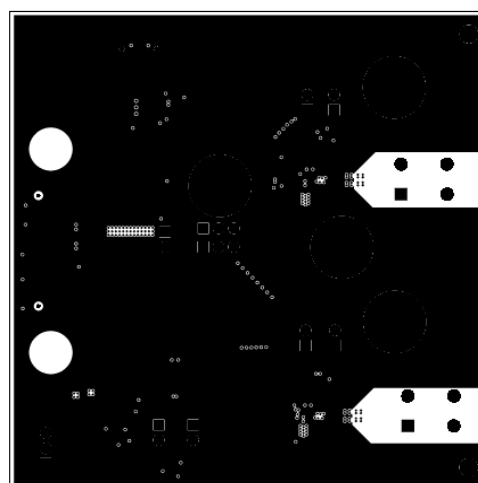



Figure 4-12. Layer 4

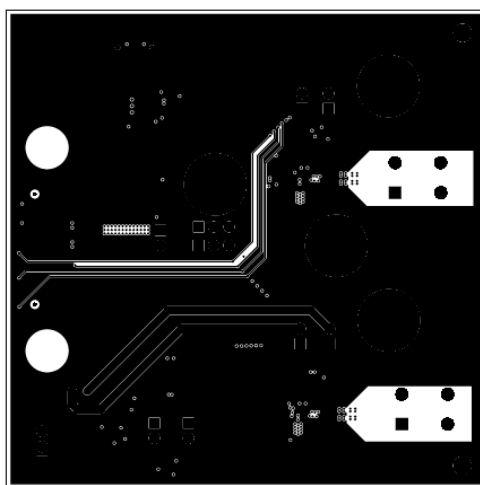


**Figure 4-13. Layer 5**

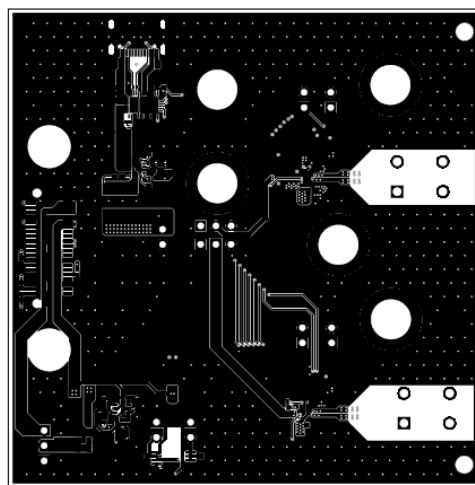

**Figure 4-14. Layer 6**

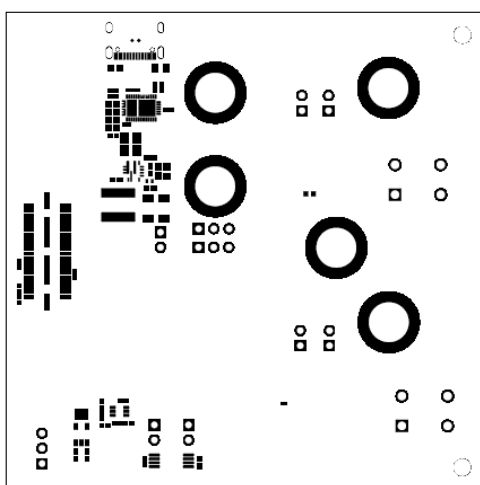

**Figure 4-15. Bottom Solder Mask**

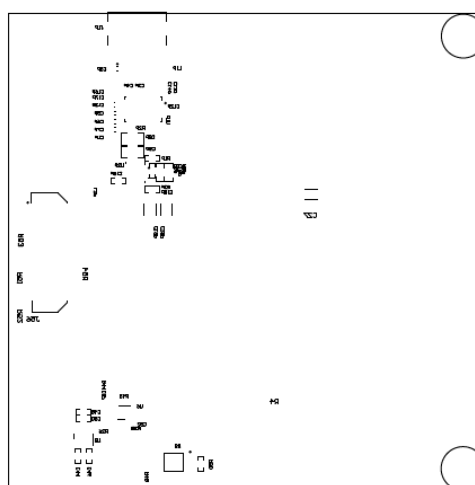

**Figure 4-16. Bottom Overlay**

## 5 Summary

The flexible configuration of TAS2120 makes it possible to supply a companion TAS2320 using the integrated boost in TAS2120. This greatly simplifies the system implementation for stereo or woofer-tweeter applications, reducing the BOM, design size and cost.

## 6 References

1. Texas Instruments, [TAS2120 8.2W Mono Digital Input Class-D Speaker Amp with Integrated 14.75V Class-H Boost](#), data sheet.
2. Texas Instruments, [TAS2320 15W Mono Digital Input Class-D Speaker Amp with 15V Support](#), data sheet.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2025, Texas Instruments Incorporated