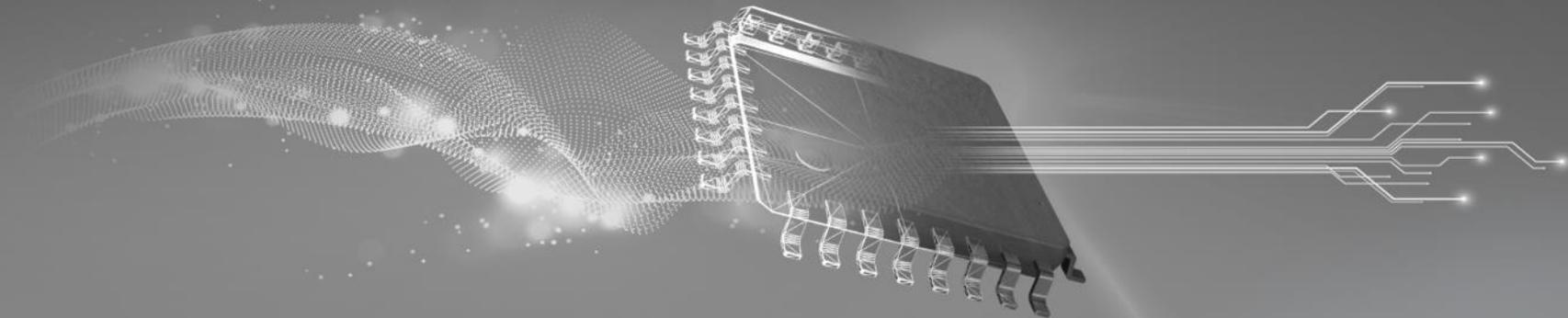


TI TECH DAYS




New TI smart analog and smart DAC for adding intelligence to analog without software at low cost

Uttama Sahu

Data Converters - DAC


Abstract

- System designers often need simple software solutions to attain predictable system power up and tunable set points
- TI's innovative smart AFE and smart DAC portfolio provides simple intelligence to an analog system designer without the need for MCUs
- TI's smart analog products, have NVM and factory programmable state machines, internal ADCs, DACs, PWM generators, custom waveform generators
- Analog and software engineers can reduce system costs, remove tiny MCUs, and expedite design cycles

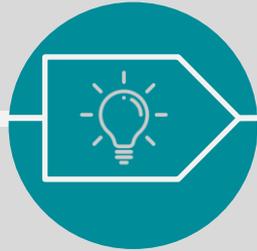

Smart DACs

Control w/o software

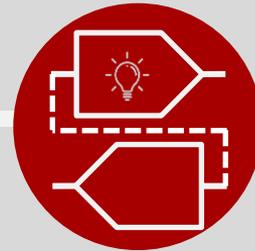



Smart AFEs

Sensing and control w/o software


Agenda

- Current day challenges in system design
- What are smart DACs and smart analog
- Example smart DACs
- Smart DAC applications
- Example smart analog
- Smart analog applications
- Summary

Current-day challenges in system design






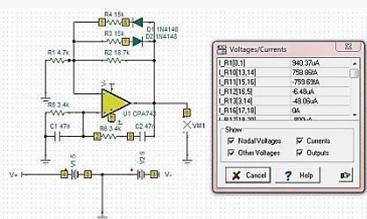
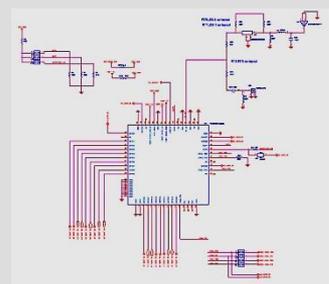
	Design	Pros	Cons																
Discrete circuit	 <p>The image shows a circuit schematic with an operational amplifier (U1) and several resistors (R1, R2, R3, R4, R5, R6, R7, R8, R9, R10, R11, R12, R13, R14, R15, R16, R17, R18, R19, R20, R21, R22, R23, R24, R25, R26, R27, R28, R29, R30, R31, R32, R33, R34, R35, R36, R37, R38, R39, R40, R41, R42, R43, R44, R45, R46, R47, R48, R49, R50, R51, R52, R53, R54, R55, R56, R57, R58, R59, R60, R61, R62, R63, R64, R65, R66, R67, R68, R69, R70, R71, R72, R73, R74, R75, R76, R77, R78, R79, R80, R81, R82, R83, R84, R85, R86, R87, R88, R89, R90, R91, R92, R93, R94, R95, R96, R97, R98, R99, R100). A simulation window titled 'Voltages/Currents' is open, showing a table of values for various nodes in the circuit.</p> <table border="1"><thead><tr><th>Node</th><th>Value</th></tr></thead><tbody><tr><td>U1P101(1)</td><td>940.37uA</td></tr><tr><td>U1P101(1,14)</td><td>759.865A</td></tr><tr><td>U1P101(1,5)</td><td>-759.879A</td></tr><tr><td>U1P101(5)</td><td>4.48uA</td></tr><tr><td>U1P101(14)</td><td>-48.05uA</td></tr><tr><td>U1P101(20)</td><td>0A</td></tr><tr><td>U1P101(20,1)</td><td>0A</td></tr></tbody></table>	Node	Value	U1P101(1)	940.37uA	U1P101(1,14)	759.865A	U1P101(1,5)	-759.879A	U1P101(5)	4.48uA	U1P101(14)	-48.05uA	U1P101(20)	0A	U1P101(20,1)	0A	<ul style="list-style-type: none">• Low Cost• Optimized design	<ul style="list-style-type: none">• Difficult to design• Difficult to scale / reuse• Needs strong analog design expertise• Many components need bigger area
Node	Value																		
U1P101(1)	940.37uA																		
U1P101(1,14)	759.865A																		
U1P101(1,5)	-759.879A																		
U1P101(5)	4.48uA																		
U1P101(14)	-48.05uA																		
U1P101(20)	0A																		
U1P101(20,1)	0A																		
MCU-based circuit	 <p>The image shows a complex circuit schematic with a central microcontroller unit (MCU) and numerous peripheral components, including resistors, capacitors, and integrated circuits, connected to various pins of the MCU.</p>	<ul style="list-style-type: none">• Manages complexity• Easy to reuse	<ul style="list-style-type: none">• Software dependence for simple logic and configuration• Higher R&D time and cost• Software maintenance and certification overhead																

Why smart DACs and smart AFEs

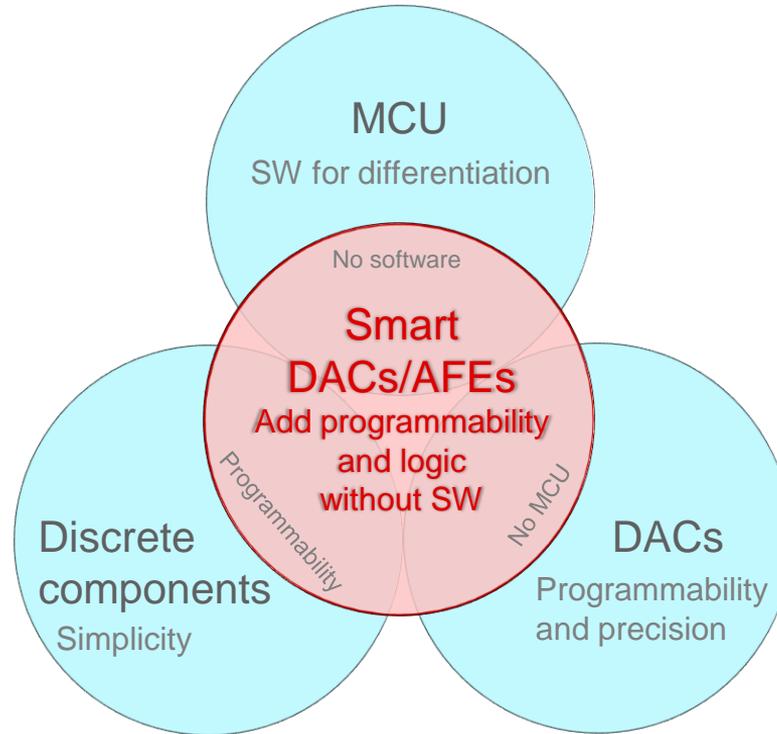


Analog design is fun. Adding programmability is not ... **Now you have smart DACs and smart AFEs**

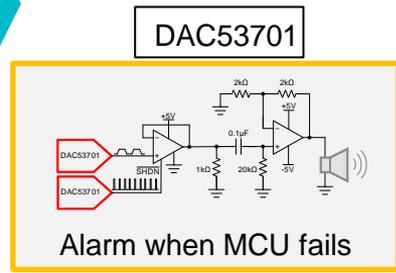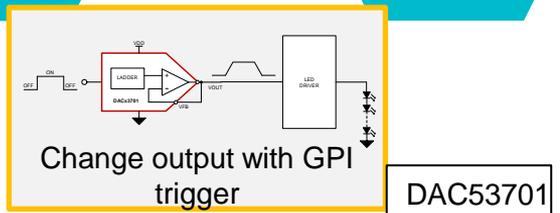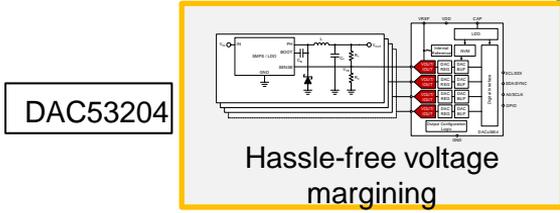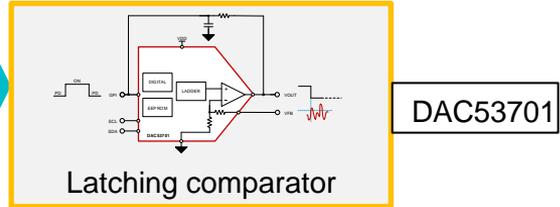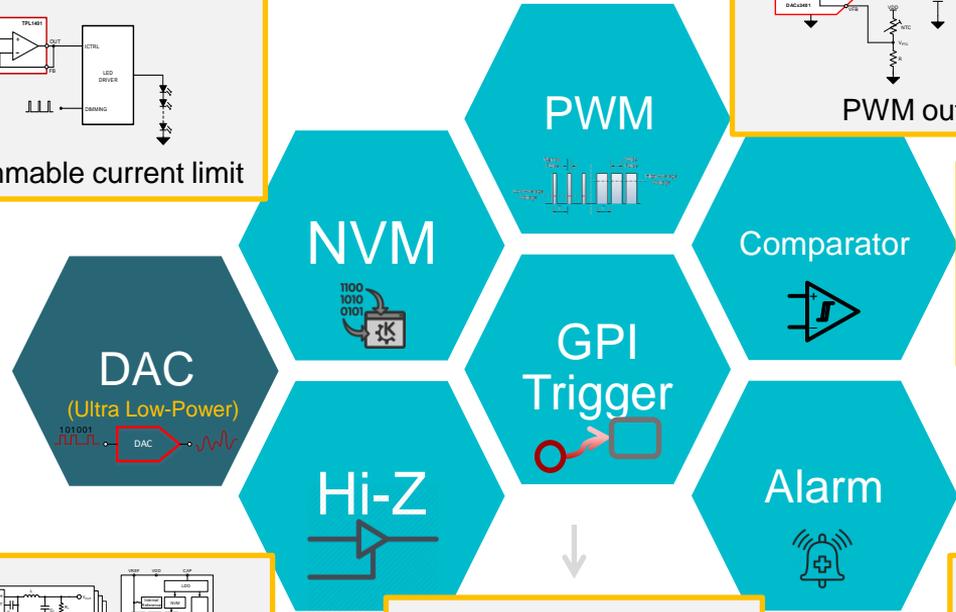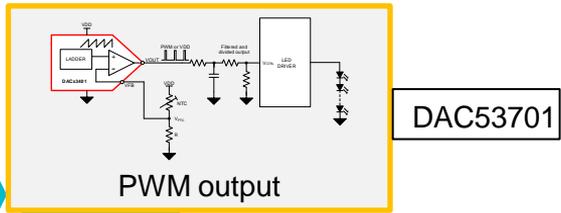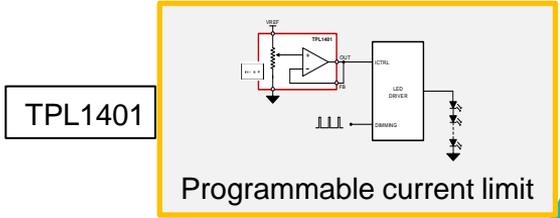What is a smart DAC? - control w/o software





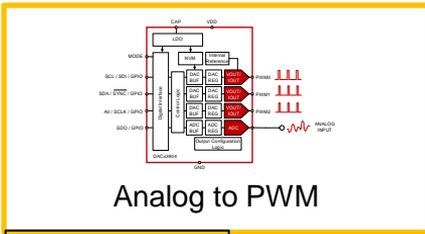What is smart AFE? - sensing and control (w/o software)




Analog to PWM

AFE539B4-Q1

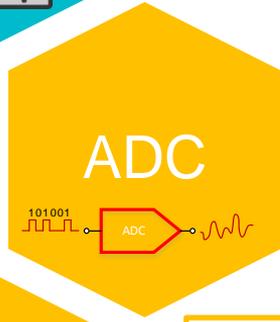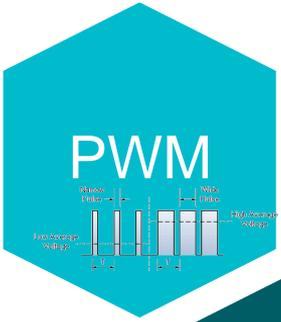


AFE53902-Q1


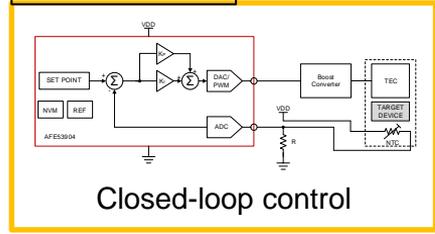


Closed-loop control

DAC53902-Q1

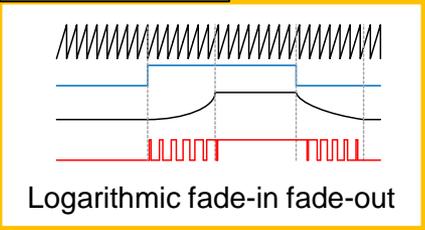

Logarithmic fade-in fade-out

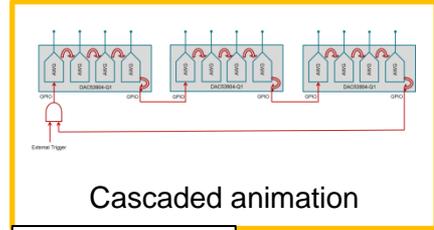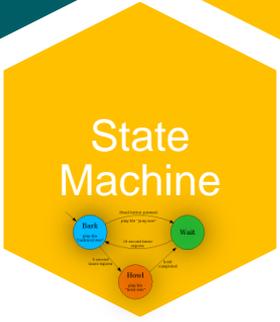


Cascaded animation

DAC539x4-Q1

An example smart DAC


- Internal reference with 1% accuracy
- User programmable Nonvolatile memory
- Buffered wiper for improved load regulation
- Hi-Z or programmable start-up using NVM
- Lock bit to protect accidental writes to register or NVM
- I2C interface
- Wide temperature range: -40°C to $+125^{\circ}\text{C}$
- Small package WQFN-8 (2x2)

TPL1401

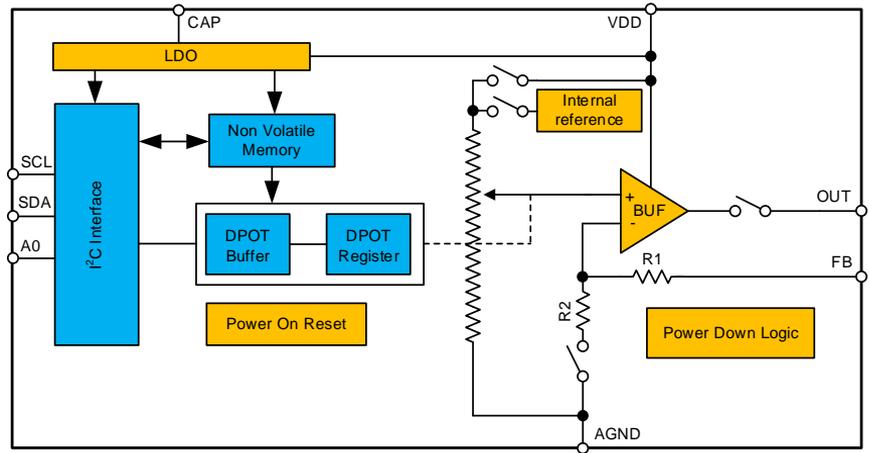


Generating a DC set-point

Resistor divider

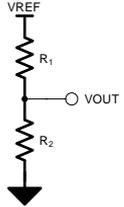


- Simple circuit
- No programmability
- No load regulation
- External reference

LASER trimming

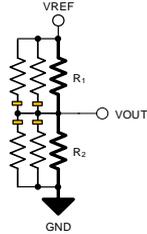


- Limited programmability
- No load regulation
- External reference

Shunt regulator

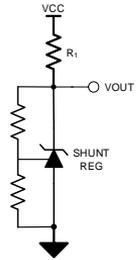


- No programmability
- No load regulation

Load regulation

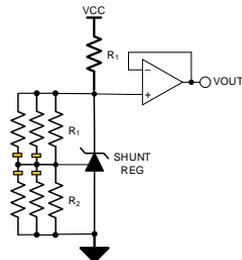


- Large area
- Limited programmability

TPL1401 differentiation

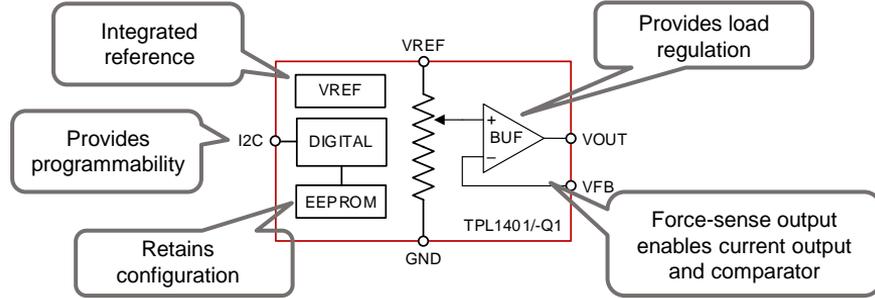


Example application

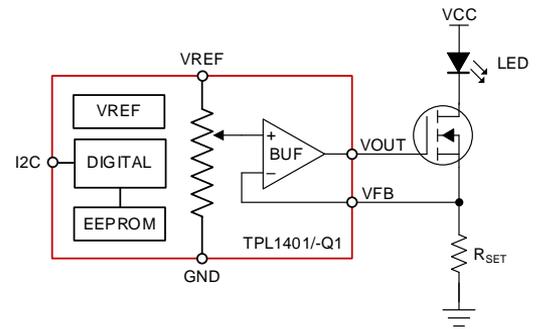


Adjustable current limit


LED driver, DC-DC converter

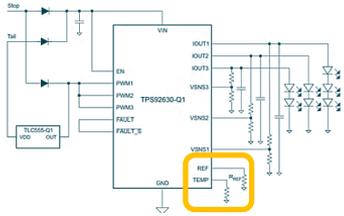


E-fuse, High-side switch

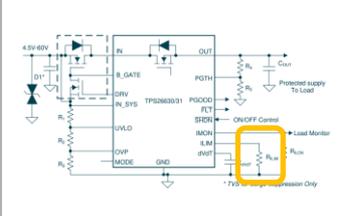


Power amplifier

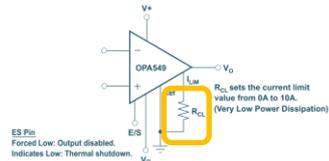

Standalone battery charger

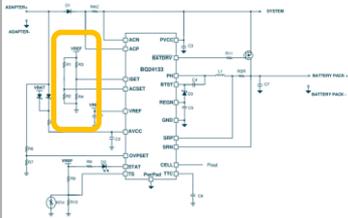


Standard digipot

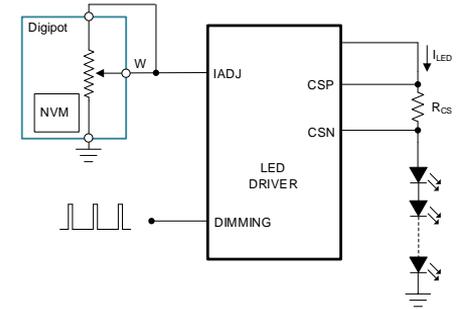


- Digipots are commonly available in 20% tolerance
- Higher accuracy digipots are expensive

TPL1401 differentiation

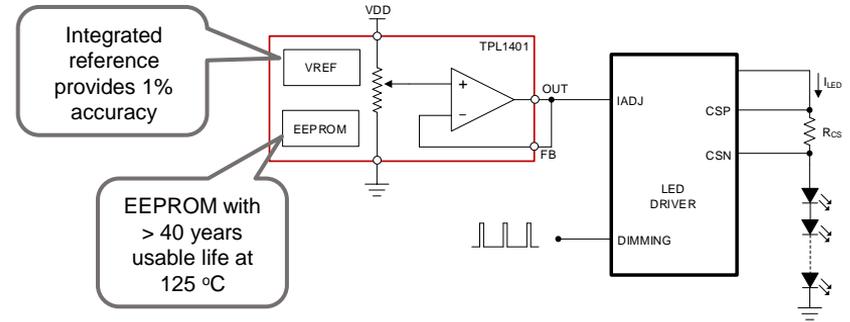


LASER diode analog power control (APC)

Resistor divider

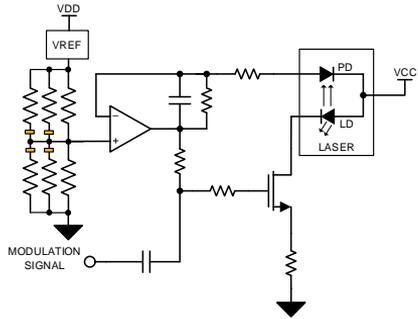

- External reference
- Limited programming steps
- Larger area

Standard digipot

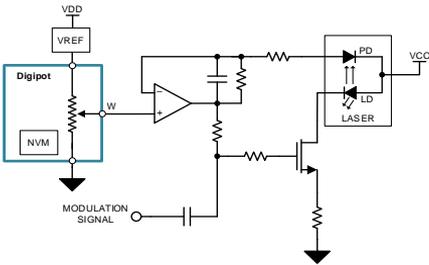


- External reference
- Digital programmability
- Larger area

TPL1401 differentiation

Program at factory and eliminate run-time programming

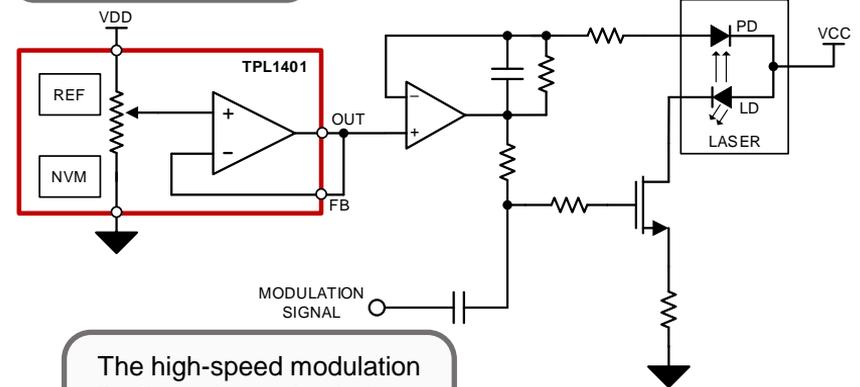Simple way to set an accurate bias point for the LASER




The high-speed modulation DAC need not take the load of controlling the biasing dynamically

An example smart DAC



- GPIO configurable as power-down, PWM input, function trigger, or fade-in fade-out trigger
- User programmable Nonvolatile memory
- PWM output using free-running triangular waveform and FB pin
- I2C interface
- Wide temperature range: -40°C to $+125^{\circ}\text{C}$
- Small package WQFN-8 (2x2)

DAC53701-Q1

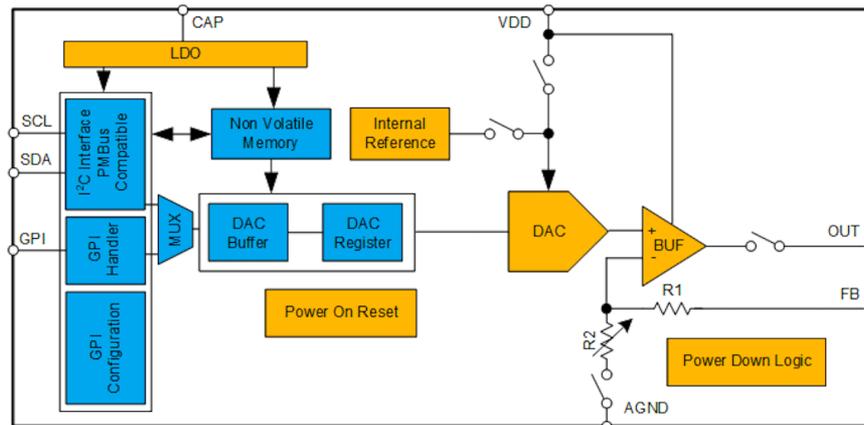

Appliance light fade-in fade-out

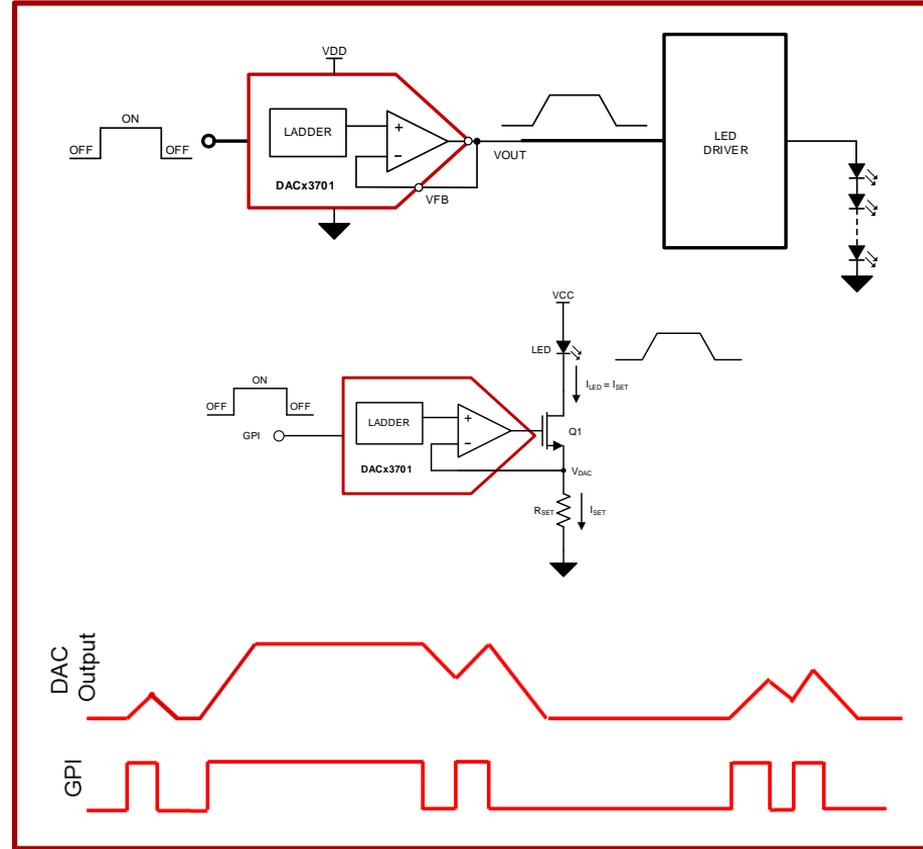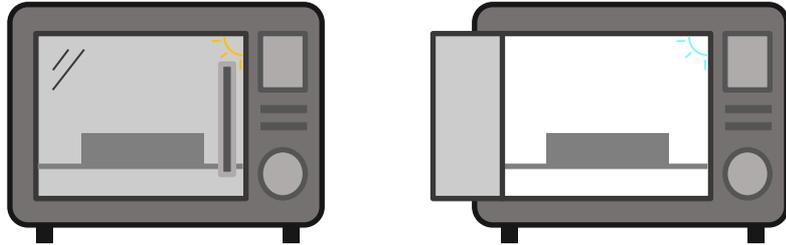- GPI based fade-in fade-out
- Programmable slew rates from milliseconds to 5 seconds
- Programmable min and max output levels
- GPI can be directly connected to mechanical switch without MCU/software
- DAC can drive either an LED driver or directly drive LEDs using a MOSFET






Voltage margining and scaling

- Hi-Z power-down by default
- Digital slew rate control for glitch-free voltage scaling
- GPI to take the output to Hi-Z or other safe level when software crashes or during brown-out
- I2C and PMBus compatible interface
- NVM for predictable power-up


$$I_{\text{MARGIN}} = \left(\frac{V_{\text{OUT}} \times (1 + \text{MARGIN}) - V_{\text{FB}}}{R_1} \right) - I_{\text{NOMINAL}}$$

$$R_3 = \frac{|V_{\text{DAC}} - V_{\text{FB}}|}{I_{\text{MARGIN}}}$$

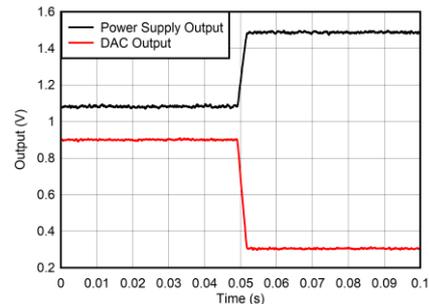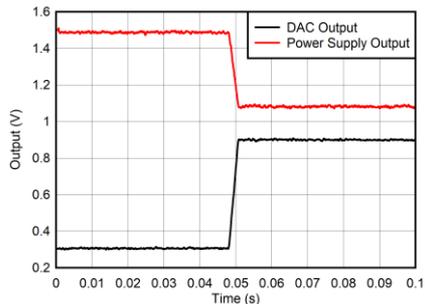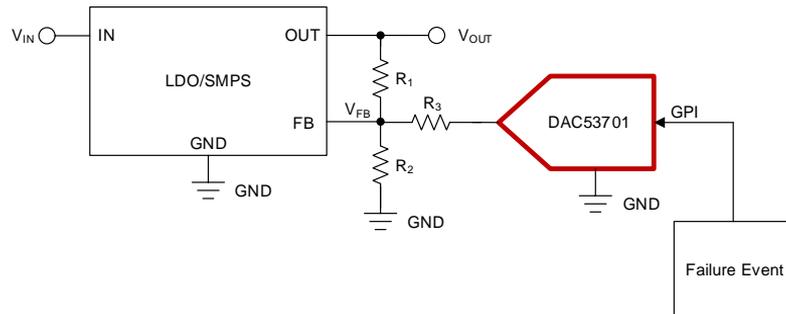

Programmable comparator

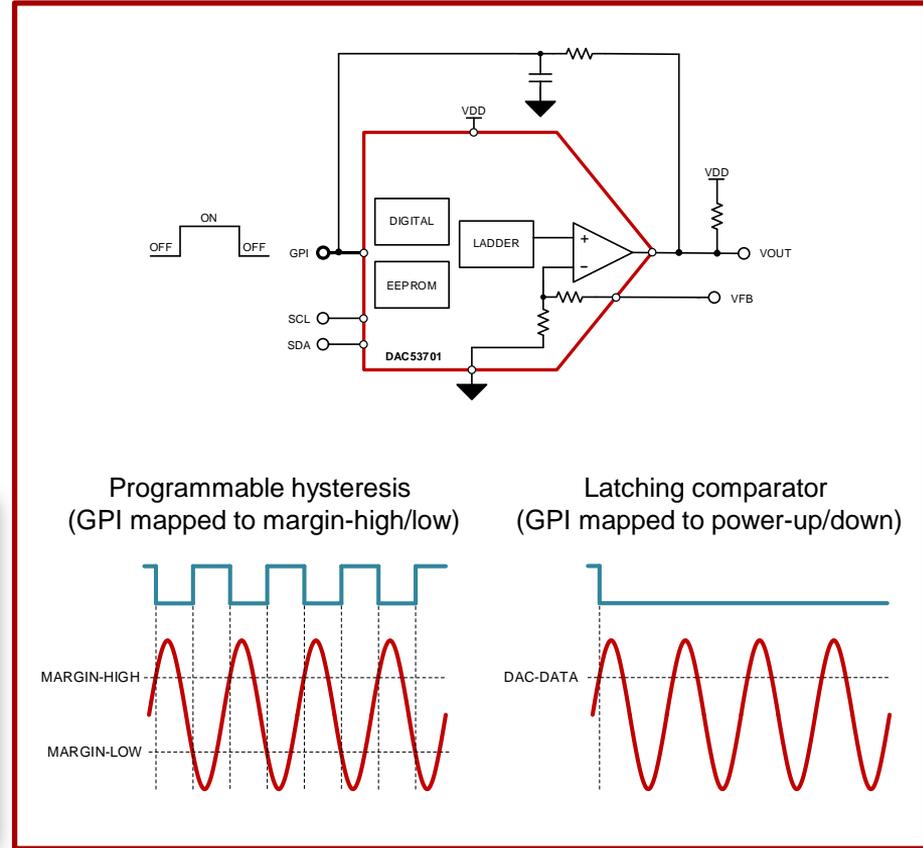- Programmable hysteresis and latching functions independent of MCU
- 10-bit comparator threshold
- 10-bit hysteresis programmed using margin-high and margin-low registers
- Latching comparator function
- EEPROM retention > 40 years at 125 °C operating temperature, suitable for industrial applications



Programmable comparator

- Comparator threshold is programmed in DAC-DATA register
- GPI is unmapped

Programmable hysteresis


- GPI mapped to margin-high (GPI HIGH) and margin-low (GPI LOW)
- DAC-DATA is same as either margin-high or margin-low
- DAC output is pulled up by a resistor to VDD

Latching comparator

- GPI mapped to power-up (GPI HIGH) and power-down to 10K (GPI LOW)
- DAC-DATA is the comparator threshold
- DAC output is pulled up by a resistor to VDD

Medical alarm

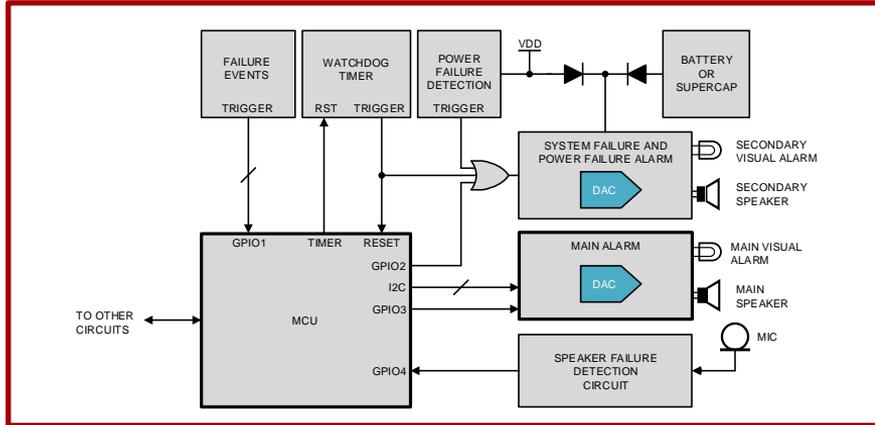- In-built alarm timings as per IEC60601-1-8 standard – register based configuration
- One DAC is used for generating the trapezoid with timing and gain control
- Another DAC is used to generate the alarm tone
- Directly trigger high-priority alarm using GPI
- Low-power consumption enables smaller battery back-up for power failure alarm



Pulse

- Pulse frequency shall be between 150 Hz and 1 kHz
- There shall be 4 harmonics between 300 Hz and 4 kHz
- These 4 harmonics shall be within ± 15 dB of each other
- The harmonics shall be measured in the acoustic domain

Pulse Envelope


- Specifies the rise and fall times (7.5 ms to 100 ms)
- Measured in the acoustic domain
- This signal block repeats within an alarm burst

Burst

- The pattern of the burst varies based on the alarm priority
- There are 3 alarm priorities
- Medical equipment manufacturers choose different timings and frequency as per their preference

Temperature to PWM converter

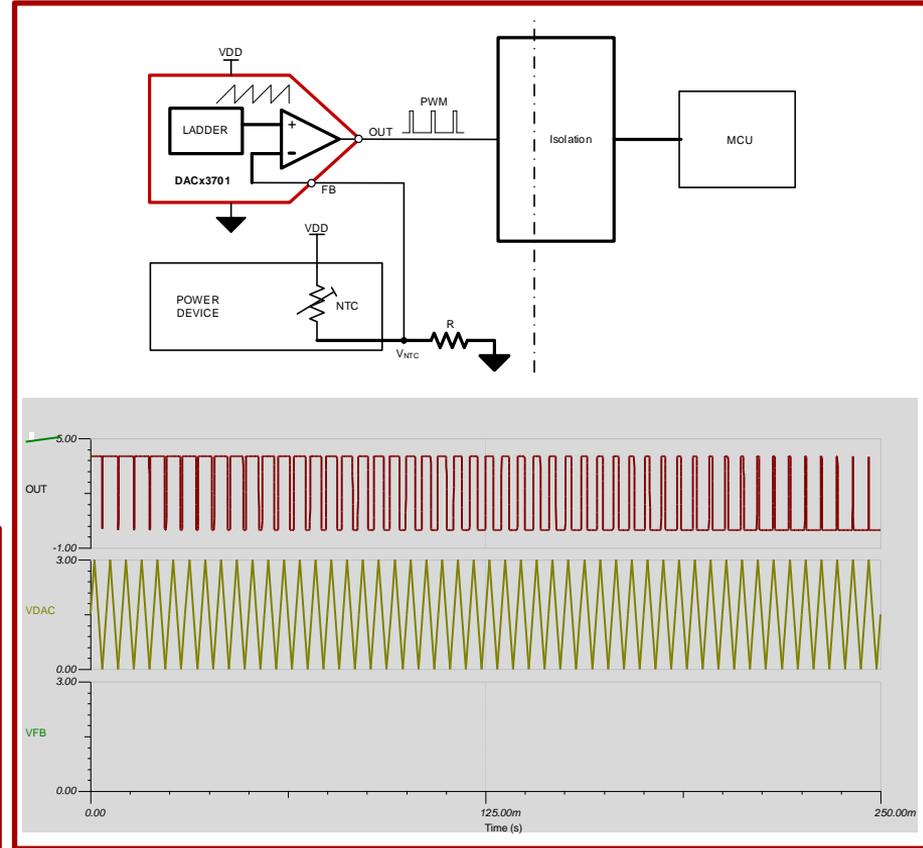- NTC resistance to PWM conversion
- PWM interfaces needs only single-wire – suitable for isolation barriers
- PWM duty cycle proportional to NTC resistance
- Factory programming of PWM frequency through triangular / sawtooth waveform in NVM
- No run-time software required




$$f_{\text{TRIANGLE-WAVE}} = \frac{1}{2 \times \text{SLEW_RATE} \times \left(\frac{\text{MARGIN_HIGH} - \text{MARGIN_LOW} + 1}{\text{CODE_STEP}} \right)}$$

$$f_{\text{SAWTOOTH-WAVE}} = \frac{1}{\text{SLEW_RATE} \times \left(\frac{\text{MARGIN_HIGH} - \text{MARGIN_LOW} + 1}{\text{CODE_STEP}} \right)}$$

STOP tail lighting

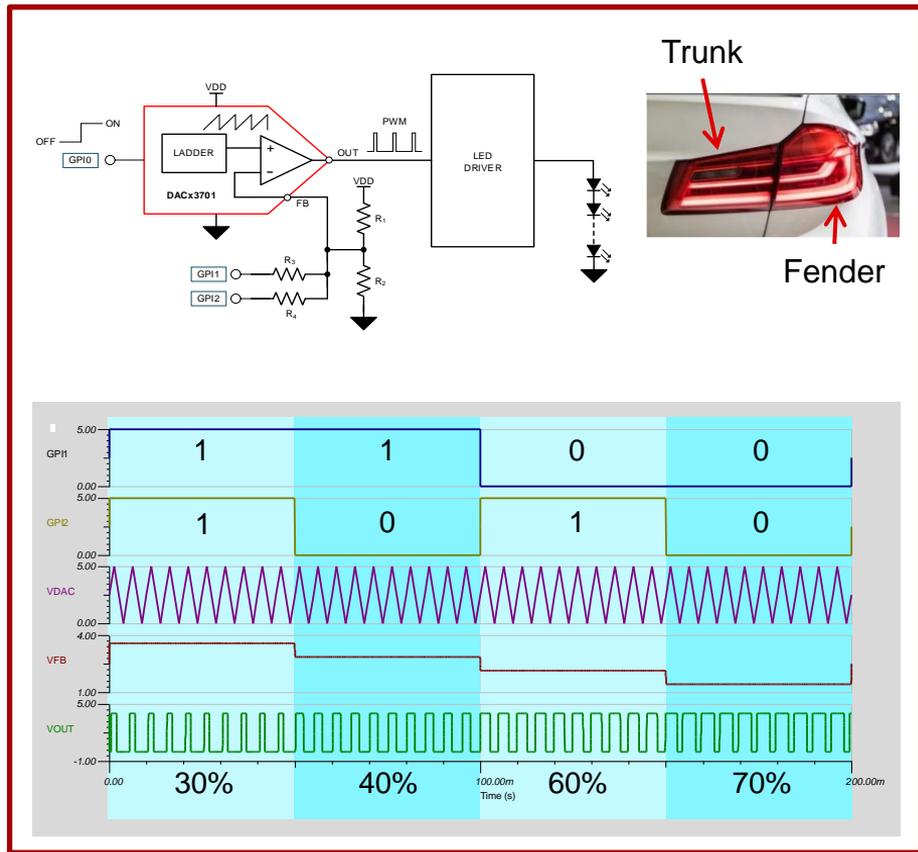- PWM (~200 Hz) with constant duty cycle
- GPI based dimming when trunk is opened or closed
- Software programmability of PWM frequency through triangular / sawtooth waveform
- Better intensity matching between the trunk and fender lights (< 1% duty cycle accuracy) as compared to 555 timers




$$f_{\text{TRIANGLE-WAVE}} = \frac{1}{2 \times \text{SLEW_RATE} \times \left(\frac{\text{MARGIN_HIGH} - \text{MARGIN_LOW} + 1}{\text{CODE_STEP}} \right)}$$

$$f_{\text{SAWTOOTH-WAVE}} = \frac{1}{\text{SLEW_RATE} \times \left(\frac{\text{MARGIN_HIGH} - \text{MARGIN_LOW} + 1}{\text{CODE_STEP}} \right)}$$

LED and temperature

LED reliability

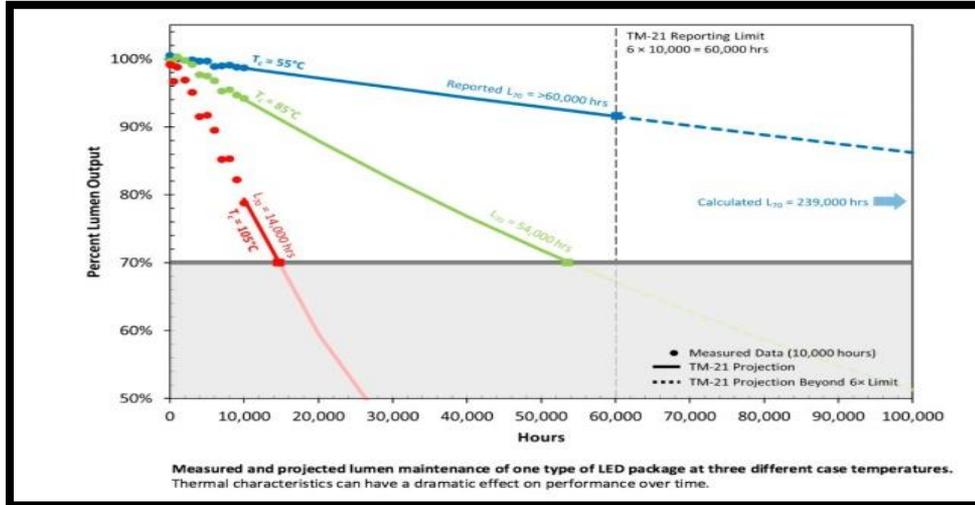

Source: <https://www.linkedin.com/pulse/high-temperature-enemy-led-performance-what-you-need-know-floroiu/>


Daytime running light (DRL)



- LED reliability is significantly determined by the operating temperature
- LEDs in DRLs are heated by both self-heating and sunlight

Single-slope thermal foldback

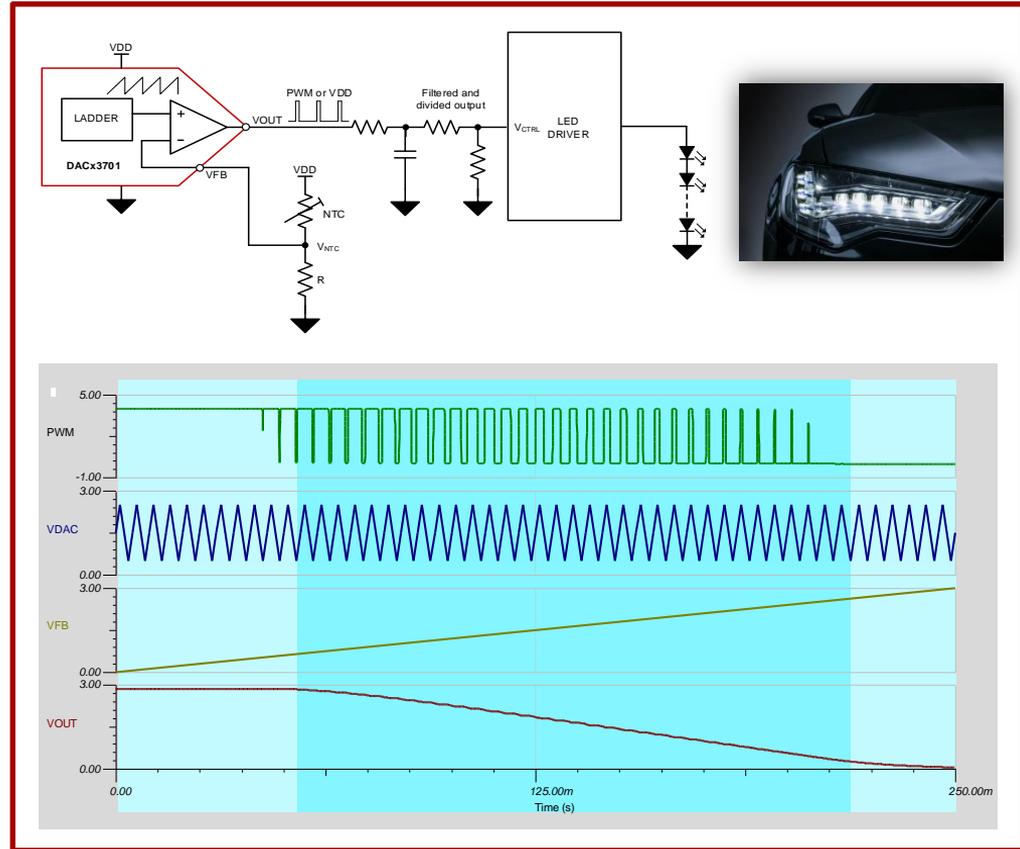- Processor-less single-slope thermal foldback for DRL
- Software programmable knee point and slope
- PWM with duty cycle following foldback curve
- Software programmability of PWM frequency through triangular / sawtooth waveform
- Optional voltage output with RC filter




$$f_{\text{TRIANGLE-WAVE}} = \frac{1}{2 \times \text{SLEW_RATE} \times \left(\frac{\text{MARGIN_HIGH} - \text{MARGIN_LOW} + 1}{\text{CODE_STEP}} \right)}$$


$$f_{\text{SAWTOOTH-WAVE}} = \frac{1}{\text{SLEW_RATE} \times \left(\frac{\text{MARGIN_HIGH} - \text{MARGIN_LOW} + 1}{\text{CODE_STEP}} \right)}$$

An example Smart analog front end (AFE)

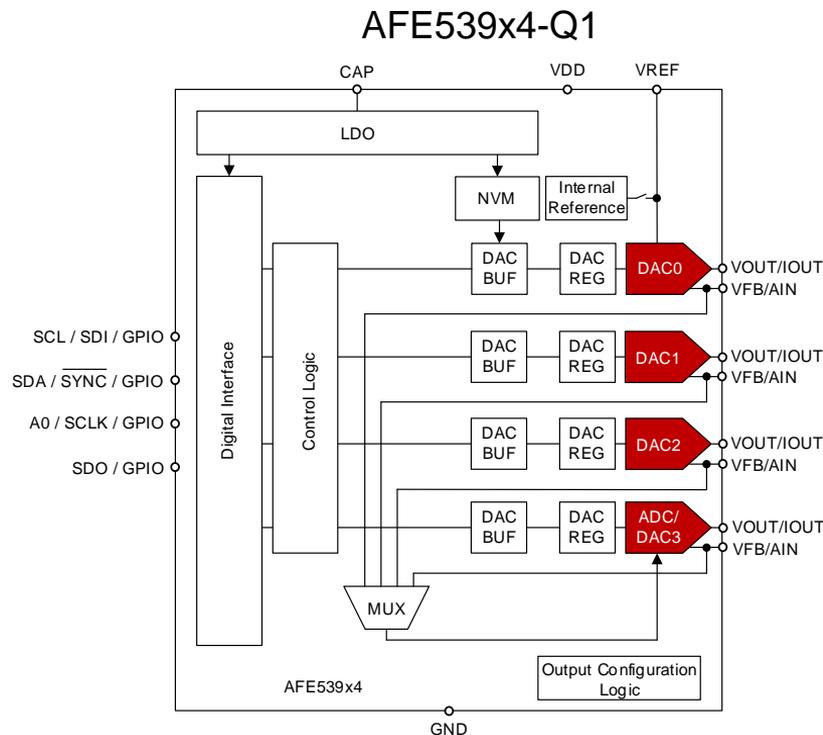- User programmable Nonvolatile Memory (NVM/EEPROM)
 - I2C and SPI mode auto-detection
 - GPIO interface
 - PWM output
 - Hi-Z output during power-off condition
 - 10-bit ADC mode for all channels
 - Control logic that supports look-up table and closed-loop control
-
- Wide Temperature range: -40°C to +125°C
 - Small package WQFN-16 (3x3)




TEC control

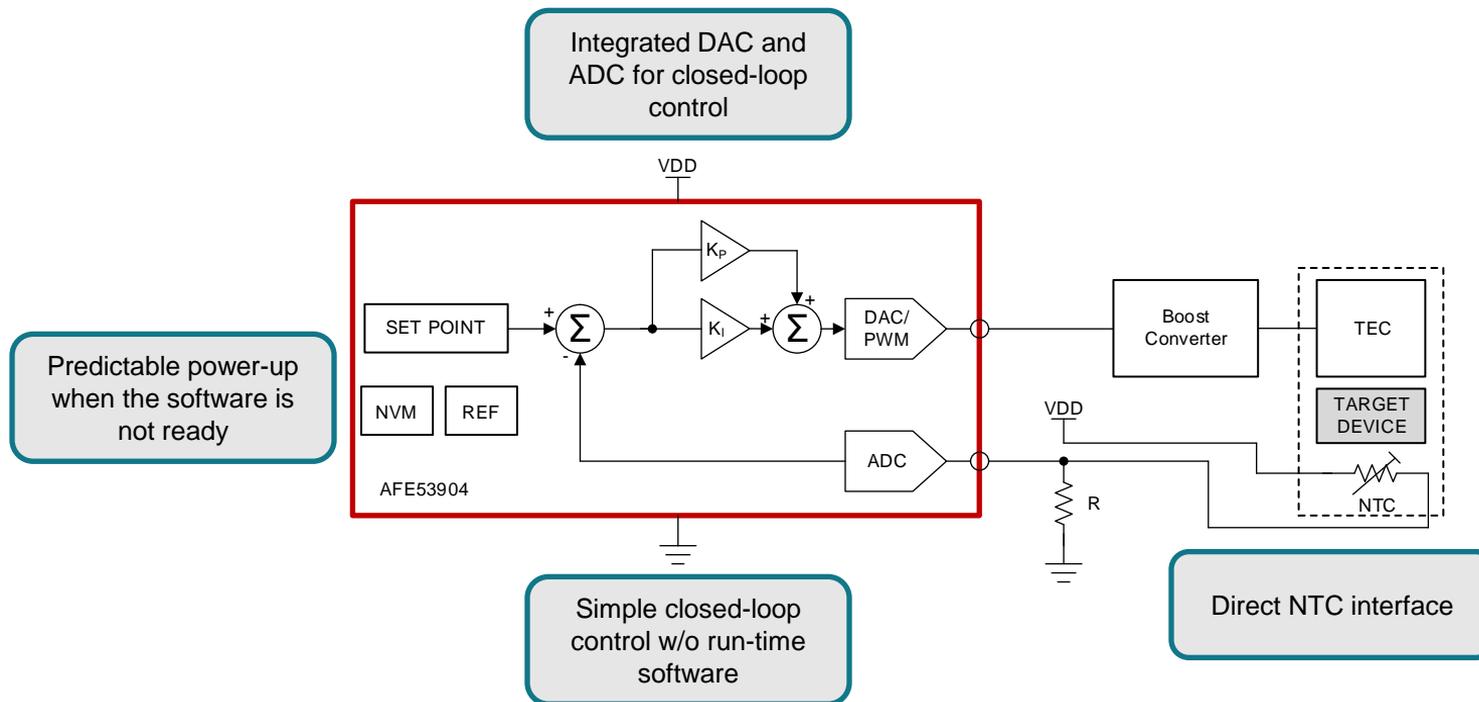


TPL1401 application summary

- Losing yield at factory? Does the voltage need tuning at factory or at the field?
 - Does the PCB need HW change for every new revision?
- Are you struggling to find the right way to generate a DC set-point?

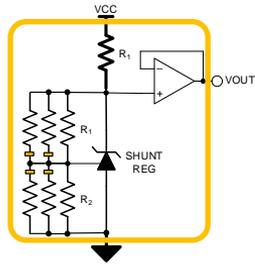
Voltage divider, Adjustable shunt regulator




Adjustable current limit

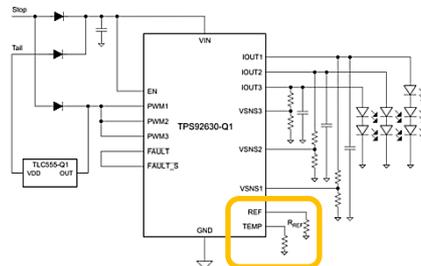


Adjustable reference

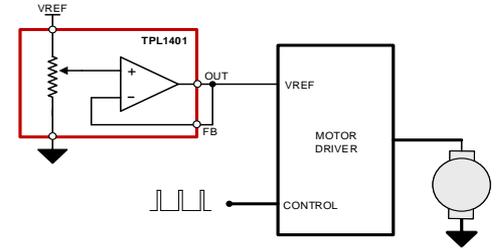


LASER diode

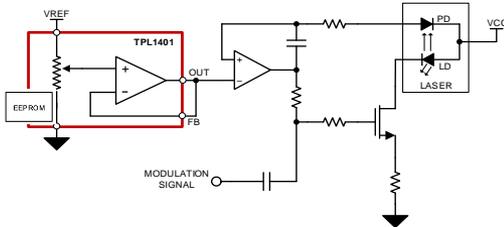

LEDs

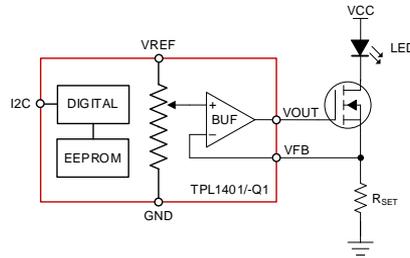


Microphone tuning

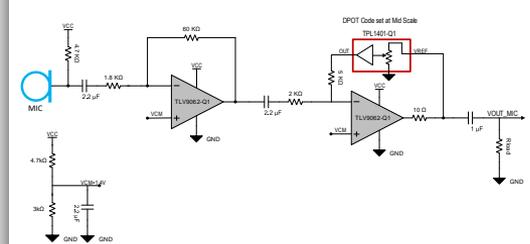


DAC53701 application summary

- Are you using an MCU just to create an adjustable PWM? Are you stuck with a 555 timer?
 - Are you avoiding simple fade-in fade-out effects in lighting because of cost?
 - Do you often notice fault management designs to be tricky?


Fade-in fade-out

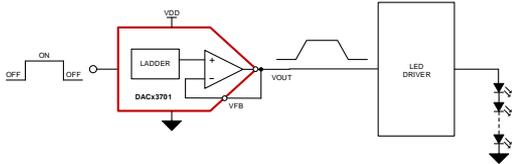


Medical alarm

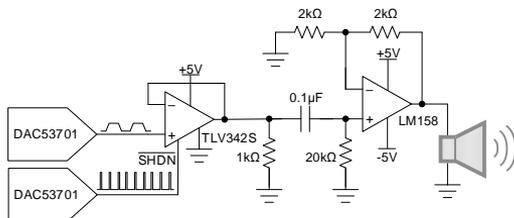


Programmable comparator

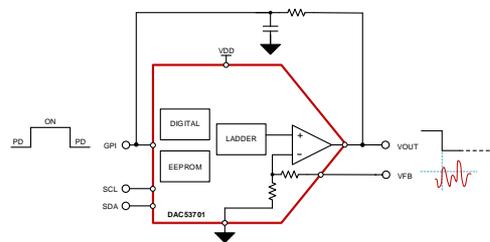


Voltage margining and scaling

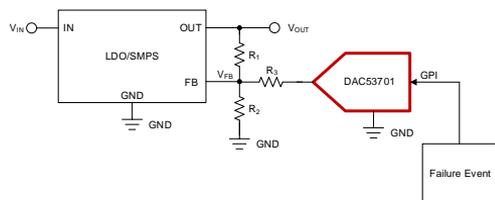

PWM output

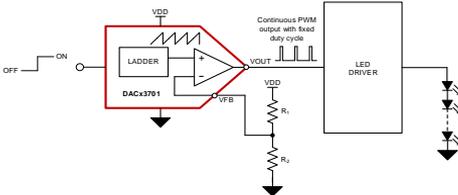


Temperature/Resistance to PWM

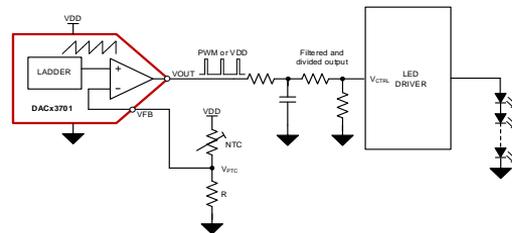


AFE539x4 application summary

- Are you using an MCU to create simple control loops?
- Does your system have shortage of GPIOs or have the need for long-distance control over GPIOs?
- Are you burdened by software to create LED animations?


TEC control, PI control

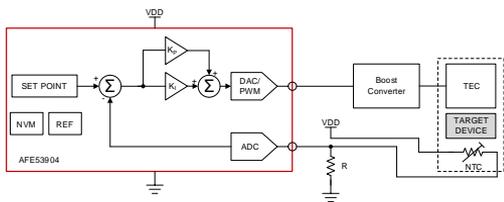


Multi-slope thermal foldback

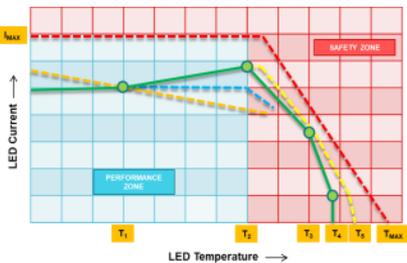


LED animation

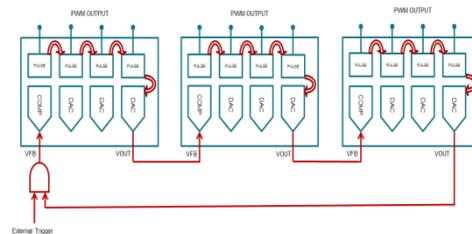


Logarithmic fade-in fade-out

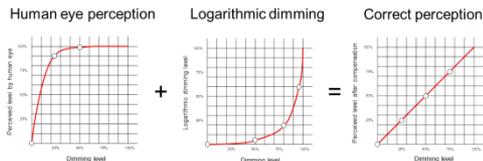

PWM IO expander

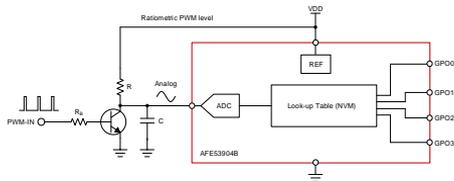

Dynamic headroom control

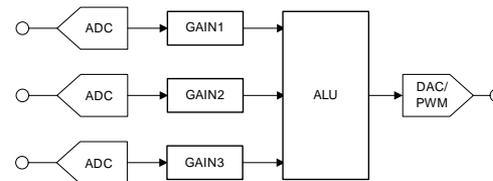



©2020 Texas Instruments Incorporated. All rights reserved.

The material is provided strictly "as-is" for informational purposes only and without any warranty.
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated