

Varying UCC27221 and UCC27222 Gate Drive Voltage by Overriding the VLO Regulator

Steve Mappus

Power Supply Control Products

ABSTRACT

The UCC2722x contains an internal 6.5-V regulator, from which the gate drive voltages for the high and low-side MOSFETs of a synchronous buck power stage are derived. In some instances it may be desirable to drive the MOSFET gates with a voltage other than 6.5 V. The output driver stage of the UCC2722x has an absolute maximum voltage rating of 10 V. However it is still possible to bypass the internal regulator and produce gate drive voltages other than 6.5 V, but limited to 9 V.

Contents


1	Introduction	1
2	Inside the UCC2722x	2
3	Recommended VLO/VPLO Configuration	3
4	Driving PVLO and VHI with External Voltage Source	4
5	Driving PVLO and VHI with Independent External Voltage Sources	5
6	Conclusion	5
7	References	5

1 Introduction

Synchronous rectifiers are often used in place of the freewheeling diode commonly found in a classical buck converter. Using a synchronous buck driver that includes Predictive Gate Drive™ technology to drive the upper control MOSFET and lower synchronous MOSFET, can result in a substantial overall efficiency increase for high-frequency, low-voltage applications. While most of the efficiency savings is attributed to the non-existence of body-diode conduction, additional increases can sometimes be gained by properly matching the optimal gate drive voltage with the MOSFETs being driven. Driving the MOSFET gate with a higher voltage, results in a lower associated on-resistance, $R_{DS(on)}$. There are however, additional factors such as gate charge losses and switching losses that must also be considered. Lowering the MOSFET on-resistance is especially critical for the synchronous rectifier, since in most cases the power loss due to the freewheeling current through the MOSFET channel resistance is the highest single contributor to total power dissipated within the synchronous rectifier.

3 Recommended VLO/PVLO Configuration

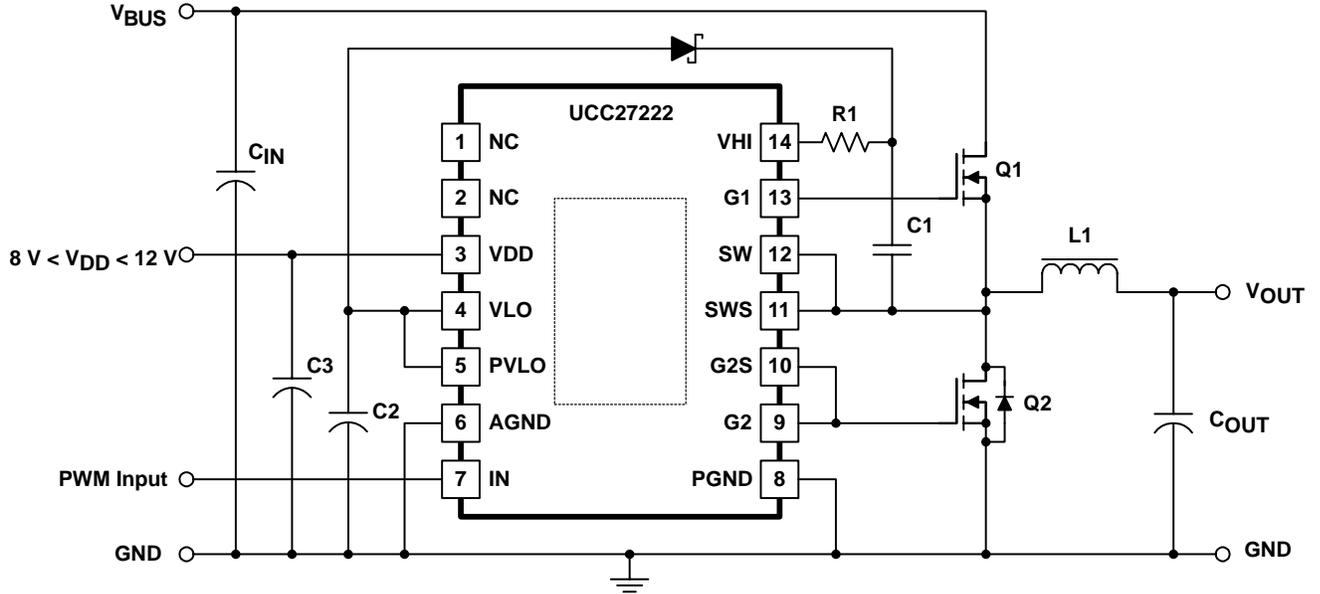Configuring the UCC27222 VLO/PVLO drive as recommended in the data sheet makes 6.5V available for driving both gates of the synchronous buck. A typical application example is shown in Figure 2.




UDG-03101

Figure 2. Gate Voltage Provided From VLO/PVLO

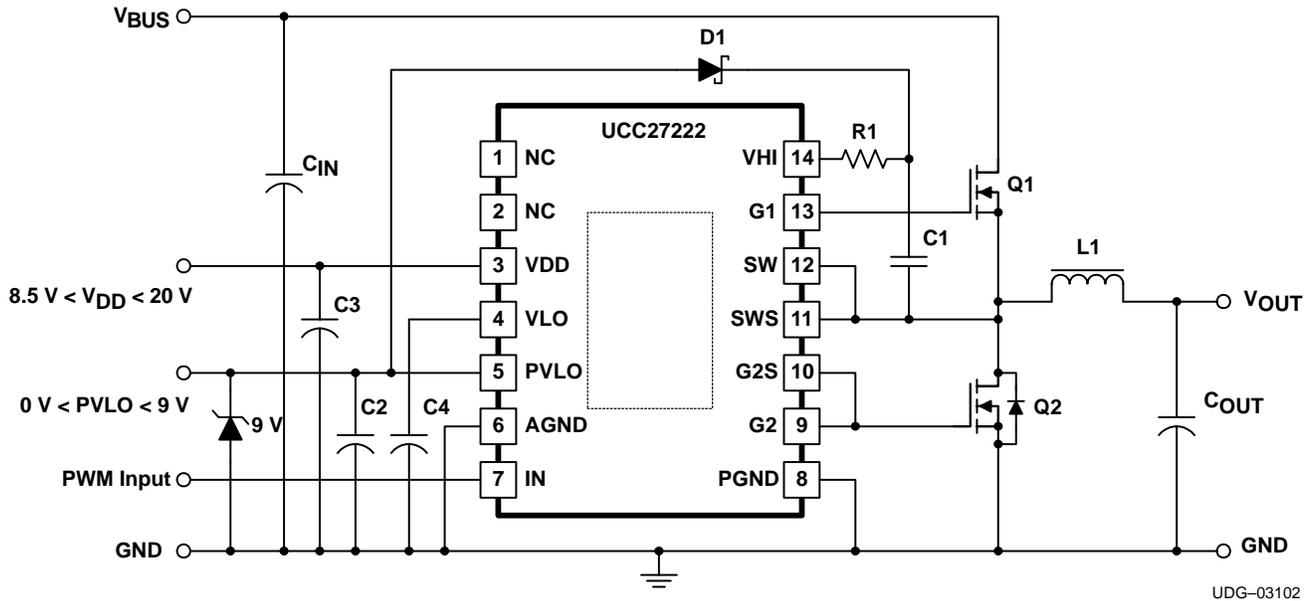6.5 V was chosen as an optimal voltage for driving logic level MOSFETs typically found in most synchronous low-voltage, buck power stages. As the gate voltage is increased the on resistance of the MOSFET decreases. However, the trade-off lies in the fact that as the gate voltage increases, the associated gate charge also increases. Higher gate charge and gate drive voltage results in increased switching losses and losses in the UCC2722x driver device. By numerically characterizing gate voltage versus charge and gate voltage versus on resistance, the optimal gate drive voltage was found to be 6.5 V and so became the defined voltage for the VLO regulator.

4 Driving PVLO and VHI With External Voltage Sources

In some instances it may be desirable to drive the MOSFETs with a voltage either higher or lower than VLO. However, the output drive stage of the UCC2722x, has an absolute maximum voltage limit of 10 V. For applications desiring a gate drive other than 6.5 V, the UCC2722x can be configured as shown in Figure 3.



UDG-03102

Figure 3. PVLO and VHI Gate Voltage Provided From External Sources

For the application circuit shown in Figure 3, the PVLO voltage is supplied by some other available bias source up to 9 V. To prevent possible damage to the output stage of the UCC2722x, it is advisable to clamp the PVLO voltage with a 9-V zener diode, as shown in Figure 3. For this configuration, the VLO regulator output is now used strictly for biasing the predictive delay control circuitry internal to the device, while PVLO provides the necessary gate drive voltage for G1 and G2.

5 Driving PVLO and VHI With Independent External Voltage Sources

To drive the gates of Q1 and Q2 using different gate drive voltages, the UCC2722x can be configured as shown in Figure 4.

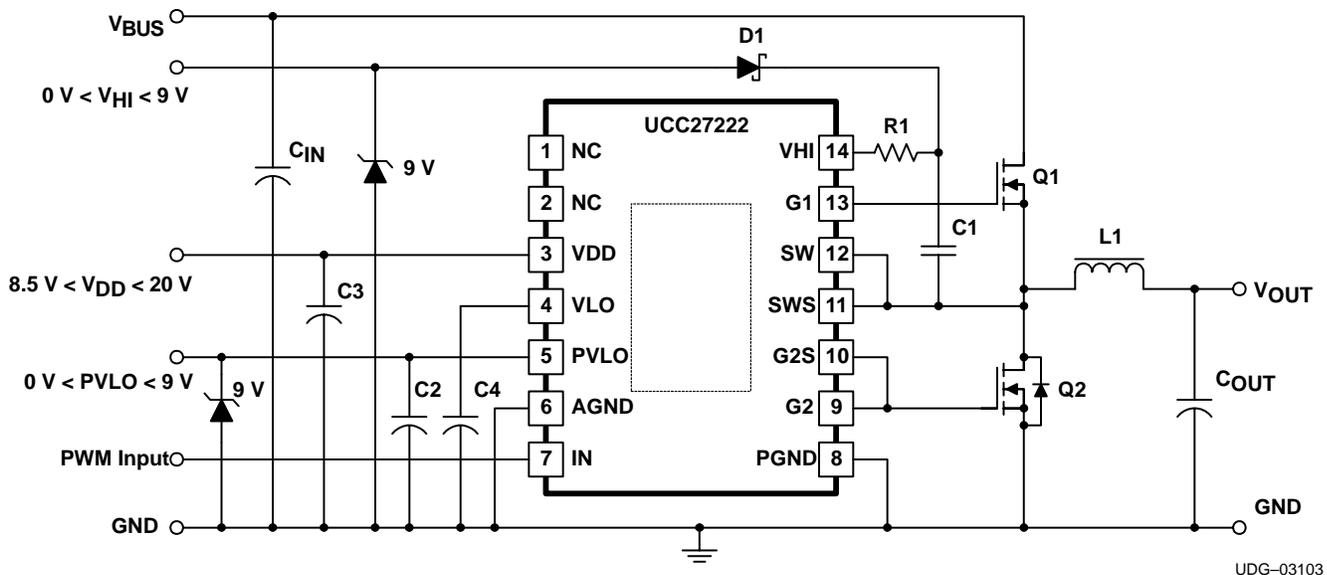


Figure 4. PVLO and VHI Gate Voltage Provided From Independent Sources

Similar to the application circuit shown in Figure 3, it is recommended to clamp VHI and PVLO voltage sources with a 9-V zener protection diode. VHI is now boosted to a voltage equal to VHI above V_{BUS} making the gate to source voltage to Q1 equal to VHI minus the diode drop associate with D1. For the low-side MOSFET, the gate to source voltage of Q1 is now provided directly from the external PVLO voltage source.

6 Conclusion

For most applications where the UCC2722/1/2 is used to drive low voltage, logic level MOSFETs, 6.5 V should be very close to an optimal gate drive voltage amplitude. However, if system voltages other than 6.5 V are readily available, and the $R_{DS(on)}$ of the synchronous MOSFET can be lowered enough to offset the additional gate charge loss introduced by increasing the gate drive voltage amplitude, then there may be some cases that would benefit from using the application circuits introduced in Figure 3 or Figure 4.

7 References

UCC27221/UCC27222 High-Efficiency Predictive Synchronous Buck Driver Datasheet, (SLUS486A)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2003, Texas Instruments Incorporated