

Gate Drive Outputs on the UCC28950 and UCC28951-Q1 During Burst Mode Operation

Application Report



Literature Number: SLUA787

October 2016

Gate Drive Outputs on the UCC28950 and UCC28951-Q1 During Burst Mode Operation

Colin Gillmor

ABSTRACT

The UCC28950/UCC28951-Q1 phase-shifted full-bridge controllers offer several features to improve power conversion efficiency at light loads. In particular, as the load current drops below the DCM threshold the duty cycle applied to the transformer reduces and eventually the device enters a burst mode. This application note describes how a user can design their gate driver circuits to operate correctly in burst mode.

1 Introduction

Narrow pulse widths (less than 50% duty cycle) may be observed in the first OUTD pulse of a burst and at start-up.

NOTE: The greyed out area in [Figure 1](#) is not ensured.

Typical examples of this behavior are shown in [Figure 2](#) through [Figure 5](#). The initial OUTD pulse (blue) is sometimes full width but sometimes very narrow. The T_{ON} pulse (the OUTA/OUTD overlap time) is unaffected. This means that if the design uses a gate drive transformer, then the correct gate drive is always applied to the switches in the H bridge.

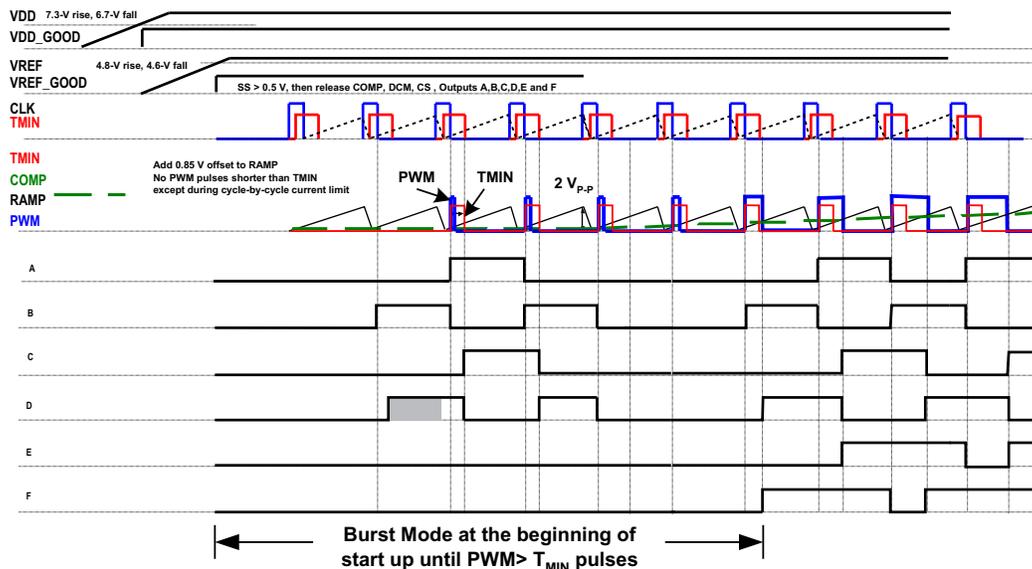


Figure 1. UCC28950/UCC28951-Q1 Startup and Burst Mode Timing Diagram (The Area in Grey is Not Ensured)

2 Gate-Drive Testing

If the designer wishes to use a gate drive device, such as the [UCC27714](#), then some additional testing must be done to make sure that the bootstrap capacitor (C_{BOOT} in [Figure 6](#)) is fully charged by the short OUTD pulse. If this is not done, then the next OUTC pulse may not be delivered to the gate of QC. If this happens, QC will not be turned on and current will flow through its body diode instead of its channel. At the start of the next T_{ON} interval QD is turned on again. The resulting reverse recovery current in the body diode of QC can appear as a shoot through current and QC and QD may fail short.

2.1 Typical Waveforms of a Gate-Drive Device

Yellow = OUTA, red = transformer primary, blue = OUTD

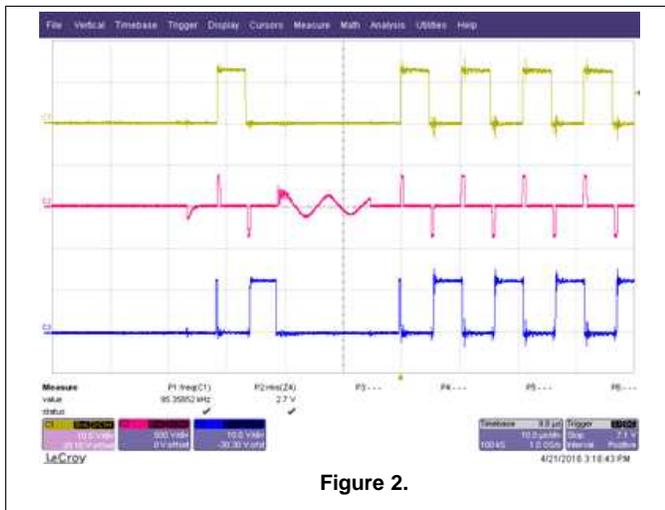


Figure 2.

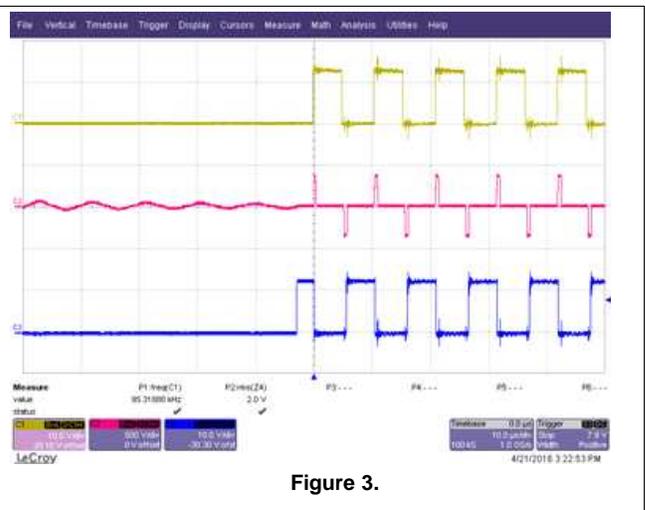


Figure 3.

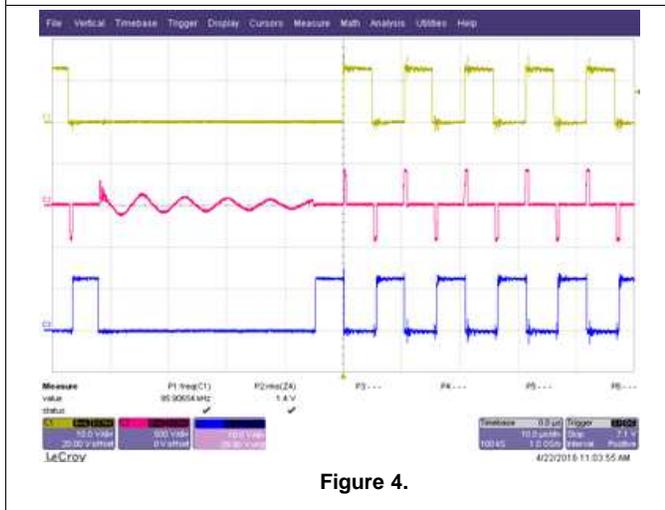


Figure 4.

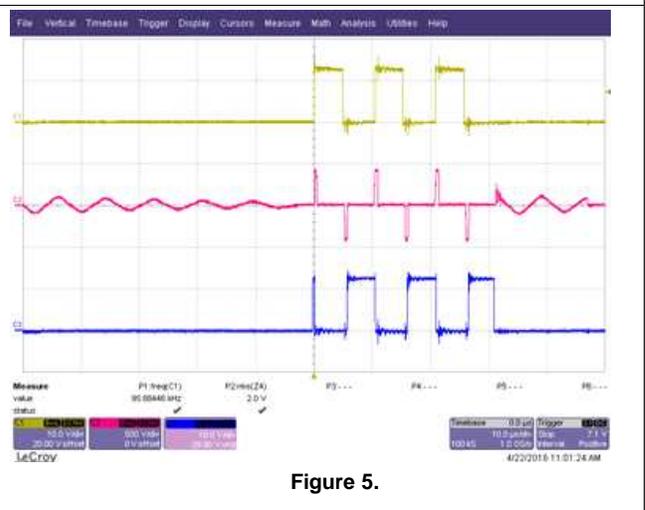


Figure 5.

3 Design Recommendations

A successful gate-driver design requires that the designer follow a few rules.

- Keep R_{CHG} small.
- D_{CHG} must have a high-peak current capacity.
- Use $CV_{\text{CC}} \geq 10 \times C_{\text{BOOT}}$. C_{boot} should be chosen so that $Q_{\text{BOOT}} \geq 10 \times Q_g$.
- Optimize the layout to minimize parasitic impedances in the charging paths outlined in red in [Figure 6](#).

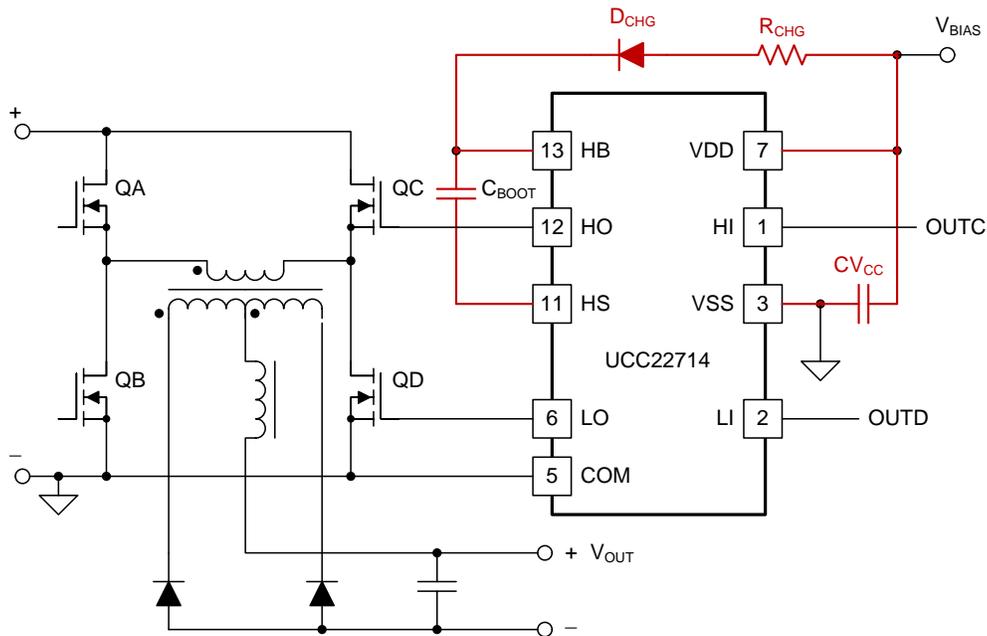


Figure 6. Simplified Gate Driver Schematic

4 Conclusion

The UCC28950 and UCC28951-Q1 offer a burst mode of operation which may be used to improve power conversion efficiency at light loads. To successfully use a device-based gate-driver circuit the designer must pay careful attention to the design of the bootstrap capacitor charging networks.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com