

UCC28880, UCC28881 Audible Noise Reduction Techniques

Mike O'Loughlin

1 Introduction

The economical [UCC28880](#) and [UCC28881](#) high voltage switcher/controllers were designed for offline buck converters for low power applications to meet size and cost constraints. These devices use an On/Off control scheme, like many others available today, that could potentially allow the effective switching frequency to drop into the audible band and generate noise. By following the recommended design techniques in this application note for [UCC28880](#) and [UCC28881](#) the problem can be avoided by staying quite over the entire operating range.

2 Functional Schematic

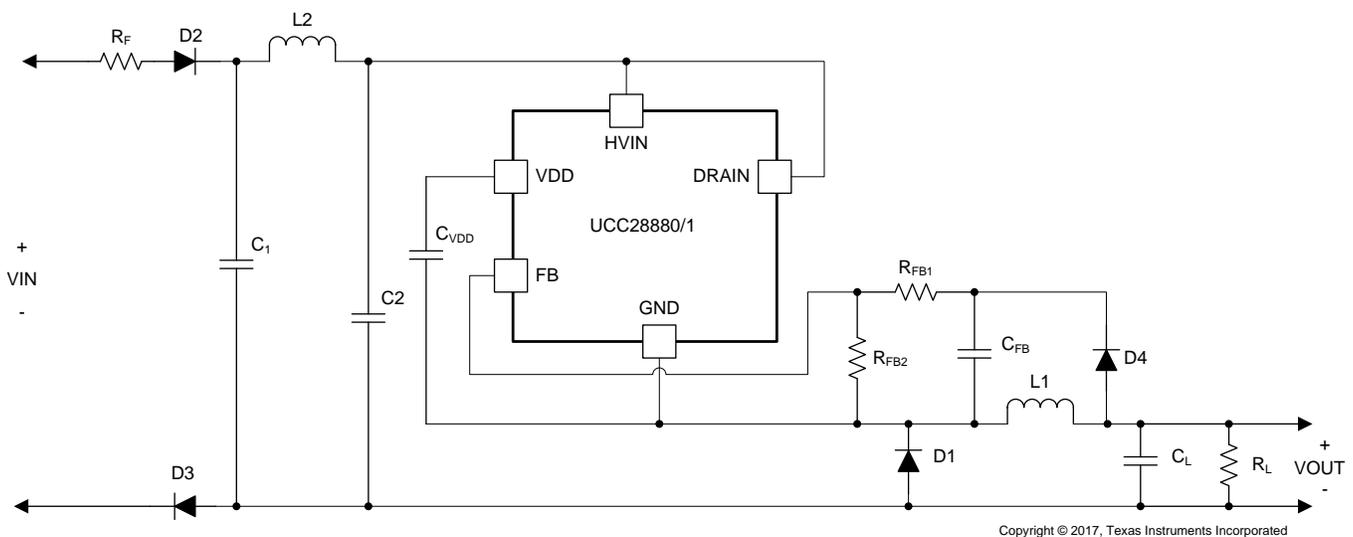


Figure 1. Offline High-Side Buck Converter with On and Off Control

3 Circuit Operation

The UCC28880 and UCC28881 uses what is known as On/Off control. This control scheme samples the output during the freewheeling period through the R_{FB1} and R_{FB1} resistor dividers and when the voltage at the feedback pin is less than 1.02 V it delivers 62-kHz of pulse width modulated (PWM) packets to maintain the output voltage. The PWM packets are controlled by peak current mode control.

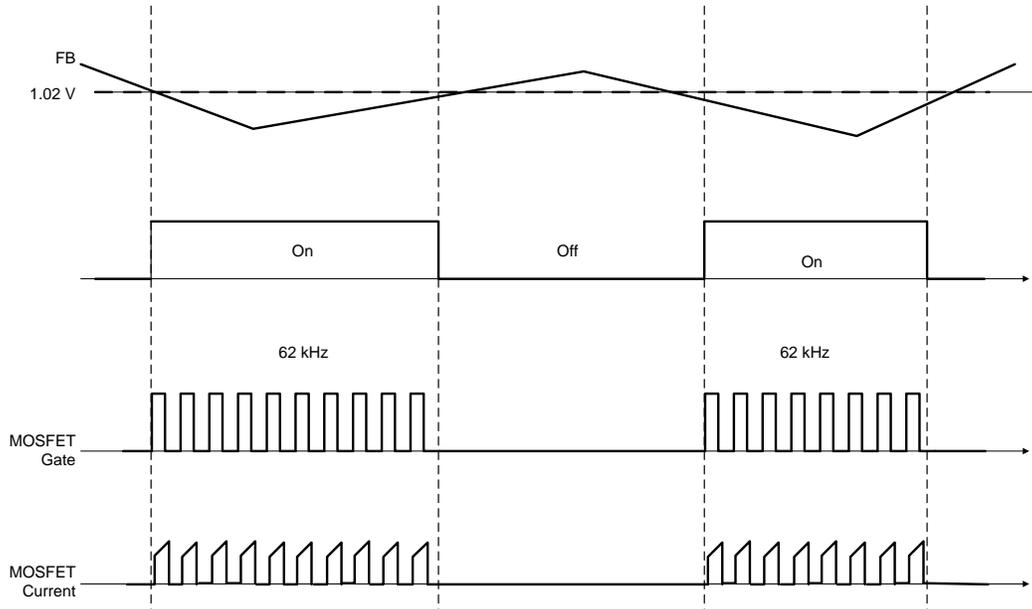


Figure 2. On/Off Control Diagram

The output inductor (L_1) is sized based on internal peak current limit (I_{LIMIT}), output current (I_{OUT}) and PWM switching frequency of typically 62 kHz. The inductor selected should as close to the calculated value as possible.

Table 1. UCC28880 I_{LIMIT} Specification

PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
I_{LIMIT}	Current limit	Static, -40°C			300	mA
		Static, 25°C	170	210	260	mA
		Static, 125°C	140			mA

Table 2. UCC28881 I_{LIMIT} Specification

PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
I_{LIMIT}	Current limit	Static, -40°C			630	mA
		Static, 25°C	330	440	570	mA
		Static, 125°C	315			mA

NOTE: $V_{HVIN} = 30\text{ V}$, $T_A = T_J = -40\text{ °C}$ to 125 °C in Table 1 and Table 2.

$$I_{OUT} < 0.9 \times I_{LIMIT} \tag{1}$$

$$L_1 = \frac{V_{OUT} \times \left(1 - \frac{V_{OUT}}{V_{IN}}\right)}{2 \times (I_{LIMIT} - I_{OUT}) \times 62\text{ kHz}} \tag{2}$$

Resistors R_{FB1} and R_{FB2} are also used to adjust the output voltage and capacitor C_{FB} is used to set PWM packet timing (t_{FB}). The initial t_{FB} is set to $1/10^{\text{th}}$ the product of the output capacitance (C_L) and load impedance (R_L) and then will be fine-tuned based on actual circuit performance.

$$t_{FB} = (R_{FB1} + R_{FB2}) \times C_{FB} = C_L \times R_L \times 0.1 \quad (3)$$

Control Methodology will operate in the Audible Range (<20 kHz).

Due to variations in peak current (I_{LIMIT}) at maximum load the effective switching frequency will vary from 62 kHz down to 31 kHz. As the load decreases below 80% the converter can and will enter the audible range (<20 kHz) The output ripple voltage and inductor ripple current will look similar to [Figure 3](#) as the load decreases.



Figure 3. Output Ripple Voltage ($V_{OUT} = CH1$) and Inductor Ripple Current ($I_{L1} = CH4$)

4 Sources of Audible Noise

Any components in the design that have energy packets being delivered through them at 20 kHz or less can vibrate. This can include capacitors, diodes, inductor's wires, connectors.

5 Determining the Source of Audible Noise

CAUTION

Follow high-voltage safety practices.

1. A sheet of paper can be rolled up into a tube and used like a hearing aid. Put one side of the paper tube to your ear and point the other end of the tube toward the power supply circuit board in operation. This can help you find the audible component.
2. A non-conductive stick can be used to determine which device is vibrating and creating the audible noise. A number 2 wooden pencil with an eraser can be used for this. Touch the suspected component that is contributing to the audible noise. If the sound dulls this may be the source of the audible noise.

6 Things the Designer Can Do to Reduce Audible Noise

1. Select the output inductor (L_1) as close to the recommended value as possible. This will ensure at full load the effective switching frequency is as close to the maximum as possible. This calculation was covered earlier in this application note.
2. Set the t_{FB} time constant as small as possible to get the converter to operate at the maximum frequency possible. This may affect load regulation of the power converter and may require pre-load resistor (R_L) as shown in [Figure 1](#). A Zener clamp or a series pass regulator on the output may be required to regulate the output voltage at light loads. Please refer to [Figure 4](#) for the circuit configuration.

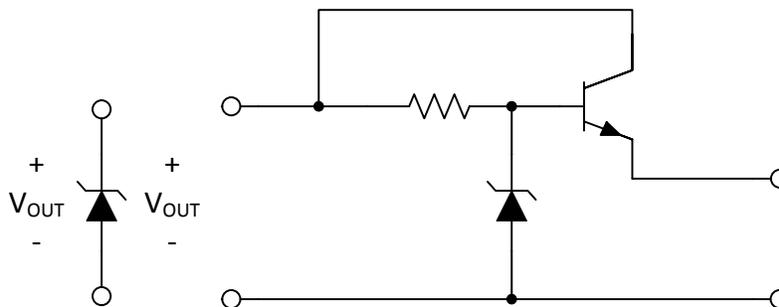


Figure 4. Zener Shunt or Series Pass Regulator to Improve Load Regulation

3. Select a buck inductor (L_1) that is varnished and/or encased in magnetic potting material. TDK and Würth have a family of inductors that are encased in potting material. Avoid inductors that are not varnished and/or encased in magnetic potting material. Examples of these types of inductors can be found in [Figure 5](#).



Figure 5. Potted and Varnished Inductor, Inductor without Varnishing and Potting.

4. Use electrolytic input and output capacitors because they are less likely to create audible noise over ceramic capacitors that have piezoelectric characteristics. Please note that some electrolytic capacitors can vibrate and create audible noise as well. They may have to be attached to the board in rubber silicon or encased in potting material to reduce vibrations and make the design less audible.
5. Glue down any possible components that could vibrate with epoxy, rubber silicon or other like adhesive.
6. In rare cases it may be necessary to varnish/encase the entire power supply in potting material to reduce audible noise. There are many companies that make these electronics insulation resins and polymers for these applications such as Elantas Electrical Insulation, Epic Resins and ITW Engineered Polymers.



Figure 6. Potted Power Supply

7. After the initial design is complete and the audible noise is removed. It is recommended to do temperature, production and verification testing. This process should involve multiple boards and devices to verify the design.

7 Summary

The [UCC28880](#) and [UCC28881](#) economic offline buck converters use an On/Off control technique that can make the design susceptible to audible noise (<20 kHz). As this application note discussed, the audible noise can be reduced by properly selecting input and output capacitors; as well as, inductors that are varnished and encased in magnetic potting materials. In some cases, it may require varnishing and/or encasing the design in potting material.

8 Recap of Recommendations

1. Select the output inductor (L_1) as close to the recommended value as possible.
2. Set the tFB time constant as small as possible to get the converter to operate at the maximum frequency possible.
 - (a) Preloading, Zener and/or series pass regulator may be needed to improve load regulation.
3. Select a buck inductor (L_1) that is varnished and/or encased in magnetic potting material.
4. Avoid using ceramic capacitors for input and output capacitors; electrolytic capacitors are a better choice.
5. Glue down components that can vibrate.
6. Encapsulate the power supply in potting material.
7. Conduct temperature, production and verification testing to account for variations in component and device tolerances.

9 Reference Material

1. [UCC28880](#) Data Sheet, High Voltage Switch for Non-isolated AC/DC Conversion
2. [UCC28881](#) Data Sheet, 700-V, 225-mA Low Quiescent Current Off-Line Switcher

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated