

Minimizing Buck-Boost (Inverting) Converter High-Frequency Switching Noise

Jeff Falin

HPA Portable Power Applications

ABSTRACT

This application report explains how to use proper board layout and bypass capacitors to reduce high-frequency switching noise generated by a buck-boost (inverting) switching converter.

1 Description of the Problem

Various nodes of a switching converter can generate high amplitude switching noise in the 100-MHz+ range. [Figure 1](#) shows an a-coupled voltage measurement taken at the input (CH1-**top**, brown) and output (CH2-**bottom**, blue) of a TPS63700 configured to provide $V_{OUT} = -12\text{ V}$ at 150 mA from $V_{IN} = 5\text{ V}$. The time scale is 80 ns/div. The ground loop on each voltage probe was minimized.

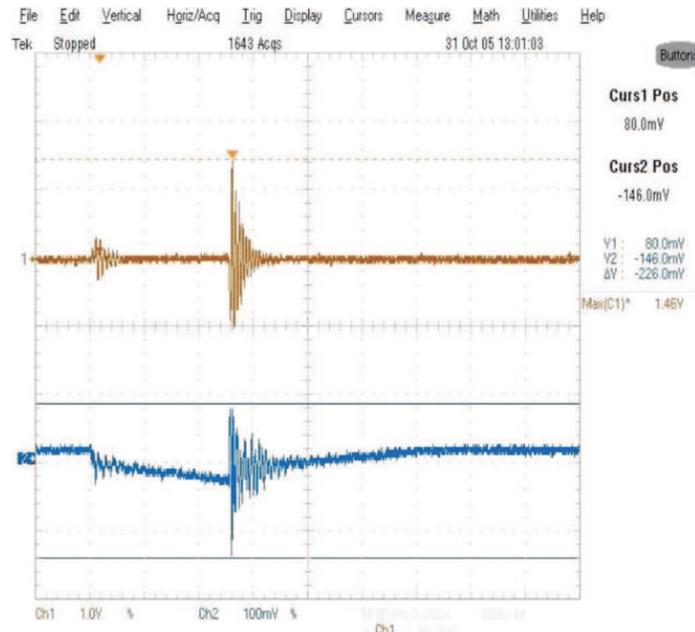


Figure 1. High-Frequency Switching Noise Measurement Using Bad Board Layout

Switching noise over 200 MHz and 220 mV_{pk-pk} on the output and over 2 V_{pk-pk} on the input is present. [Figure 2](#) shows the board layout. Multiple 25-V ceramic output capacitors (C7–C10) are used in parallel due to the unavailability of a single 22-μF, 25-V-rated output capacitor. Notice that the output capacitors (C7–C10) and diode D1 are far from the IC and that the input capacitor (C1) and output capacitors (C7–C10) share a common ground plane.

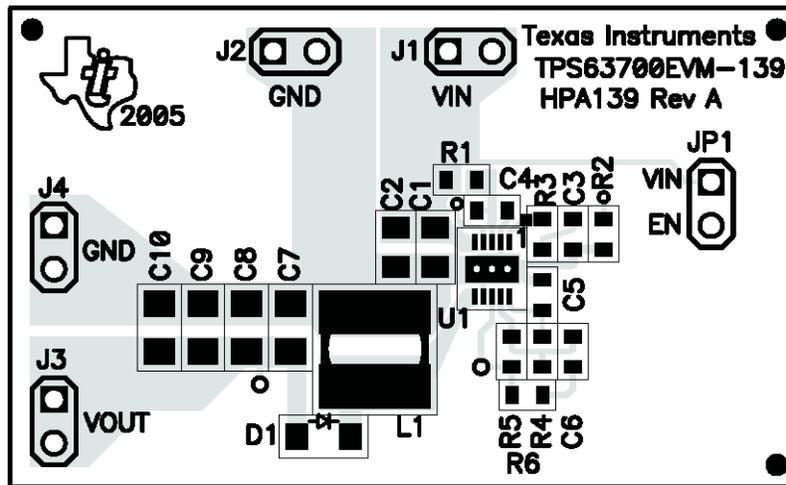


Figure 2. Inverter Bad Board Layout

The *critical loop*, shown in blue in Figure 3, is created by the parasitic inductances and capacitances, shown in red, in the inverter power stage. These parasitic capacitances and inductances interact at each switching cycle to produce the switching noise seen at V_{IN} and V_{OUT} in Figure 1. Where possible, the designer must select FETs and diodes with minimal parasitic capacitances. Through proper board layout, the designer must minimize the parasitic inductances, $L_{PAR\#}$, by placing the bulk input capacitor as close as possible between the power switch, Q1, and a single power ground point, close to the converter IC's power ground pin. The bulk output and the bulk output capacitance also must be placed as close as possible between the diode, D1, and the same power ground point. Additional high-frequency bypass capacitors, C_{IN-BYP} and $C_{OUT-BYP}$, in the range of 0.01 μF to 0.47 μF , are best at reducing the ringing seen between V_{IN} and ground and V_{OUT} and ground.

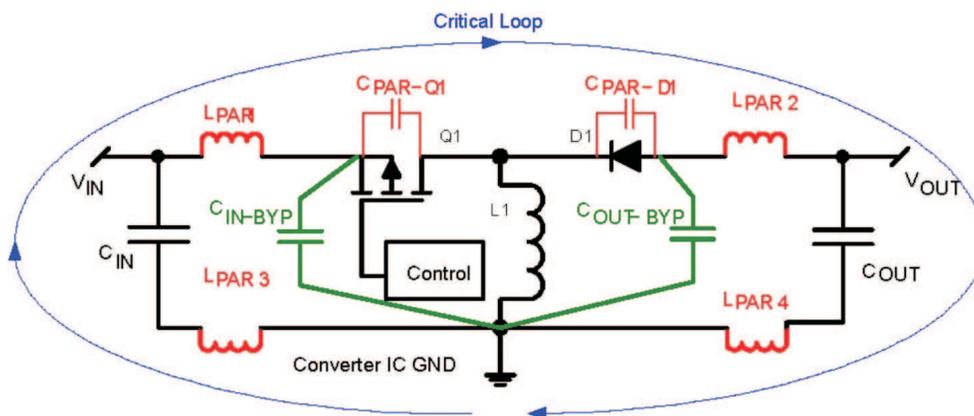


Figure 3. Buck-Boost (Inverting) Converter Schematic

2 Implementation of Solution

Figure 4 shows the layout for the TPS63700 after implementing the previously mentioned recommendations. High-frequency bypass capacitors C2 on the input voltage and C7 on the output voltage were added and placed as close between V_{IN} and power ground and V_{OUT} and power ground as possible. Also, note that the input and output grounds do not share a ground plane except at a point close to the IC.

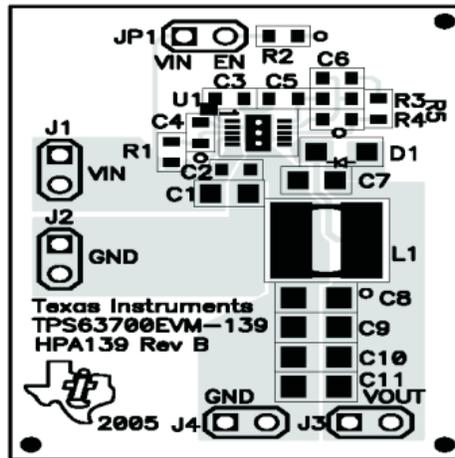


Figure 4. Inverter Improved Board Layout

Figure 5 shows switching noise measured under the same conditions used in Figure 1 but with the improved board layout. The time scale is 40 ns/div. Switching noise has been reduced to about 170 mV on the output and under 500 mV_{pk-pk} on the input.

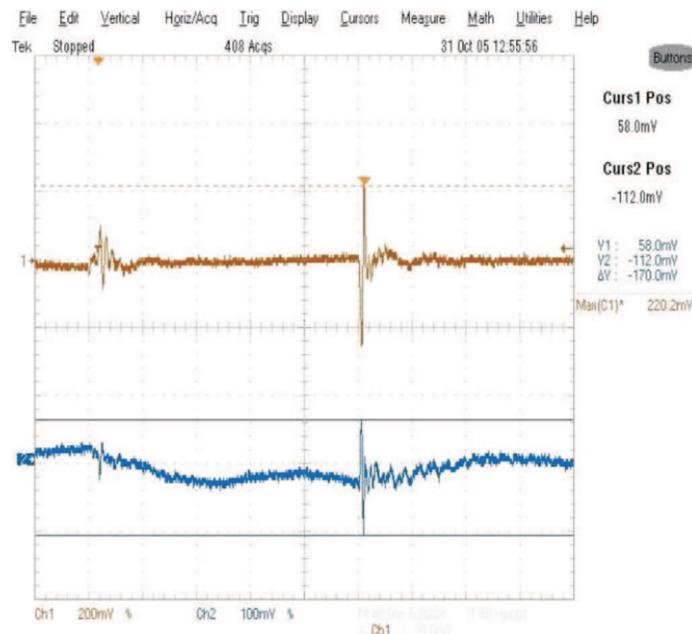


Figure 5. High-Frequency Switching Noise on Output of Inverter Using Improved Board Layout and Bypass Capacitors

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video
Wireless	www.ti.com/wireless-apps

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated