

High Integration, High Efficiency Power Solution Using DCDC Converters for TMS320C2834x Microcontrollers

Ambreesh Tripathi

PMP - DC/DC Low_power Converters

ABSTRACT

This reference design is intended for users designing with the TMS320C2834x Microcontrollers. This design, employing sequenced power supplies, describes a system with an input voltage of 5V, and uses a high-efficiency DCDC Converter with integrated FETs for a simple and integrated design.

Contents

1	Introduction	1
2	Power Requirements	2
3	Features	2
4	List of Material	3
5	Test Results	5

List of Figures

1	PMP5000 Reference Design Schematic	3
2	Shows Sequencing in Start up Waveform.....	5
3	Efficiency vs Output Current (TPS65000)	5

List of Tables

1	TMS320C2834x Power Specs	2
2	PMP5000 List of Material	3

1 Introduction

In multi-voltage architectures, coordinated management of power supplies is necessary to avoid potential problems and obtain reliable performance. Power supply designers must consider the timing and voltage differences between core and I/O voltage supplies during power up and power down operations.

Sequencing refers to the order, timing, and differential in which the two voltage rails are powered up and down. A system designed without proper sequencing may be at risk for two types of failures. The first failure represents a threat to the long term reliability of the dual voltage device, while the second failure poses the possibility of immediate damage to interface circuits in the processor or system devices such as memory, logic, or data converter ICs.

Another potential problem with improper supply sequencing is bus contention. Bus contention is a condition when the processor and another device both attempt to control a bi-directional bus during power up, which may also affect I/O reliability. Power supply designers should check the requirements regarding bus contention for individual devices.

The power-on sequencing for TMS320C2834x Microcontrollers are shown in the Power Requirements table below. As mentioned in the table, all voltage rails should be powered up within 5ms.

2 Power Requirements

The power requirements are as specified in [Table 1](#).

Table 1. TMS320C2834x Power Specs

	PIN NAME(s)	VOLTAGE (V)	I _{max} (mA)	TOLERANCE	SEQUENCING ORDER	TIMING DELAY
Core	VDD	1.1 / 1.2 ⁽¹⁾	1000 ⁽²⁾	±5%	1	All voltage rails should be powered up within 5ms
I/O	VDD18	1.8	80	±5%	2	
I/O	VDDIO	3.3	200	±5%	2	

(1) CVDD = 1.2V for 300MHz devices; CVDD = 1.1V for 200MHz.

(2) Max current on VDD at 300MHz is 1000mA; max current on VDD at 200MHz is 600mA.

3 Features

The design uses the following high-efficiency DCDC Converter with integrated FETs.

Devices:	TPS65000
Power supply specs:	
V _{in}	5 V ± 10%
V _{out1}	1.1 V/1.2 V ± 5% at 1000 mA
V _{out2}	1.8 V ± 5% at 80 mA
V _{out3}	3.3 V ± 5% at 200 mA
Sequencing	1) V _{out1} 2) V _{out2} and V _{out3}

TPS65000

- Step-Down Converters
 - Spread Spectrum Clock (SSC) Generation
 - For Reduced EMI
 - 2.25MHz Fixed Frequency Operation
- LDOs
 - Adjustable output voltage
 - Up to 300mA Output Current
 - Separate power Input and Enable

More information on the Devices can be found from the datasheet.

TPS65000 [SLVS810](#)

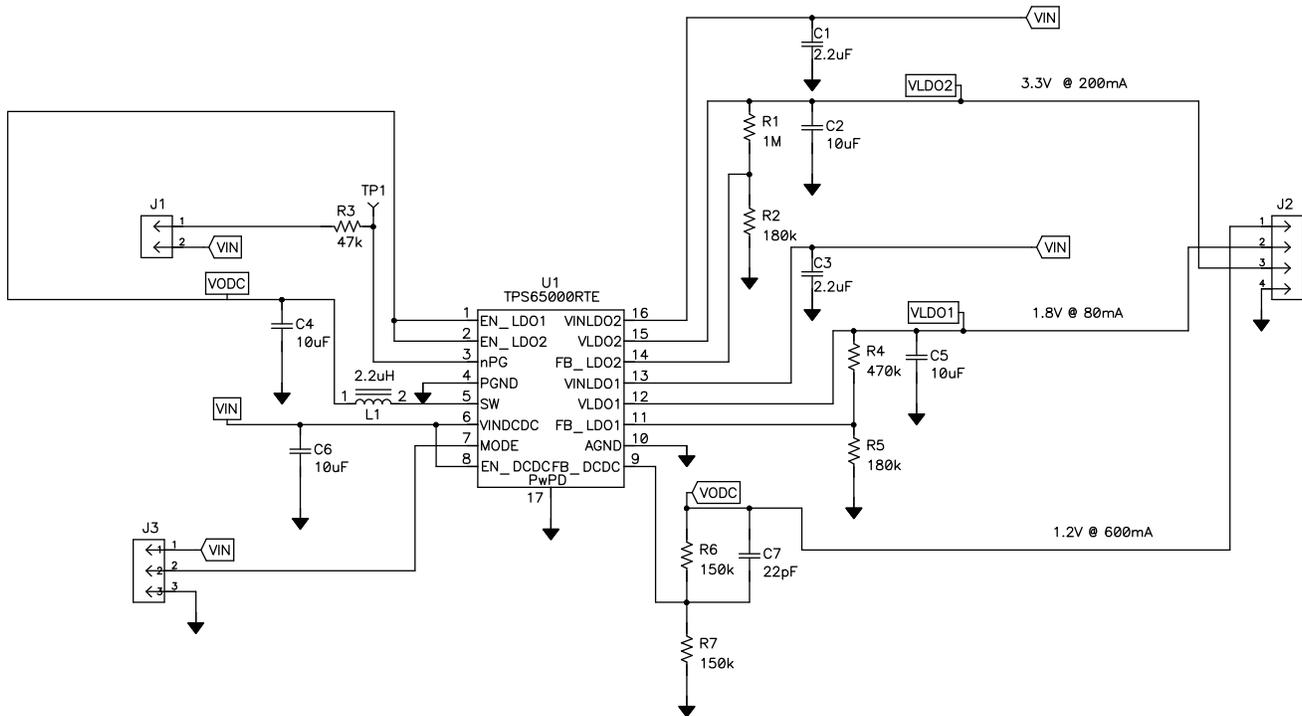


Figure 1. PMP5000 Reference Design Schematic

Proper sequencing is achieved in the design with the use of enable pins. The Core 1.2V at 1000mA (Step Down Converter in TPS65000) comes first, which in turn enables the LDOs of the device thus, following the required sequence.

4 List of Material

Table 2. PMP5000 List of Material

Count	RefDes	Value	Description	Size	Part Number	MFR	AREA
2	C1	2.2 µF	Capacitor, Ceramic, vV, [temp], [tol]	0603	GRM39yyyxxxKvvvA	Murata	5650
4	C2	10 µF	Capacitor, Ceramic, 10 µF, 10V, X5R, 10%,	0805	GRM21BR61A106KE19L	Murata	10560
	C3	2.2 µF	Capacitor, Ceramic, vV, [temp], [tol]	0603	GRM39yyyxxxKvvvA	Murata	5650
	C4	10 µF	Capacitor, Ceramic, 10 µF, 10V, X5R, 10%,	0805	GRM21BR61A106KE19L	Murata	10560
	C5	10 µF	Capacitor, Ceramic, 10 µF, 10V, X5R, 10%,	0805	GRM21BR61A106KE19L	Murata	10560
	C6	10 µF	Capacitor, Ceramic, 10 µF, 10V, X5R, 10%,	0805	GRM21BR61A106KE19L	Murata	10560
1	C7	22 pF	Capacitor, Ceramic, 22 µF, 6.3V, X5R, 20%,	0805	GRM21BR60J226ME39L	Murata	10560
1	J1	PTC36SAAN	Header, Male 2-pin, 100 mil spacing, (36-pin strip)	0.100 inch x 2	PTC36SAAN	Sullins	
1	J2	PTC36SAAN	Header, Male 4-pin, 100 mil spacing, (36-pin strip)	0.100 inch x 4	PTC36SAAN	Sullins	50000
1	J3	PTC36SAAN	Header, Male 3-pin, 100 mil spacing, (36-pin strip)	0.100 inch x 3	PTC36SAAN	Sullins	0.043 inch
1	L1	2.2 µH	Inductor, SMT Multi-layer, yyA, zzmillionhm	2520 mm	MIPS2520D2R2	FDK Corp.	20400
1	R1	1M	Resistor, Chip, 1/10W, 1%	0805	CRCW0805-xxxx-F	Vishay	15,300
2	R2	180k	Resistor, Chip, 1/10W, 1%	0805	CRCW0805-xxxx-F	Vishay	15,300
1	R3	47k	Resistor, Chip, 1/10W, 1%	0805	CRCW0805-xxxx-F	Vishay	15,300

Table 2. PMP5000 List of Material (continued)

Count	RefDes	Value	Description	Size	Part Number	MFR	AREA
1	R4	470k	Resistor, Chip, 1/10W, 1%	0805	CRCW0805-xxxx-F	Vishay	15,300
	R5	180k	Resistor, Chip, 1/10W, 1%	0805	CRCW0805-xxxx-F	Vishay	15,300
2	R6	150k	Resistor, Chip, 1/10W, 1%	0805	CRCW0805-xxxx-F	Vishay	15,300
	R7	150k	Resistor, Chip, 1/10W, 1%	0805	CRCW0805-xxxx-F	Vishay	15,300
1	TP1	10000	Through Hole, 0.040 Dia		STD	STD	0.100 x 0.100 inch
1	U1	TPS65000RTE	IC, 2.25MHz Step-Down Converter W/ dual LDO and SVS	QFN-16	TPS65000RTE	TI	83200
Notes: 1. These assemblies are ESD sensitive, ESD precautions shall be observed. 2. These assemblies must be clean and free from flux and all contaminants. Use of no clean flux is not acceptable. 3. These assemblies must comply with workmanship standards IPC-A-610 Class 2. 4. Ref designators marked with an asterisk (***) cannot be substituted. All other components can be substituted with equivalent MFG's components.							

5 Test Results

The startup waveform, shown in [Figure 2](#), demonstrates that the required sequencing order is followed.

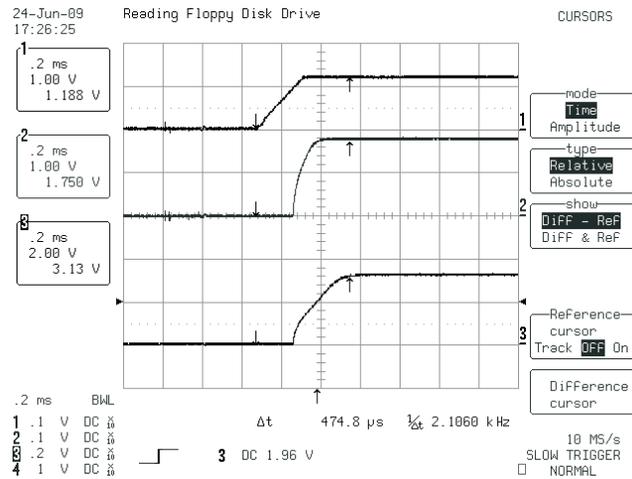


Figure 2. Shows Sequencing in Start up Waveform

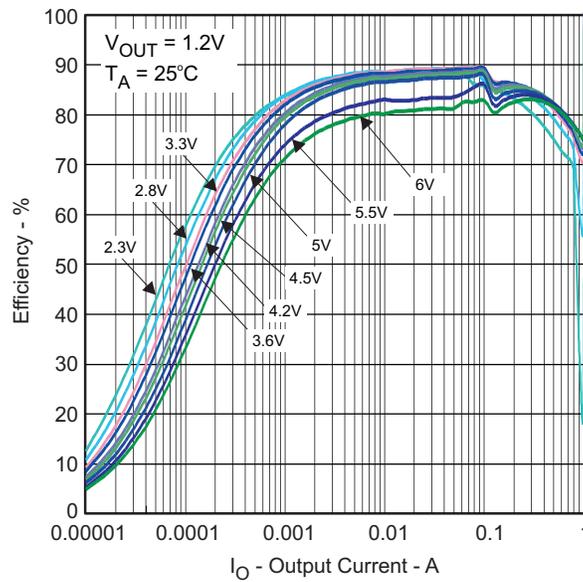


Figure 3. Efficiency vs Output Current (TPS65000)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated