

Simple CC/CV Charger using TPS54331

S.Nikhil

Abstract


The TPS54331 is a non-synchronous buck converter that integrates a low $R_{DS(on)}$ high side MOSFET and is designed to provide up to a 3A output from an input voltage source of 3.5 V to 28 V. This application note explains the procedure of converting a simple buck converter into a CC/CV charger with low component count for charging a SMF Lead Acid Battery. This concept can be extended to multiple parts in the same family.

Specifications

Vin	Input Voltage Range	16.5V to 21V
Battery Specifications	Capacity	12V, 7.2Ah
Output Specifications	Charging Current	0.3C
	Voltage during CV Mode Charging	14.2V
Fsw	Switch Frequency	570KHz

Design Notes

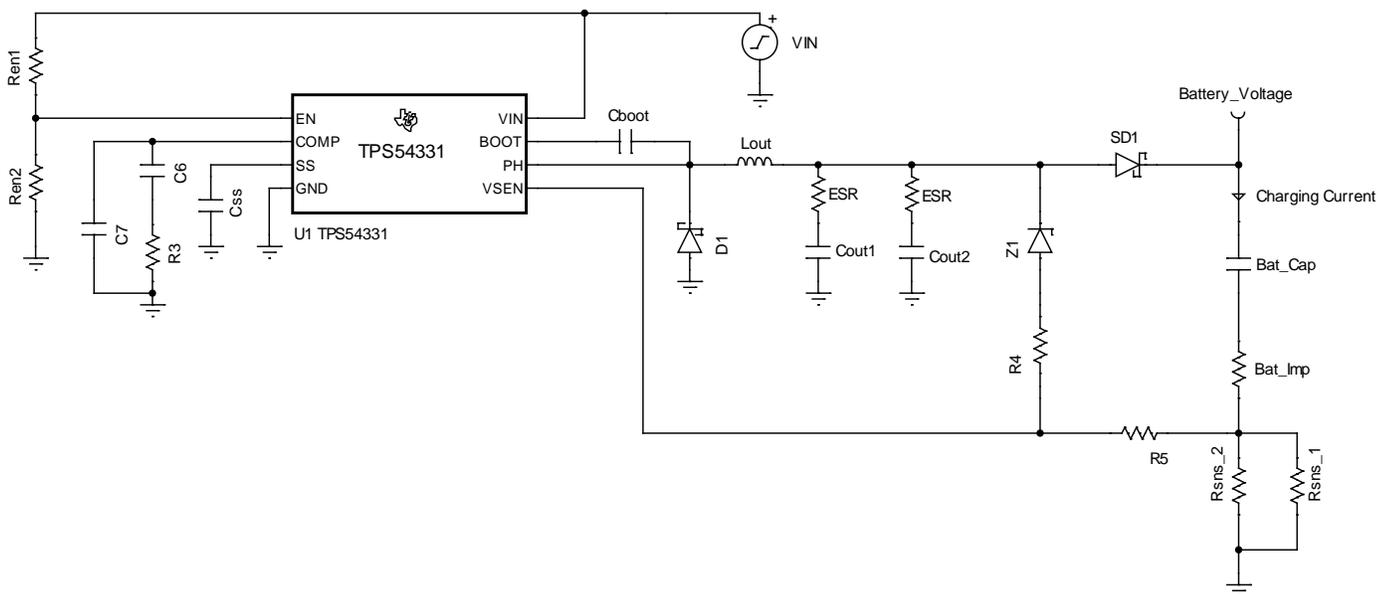Shown below is the generic schematic of the implementation.



Circuit Explanation

Assuming that we connect an uncharged battery to the output terminals, when the circuit is enabled, the Zener diode Z1 is reverse biased and will not conduct. Since the battery can consume all the current given to it, limiting the current is mandatory. During this stage, the current sensing resistor will provide the necessary closed loop feedback to the chip to maintain a constant current (CC) based charging. As the battery starts charging the voltage starts building on the battery and reaches the value of the zener voltage breakdown limit. Once it exceeds this value, the zener will now maintain a constant voltage (CV) of $V_z + V_{ref}$ on the battery. The resistors R4 and R5 are added to have better control of voltage during the CV mode of charging rather than depending only the breakdown tolerance between different zener diodes. The constant voltage output with these resistors is governed by the equation:

$$V_{out} = V_z + (V_{ref} \times \frac{R_4 + R_5}{R_5})$$

Effect of different values of the R4 and R5 in CV Mode

1. If R4 is 0, then $V_{out} = V_z + V_{ref}$
2. If $R_4 \gg R_5$, then V_{out} will rise abnormally resulting in damage to the life of the battery and the device.
3. If R5 is 0, then V_{out} will rise abnormally resulting in damage to the life of the battery and the device.
4. If $R_5 \gg R_4$, then will be $V_{out} \sim V_z + V_{ref}$.

All these effects can be visualized in the simulation. The results are shown in the last section.

Selection of Power Stage Components (Inductor, Capacitors, Freewheeling Diode and Protection Diode)

The power stage components are designed using the standard equations given the datasheet of this device (<http://www.ti.com/lit/ds/symlink/tps54331.pdf>). Based on the above specifications

- $L_{out} (\text{min}) = 13.55\mu\text{H}$, Selected **Lout – 15 μH**
- Diode D1 needs to carry a maximum current of $I_{out} \times (1-D)$ and must have a voltage rating of $> V_{inmax} + 0.7$, Selected **D1 - MBR340**
- Selected **Cout1 and 2 – 47 μF , 5m ESR**
- Since the battery can discharge into the resistors R4 and R5 if the power supply is turned off, a battery current leakage prevention diode is added at the output. **SD1 – MBRS340**

Connecting the battery

Connect the battery positive to the Output terminal and the battery negative to the Current Sense Resistor. In the schematic above the battery is modeled as a large capacitor (battery capacitance) with a series resistor (battery impedance) to produce the required charging characteristics.

Selection of Sense Resistor (RSNS)

The sense resistors are chosen according to the required charging current and buck converter feedback sense voltage available on the VSEN pin. For TPS54331 it is 0.8V. For a charging current of 2A, the sense resistor value will be:

$$R_{sns} = \frac{V_{sns}}{I_{out}} = 0.4 \Omega$$

The power rating of the resistor needs to be

$$P_{rsns} = I_{out}^2 \times R_{sns} = 1.6 W$$

To thermally size the resistor correctly we chose two resistors in parallel. $R_{sns_1} = 800m\Omega$ and $R_{sns_2} = 800m\Omega$

Selection of Z1

Depending the desired battery voltage required, select either a 13V or 12V Zener.

Selection of R4 and R5

For producing a 14.2V Output, using a 12V Zener and a diode drop of 0.3V on SD1, we can make $R4 = 85\Omega$ and $R5 = 40\Omega$.

Selection of Compensation Components (R3, C6 and C7)


The TPS54331 follows current mode compensation and has a transconductance amplifier for the error amplifier. The error amplifier compares the VSENSE voltage to the internal effective voltage reference presented at the input of the error amplifier. Since the reference feedback is coming from the voltage developed across the sense resistor, the compensation will be similar to that of a normal voltage feedback based output and can be calculated as per the standard equations in the datasheet and the components R3, C6 and C7 can be connected as shown in the schematic on the first page. So we can use $R3 = 29.4k\Omega$, $C6 = 1nF$, $C7 = 47pF$.

Enable Circuit

Enable can be adjusted to either work from a external controller or in a self enabled mode. Care should be taken to ensure that the enable signal should not exceed 6V. By using $R_{en1} = 332k\Omega$ and $R_{en2} = 68.1k\Omega$, the enable is between 2.7V to 3.5V.


Final Circuit

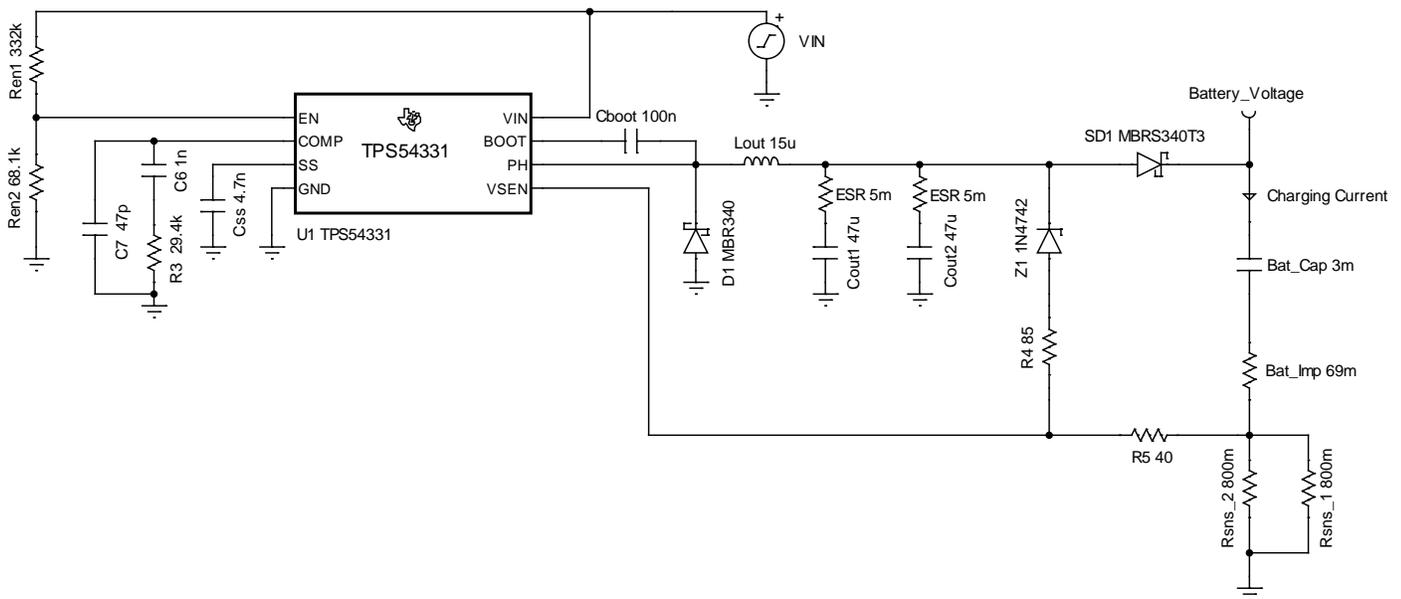The final circuit after the adding the designed values are:




Simulation Results

Complete CC/CV Charging Profile Waveform

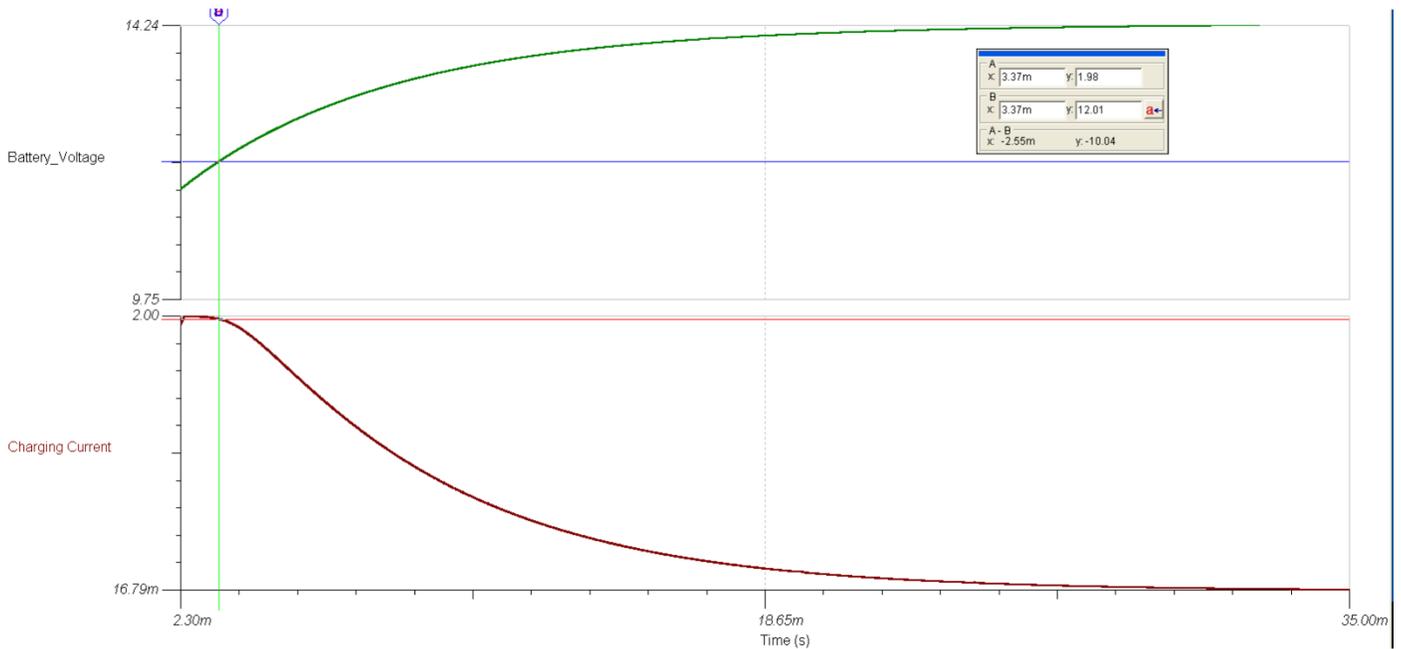

The initial condition assumed it that the battery is in a discharged mode. As observed, the CC Mode lasts till the 12V zener breaks down. At 12V, the CV Mode beings and the current begins to reduce. The voltage builds to $V_z = 12V + 2.5V$ due to the resistor network of R4 and R5.

CC Mode Current Waveform

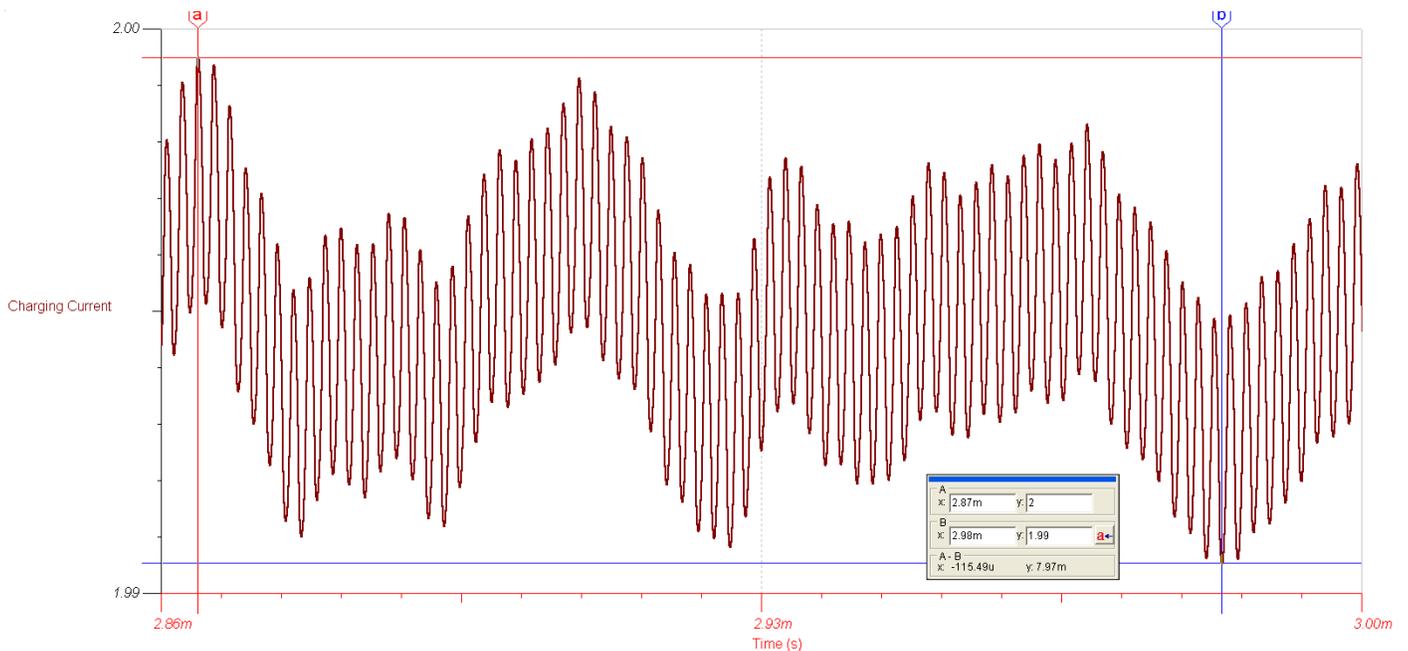

The current ripple during the CC Mode is found to be around 8mA. The ripple frequency noticed is that of the switching frequency.

Conclusion

Although it may not be the most accurate way to do a CC/CV charger due to the regulation of the zener, a simple low cost solution can still be realized. Depending on charging current requirements we can have discrete implementation of the converter.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com