

Rakesh Panguloori

Introduction

The advent of smart electricity meters brought standardized advanced metering infrastructure (AMI) to facilitate basic requirements for installation, metering, maintenance, privacy, and security. As shown in Figure 1, the AMI has five communication ports P₀-P₄, of which ports P₁ and P₃ are critical.

Port P₁ (also called *user port*) provides interface with the end consumer and is designed for in-house communication to provide real-time data for further analysis via Other Services Module (OSM) such as in-home displays. P₁ is a read-only interface. Port P₃ supports two-way communication and acts as interface to an external communications module.

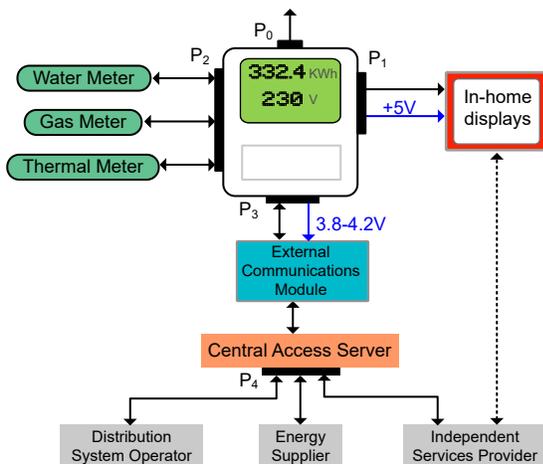


Figure 1. Illustration of Smart Metering Infrastructure

The ports P₁ and P₃ includes both power and data lines, and should be designed in such a way that they do not interfere with the metrology of the electricity meter under any external faults. These two ports should comply to safety protection requirements as per IEC 60747-5-5, and Dutch P1 Companion standards. [eFuses in Smart Electricity Meters](#) Application Brief highlights how the protection functions of TI eFuse and power MUX devices safeguard Port P₃ of the electricity meter from an external communication module malfunction or faults. This article addresses the protection solution for the user port P₁.

Port P1 Protection Requirements

The port P₁ provides galvanically isolated power to OSM on +5 V rail with maximum continuous current I_{L_CONT} of 250 mA. The protection requirements on +5 V power supply line at port P₁ side are

- Overload protection should trigger for currents above I_{L_CONT} + 10 mA (for example, 260 mA) but within I_{L_MAX} <= 300 mA
- Short-circuit protection
- Overvoltage protection from external overvoltage > 5.9 V, caused by or a failure at OSM side or by an incorrect connection. Similarly, OSM device should be protected from an overvoltage caused by a failure at metering system side, and should limit the voltages to less than 15 V.
- For sustained overload or short-circuit faults, current should fold back to maximum of 50 mA to reduce system operating temperatures and to avoid any harmful effects. The fold back current profile is illustrated in Figure 2

Implementing all these protection features could result in a large discrete circuit. In addition, realizing the foldback current limiting can be tricky to implement as it needs a means to detect overload and then adjust the current limit reference. All these discretely occupies significant board space and could not be possible to accommodate in a space constraint smart meter.

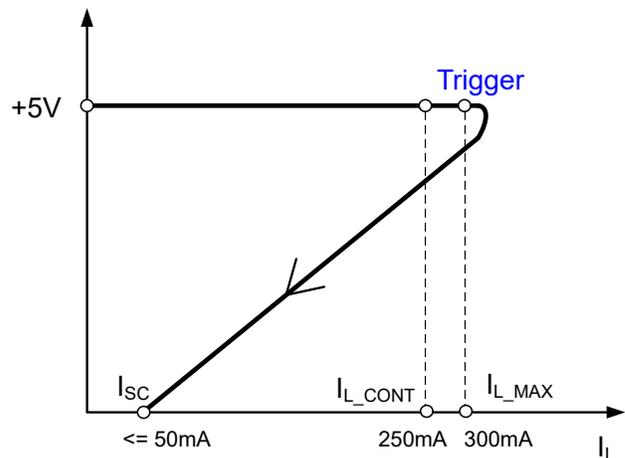


Figure 2. Fold Back Current Limiting Characteristics

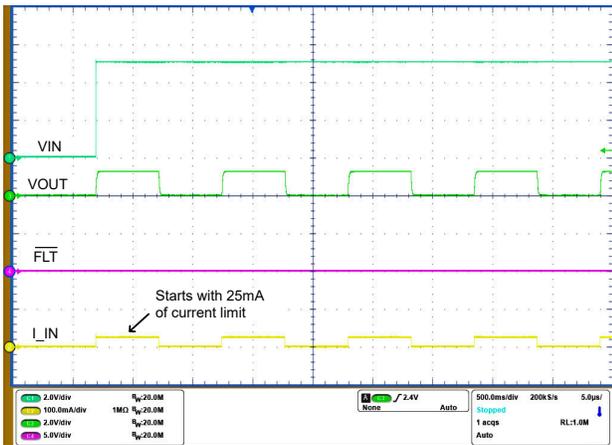


Figure 6. Startup Failure due to Reduced Current Limit with Fold Back Feature

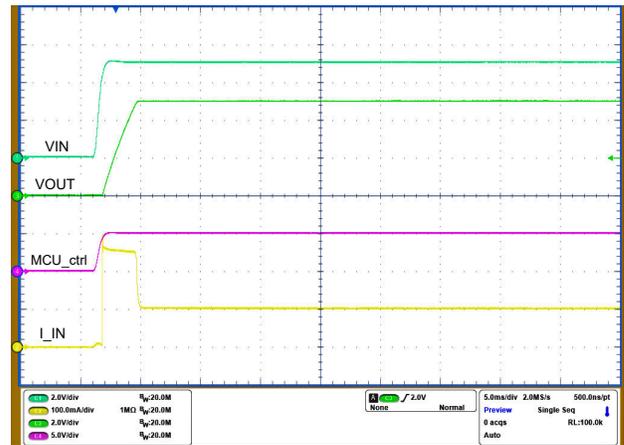


Figure 7. Successful Startup with a Reset Signal from MCU

Conclusion

The port P₁ in smart meter acts as interface with the end consumer and hence demands stringent protection to avoid influencing the metering system as well as protecting the OSM (Other Service Module) devices such as in-house displays. The full suite of protection features from TPS2662 eFuse along with the fold back current limiting approach presented in this article makes it a suitable solution for the protection of P₁ ports in smart meters.

References

1. Texas Instruments, *eFuses in Smart Electricity Meters*, application brief.
2. Texas Instruments, *TPS2662x 60-V, 800-mA Industrial eFuse with Integrated Input and Output Reverse Polarity Protection*, data sheet.
3. Dutch Smart Meter Requirements, *P1 Companion Standard*, 2016.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated