

TPS23750 PMP1360 12 V at 1 A PoE PD

PMP1360 is a high efficiency, isolated, non-synchronous flyback Power-over-Ethernet PD power-supply reference design intended to ease implementation of PoE in devices such as IP phones, WLAN AP's and security cameras. The reference design uses a TPS23750 PoE Powered Device Controller with integrated, current-mode DC/DC controller. The TPS23750 implements all necessary detection, classification, inrush current limiting and UVLO functions necessary to comply with the IEEE802.3af Power-over-Ethernet standard. The 48-V PoE input is converted to 12 V at 1 A at the output. This reference design is optimized for 86% efficiency in the smallest board area possible. The schematic diagram is shown in [Figure 8](#).

Contents

1	Performance.....	2
	1.1 Efficiency.....	2
	1.2 Turn On Response	2
	1.3 Output Ripple and Noise.....	3
	1.4 Input Ripple and Noise.....	4
	1.5 Dynamic Loading	4
	1.6 Stability Analysis (Loop Gain).....	5
2	Reference Design Schematic and Bill of Materials.....	6

List of Figures

1	Efficiency.....	2
2	Turn-On Response, No Load	2
3	Turn-On Response, 1-A Load.....	3
4	Output Ripple Voltage With 48-V Input and 1-A Load (across C10).....	3
5	Input Ripple Voltage With 48-V Input and a 1-A Load (across J2-1 and 3)	4
6	Output Voltage Transient Response	4
7	Loop Gain.....	5
8	TPS23750 Power-Over-Ethernet PD Power Supply Reference Design	6

List of Tables

1	Bill of Materials.....	7
---	------------------------	---

1 Performance

1.1 Efficiency

Efficiency was measured with the following loads and 48-V input at J2 and J4,

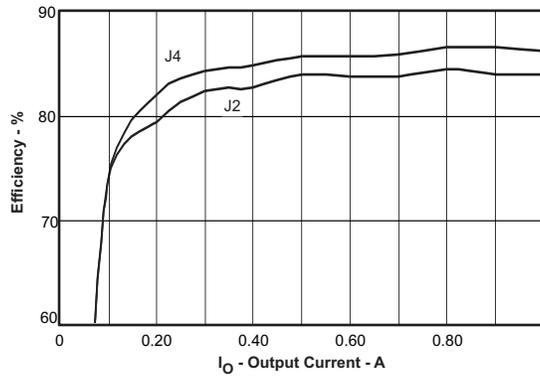


Figure 1. Efficiency

1.2 Turn On Response

The turn-on response with a 48-V input and 0-A load is shown in Figure 2.

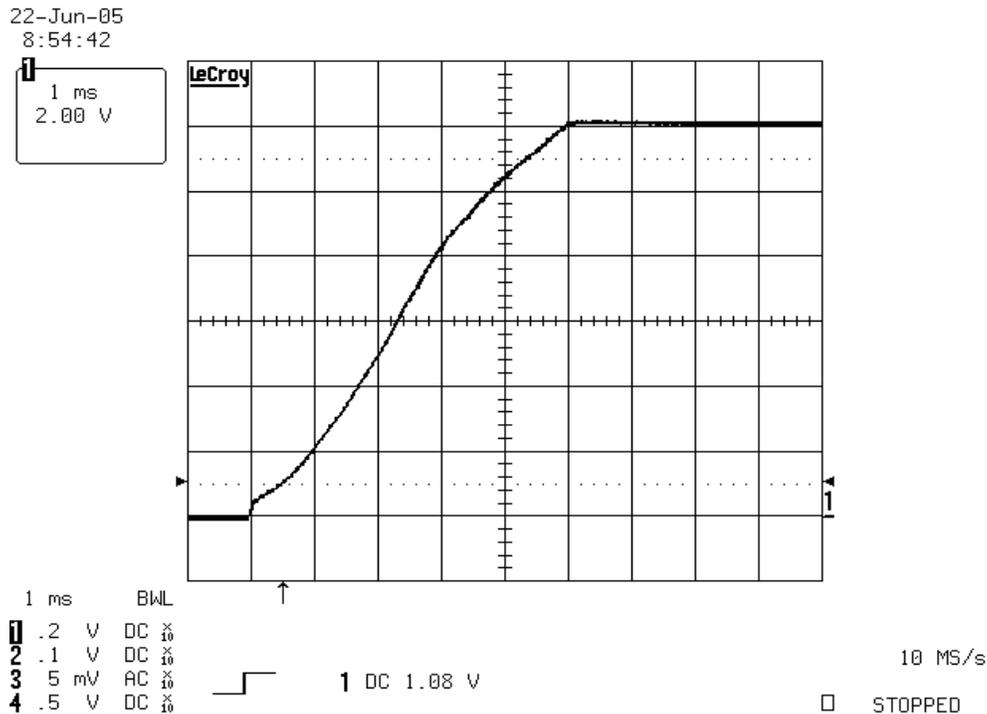


Figure 2. Turn-On Response, No Load

The turn-on response with a 48-V input and 1-A load is shown in Figure 3.

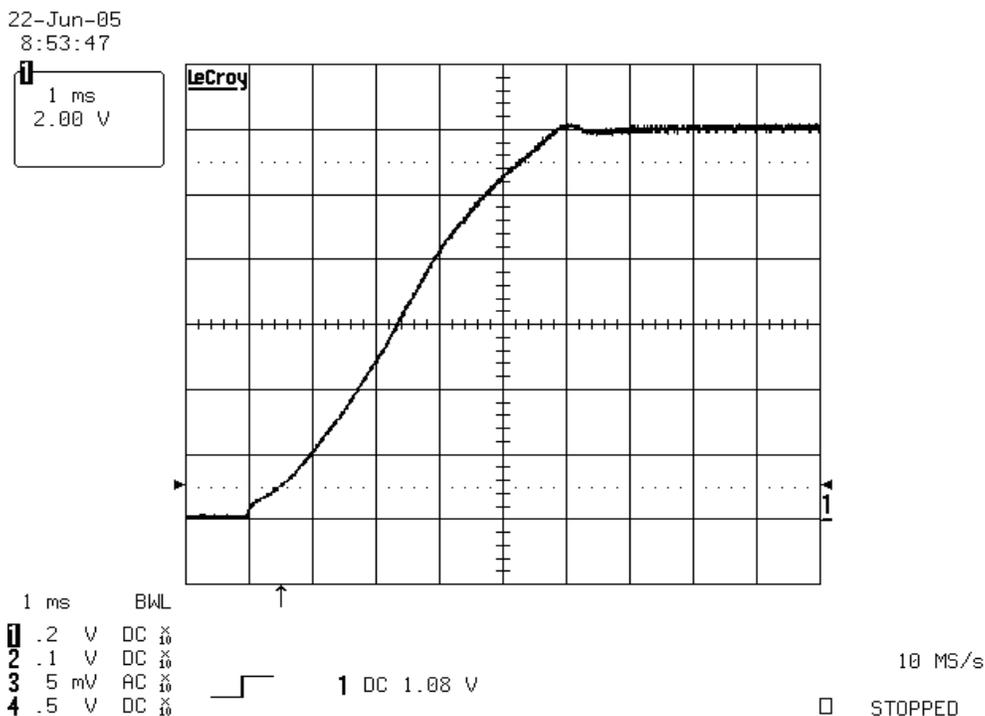


Figure 3. Turn-On Response, 1-A Load

1.3 Output Ripple and Noise

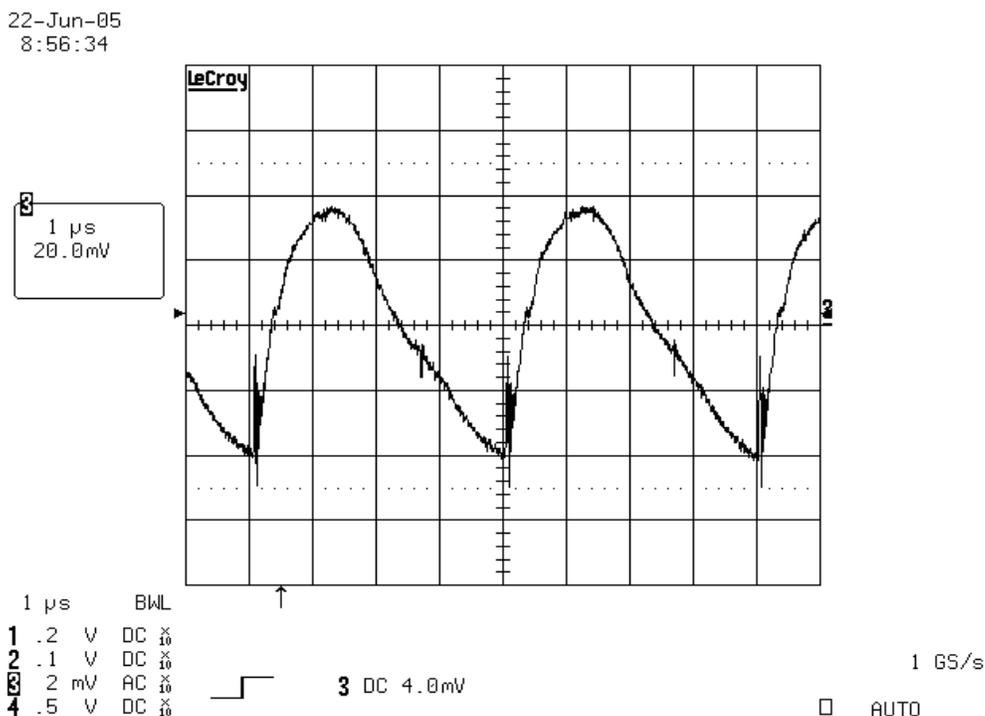


Figure 4. Output Ripple Voltage With 48-V Input and 1-A Load (across C10)

1.4 Input Ripple and Noise

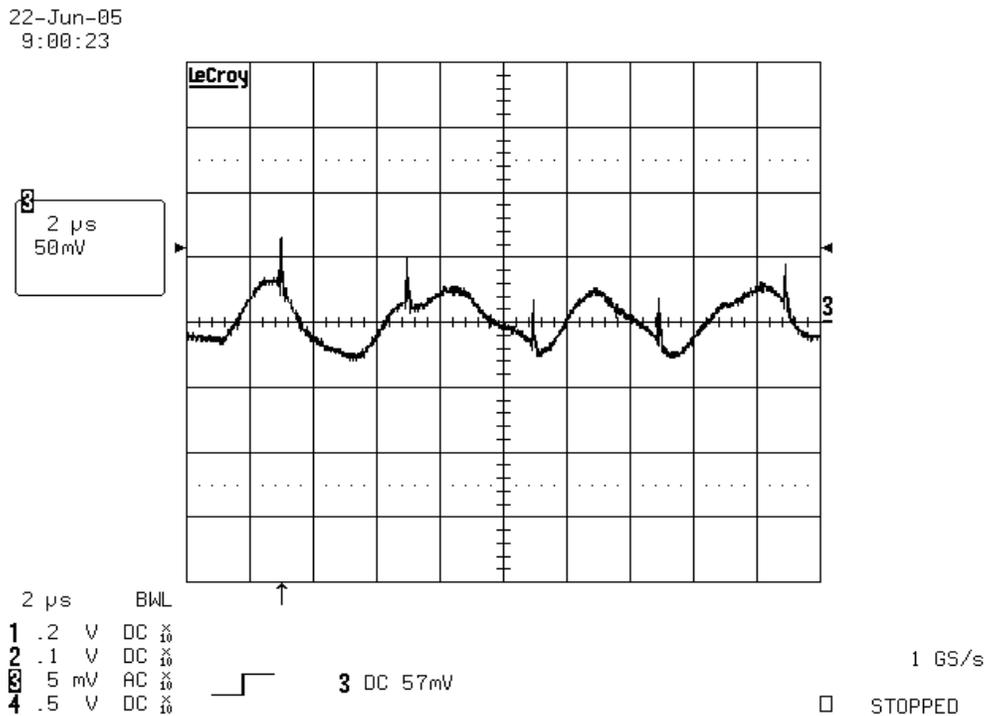


Figure 5. Input Ripple Voltage With 48-V Input and a 1-A Load (across J2-1 and 3)

1.5 Dynamic Loading

The output voltage transient response was measured with a load step from 50% to 100% and 100% to 50%.

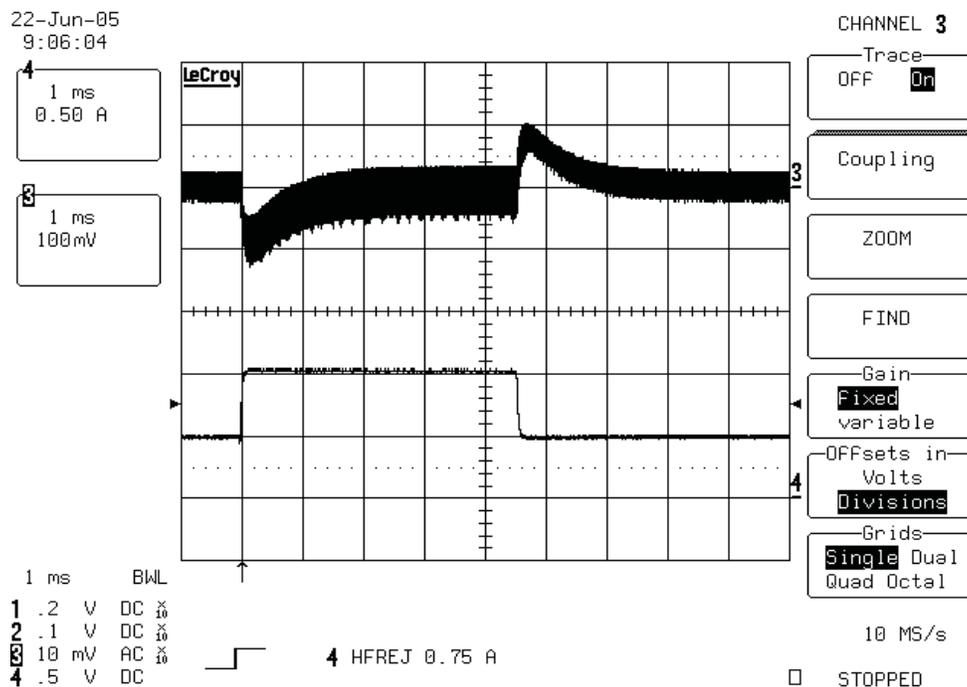


Figure 6. Output Voltage Transient Response

1.6 Stability Analysis (Loop Gain)

Figure 7 shows the loop gain of the converter. The bandwidth is 3 kHz, the phase margin is 90°, and the gain margin is 20 dB.

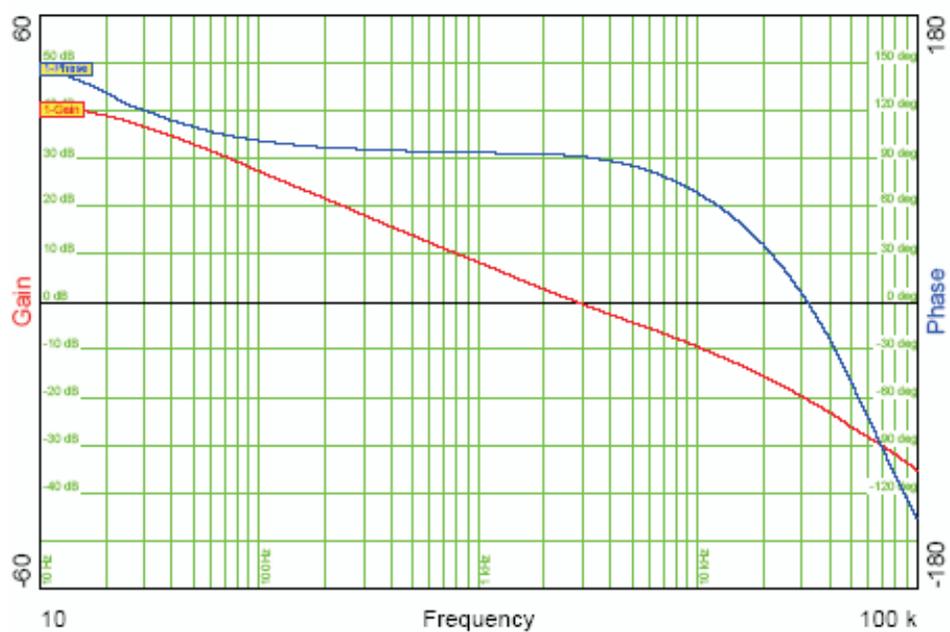


Figure 7. Loop Gain

2 Reference Design Schematic and Bill of Materials

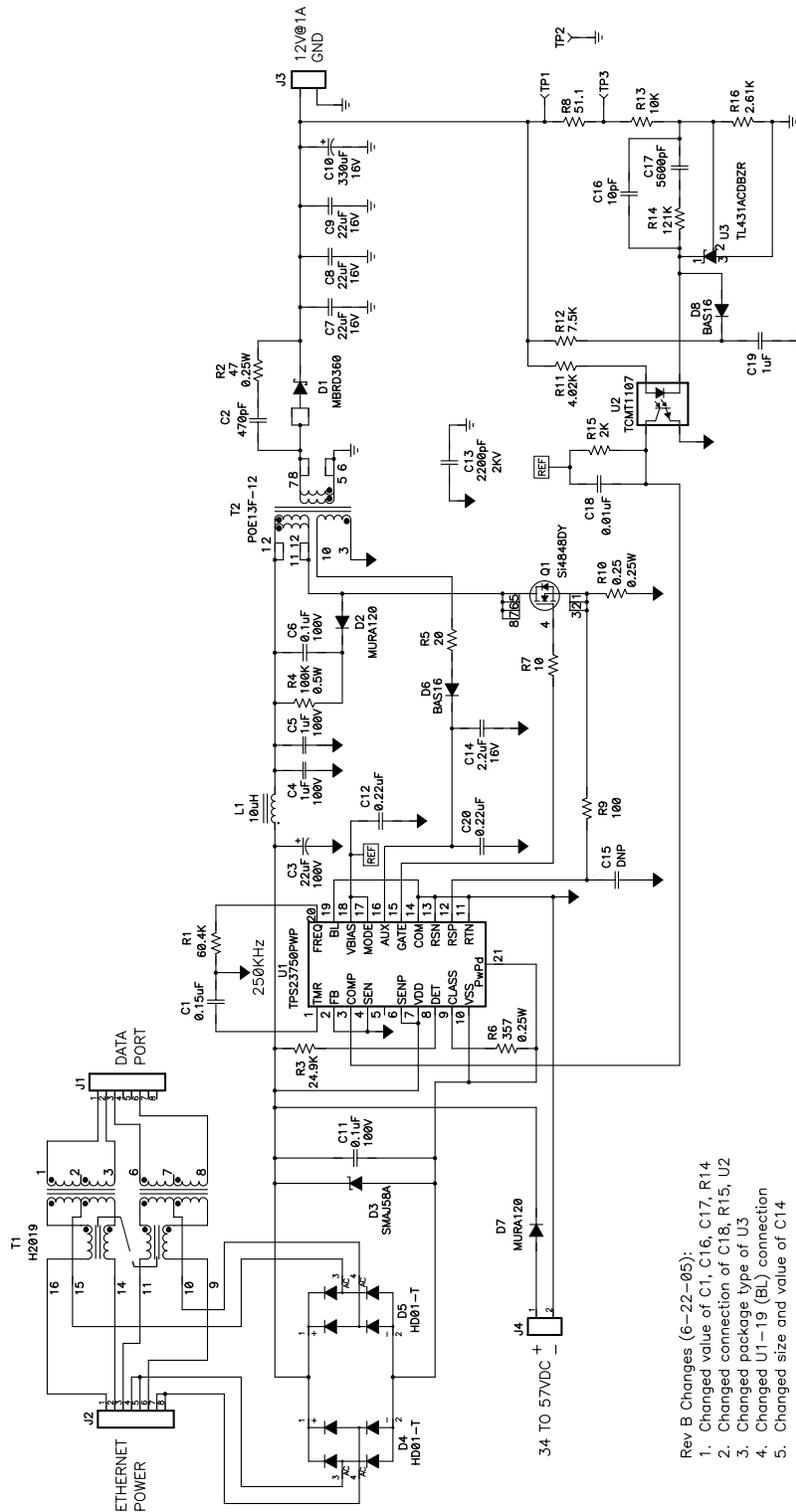


Figure 8. TPS23750 Power-Over-Ethernet PD Power Supply Reference Design

Table 1. Bill of Materials

Count	RefDes	Description	Size	MFR	Part Number
1	C16	Capacitor, Ceramic, 10pF, 50V, C0G, 5%	603	Std	Std
1	C17	Capacitor, Ceramic, 5600pF, 50V, X7R, 5%	603	Std	Std
1	C18	Capacitor, Ceramic, 0.01 μ F, 50V, X7R, 10%	603	Std	Std
1	C1	Capacitor, Ceramic, 0.15 μ F, 16V, X7R, 10%	603	Std	Std
1	C2	Capacitor, Ceramic, 470pF, 100V, C0G, 5%	805	Std	Std
2	C6, C11	Capacitor, Ceramic, 0.1 μ F, 100V, X7R, 10%	805	TDK	C2012X7R2A104K
2	C12, C20	Capacitor, Ceramic, 0.22 μ F, 25V, X7R, 10%	805	Std	Std
1	C19	Capacitor, Ceramic, 1 μ F, 16V, X7R, 10%	805	Std	Std
1	C14	Capacitor, Ceramic, 2.2 μ F, 16V, X7R, 10%	805	TDK	Std
2	C4, C5	Capacitor, Ceramic, 1 μ F, 100V, X7R, 10%	1210	TDK	C3225X7R2A105K
3	C7, C8, C9	Capacitor, Ceramic, 22 μ F, 16V, X5R, 20%	1210	TDK	C3225X5R1C226M
1	C13	Capacitor, Ceramic, 2200pF, 2kV, X7R, 10%	1812	TDK	C4532X7R3D222K
1	C3	Capacitor, Aluminum, 22 μ F, 100V, 20%	8x10mm	Panasonic	EEVFJ2A220P
1	C10	Capacitor, Aluminum, 330 μ F, 16V, 20%	8x10,2mm	Panasonic	EEVFK1C331P
1	D1	Diode, Schottky, 3A, 60V	DKPAK	On Semi	MBRD360
2	D2, D7	Diode, Rectifier, 1A, 200V	SMA	On Semi	MURA120
1	D3	Diode, TVS, 58-V, 1W	SMA	Diodes, Inc	SMJ58A
2	D4, D5	Bridge Rectifier, 100V, 0.8V	MINI DIP4	Diodes, Inc	HD01-T
2	D6, D8	Diode, Switching, 200mA, 75V, 225mV	SOT-23	On Semi	BAS16LT1
2	J1, J2	Connector, Jack, Modular, 8 POS	0.705 X 0.820	AMP	520252
2	J3, J4	Terminal Block, 2-pin, 6-A, 3,5 mm	0.27 x 0.25	OST	ED1514
2	TP1, TP3	Test Point, Red, 1 mm	0.038	Keystone	5000
1	TP2	Test Point, Black, 1 mm	0.038	Keystone	5001
1	L1	Inductor, SMT, 10 μ H, 1.1A, 160 m Ω	0.26 x 0.09	Coilcraft	DO1608C-103
1	Q1	MOSFET, N-ch, 150V, 3.7A, 85 m Ω	SO-8	Vishay	Si4848DY
1	R7	Resistor, Chip, 10 Ω , 1/16W, 5%	603	Std	Std
1	R5	Resistor, Chip, 20 Ω , 1/16W, 5%	603	Std	Std
1	R8	Resistor, Chip, 51.1 Ω , 1/16W, 1%	603	Std	Std
1	R9	Resistor, Chip, 100 Ω , 1/16W, 1%	603	Std	Std
1	R15	Resistor, Chip, 2.00 k Ω , 1/16W, 1%	603	Std	Std
1	R16	Resistor, Chip, 2.61 k Ω , 1/16W, 1%	603	Std	Std
1	R11	Resistor, Chip, 4.02 k Ω , 1/16W, 1%	603	Std	Std
1	R12	Resistor, Chip, 7.50 k Ω , 1/16W, 1%	603	Std	Std
1	R13	Resistor, Chip, 10.0 k Ω , 1/16W, 1%	603	Std	Std
1	R3	Resistor, Chip, 24.9 k Ω , 1/16W, 1%	603	Std	Std
1	R1	Resistor, Chip, 60.4 k Ω , 1/16W, 1%	603	Std	Std
1	R14	Resistor, Chip, 121 k Ω , 1/16W, 1%	603	Std	Std
1	R10	Resistor, Chip, 0.25 Ω , 0.25W, 5%	1206	Std	Std
1	R6	Resistor, Chip, 357 Ω , 1/4W, 1%	1206	Std	Std
1	R2	Resistor, Chip, 47 Ω , 0.25W, 5%	1206	Std	Std
1	R4	Resistor, Chip, 100 k Ω , 0.5W, 5%	2010	Std	Std
1	T1	Xfmr, Center-tapped, Voice Over IP	0.500 x 0.370	Pulse	H2019
1	T2	Transformer, SMT for PoE/PD, 12V, 13W, 1.1A	0.677 x 0.865 in	Coilcraft	POE13F-12
1	U2	IC, Photocoupler, 3750VRMS, 80-160% CTR	MF4	Vishay	TCMT1107
1	U3	IC, Precision Adjustable Shunt Regulator	SOT23-3	TI	TL431ACDBZR
1	U1	IC, IEEE 802.3af Integrated primary side controller	PWP20	TI	TPS23750PWP

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
Low Power Wireless	www.ti.com/lpw

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265