

TI *Live!* INDIA AUTOMOTIVE SEMINAR

BING LU

ISOLATED BIAS SUPPLY SOLUTIONS FOR ISOLATED
GATE DRIVERS

Agenda

- Inverter and isolated gate driver bias supply architectures
- Different ways of creating isolated bias supply
 - Control method
 - Topology
 - Transformer
- LLC based open-loop isolated bias supply
 - Operation principles
 - Voltage regulation
- Isolated bias supply with integrated transformers
 - Power density improvement
 - Voltage regulation

Inverters in different applications




Traction inverter



UPS




Motor drive

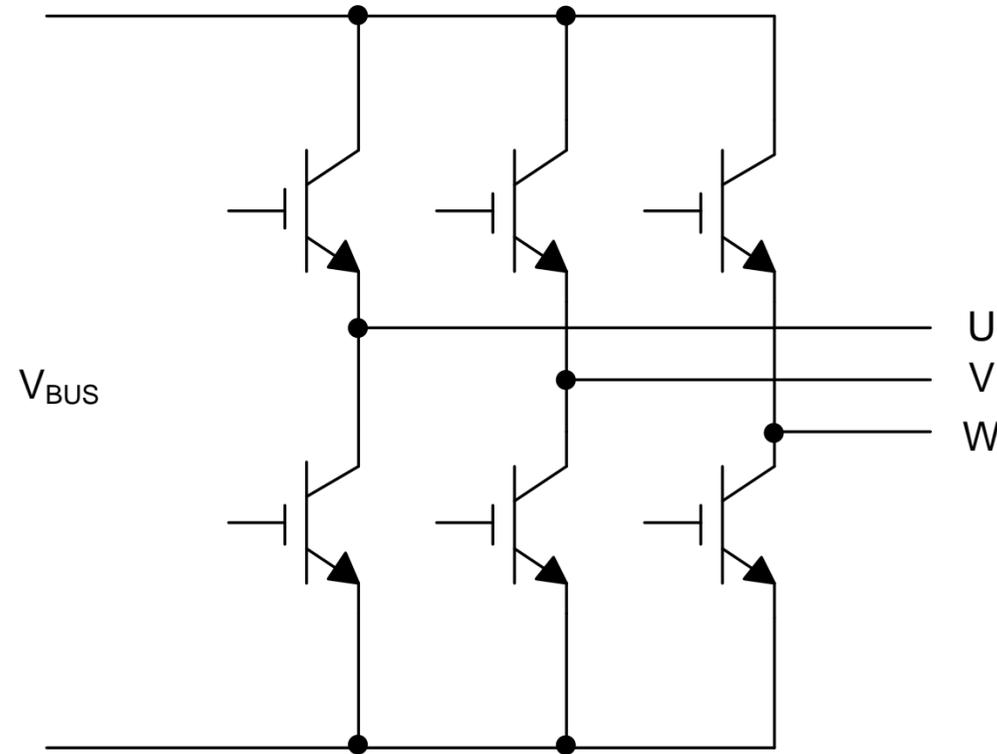


On-board charger

Example: inverter isolation bounds

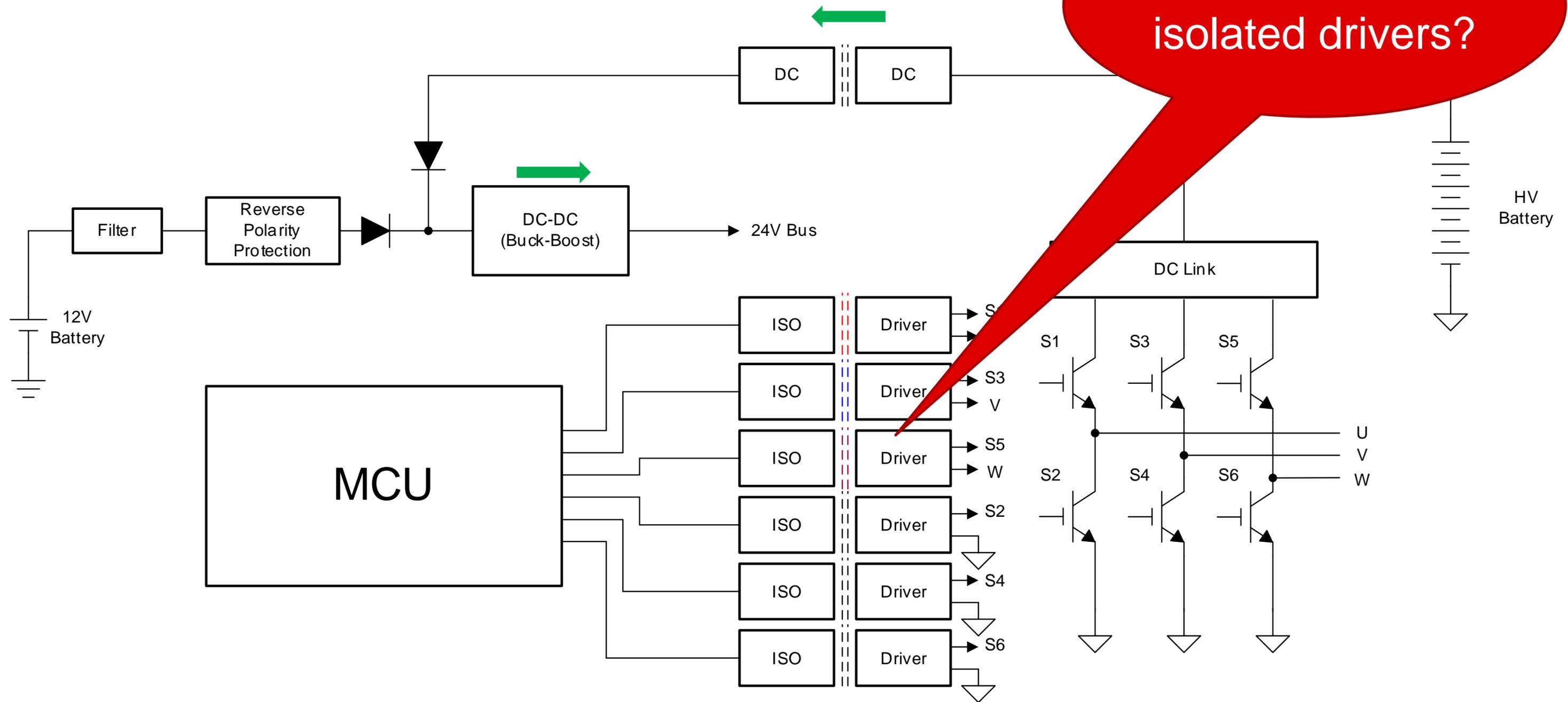


Different gate driver architectures


Centralized

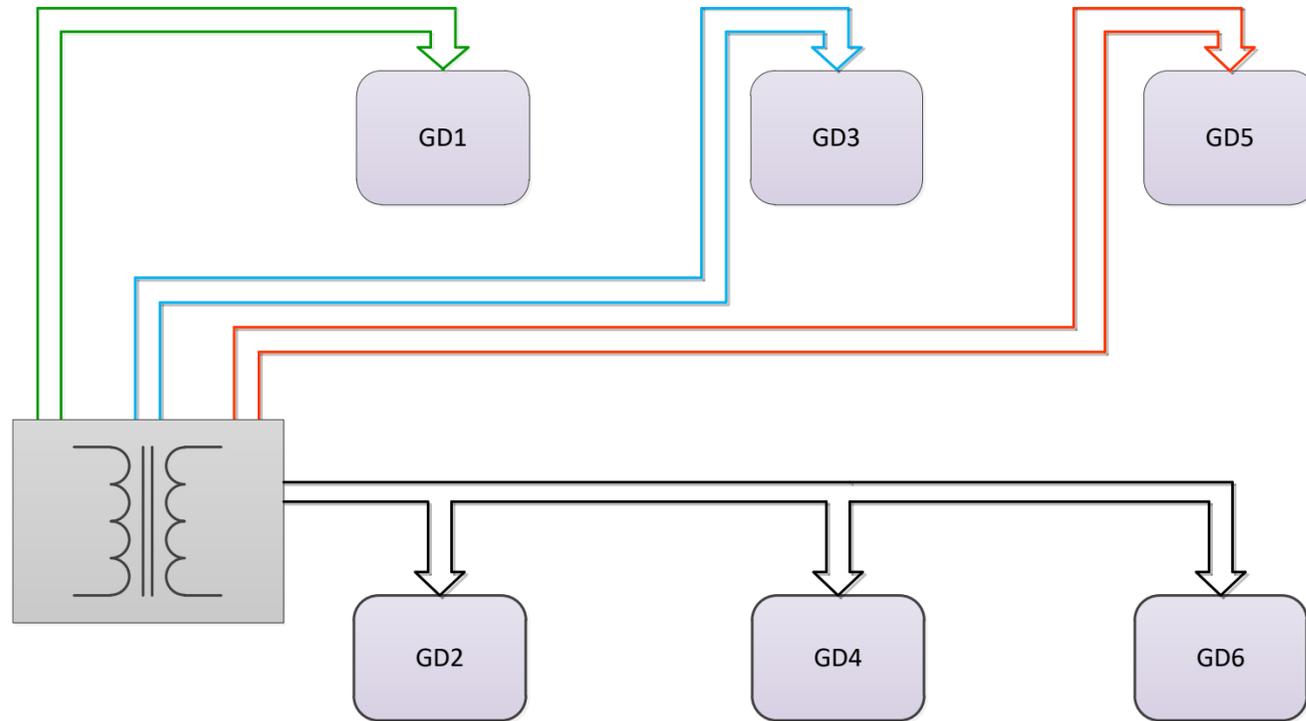

Semi-distributed

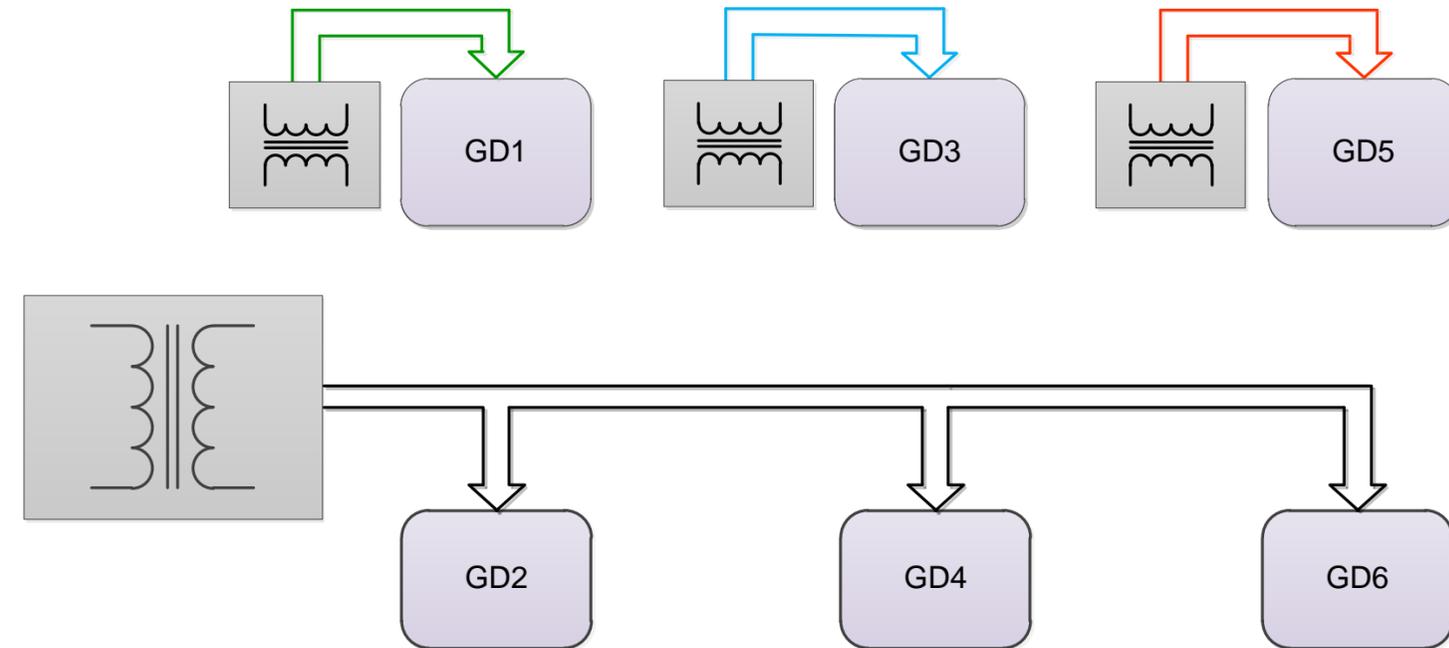


Distributed

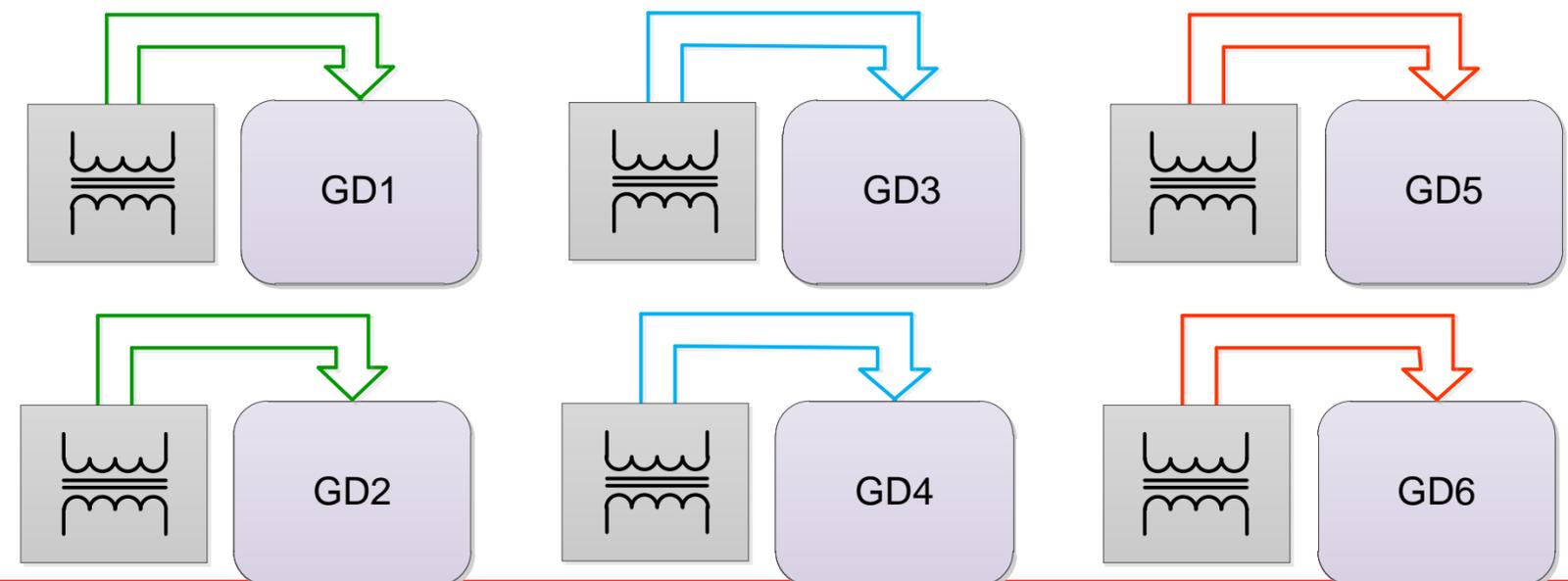

- Centralized system has lowest cost, but heavy and difficult to manage fault
- Distributed systems distribute the weight and fault, but more expensive
- Semi-distributed is somewhere in the middle

Output voltage control

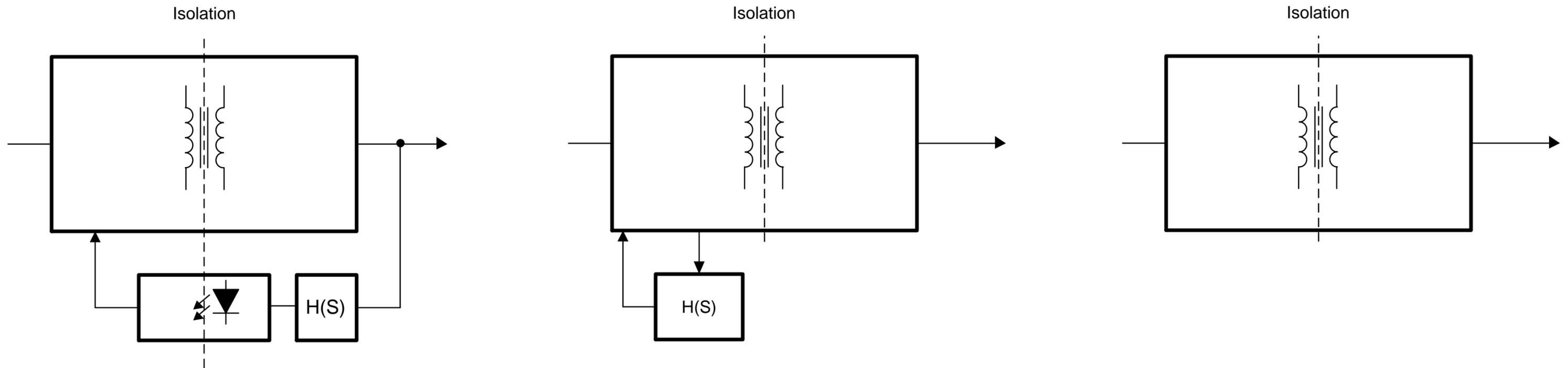

**Close loop
Secondary side feedback**

- Well regulated output
- No need pre-regulator
- **More components**
- **Less reliable due to the opto coupler**

**Close loop
Primary side feedback**

- Semi regulated output
 - Determined by cross regulation
- No need pre-regulator
- **Noise sensitive due to the output voltage sampling method**


**Open loop
No feedback**

- No control loop, robust operation
- Less noise
 - Coupling only through the transformer
- **Unregulated output, need pre-regulator**


Open-loop control provides a robust solution

Topologies used for isolated bias supply


Flyback

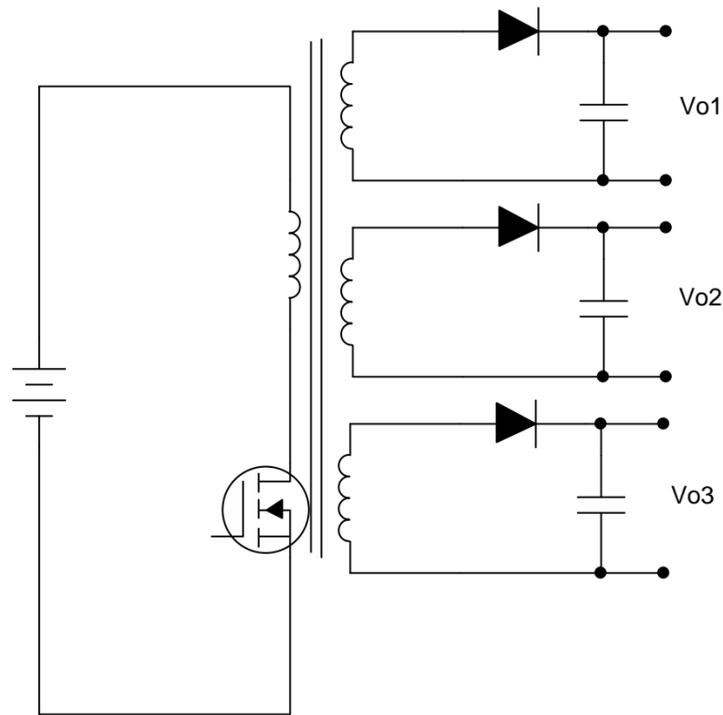


Push-pull

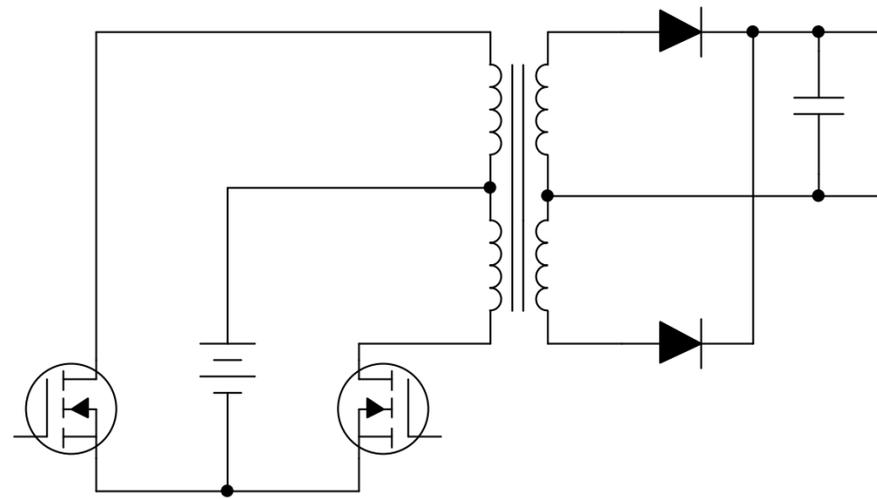


LLC

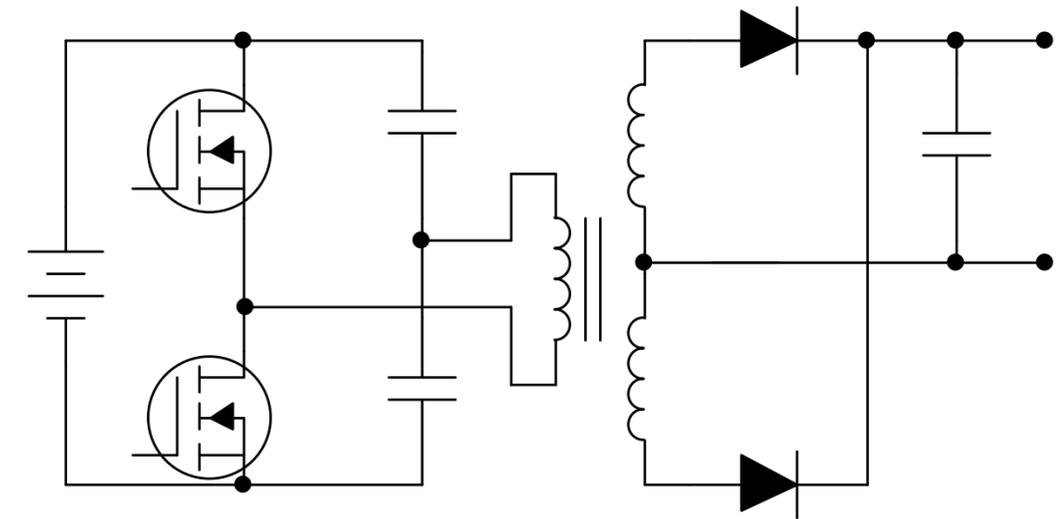

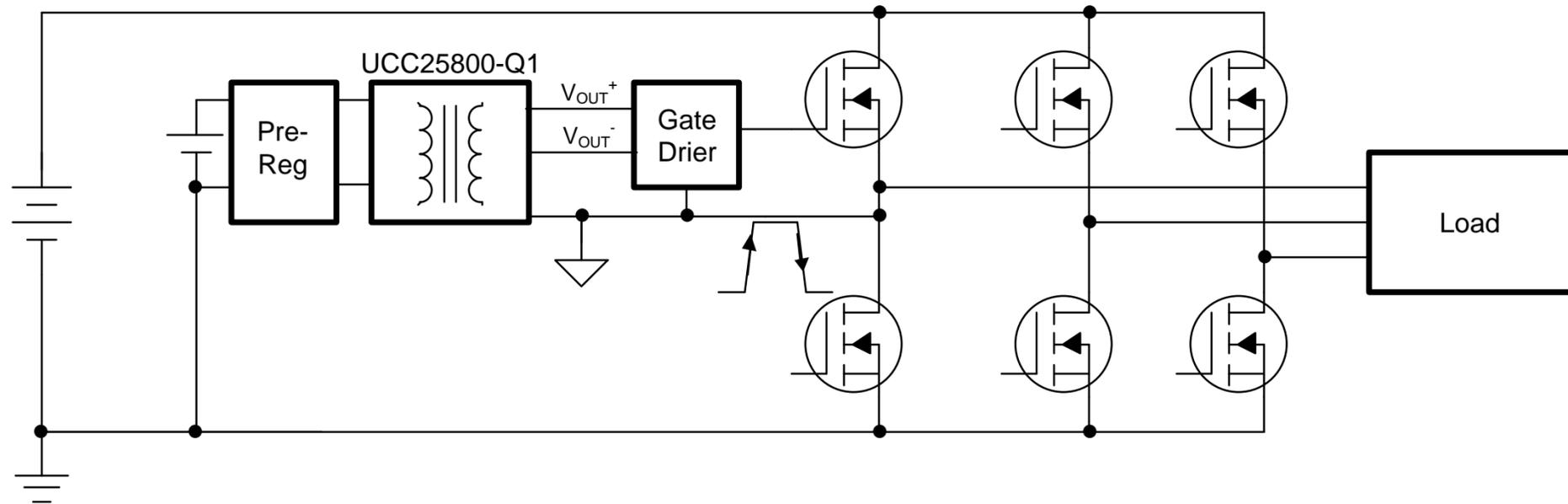Transformer parameter impacts to system EMI




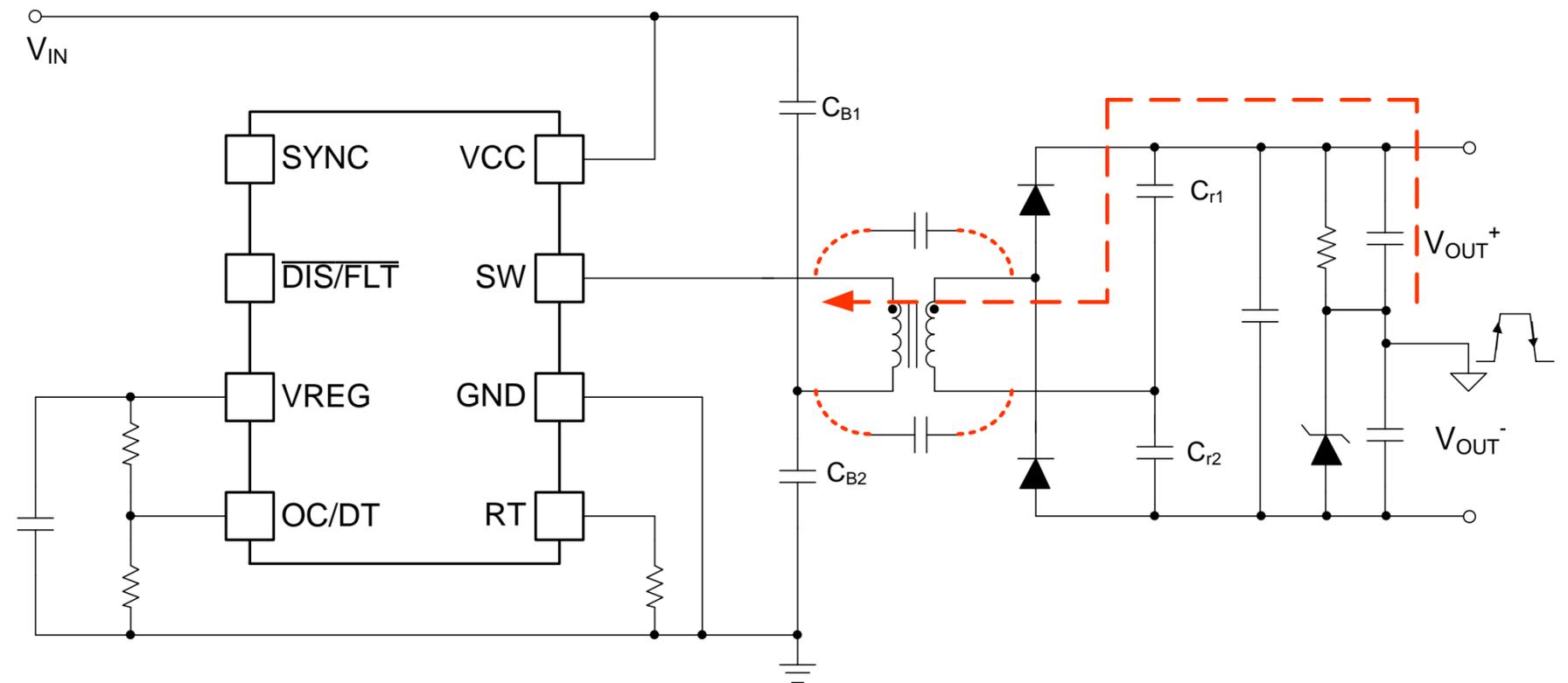- High dv/dt couples through transformer parasitic capacitor to the primary side
- Higher EMI noise
- Extra loss
- More noise to the controller, CMTI issue
- It gets worse with SiC or GaN devices with higher dv/dt



Transformer structure: less parasitic capacitance

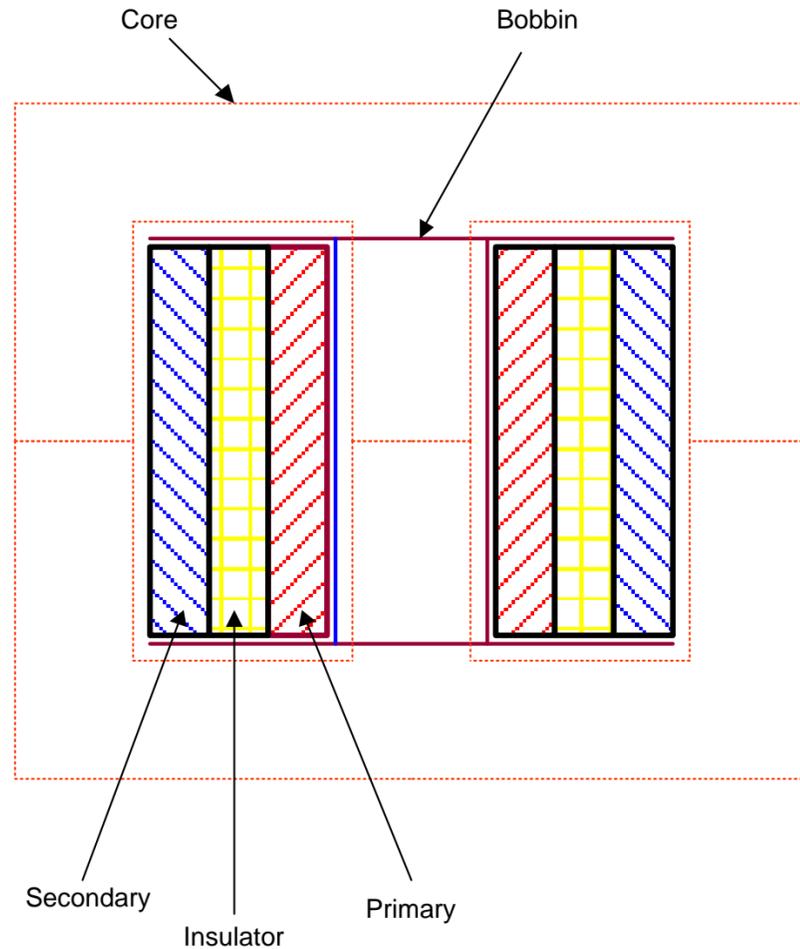
Typical two-winding PSR Flyback transformer



The capacitance can be reduced by increasing the insulator thickness


Less effective due to the large surface area

Typical LLC transformer

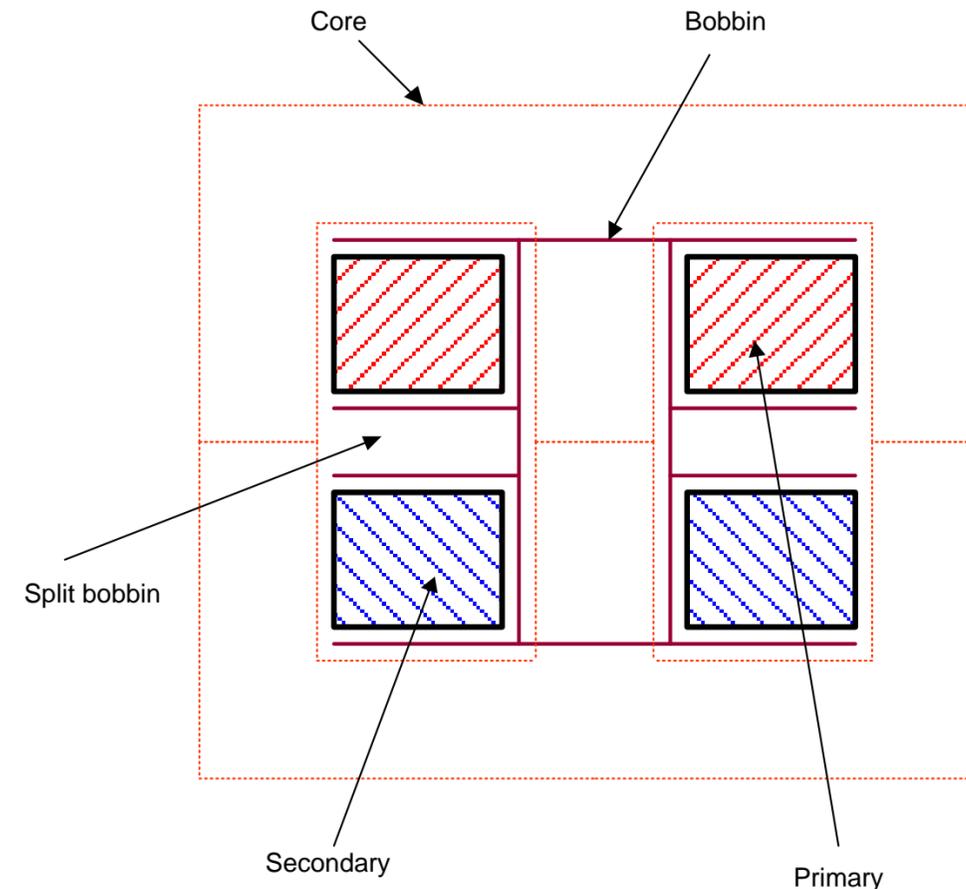

Split bobbin reduces the capacitance by reducing the surface area and increasing the distance


Much smaller capacitance can be achieved

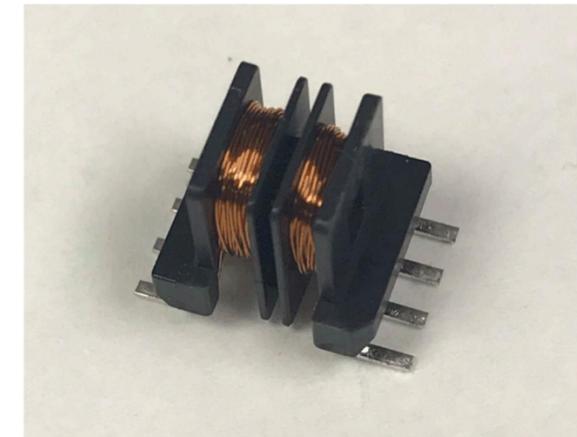


Increasing the distance reduces the capacitance while increasing the leakage inductance

How topologies respond to leakage inductance


Flyback

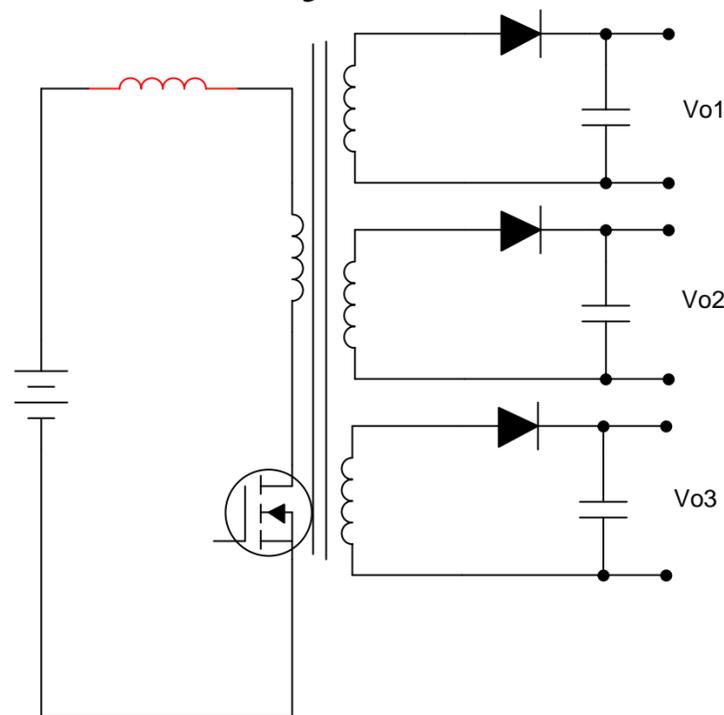

Push-pull

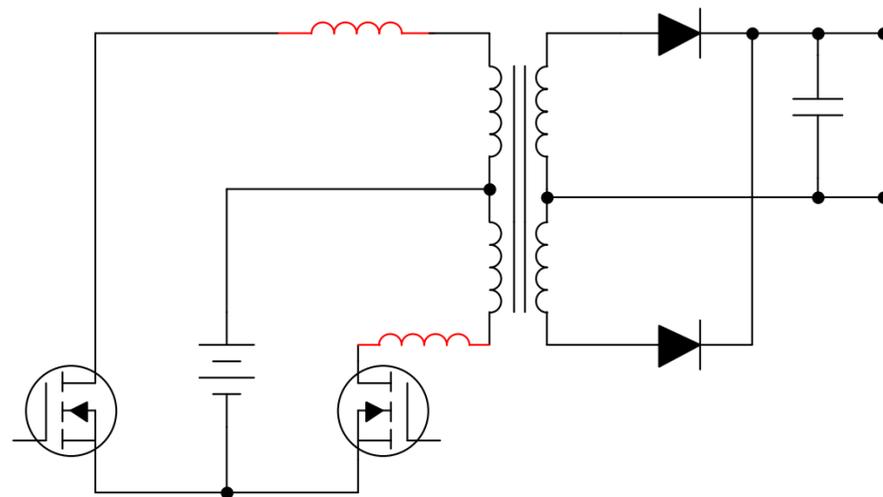


LLC

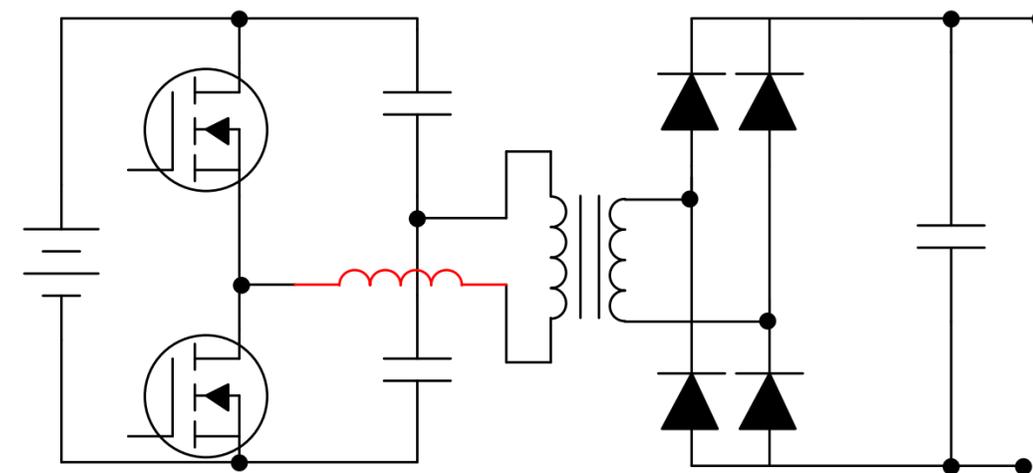

- Leakage energy can't be transferred to secondary side
- Leakage causes
 - More EMI noise due to ringing
 - More loss
 - More device stress
- Leakage needs to be minimized

- Leakage is part of resonant circuit
- Leakage energy is fully recovered
- No extra ringing caused by the leakage
- **No limitations on the leakage inductance**



LLC converter

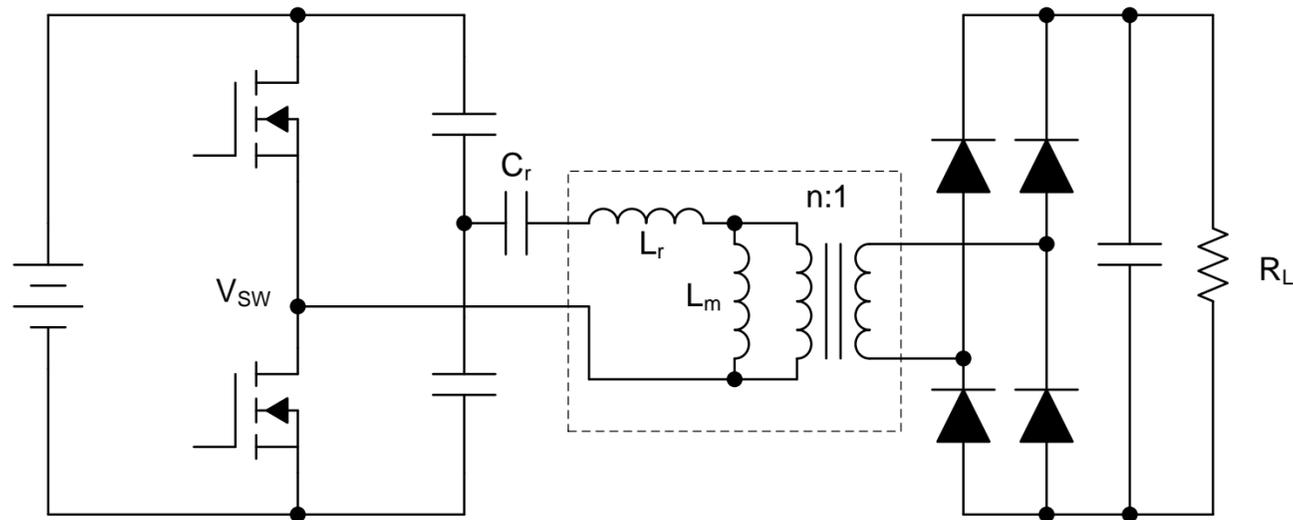

$$f_0 = \frac{1}{2\pi\sqrt{L_r C_r}}$$





$$Q_e = \frac{\sqrt{L_r/C_r}}{R_e}$$

$$R_e = \frac{8n^2}{\pi^2} R_L$$

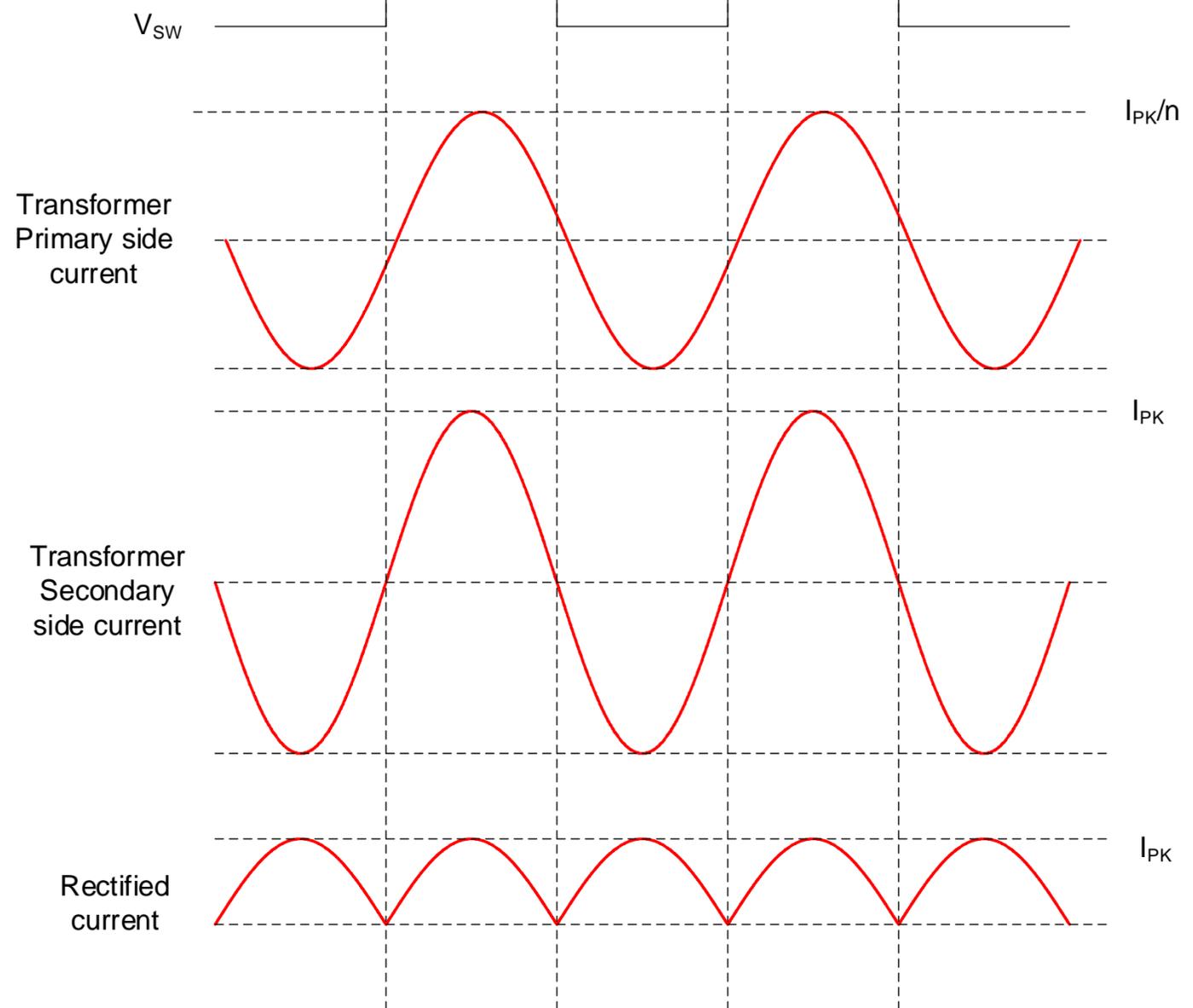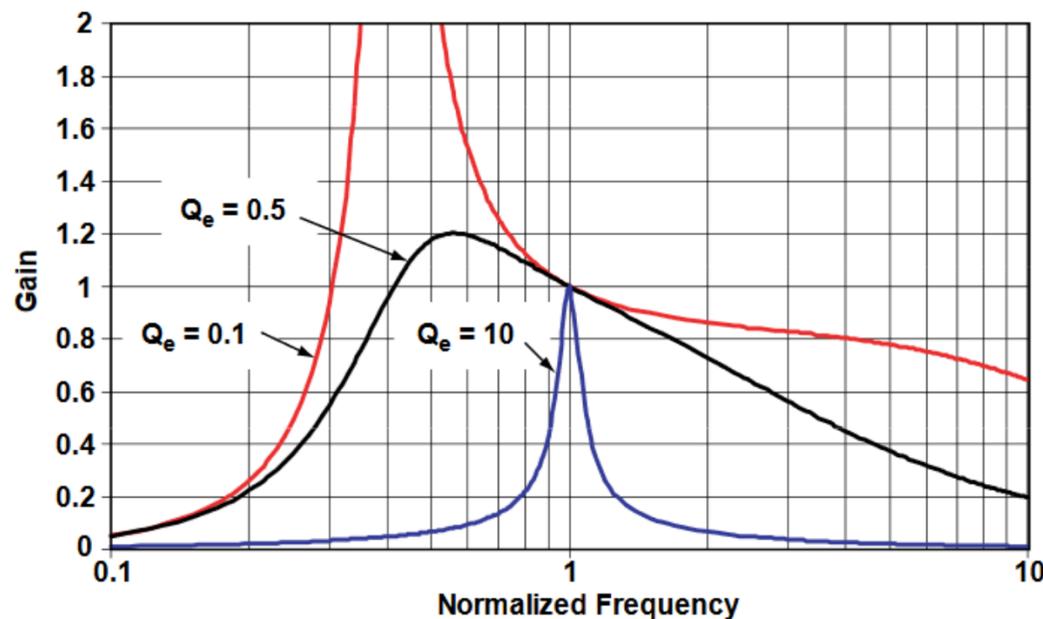


- At resonant frequency, the impedance of resonant tank is equal to zero, input and output is shorted through the transformer. Fixed frequency open-loop control is possible.
- The leakage inductance of the transformer can be used as the resonant inductor

Transformers for isolated bias supply

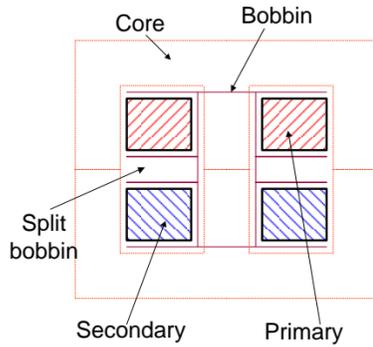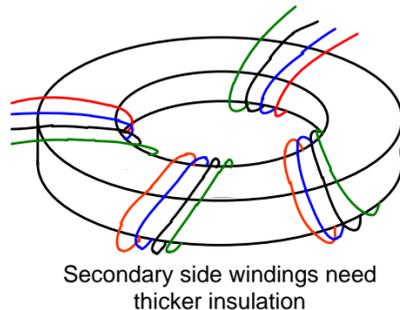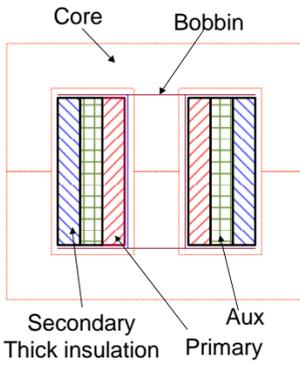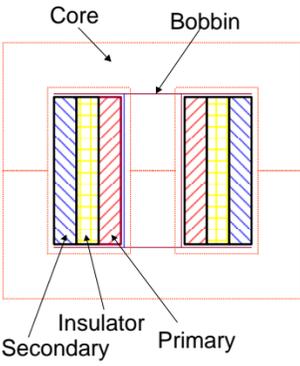	LLC transformer	Push-pull transformer	Three-winding flyback	Two-winding PSR flyback
				
$C_{Pri-Sec}$	<2pF	~10 pF	~20 pF	~20 pF
CMTI	>150V/ns	Worse than LLC	Worse than LLC	Much worse than LLC
Cost	1X	>1.15	>1.3X	>1.18X
EMI	Best	Good	Poor	Poor
Regulation	Good	Good	Better	Best

LLC converter provides an order of amplitude capacitance reduction


Open-loop LLC voltage regulation

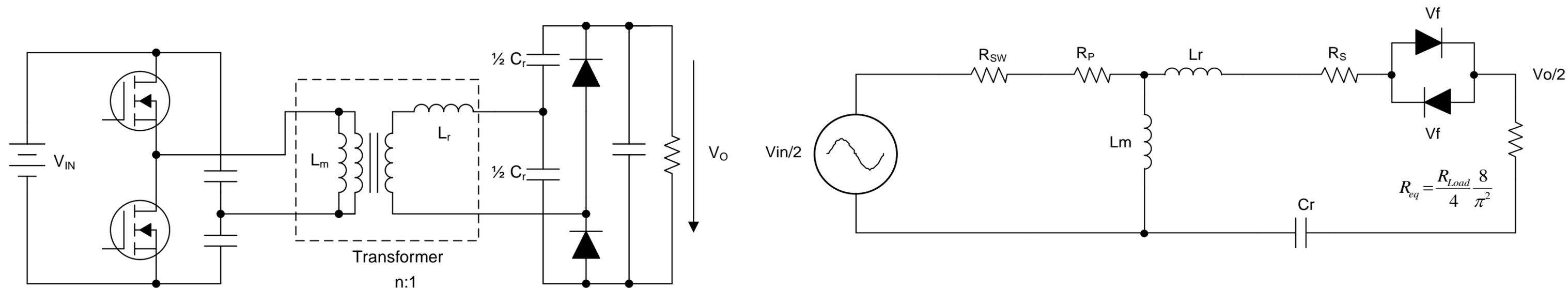

$$v_o \approx \frac{v_{in}}{n} - \frac{\pi^2}{2} \left(\frac{R_{SW}}{n^2} + \frac{R_P}{n^2} + R_S \right) \cdot I_o - 2v_f$$


- The voltage regulation is determined by transformer turns ratio and resistive loss, as well as the diode drop
- It is critical to keep the resistive loss low to get best load regulation

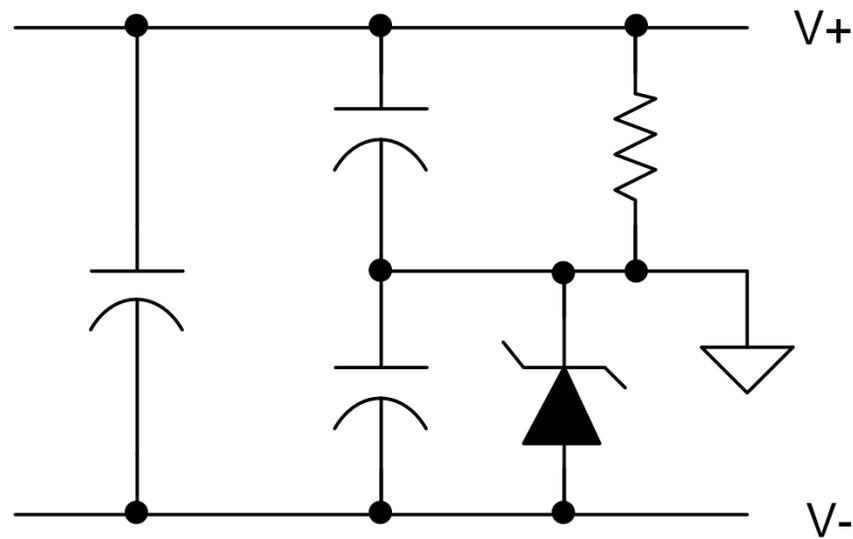Split single output voltage into dual outputs




Zener split

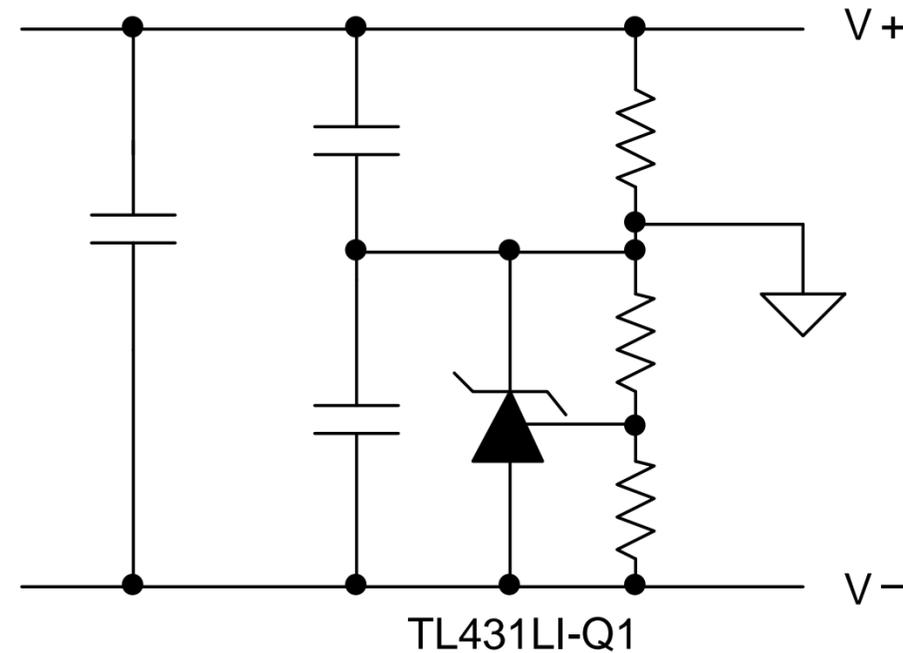- **Lowers cost**
- **Unregulated outputs**



Shunt Regulator

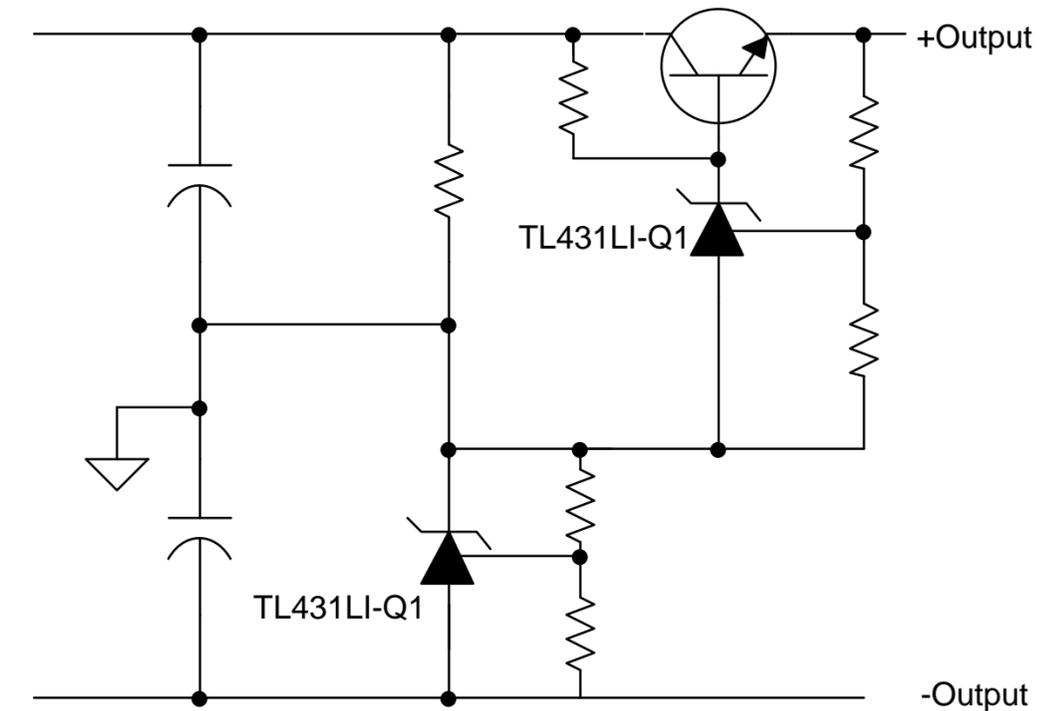- **Higher cost**
- **Regulated negative output**
- **Unregulated positive output**



Shunt Regulator & Linear regulator

- **Highest cost**
- **Regulated output**

UCC25800-Q1




Low-cost LLC transformer driver with high performance

Features

- Operation from 9 V to 34 V (40 V Abs Max)
- 6 W from 24-V input, Up to 10 W from 34-V input
- Integrated half-bridge MOSFETs
- Programmable fixed switching frequency up to 1.2 MHz
 - 1.2 MHz default, resistor settable 100 kHz – 1 MHz
 - Frequency accuracy +/-6% maximum over temperature
 - External SYNC function
- Drive multiple transformers with one UCC25800-Q1
- Automatic dead time adjustment with programmable maximum
- Integrated soft-start
- Disable pin with fault code output
- Two-level over current protection
 - Programmable via external resistor
 - UCC25800L is latched after over current
 - UCC25800R is retry after over current
- Over Temperature Protection
 - 160°C Junction
 - 10°C Hysteresis
- AEC Q100 Qualified

Benefits

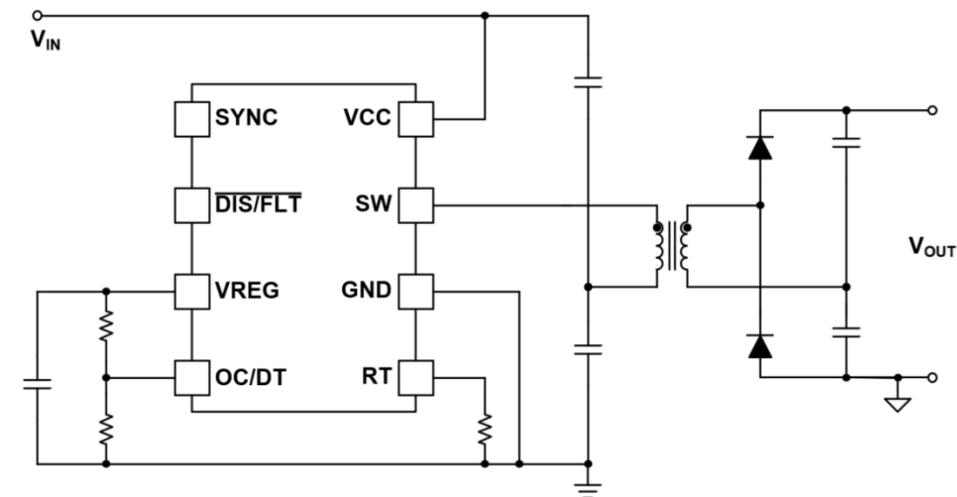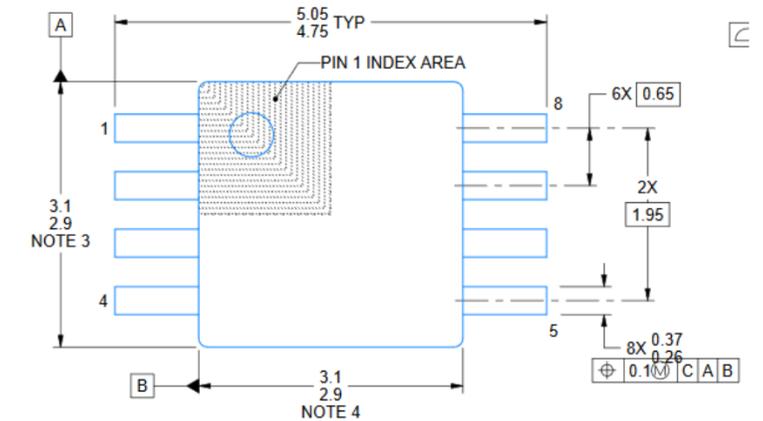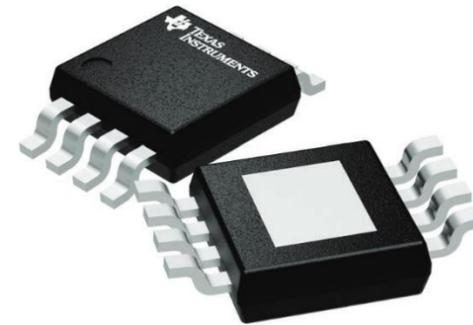- Low common mode noise due to minimal interwinding capacitance in transformer
- Simple design, highly integrated, no bootstrap capacitor
- High switching frequency for smaller size and more robustness



[Disclaimer: Specs, features & pinouts subject to change without prior notice.]

UCC25800-Q1 measurement data


UCC25800 EVM with LM5156 pre-regulator




Predictable startup of +/- rails



1% Load regulation

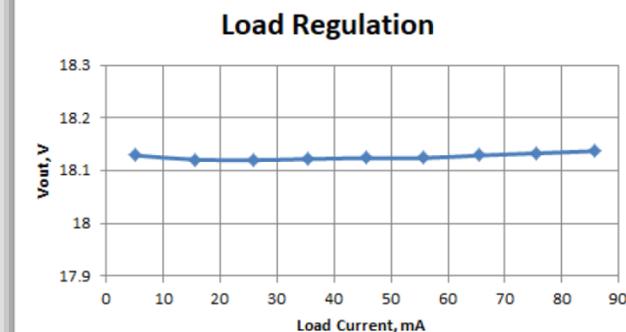


Surpasses CISPR 25 class 5 EMI standard

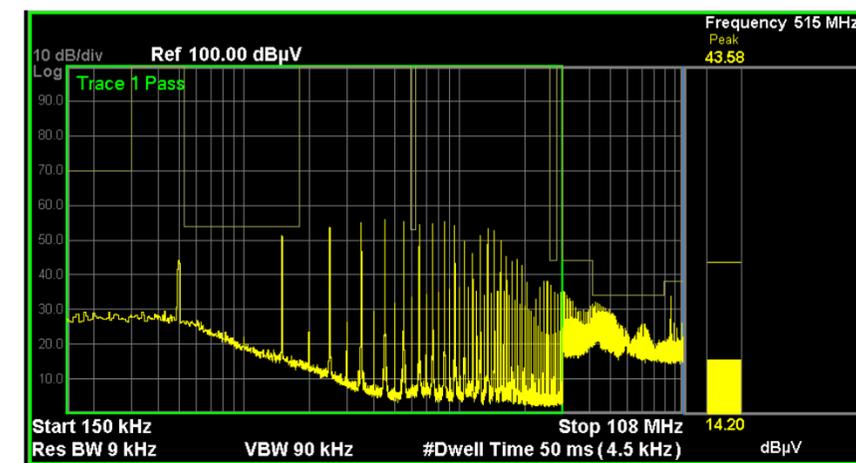


Pass - LLC Board Only with Filter

PARAMETER	SPECIFICATIONS
Input voltage range	6V – 26V
Output voltage and current	+18V / -5V
Switching frequency	2.2MHz and 500 kHz
Isolation	Yes, 2500 VAC (1 sec)
Topology	SEPIC + Open loop LLC transformer driver

EMI noise performance comparison

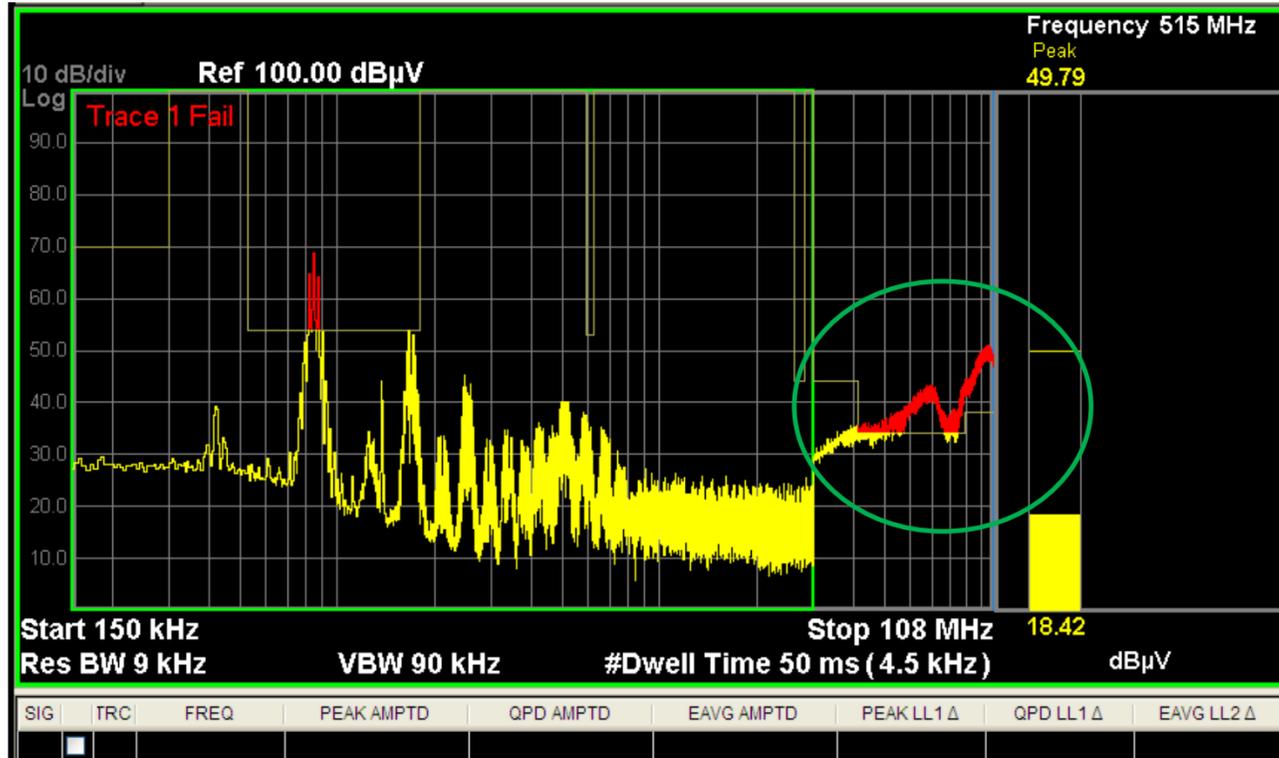


5-V push-pull

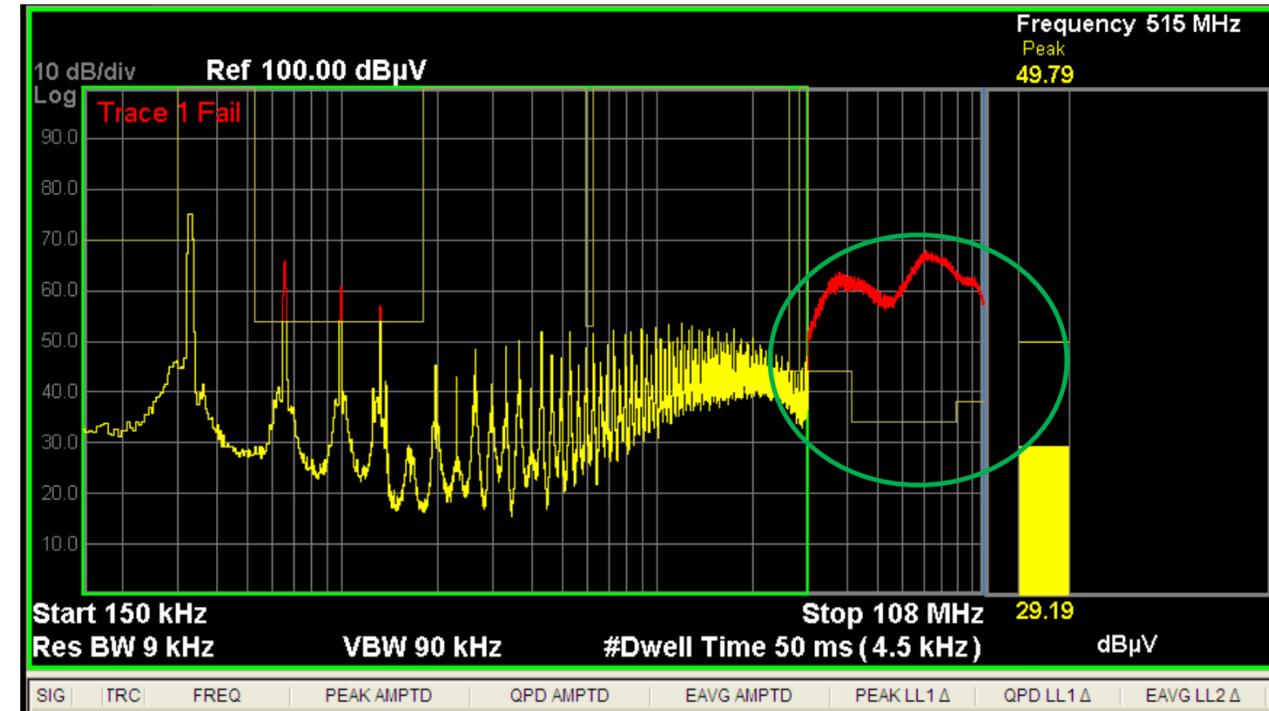

24-V Flyback


24-V LLC

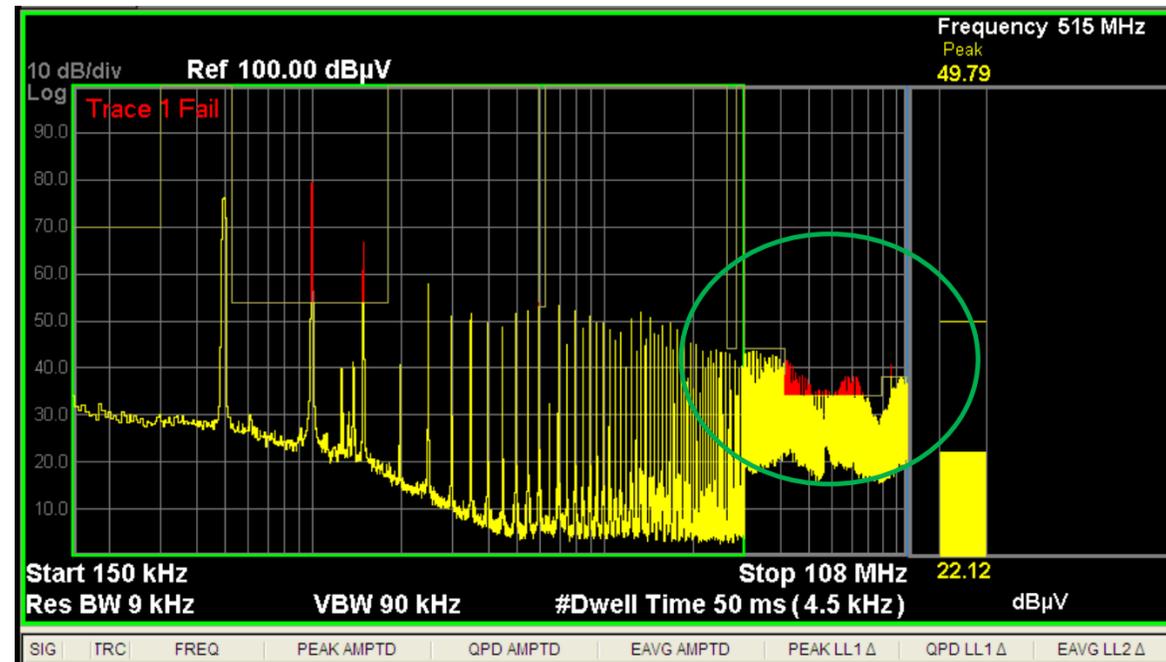


LLC has much lower high frequency EMI noise, which is the most difficult to filter out

*No EMI filter added on any topologies

CMTI performance of UCC25800 based LLC

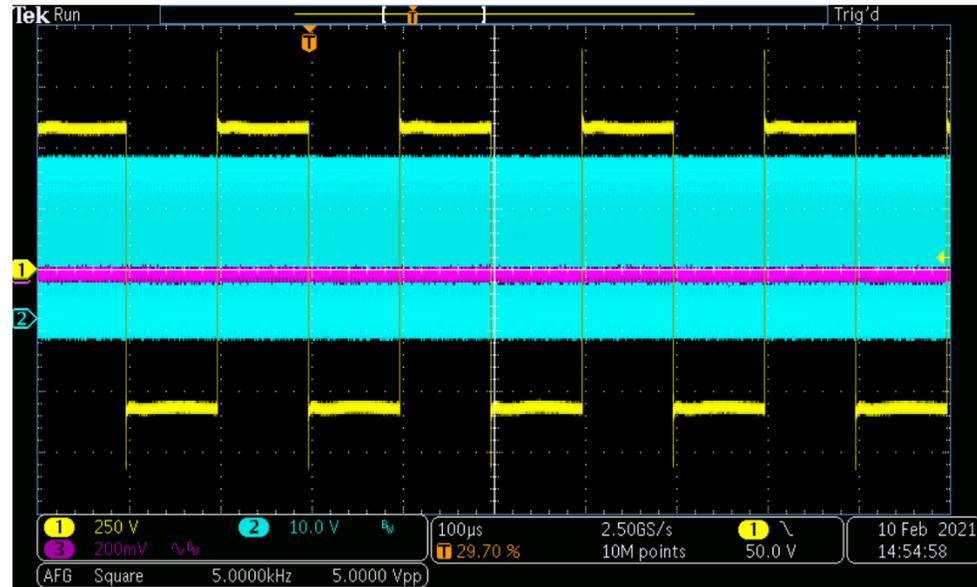

165 V/ns

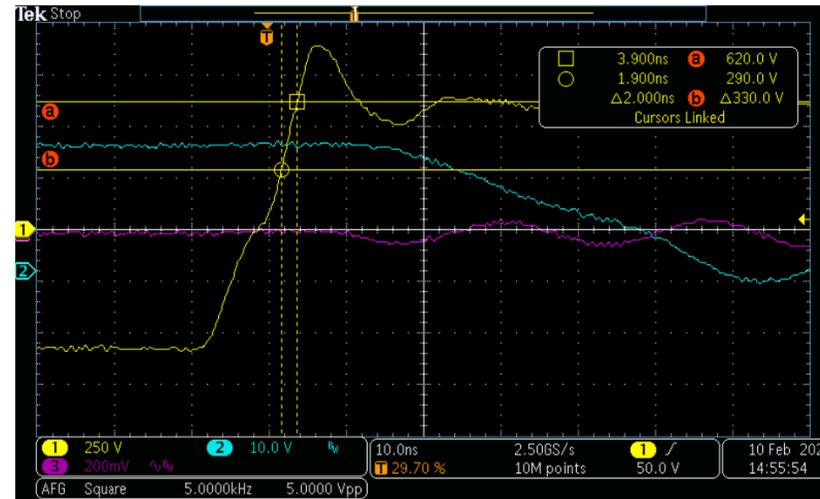


155 V/ns




Switch node

Strike voltage

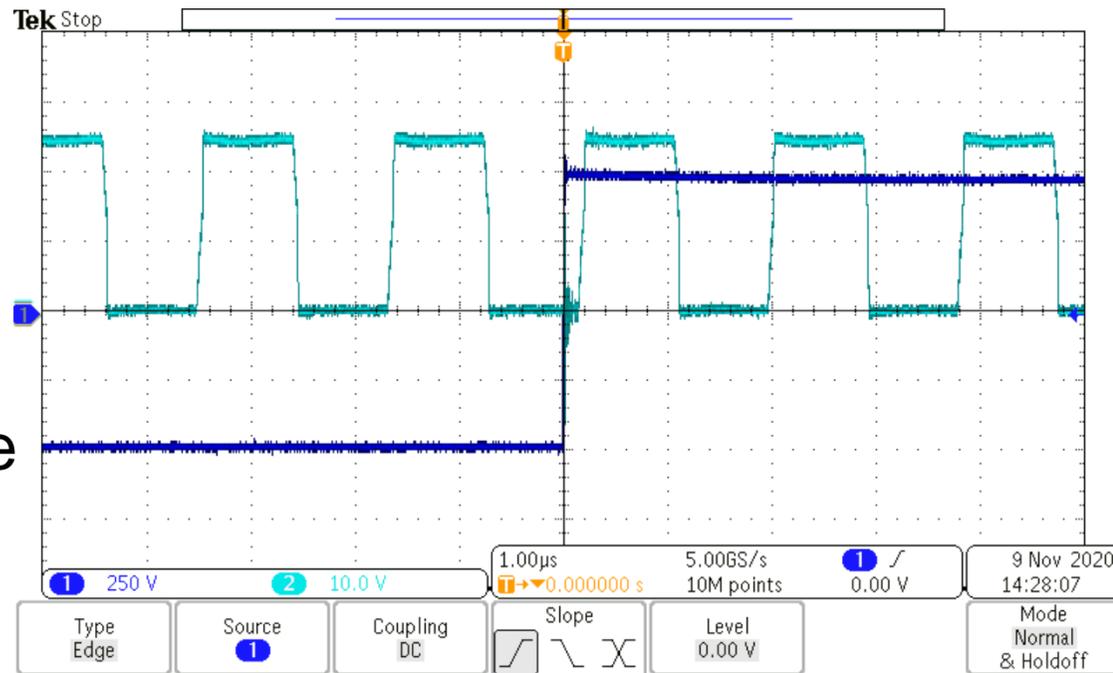

Switch node


Strike voltage

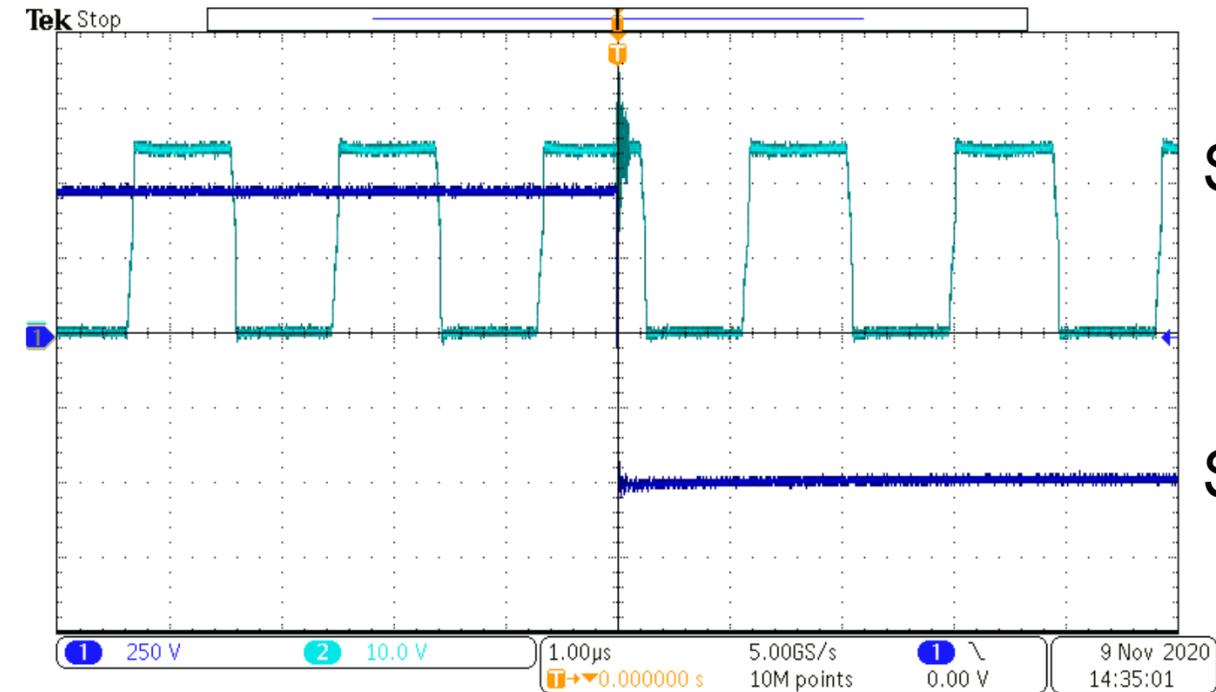

Operation is not affected by >150 V/ns CMTI

Transformer design considerations

- Transformer design is simple
 - Two windings
 - Turns ratio is roughly the voltage ratio between the input and output voltage (plus the diode drop)
 - Square voltage on primary side, setting up the volt-second rating
 - Lowest R_{ac} possible
 - No airgap
- Once the transformer is made, measure the leakage inductance from secondary side
 - Short the primary side while measuring
- Match the leakage inductance with resonant capacitor


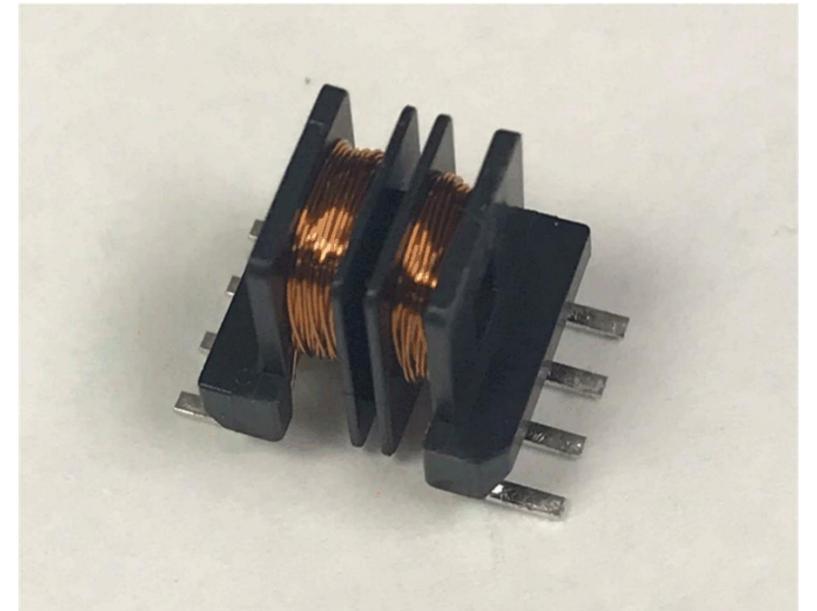


Part number (Würth)	Turn ratio	Leakage inductance	Input / Output
750319331	1:1	1.4 μH	24 V/24 V
750319177	1.67:1	1.48 μH	15 V/24 V
750319177	1:1.67	0.53 μH	24 V/15 V

How to further simplify the design




UCC25800-Q1 based open-loop LLC

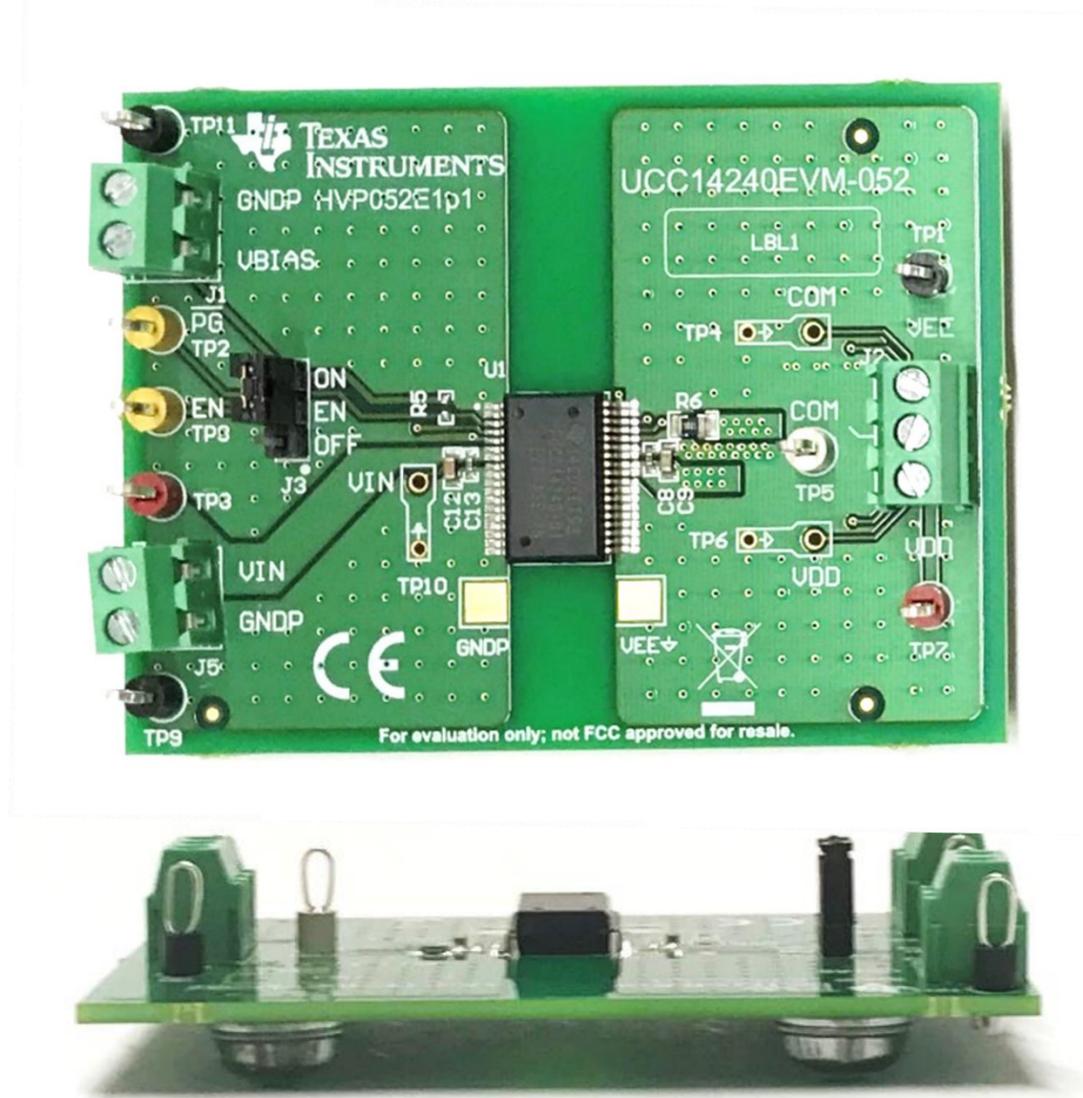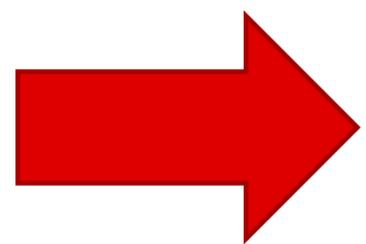

UCC14240-Q1
1.5-W, high-efficiency, 3-kVRMS isolated
DC/DC converter


Gate driver voltage accuracy requirement

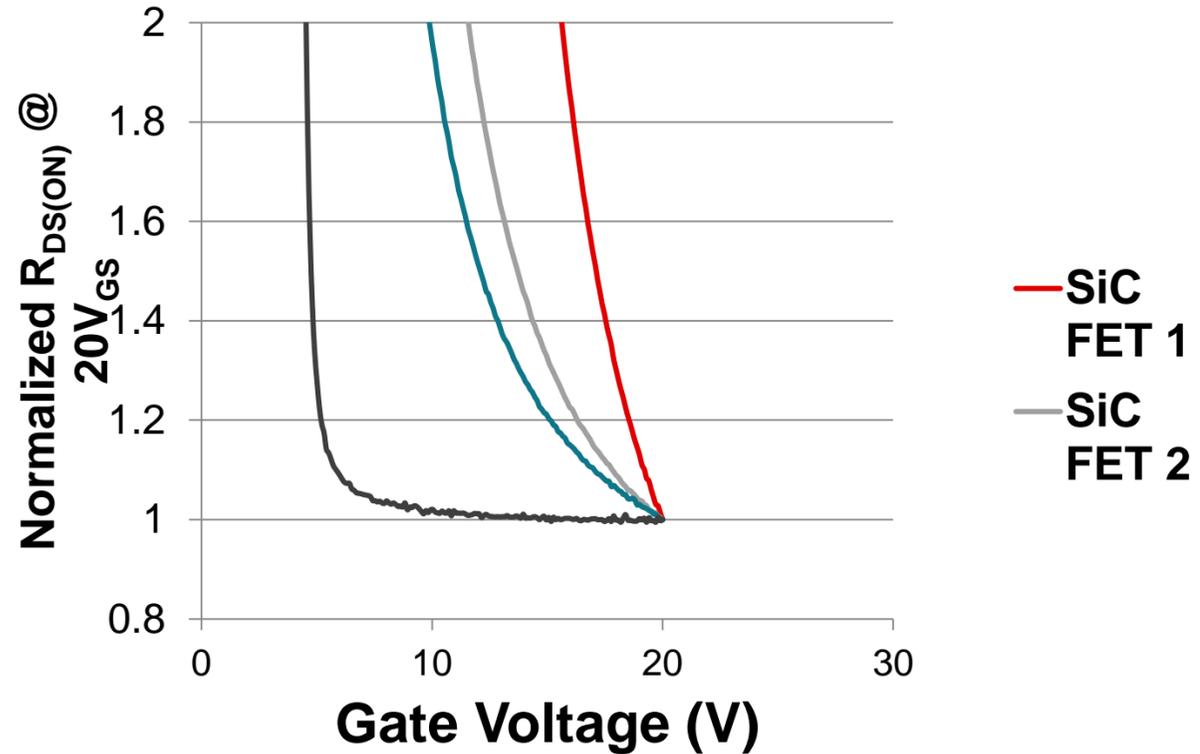Gate voltage effect on $R_{DS(ON)}$ sensitivity




$$\text{Conduction Loss} = I_{RMS}^2 \times R_{DS(ON)}$$

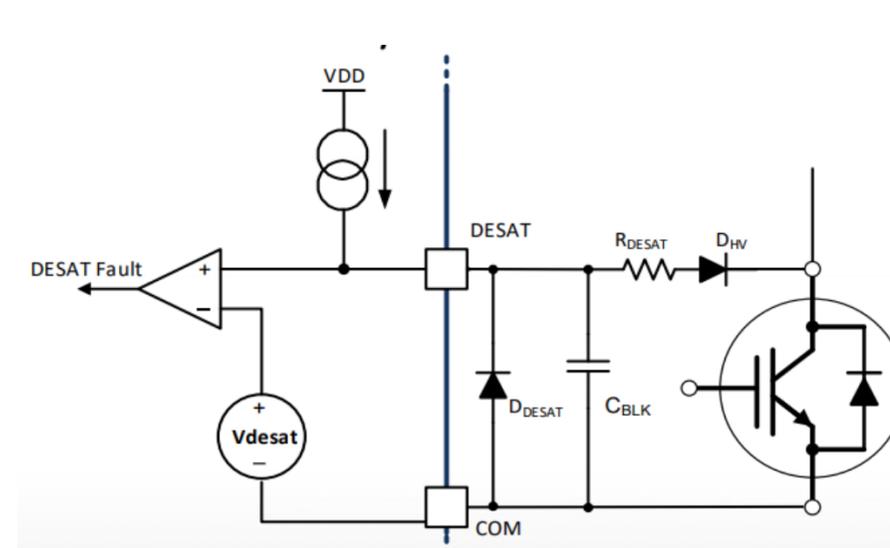Gate voltage effect on over-current detection



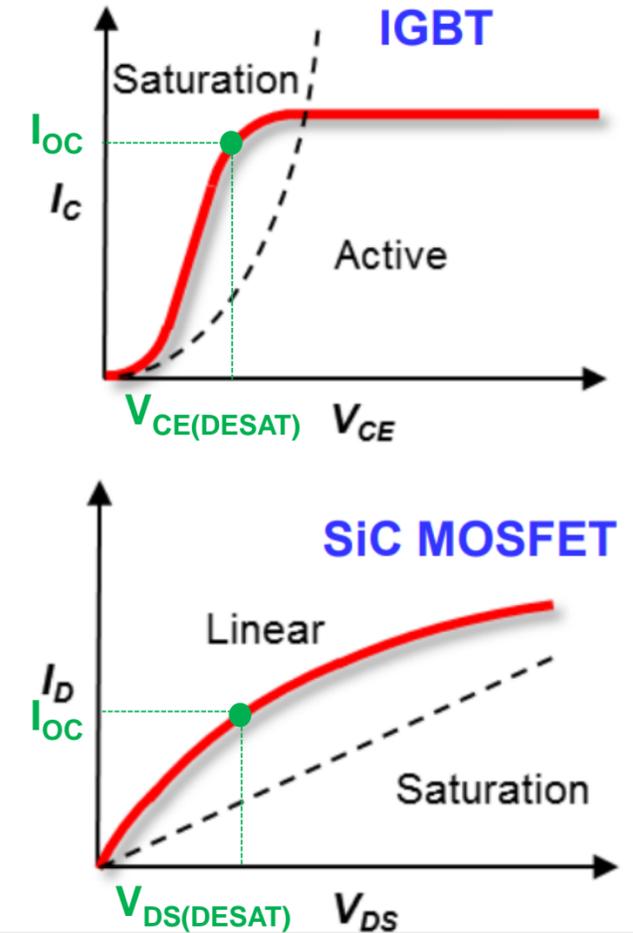V_{GS} change affects I_{OC} correlation with $V_{CE(DESAT)}$ or $V_{DS(DESAT)}$ setting



	Si MOSFET	SiC MOSFET	IGBT
Positive rail (V_P)	+12V, +15V	+18V, +20V (5%, 3%, 1%)	+15V, +18V
Negative rail (V_N)	0V	-5V, -4V, -3V	-8V or 0V



Tight bias voltage regulation improves efficiency and OCP accuracy

Isolated DC-DC module with integrated transformer

Technology shift for isolated gate driver bias supplies


Decades of **bulky transformers** ...

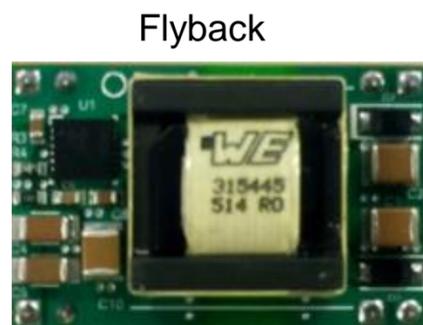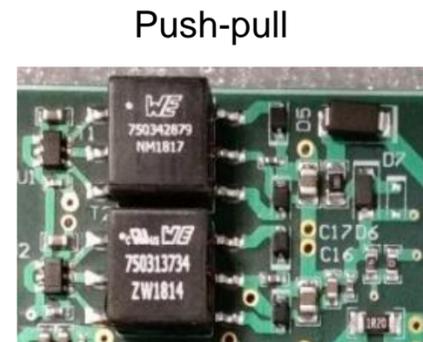- Bulky – prone to vibrations
- High radiated EMI
- Large footprint & height
- Difficult to design




Introducing the **UCC14240-Q1**

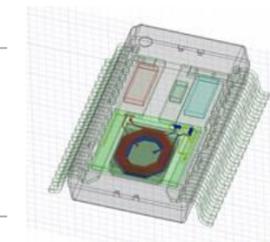- 1.5W high-efficiency isolated DC/DC power supply
- Industry's smallest, most accurate & easiest-to-use
- Proprietary integrated transformer technology
- No bulky, noisy transformers




2X smaller PCB area, lower BoM

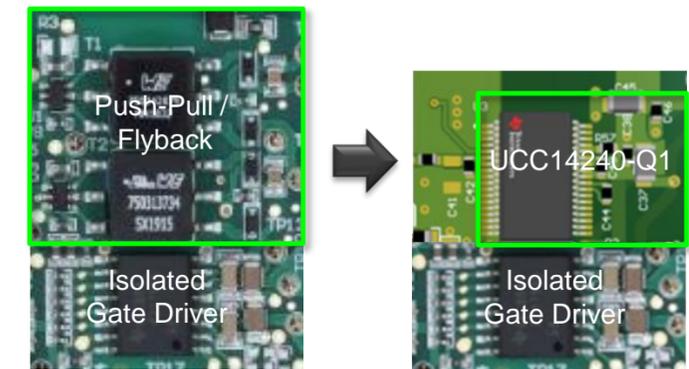

2X lower height

7.5mm Height

3.5mm Height

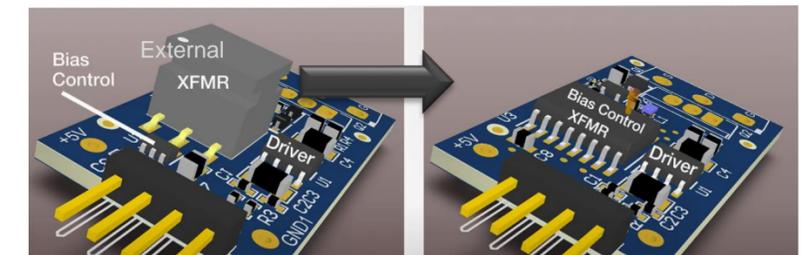


TI integrated gate drive bias supply

Can be configured as two outputs or single output

Two Outputs: $V_{POSITIVE}$ & $V_{NEGATIVE}$

VIN = 24 V or 12 V

VOUT = Both Adjustable
<1.3% accuracy

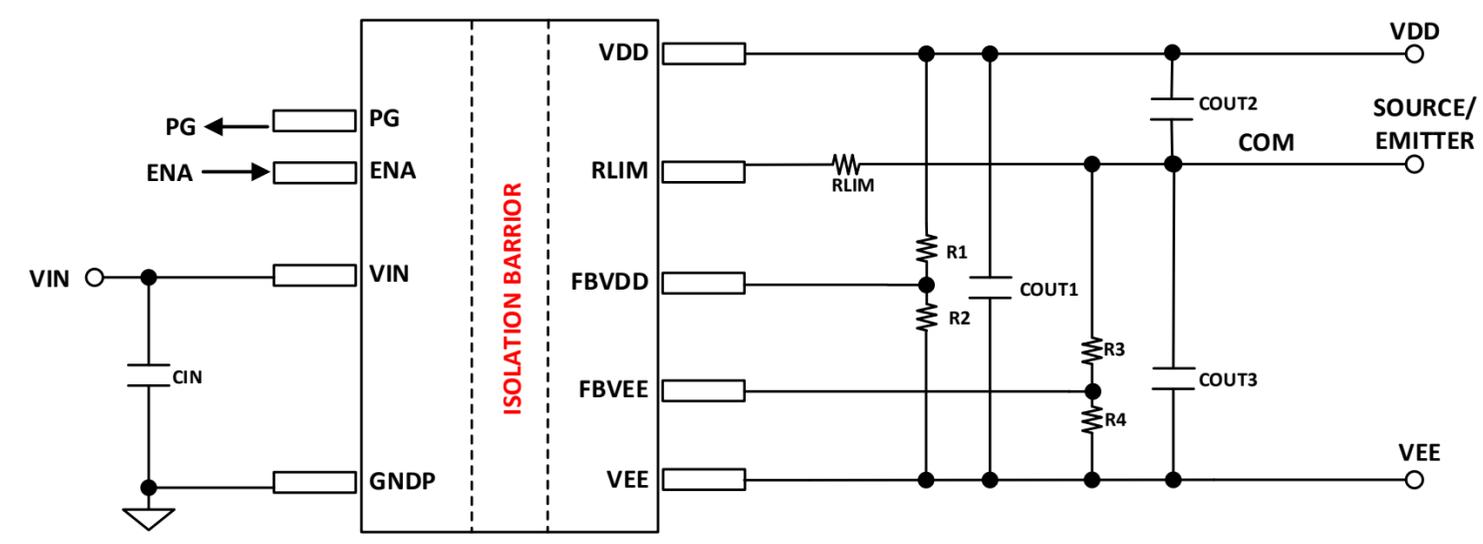


- Higher inverter efficiency
- More accurate inverter current limit

Single Output: $V_{POSITIVE}$

VIN = 24 V or 12 V

VOUT = Adjustable
<1.3% accuracy

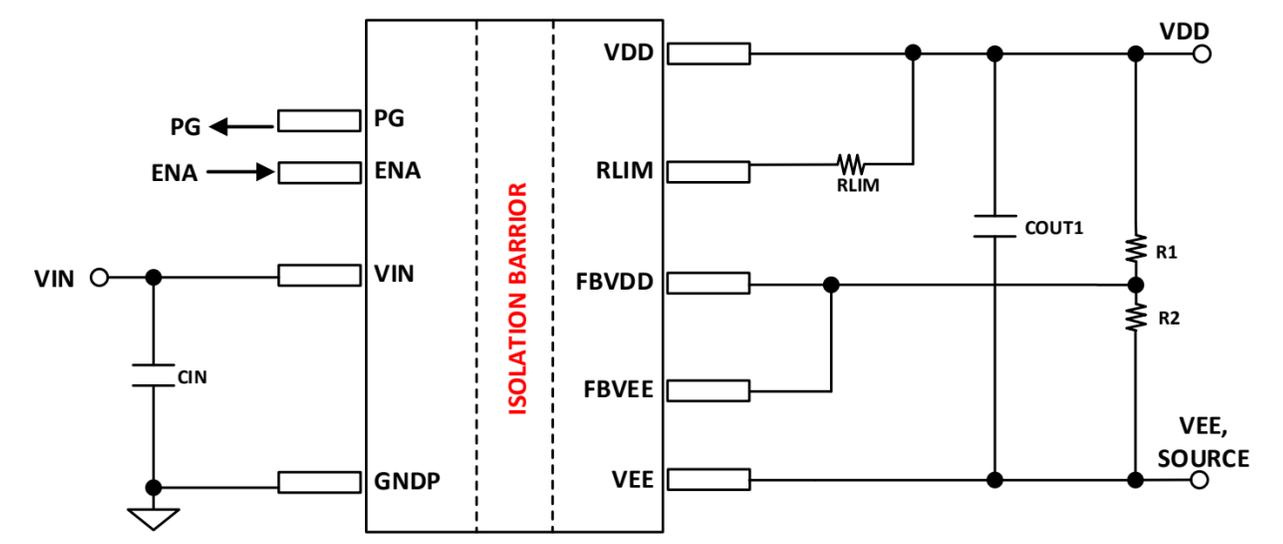

- Higher inverter efficiency
- More accurate inverter current limit

[Link to datasheet](#)

[Link to EVM](#)




[Order Soon](#)


[Disclaimer: Specs, features & pinouts subject to change without prior notice.]

UCC14240-Q1 Best-in-class regulation

Compact PCB Implementation

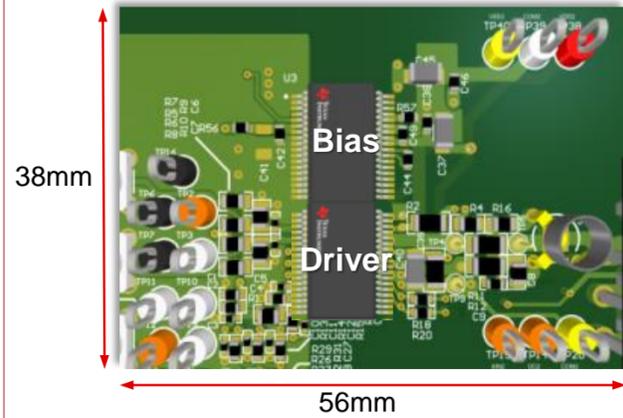

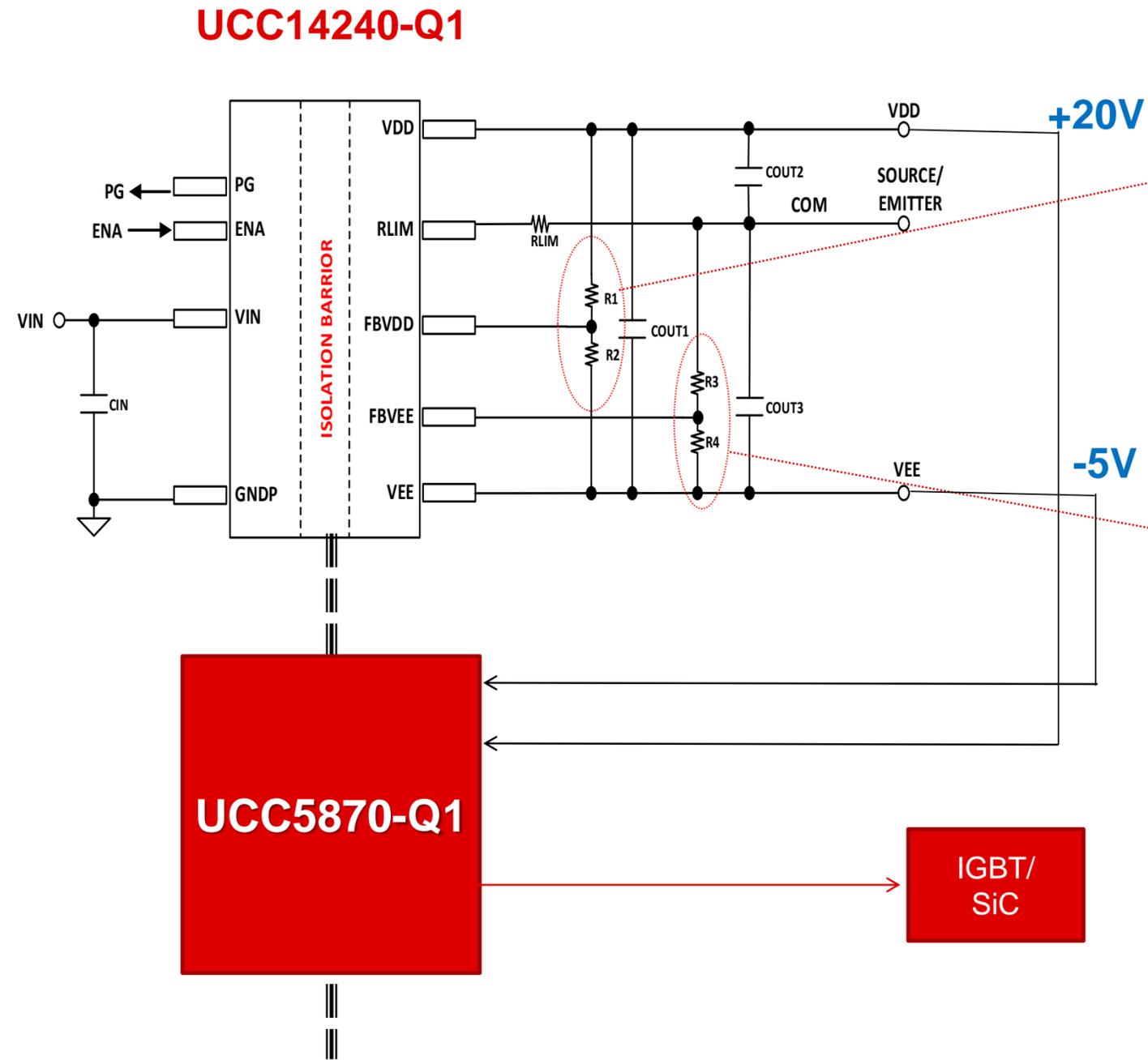- 1.3% regulation over -40°C to 150°C
- No need post regulator
- Programmable positive and negative rail outputs



R1 & R2 control the $V_{out\Delta}$ (18-25V)

R3 & R4 control the negative and the positive voltages

UCC14240-Q1



3.55 mm height dual output gate drive bias w/ integrated XFMR

Features

- Isolated power module with integrated transformer
- 3.55 mm height, 12.8 mm x 10.3 mm with leads (8mm creepage)
- 1.5-W output power at $T_a = 105^\circ\text{C}$
- Input voltage range
 - 24V nominal
 - 21V – 27V, 32V Abs,max
- Dual adjustable output voltages
 - VDD to VEE Range 18 V to 25 V, $\leq 1.3\%$ accuracy
 - COM to VEE Range 2.5 V to VDD, $\leq 1.3\%$ accuracy
 - $\leq 1.3\%$ Accuracy -40°C to 150°C
- Isolated DCDC for driving: IGBTs, SiC FETs, Si FETs, sys rails
- 3.5pF primary-to-secondary capacitance with low emissions
- Wide temperature range:
 - T_j : -40 to 150°C
 - T_a : -40 to 125°C
- UVLO, OVLO, PG, soft-start, short-circuit, power-Limit, and over temperature protection, CMTI > 150kV/us
- Basic isolation
 - 3kVrms (60s)
 - 1.2kVpk working
 - 5kV surge
- AEC-Q100 auto grade



Benefits

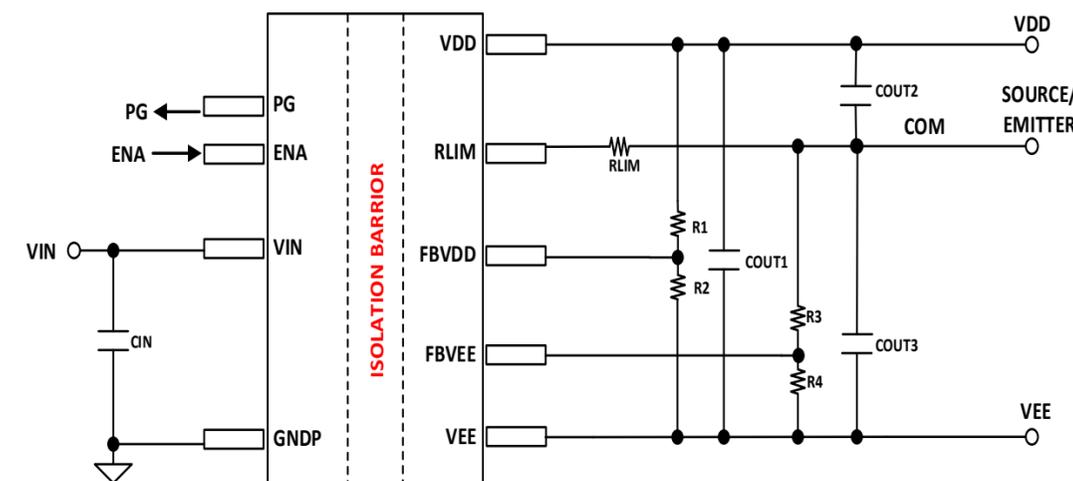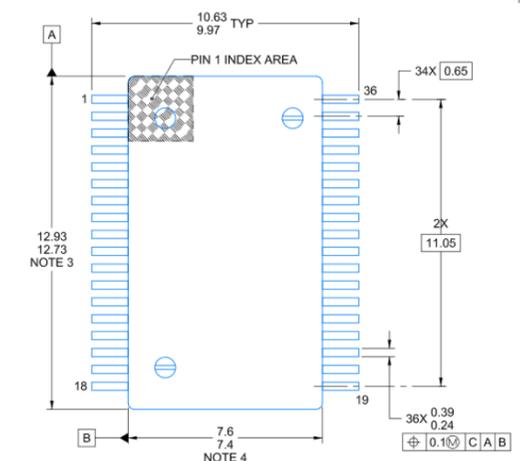- Integrated solution enables smaller BOM, reduced board space and helps with easier system certification
- High accuracy to reduce size of IGBTs / SiC switches
- Soft start enables minimal overshoot current,
- Low EMI, high CMTI, high isolation voltage



[Disclaimer: Specs, features & pinouts subject to change without prior notice.]


UCC14240-Q1 total solution comparison

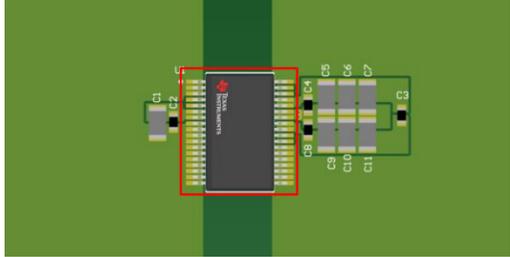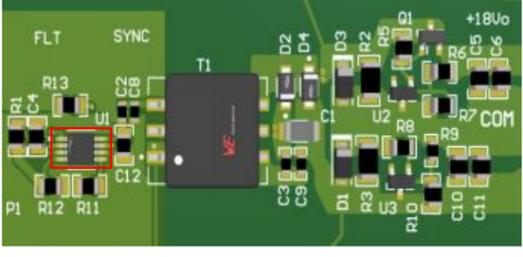	Integrated Transformer UCC14240	LLC Resonant UCC25800	Push-Pull SN6505	Flyback LM(2)5180	Half Bridge UCC28C42-Q1
	 <p>UCC14240 Product Folder</p>	 <p>UCC25800 Product Folder</p>	 <p>SN6505B Product Folder</p>	 <p>LM25180 Product Folder UCC2813 Product Folder</p>	
Total PCB Area	220 mm ²	525 mm ²	550 mm ²	600 mm ²	560 mm ²
Maximum Height	3.55 mm	9 mm	8 mm	13 mm	10 mm
Vin / Power	21V – 27V 1.5W at 105°C (Distributed Architecture)	9V – 34V < 10W (Centralized Architecture)	2.25V – 5.5V < 5W	4.5V – 65V > 10W	Controller >10W
Cpri-sec	3.5pF	< 1.5pF	7pF	~20pF	~20pF


UCC14240-Q1 measurement data

UCC14240 EVM

SMALL
AREA

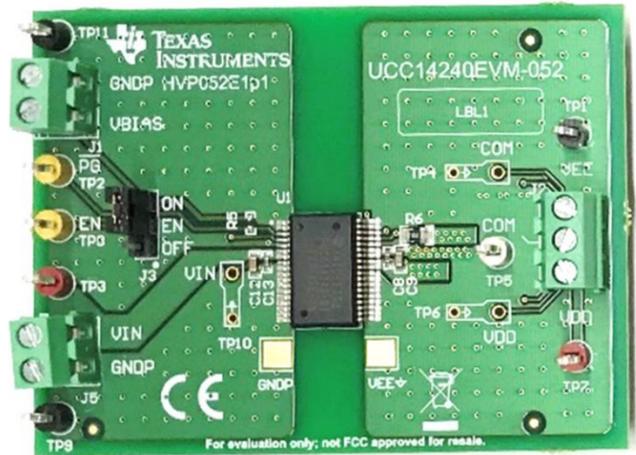

LOW
HEIGHT

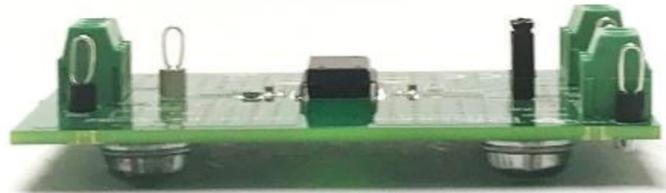


PARAMETER	SPECIFICATIONS
Input voltage range	21 V – 27 V
Dual Output voltage	+25 V / -5 V (programmable)
Regulation	≤ 1.3% accuracy
Isolation	Basic, 3k Vrms


Soft startup of +/- rails




< 1% load regulation

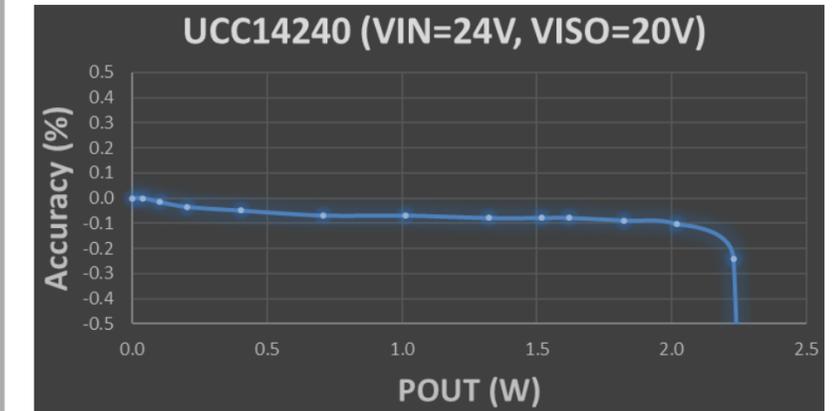

60% peak efficiency

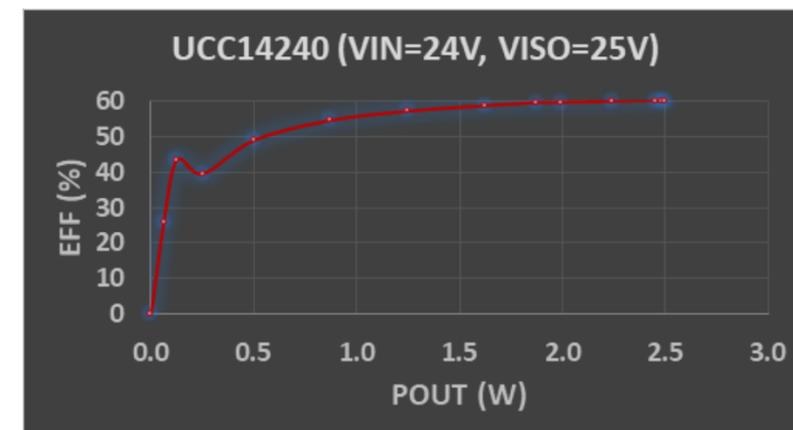

Cool 2-W out

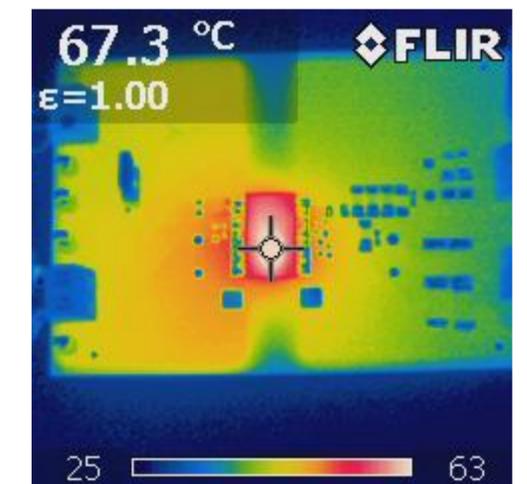

Summary

- Isolated bias supply is needed for biasing the isolated gate drivers in the inverters
- The open loop LLC converter provides a simple, robust solution
 - Less EMI
 - High CMTI
 - Good voltage regulation
 - Multiple output capability
- Integrated transformer solution provides
 - Highest level of integration, minimum external components
 - Highest power density, lowest profile
 - Best-in-class regulation, no post regulator needed



© Copyright 2021 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated