

AN-1227 LM3485 Evaluation Board

1 Introduction

The LM3485 is a hysteretic P-FET buck controller that uses a pulse-frequency modulation (PFM) scheme to regulate the output voltage. This LM3485 demo board and the recommended components are intended to demonstrate the performance with a 3.3 V output from a 12 V source. The demo board can be used with source voltages from 7 V to 28 V to deliver output load currents up to 1A. By changing the size of a single resistor, regulated output voltages from 1.242 V to 5 V can be obtained.

The circuit schematic is shown in [Figure 1](#) and the bill of materials is given in [Table 1](#).


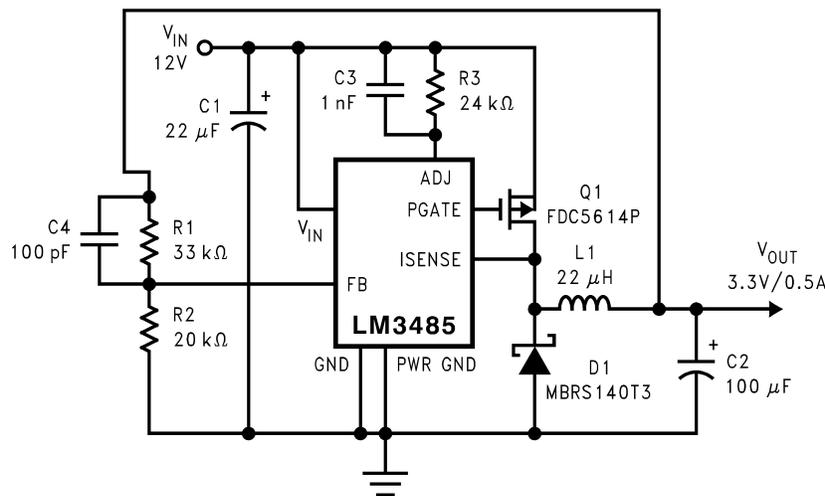


Figure 1. Regulator With 3.3 V Output at 0.5A

Table 1. Bill of Materials (BOM)

Code	Description	Manufacturer
C1	Input Capacitor CAP-Tantalum 22 µF 35 V EEJL1VD226R	Panasonic
C2	Output Capacitor CAP-POSCAP 100 µF 6.3 V 6TPC100M	Sanyo
C3	C _{ADJ} CAP-Ceramic Chip 1nF 50 V GRM39X7R102K50	Murata
C4	C _# CAP-Ceramic Chip 100pF 50 V GRM39X7R101K50	Murata
D1	Catch Diode Schottky Diode 1A 30 V MBR5130T3	On Semiconductor
L1	Inductor 22 µH LQH66SN220M01L	Murata
Q1	P-channel MOSFET -60 V FDC5614P	Fairchild
R1	Feedback high side resistor Chip Resistor 33 KΩ MCR10EZHF3302	Rohm
R2	Feedback low side resistor Chip Resistor 20 KΩ MCR10EZHF2002	Rohm
R3	R _{ADJ} Chip Resistor 24KΩ MCR10EZHF2402	Rohm
U1	Buck Controller LM3485	Texas Instruments

2 Output Voltage Current Limit Setting

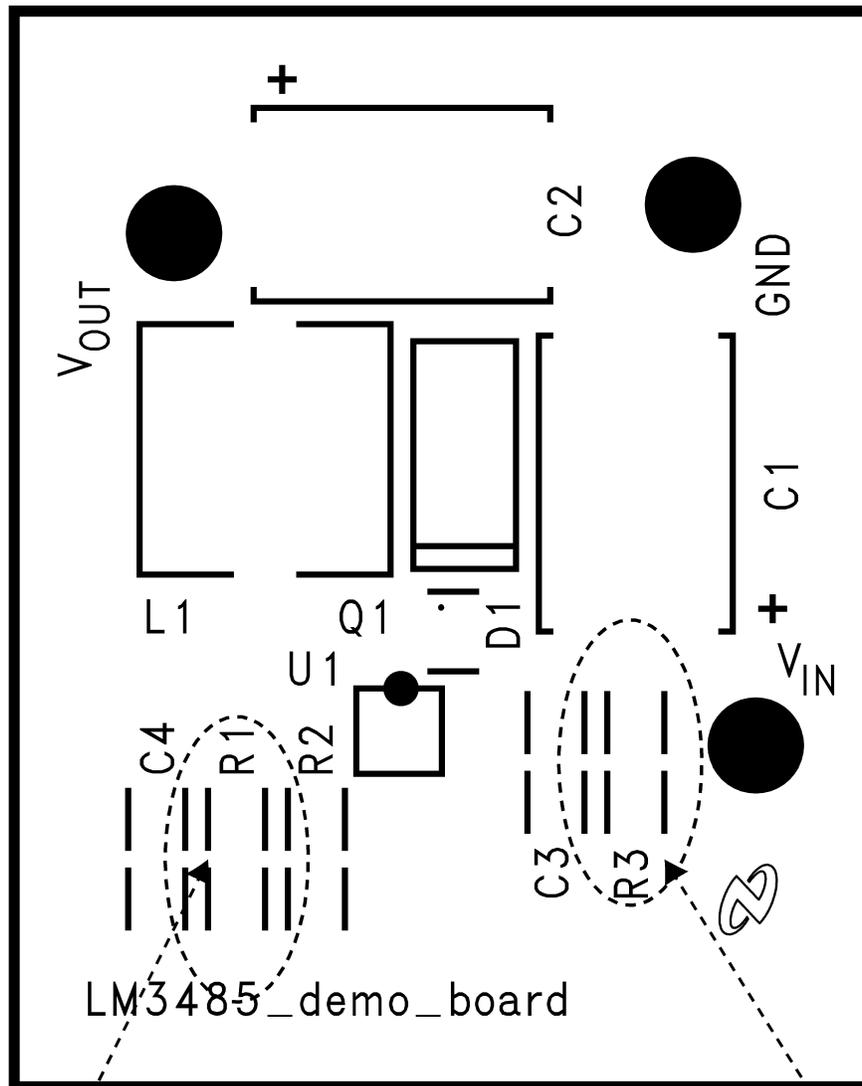

Output Voltage setting

Find the value of R1 by:

$$R1 = (V_{OUT}/1.242 - 1) \times 20k$$

For 1.242V minimum output voltage, the output node is connected to the FB pin directly. Delete R2 and C4 and replace R1 with a short circuit.

Current Limit setting

Find the value of R3 by:

$$R3 = (R_{DS(on)} \times I_{ind_peak})/I_{CL}$$

Figure 2. Component Location (Top Side)

3 Layout Fundamentals

The LM3485 can work in a wide range of applications. For your application circuit, proper layout for the buck regulator should be implemented by following a few simple guidelines.

1. Place the power components, which are the MOSFET, diode, inductor and filter capacitors, close together. Make the traces between them as short and as wide as possible.
2. Place the trace for the Gate of the external PFET as close as possible to the PGATE pin of the LM3485.
3. Separate any noise sensitive traces, primarily in the voltage feedback path, from noise source traces associated with the inductor.
4. Keep the trace short between the ground pin of the input capacitor and the anode of the diode.
5. Ensure the ground is low impedance.

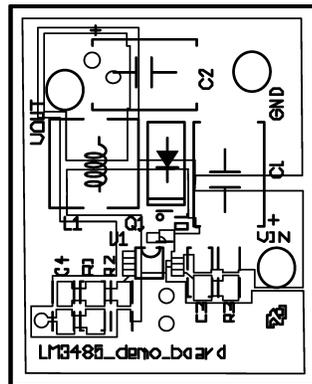


Figure 3. Top Layer

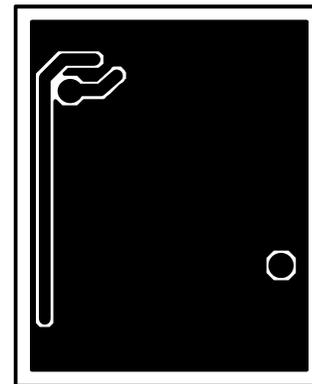


Figure 4. Bottom Layer

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com