

# AN-2169 LMZ10501 and LMZ10500 SIMPLE SWITCHER® Nano Module Low Output Ripple Designs

---

## ABSTRACT

The LMZ10501 and LMZ10500 SIMPLE SWITCHER nano modules are easy-to-use DC-DC solutions optimized for space-constrained applications. The LMZ10501 is capable of driving up to 1A load with excellent power conversion efficiency, line and load regulation. The LMZ10500 is a 650mA version module and is pin-to-pin compatible with the LMZ10501.

## Contents

1	Introduction .....	2
2	Board Specifications .....	2
3	Low Output Ripple Options .....	2
	3.1 Output Ripple Option A .....	3
	3.2 Output Ripple Option B .....	4
	3.3 Output Ripple Option C .....	5
4	Tips and Tricks for Output Ripple Measurements .....	6

## List of Figures

1	Schematic for Design A .....	3
2	Output Voltage Ripple Design A $V_{IN} = 5V$ , $I_{OUT} = 1A$ .....	4
3	Schematic for Design B .....	4
4	Output Voltage Ripple Design B $V_{IN} = 5V$ , $I_{OUT} = 1A$ .....	5
5	Schematic for Design C .....	5
6	Output Voltage Ripple Design C $V_{IN} = 5V$ , $I_{OUT} = 1A$ .....	6
7	Oscilloscope 10X Probe .....	6
8	Custom 1X Low Noise Probe Diagram.....	7
9	Custom 1X Low Noise Probe Picture .....	7

## List of Tables

1	LMZ10501 and LMZ10500 Bill of Materials (BOM), $V_{IN} = 2.7V$ to $5.5V$ , $V_{OUT} = 1.8V$ , $I_{OUT (MAX)} = 1000mA$ / $650mA$ .....	3
2	LMZ10501 and LMZ10500 Bill of Materials (BOM), $V_{IN} = 2.7V$ to $5.5V$ , $V_{OUT} = 1.8V$ , $I_{OUT (MAX)} = 1000mA$ / $650mA$ .....	4
3	LMZ10501 and LMZ10500 Bill of Materials (BOM), $V_{IN} = 2.7V$ to $5.5V$ , $V_{OUT} = 1.8V$ , $I_{OUT (MAX)} = 1000mA$ / $650mA$ .....	5

SIMPLE SWITCHER is a registered trademark of Texas Instruments.  
All other trademarks are the property of their respective owners.




## 1 Introduction


The LMZ10501 and LMZ10500 can deliver output voltage with exceptionally low output ripple. This application report demonstrates how to achieve output voltage ripple in the 4mV – 10mV pk-pk range. There are three different configurations that can be used, based on the application's ripple requirements: [Section 3.1](#) is the default evaluation board configuration with 10mV pk-pk ripple, [Section 3.2](#) achieves 6mV pk-pk of ripple, and [Section 3.3](#) demonstrates ripple configuration at 4mV pk-pk. In addition, this document provides several tips and tricks on how to measure small amplitude ripple on a typical lab bench.

## 2 Board Specifications

- $V_{IN} = 2.7V$  to  $5.5V$
- $V_{OUT} = 1.8V$
- 1A max load
- 2MHz switching frequency
- 4 layers PCB with 1oz copper
- 4.3 x 4.3 cm (1700 x 1700 mil) PCB size

## 3 Low Output Ripple Options

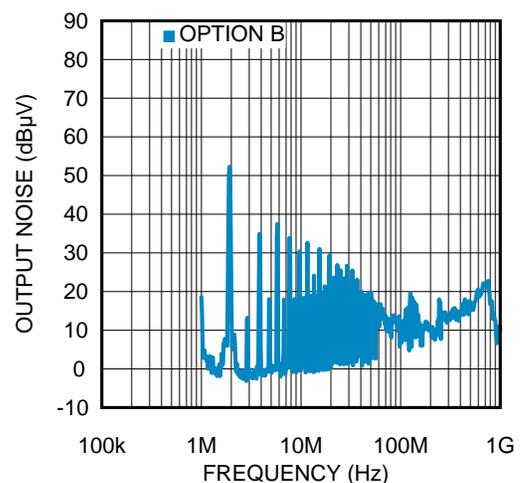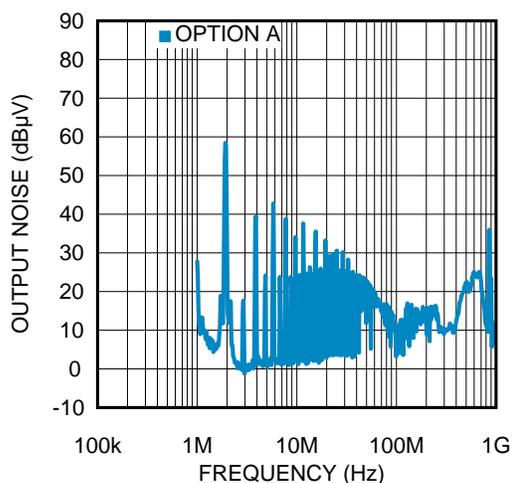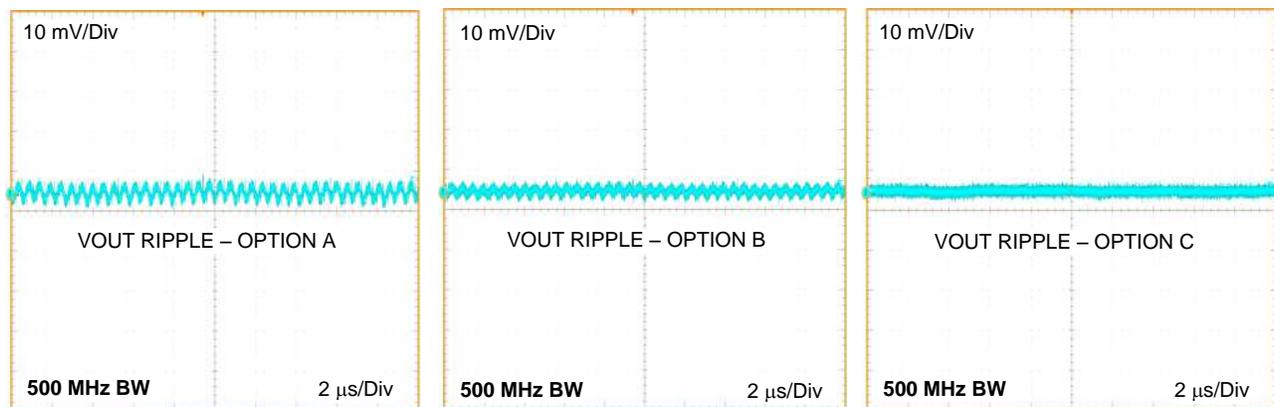

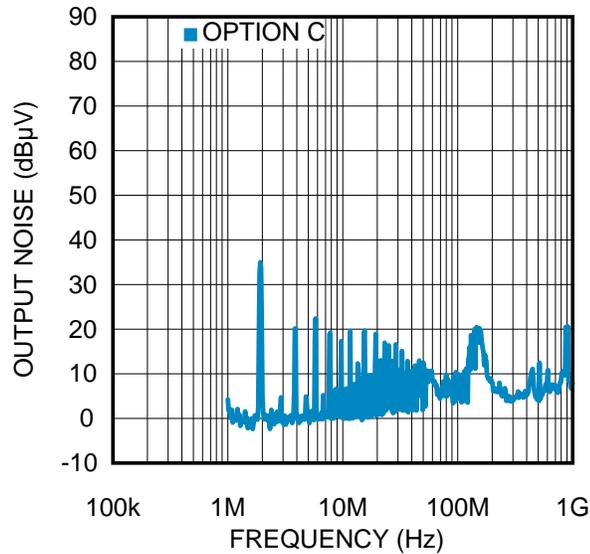

### 3.1 Output Ripple Option A


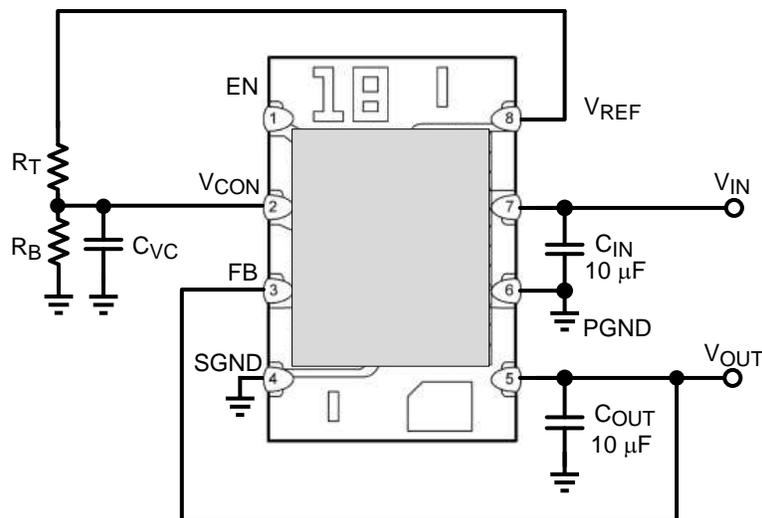


Figure 1. Schematic for Design A


Table 1. LMZ10501 and LMZ10500 Bill of Materials (BOM),  $V_{IN} = 2.7V$  to  $5.5V$ ,  $V_{OUT} = 1.8V$ ,  $I_{OUT (MAX)} = 1000mA / 650mA$

Quantity	Designator	Description	Case Size	Manufacturer	Manufacturer P/N
1	U1	SIMPLE SWITCHER Nano Module	SE08A	Texas Instruments	LMZ10501SE or LMZ10500SE
2	$C_{IN}, C_{OUT}$	10 $\mu F$ , X5R, 10V	0805	KEMET	C0805C106K8PACTU
1	$C_{VC}$	1000 pF	0603	TDK	C1608C0G2A102J
1	$R_B$	82.5 k $\Omega$	0603	Vishay-Dale	CRCW060382K5FKEA
1	$R_T$	187 k $\Omega$	0603	Vishay-Dale	CRCW0603187KFKEA

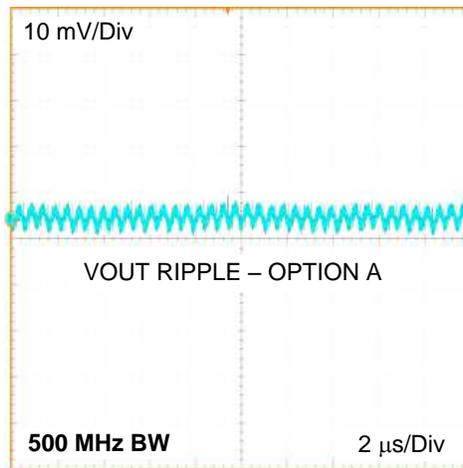

**Figure 2. Output Voltage Ripple Design A**  
 $V_{IN} = 5V, I_{OUT} = 1A$

### 3.2 Output Ripple Option B

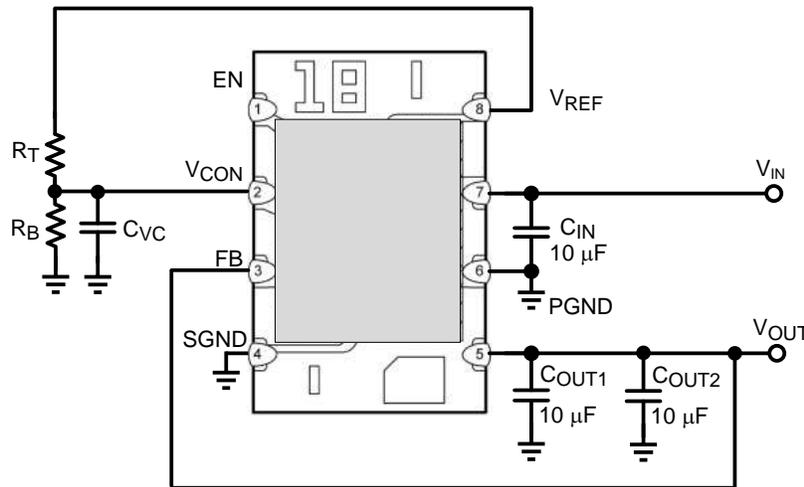

**Figure 3. Schematic for Design B**

**Table 2. LMZ10501 and LMZ10500 Bill of Materials (BOM),  $V_{IN} = 2.7V$  to  $5.5V$ ,  $V_{OUT} = 1.8V$ ,  $I_{OUT (MAX)} = 1000mA / 650mA$**

Quantity	Designator	Description	Case Size	Manufacturer	Manufacturer P/N
1	U1	SIMPLE SWITCHER Nano Module	SE08A	Texas Instruments	LMZ10501SE or LMZ10500SE
3	$C_{IN}, C_{OUT1}, C_{OUT2}$	10 $\mu F$ , X5R, 10V	0805	KEMET	C0805C106K8PACTU
1	$C_{VC}$	1000 pF	0603	TDK	C1608C0G2A102J
1	$R_B$	82.5 k $\Omega$	0603	Vishay-Dale	CRCW060382K5FKEA
1	$R_T$	187 k $\Omega$	0603	Vishay-Dale	CRCW0603187KFKEA

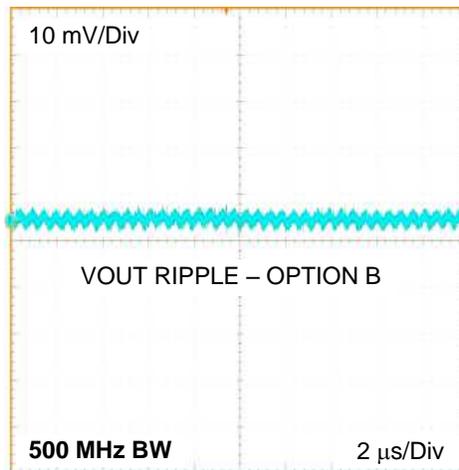


Figure 4. Output Voltage Ripple Design B  
 $V_{IN} = 5V$ ,  $I_{OUT} = 1A$

### 3.3 Output Ripple Option C


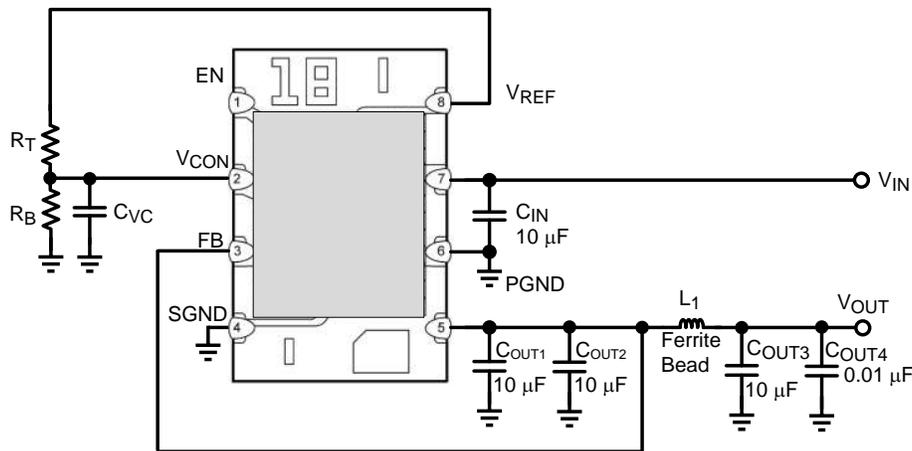


Figure 5. Schematic for Design C

Table 3. LMZ10501 and LMZ10500 Bill of Materials (BOM),  $V_{IN} = 2.7V$  to  $5.5V$ ,  $V_{OUT} = 1.8V$ ,  $I_{OUT (MAX)} = 1000mA / 650mA$


Quantity	Designator	Description	Case Size	Manufacturer	Manufacturer P/N
1	U1	SIMPLE SWITCHER Nano Module	SE08A	Texas Instruments	LMZ10501SE or LMZ10500SE
4	$C_{IN}$ , $C_{OUT1}$ , $C_{OUT2}$ , $C_{OUT3}$	10 $\mu F$ , X5R, 10V	0805	KEMET	C0805C106K8PACTU
1	$C_{OUT4}$	0.01 $\mu F$	0805	Johanson Dielectrics Inc	500R15W103KV4T
1	$C_{VC}$	1000 pF	0603	TDK	C1608C0G2A102J
1	$L_1$	100 $\Omega$ at 100MHz Ferrite bead	0805	TDK	MPZ2012S101A
1	$R_B$	82.5 k $\Omega$	0603	Vishay-Dale	CRCW060382K5FKEA
1	$R_T$	187 k $\Omega$	0603	Vishay-Dale	CRCW0603187KFKEA

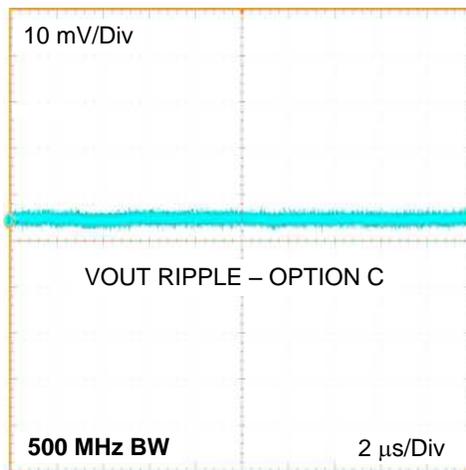

**Figure 6. Output Voltage Ripple Design C**  
 $V_{IN} = 5V, I_{OUT} = 1A$


#### 4 Tips and Tricks for Output Ripple Measurements

Taking proper output ripple measurements can be challenging. It is important to have a probe with a small ground loop to avoid picking up noise. One way to take a proper measurement is shown in [Figure 7](#). The 10x oscilloscope probe on the left has its ground wire forming a large loop which acts as an antenna and picks up noise. Such measurements will show high spikes on the oscilloscope screen. It is possible to improve this measurement by reducing the area of the ground loop. This is done by using a piece of bare wire and wrapping it around the scope probe's ground like shown in [Figure 7](#). The probe is then inserted in hollow turret points mounted across the output capacitor. This 10x probe is adequate for measuring noise down to the 10mV range.

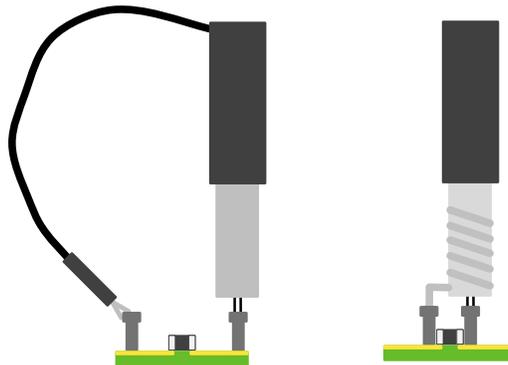


**Figure 7. Oscilloscope 10X Probe**

A simple, custom made 1x probe can be used for measurements under 10mV. This probe is shown below in [Figure 8](#). A piece of coaxial cable is laid flat against the board and soldered directly to the output capacitor of the switching regulator. The coaxial cable then connects to a small board which has a series 0.1μF AC coupling (DC blocking) capacitor. The other end of the coupling capacitor board connects to a coaxial cable which connects to an external 50Ω termination on the scope channel. One can also use the internal 50Ω termination on the scope. The measurements for the three designs in this application report were taken using a probe like the one shown in . The AC coupling capacitor and the 50Ω termination form a high pass filter with a cutoff frequency at  $1 / (2\pi RC)$ . In this case, the capacitor is 0.1μF which results in a cutoff frequency at 31.8kHz. Since the switching frequency of the regulator in the three designs is at 2MHz, this cutoff frequency is suitable for output ripple measurements.

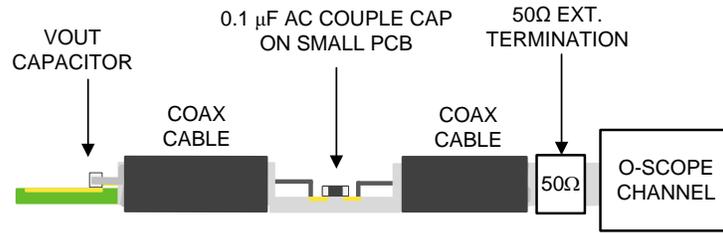

**Figure 8. Custom 1X Low Noise Probe Diagram**

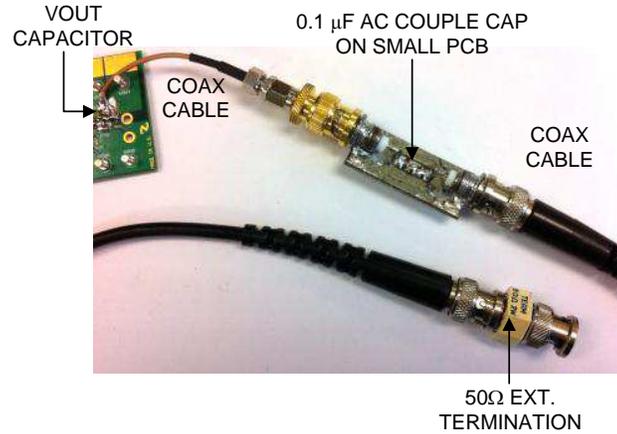

**Figure 9. Custom 1X Low Noise Probe Picture**

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)