

# The Impact of an Isolated Gate Driver's Input Stage for Motor-drive Applications



Sean Alvarado

You have many options when selecting an isolated gate driver for the power stage in motor-drive applications. Gate drivers can be simple or complex, with features such as an integrated Miller clamp, split outputs or an undervoltage (UVLO) lockout reference to the emitter of an insulated gate bipolar transistor (IGBT).

There are two options for input stages: a voltage input stage or current input stage. In this article, I'll introduce both input stage options and provide a few details you should consider when selecting a gate driver with an input stage for your application.

## Voltage input stage

Voltage input devices accept a complementary metal-oxide semiconductor pulse-width modulation (PWM) signal directly into the gate driver on the low-voltage or primary side. [Figure 1](#) shows an example of a typical voltage input isolated gate driver. The input pins, IN+ and IN-, are easy to drive with logic-level control signals available with most microcontrollers (MCUs). Although IN+ and IN- are on the primary side, a voltage gate driver only requires one of the inputs to receive a signal in order to function. Having both IN+ and IN- allows you to configure the PWM input signal as inverting or noninverting.

If you need more noise immunity, you can implement complementary or inverted logic PWM inputs. And if you choose only a single-input pin for your application, you can use the other pin for enable or disable functionality, as described in the application note, [“Enable Function with Unused Differential Input.”](#)

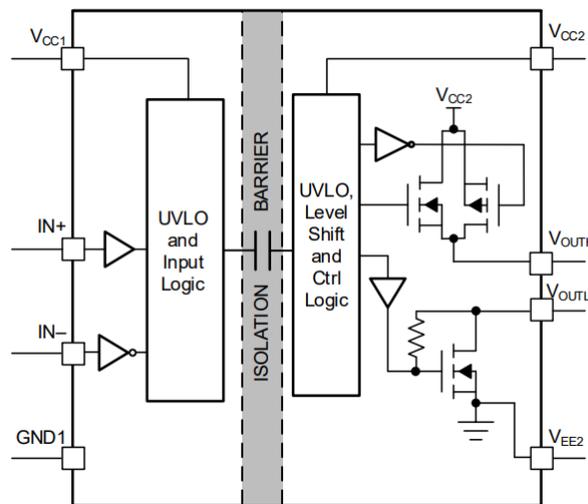



Figure 1. Single-channel isolated gate driver with voltage input stage

## Current input stage

Current input devices use a current signal into the gate driver on the primary side. [Figure 2](#) shows an example of a typical current input isolated gate driver. These devices are also referred to as optocompatible to match legacy optocouplers. In a legacy optocoupler, a current signal drives an LED inside the device to illuminate when you want the gate driver to turn on. The light emitted by the LED is received by a photodetector. The LED and

photodetector are physically separated inside the optocoupler, which creates galvanic isolation from the gate driver's primary to secondary side.


TI drivers use an emulated diode (e-diode) that helps improve reliability over a gate driver's lifetime. TI's optocompatible gate-driver devices use capacitive isolation paired with the e-diode to enable a pin-to-pin solution that is a drop-in upgrade to optical-based gate drivers. The e-diode input stage is not susceptible to effects that can reduce the lifetime of optocoupler gate drivers, such as degradation from higher temperatures or stressing of the input forward current that can both diminish the brightness of an LED. TI optocompatible solutions with the e-diode can help increase system lifetimes in motor-drive applications and operate across a wider ambient temperature range. You can learn more about this topic in the technical article, ["Replace your aging optocoupler gate driver."](#)

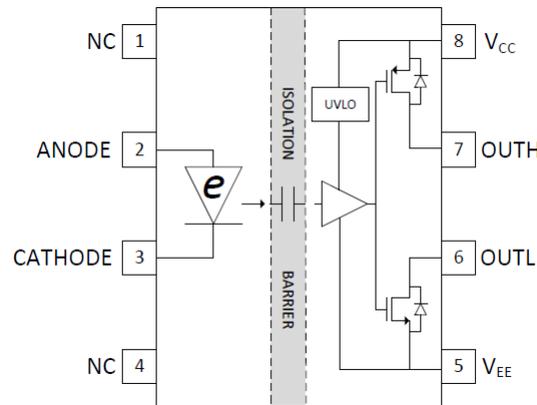

**Figure 2. Single-channel isolated gate driver with current (optocompatible) input stage**

There are system-level differences between voltage and current input gate drivers. A voltage-based solution requires fewer external components, and thus has a smaller total solution size. The MCU can drive voltage-based drivers directly, while current-based drivers need an external buffer to translate the voltage signal from the MCU into a current fed into the gate driver.


Figure 3 compares voltage input and current input gate drivers, as well as the external components required to drive an IGBT. Many designers have traditionally used current input devices to help improve noise immunity for the gate driver. Compared to a voltage signal, current signals are less susceptible to noise such as electromagnetic interference over longer distances. Adding low-pass filters to IN+ and IN- can also help increase the gate driver's noise immunity and preserve signal integrity.

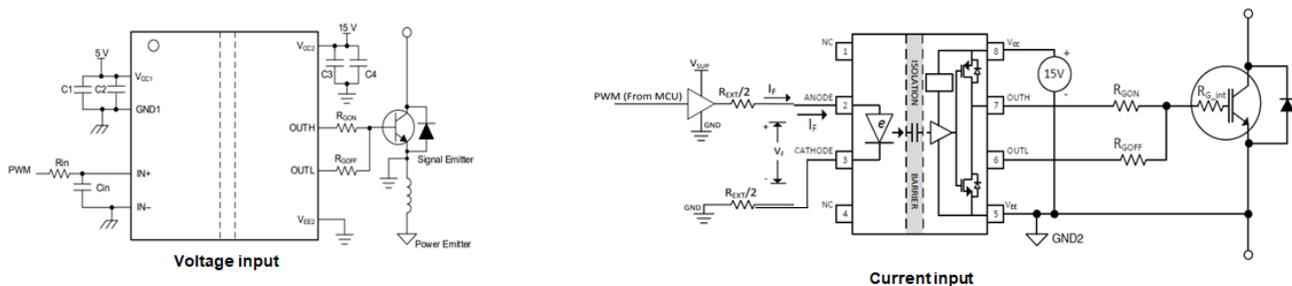

**Figure 3. Comparing voltage input and current input gate drivers**

Interlock helps prevent shoot-through in motor-drive power stages, protecting the power switches in high- and low-side configurations. It is possible to achieve interlock with a current input stage gate driver by connecting the anode of the high-side driver to the cathode of the low-side driver, and vice versa. For voltage input stage gate drivers that have a single input, you can implement interlock with external logic components, or connect IN+ of the high-side driver to IN- of the low-side driver (and vice versa) if the gate driver supports both IN+ and IN-.

Figure 4 shows a typical interlock example with a current input gate driver.

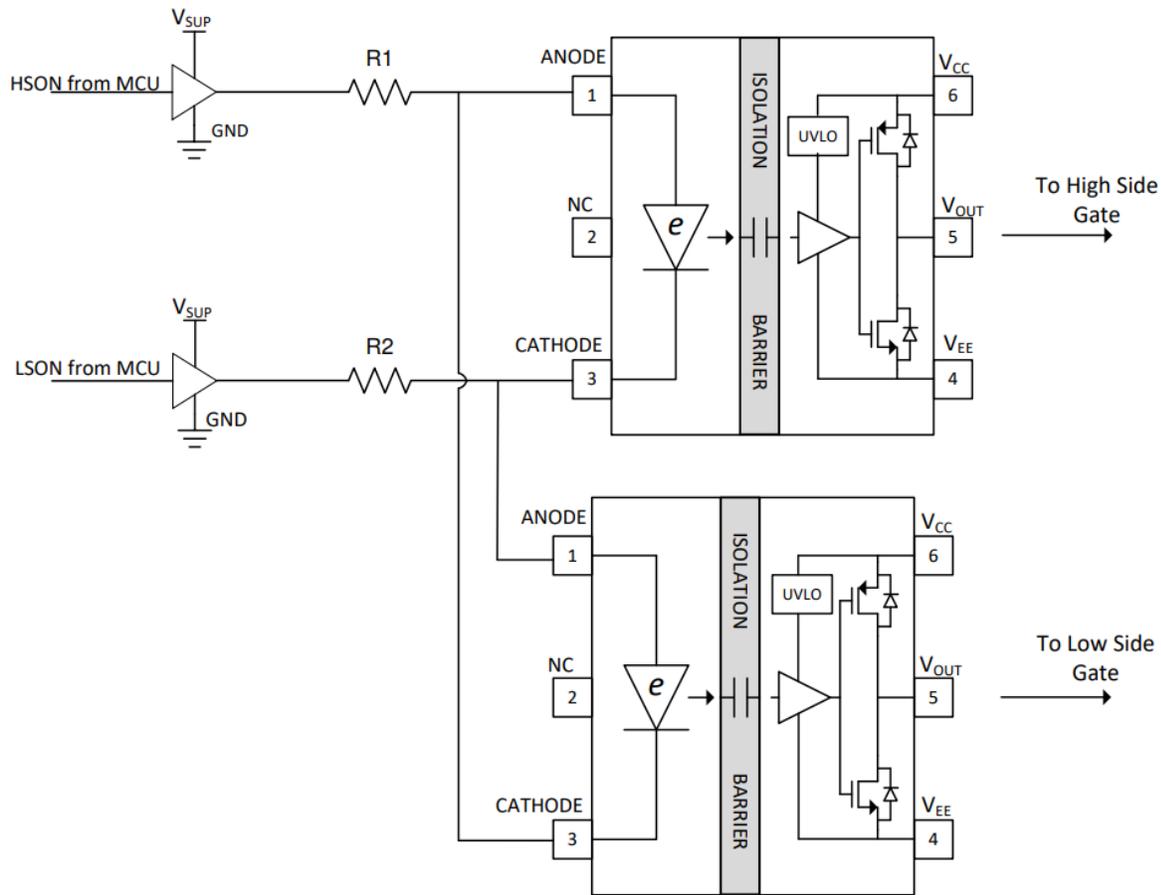

**Figure 4. Interlock example with current input gate driver**

TI offers gate drivers for both voltage or current input options, compared below in [Table 1](#).

**Table 1. Simple isolated gate drivers with alternative pinout options**

TI gate driver family	Input type	Miller clamp	Split output	Emitter-referenced UVLO	Simple single output
UCC23514	Current	UCC23514M	UCC23514S	UCC23514E	UCC23514V
UCC5310 UCC5320 UCC5350 UCC5390	Voltage	UCC5310MC, UCC5350MC	UCC5320SC, UCC5350SB, UCC5390SC	UCC5320EC, UCC5390EC	–

A gate driver's input stage has several implications for your motor-drive application, with system requirements dictating your selection. Whether you need to reduce the total solution size, maximize noise immunity or implement shoot-through protection, TI has many options to help you design your next motor-drive power stage.

#### Additional resources

- Watch the training video, [“How High-Voltage Isolation Technology Works – Capacitive Structure.”](#)
- Download the white paper, [“How Capacitive Isolation Solves Key Challenges in AC Motor Drives.”](#)
- Evaluate the UCC5320 with the [UCC5320SC isolated gate driver evaluation module](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated