

Design Advantage of D-CAP Control Topology



Xiao Xu

Texas Instruments first implemented the D-CAP™ control topology in 2004 on a double-data-rate (DDR) controller, the TPS51116. TI developed D-CAP technology as a form of current-mode control using the output capacitor equivalent series resistance (ESR) as the sense element. The name “D-CAP” refers to the current information that’s directly sensed across the output capacitors.

The first D-CAP controller was realized using an adaptive constant on-time (COT) modulator. Today, TI has a family of products using different modulators and evolving derivatives of the D-CAP control topology, such as the D-CAP2™ control scheme and D-CAP3 control mode. [Figure 1](#) shows the evolution of the D-CAP family.

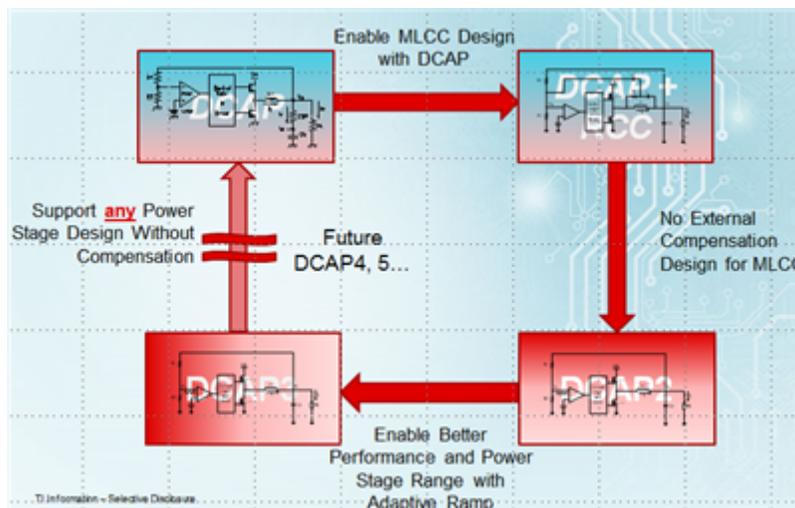


Figure 1. D-CAP Family Evolution Chart

After several iterations, each improving upon the last, TI introduced the D-CAP3 control mode as an optimized D-CAP control loop with adaptive internal ramp compensation to support a wide range of external power-stage designs. In addition, the D-CAP3 control mode implements a ramp offset cancellation technique to improve V_{OUT} setpoint accuracy performance. Unlike the D-CAP control topology, D-CAP3 control mode can stabilize almost any power-stage design using all multilayered ceramic capacitors (MLCCs), MLCCs plus bulk capacitors (with significant ESR) or bulk capacitor combinations. [Table 1](#) below shows the general power supply considerations for the DCAP family of modulators.

Table 1. Power-supply Design Considerations for D-CAP Family Modulators

The control element inherent to the D-CAP3 loop is the internal ramp, which is designed to emulate the inductor ripple current. For example, you can select the internal ramp of the TPS548D22 based on output voltage, duty cycle and switching frequency through the pin-strap configurations of the FSEL pin.	D-CAP control topology	D-CAP2 control scheme	D-CAP3 control mode
Control element	Uses the ESR of the output capacitor as the control element	Built-in RC emulates inductor current ripple	Built-in RC is adaptive to Fsw, output voltage and V_{IN}
Modulator	Fixed frequency or COT	Fixed frequency or COT	Fixed frequency or COT
Stability range	☺	☺☺	☺☺☺
Low component count	☺	☺☺	☺☺☺
Fast transient response	☺☺	☺	☺
Light load operation	☺☺	☺☺	☺☺
Fixed frequency	☺☺	☺☺	☺☺
Ceramic output capacitor support	☺	☺☺	☺☺☺
V_{OUT} setpoint accuracy	☺	☺☺	☺☺☺
Stackable and sync support	Only if using a fixed-frequency modulator		
Multiphase support capability*			

*Additional circuitries are required for current share and phase management

The TPS548D22 works well with any output capacitor combination. In a typical TPS548D22 converter design, there are three primary considerations for selecting the value of the output capacitance: transient requirements, output voltage ripple and stability.

The TPS548D22 is a 40A converter, so for any given proper set of design constraints, the transient requirements generally dominate the output stage (output inductor and capacitor bank) design. A tight ripple specification (along with a tighter DC specification) is becoming critical in some high-end and high-performance application-specific integrated circuit (ASIC) and field-programmable gate array (FPGA) designs. In applications where accuracy is critical, you will need to design the output power stage to meet the ripple and DC criteria. There is a minimum capacitance requirement in terms of small-signal stability. This requirement is in place to prevent subharmonic multiple pulsing behavior in a COT modulator.

Generally speaking, if the converter is properly designed for both the transient and ripple requirements, the minimum capacitance requirement is considered satisfied, but you should still double-check the minimum capacitance requirement by using Equation 6 in the TPS548D22 data sheet.

In summary, D-CAP based control topology brings convenience to the power supply designer that is designing high performance POL converters. Consider TI's SWIFT™ TPS548D22 synchronous step-down converter for your next design.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated