

How to Use an LDO to Protect a Power Source



Emrys Maier

This post is co-authored Aditya Ambardar.

Designers often face the challenge of protecting power sources from abrupt shorts or continuous high draw of current, because loads can behave unpredictably in many industrial and automotive applications. Low-dropout (LDO) regulators often power these loads, but have no built-in protection. In this post, we'll discuss a concept to effectively increase the LDO regulator's impedance, thus protecting the input from unpredictable load conditions.

Figure 1 shows the basic internal functionality of the single-channel LP2951. On the right-hand side, you can see that there are two resistors connected in sequence. When this device is connected for a 5V regulated output, V_{TAP} is tied directly to feedback, and sense is connected directly to output. Note that this produces a voltage divider from the output voltage to ground, with the reduced voltage being sent to the error amplifier. This feedback loop is what keeps the output at 5V.

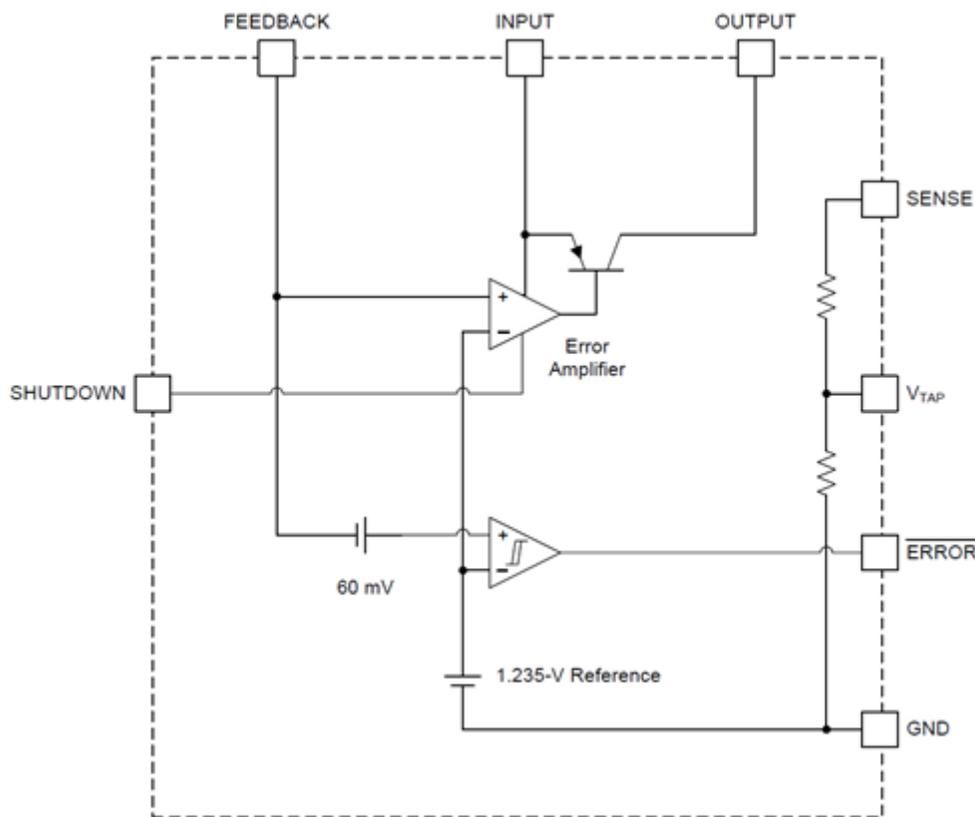


Figure 1. Functional Diagram for the LP2951

Using the two resistors inside the device is just one way to configure it. By using an external voltage divider, it's possible to choose any voltage within the device's output range. The process for doing this is described in the data sheet, but to keep a specific voltage on the output is simple. By using an external circuit, the current limit of this part can be reduced from the factory setting to a user-selectable level. For example, let's take a look at how you would use this technique to reduce the output voltage if the current draw is getting too high.

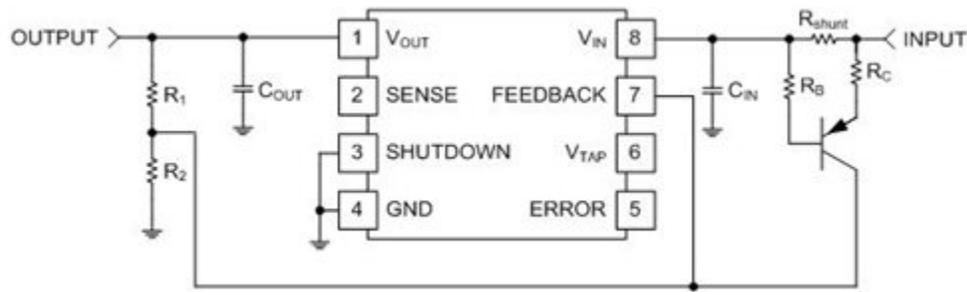


Figure 2. A Current-limiting Circuit for the LP2951

Figure 2 shows the full circuit used. Since the input current will be the same as the output current, you can place the shunt resistor on the input side to directly monitor the output current without affecting the output voltage.

On the right side, the input feeds into a shunt resistor and then directly to the V_{IN} pin. With no current flowing, the voltage across R_{shunt} will be zero and V_{BE} for the PNP transistor will also be zero, which means that the transistor will be off and no current will flow through R_C . The added PNP circuit will have no impact on the voltage divider on the left side of the diagram, and the LP2951 will work normally. See the equation example below.

$$R_{shunt} = \frac{V_{BE}}{I_{cutoff}} \quad (1)$$

Once some current starts to flow through R_{shunt} , it will develop a voltage and eventually will turn on the PNP transistor because $V_{BE} > V_F$ and the transistor will conduct. The transistor will force additional current into the feedback node and the output will change accordingly. The shunt resistor value is calculated by deciding on a desired cutoff current, I_{cutoff} , and using Equation 1.

The added voltage at feedback will make the LP2951 “think” that it is outputting more than the required voltage, and the output will reduce in voltage. The beauty of this circuit is that the shunt resistor value selects the output current limit. A larger resistor will produce the threshold voltage at a lower current and will roll off the output voltage sooner. The value of R_C allows designers to choose the final rolloff value at the output by controlling the amount of current added to the node.

Any values of R_1 and R_2 that meet this ratio will work, but to reduce power consumption, values in the 10 to 100 k Ω range are best. Choosing R_2 to be 10k Ω , R_1 is easily calculated as 30.49k Ω . Using a standard value of 33k Ω will not result in much error ($V_{OUT} = 4.977V$). See Equation 2:

$$V_{OUT} \cong 1.235 \left(1 + \frac{R_1}{R_2} \right) \therefore \frac{R_1}{R_2} = \frac{5}{1.235} - 1 = 3.049 \quad (2)$$

In order to force the output to a lower voltage, you need to trick the device into thinking that the output is increasing, which means that you need to force a higher voltage at the feedback node. The amount of voltage that you will need to add is determined by speculating that the output reaches the lower voltage, and calculating the difference between the feedback node voltage at 5V and the selected lower voltage. The feedback voltage at 5V will be 1.235V (by definition) and the voltage at the lower voltage will be defined by Equation 3:

$$V_{FB} = V_{OUT} \frac{R_1}{R_1 + R_2} \quad (3)$$

The difference between the two voltages is what you must add to the node to force the output to the lower voltage, or ΔV . To add the desired voltage to the feedback node, additional current must pass through that resistor. Equation 4 calculates the amount of current required:

$$\Delta I = \frac{\Delta V}{\frac{R_1 R_2}{R_1 + R_2}} \quad (4)$$

The value of R_B is not important because very little current will pass through it in this circuit. We recommend a value of 10k, but any value from 1k to 100k would be acceptable.

Now that the desired collector current has been found, you can calculate the final component value. R_C is calculated using Kirchhoff's voltage law, drawing a loop through the base-emitter junction of the transistor and the shunt resistor. See [Equation 5](#):

$$R_{shunt} I_{in} + I_B R_B - V_{EB} + I_C R_C = 0 \quad (5)$$

You can assume that $I_B R_B$ is approximately zero, so the only remaining unknowns are V_{EB} and R_C . The data sheet of the selected transistor will include V_{EB} , and you can easily calculate R_C after that.

The [LP2951](#) gives designers the capability to control its output with more than a simple resistor network. By using active components properly, you can link the output to the input current and protect sensitive circuitry. This circuit is certainly not the only solution available, but it is a simple one that anyone can test out and use.

Additional Resources

- Download the [LP2951 datasheet](#).
- Read the application note, "[LDO Noise Demystified](#)."
- Check out all of [TI's LDOs](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated