

Guy Nicholson



As a designer, choosing the right power supply topology is essential. Making the wrong choice means angry customers and lost time and money. When looking at voltage regulation, the usual trade-offs of size, efficiency, accuracy and voltage ripple are important. But so too is the topology of the solution. Should it be an inductor-based [converter](#), linear regulator ([LDO](#)) or [charge pump](#)? While charge pump ICs aren't the optimal solution for every design, they do possess several advantages over an inductive converter and increased efficiency over an LDO. Let's explore a few reasons to consider a charge pump.

Charge Pumps Are Simpler, Smaller and Come in the Same Building-block Capabilities as Inductive DC/DC Converters

A charge pump converter provides an easy-to-use, small solution size, with ruggedness not found in inductive DC/DC converters. Charge pumps also can be found in [boost](#), [buck](#) and [inverting](#) flavors, just like their magnetic brethren, without the inductor cost, height and printed circuit board (PCB) area requirements.

If you compare a charge pump-based buck regulator against an inductive solution, you can eliminate the inductor. The trade-off is about 10-20% lower efficiency than an inductive buck, but the charge pump saves space on your board. Charge pump circuits also are great for inverting an input voltage and for boosting. See [Figure 1](#) for an example of how to use a boost charge pump.

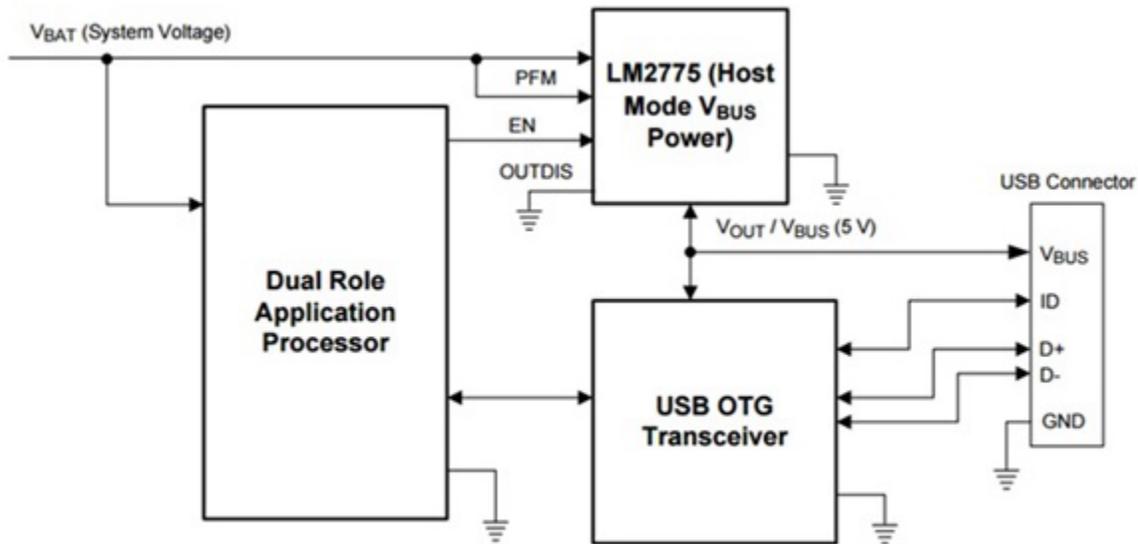


Figure 1. The LM2775 Is Often Used for Universal Serial Bus (USB) On-the-Go (OTG)/Mobile HDMI Applications

In [Figure 1](#), the regulated 5V output mode on the [LM2775](#) (a switched capacitor 5V boost converter) is often used for a USB OTG/mobile HDMI application. You can enable/disable the [LM2775](#) by applying a logic signal on only the EN pin, while grounding the OUTDIS pin. Depending on the USB/HDMI mode of the application, you could also enable the [LM2775](#) to drive the power bus line (host), or disable it to put its output in high impedance, allowing an external supply to drive the bus line (slave). In addition to the high-impedance back-drive protection, the output current-limit protection is 200mA (typical), well within USB OTG and HDMI requirements.

Charge Pumps Offer Greater Efficiency than LDOs

Charge pump regulators have approximately 20% greater efficiency over an LDO, while only increasing the solution size by adding two small ceramic capacitors. [Figure 2](#) shows an example of where a charge pump could be used versus an LDO, as long as output ripple is not a huge design issue. In this situation, regulation is achieved by current control through the input-connected switches or pulse-frequency modulation. Most devices of this nature also include a low-impedance pass mode for when the input to output ratio approaches 1. This gain and efficiency and switch to pass mode is highlighted in the efficiency curve of the [LM2771](#), low-ripple 250mA switched-capacitor step-down DC/DC converter, regulating the output voltage at 1.5V. In this application, the curve highlights that a 30% efficiency gain is possible by using a regulated charge pump circuit ([Figure 2](#)).

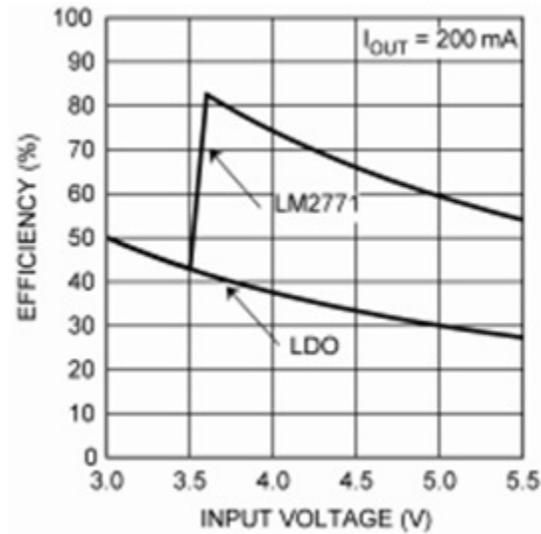


Figure 2. The Curve Highlights a 30% Efficiency Gain Using a Regulated Charge Pump versus a LDO

While a charge pump may not be the optimal solution for every DC/DC converter design, it does provide several advantages over inductive converters, including lower cost and smaller PCB size. A charge pump IC also provides increased efficiency over an LDO. To learn more about specific situations for which charge pumps are ideal, check out my next blog coming up in July.

Additional Resources:

- Browse product tables for:
 - [Charge-pump step-down solutions.](#)
 - [Charge-pump step-up solutions.](#)
 - [Charge-pump inverting solutions.](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated