

Extending battery life with a boost converter



Nini Zhong

A device's quiescent current, or I_Q , is an important parameter for low-power, energy-efficient end equipment such as continuous blood glucose monitors (CGMs). The current drawn by the integrated circuit at light or no loads significantly influences power losses in standby mode and the total run time of the system.

The load powered by the battery is not actually always on but is a pulse-width modulation (PWM) load, meaning that the load is made up of two periods: t_{PWM} and $t_{Standby}$, shown in Figure 1. While $t_{Standby}$ takes up 99.9% of the total load cycle, denoted as T in Figure 1, it is still important to improve efficiency, especially light-load efficiency.

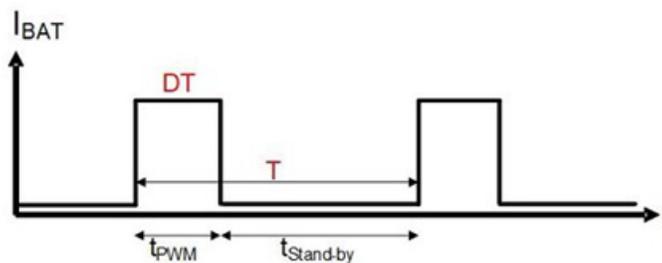


Figure 1-1. Load condition of a battery system

The challenge is to decrease power losses in standby mode and to limit current spikes and decrease the duty cycle during the on-pulse period, thus enhancing efficiency and extending battery life. A boost converter with low I_Q can help cut down the total power losses for a battery.

Choose a low- I_Q boost converter to enhance overall efficiency

A CGM shows why it's important to minimize I_Q to extend battery life. Figure 2 shows a CGM power block: a sensor to read the glucose concentration, a transmitter to capture the glucose reading, and a wireless receiver for communication and display. The transmitter, consisting of a coin-cell battery, boost converter and analog front end (Figure 3) consumes the most power.

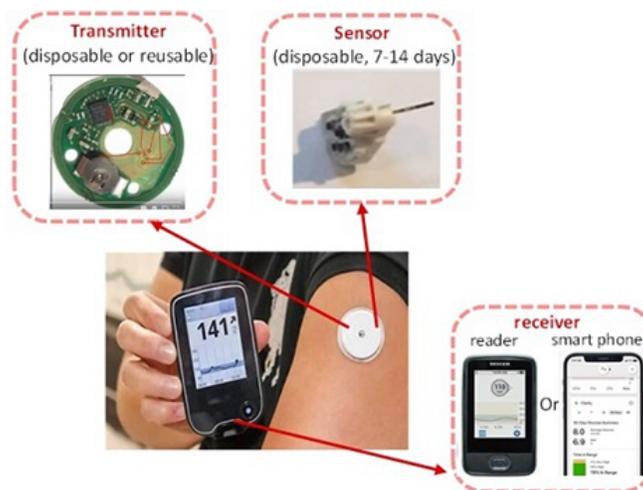


Figure 1-2. Power architecture of a CGM

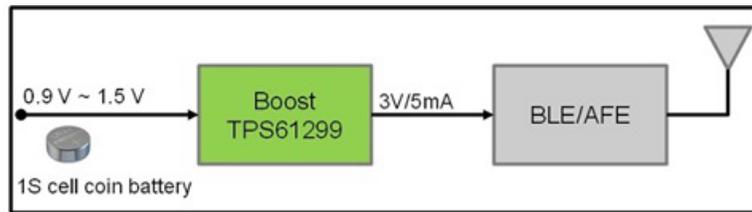


Figure 1-3. Power architecture of a CGM transmitter

Figure 4 shows the load current of the analog front end. As you can see, the transmitter is in standby mode 99% of the time.

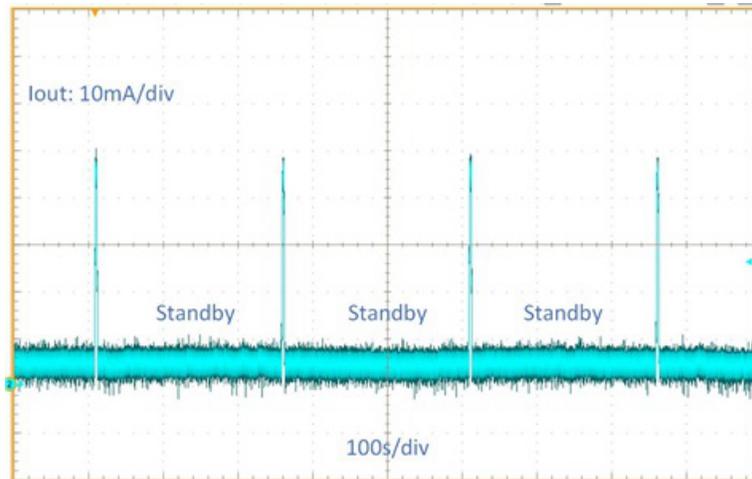


Figure 1-4. Current consumption vs. time in a CGM transmitter

Equation 1 calculates the total power supplied by the battery during one load cycle as:

$$P_{total} = DT \frac{P_{on_pulse}}{eff1} + (1 - D)T \frac{P_{standby}}{eff2} \quad (1)$$

Lowering the I_Q could directly improve efficiency in standby mode.

TI's TPS61299 boost converter only consumes 95 nA of I_Q from V_{OUT} , making it possible to increase efficiency 39% under the typical standby conditions of a CGM: $V_{IN} = 3.0\text{ V}$, $V_{OUT} = 3.3\text{ V}$ and standby $I_{OUT} = 10\text{ }\mu\text{A}$ (Figure 5). An on-pulse load of 30 mA lasting 600 ms every 288-s load cycle translates to as much as 2.53 W of power saved per day. This efficiency increase in standby mode can ultimately lengthen battery life by 20%.

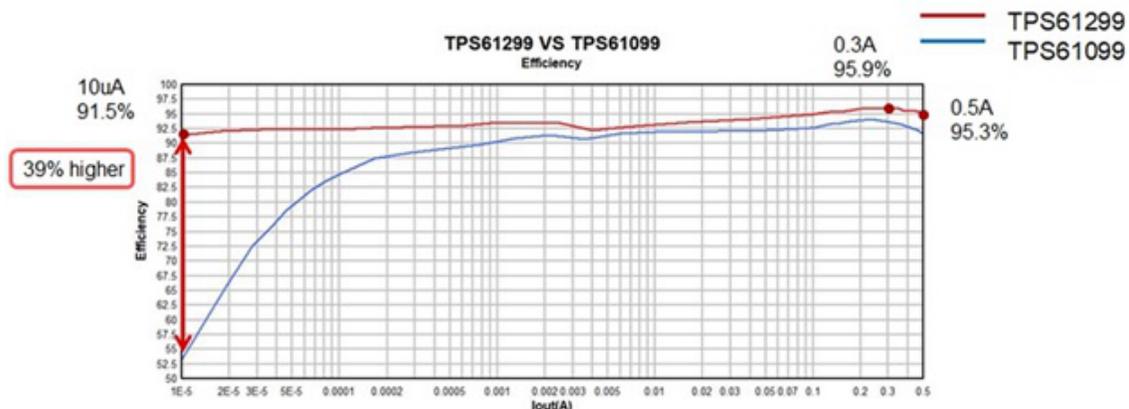


Figure 1-5. Efficiency curve of the TPS61299 and a 600-nA I_Q device

Limit the discharge current from the battery

Although high-energy-density, low-discharge coin-cell batteries are extremely popular, their main drawback is a high equivalent series resistance (ESR) and limited current capability. For a PWM load application, the duty cycle is small, and high current pulses add to the high inrush current spikes, which are much higher than the discharge current and have detrimental effects on battery capacity and battery life – especially when using a supercapacitor. Also, as the battery ages, the ESR increases, and the power loss caused by current spikes increases accordingly.

Battery capacity is inverse with discharge current, and battery life is linear with capacity, as shown in [Figure 6](#). Decreasing the discharge current from 500 mA to 100 mA doubles the battery life.

The TPS61299 boost converter family, available in input current limits from 5 mA to 1.5 A, accurately limits discharge current during the on-pulse period, helping prolong battery life.

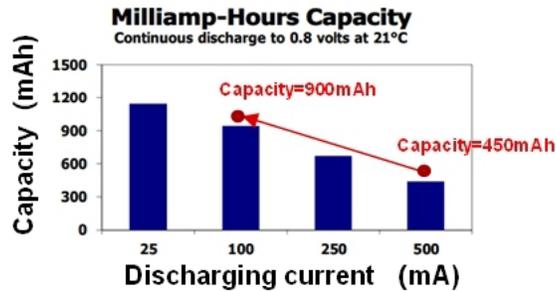


Figure 1-6. Battery life vs. discharge current

Select a device with fast transient response times

Decreasing the on-pulse width of the load to decrease the total power loss also extends overall battery life.

[Figure 7](#) illustrates the load condition cycle-by-cycle of a smartwatch LED. The PWM load covers two stages: transient time (t_{tran}) and sampling time (t_{sample}). t_{tran} measures how fast the boost converter regulates back to the targeted output voltage after an abrupt change in load current or supply voltage. t_{sample} is a constant value once the photodiode settles.

Shortening t_{tran} can largely narrow the PWM time (t_{PWM}), widening the blanking time (t_{BLANK}) in turn and enabling a longer low- I_Q working state. Assuming that it is possible to decrease t_{tran} from 100 μs to 10 μs , with a 10- μs t_{sample} the cycle time is 250 μs , enabling an extension of t_{BLANK} from 140 μs to 230 μs , as shown in [Figure 8](#).

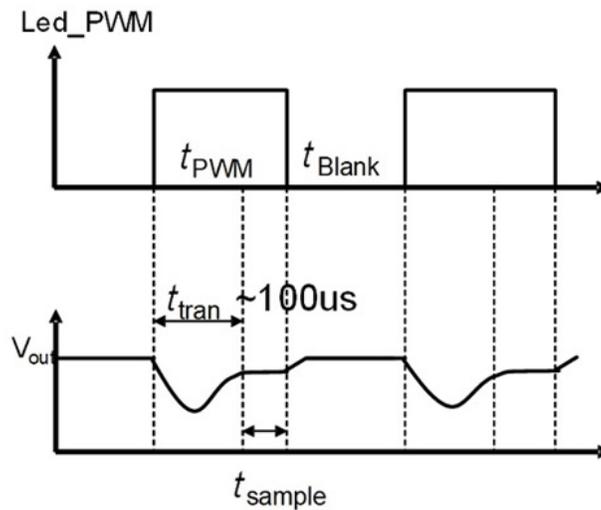


Figure 1-7. Traditional PWM load

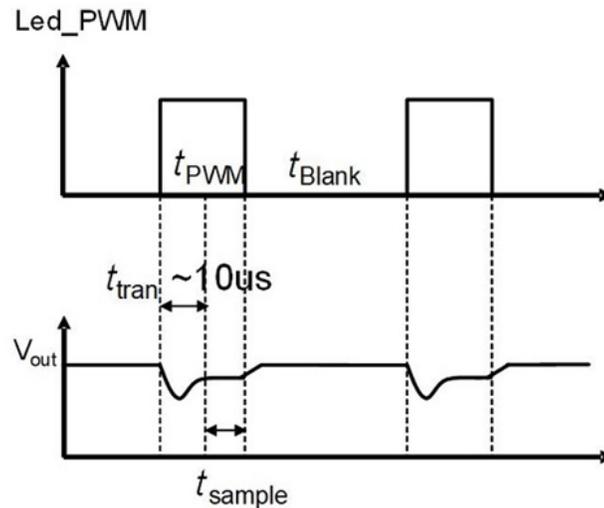


Figure 1-8. PWM load with fast transient performance

It is always a struggle to maintain low I_Q to achieve high efficiency during t_{BLANK} and a shortening t_{tran} . Low- I_Q devices always suffer from longer response times because it is challenging to recharge the internal parasitic capacitors with very low I_Q .

Nevertheless, the TPS61299 can achieve faster transient response times with a wider bandwidth. For example, as shown in [Figure 9](#), the typical settling time with an output-current step up from 0 mA to 200 mA under 3.6-V input and 5-V output conditions is 8 μ s.

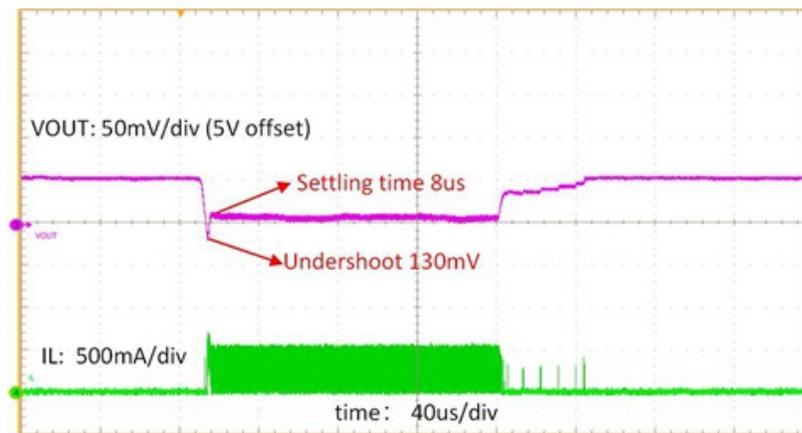


Figure 1-9. Transient waveform of the TPS61299

Conclusion

The TPS61299 boost converter simultaneously integrates three of the most effective ways for designers to reduce total battery power losses:

- Choose a low- I_Q boost converter to enhance overall efficiency.
- Limit the discharge current from the battery.
- Select a device with fast transient response time.

Above all, higher efficiency and lower power losses for boost converters will continue to be trends in battery applications, while lower $R_{DS(on)}$ and an optimized control loop may also contribute to lengthening battery life.

Additional resources

- Download the application note, “Advantages of the TPS61299 with Fast Transient Performance in Smartwatch Applications.”

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated