


Test Report: PMP21384

PMP21384: Universal AC Input Integrated FET Buck Converter Reference Design



Description

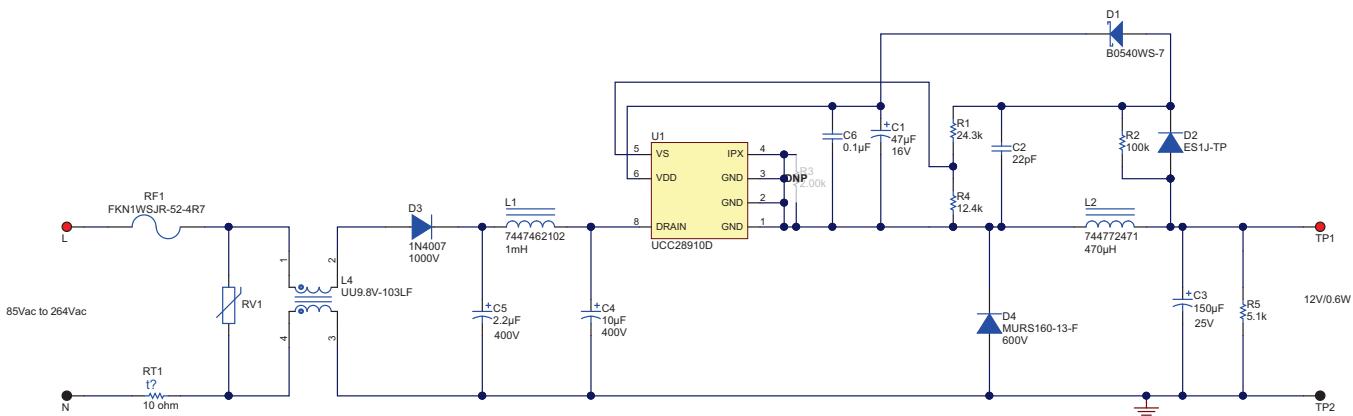This reference design utilizes the UCC28910 device, with its integrated 700-V FET, to implement an AC-to-DC high-side buck converter.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
V_{IN}	85 V _{AC} –264 V _{AC}
V_{OUT}	12 V
I _{out}	50 mA nominal, 150 mA peak

2 Testing and Results

2.1 Efficiency Graphs

Figure 1 shows the converter efficiency for a 120 V_{AC} and 230 V_{AC} input with a 12-V output.

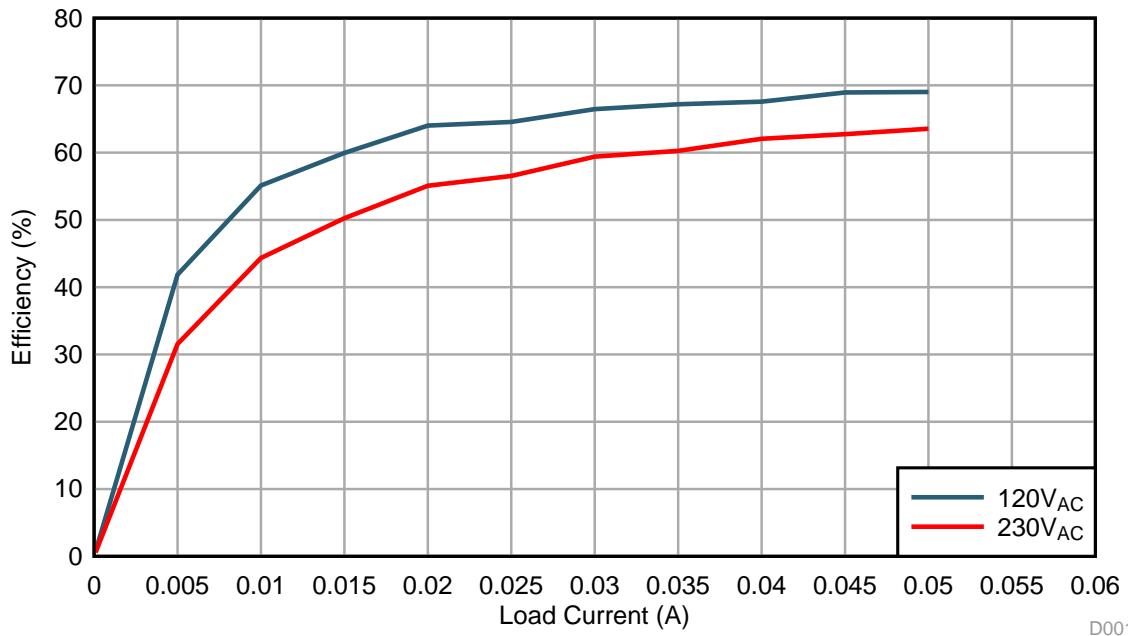


Figure 1. Converter Efficiency, 120 V_{AC}, 230 V_{AC}, 12-V Output

2.2 Efficiency Data

Table 2 and Table 3 list the efficiency data for 120 V_{AC} and 230 V_{AC} input with 12-V output.

Table 2. Efficiency Data 120 V_{AC} Input With 12-V Output

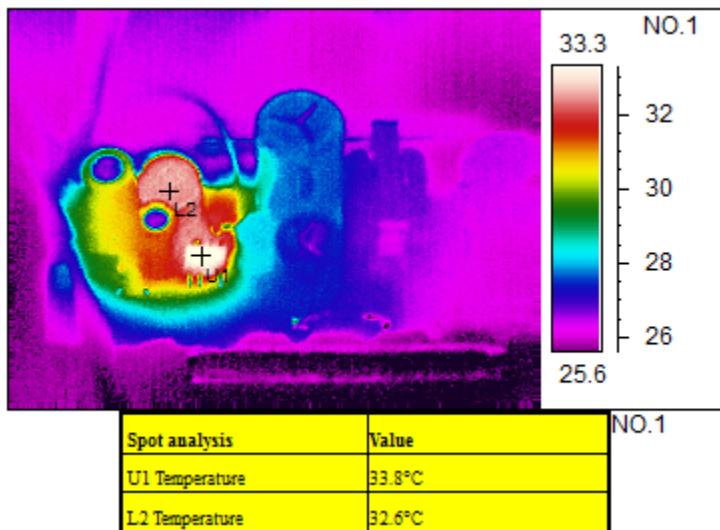
Iout	Vout	Vin AC	lin Arms (mA)	Pin	Pout	Losses	Efficiency
0.000	12.030	120.2	0.00000	0.0000	0.00	0.00	0.0%
0.005	11.990	120.2	4.5210	0.1432	0.06	0.08	41.9%
0.010	11.960	120.2	6.740	0.2170	0.12	0.10	55.1%
0.015	11.950	12.2	8.830	0.2990	0.18	0.12	59.9%
0.020	11.940	120.2	10.820	0.3730	0.24	0.13	64.0%
0.025	11.930	120.2	12.880	0.4620	0.30	0.16	64.6%
0.030	11.920	120.2	14.700	0.5380	0.36	0.18	66.5%
0.035	11.940	120.2	16.590	0.6220	0.42	0.20	67.2%
0.040	11.960	120.2	18.590	0.7080	0.48	0.23	67.6%
0.045	11.960	120.2	20.230	0.7807	0.54	0.24	68.9%
0.050	11.950	120.2	22.010	0.8658	0.60	0.27	69.0%

Table 3. Efficiency Data 230 V_{AC} Input With 12-V Output

I _{out}	V _{out}	V _{in AC}	I _{in Arms} (mA)	P _{in}	P _{out}	Losses	Efficiency
0.000	12.040	230.2	0.00000	0.0000	0.00	0.00	0.0%
0.005	11.990	230.2	3.2420	0.1900	0.06	0.13	31.6%
0.010	11.970	230.2	4.660	0.2700	0.12	0.15	44.3%
0.015	11.960	230.2	6.040	0.3570	0.18	0.18	50.3%
0.020	11.950	230.2	7.390	0.4340	0.24	0.20	55.1%
0.025	11.940	230.2	8.782	0.5280	0.30	0.23	56.5%
0.030	11.940	230.2	10.000	0.6030	0.36	0.24	59.4%
0.035	11.930	230.2	11.290	0.6930	0.42	0.28	60.3%
0.040	11.930	230.2	12.460	0.7690	0.48	0.29	62.1%
0.045	11.920	230.2	13.650	0.8550	0.54	0.32	62.7%
0.050	11.910	230.2	14.810	0.9370	0.60	0.34	63.6%

2.3 Thermal Images

The thermal image in [Figure 2](#) shows operation at 120 V_{AC} input and 12 V at 50-mA output, with no airflow. The board ran for 20 minutes with these conditions before the thermal image was taken.

**Figure 2. Thermal Image, 120 V_{AC} Input, 12 V at 50-mA Output**

The thermal image in [Figure 4](#) shows operation at 230V input and 12 V at 50-mA output, with no airflow. The board ran for 20 minutes with these conditions before the thermal image was taken.

Figure 3.

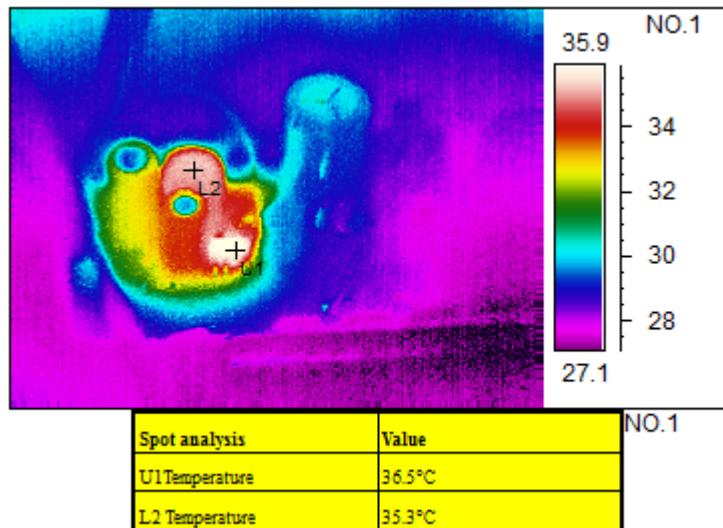


Figure 4. Thermal Image, 230 V_{AC} Input, 12 V at 50-mA Output

2.4 Dimensions

[Figure 5](#) shows the PMP21384 device dimensions.

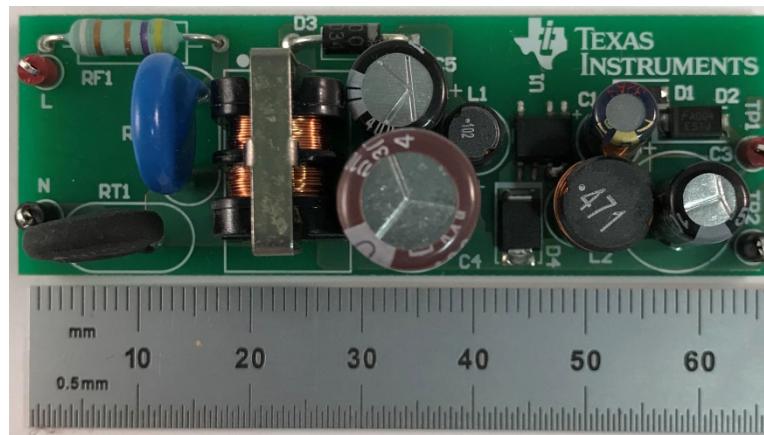


Figure 5. PMP21384 Device Dimensions

3 Waveforms

3.1 Switching

Figure 6 shows the switch node voltage. The input voltage is 85 V_{AC} and the 12-V output is loaded to 50 mA (100 V/div, 20 μ s/div).

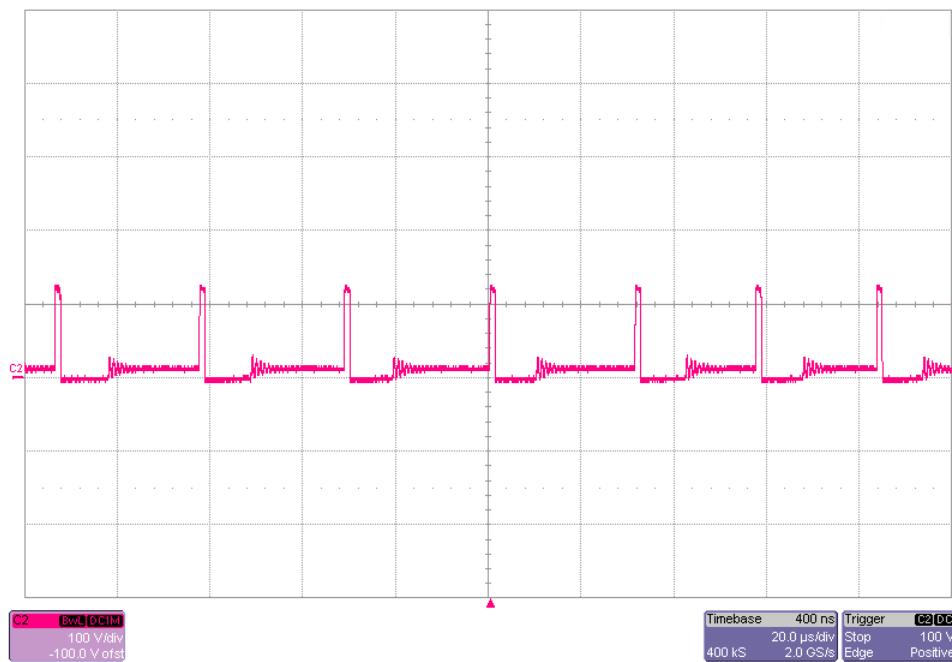


Figure 6. Switch Node Voltage, $V_{IN} = 85$ V_{AC}, 12-V $V_{OUT} = 50$ -mA Load

Figure 7 shows the switch node voltage where the input voltage is 120 V_{AC} and the 12-V output is loaded to 50 mA (100 V/div, 20 μ s/div).

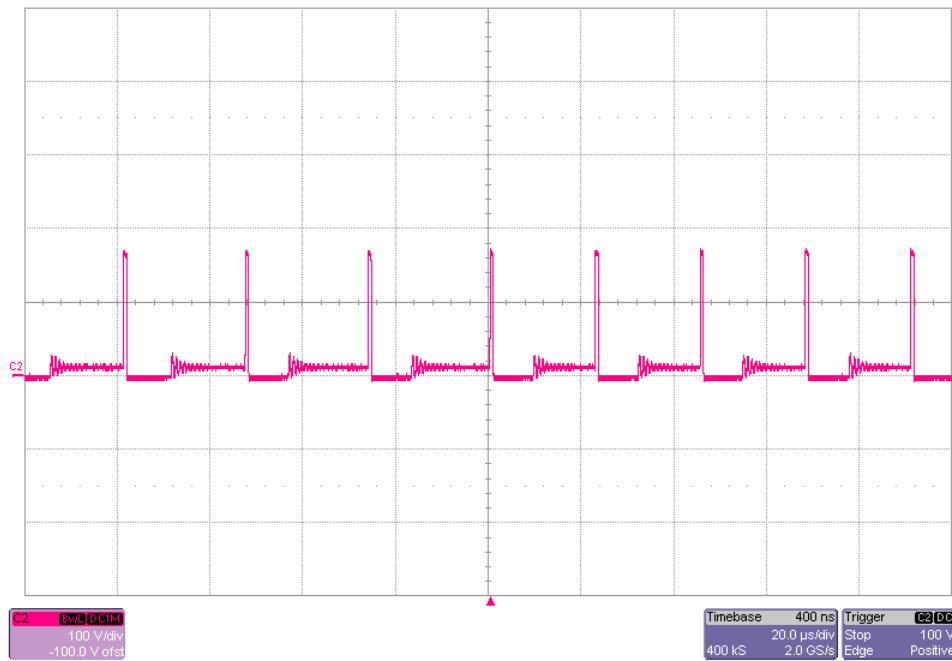


Figure 7. Switch Node Voltage, $V_{IN} = 120$ V_{AC}, 12-V Output Load = 50 mA

Figure 8 shows the switch node voltage where the input voltage is 264 V_{AC} and the 12-V output is loaded to 50 mA (100 V/div, 20 μ s/div).

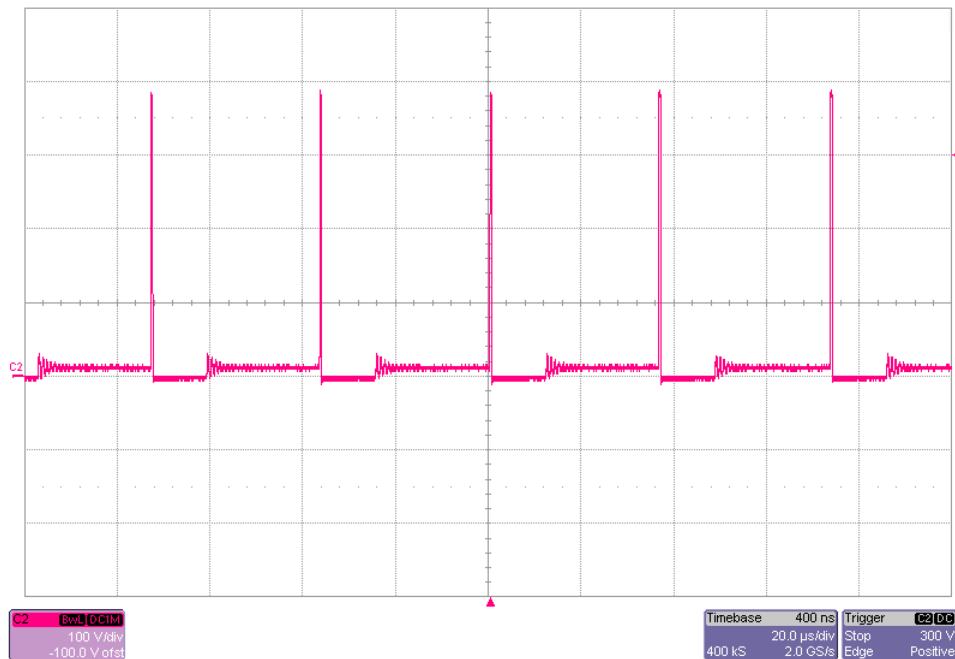


Figure 8. Switch Node Voltage, $V_{IN} = 264 \text{ V}_{AC}$, 12-V Output Load = 50 mA

3.2 Output Voltage Ripple

Figure 9 shows the output ripple voltage. The image was taken with the 12-V output loaded to 50 mA and the input voltage set to 120 V_{AC} (50 mV/div, 200 μ s/div).

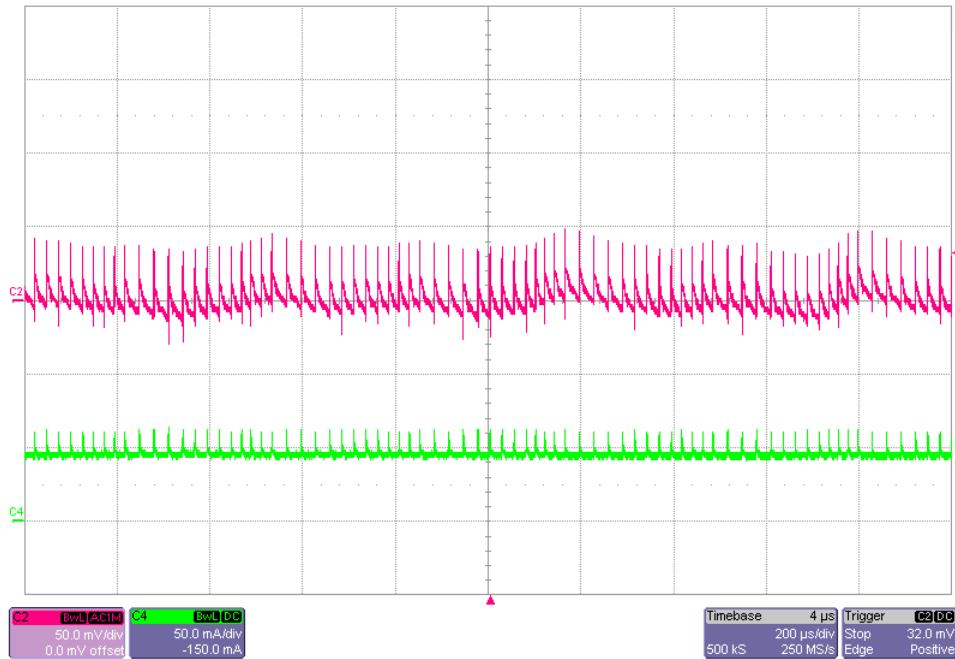


Figure 9. Output Voltage Ripple, $V_{IN} = 120 \text{ V}_{AC}$, 12 V $V_{OUT} = 50\text{-mA}$ Load

Figure 10 shows the output ripple voltage. The image was taken with the 12-V output with no load and the input voltage set to 120 V_{AC} (50 mV/div, 5 ms/div).

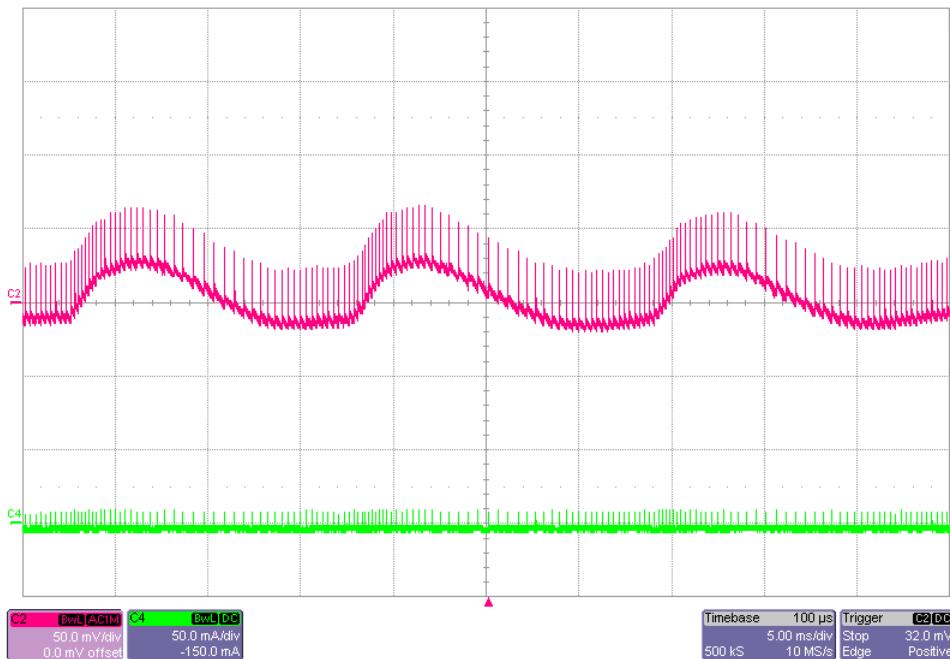


Figure 10. Output Voltage Ripple, V_{IN} = 120 V_{AC}, 12 V V_{OUT} = 0-mA Load

Figure 11 shows the output ripple voltage. The image was taken with the 12-V output loaded to 50 mA and the input voltage set to 230 V_{AC} (50 mV/div, 200 µs/div).

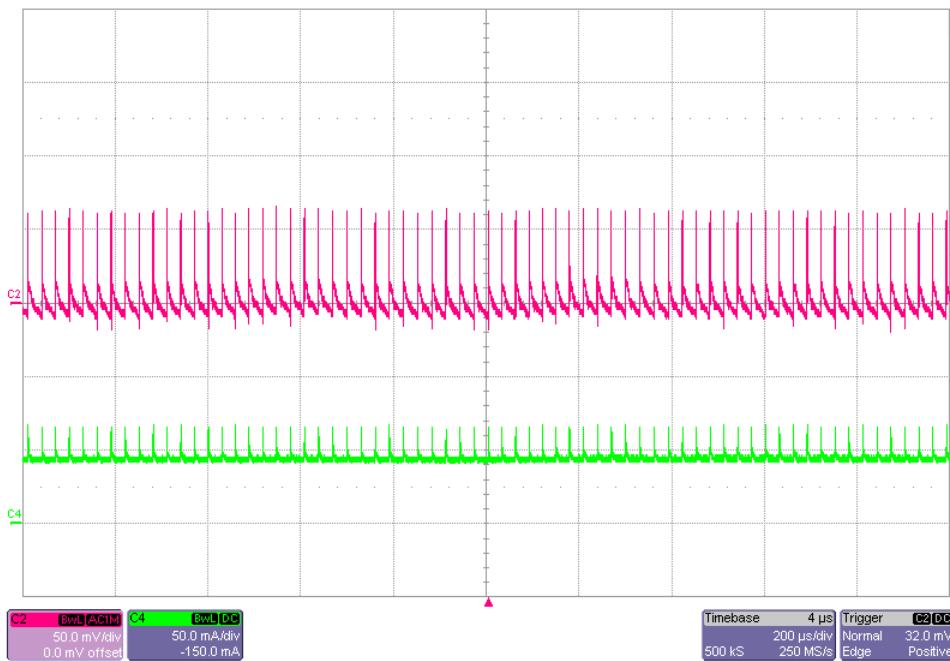


Figure 11. Output Voltage Ripple, V_{IN} = 230 V_{AC}, 12 V V_{OUT} = 50-mA Load

Figure 12 shows the output ripple voltage. The image was taken with the 12-V output with no load and the input voltage set to 230 V_{AC} (50 mV/div, 5 ms/div).

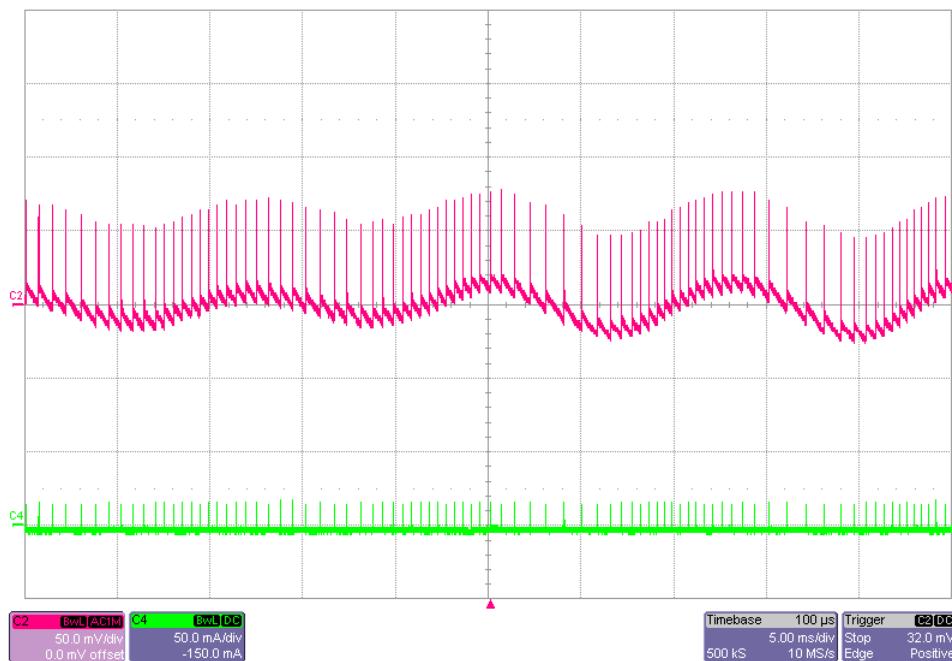


Figure 12. Output Voltage Ripple, V_{IN} = 230 V_{AC}, 12 V V_{OUT} = 0-mA Load

3.3 Load Transients

Figure 13 shows the 12-V output voltage when the load current is stepped from 50 mA to 150 mA with an input voltage of 120 V_{AC} (500 mV/div, 50 mA/div, 5 ms/div).

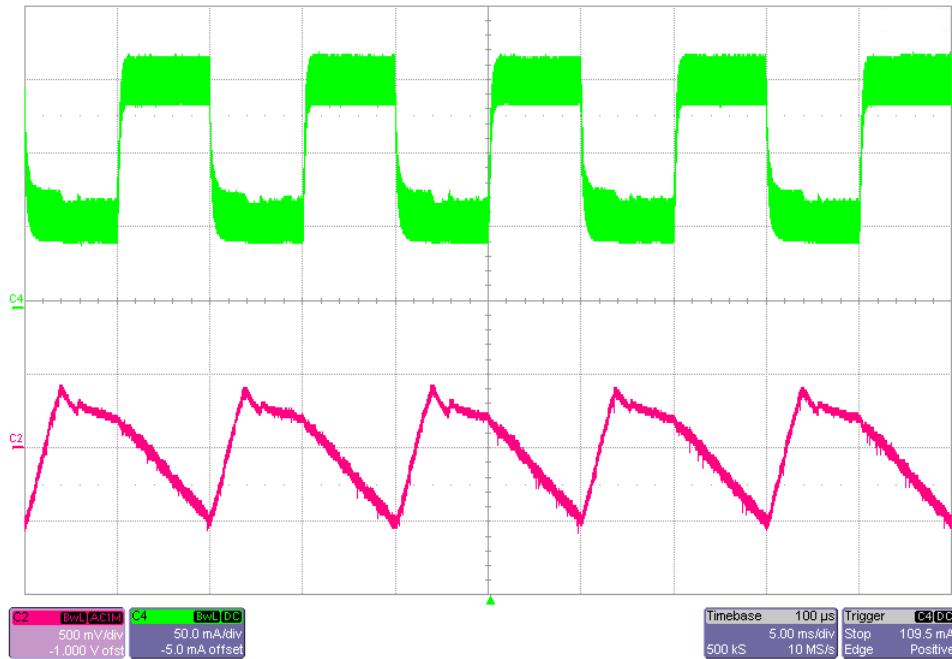


Figure 13. Load Transients, V_{IN} = 120 V_{AC}, 12 V V_{OUT} From 50-mA to 150-mA Load

Figure 14 shows the 12-V output voltage when the load current is stepped between 50 mA and 150 mA with an input voltage of 230 V_{AC} (500 mV/div, 50 mA/div, 5 ms/div).

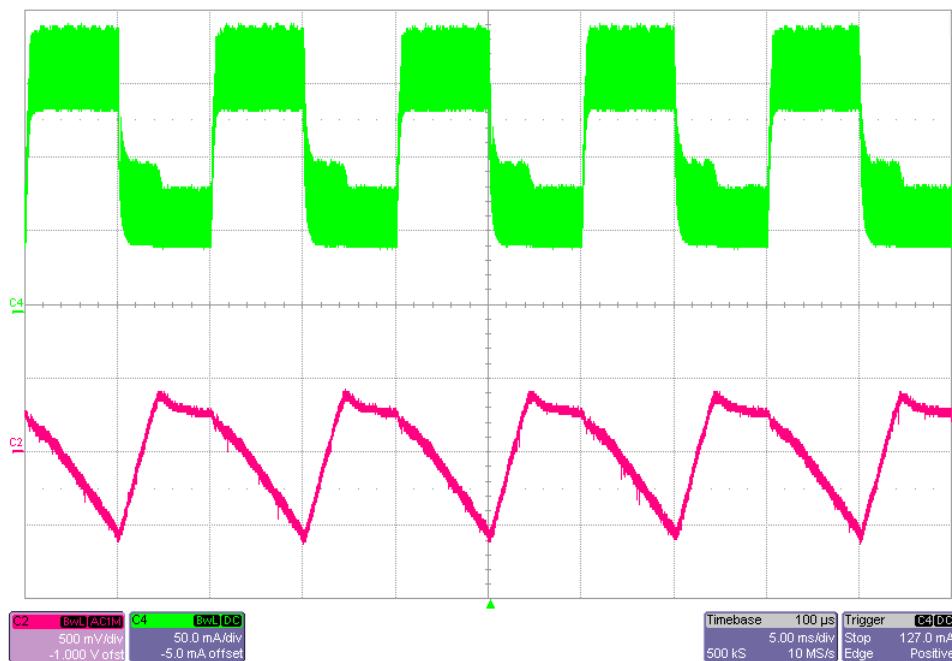


Figure 14. Load Transients, $V_{IN} = 230 \text{ V}_{AC}$, 12 V V_{OUT} From 50-mA to 150-mA Load

3.4 Start-up Sequence

Figure 15 shows the output voltage startup waveform after the application of 85 V_{AC} and output loaded to 0 A (5 V/div, 20 ms/div).

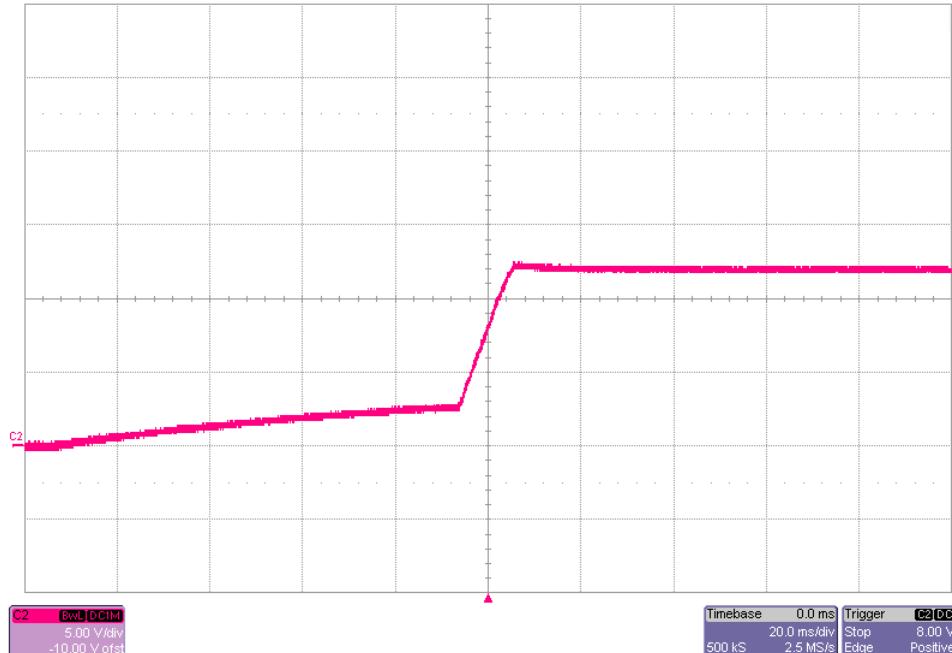


Figure 15. Output Voltage Startup Waveform, 85 V_{AC}, $V_{OUT} = 0\text{-mA}$ Load

[Figure 16](#) shows the output voltage startup waveform after the application of 85 V_{AC} and output loaded to 50 mA (5 V/div, 20 ms/div).

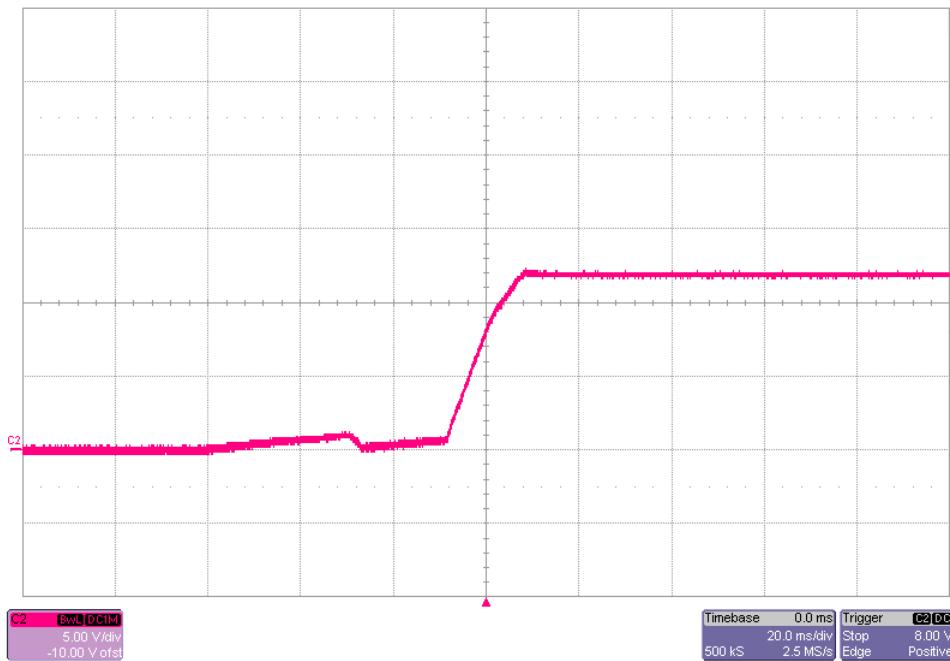


Figure 16. Output Voltage Startup Waveform, 85 V_{AC}, V_{OUT} = 50-mA Load

[Figure 17](#) shows the output voltage startup waveform after the application of 120 V_{AC} and output loaded to 0 A (5 V/div, 20 ms/div)

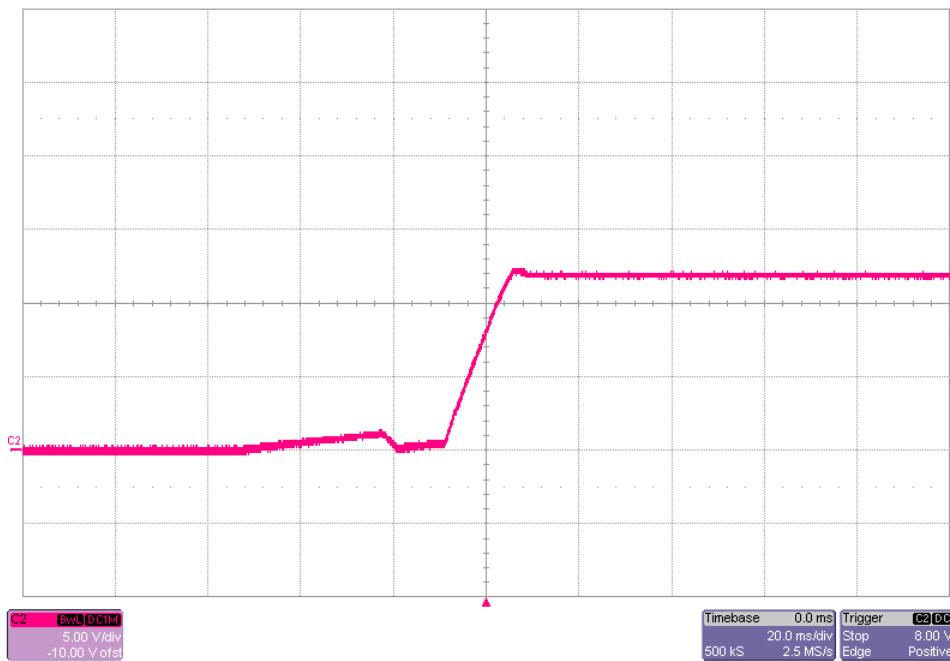


Figure 17. Output Voltage Startup Waveform, 120 V_{AC}, V_{OUT} = 0-mA Load

[Figure 18](#) shows the output voltage startup waveform after the application of 120 V_{AC} and output loaded to 50 mA (5 V/div, 20 ms/div).

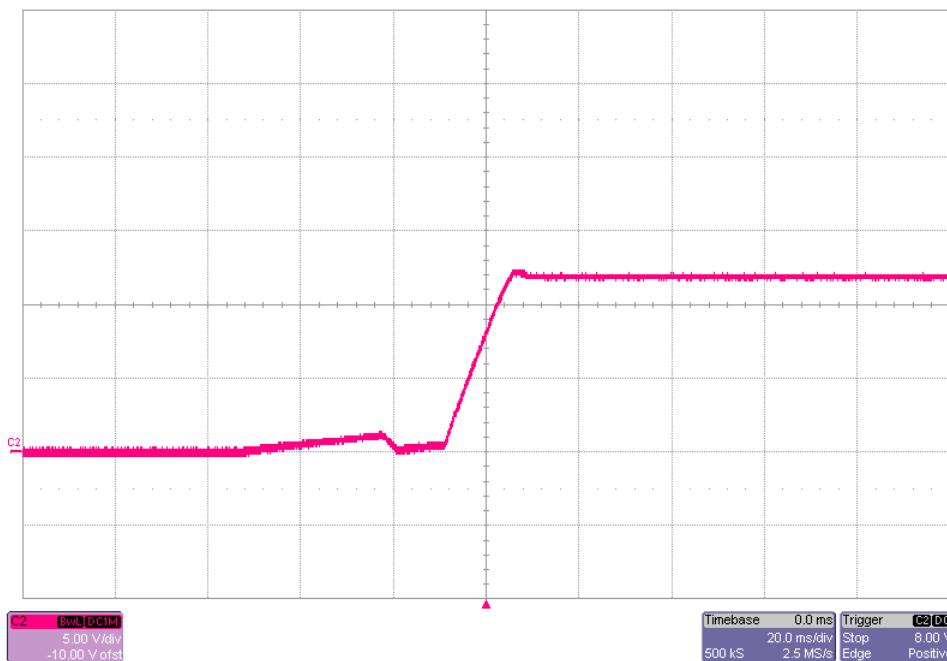


Figure 18. Output Voltage Startup Waveform, 120 V_{AC}, V_{OUT} = 50-mA Load

[Figure 19](#) shows the output voltage startup waveform after the application of 230 V_{AC} and output loaded to 0 A (5 V/div, 20 ms/div).

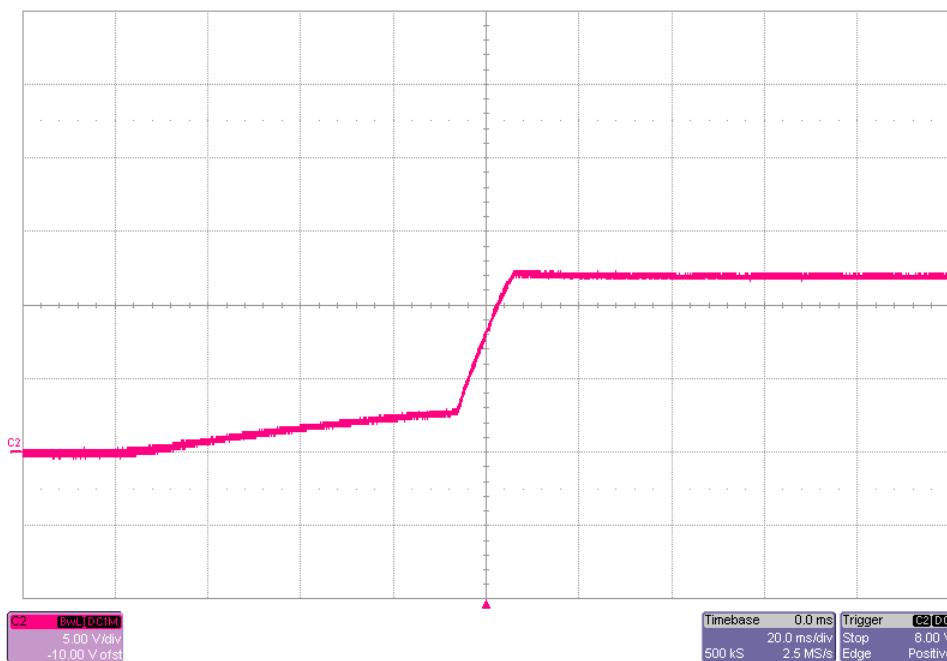


Figure 19. Output Voltage Startup Waveform, 230 V_{AC}, V_{OUT} = 0-mA Load

[Figure 20](#) shows the output voltage startup waveform after the application of 230 V_{AC} and output loaded to 50 mA (5 V/div, 20 ms/div).

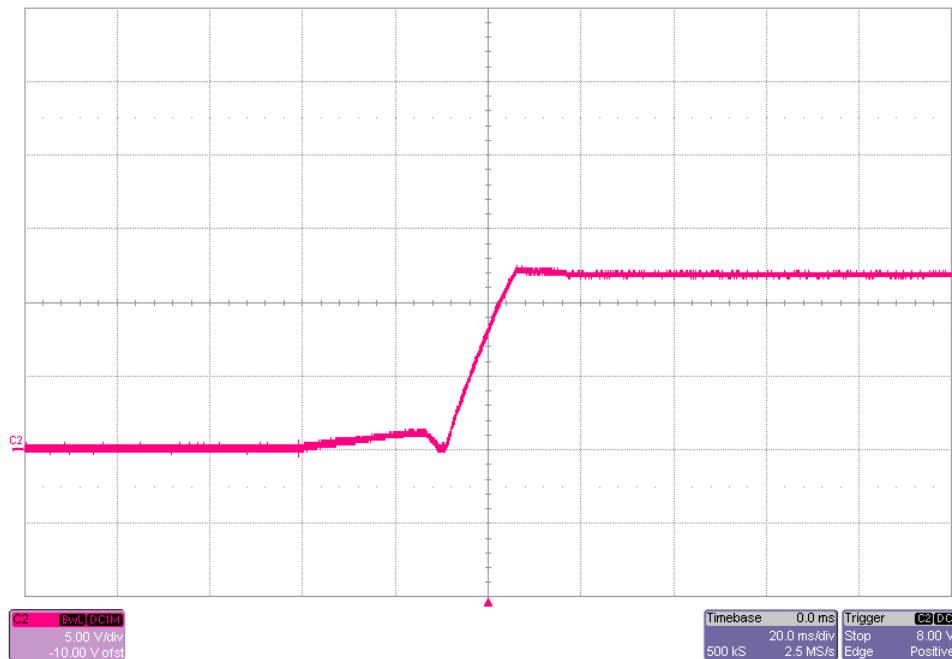


Figure 20. Output Voltage Startup Waveform, 230 V_{AC}, V_{OUT} = 50-mA Load

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated