

Test Report: PMP22021

Compact Isolated DC-DC Flyback Reference Design



Description

This reference design uses LM5022 to make an isolated 3.3-V output capable of 1.1-A from a 9-V to 15-V input. All components are placed on one side of the board to reduce assembly complexity and cost. A secondary filter reduces the output ripple to under 30-mV peak-to-peak. The design can achieve 80% efficiency across input conditions.

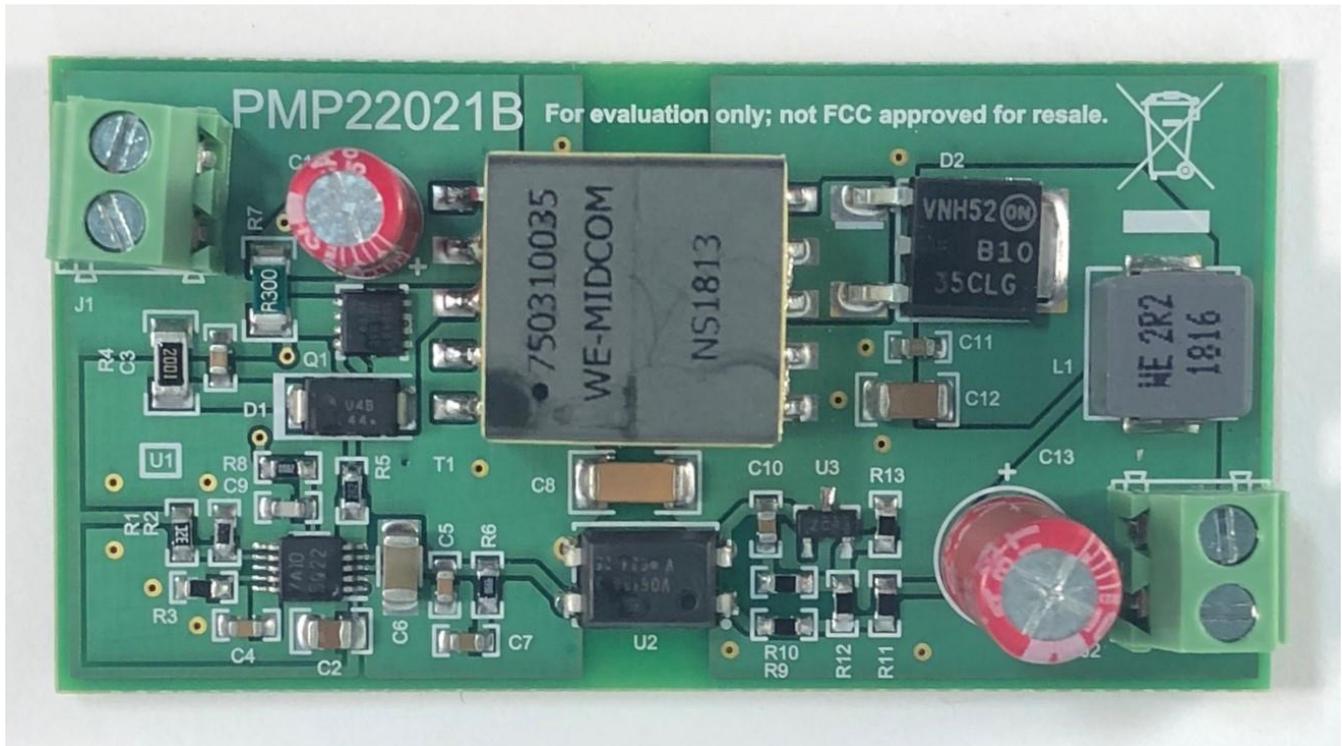


Figure 1. Board Top



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage Range	9 Vdc – 15 Vdc, 12 Vdc nominal
Output Voltage 1	3.3 V +/- 1%
Output Current 1	1.1 A
Switching Frequency	200 kHz

2 Testing and Results

2.1 Efficiency Graphs

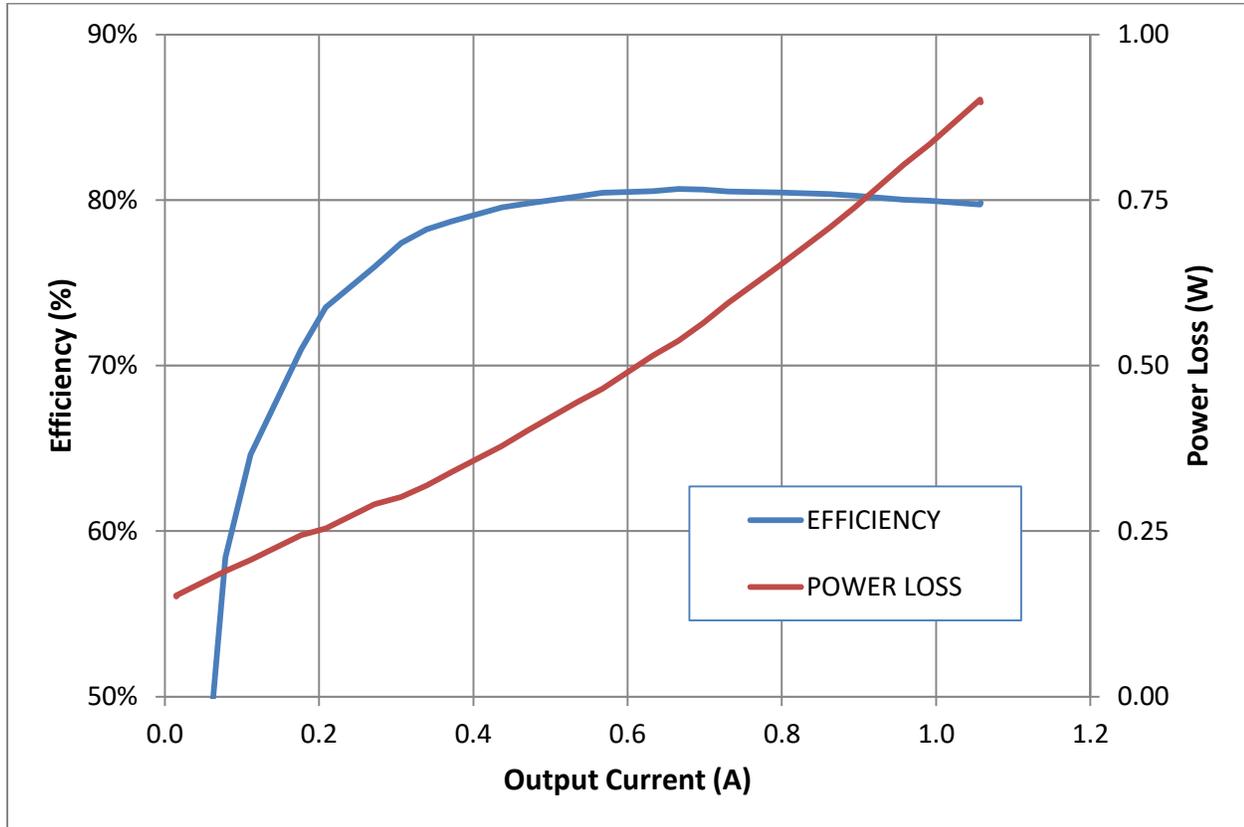


Figure 2. Efficiency with 9 Vdc Input

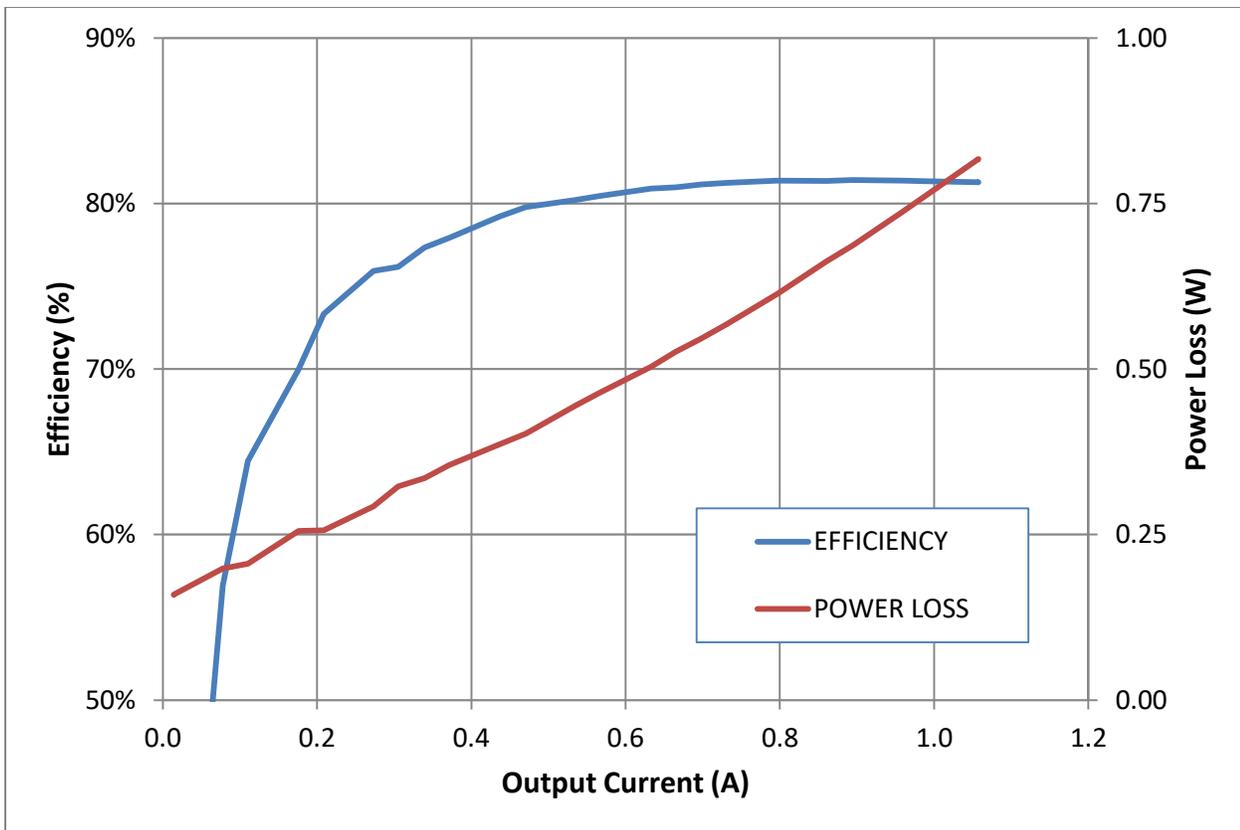


Figure 3. Efficiency with 12 Vdc Input

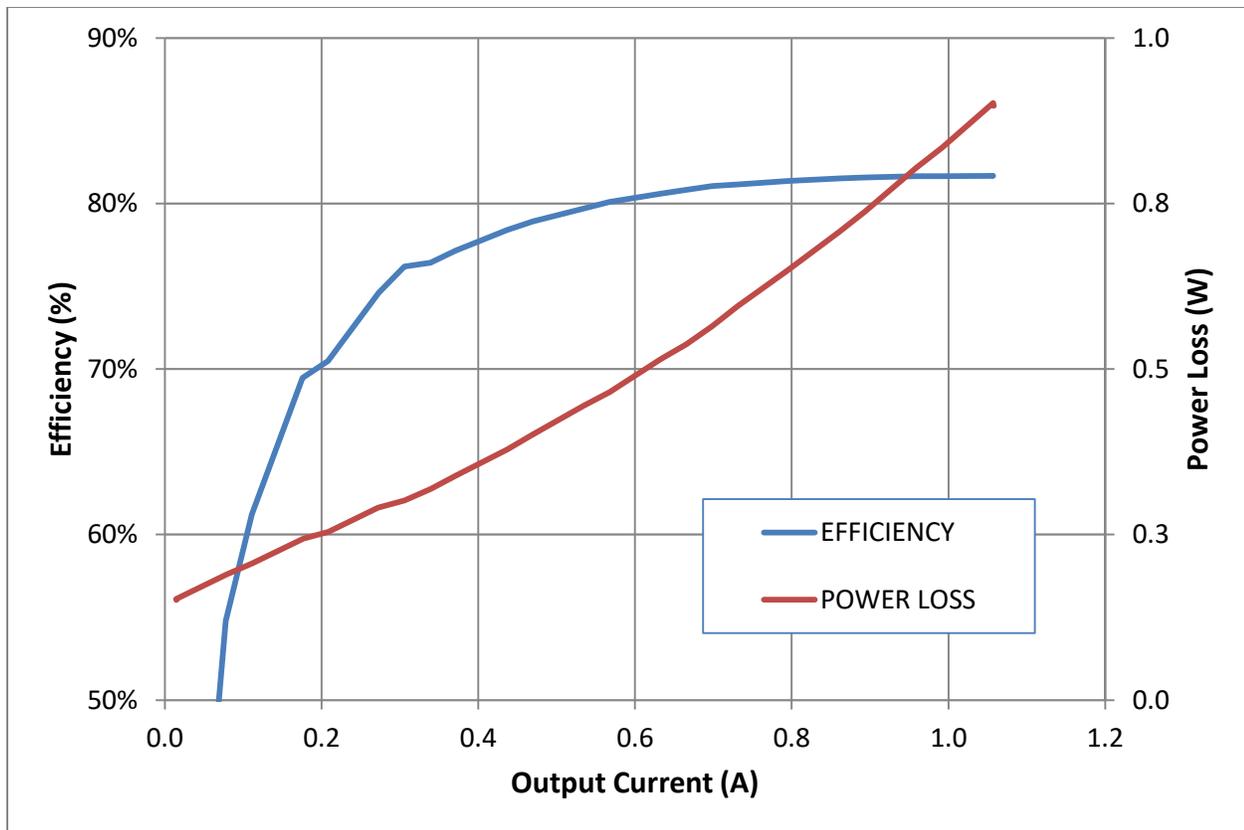


Figure 4. Efficiency with 15 Vdc input

2.2 Efficiency Data

	Input Voltage (V)	Input Current (A)	Input Power (W)	Output Voltage (V)	Output Current (A)	Output Power (W)	Efficiency (%)	Power Loss (W)
9 Vin	8.926	0.023	0.201	3.388	0.015	0.050	24.89	0.151
	8.946	0.135	1.208	3.377	0.272	0.918	75.97	0.290
	8.878	0.253	2.244	3.370	0.534	1.800	80.21	0.444
	8.804	0.378	3.324	3.363	0.795	2.675	80.46	0.649
	8.727	0.510	4.448	3.355	1.058	3.550	79.82	0.898
12 Vin	11.950	0.017	0.207	3.390	0.014	0.048	23.17	0.159
	11.938	0.102	1.215	3.378	0.273	0.922	75.92	0.292
	11.916	0.189	2.246	3.371	0.534	1.802	80.21	0.444
	11.863	0.277	3.291	3.365	0.796	2.678	81.38	0.613
	11.809	0.370	4.367	3.358	1.057	3.550	81.29	0.817
15 Vin	14.969	0.016	0.236	3.391	0.014	0.048	20.47	0.188
	14.725	0.084	1.236	3.379	0.273	0.922	74.59	0.314
	14.938	0.151	2.260	3.372	0.534	1.801	79.70	0.459
	14.897	0.221	3.292	3.366	0.796	2.678	81.37	0.613
	14.855	0.293	4.347	3.360	1.057	3.550	81.66	0.797

Figure 5. Efficiency data from light load, one quarter load, half load, third quarter load, and full load

2.3 Thermal Images

Thermal images were taken after 10 minutes of running with the output at 1.1 A with a 12 Vdc input and no airflow.



Figure 6. Board Top

3 Waveforms

3.1 Switching

The switch node was measured with the main 15 V output at full load.

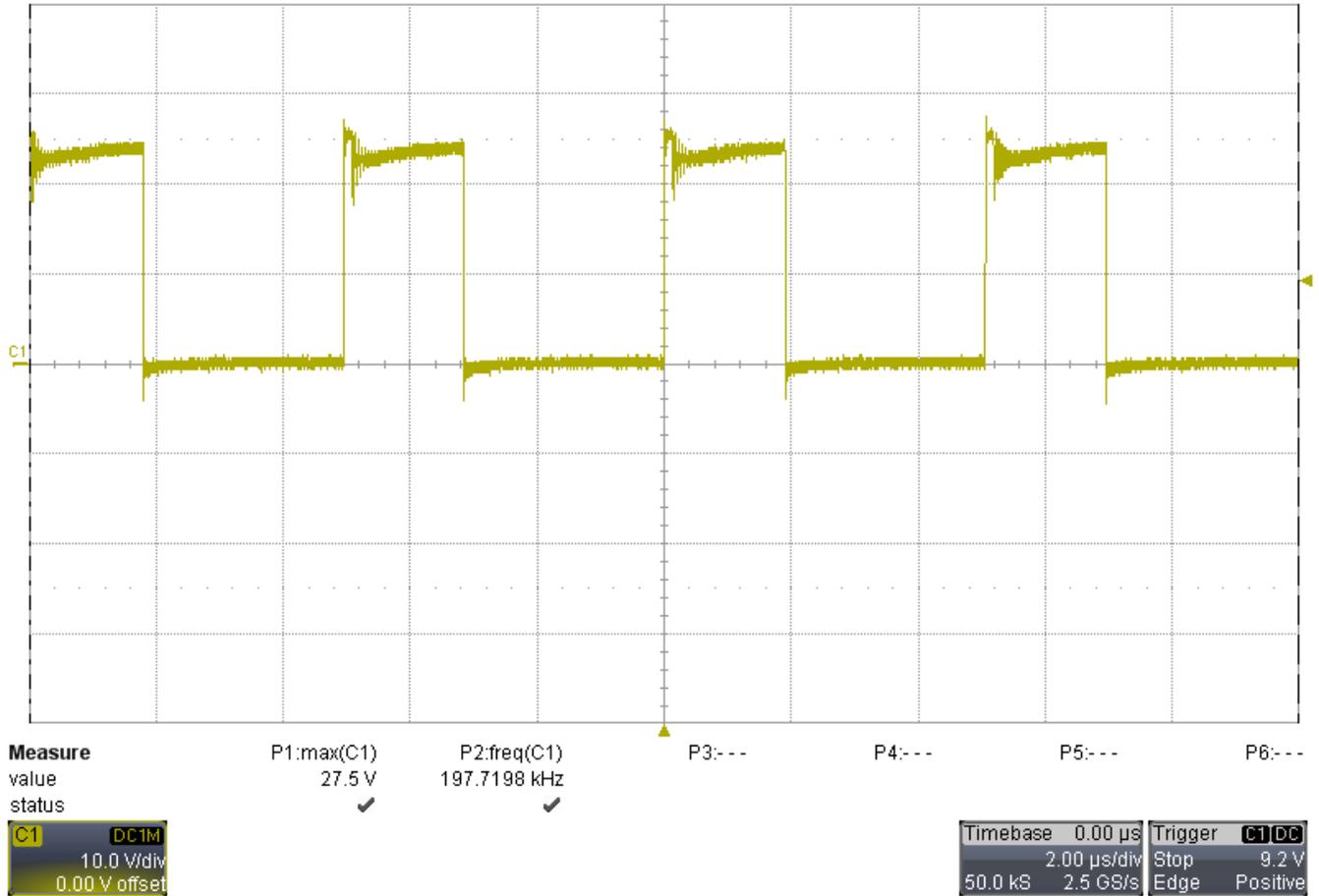


Figure 7. Primary Switching Node with 9 Vdc input

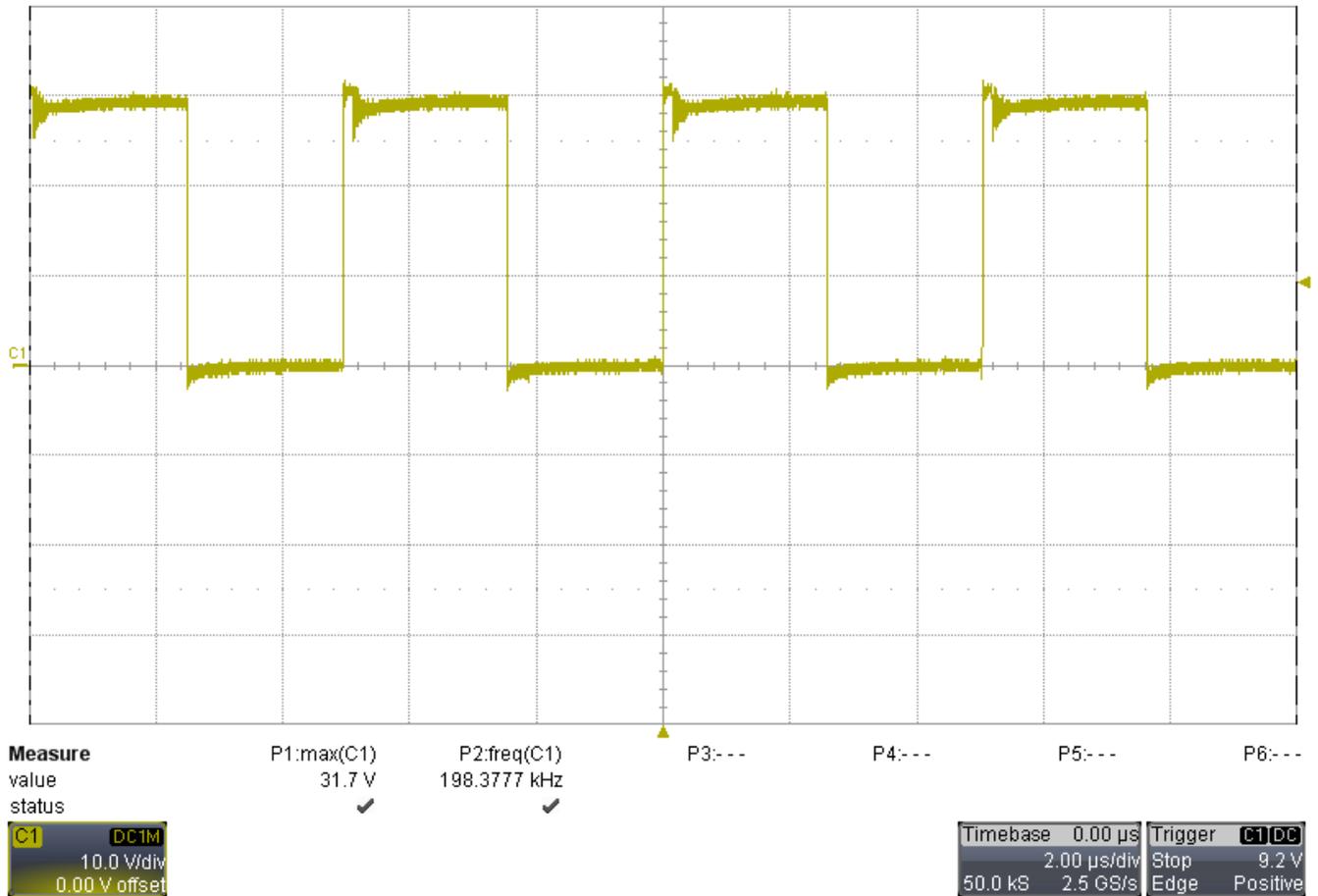


Figure 8. Primary Switching Node with 15 Vdc input

3.2 Output Voltage Ripple

Measurements were taken using the tip and barrel method across the output cap with the output at full load and a 12 Vdc input.

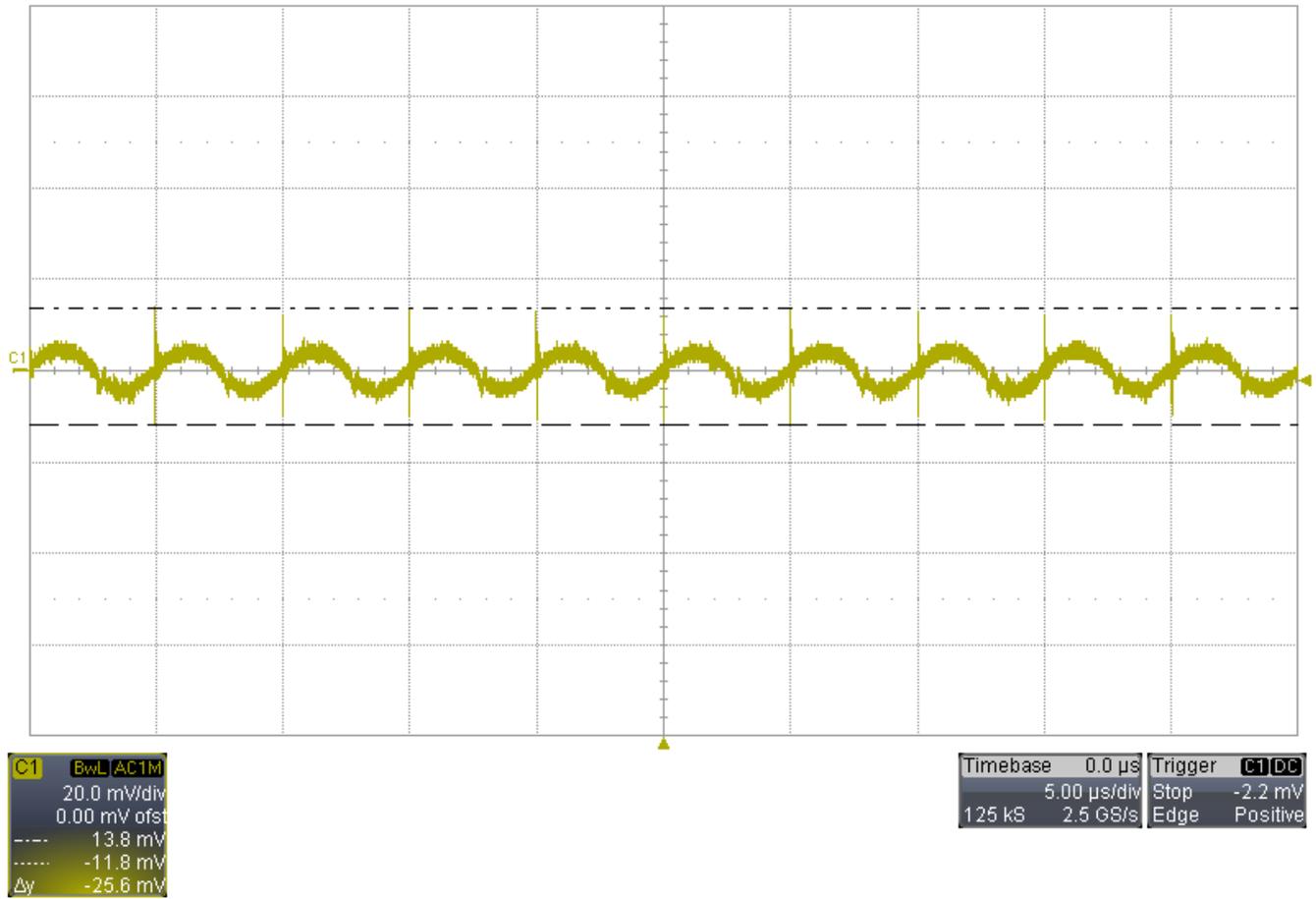


Figure 9.

3.3 Load Transients

For this measurement the output was stepped between 0.1 and 1 A with a 12 Vdc input

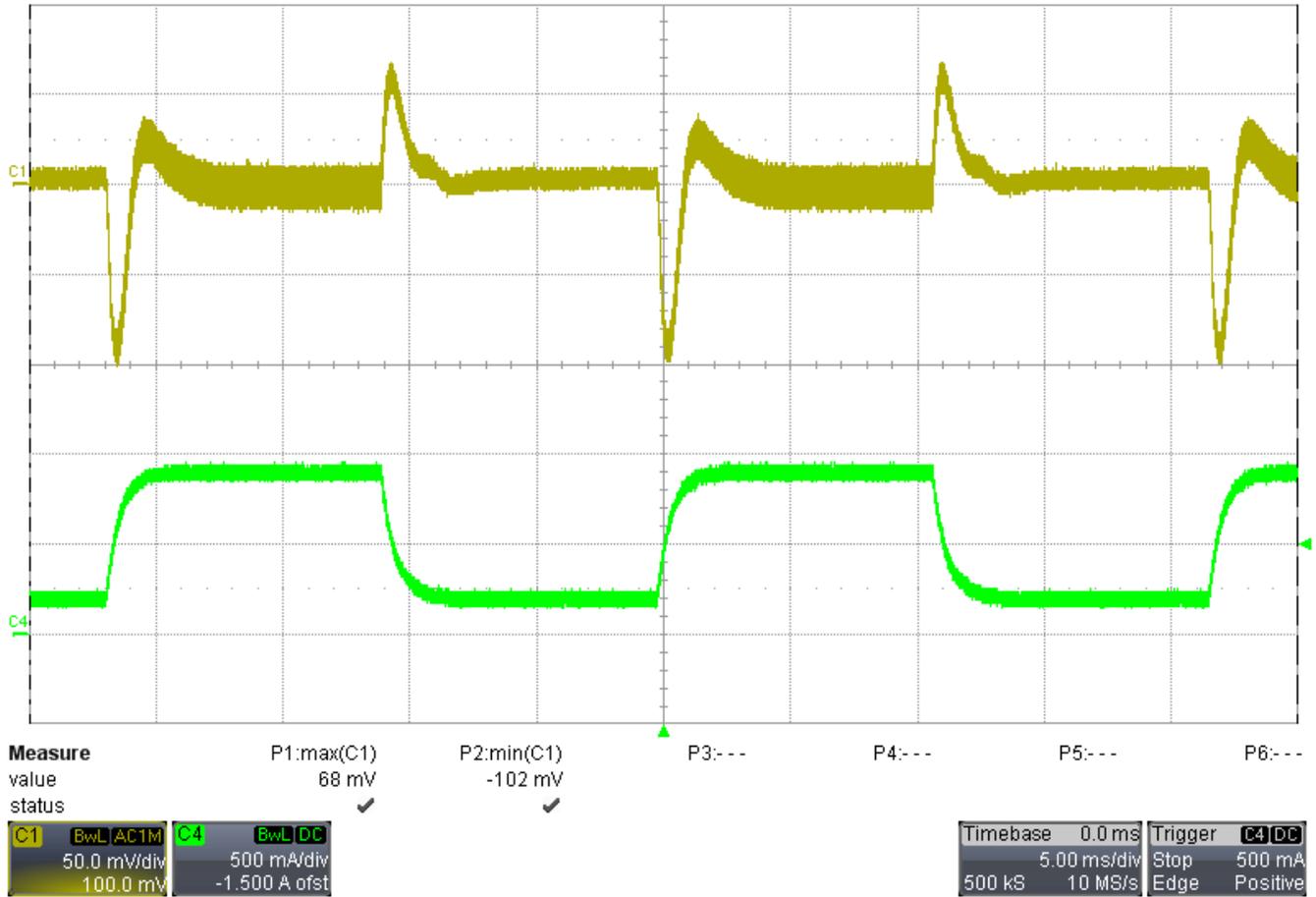


Figure 10.

3.4 Control Loop/Stability

For this measurement the 3.3 V output was loaded to 1.1 A. Measurements are shown for 9 V, 12 V, and 15 V input cases. The table below shows the bandwidth and phase margin measurements for the different input voltages.

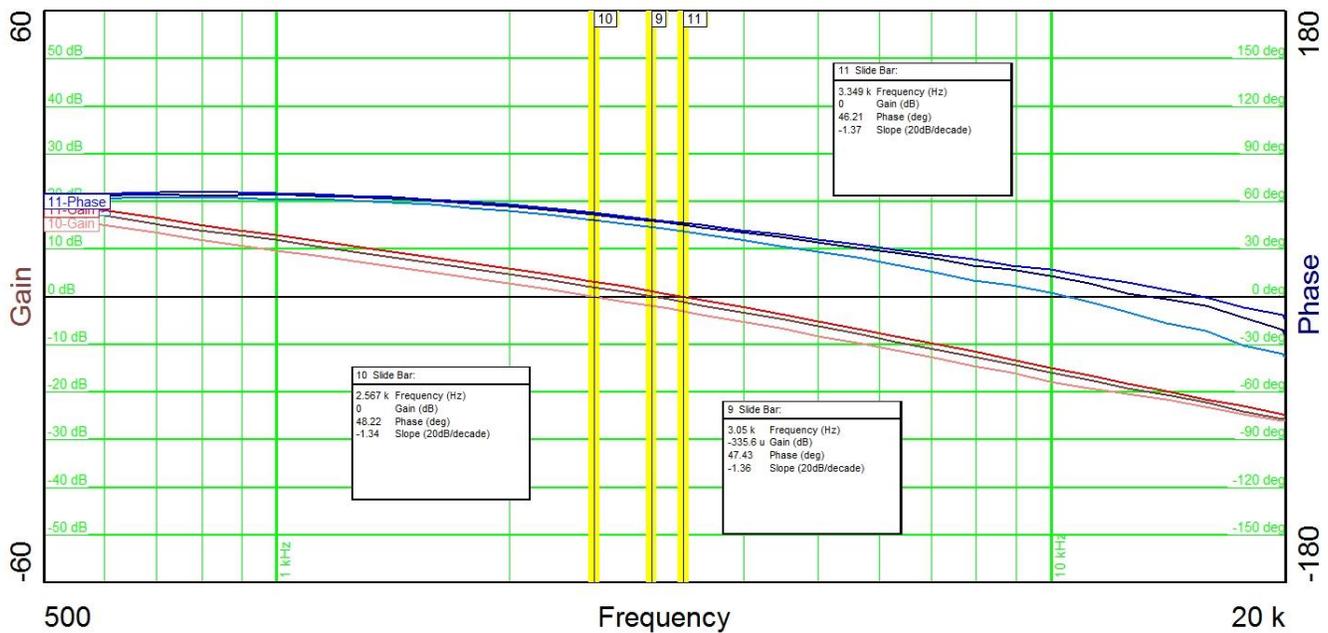


Figure 11.

Input Voltage (V)	Bandwidth (kHz)	Phase Margin (degrees)
9	2.567	48.22
12	3.050	47.43
15	3.349	46.21

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated