

TI Designs: Reference Design Monitoring Voltage Rails on Delfino™ with TPS3702



TI Designs

TI Designs provide the foundation that you need including methodology, testing and design files to quickly evaluate and customize a system. The designs offer the theory, component selection, and simulation of the circuits. TI Designs help you accelerate your time to market

Circuit Description

The C2000™ Delfino™ microcontroller demands a tight tolerance on both of its supply rails; this TI Design monitors the two voltage rails and asserts a reset when either rail is not within its specified supply voltage range. The TPS3702 window comparators monitor for both undervoltage and overvoltage faults on each voltage rail and incorporate glitch immunity and hysteresis to ensure proper resets.


Design Resources

[TI Design Number](#)
[Design Archive](#)
[TPS3702](#)
[TPS62420](#)
[TMS320F28377D](#)
[Other EVMs / TI Designs](#)

Design Folder
All Design files
Product Folder
Product Folder
Product Folder
Tools Folder



 [Ask The Analog Experts](#)
[WEBENCH® Design Center](#)
TI Precision Designs Library



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments
WEBENCH is a registered trademark of Texas Instruments

1 Design Parameters

Table 1: TMS320F28377D Electrical Specifications

| Device | Parameter | Description | Specification | Tolerance | Max Current Consumption |
|----------------------------|-----------|----------------------------|---------------|-----------|-------------------------|
| Delfino Microcontroller | VDD3VFL | Flash power pins | 3.3 V | ± 5 % | 40 mA * |
| | VDDOSC | On-chip crystal oscillator | 3.3 V | ± 5 % | - |
| | VDDIO | Digital I/O power pins | 3.3 V | ± 5 % | 55 mA * |
| | VDDA | Analog power pins | 3.3 V | ± 5 % | 25 mA * |
| | VDD | Digital logic power pins | 1.2 V | ± 5 % | 480 mA * |

* All I/O pins are left unconnected.

Table 2: TPS62420 Electrical Specifications

| Device | Parameter | Description | Specification | Tolerance | Max Current Output |
|----------|-----------|-------------------------------|---------------|-----------|--------------------|
| TPS62420 | VIN | Input voltage | 5 V | | |
| | Vout1 | First channel output voltage | 3.3 V | ± 1% | 600 mA |
| | Vout2 | Second channel output voltage | 1.2 V | ± 1% | 1000 mA |

2 Theory of Operation

The Delfino™ microcontroller, TMS320F28377D, requires two supply voltage rails for operation: 3.3 V and 1.2 V. There is a $\pm 5\%$ tolerance associated with each rail, as shown in Table 1. An adjustable dual DC/DC converter, TPS62420, was selected to generate both rails. To ensure that each rail is within its specified range, both are monitored by a window voltage detector, TPS3702, which features undervoltage (UV) and overvoltage (OV) detection. Any deviation from the specified supply voltage range will trigger a reset signal that will be read by the microcontroller.

In order to power up the microcontroller properly, the 3.3 V rail needs to be powered on first, followed by the 1.2 V rail, as shown in Figure 2. To do this, a resistor and capacitor were placed on the second channel enable pin, EN2, of the TPS62420, creating an RC delay between the start of each rail's ramp, as shown in Figure 3. A diode was also added between the two output rails to ensure that the 3.3 V rail is always higher than the 1.2 V rail per specification.

In order to monitor both rails simultaneously, both window comparators' OV outputs are wire-OR'ed to a general purpose input/output (GPIO) pin of the microcontroller. When the microcontroller reads a low output signal (OV is active-low), it will run an interrupt to hold the microcontroller in reset until normal operating conditions resume. The UV outputs of each TPS3702 are also wire-OR'ed and connected directly to the microcontroller's reset pin, asserting a system reset when an undervoltage condition is detected on either rail.

2.1 Design

2.1.1 Sense Accuracy

The TMS320F28377D specifies a $\pm 5\%$ tolerance for both of its supply rails. A $\pm 5\%$ tolerance for the 3.3 V rail specifies a range from 3.13 V to 3.46 V. The TPS3702 monitors various voltages including 3.3 V. It also features two built-in window threshold options that can be chosen by setting the SET pin high or low. The TPS3702CX33 was selected with the SET pin pulled high to enable the $\pm 4\%$ window threshold option. This yields a nominal overvoltage threshold of 3.17 V and a nominal undervoltage threshold of 3.43 V. However, once the $\pm 0.9\%$ tolerance for each of the thresholds is factored in, the overvoltage threshold voltage may vary from 3.40 V to 3.46 V depending on system conditions. The undervoltage threshold can vary from 3.14 V to 3.19 V. This is depicted in Figure 1. Setting the thresholds in this manner prevents the voltage rail from deviating outside the specified $\pm 5\%$ without triggering a reset.

The same approach was used when selecting TPS3702CX12 to monitor the 1.2 V rail.

 


Figure 1: TPS3702 voltage thresholds

For more information on TPS3702 device selection, please refer to the [Device Nomenclature section of the TPS3702 datasheet](#).

2.1.2 Pull Up Resistor Sizing for Current Consumption

The TPS3702 features open drain outputs that require a pull-up resistor from their output pins to the desired pull-up voltage. The pull-up resistance is typically in the range of 10 k Ω – 1 M Ω . Higher resistance keeps current consumption low. Take, for example, a resistor of 10k Ω pulled up to 3.3 V; when the signal is active there will be a current draw of 0.33 mA.

In this design, however, it is not expected that the signal will be active for long periods of time. Therefore, current consumption is not a pressing concern. Instead, 2.2 k Ω resistors were used resulting in a current draw of 1.5mA. This was done deliberately to boost immunity to noise. Due to concerns of electromagnetic interference, the current was increased to limit the chances of a false signal being read by the microcontroller.

2.1.3 Enabling an Interrupt

Both fault conditions, undervoltage and overvoltage, are monitored by the microcontroller. The undervoltage output signal is directly connected to the microcontroller's reset pin. The overvoltage output signal, on the other hand, is connected to a GPIO set up as an external interrupt. Another option is to launch a non-maskable interrupt when an overvoltage condition occurs. This can commence shutdown routines and hold the microcontroller in an internally initialized reset.

A sample code to initialize an external interrupt can be found in the appendix.

3 Component Selection

3.1 *TPS3702*

The TPS3702 is an integrated overvoltage and undervoltage window detector. It has high threshold accuracy (0.9% max) which facilitates proper resets. A SET pin, which can be pulled high or low, allows the user to change the width of the window, i.e. the overvoltage and undervoltage thresholds. It is also equipped with a built-in hysteresis to prevent oscillatory behavior on the rail from affecting the reset signal. Built-in glitch immunity prevents transient voltage spikes from triggering an unnecessary reset signal.

The TPS3702CX33 is used to monitor the 3.3 V rail. The SET pin is pulled high so the undervoltage and overvoltage thresholds correlate to a $\pm 4\%$ window. There is a 0.55% nominal hysteresis associated with both the undervoltage and overvoltage thresholds.

The TPS3702CX12 is used to monitor the 1.2 V rail. The SET pin is pulled high so the undervoltage and overvoltage thresholds correlate to a $\pm 4\%$ window. There is a 0.55% nominal hysteresis associated with both the undervoltage and overvoltage thresholds.

For more information on TPS3702 device selection, please refer to the [Device Nomenclature section of the TPS3702 datasheet](#).

3.2 *TMS320F28377D Delfino™ Microcontroller*

The Delfino™ TMS320F2837xD is a powerful 32-bit floating-point microcontroller unit (MCU) designed for advanced closed-loop control applications such as industrial drives and servo motor control; solar inverters and converters; digital power; transportation; and power line communications.

3.3 *TPS62420*

The TPS62420 is DC/DC converter that generates two voltage rails. It has independent enable pins for each channel which are necessary to achieve the required power up sequence for the microcontroller. It also features a power save mode at light current loads and an easy scale interface function which can change the output voltage of either rail through a serial interface. It operates at 95% peak efficiency.

4 Simulation

No TINA simulations were generated for this project.

4.1 Timing Diagram

 


Figure 2: System timing diagram

4.2 Block Diagram

 


Figure 3: Block diagram showing UV and OV detection

5 Measurements and Verification

 


Figure 4: Start-Up

 


Figure 5: Reset asserted for an undervoltage fault on the 3.3 V rail

 


Figure 6: Reset asserted for an overvoltage fault on the 3.3 V rail

 


Figure 7: Reset asserted for an undervoltage fault on the 1.2 V rail

 


Figure 8: Reset asserted for an overvoltage fault on the 1.2 V rail

 


Figure 9: Shut-down

 


Figure 10: Brownout condition – 5 V input voltage dropping to 2.4 V for 10 µs

 


Figure 11: Slow shut down with diode maintaining bias between 3.3 V and 1.2 V rails

6 About the Author

Cynthia Sosa is an Applications Engineer in the Linear Power business unit since she joined TI. She received her BSEE from the University of Texas at El Paso.

7 Acknowledgements & References

1. [TPS3702 Datasheet](#)
2. [TMS320F28377D Datasheet](#)
3. [TMS320F2837xD Technical Reference Manual](#)
4. [TPS62420 Datasheet](#)

I would like to thank Brett Larimore and his team for their immense knowledge and William Stevers for his immense support. Also to my own team members, especially Kyle Van Renterghem for being so willing to take on this project and all that came with it.

Appendix A.

A.1 Schematic

 


Figure A-1: Page 1 of electrical schematic

 


Figure A-2: Page 2 of electrical schematic

A.2 Sample Test Code

```

// FILE: OverVoltageInterrupt.c

// TITLE: Soprano Example External Interrupt Test Program.

// This program sets up GPIO0 as XINT1. A GPIO signal is used to trigger the interrupt
// GPIO30 triggers XINT1, jumper this two pins together

// User needs to externally connect these pins for the program to work properly.

// XINT1 input is synced to SYSCLKOUT.

// When the ISR is triggered, it will flag OverVoltageFlag to 1 (default is 0)

// The interrupt is only fired once -- if ResetOverVoltageISR is set to 1 in the // watch window (the default), //
the OverVoltageFlag will clear and the ISR will // be reenabled.

// ResetOverVoltageISR (default 1) activates the ISR if set to 0, resets ISR when set to 1. 0 simulates the
desired fail condition.

////////////////////////////////////

#include "F28x_Project.h" // Device Headerfile and Examples Include File

interrupt void xint1_isr(void); // Prototype statements for functions found // // within this file.

// Global variables for this example

volatile Uint32 Xint1Count;

Uint32 LoopCount,OverVoltageFlag,ResetOverVoltageISR;

void main(void)
{
    InitSysCtrl() // Initialize System Control:
    DINT; // Disable CPU interrupts

// Initialize PIE control registers to their default state, all PIE interrupts disabled and flags are cleared.
    InitPieCtrl();

// Disable CPU interrupts and clear all CPU interrupt flags:
    IER = 0x0000;
    IFR = 0x0000;

// Initialize the PIE vector table with pointers to the shell Interrupt
// Service Routines (ISR).
    InitPieVectTable();
  
```

```

// Interrupts that are used in this example are re-mapped to ISR functions found within this file.
EALLOW;           // This is needed to write to EALLOW protected registers
PieVectTable.XINT1_INT = &xint1_isr;
EDIS;             // This is needed to disable write to EALLOW protected registers

// User specific code, enable interrupts:
// Clear the variables
Xint1Count = 0;   // Count XINT1 interrupts, used with resetISR to limit the number of ISR calls to //
one per "over-voltage" event
OverVoltageFlag = 0; // ISR flag (default is 0)
ResetOverVoltageISR = 1;

// Enable XINT1 in the PIE: Group 1 interrupt 4
// Enable INT1 which is connected to WAKEINT:
PieCtrlRegs.PIECTRL.bit.ENPIE = 1; // Enable the PIE block
PieCtrlRegs.PIEIER1.bit.INTx4 = 1; // Enable PIE Group 1 INT4
IER |= M_INT1; // Enable CPU INT1
EINT; // Enable Global Interrupts

// GPIO0 is an input
EALLOW;
GpioCtrlRegs.GPAMUX1.bit.GPIO0 = 0; // GPIO
GpioCtrlRegs.GPADIR.bit.GPIO0 = 0; // input
GpioCtrlRegs.GPAQSEL1.bit.GPIO0 = 0; // XINT1 Synch to SYSCLKOUT only
EDIS;

// GPIO30 is an output, starts high
EALLOW;
GpioDataRegs.GPASET.bit.GPIO30 = 1; // Load the output latch (high)
GpioCtrlRegs.GPAMUX2.bit.GPIO30 = 0; // GPIO
GpioCtrlRegs.GPADIR.bit.GPIO30 = 1; // output
EDIS;

```

```
// GPIO0 is XINT1
GPIO_SetupXINT1Gpio(0);

// Configure XINT1
XintRegs.XINT1CR.bit.POLARITY = 0;    // Falling edge interrupt

// Enable XINT1
XintRegs.XINT1CR.bit.ENABLE = 1;

while(1)
{
    LoopCount++;
    // ResetOverVoltageISR can be set in the watch window
    if(OverVoltageFlag == 1 && ResetOverVoltageISR == 1)
    {
        OverVoltageFlag = 0;
        GpioDataRegs.GPASET.bit.GPIO30 = 1;           // raise GPIO30 (disabling ISR)
        PieCtrlRegs.PIEACK.all = PIEACK_GROUP1;      // reenable interrupt
    }
    else if(ResetOverVoltageISR == 0)
    {
        GpioDataRegs.GPACLEAR.bit.GPIO30 = 1;
        // take GPIO0 low, triggers ISR (this simulates the "over-voltage" condition)
    }
}

// Insert all local Interrupt Service Routines (ISRs) and functions here:
// If local ISRs are used, reassign vector addresses in vector table
interrupt void xint1_isr(void)
{
    Xint1Count++;    // counts the number of ISR triggers-- the ISR should ONLY be triggered when an //
    "over-voltage" is detected
}
```

```
OverVoltageFlag = 1; // flags the "over-voltage" condition
// User specific requirements to correct the condition would be placed here
}
```

A.3 Test and Measurements

 


Figure A-3: Load Transient Response – 0 mA to 500 mA on 3.3 V rail

 


Figure A-4: Load Transient Response – 77 mA to 140 mA on 3.3 V rail

 


Figure A-5: Load Transient Response – 0 mA to 250 mA on 1.2 V rail

 


Figure A-6: Load Transient Response – 250 mA to 400 mA on 1.2 V rail.

 


Figure A-7: Load Transient Response – 30 mA to 480 mA on 1.2 V rail

 


Figure A-8: Reset asserted while 3.3V rail is low and 1.2V rail is high

 


Figure A-9: Reset asserted while 3.3V rail is high and 1.2V rail is low

 


Figure A-10: Displaying how low 3.3V rail reaches until reset is asserted.

Appendix B.

B.1 Bill of Materials



| Item | Qty | Reference | Value | Part Description | Manufacturer | Manufacturer Part Number | Alternate Part | PCB Footprint |
|------|-----|---|---------|---|-----------------------|--------------------------|----------------|--------------------------|
| 1 | 6 | C1, C5, C7, C8, C10, C11 | 10 µF | CAP, CERM, 10 µF, 25 V, +/- 20%, X5R, 0603 | TDK | C1608X5R1E106M080AC | | C1608X5R1E106M080AC |
| 2 | 2 | C2, C4 | 22 µF | CAP, CERM, 22 µF, 10 V, +/- 20%, X5R, 0603 | TDK | | | |
| 3 | 1 | C3 | 33 pF | CAP, CERM, 33 pF, 100 V, +/- 5%, COG/NPO, 0603 | AVX | 06031A3301AT2A | | 06031A3301AT2A |
| | | C6, C9, C16, C17, C18, C19, C20, C21, C22, C23, C24, C25, C26, C27, C28, C29, C30, C31, C32, C33, C34, C35, C36, C37, C38, C39, C40, C41, C42, C43, C44, C45, C46, C47, C48, C49, C50, C51, C54, C55, C56, C57, | | | | | | |
| 9 | 44 | C58, C59 | 0.1 µF | CAP, CERM, 0.1 µF, 16 V, +/- 20%, X7R, 0603 | Kemet | C0603C104M4RACTU | | C0603C104M4RACTU |
| 10 | 4 | C12, C13, C14, C15 | 2.2 µF | CAP, CERM, 2.2 µF, 25 V, +/- 10%, X5R, 0402 | TDK | C1005X5R1E225K0508C | | C1005X5R1E225K0508C |
| 11 | 2 | C52, C53 | 15 pF | CAP, CERM, 15 pF, 50 V, +/- 5%, COG/NPO, 0402 | MuRata | GRM1555C1H150JA01D | | GRM1555C1H150JA01D |
| 12 | 1 | D1 | | Diode, Schottky, 20 V, 0.5 A, 1.0x0.35x0.6mm | Central Semiconductor | CFSH05-20L CT-ND | | CFSH05-20L TR |
| 13 | 1 | J1 | | Header, 2x7 pin, 100mil spacing, Straight, 4 Wall | 3M | 2514-6002UB | | HEADER_14PJTAG |
| 14 | 1 | L1 | 2.2 µH | Inductor, Drum Core, Ferrite, 2.2 µH, 1 A, 0.11 ohm, SMD | Bourns | SRU2016-2R2Y | | SRU2016-2R2Y |
| 15 | 1 | L2 | 3.3 µH | Inductor, Drum Core, Ferrite, 3.3 µH, 0.6 A, 0.32 ohm, SMD | Bourns | SRU2009-3R3Y | | SRU2009-3R3Y |
| 16 | 2 | L3, L4 | 220 ohm | Ferrite Bead, 220 ohm @ 100 MHz, 0.2 A, 0402 | MuRata | BLM158B221SN1D | | BLM158B221SN1D |
| 17 | 2 | L5, L6 | 60 ohm | Ferrite Bead, 60 ohm @ 100 MHz, 3.5 A, 0603 | TDK | MPZ1608S600A | | MPZ1608S600A |
| 18 | 1 | R1 | 0 | RES, 0, 5%, 0.063 W, 0402 | Vishay-Dale | CRCW04020000Z0ED | | CRCW04020000Z0ED |
| 19 | 1 | R2 | 806 k | RES, 806 k, 1%, 0.125 W, 0805 | Vishay-Dale | CRCW0805806KFKEA | | CRCW0805806KFKEA |
| 20 | 1 | R3 | 178 k | RES, 178 k, 1%, 0.125 W, 0805 | Vishay-Dale | CRCW0805178KFKEA | | CRCW0805178KFKEA |
| 21 | 1 | R4 | 205 k | RES, 205 k, 1%, 0.125 W, 0805 | Vishay-Dale | CRCW0805205KFKEA | | CRCW0805205KFKEA |
| 22 | 1 | R5 | 200 k | RES, 200 k, 1%, 0.125 W, 0805 | Vishay-Dale | CRCW0805200KFKEA | | CRCW0805200KFKEA |
| 23 | 1 | R6 | 22.0 k | RES, 22.0 k, 1%, 0.1 W, 0603 | Yageo America | RC0603FR-0722KL | | RC0603FR-0722KL |
| 24 | 1 | R7 | 39 | RES, 39, 5%, 0.063 W, 0402 | Vishay-Dale | CRCW040239R0JNED | | CRCW040239R0JNED |
| 25 | 4 | R8, R10, R11, R12 | 2.20 k | RES, 2.20 k, 1%, 0.1 W, 0603 | Yageo America | RC0603FR-072K2L | | RC0603FR-072K2L |
| 26 | 1 | R9 | 10.0k | RES, 10.0 k, 1%, 0.063 W, 0402 | Vishay-Dale | CRCW040210K0FKED | | CRCW040210K0FKED |
| 27 | 0 | R13 | DNP | RES, 5%, 0.063 W, 0402 | | CRCW040210K0FKED | | CRCW040210K0FKED |
| 28 | 1 | U1 | | Dual-Core Delfino Microcontroller, PTP0176F | Texas Instruments | TMS320F28377DPTP | | TMS320F28377DPTP |
| 29 | 1 | U2 | | Buck Adjustable Regulator with 2.5 to 6 V Input and 0.6 to 6 V Output | Texas Instruments | TPS62420DRCR | | TPS62420DRCR |
| 30 | 1 | U3 | | High-Accuracy, Fixed-Threshold OV/UV Monitor, DDC0006A | Texas Instruments | TPS3702CX33DDCR | | TPS3702CX33DDCR |
| 31 | 1 | U4 | | High Accuracy Fixed Threshold OV/UV Monitor, DDC0006A | Texas Instruments | TPS3702CX12DDC | | TPS3702CX12DDC |
| 32 | 1 | Y2 | | Crystal, 20 MHz, 10 pF, SMD | Abracon Corporation | ABM38-20.000MHZ-10-1-U-T | | ABM38-20.000MHZ-10-1-U-T |

Figure B-1: Bill of Materials

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.