

TIDA-00657 Test Report

Wang Li

BMS/HPC

Abstract

TI design TIDA-00657 is an SMBus 1- to 4-cell hybrid power boost mode battery charge controller with power and processor hot monitoring. The input voltage range is between 4.5 V and 24V, with a programmable output of 1–4 cells charge voltage and 128-mA to 8.128-A charge current. The first application circuit illustrates how [bq24780S](#) can be implemented. The [second applications circuit](#) shows how pairing the bq24780S with the [ADS7924](#) allows for autonomous monitoring of the analog output pins of the battery charger and provides a threshold alarm to the overall system.

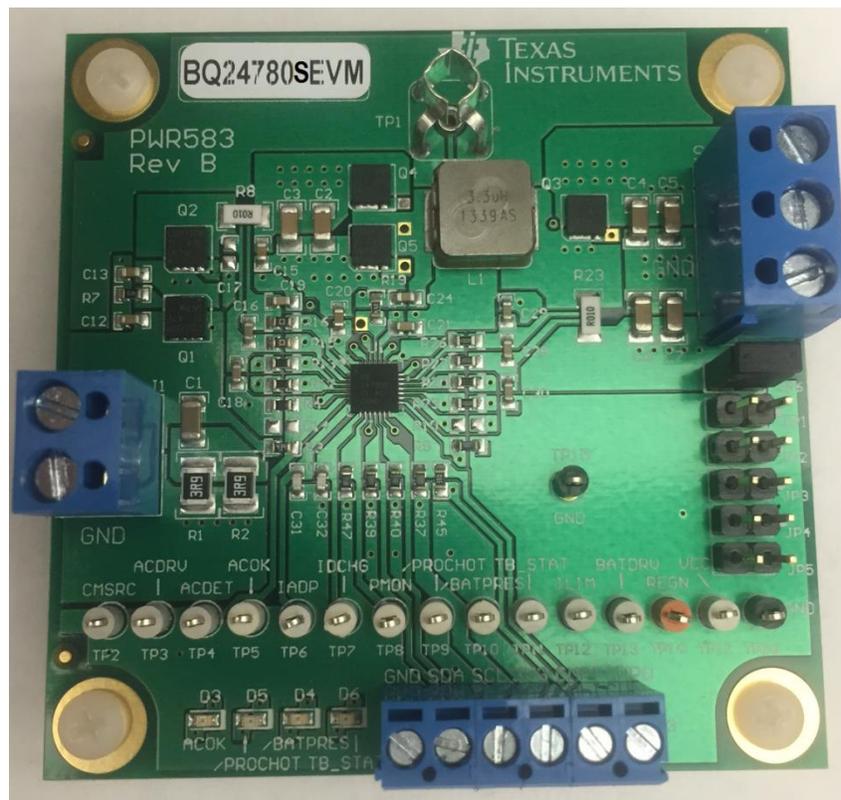


Figure 1. Board Photo

Document History

| Version | Date | Author | Notes |
|---------|---------|--------------|----------------------|
| 1.0 | 07/2015 | Wang Li | First release |
| 2.0 | 9/14/17 | Cynthia Sosa | Implementing ADS7924 |

WARNING: EXPORT NOTICE

Recipient agrees to not knowingly export or re-export, directly or indirectly, any product or technical data (as defined by the U.S., EU, and other Export Administration Regulations) including software, or any controlled product restricted by other applicable national regulations, received from Disclosing party under this Agreement, or any direct product of such technology, to any destination to which such export or re-export is restricted or prohibited by U.S. or other applicable laws, without obtaining prior authorization from U.S. Department of Commerce and other competent Government authorities to the extent required by those laws. This provision shall survive termination or expiration of this Agreement.

According to our best knowledge of the state and end-use of this product or technology, and in compliance with the export control regulations of dual-use goods in force in the origin and exporting countries, this technology is classified as follows:

US ECCN: 3E991

EU ECCN: EAR99


And may require export or re-export license for shipping it in compliance with the applicable regulations of certain countries.

Bench Set up

- TIDA-00657 was tested on a bench setup using bq24780SEVM-583. The test equipment are as follows:
 - Oscilloscope: Tektronix TDS5054B
 - Passive Voltage Probes: Tektronix P6139A – 500 Mhz, 8 pF, 10 MΩ, 10x
 - Current Probe: Tektronix TCP202A Current Probe
 - Power Supply: Agilent E3634A 25V/7A, KEPCO BOP36-6M 36V/6A; 3.3V/1A bias supply
 - Electronic Load: HP 6060B 60V/6A
 - Multi-meter: HP 34401A

Application Circuits

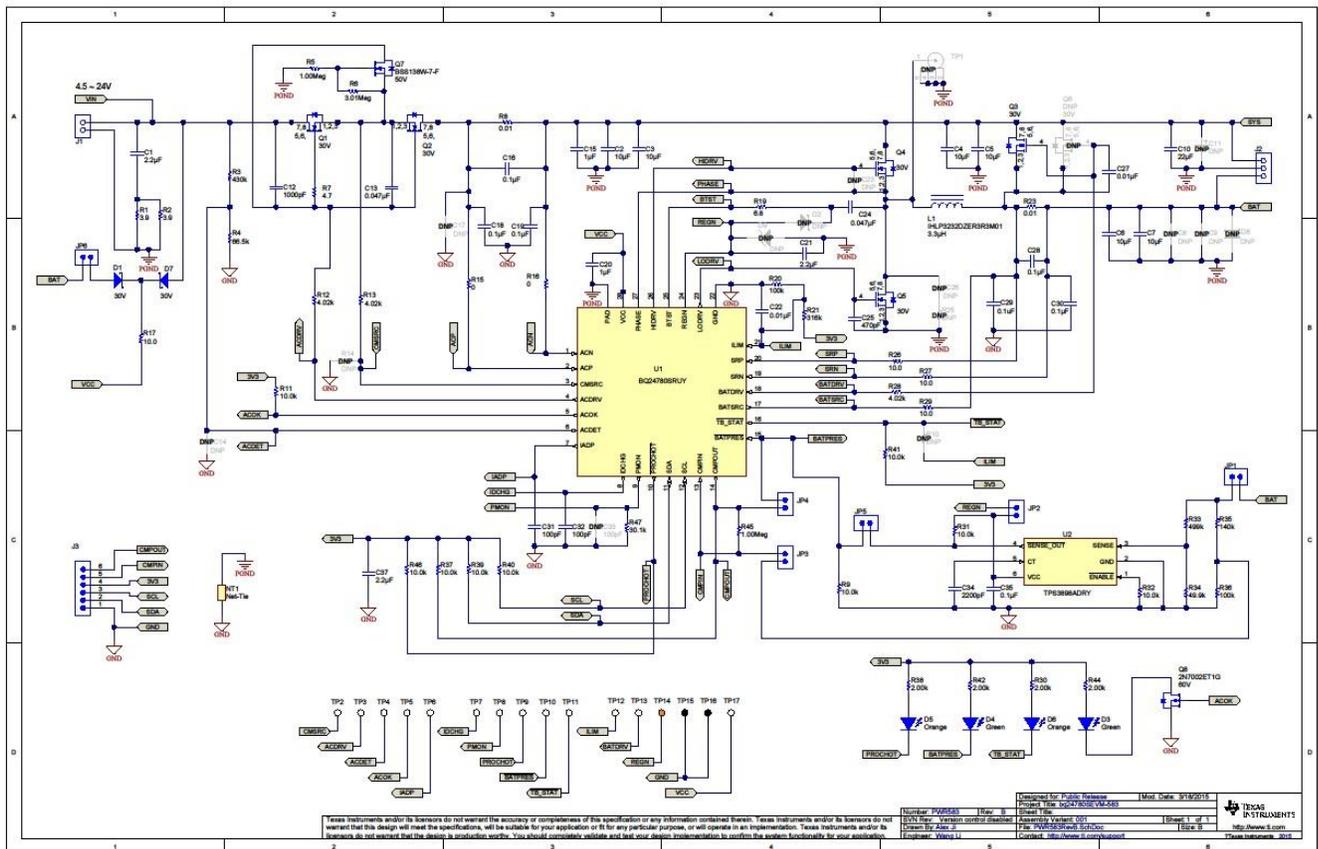- The application circuit shown in Figure 2 illustrates the implementation of a Li-Ion battery charger using bq24780S.



Efficiency

- Figure 3 shows the charging efficiency across the charge current range with the bq24780S at 25°C.

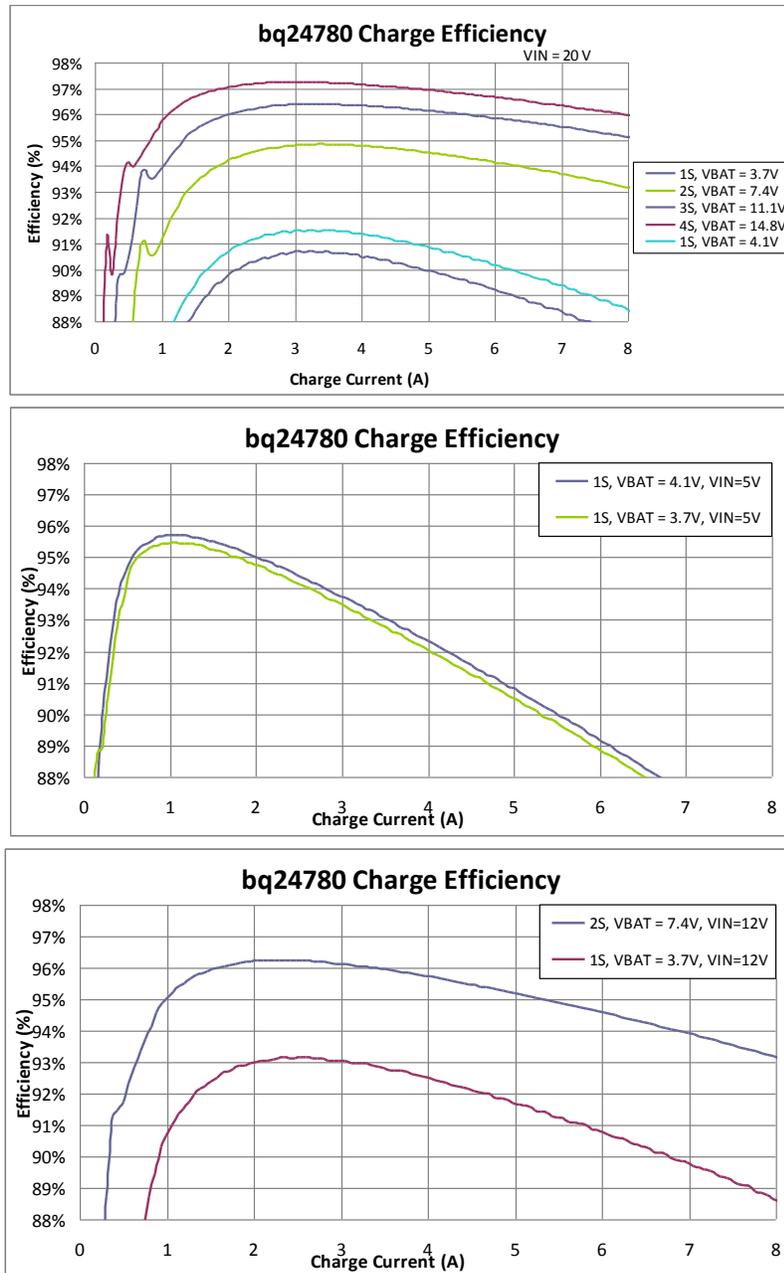


Figure 3. TIDA-00657 Charging Efficiency

Accuracy

- Figure 4 shows the bq24780S charge voltage accuracy across at 25°C

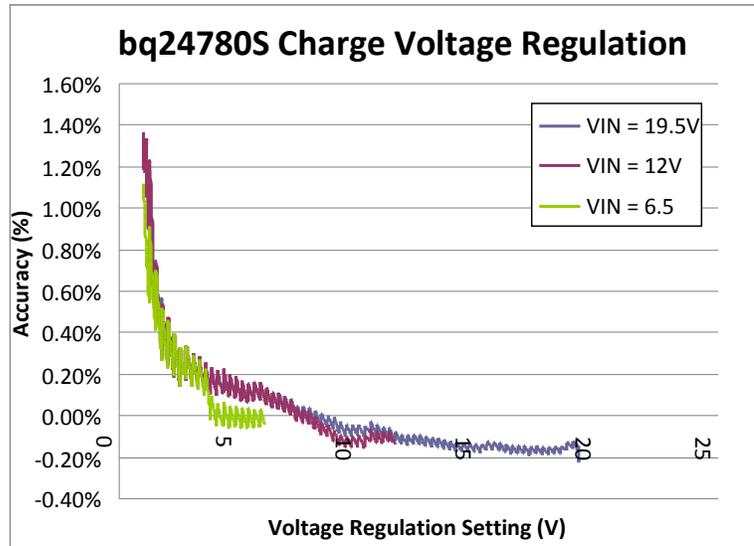


Figure 4. TIDA-00657 Charge Voltage Accuracy

- Figure 5 shows the bq24780S charge current accuracy at 25°C.

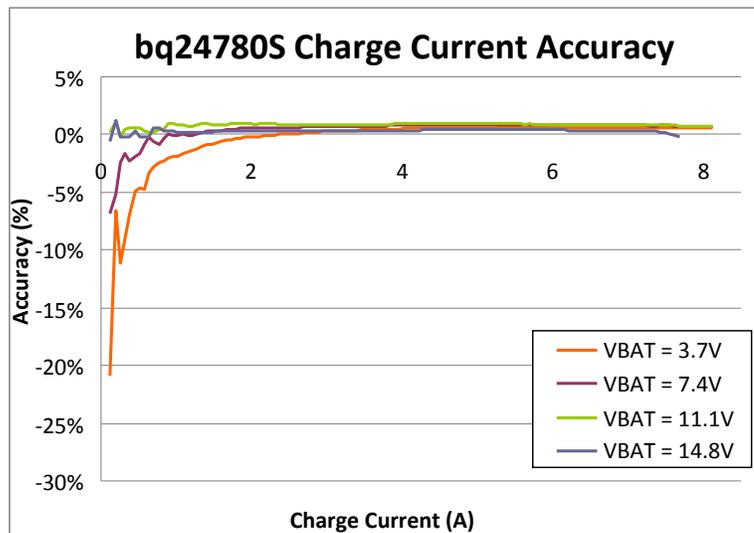


Figure 5. TIDA-00657 Charge Current Accuracy

- Figure 6 shows the bq24780S input current accuracy at 25°C.

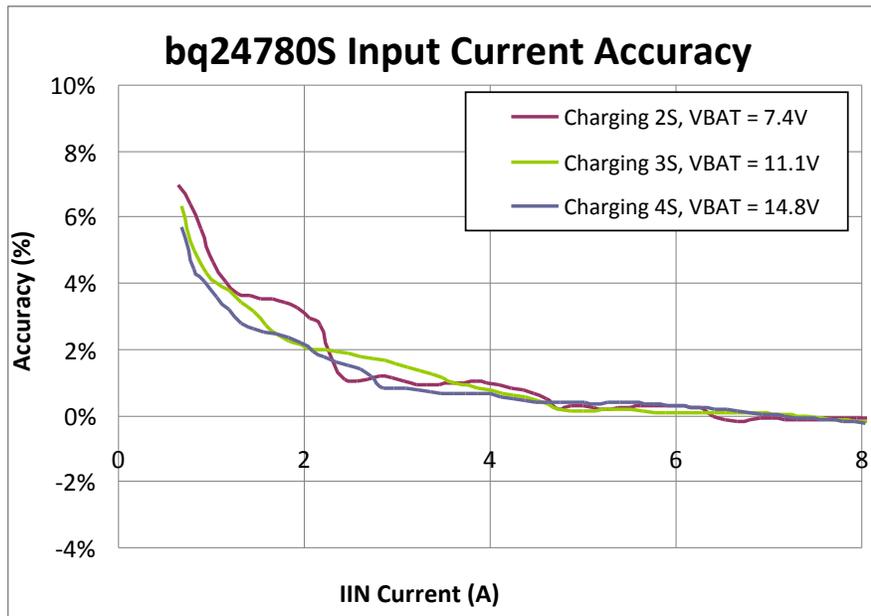


Figure 6. TIDA-00657 Input Current Accuracy

PMON Functions

- BATFET System Reset

PMON pin output current is proportional to the total power from the adapter and battery. The ratio is selectable through SMBus. Place a resistor from PMON pin to GND to generate PMON voltage. The resistor value is set so that the PMON voltage at peak system load doesn't exceed 3V. The PMON output voltage is clamped to 3.3 V. Place a 100-pF (or less) ceramic decoupling capacitor from PMON pin to GND. This pin can be floating if this output is not in use.

$$I_{PMON} = K_{PMON} \times (V_{IN} \times I_{IN} - V_{BAT} \times I_{BAT}) \quad (1)$$

IBAT>0 during battery charging, IBAT<0 during battery discharging

K_{PMON}: PMON Gain, REG0x3B[9]

Table 2. ChargeOption1 Register (REG0x3BH)

| BIT | BIT NAME | DESCRIPTION |
|---------|--|--|
| [13:12] | Input/Discharge Sense Resistor Ratio (RSNS_RATIO) | For PMON calculation. 00: RAC and RSR 1:1 (10mohm) <default @ POR> 01: RAC and RSR 2:1 (20mohm/10mohm) 10: RAC and RSR 1:2 (10mohm/20mohm) 11: Reserved |
| [10] | EN_PMOM | PMON output enable. 0: Disable PMON output to minimize Iq <default @ POR> 1: Enable PMON output |
| [9] | PMON Gain (PMON_RATIO) | Ratio of PMON output current vs total input and battery power with 10mohm sense resistor. With the sense resistor is 10mohm (RAC and RSR) 0: 0.25uA/W 1: 1uA/W <default @ POR> With the sense resistor is 20/10mohm or 10mohm/20mohm (RAC and RSR) 0: 0.125uA/W 1: 0.5uA/W <default @ POR> |

Figure 7 shows the bq24780S PMON accuracy at 25°C.

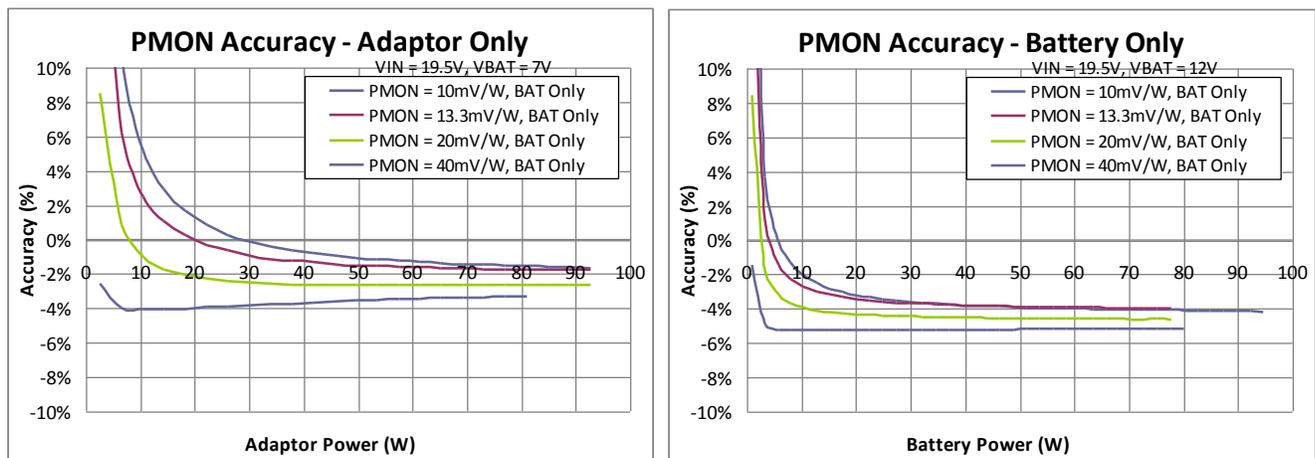


Figure 7. TIDA-00657 PMON accuracy

/PROCHOT Functions

The processor hot function in bq24780S monitors these events, and PROCHOT pulse is asserted.

The PROCHOT triggering events include:

- ICRT: adapter peak current
- INOM: adapter average current (110% of input current limit)
- IDCHG: battery discharge current
- VSYS: system voltage on SRN for 2s - 4s battery
- ACOK: upon adapter removal (ACOK pin HIGH to LOW)
- BATPRES: upon battery removal (BATPRES pin LOW to HIGH)
- CMPOUT: Independent comparator output (CMPOUT pin HIGH to LOW)

The threshold of ICRT, IDCHG or VSYS, and the deglitch time of ICRT, INOM, IDCHG or CMPOUT are programmable through SMBus. Each triggering event can be individually enabled in REG0x3D[6:0].


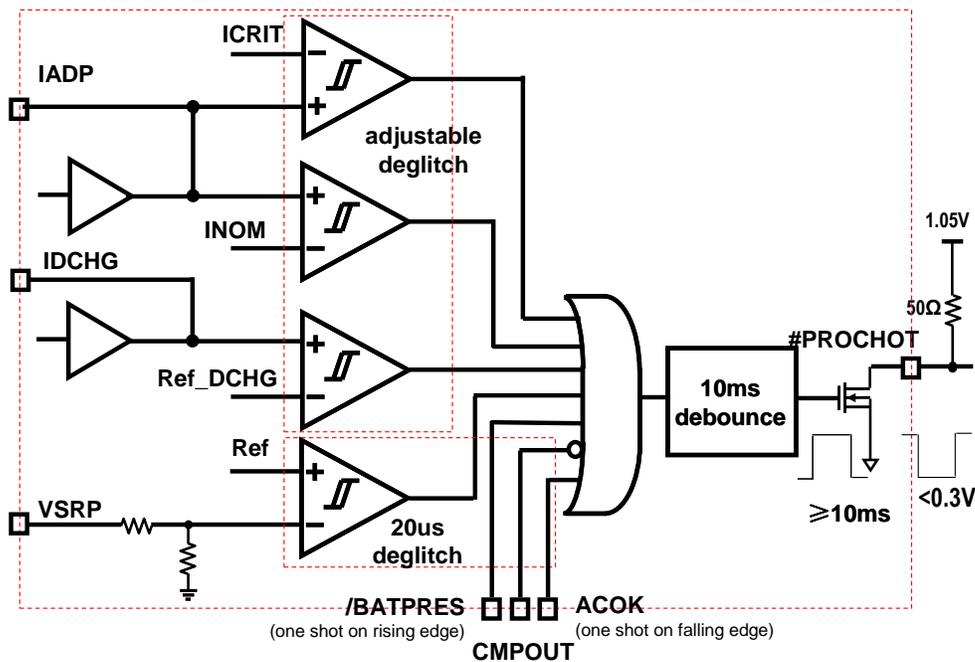


Figure 8 /PROCHOT block diagram

ProchotOption1 Register (REG0x3D[6:0])

| BIT | BIT NAME | DESCRIPTION |
|-------|-------------------------------------|---|
| [6:0] | /PROCHOT envelop selector (PROFILE) | <p>When adapter is present, the /PROCHOT function is enabled by the below bits.</p> <p>When adapter is removed, ICRT, INOM /BATPRES and ACOK functions are automatically disabled in the /PROCHOT profile. Independent comparator, IDCHG and VSYS function setting are preserved.</p> <p>When all the bits are 0, /PROCHOT function is disabled.</p> <p>Bit6: Independent comparator, 0: disable <default @ POR>; 1: enable</p> <p>Bit5: ICRT, 0: disable; 1: enable <default @ POR></p> <p>Bit4: INOM, 0: disable <default @ POR>; 1: enable</p> <p>Bit3: IDCHG, 0: disable <default @ POR>; 1: enable</p> <p>Bit2: VSYS, 0: disable <default @ POR>; 1: enable</p> <p>Bit1: /BATPRES, 0: disable <default @ POR>; 1: enable (one-shot rising edge triggered)</p> <p>Bit0: ACOK, 0: disable <default @ POR>; 1: enable (one-shot falling edge triggered)</p> |

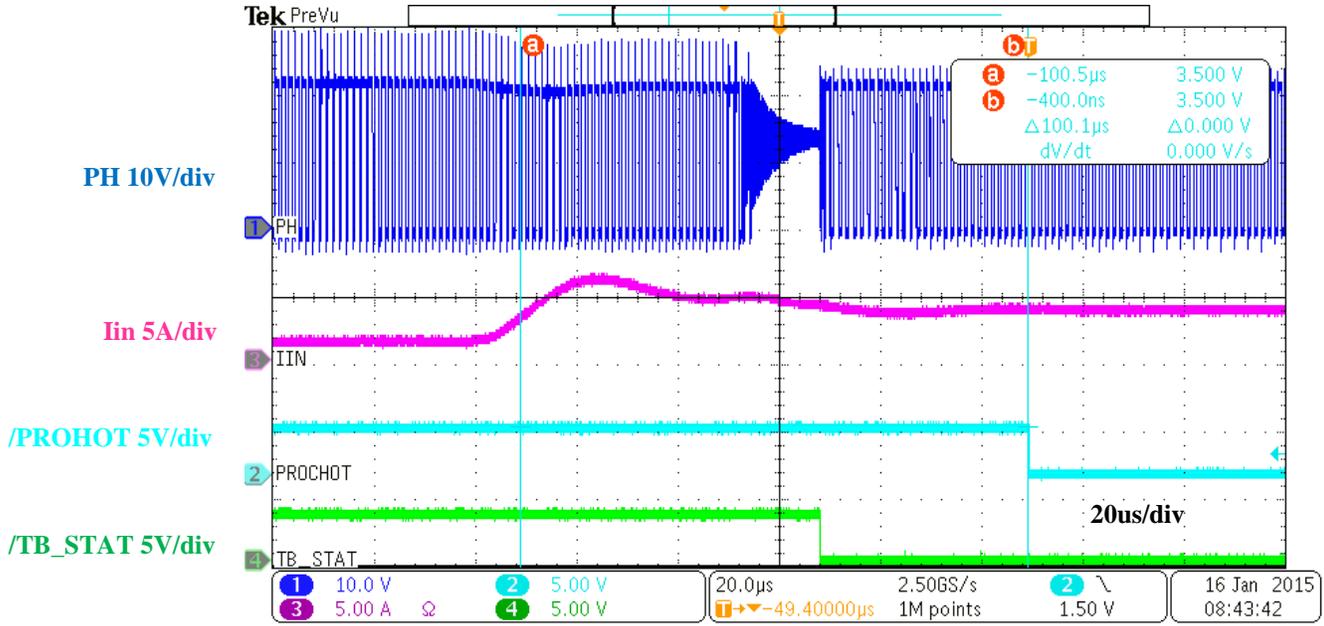

Vin=20V, VBAT = 13.3V, IIN = 2048mA, ICRIT threshold = 150%

Figure 8. TIDA-00657 /PROHOT System

Application Circuit II

- The second application circuit applies the previous implementation of the bq24780S and adds an [ADS7924](#), as shown in Figure 9 below. The [ADS7924](#) is a 12-bit, four-channel, low-power, successive approximation register (SAR) analog-to-digital converter (ADC) with a small footprint. The ADC has a digital comparator with programmable upper and lower limits for each of the four channels. Adding the ADC to the system allows the host to monitor the total power from the adapter and battery (PMON), as well as the discharge current (IDCHG) and the adapter current (IADP) of the battery. The ADC provides the host with an alarm on a dedicated interrupt output pin when any of the thresholds are crossed, allowing the host to take preventive measures.
- The remaining fourth ADC channel is available to monitor a different sensor or signal within the system.

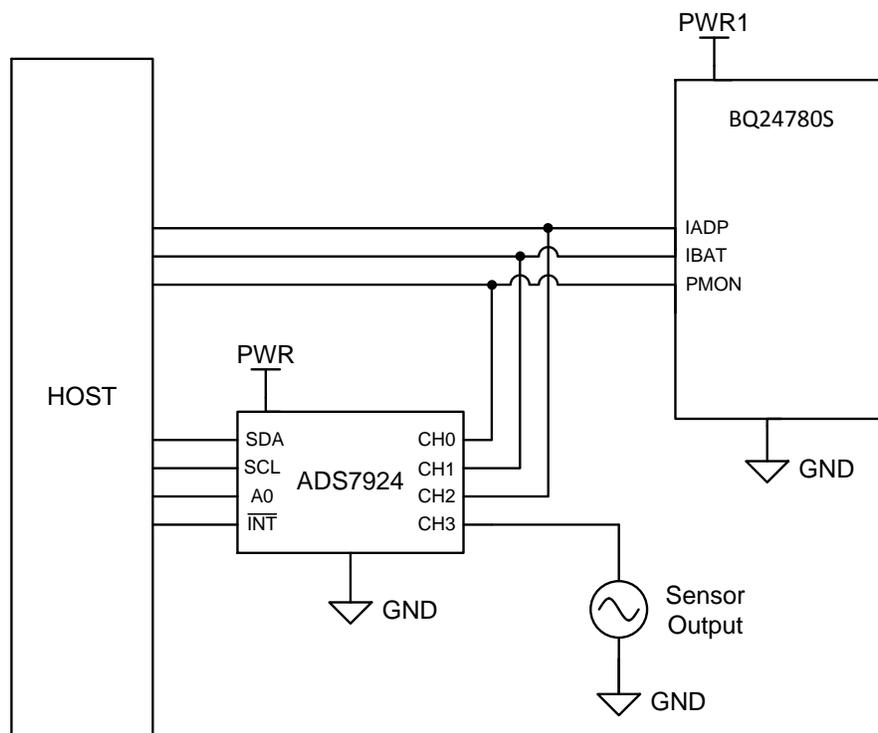


Figure 9. Block Diagram: Autonomous Monitoring Application using ADS7924

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated