
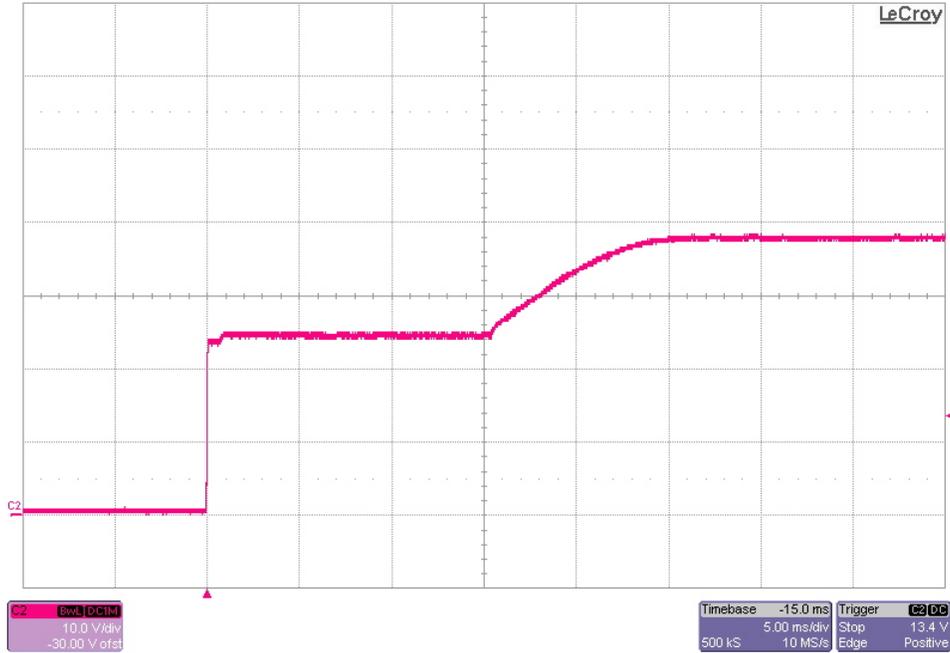

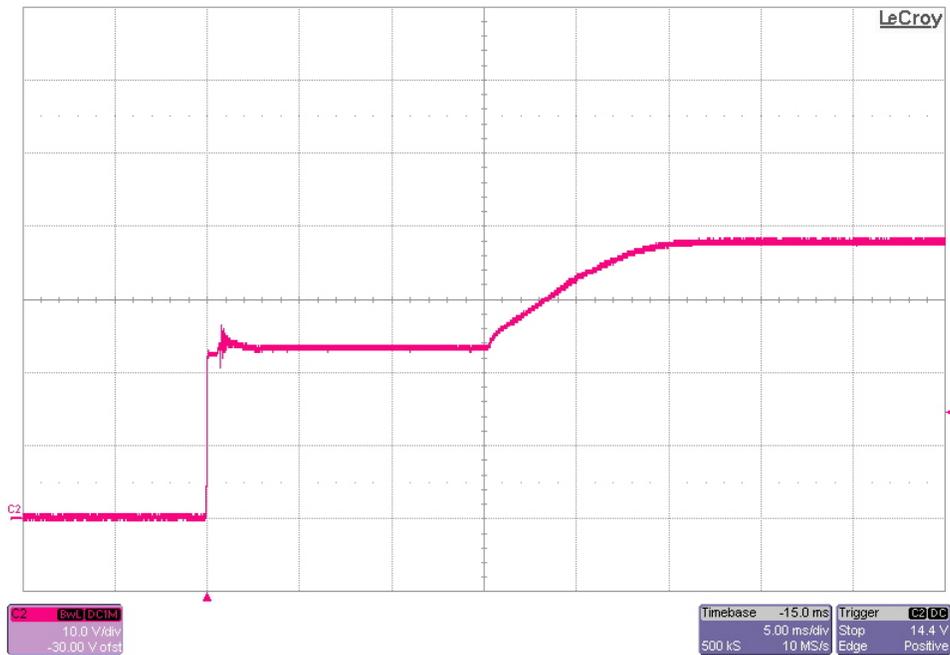
## 1 Startup

The photo below shows the output voltage startup waveform after the application of 24V in. The 38V output was loaded to 0A. (10V/DIV, 5mS/DIV)






The photo below shows the output voltage startup waveform after the application of 24V in. The 38V output was loaded to 2A. (2V/DIV, 5mS/DIV)


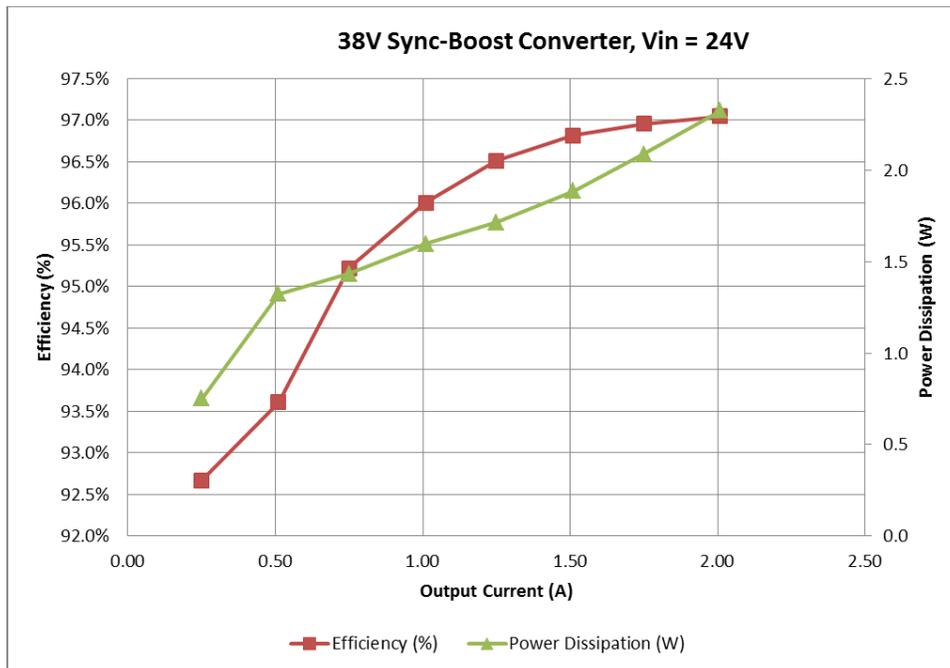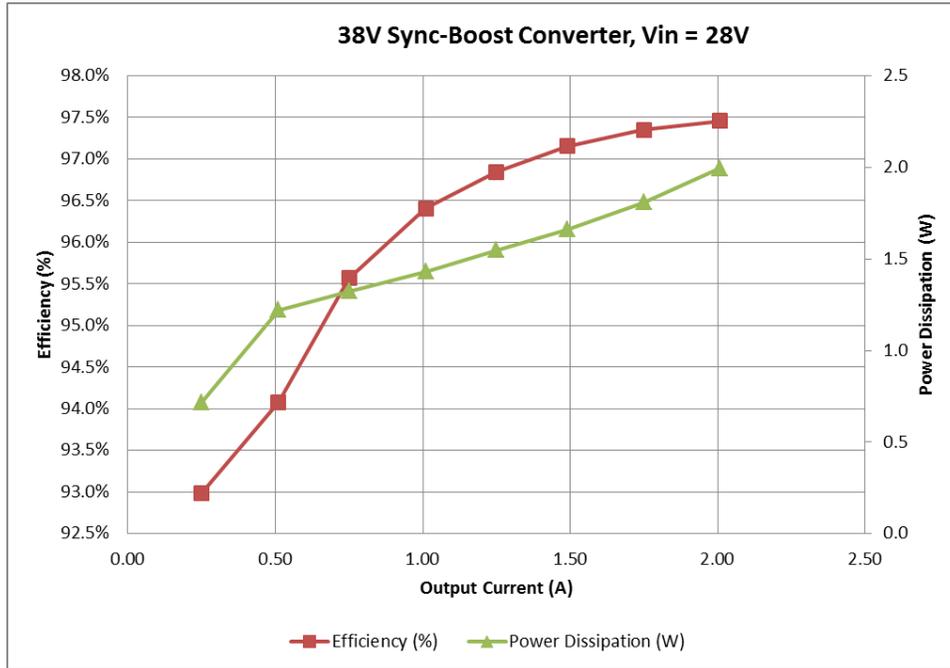
## 2 Efficiency


The 38V sync boost converter efficiency is shown below.



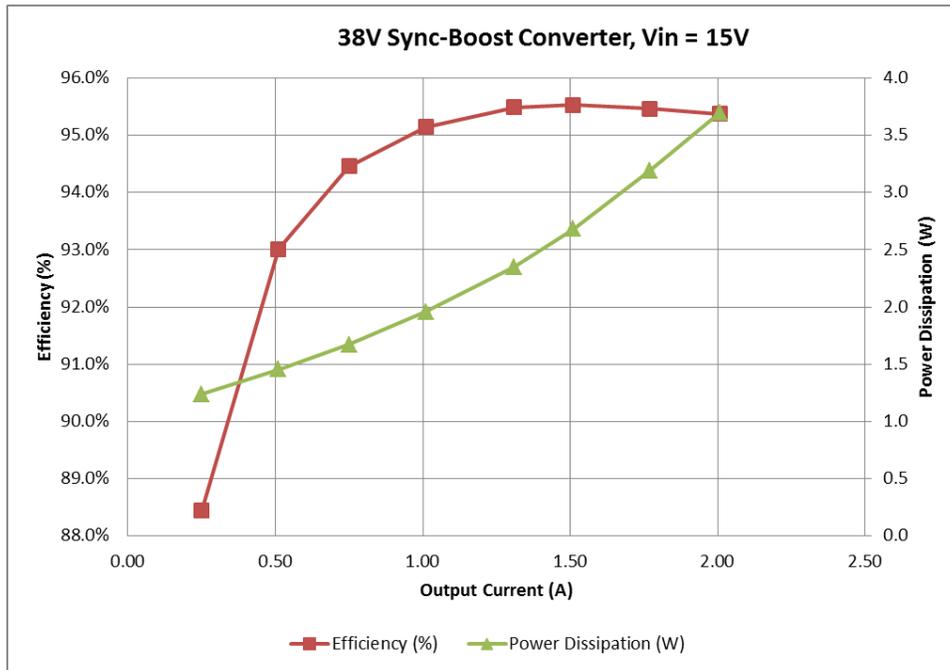

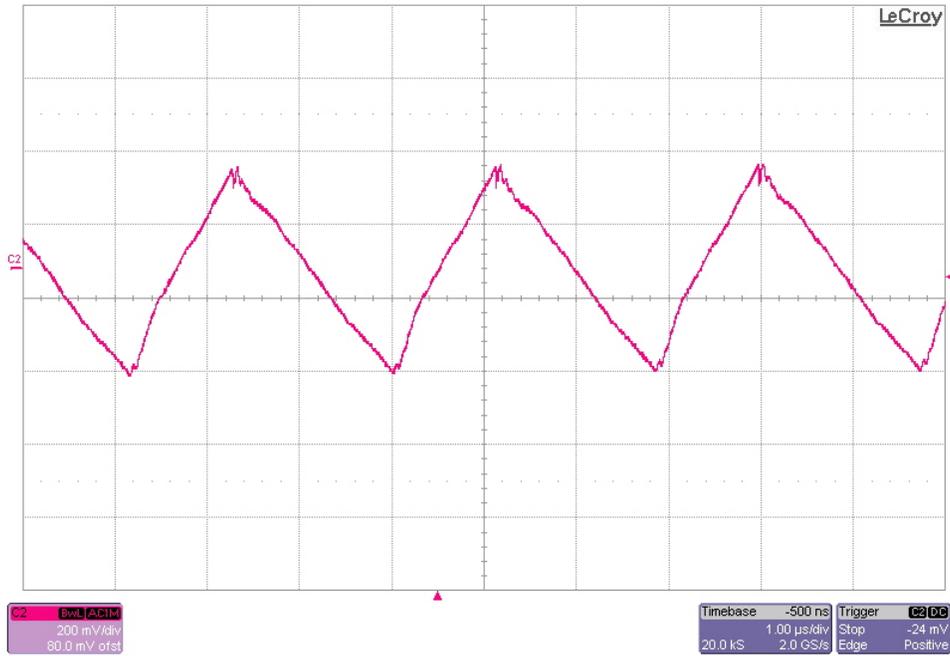
## 3 Output Ripple Voltage


The 38V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 2A. The input voltage is set to 15V. (200mV/DIV, 1uS/DIV)



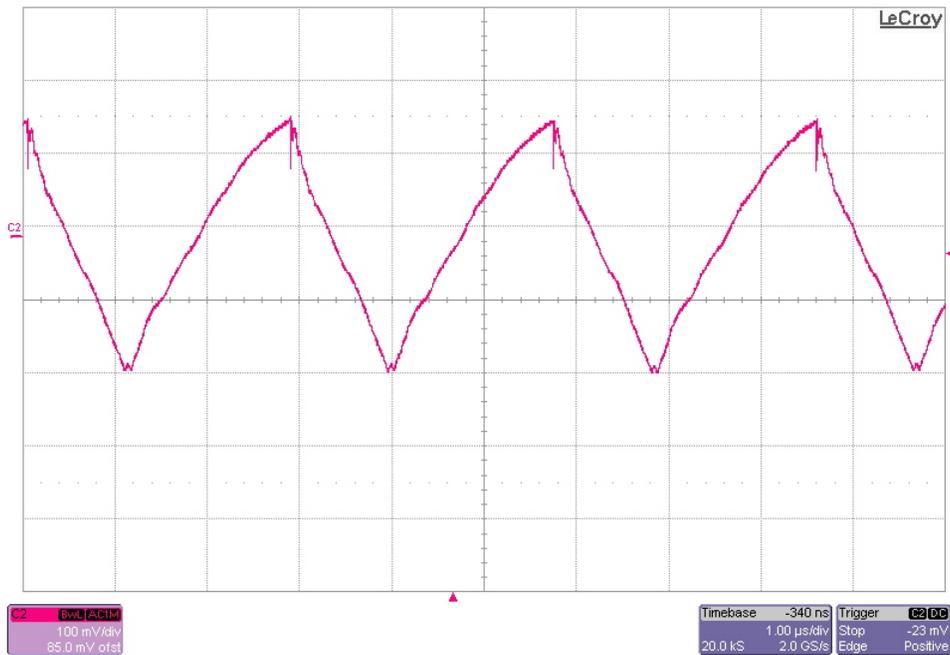The 38V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 2A. The input voltage is set to 24V. (100mV/DIV, 1uS/DIV)




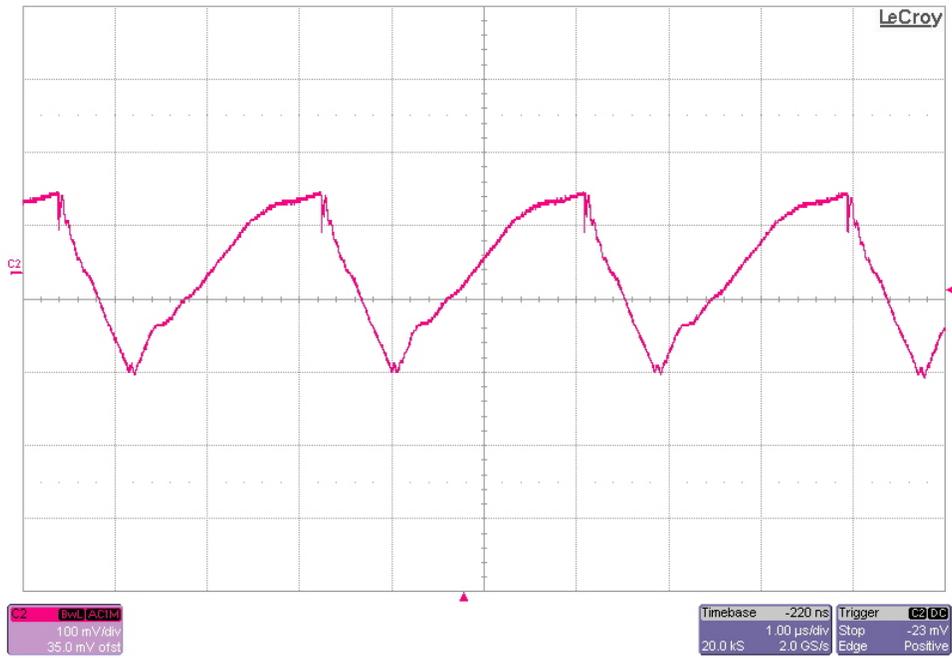The 38V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 2A. The input voltage is set to 28V. (100mV/DIV, 1uS/DIV)



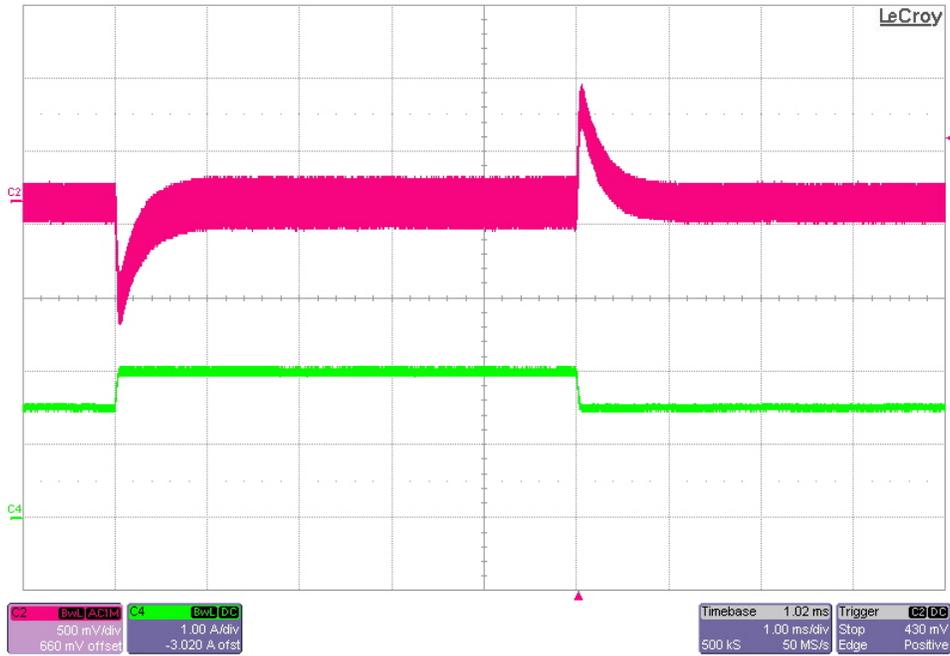
## 4 Load Transients

The photo below shows the output voltage (ac coupled) when the load current is stepped between 1.5A and 2A.  $V_{in} = 24V$ . (500mV/DIV, 1A/DIV, 1mS/DIV)




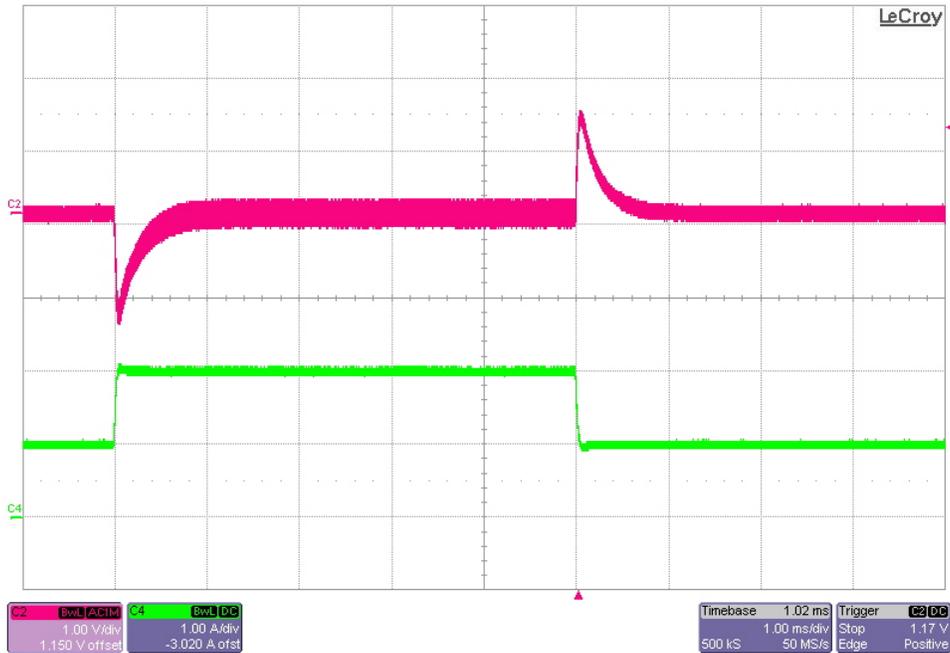The photo below shows the output voltage (ac coupled) when the load current is stepped between 1A and 2A.  $V_{in} = 24V$ . (1V/DIV, 1A/DIV, 1mS/DIV)



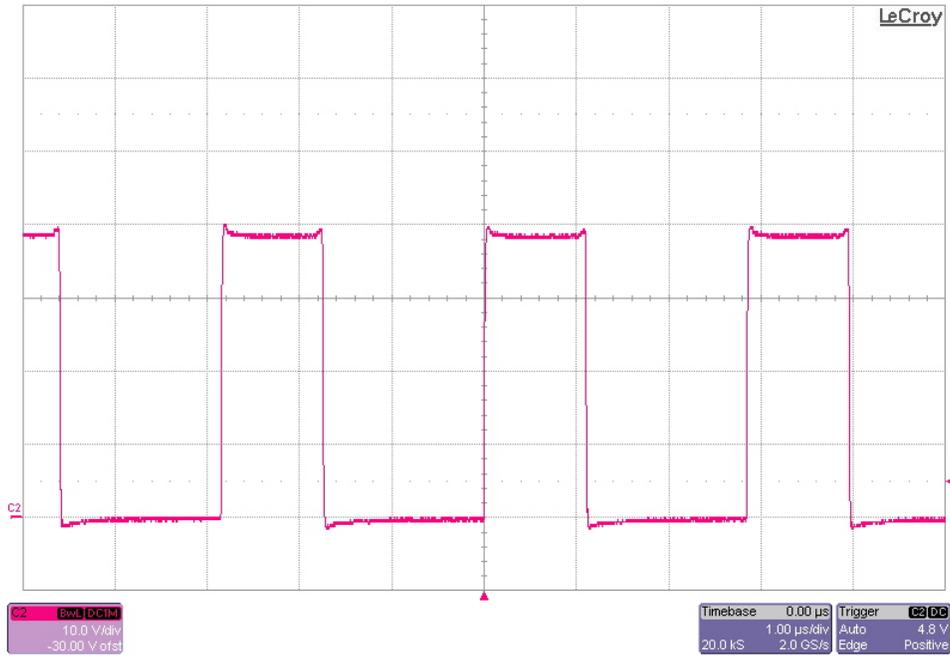
## 5 Switch Node Waveforms


The photo below shows the FET switching voltage. The input voltage is 15V and the output is loaded to 2A. (10V/DIV, 1uS/DIV)



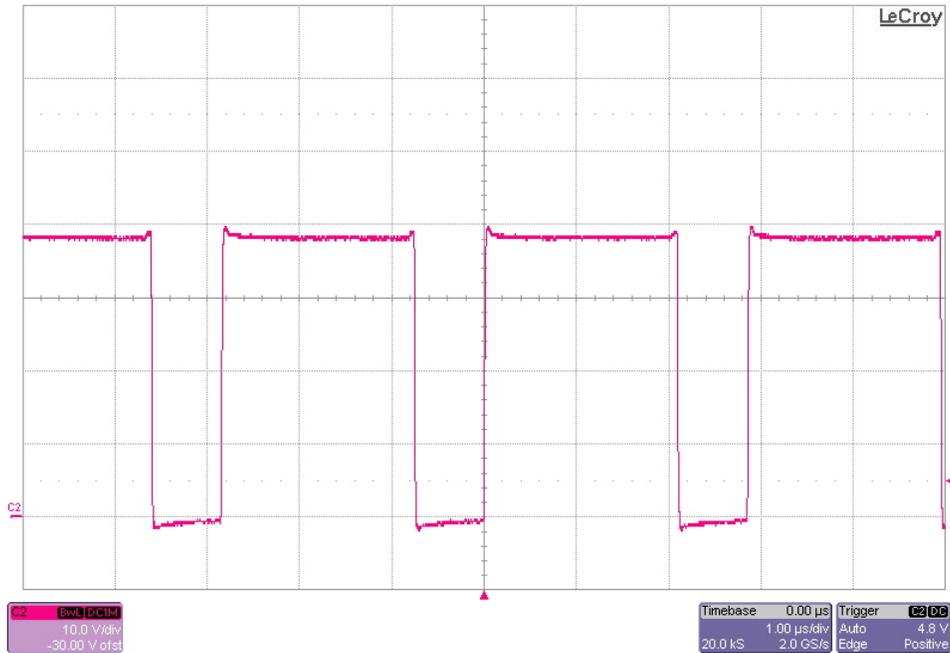
The photo below shows the FET switching voltage. The input voltage is 28V and the output is loaded to 2A. (10V/DIV, 1uS/DIV)



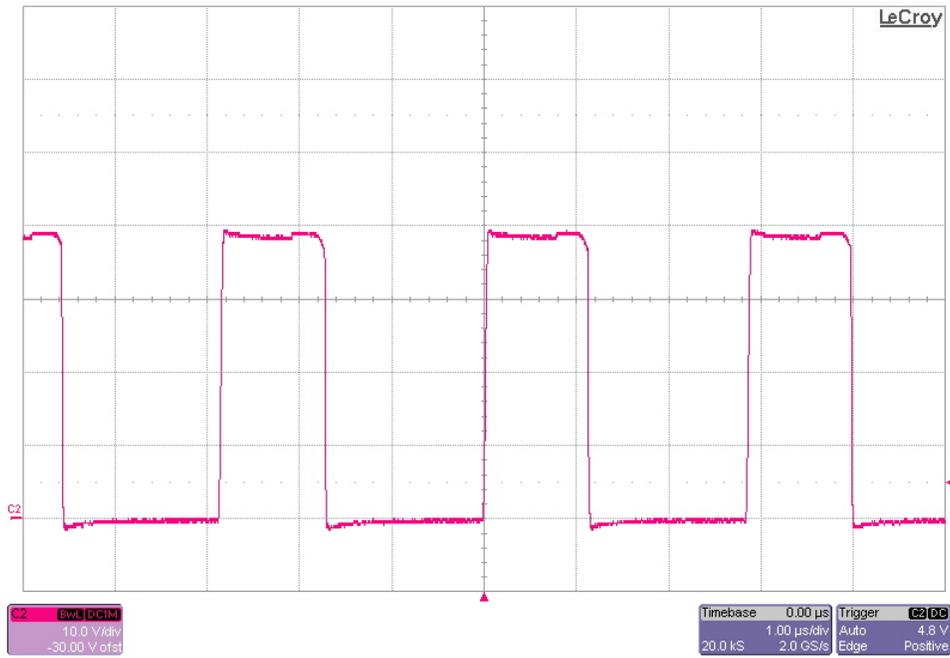The photo below shows the FET switching voltage. The input voltage is 15V and the output is loaded to 0.17A. The converter is just starting DCM operation. (10V/DIV, 1uS/DIV)



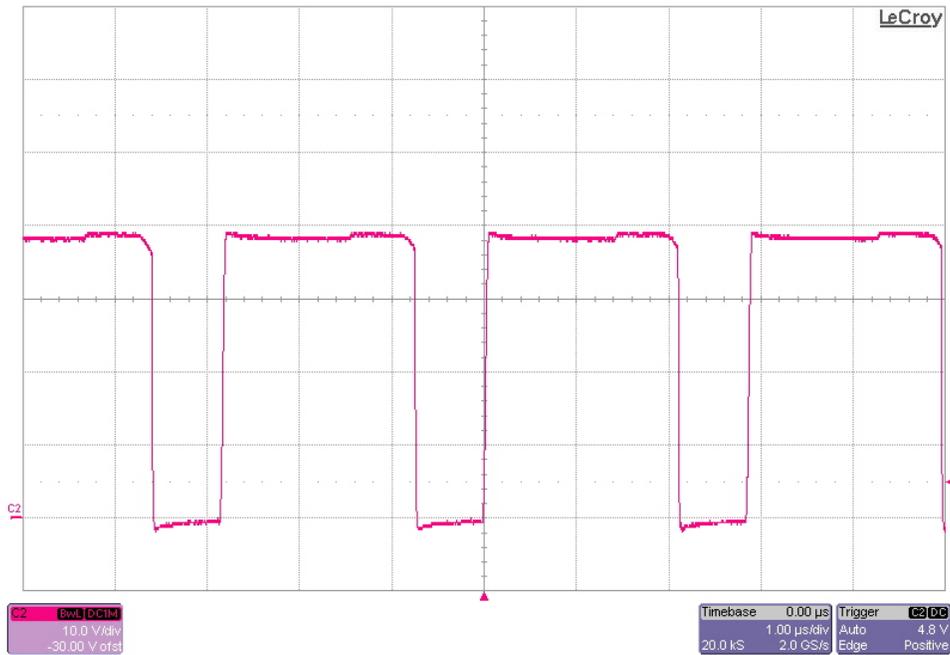The photo below shows the FET switching voltage. The input voltage is 28V and the output is loaded to 0.29A. The converter is just starting DCM operation. (10V/DIV, 1uS/DIV)




## 6 Control Loop Gain / Stability

The plot below shows the loop gain and phase margin at 15V, 24V and 28V with the output loaded to 2A.

Vin = 15V  
 Vin = 24V  
 Vin = 28V

Band Width = 6.73KHz,  
 Band Width = 11.1KHz,  
 Band Width = 13.1KHz,

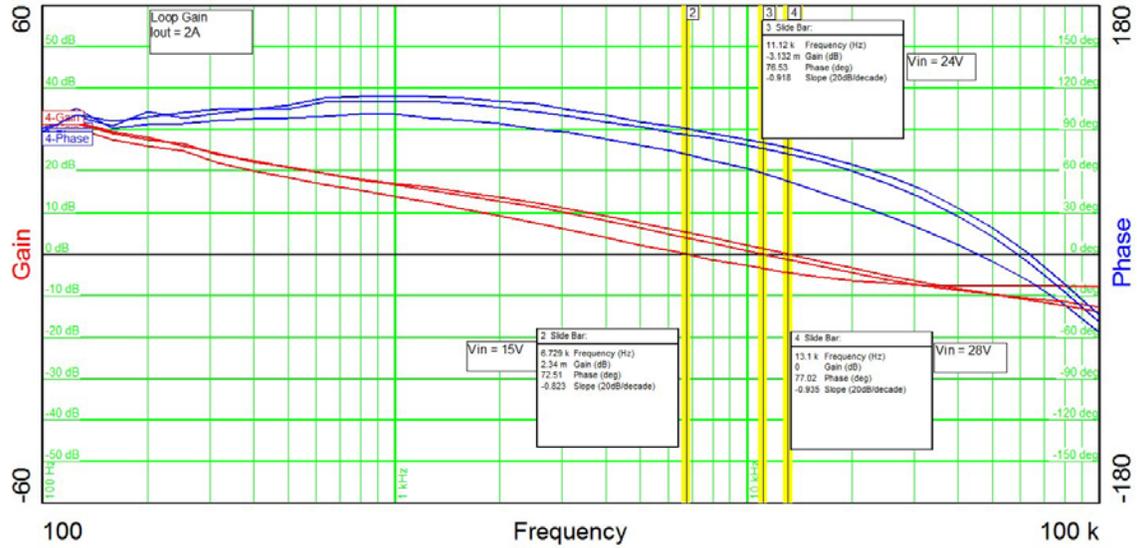
Phase Margin = 73 degrees  
 Phase Margin = 77 degrees  
 Phase Margin = 77 degrees




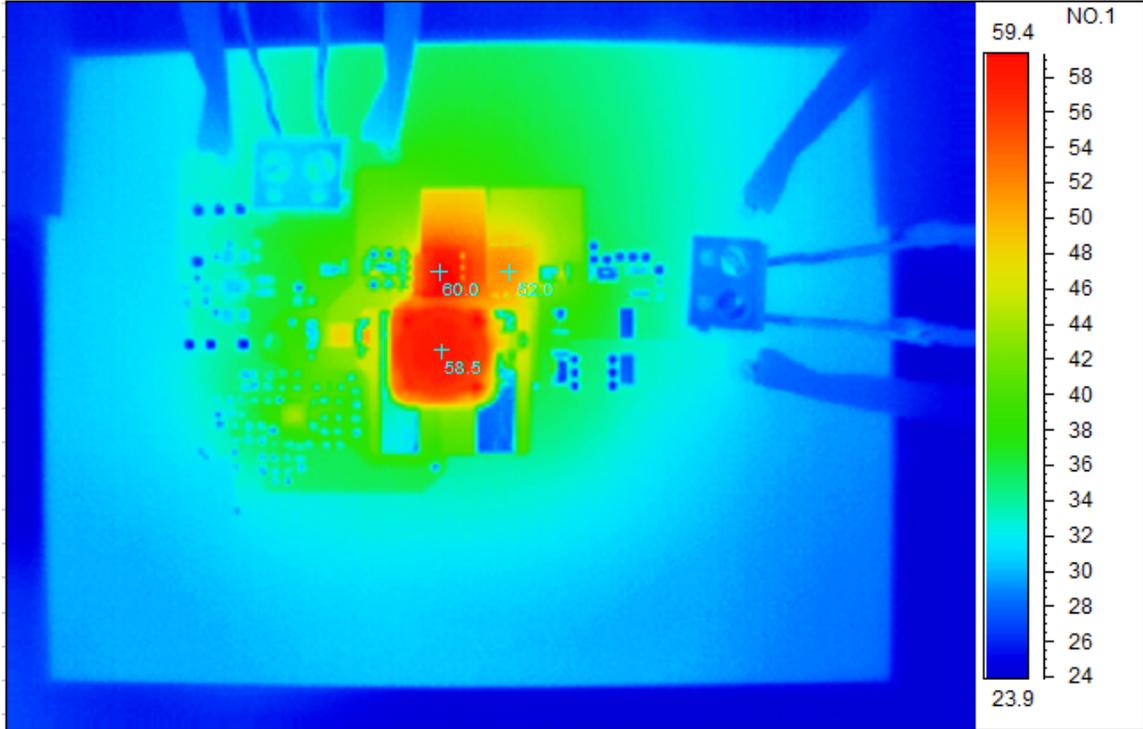
## 8 Thermal Image

A thermal image is shown below operating at 24V input and 2A output (room temp and no airflow).



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated