


PMP30373RevA Test Results

1	Startup @ Vin 12V / 36V / 60V	2
2	Shutdown @ Vin 12V / 36V / 60V	4
3	Efficiency up to 220mA load current	6
4	Load Regulation	7
5	Line Regulation	8
6	Output Ripple Voltage	9
7	Input Ripple Voltage	10
8	Load Transients	12
9	Control Loop Frequency Response	14
10	Miscellaneous Waveforms	17
10.1	Switch Node (TP4)	17
10.2	Diode D1 (TP6)	20
11	Thermal Image @ Vin 6V / 12V / 36V / 60V	23

Topology: Transission Mode Cuk Converter (= inverting SEPIC)

Device: LM5001 at switching frequency 300kHz

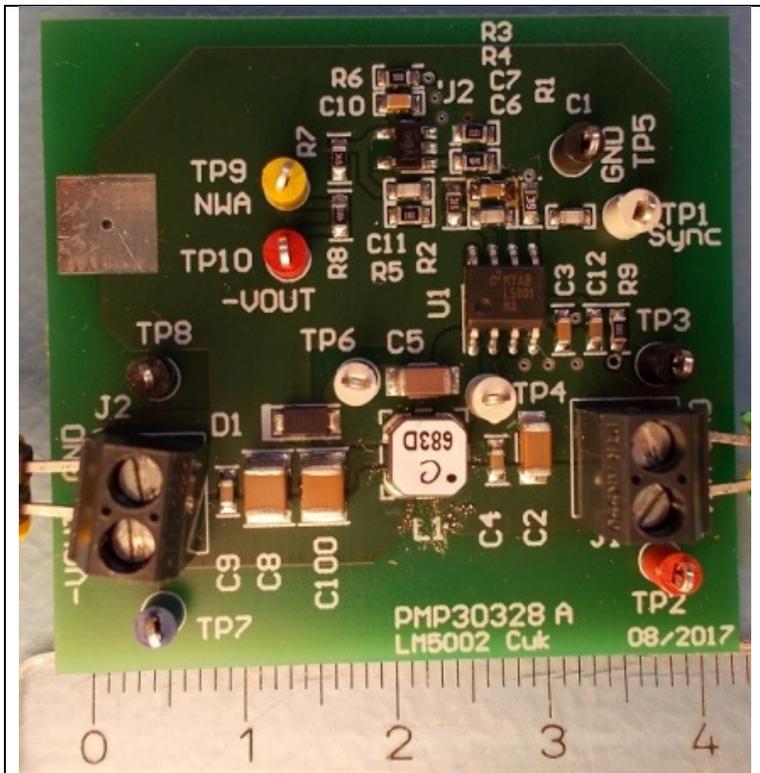Unless otherwise mentioned circuit was measured with a resistive load at 200mA output current (with resistive load). **This supply is dedicated for sensitive RF or instrumentation circuits.**



1 Startup @ Vin 12V / 36V / 60V

The startup waveform is shown in the Figure 1. The input voltage was set to 12V.

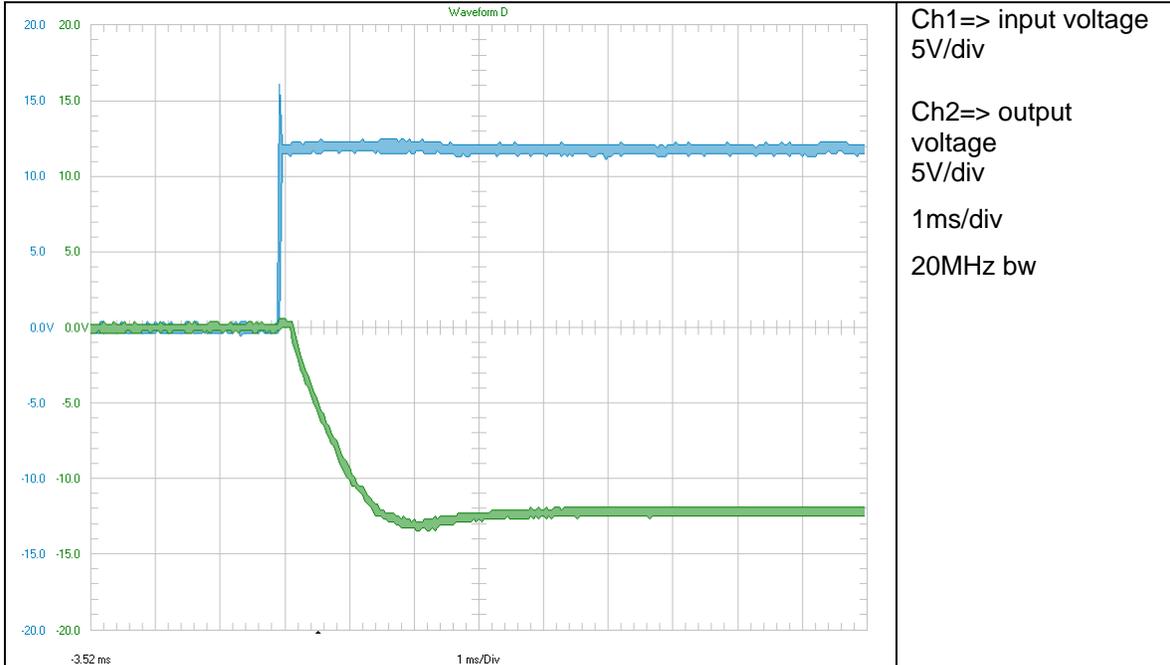


Figure 1

The startup waveform is shown in the Figure 2. The input voltage was set to 36V.

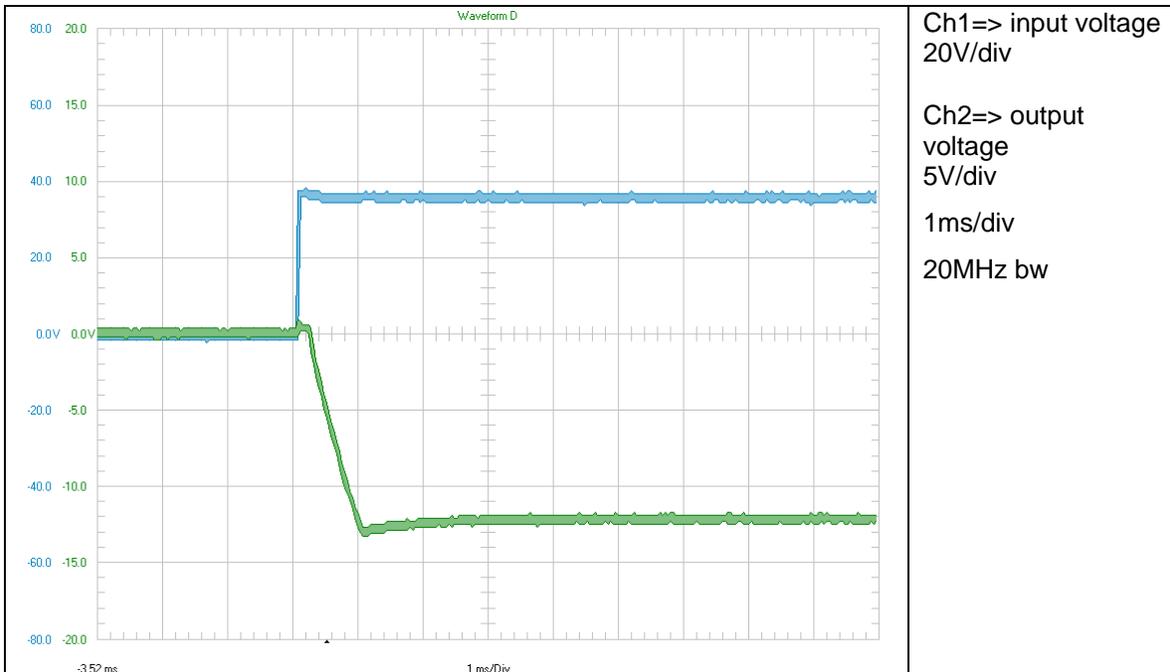


Figure 2

The startup waveform is shown in the Figure 3. The input voltage was set to 60V.

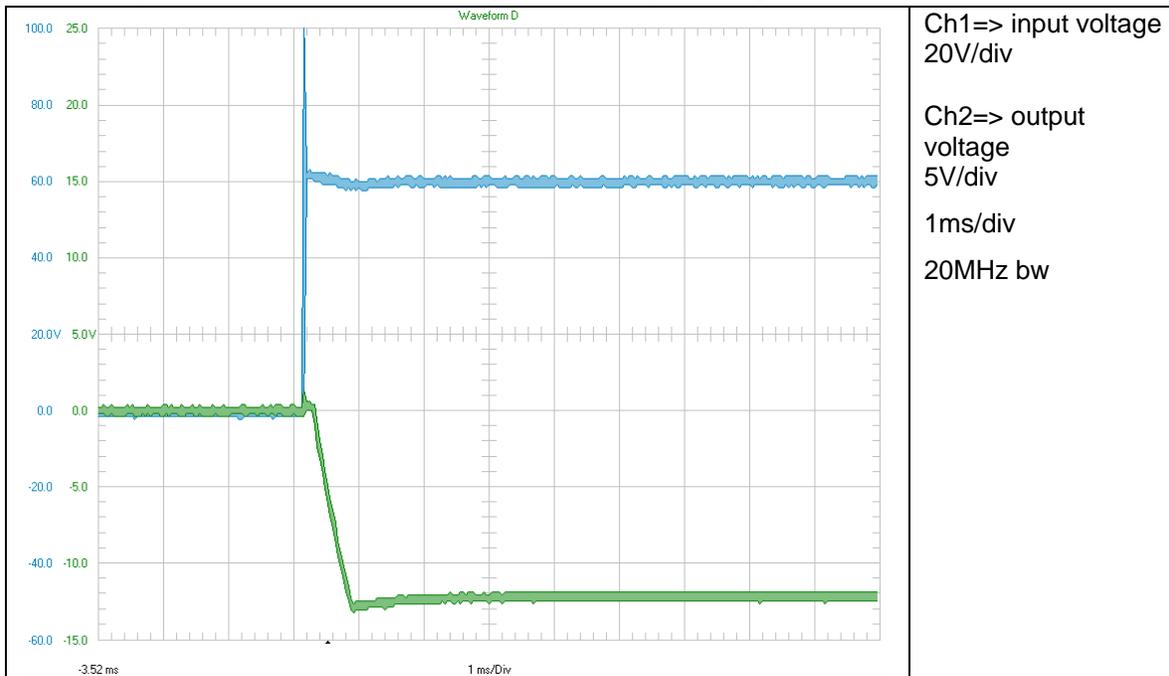


Figure 3

2 Shutdown @ Vin 12V / 36V / 60V

The shutdown waveform is shown in the Figure 4. The input voltage was set to 12V. The power supply was disconnected.

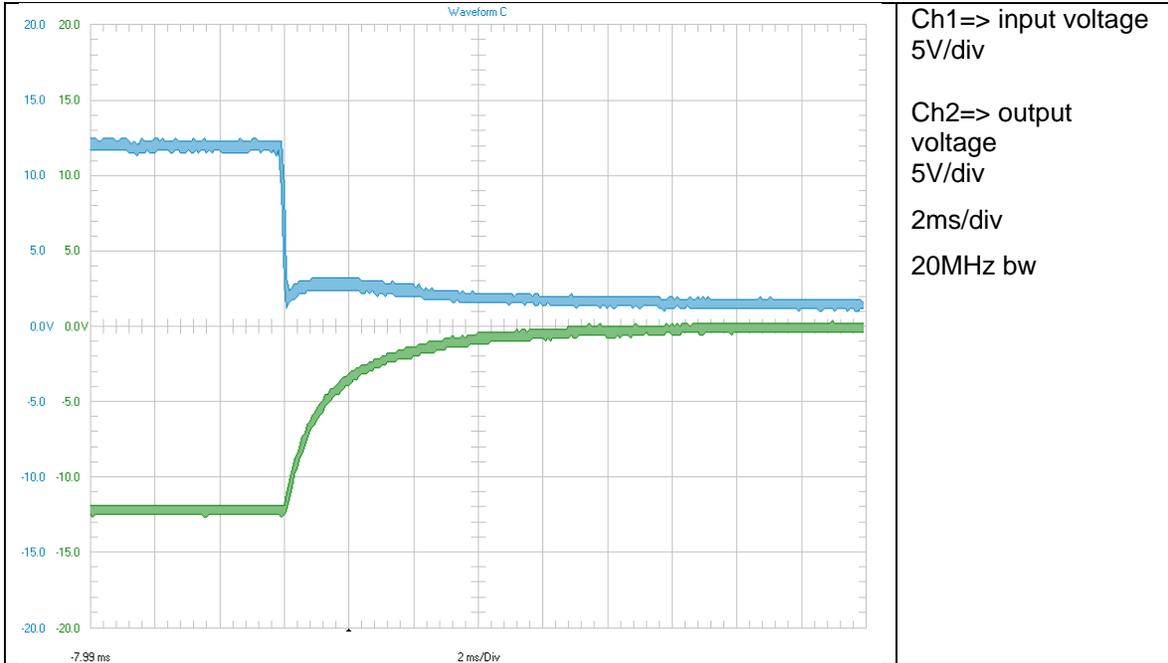


Figure 4

The shutdown waveform is shown in the Figure 5. The input voltage was set to 36V. The power supply was disconnected.

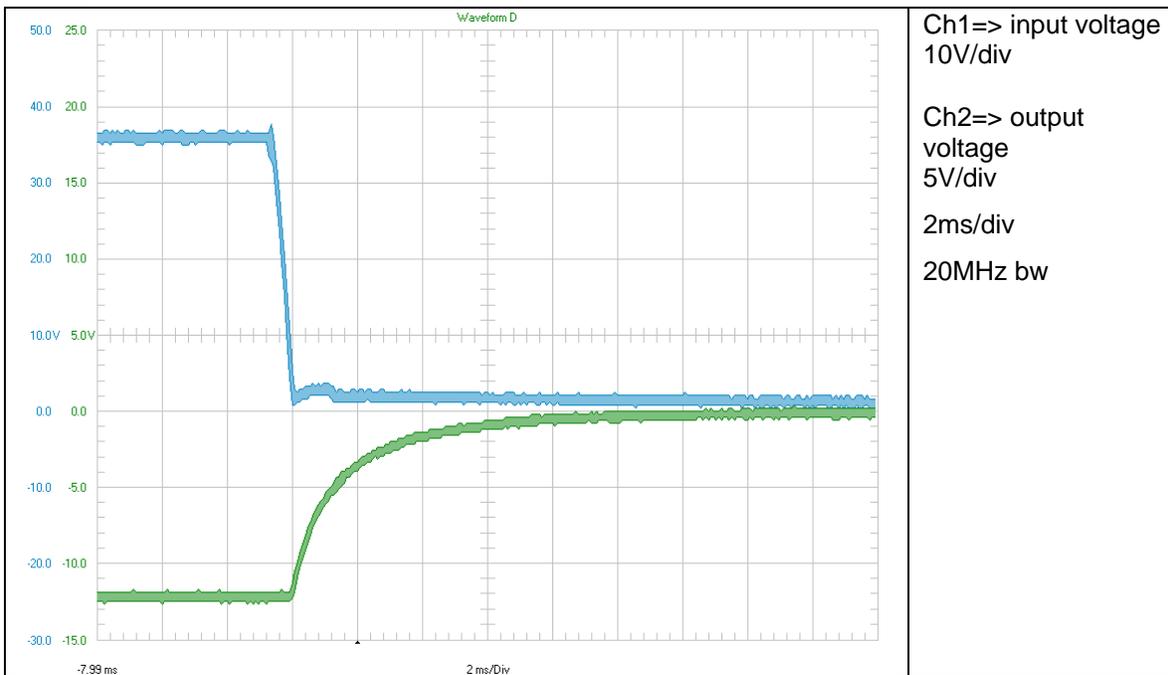


Figure 5

The shutdown waveform is shown in the Figure 6. The input voltage was set to 60V. The power supply was disconnected.

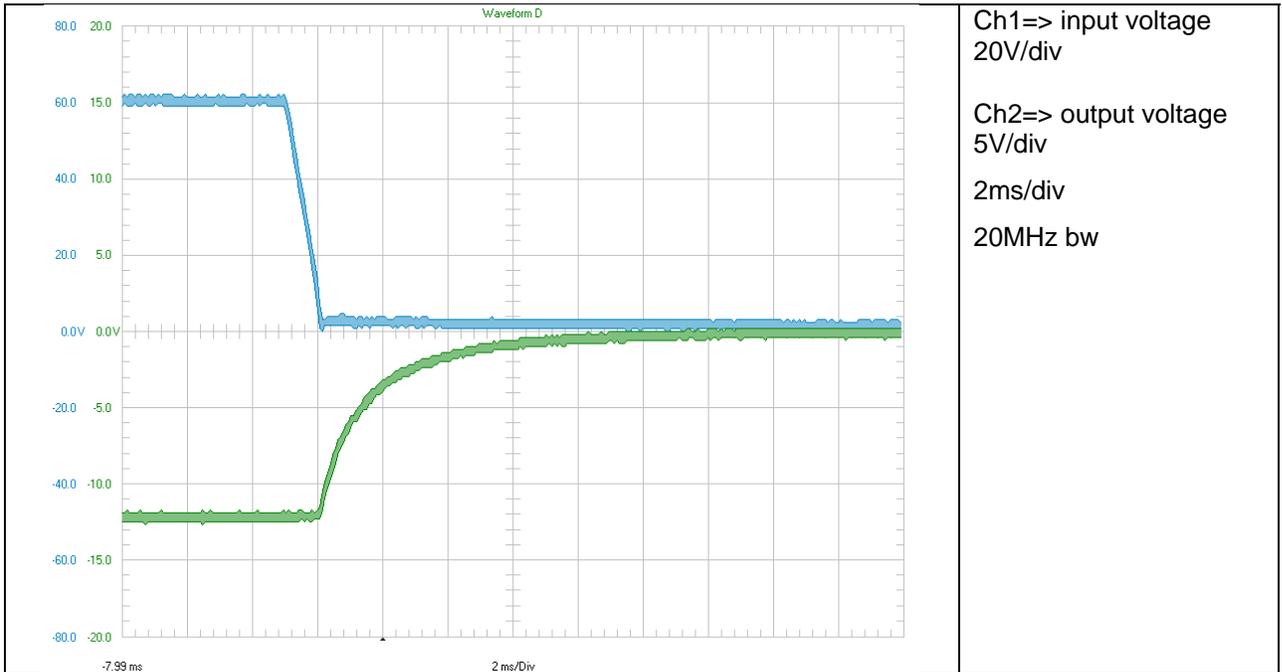


Figure 6

3 Efficiency up to 220mA load current

The efficiency is in the Figure 7 below. The input voltage was set to 6V / 12V / 36V / 60V. **Maximum load current at 6V input is 140mA** due to max. switch current and max. duty.

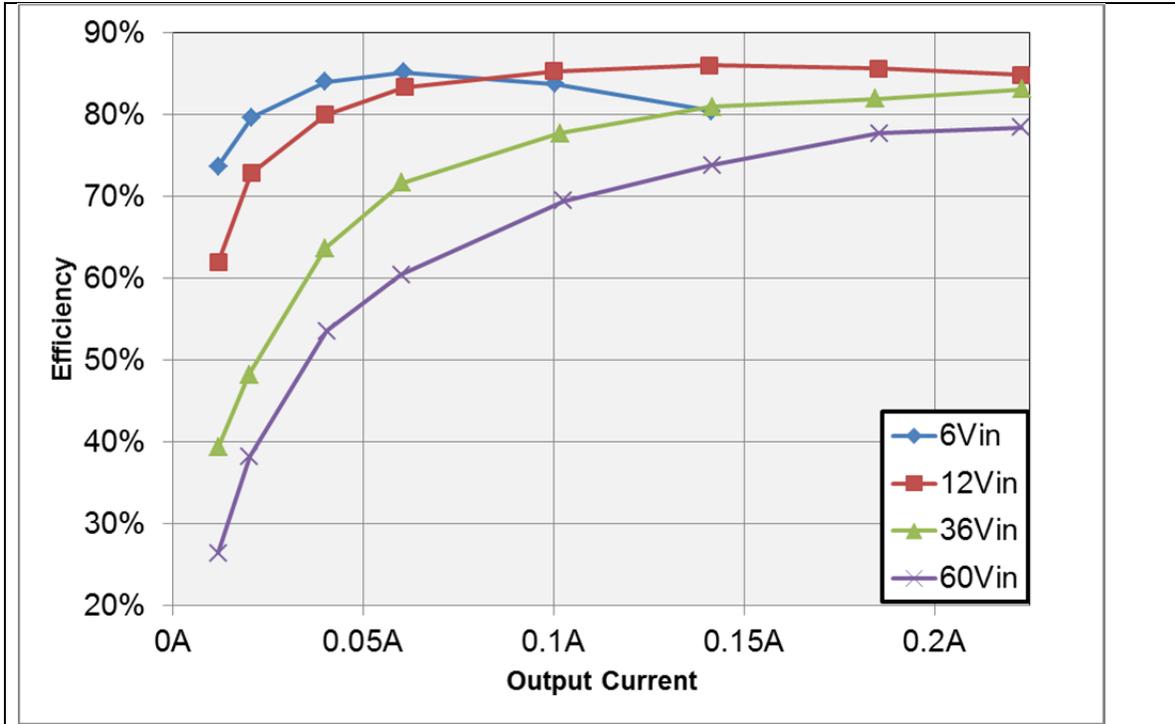


Figure 7

Figure 8 show the losses (Pin - Pout) with input voltage 6V / 12V / 36V / 60V

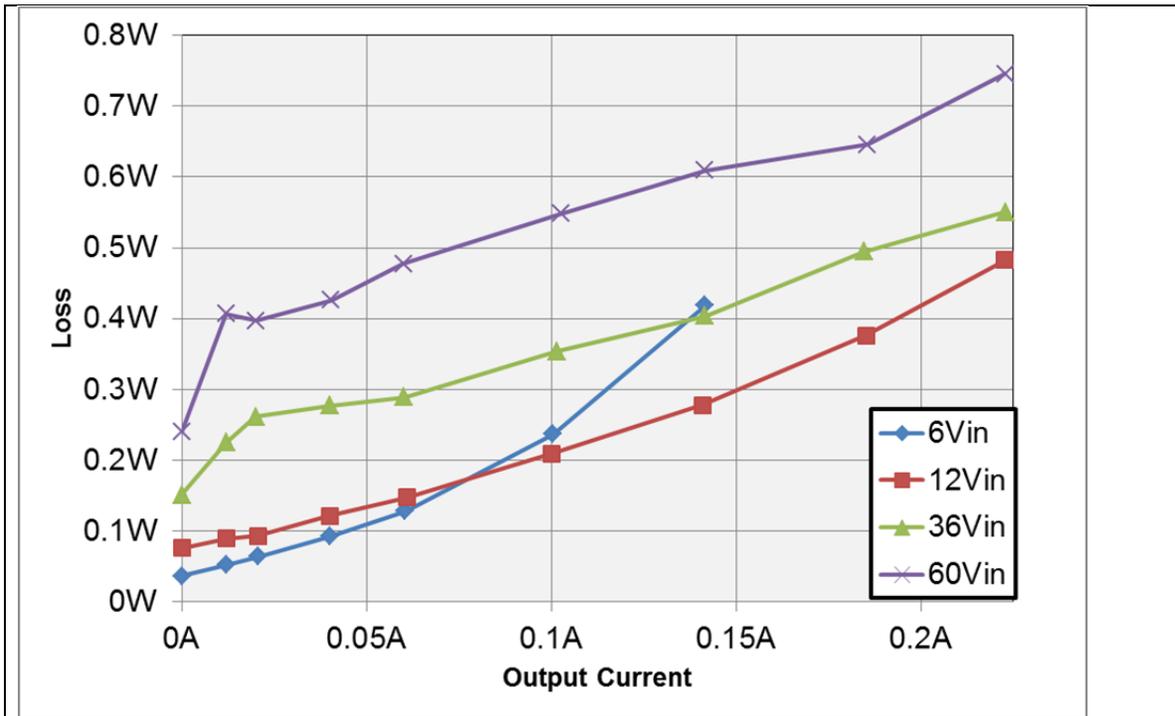


Figure 8

4 Load Regulation

The load regulation of the output is shown in the Figure 9 below.
 The input voltage was set to 6V / 12V / 36V / 60V.

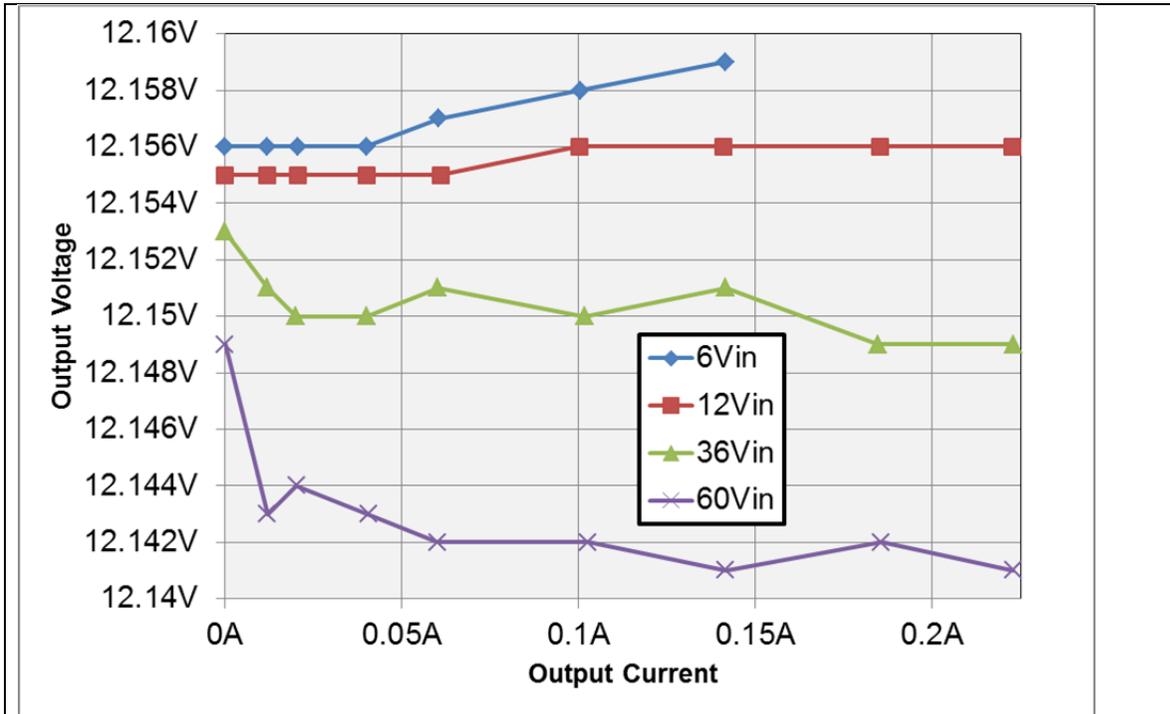


Figure 9

The deviation for load regulation is less than 20mV, means less than 0.2%

5 Line Regulation

The line regulation is shown in Figure 10. The output current was set to full load 200mA.

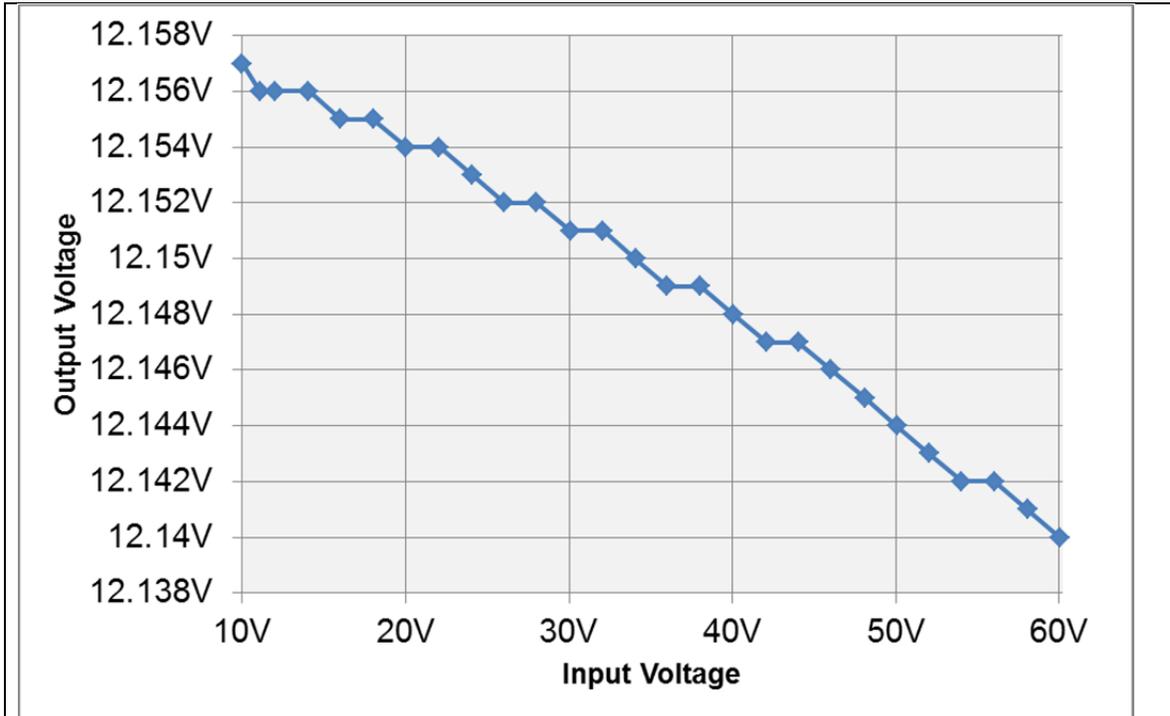


Figure 10

The deviation for line regulation is less than 20mV, means less than 0.2%

With the same setup full load efficiencies and losses were calculated - this is shown in Figure 11:

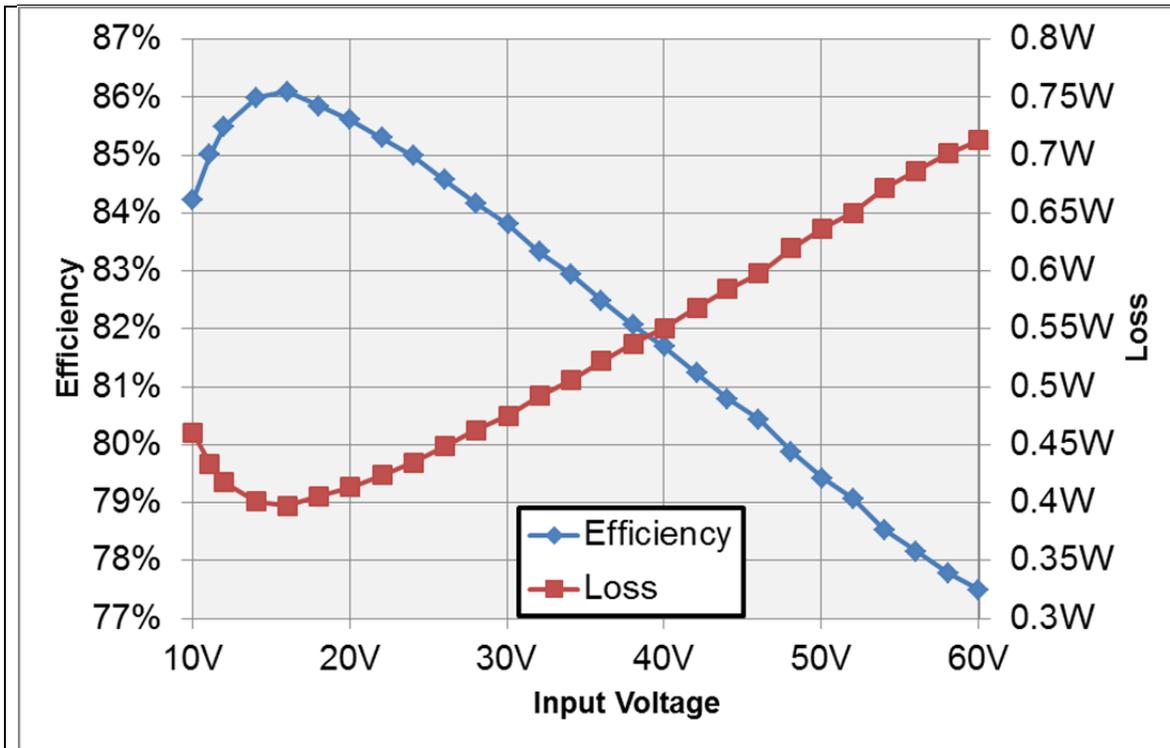


Figure 11

6 Output Ripple Voltage

The output ripple voltage is shown in Figure 12.

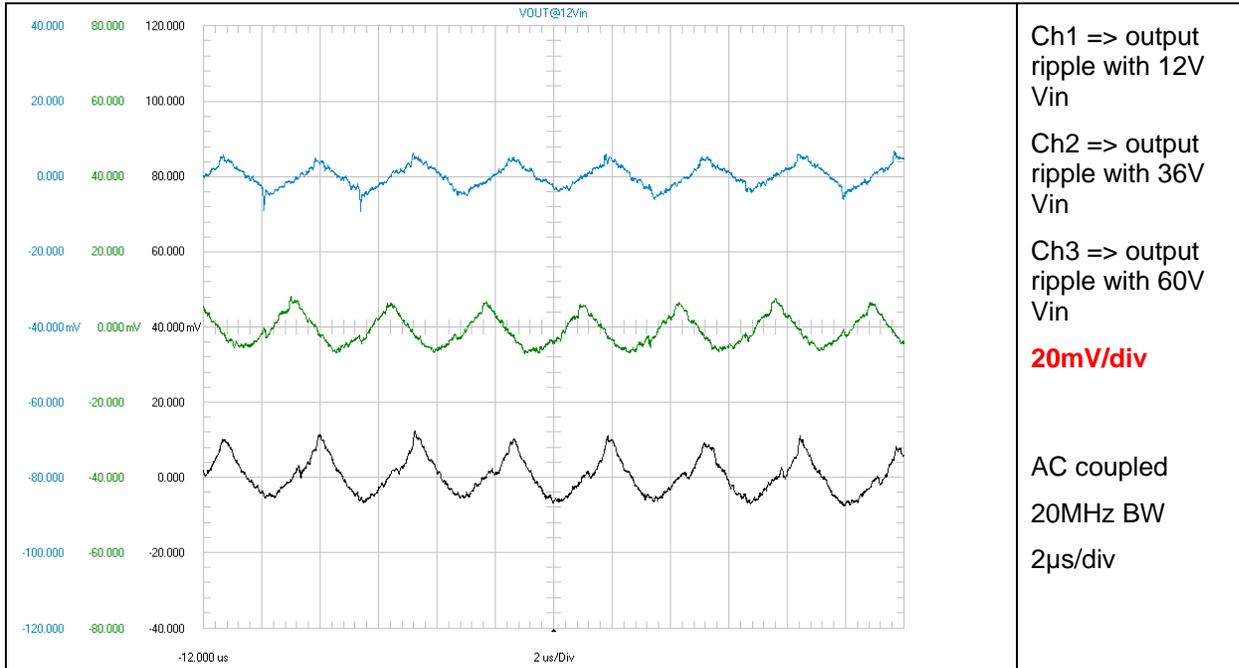


Figure 12

The maximum output ripple is around 20mVpp at 60V input voltage, again less than 0.2% ! Cuk topology provides continuous currents at input AND output, the power stage itself works w/ a filter second order to input and output - this results in low output ripple and low reflected ripple. That's the major benefit compared to inverting Buck Boost, far lower conducted emissions.

7 Input Ripple Voltage

The input ripple voltage at 12V is shown in Figure 13.

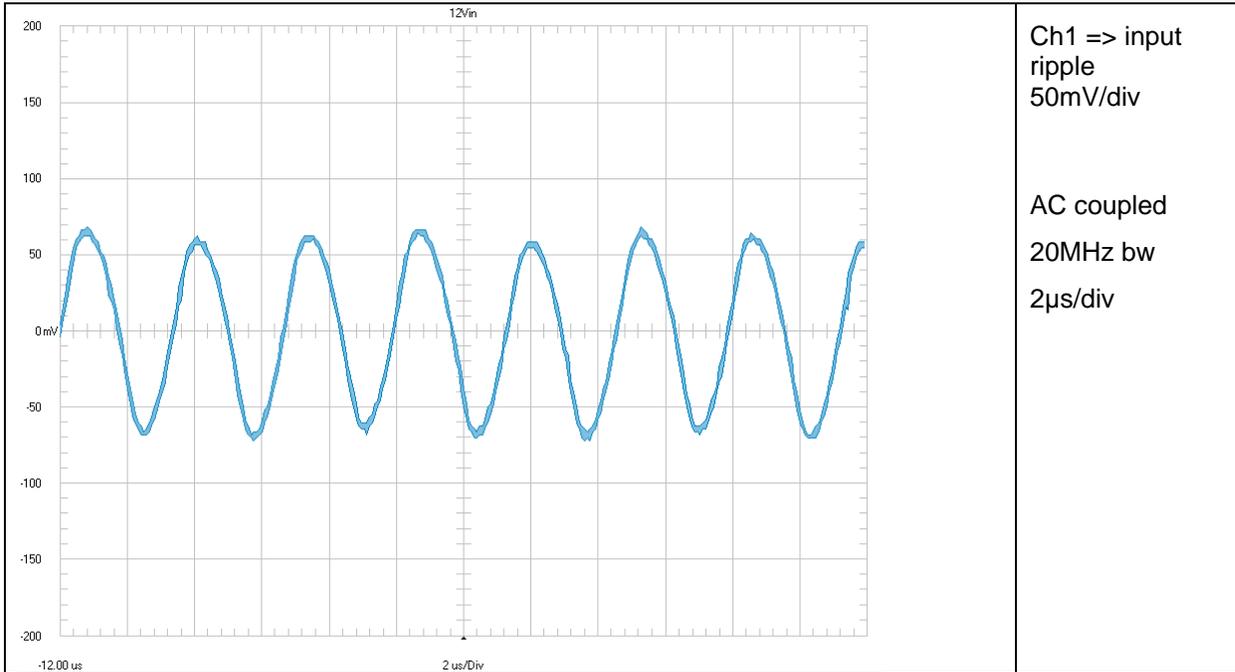


Figure 13

The input ripple voltage at 36V is shown in Figure 14

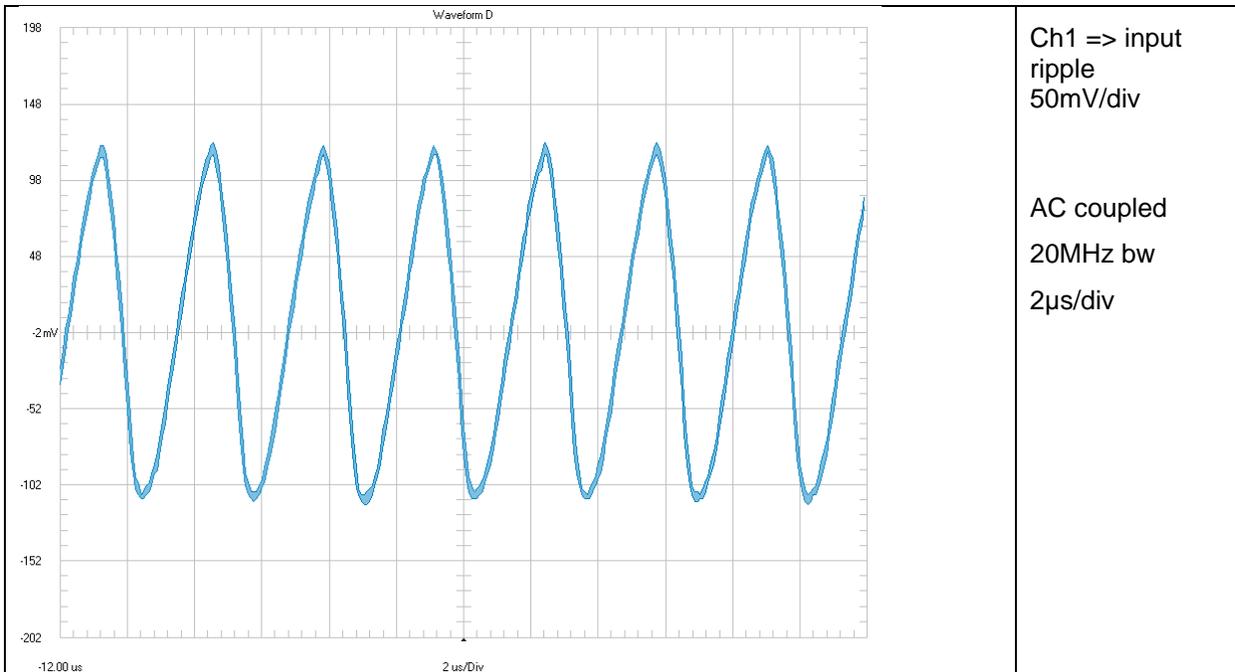


Figure 14

The input ripple voltage at 60V is shown in Figure 15.

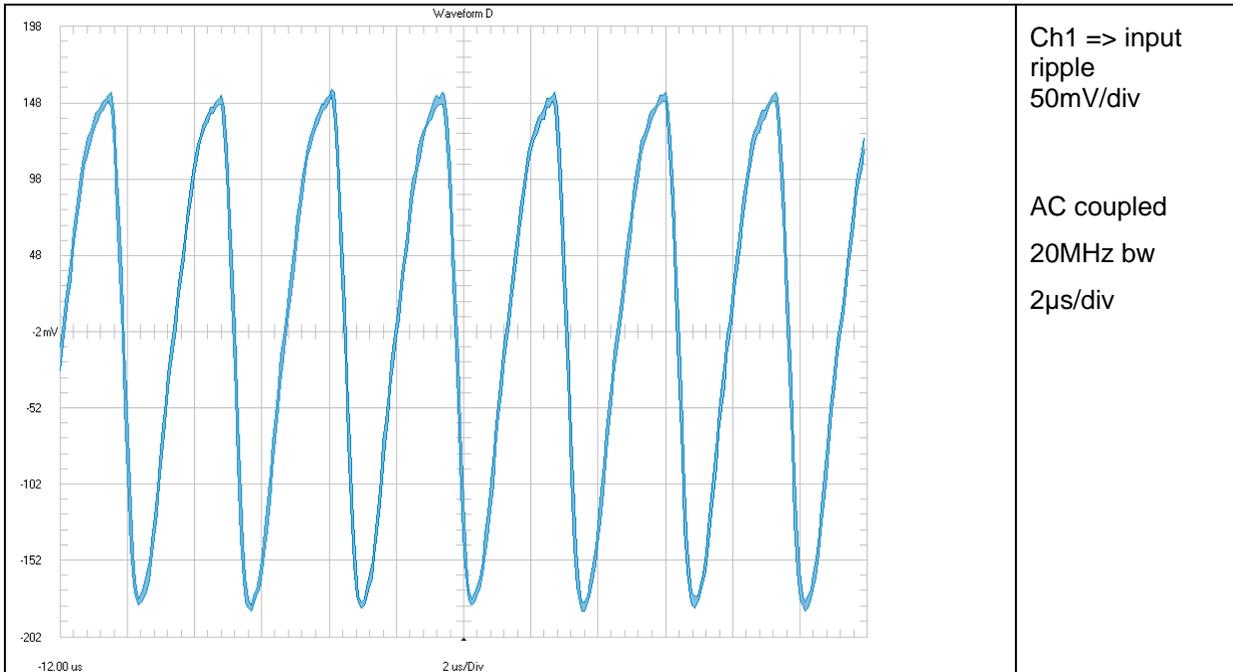


Figure 15

The reflected ripple to input is related to power source impedance, here around 350mVpp almost sinusoidal – means the RF content is far lower than at inverting Buck Boost topology.

8 Load Transients

The Figure 16 shows the response to load transients at 6V input voltage. The electronic load is switching from 0.070A to 0.14A (100Hz) (electronic load).

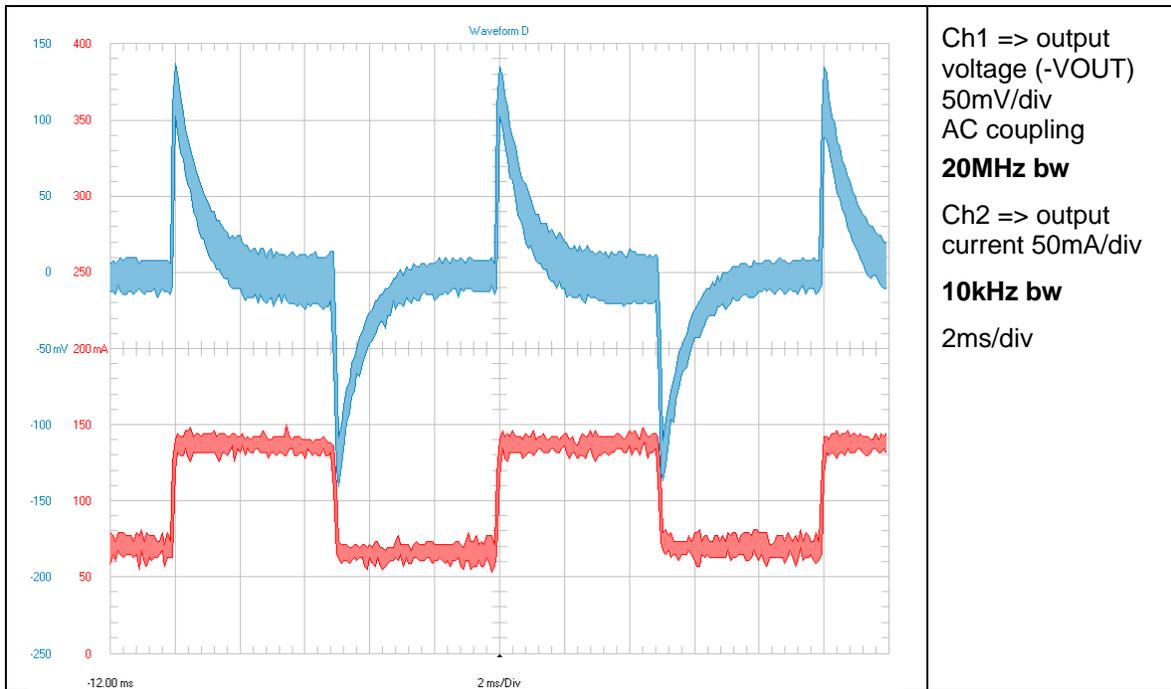


Figure 16

The Figure 17 shows the response to load transients at 12V input voltage. The load is switching from 0.1A to 0.2A (100Hz).

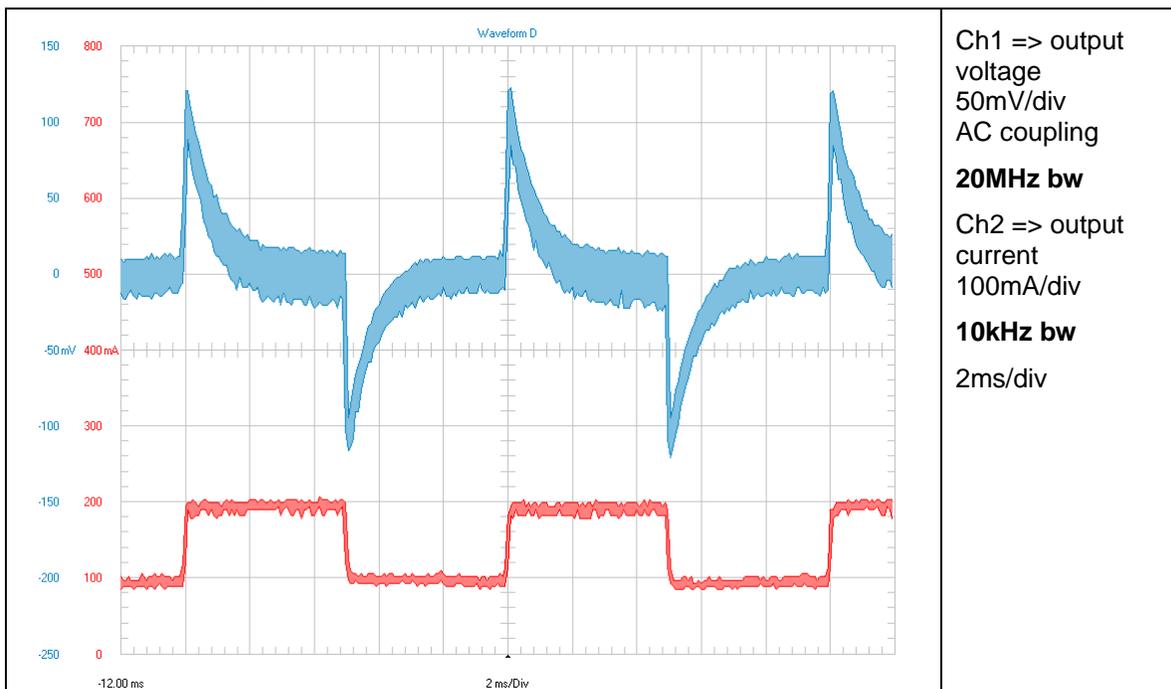


Figure 17

The Figure 18 shows the response to load transients at 36V input voltage.
The load is switching from 0.1A to 0.2A (100Hz).

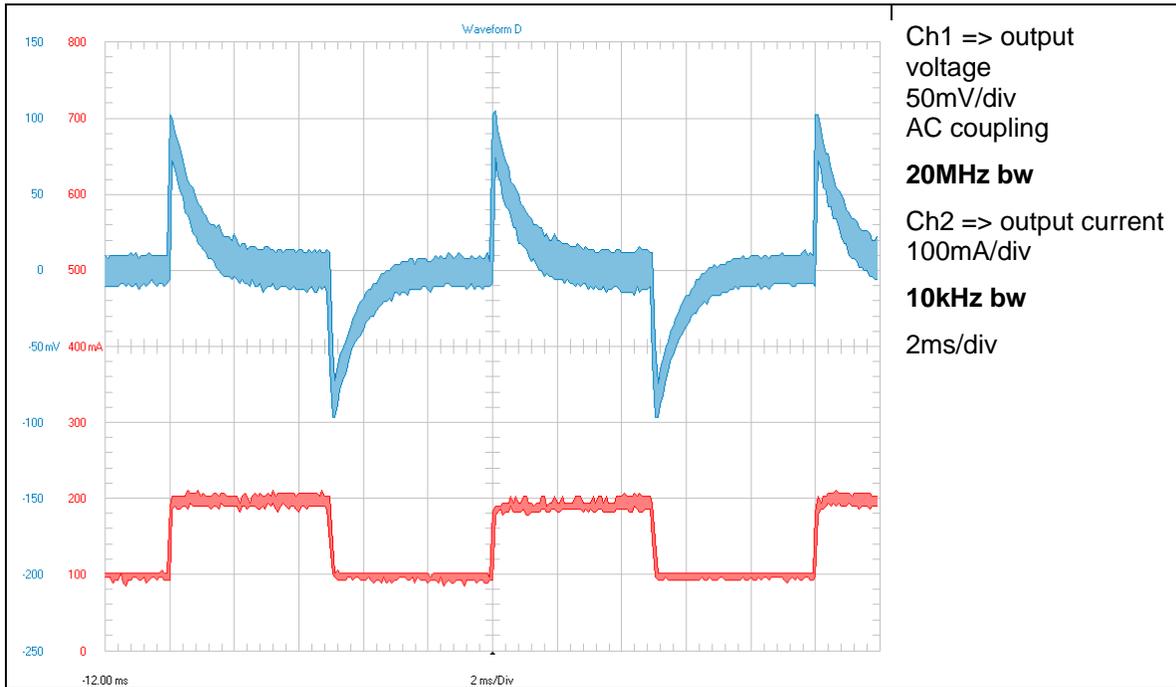


Figure 18

The Figure 19 shows the response to load transients at 60V input voltage.
The electronic load is switching from 0.1A to 0.2A (100Hz).

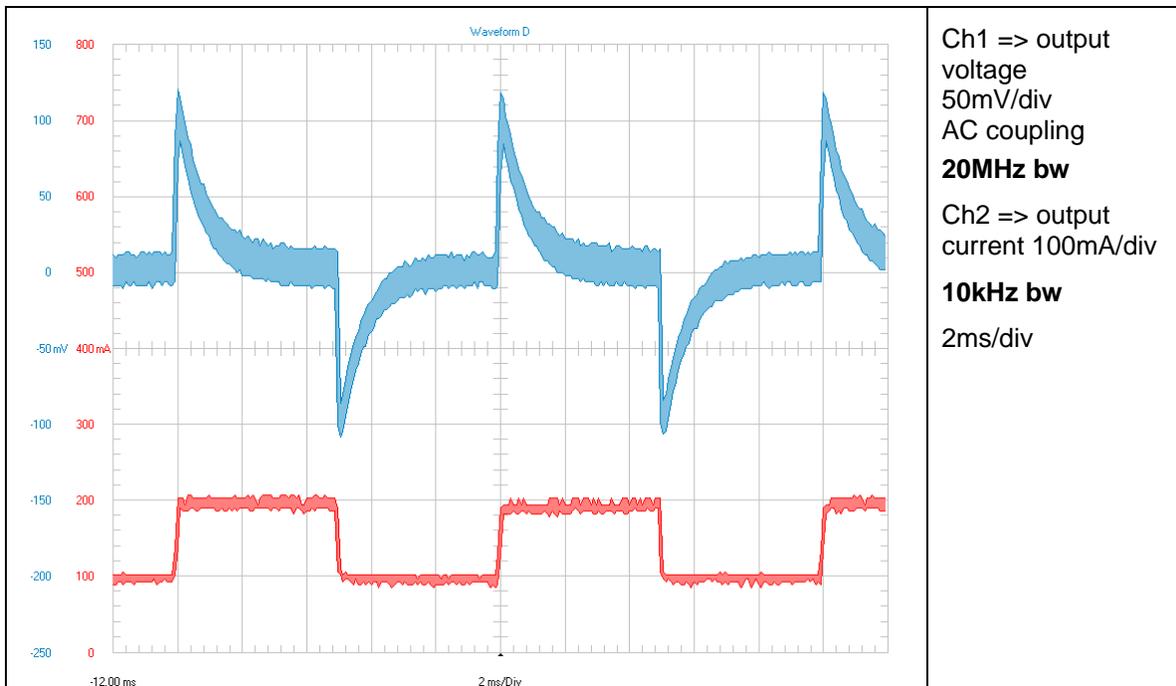


Figure 19

9 Control Loop Frequency Response

Figure 20 shows the loop response for 6V_{in}. Load is 0.14A.

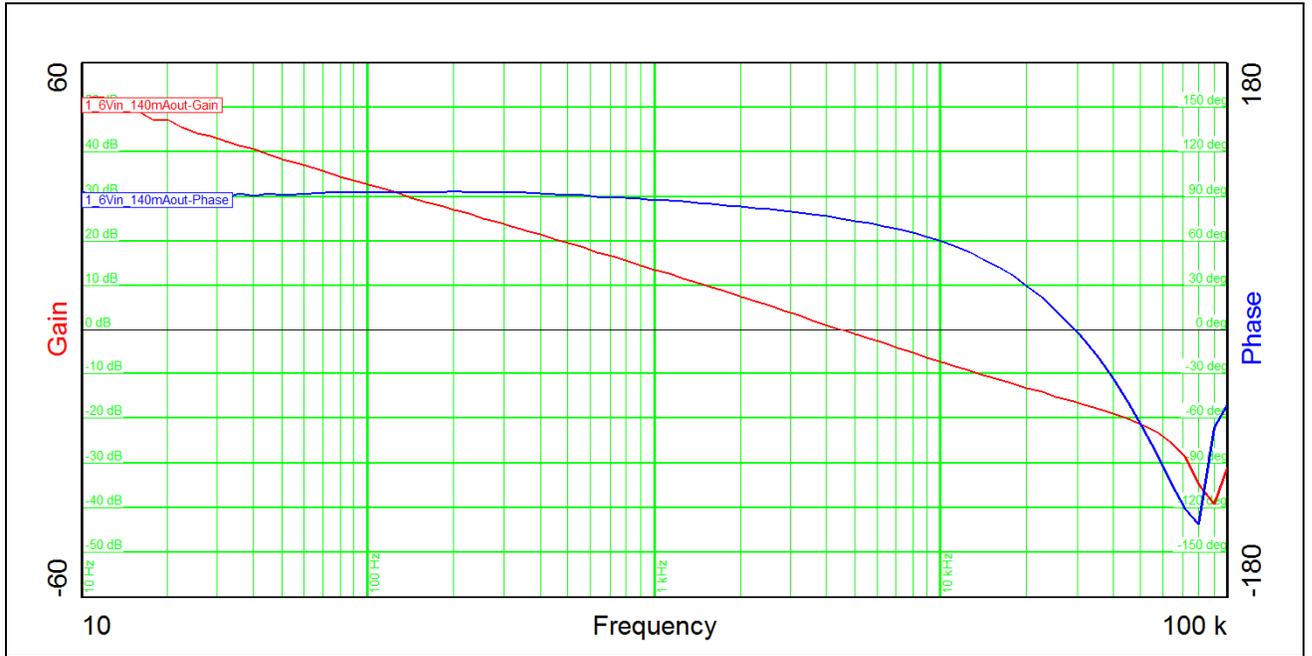


Figure 20

Figure 21 shows the loop response for 12V_{in}. Load is 0.2A.

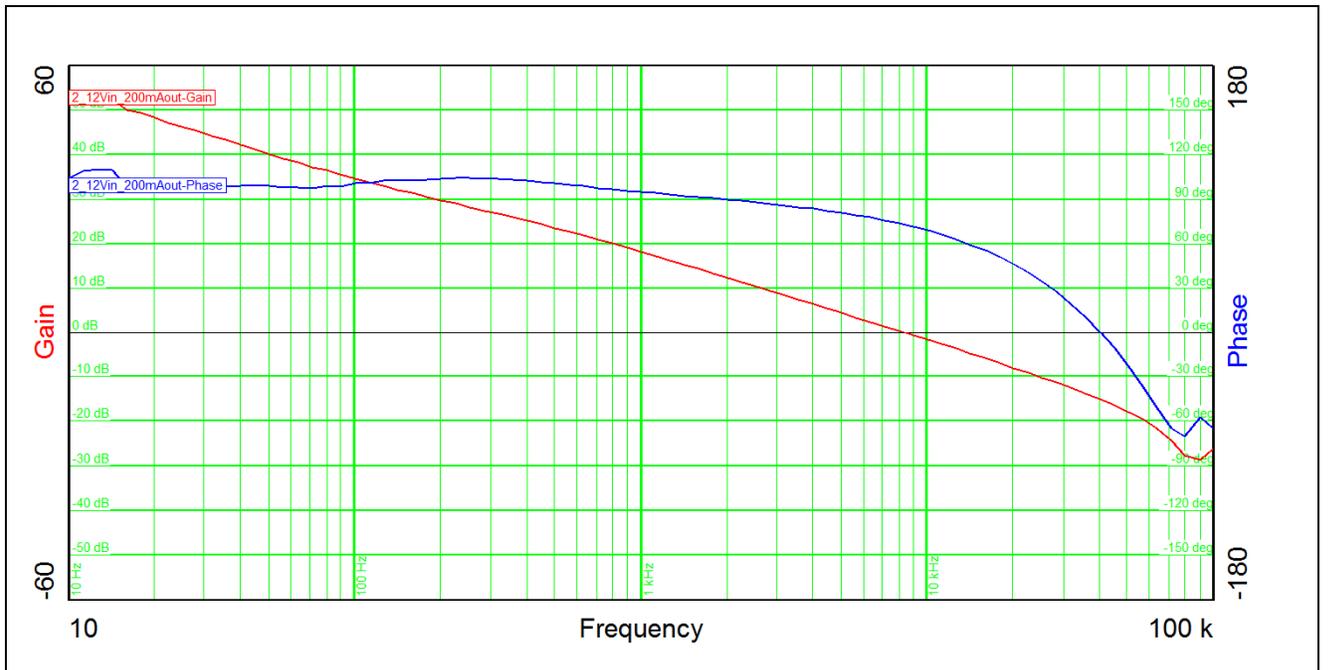


Figure 21

Figure 22 shows the loop response for 36Vin. Load is 0.2A.

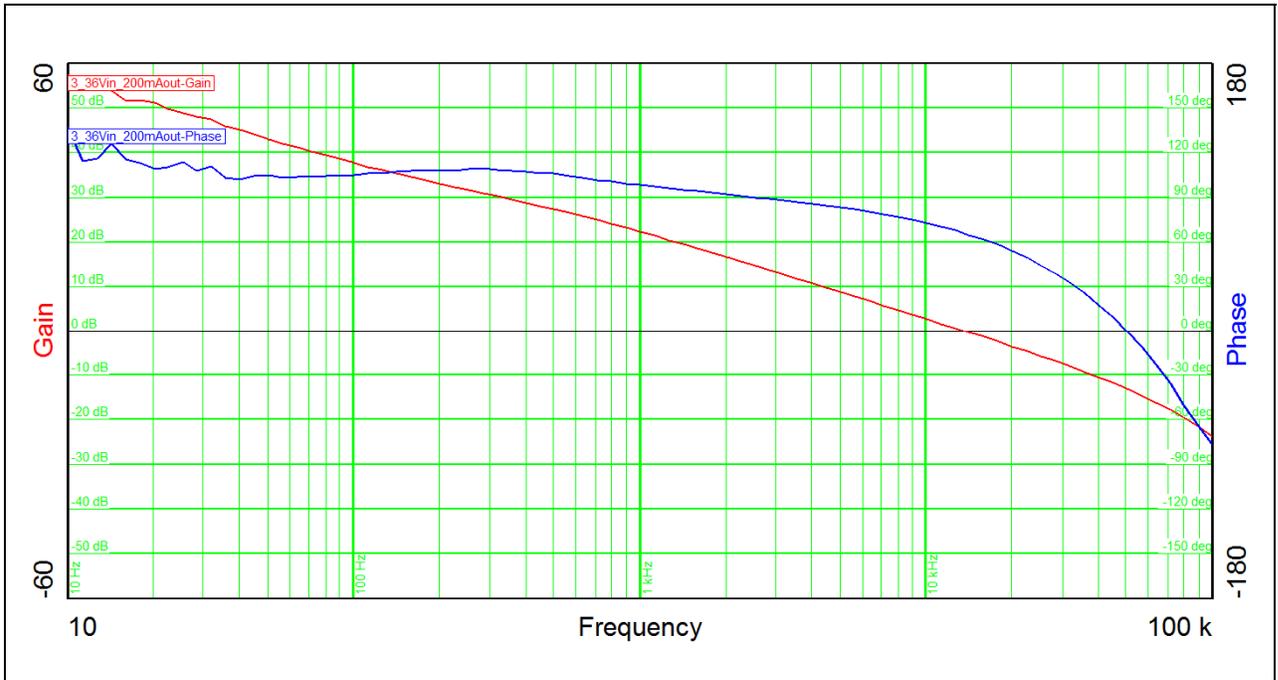


Figure 22

Figure 23 shows the loop response for 60Vin. Load is 0.2A.

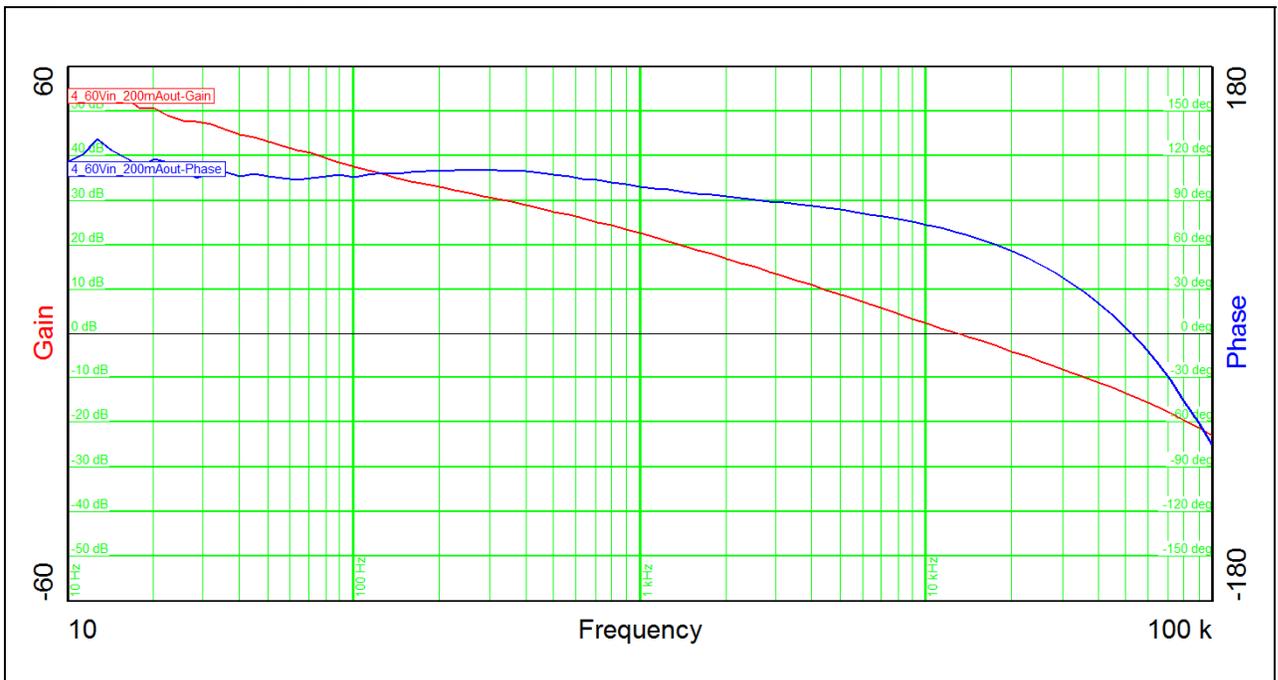


Figure 23

Table 1 summarizes the results of the above measurements

Vin	6V	12V	36V	60V
Bandwidth (kHz)	4.5	8.4	13.7	13.0
Phase margin	75°	72.8°	65.8°	68.3°
slope (20dB/decade)	-1.09	-1.04	-1.05	-1.12
gain margin (dB)	-16.3	-15.1	-13.1	-14.1
slope (20dB/decade)	-0.94	-1.35	-1.38	-1.33
freq (kHz)	29.4	40.4	50.4	52.4

Table 1

The transient response on a 50% load step is around 120mVpk, means the dynamic deviation is only 1%. The Bode plot is optimized for lowest loop bandwidth 4.5kHz at 6V input. Despite some papers describe Cuk compensation as difficult it could be shown that at low magnetizing inductance the results are perfect – a flat phase around +90 degrees and a fine gain slope at -1 (-20dB/decade).

10 Miscellaneous Waveforms

10.1 Switch Node (TP4)

The waveform of the voltage on switch node is shown in Figure 24. Input voltage was set to 12V.

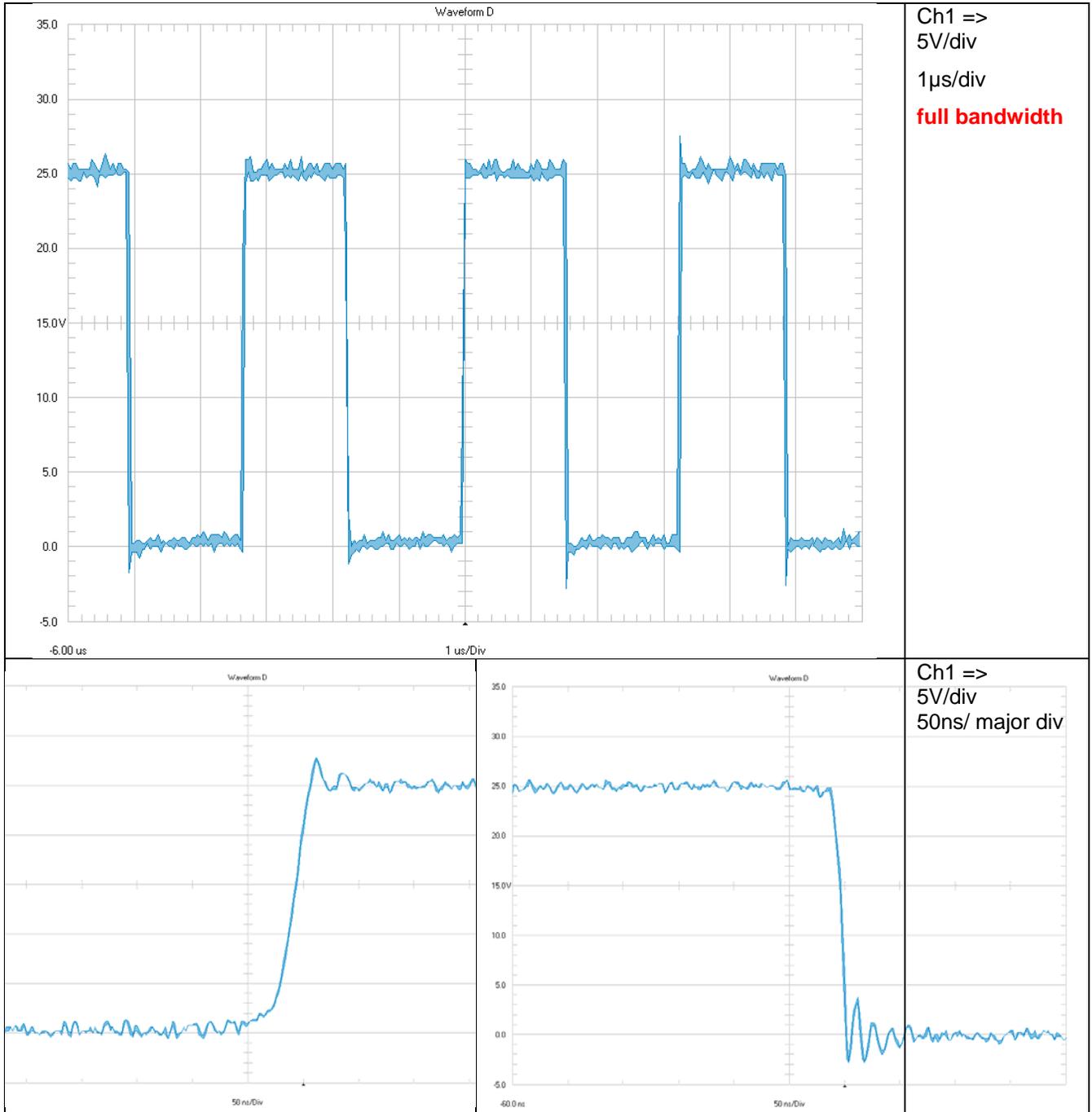


Figure 24

The waveform of the voltage on the switch node is shown in Figure 25. Input voltage was set to 36V.

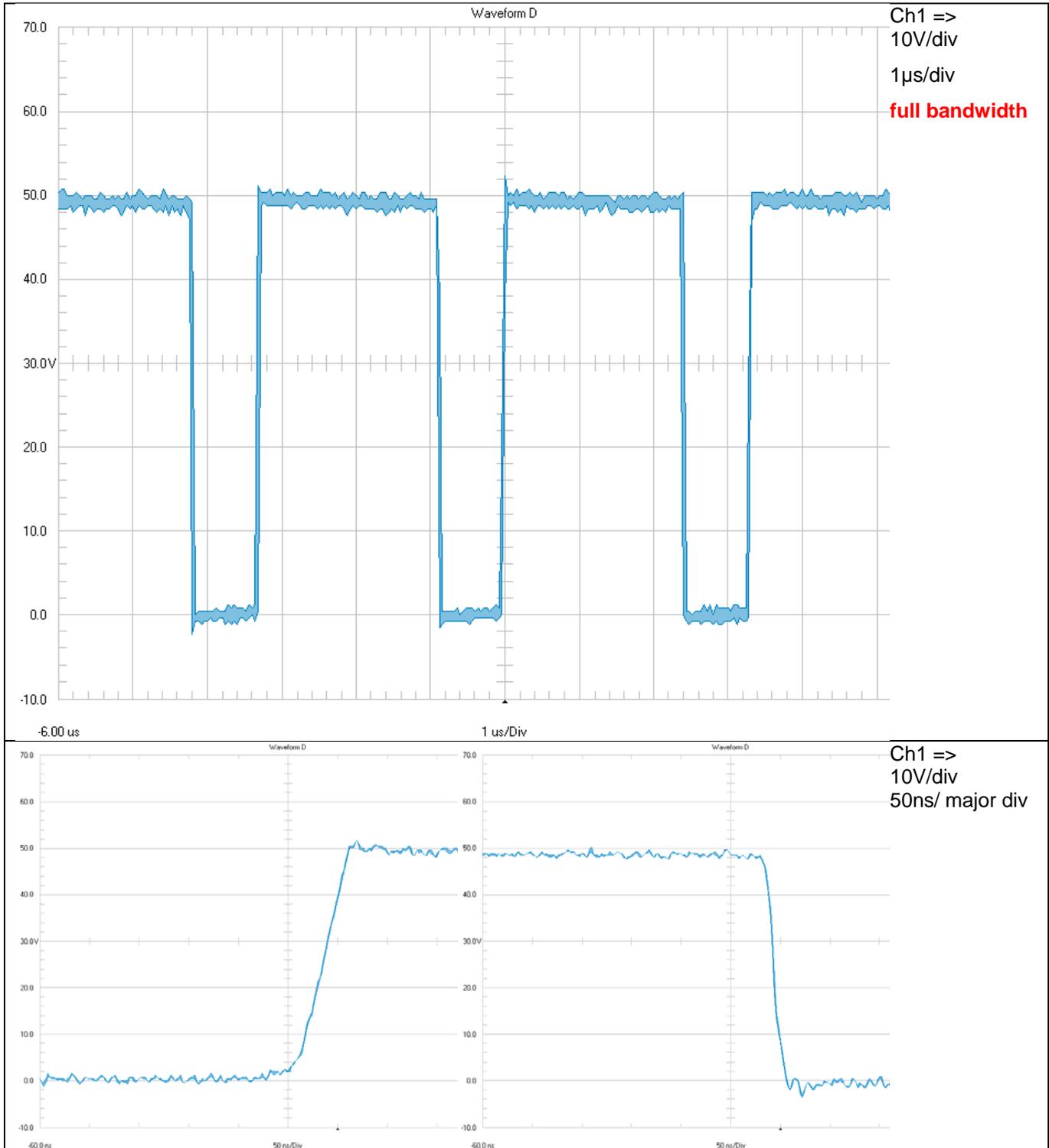


Figure 25

The waveform of the voltage on switch node is shown in Figure 26. Input voltage was set to 60V.

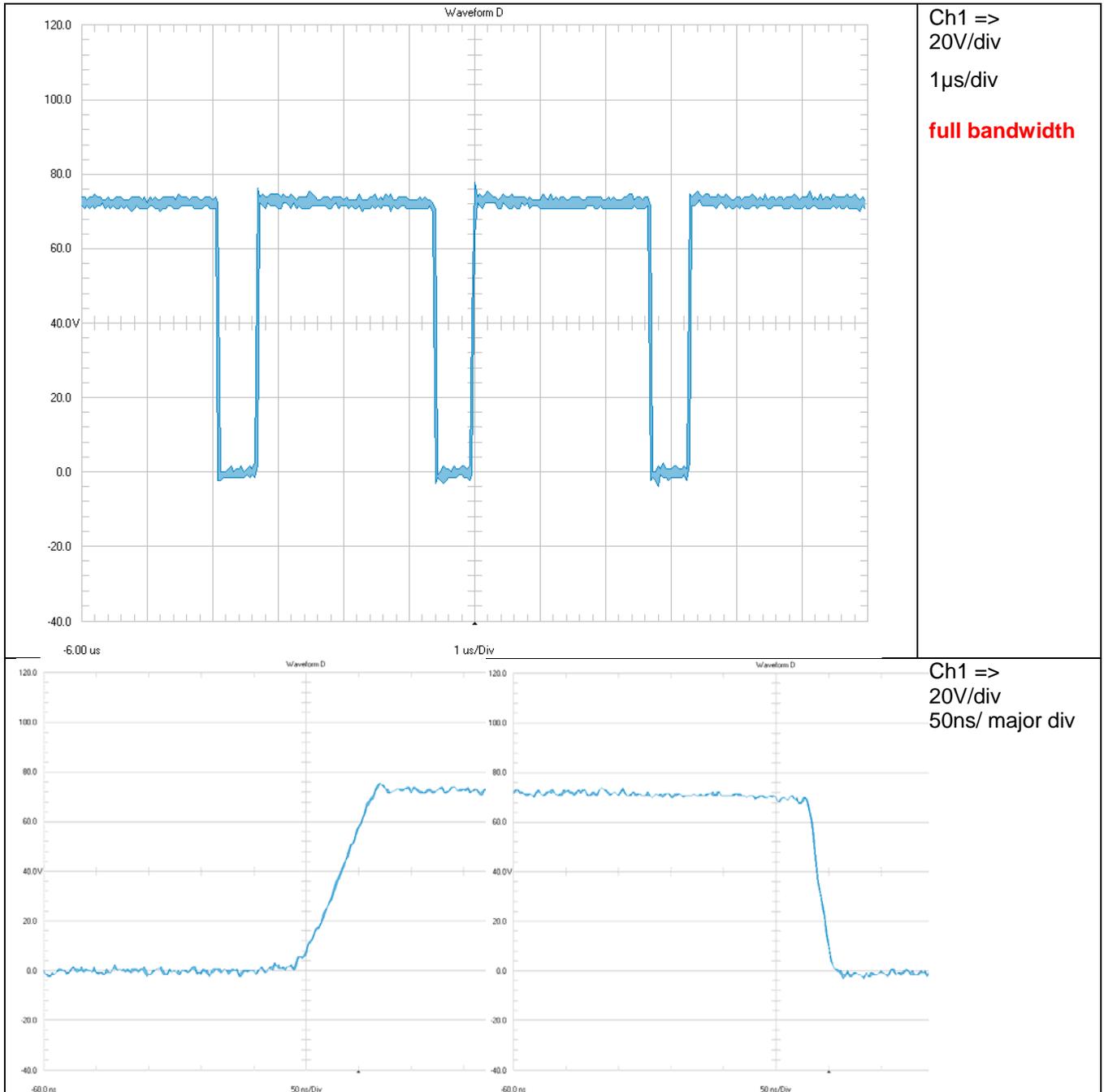


Figure 26

The drain pulse of 72V (input voltage + output voltage) shows perfect switching behavior. Despite a rise time of only 15ns there is almost NO overshoot, NO undershoot, there is NO RF ringing ! **Providing a reasonable layout to the CuK topology results in lowest radiated emissions.**

10.2 Diode D1 (TP6)

The waveform of the voltage on TP6 to GND is shown in Figure 27. Input voltage was set to 12V.

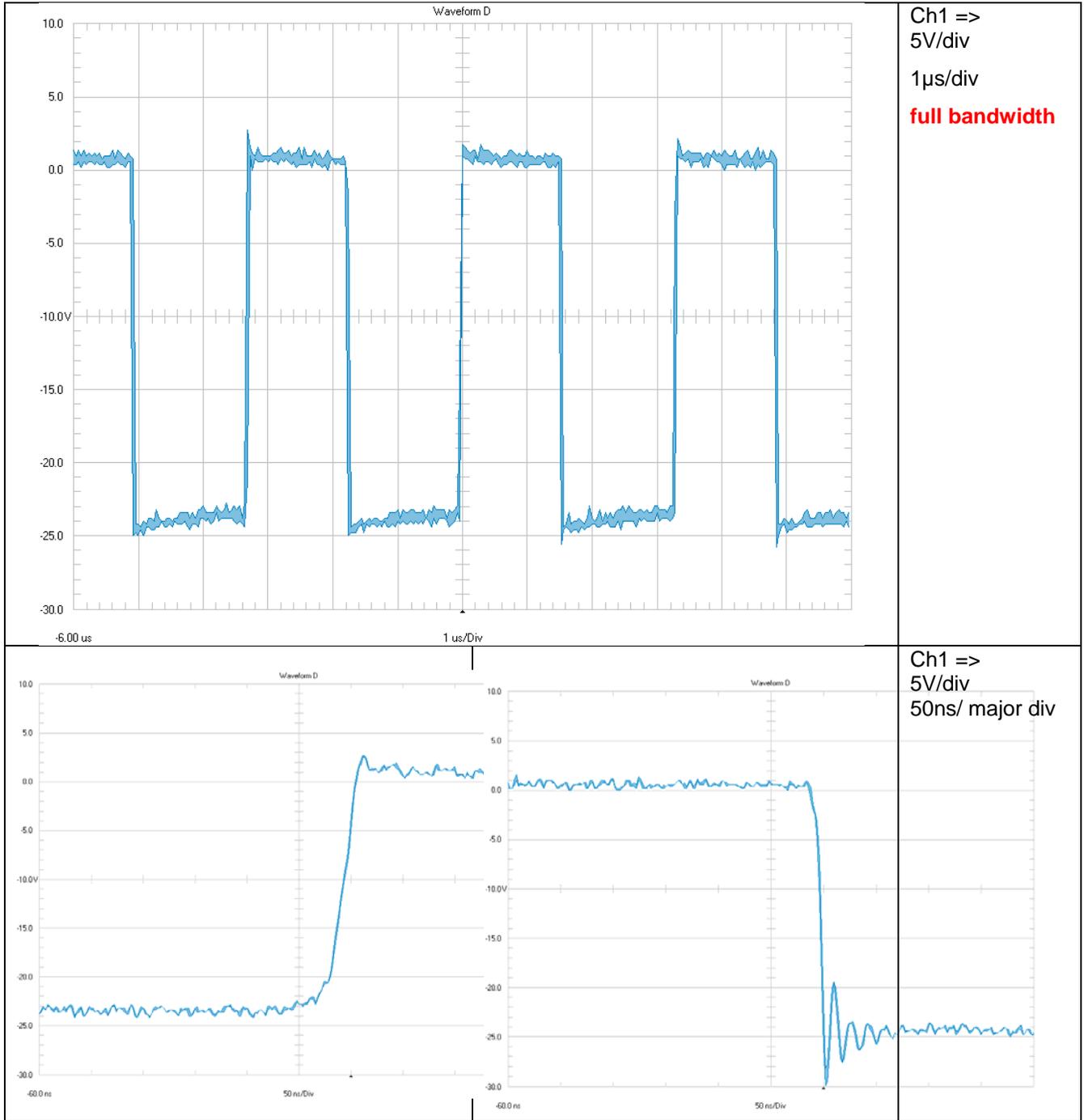


Figure 27

The waveform of the voltage on TP6 to GND is shown in Figure 28. Input voltage was set to 36V.

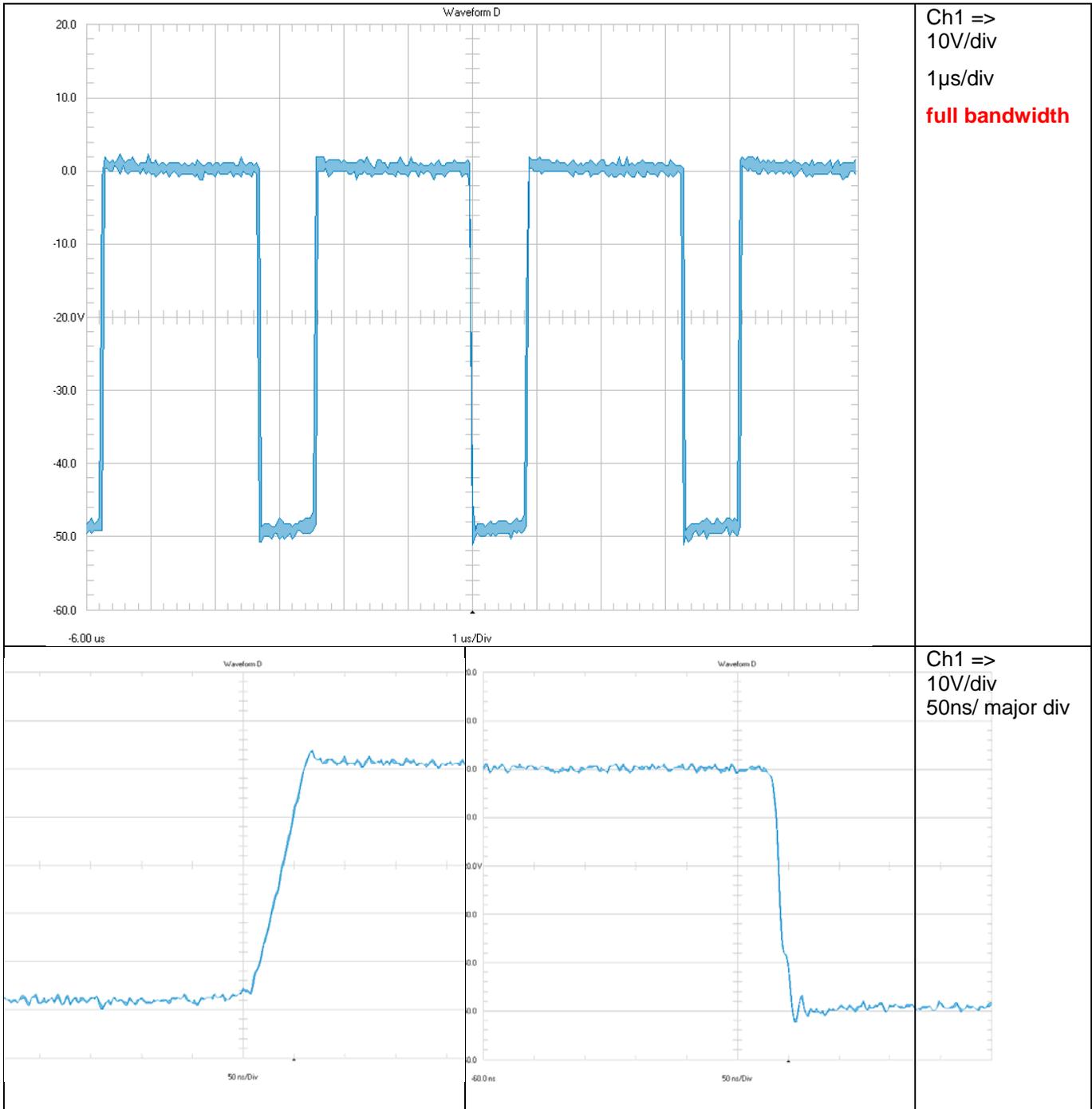


Figure 28

The waveform of the voltage on TP6 to GND is shown in Figure 29. Input voltage was set to 60V.

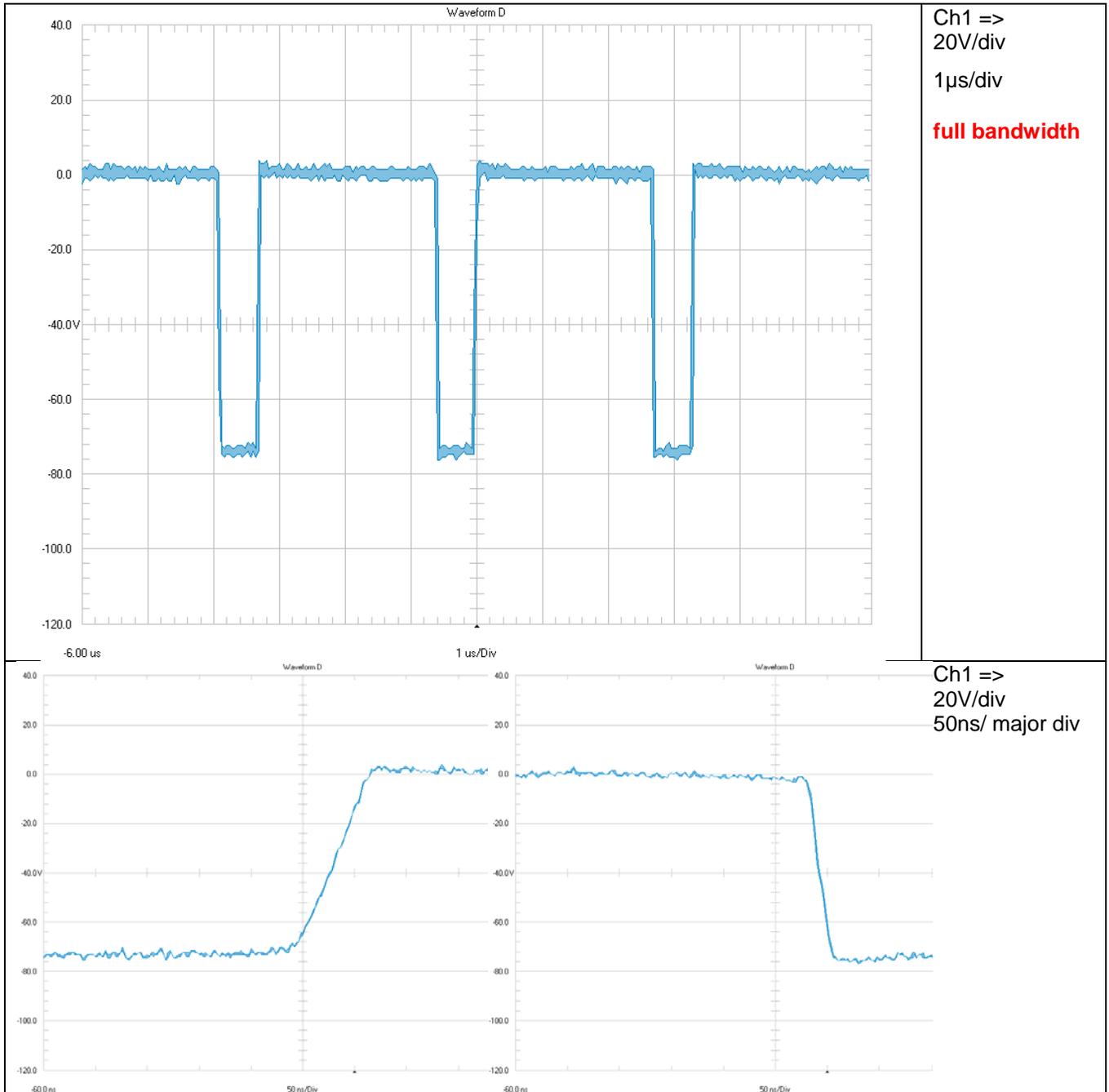


Figure 29

The flying capacitor placed in between FET drain and rectifier anode is clamping the diode as well; again no overshoot, no undershoot, no ringing – **overall NO RF distortion !**

Waveforms for Transission Mode, DCM operating:

- at 6V input < 30mA load current,
- at 10V input < 50mA load current
- at 24V input <120mA load current,
- at 36V input <160mA load current
- at 48V input <180mA load current,
- at 60V input <200mA load current (pure DCM)

11 Thermal Image @ Vin 6V /12V / 36V / 60V

Figure 30 shows the thermal image at 6V input voltage and 140mA output current.

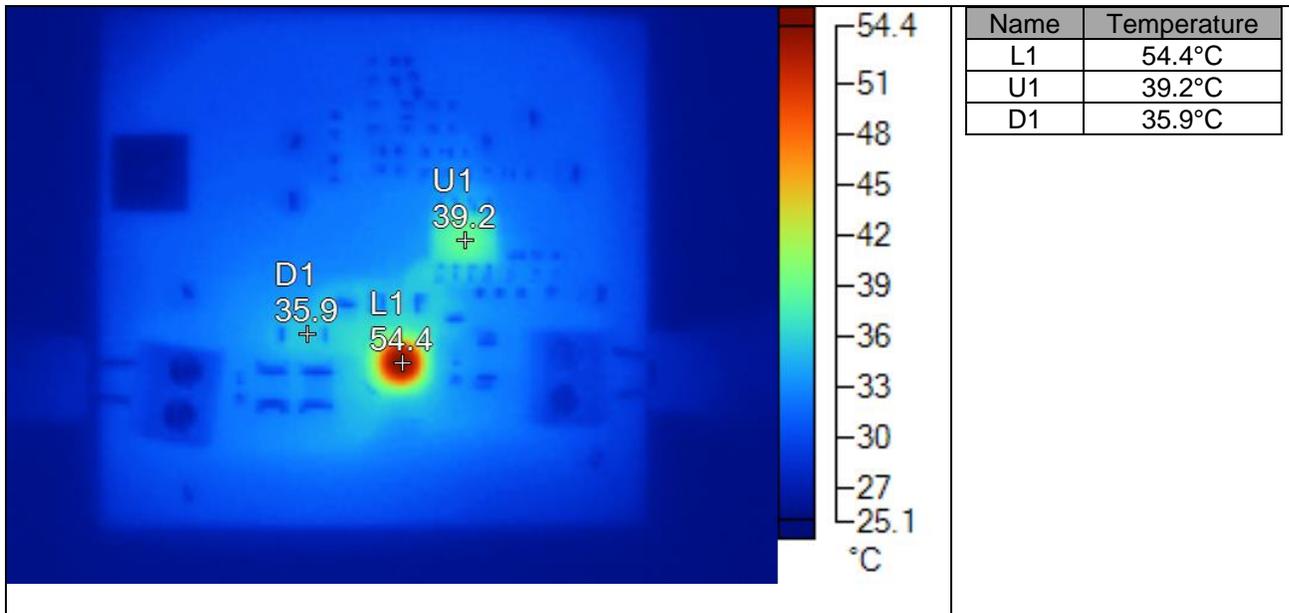


Figure 30

Figure 31 shows the thermal image at 12V input voltage and 200mA output current.

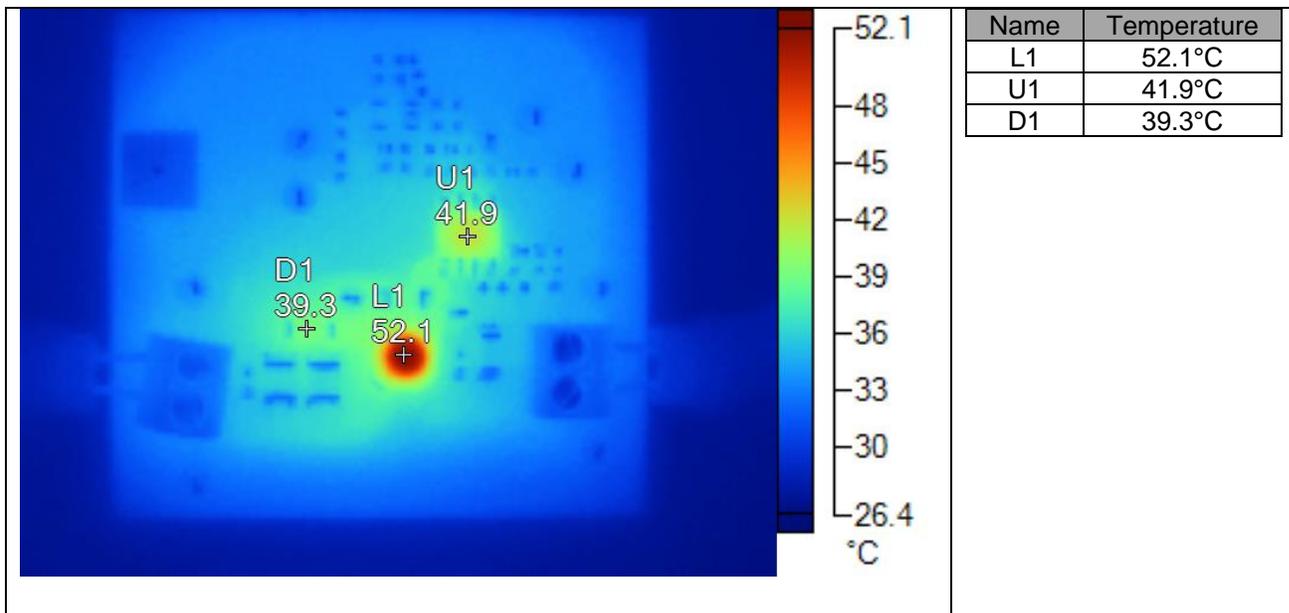


Figure 31

Figure 32 shows the thermal image at 36V input voltage and output current 200mA.

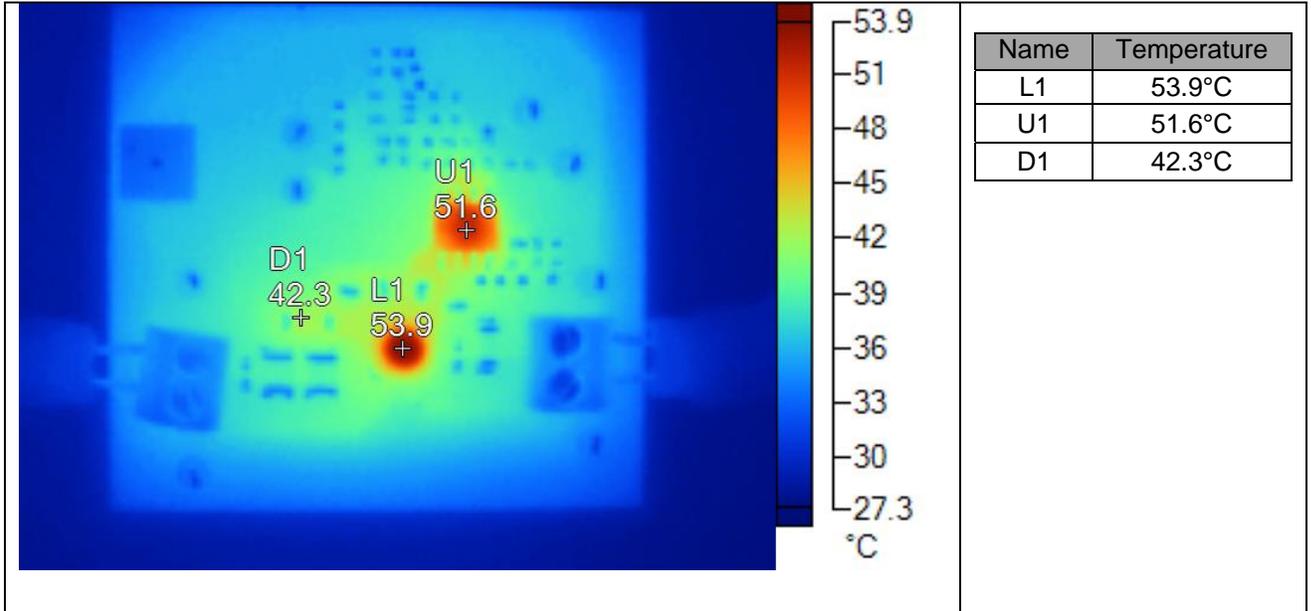


Figure 32

Figure 33 shows the thermal image at 60V input voltage and output current 200mA.

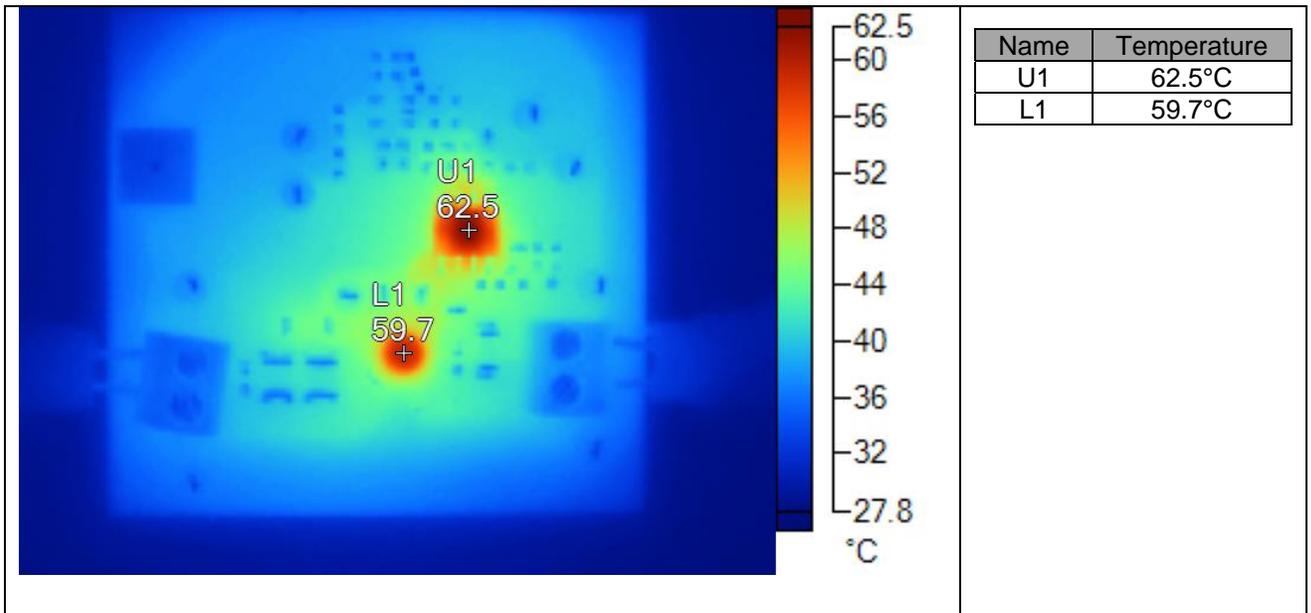


Figure 33

At high input voltage the losses at internal linear regulator and the switching losses at the internal FET are getting dominant, efficiency drops – but the temperature rise below +40K is still acceptable for industrial temperature range.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated