

Getting the Full Potential from Your ADC

John Austin

ABSTRACT

Many of today's high-resolution ADCs (Analog-to-Digital Converters) are operating from a single supply and utilize fully differential inputs. This can be a problem for single ended signals that are bipolar relative to common. This article will illustrate circuit configurations that will preserve the full-scale input range by utilizing modern features, such as Programmable Gain Amplifiers (PGAs) and internal voltage reference. It will also discuss issues that the designer must consider when selecting components utilizing these signal-conditioning circuits.

The differential inputs provide common-mode rejection eliminating much of the system noise imposed on the input signal. In most converters, the reference inputs determine the full-scale analog input range as well as the position of bipolar zero of the analog input signal.

For truly differential input ADCs without a built-in PGA, [Figure 1](#) is a proposed solution.

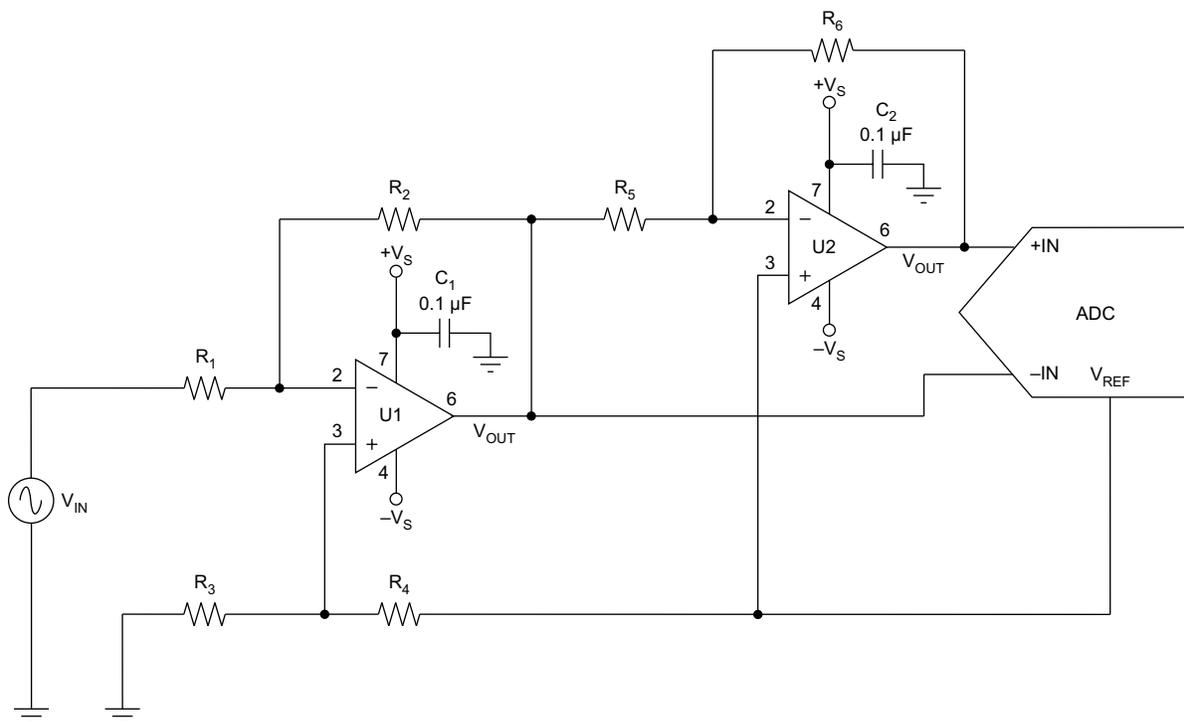


Figure 1. Circuit Schematic to Convert a Single-Ended Bipolar Input to a Unipolar Differential Output.

The transfer equations are derived using basic circuit analysis and general operational amplifier theory. See [Appendix A](#) for the detailed derivation.

$$\frac{R_2}{R_1} = G_{(U1)}$$

$$\frac{R_6}{R_5} = G_{(U2)}$$

$$\frac{R_3}{R_3 + R_4} = \frac{V_{BIAS}}{V_{REF} (G_{(U1)} + 1)} = \frac{1}{(G_{(U1)} + 1)} \quad (1)$$

For example, assuming a converter requires a full-scale differential input of 2.5Vp-p referenced at 2.5V DC operating from a single 5V supply. Knowing the DC bias value, the gain/attenuation, and the power supply, the resistor values are calculated using the equations provided. The input signal $V_{IN} = 5Vp-p$ (bipolar).

The required resistor ratios, corresponding to [Figure 1](#), are calculated as follows:

$$\frac{R_2}{R_1} = G_{(U1)} = 1/2$$

$$\frac{R_6}{R_5} = G_{(U2)} = 1$$

$$\frac{R_3}{R_3 + R_4} = \frac{V_{BIAS(U1)}}{V_s (G_{(U1)} + 1)} = (2.5) / [5(1/2 + 1)] = 1/3 \quad (2)$$

From these ratios we can determine resistor values. The resistor values used for this example were $R_1 = R_4 = R_5 = R_6 = 300k\Omega$ and $R_2 = R_3 = 150k\Omega$. [Figure 2](#) displays the input signal ($V_{IN} = 5Vp-p$ bipolar) and the differential output (V_{OUT+} and V_{OUT-}). The output corresponds to a 2.5Vp-p differential signal DC biased at 2.5V.

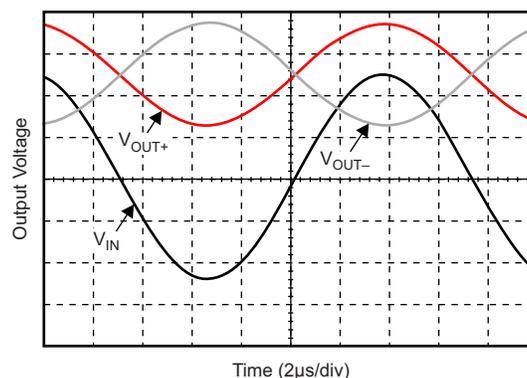


Figure 2. Scope Trace (Circuit of [Figure 1](#)), $V_{IN} = 5Vp-p$ (Bipolar), with a Corresponding Differential Output, (V_{OUT+} , V_{OUT-}) = 2.5Vp-p Biased at 2.5V DC.

If the ADC does not have an internal voltage reference, one might assume that a simple resistor divider from the power supply would suffice for the reference input to the ADC. The designer must keep in mind that any change on the voltage reference will cause a one-to-one change in the output of the converter. Resistors tend to drift and are the cause of unwanted noise. Utilizing a precision, low-drift, low-noise voltage reference is always a good design practice.

The new multi-feature ADCs, such as the ADS7870, ADS1210/ADS1211, ADS1212, and ADS1250 from Texas Instruments offer both a PGA and internal voltage reference. [Figure 3](#) implements these features providing a simple resistor network as a possible solution.

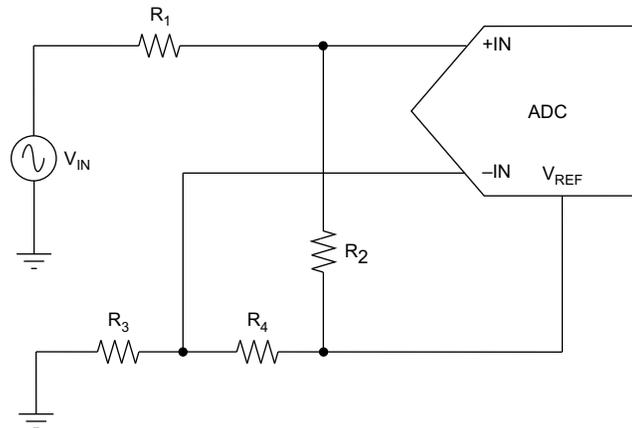


Figure 3. Utilizing a Resistive Network to Achieve Attenuation and DC Bias of the Input Signal.

This configuration can provide more accurate results and minimize the number of components. One could assume that this would not provide any better accuracy and would only bring a similar gain circuit into the ADC. Certainly this circuit would minimize components and lower cost, which would be a benefit to the designer.

The transfer equations are as follows. See [Appendix A](#) for a detailed derivation.

$$\frac{R_2}{R_1 + R_2} = 1/2$$

$$\frac{R_3}{R_3 + R_4} = \frac{R_2}{R_1 + R_2} = 1/2 \tag{3}$$

From these ratios the resistor values were chosen to be R₁ = R₂ = R₃ = R₄ = 150kΩ. The pseudo-differential value, [+In – (–In)], corresponds to a 2.5Vp-p. Utilizing a PGA setting of 2 effectively utilizes the full-scale input range.

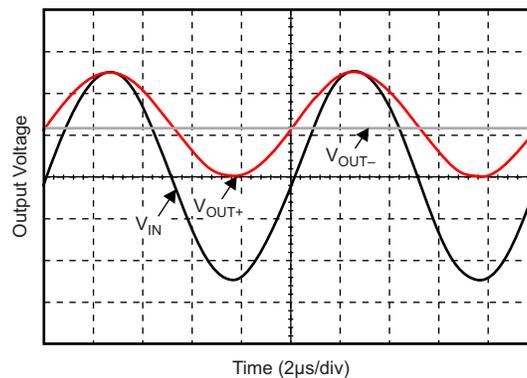


Figure 4. Scope Trace, V_{IN} = 5Vp-p V_{IN} = 5Vp-p (Bipolar), with a Corresponding Output, V_{OUT+} = 2.5Vp-p Biased at 2.5V DC, V_{OUT-} = 2.5V DC.

Loading the reference can cause undesired drift of the reference voltage. The designer must also consider the input impedance of the ADC. Low input impedance may cause signal loss. If this becomes an issue, [Figure 5](#) can be implemented.

R₄/R₃ provides the DC bias while R₂/R₁ provides the attenuation/ gain. The PGA amplifies the differential signal [+In – (–In)], effectively preserving the full-scale input range of the device.

$$\frac{R_2}{R_1} = G_{(U1)} = 1/2$$

$$\frac{R_3}{R_3 + R_4} = \frac{1}{G_{(U1)} + 1} = \frac{1}{\frac{1}{2} + 1} = \frac{2}{3}$$
(4)

From these ratios the resistor values were chosen to be $R_1 = R_3 = 100\text{k}\Omega$, $R_2 = R_4 = 200\text{k}\Omega$. The pseudo-differential value, $[+In - (-In)]$, corresponds to a 2.5Vp-p . A PGA setting of 2 maintains the full-scale range of this device. Without the PGA this circuit $[(+In) - (-In)]$ would only make use of half of the full-scale input range.

Component selection is critical when dealing with high resolution applications. The main selection criteria for the operational amplifier includes offset voltage drift and noise. DC offset, such as gain error and input offset voltage, can be taken out through software calibration or by internal calibration of the ADC.

The lowest drift amplifiers are those that are chopper stabilized, such as the Texas Instruments TLC2652. This amplifier has a supply range of $\pm 1.9\text{V}$ to $\pm 8\text{V}$, offering very low offset voltage (1mV) and low offset voltage drift ($3\text{nV}/^\circ\text{C}$). These amplifiers have limited bandwidth and generate more noise than other amplifier architectures. The TLC2652 has a maximum voltage noise of $35\text{nV}/\sqrt{\text{Hz}}$ (at 1kHz) and a typical unity-gain bandwidth of 1.9MHz . This amplifier is more suitable for low-frequency applications.

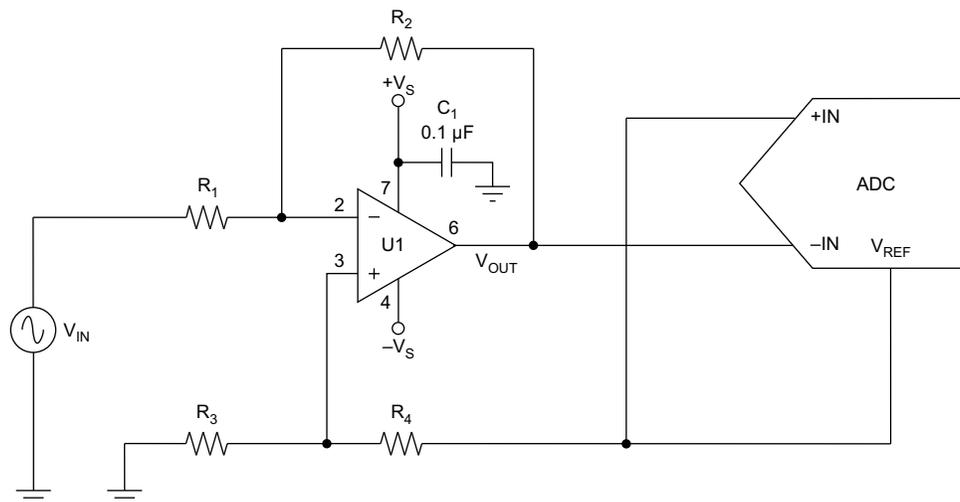


Figure 5. Circuit Schematic Utilizing the Programmable Gain Amplifier and Output Voltage Reference.

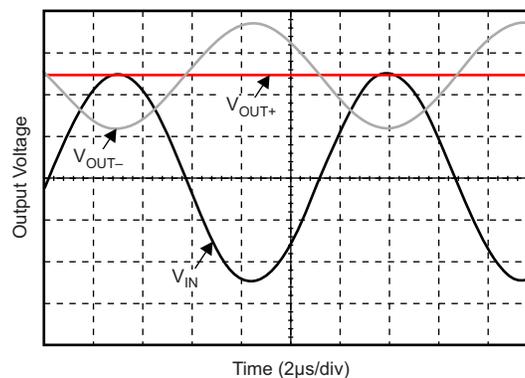


Figure 6. Scope Trace, $V_{IN} = 5\text{Vp-p}$ V_{IN} (bipolar), with a Corresponding Output, $V_{OUT+} = 2.5\text{V DC}$ $V_{OUT-} = 2.5\text{Vp-p}$ Biased at 2.5V DC

DIFET amplifiers offer low-voltage drift (100s of nV/°C), have very low noise (less than 10nV/√Hz) and offer higher unity gain bandwidth than chopper-stabilized operational amplifiers. These would be considered for higher frequency applications where noise might become a larger factor than voltage drift. The major drawback is cost.

Amplifiers implementing a bipolar process can offer good precision, higher unity-gain bandwidth, and maintain low noise at a relatively low cost. An example would be the OPA227 family of operational amplifiers. This operational amplifier has low voltage drift (300nV/°C (max)) and very low voltage noise (3nV/√Hz (max)). This amplifier has an 8MHz unity-gain bandwidth (min) and a slew rate of 2.3V/μs (min) and would be a good choice for high-frequency applications. It also provides a cost-effective solution at a price well under a dollar per channel.

CMOS amplifiers are probably the most inaccurate but the most cost effective. These are typically single-supply amplifiers. A good example is the OPA340 series from Texas Instruments. These are single-supply 2.7V to 5.5V amplifiers with an input voltage range of 300mV beyond the supply rails and an output voltage that can swing to within 1mV of the supply rails. These devices tend to have higher noise characteristics (25nV/√Hz (max)) and larger voltage drift (2.5μV/0°C (max)). They should be used in lower resolution applications where cost is of more concern than resolution.

This document has provided three signal-conditioning circuits that allow the designer to make use of a fully-differential ADC when utilizing a single-ended signal source. Operational amplifier architectures discussed have both benefits and pitfalls to consider and weigh according to the specifics of the application. The accuracy provided by these circuits is directly related to the component selection and the parameters discussed. Other design considerations are board layout, power-supply selection, and good filtering techniques.

APPENDIX A

Derivation of the transfer equations for the circuit of [Figure 1](#).

From the model for an ideal operational amplifier, we assume infinite input impedance. This implies there is no current into the operational amplifier.

$$I_{R1} = I_{R2} \tag{5}$$

$$\frac{V_{IN} - V_{2(U1)}}{R_1} = \frac{V_{2(U1)} - V_{OUT}}{R_2} \tag{6}$$

Combining terms and solving for V_{OUT-} yields:

$$V_{OUT-} \frac{R_2}{R_1} = V_{2(U1)} \left(\frac{R_2}{R_1} + 1 \right) \tag{7}$$

Making the substitution that the voltage at pin 2 is equal to the voltage at pin 3 gives:

$$V_{OUT-} = \frac{R_2}{R_1} V_{IN} + \left(\frac{R_2}{R_1} + 1 \right) (V_{3(U1)}) \tag{8}$$

The voltage at pin 3 can easily be calculated by a voltage divider.

$$V_{3(U1)} = \frac{R_3}{R_3 + R_4} (V_S) \tag{9}$$

Combining [Equation 9](#) with [Equation 8](#) yields:

$$V_{OUT-} = -\frac{R_2}{R_1} V_{IN} + V_S \left(\frac{R_2}{R_1} + 1 \right) \left(\frac{\frac{R_3}{R_3}}{R_3 + R_4} \right) \tag{10}$$

Where the DC bias value is:

$$V_{\text{BIAS}(U1)} = \left[\left(\frac{R_2}{R_1} + 1 \right) \left(\frac{R_3}{R_3 + R_4} \right) \right] V_{\text{REF}} \quad (11)$$

Equation 10 provides the final transfer equation for operational amplifier U1. The input signal is inverted with a gain/attenuation of (R_2/R_1) and a DC bias corresponding to Equation 11. If we let $(R_2/R_1) = G(U1)$ (gain) and solve for the resistor ratio $R_3/(R_3 + R_4)$, Equation 11 yields:

$$V_{\text{BIAS}(U1)} = \left[\left(\frac{R_2}{R_1} + 1 \right) \left(\frac{R_3}{R_3 + R_4} \right) \right] V_{\text{REF}} \quad (12)$$

Derivation of transfer equations for the circuit of Figure 3.

The input $+I_N$ can be calculated by:

$$+I_N = \frac{R_2}{R_1 + R_2} V_{\text{IN}} + \frac{R_1}{R_1 + R_2} V_{\text{REF}} \quad (13)$$

$-I_N$ requires the same DC voltage as the DC bias voltage of $+I_N$. This requires the resistor ratios be the same:

$$\frac{R_1}{R_1 + R_2} = \frac{R_3}{R_3 + R_4} \quad (14)$$

Solving for the resistor ratios yields:

$$\begin{aligned} \frac{R_2}{R_1 + R_2} &= \frac{+I_N}{V_{\text{IN}}} \\ \frac{R_3}{R_3 + R_4} &= \frac{R_2}{R_1 + R_2} \end{aligned} \quad (15)$$

Revision History

Changes from A Revision (March 2001) to B Revision	Page
• Changed format to the latest TI application report template.....	1

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com