

# Isolated Current-Sensing Circuit With $\pm 50\text{-mV}$ Input and Differential Output



Data Converters


Samiha Sharif

## Design Goals

Current Source		Input Voltage		Output Voltage		Single Power Supply
$I_{IN\ MIN}$	$I_{IN\ MAX}$	$V_{IN\ DIFF,\ MIN}$	$V_{IN\ DIFF,\ MAX}$	$V_{OUT\ DIFF,\ MIN}$	$V_{OUT\ DIFF,\ MAX}$	$V_{DD}$
-50 A	50 A	-50 mV	50 mV	-2.05 V	2.05 V	5 V
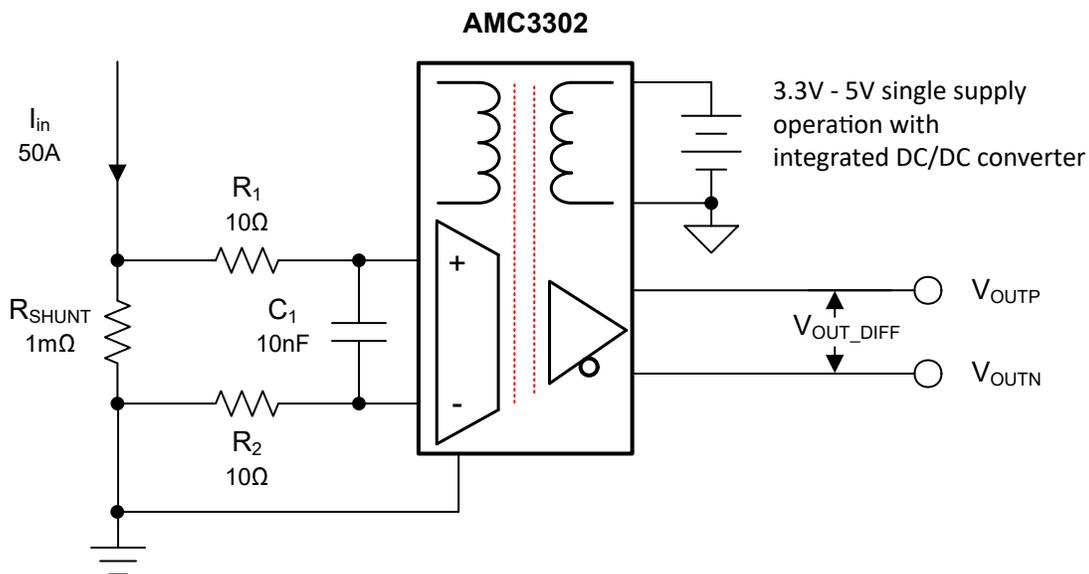
## Design Description

This isolated single-supply bidirectional current sensing circuit can accurately measure load currents from -50 A to 50 A. The linear range of the input is from -50 mV to 50 mV with a differential output swing of -2.05 V to 2.05 V and an output common-mode voltage ( $V_{CM}$ ) of 1.44 V. The gain of the isolated amplifier circuit is fixed at 41 V/V. The design requires 1200-V working voltage to ensure operator safety in a high-voltage application.



## Design Notes

1. The AMC3302 was selected due to its high accuracy, small input voltage range and the single, low-side power supply requirement of the application.
2. Select a low impedance, low-noise source for VDD which supplies the AMC3302.
3. For highest accuracy measurements, select a precision shunt resistor with a low temperature coefficient.
4. Select the current shunt resistor based on expected peak input current levels.
5. For continuous operation, do not run shunt resistors at more than two-thirds of the rated current under normal conditions as per IEEE standards. Further reducing the shunt resistance or increasing the rated wattage may be necessary for applications with stringent power dissipation requirements.

## Design Steps

1. Determine the transfer equation given the input current range and the fixed gain of the isolation amplifier.

$$V_{OUT} = I_{in} \times R_{shunt} \times 41$$

2. Determine the maximum shunt resistor value.


$$R_{shunt} = \frac{V_{inMax}}{I_{inMax}} = \frac{50 \text{ mV}}{50 \text{ A}} = 1 \text{ m}\Omega$$

3. Determine the minimum shunt resistor power dissipation.

$$\text{Power } R_{shunt} = I_{inMax}^2 \times R_{shunt} = 2500 \text{ A}^2 \times 0.001 \Omega = 2.5 \text{ W}$$

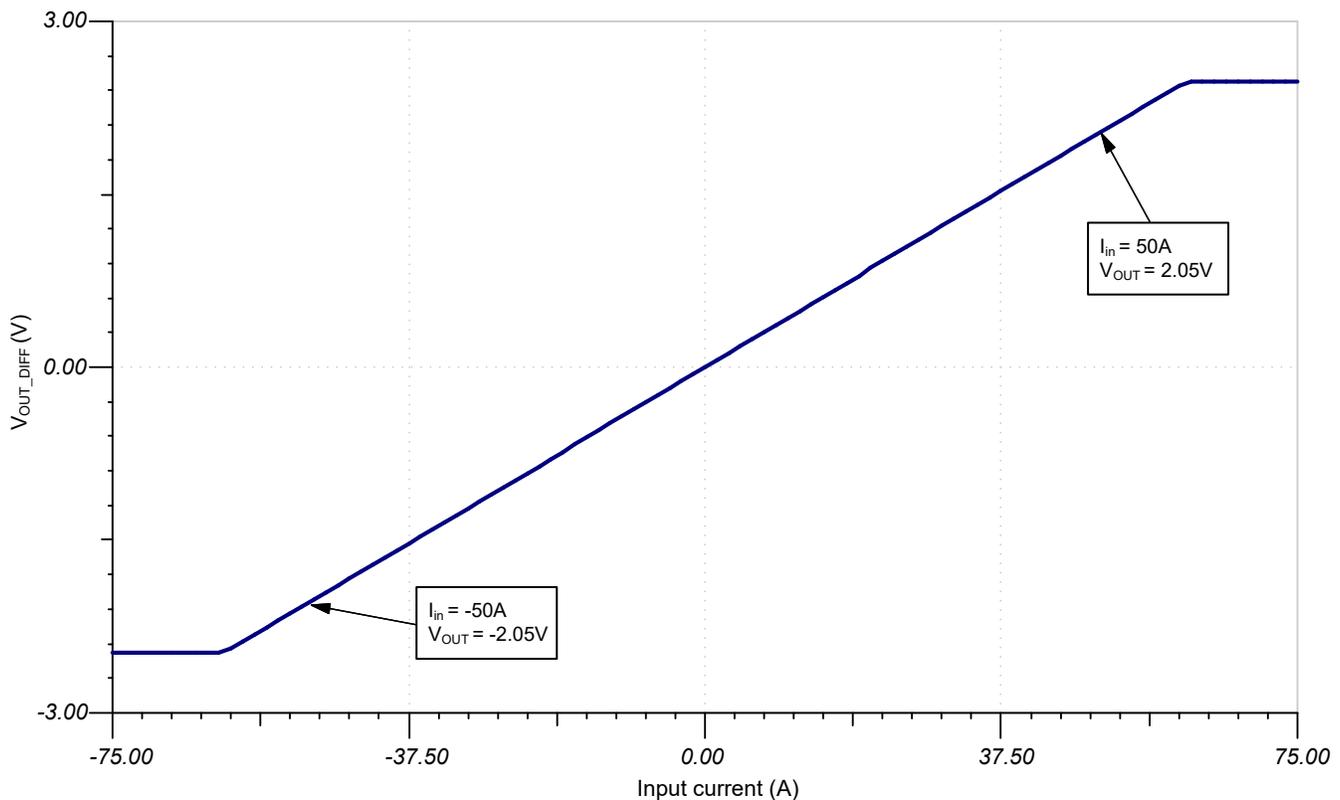
## DC Transfer Characteristics

The following plots show the simulated DC characteristics of the AMC3302 differential output. The plot shows that the output is linear with a  $\pm 50 \text{ A}$  input.



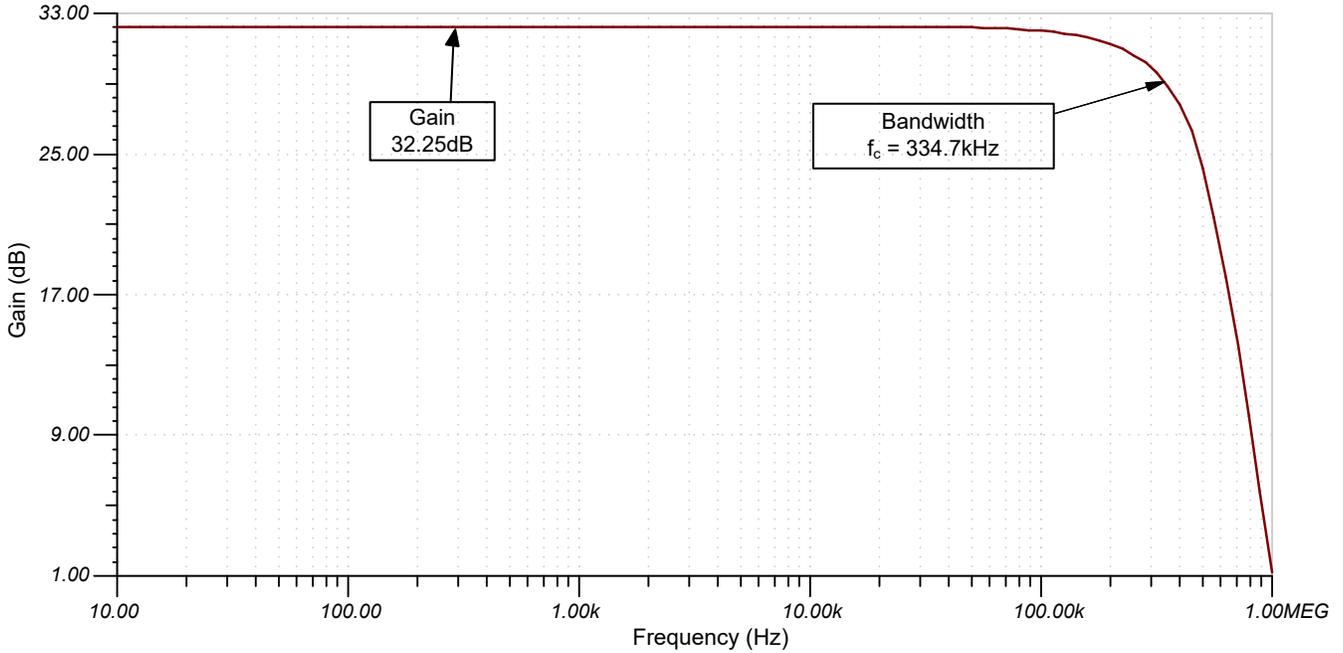
### Closed Loop AC Simulation Results

The AC sweep shows the AC transfer characteristics of the differential output. Since the AMC3302 has a gain of 41 V/V, the gain of 33.25-dB shown in the following image is expected.


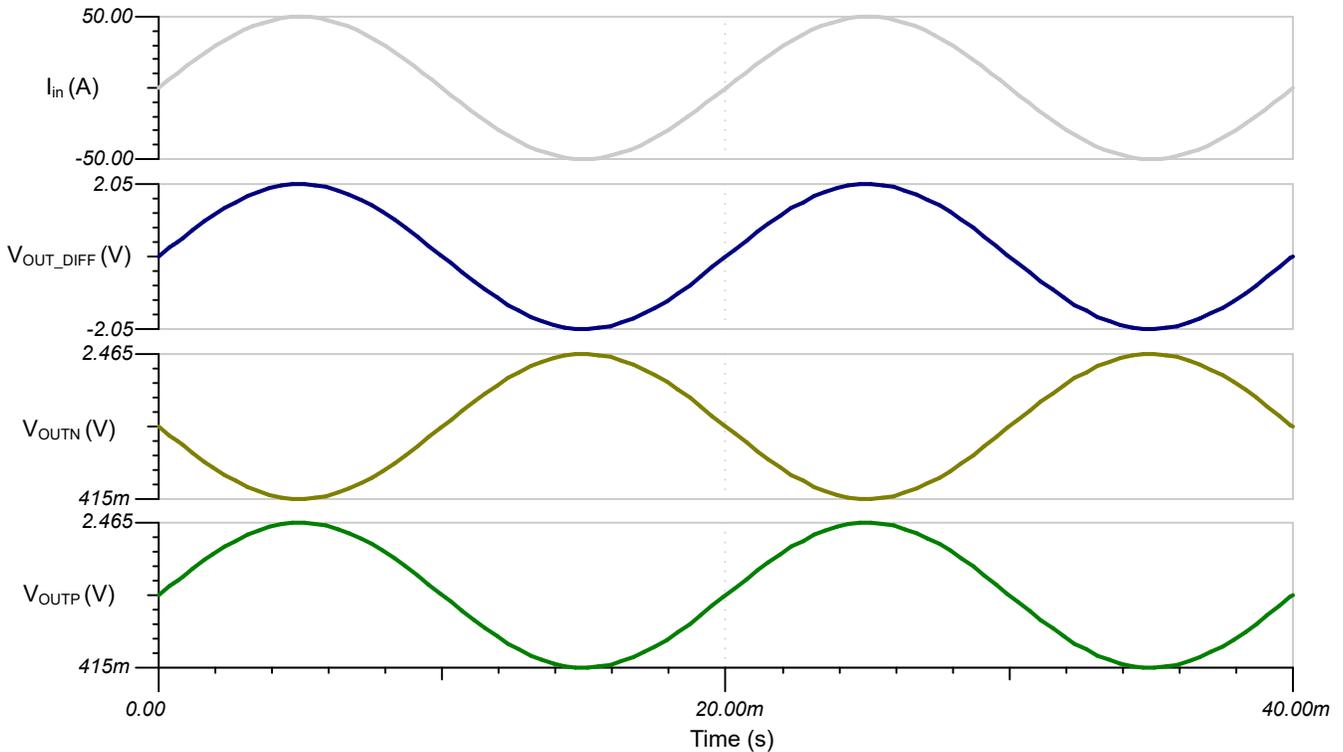
### Transient Simulation Results

The following transient simulation shows the output signals of the AMC3302 from  $-50\text{ A}$  to  $50\text{ A}$ . The differential output of the AMC3302 is  $\pm 2.05\text{ Vpk-pk}$  as expected.



## Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

## Design Featured Isolation Amplifier

AMC3302	
Working voltage	1200 V <sub>RMS</sub>
Gain	41 V/V
Bandwidth	340 kHz TYP
Linear input voltage range	±50 mV
<a href="#">AMC3302</a>	

## Design Alternate Isolation Amplifier

AMC3301	
Working voltage	1200 V <sub>RMS</sub>
Gain	8.2 V/V
Bandwidth	334 kHz TYP
Linear input voltage range	±250 mV
<a href="#">AMC3301</a>	

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated