

Isolated Zero-Cross Detection Circuit



Data Converters


Scott Cummins

Design Goals

High Side Supply	Input Voltage	Working Voltage	Low Side Supply	Output Voltage
12 V	$\pm 170 V_{pk}$ Sine Wave	$\geq 400 V_{RMS}$	3.3 V to 5.0 V $\pm 10\%$	\leq Low-Side Supply

Design Description

A zero-crossing detector circuit changes output state when the AC input crosses the zero-cross reference voltage. This design features a single chip solution for zero-crossing detection of an AC sine wave with inverting and non-inverting digital outputs. The circuit is created by setting the comparator inverting input to ground and applying a clamped sine wave to the noninverting input. The input voltage is clamped by R1 and a pair of antiparallel diodes. In this case, diodes are used instead of an attenuator to maximize the slew rate of the input near the zero-crossing, which reduces output latency. The circuit is used for AC line zero-cross detection in control circuits to reduce standby and off-mode power consumption.

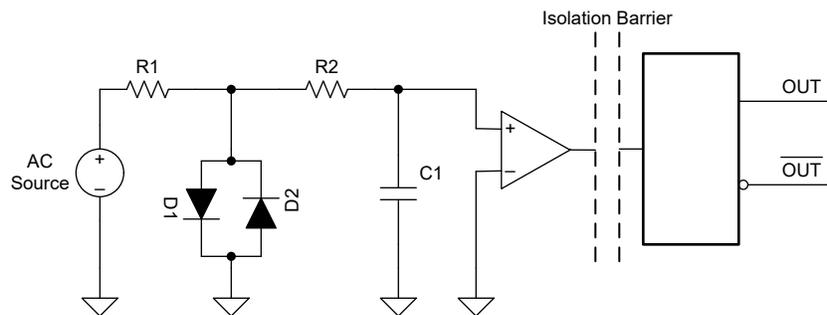

Isolated Zero-Cross Detection Circuit Schematic

Design Notes

1. The circuit must be capable of handling 750-V working voltage across the isolation barrier.
2. The maximum input voltage at IN+ must be $\pm 1 V$
3. Inverting and non-inverting output are desired
4. Maximum current flowing through R1 is $100 \mu A \pm 10\%$
5. Limit the operating voltage of each resistor in the string to $100 V \pm 10\%$ maximum
6. The input AC source voltage is $120 V_{RMS}$, higher AC voltages are easily accommodated with component modifications. See the [Alternate Design](#) section for details
7. Ensure the hysteresis voltage at the AC zero-cross is no more than $\pm 30 mV$

Design Steps

1. Determine the ideal R1 resistor value. The maximum peak input voltage of $120 V_{RMS} \times \sqrt{2} = 170 V_{PK}$. Note that the forward voltage of the diode D1 is near zero, and not included in this calculation.

$$R1 = \frac{170 V_{PK}}{100 \mu A} = 1.70 M\Omega$$

2. Divide R1 into 3 equal resistors to maintain design limits of $\leq 100 V$ per resistor:


$$R1 = \frac{1.70 M\Omega}{3} = 566.66 k\Omega$$

3. Use the [Analog Engineer's Calculator](#) to find a standard E96 1% resistor value for R1. The nearest value is 569 k Ω .
4. Select the anti-parallel diodes. Choose diodes which will provide at least ± 350 -mV forward voltage with the 100 μA supplied through R1.
5. Optional – design low-pass filter at VINP defined by R2 and C1. The frequency response is defined as:

$$F_C = \frac{1}{2\pi \times R2 \times C1}$$

Revised Design

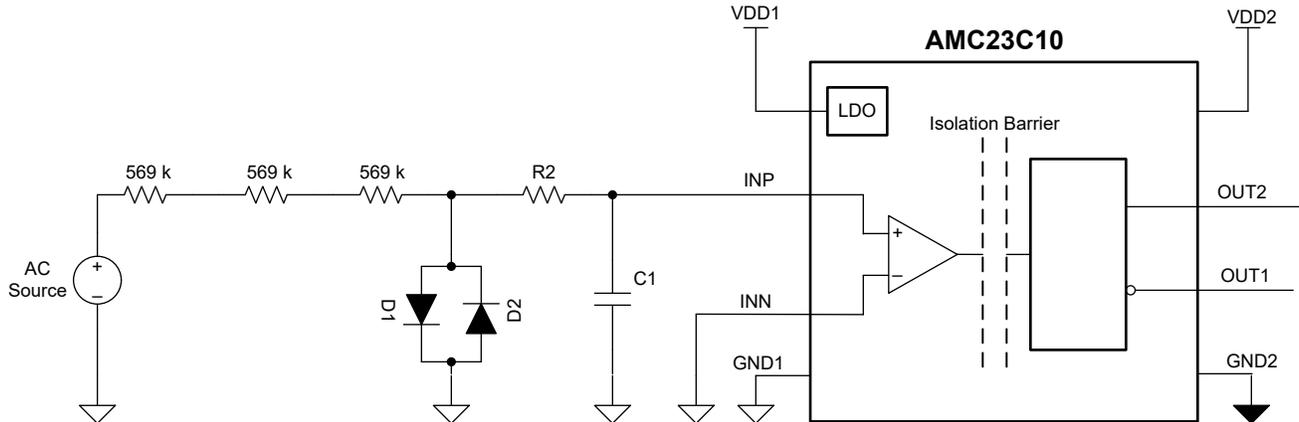
The following schematic shows implementation of the revised design using the AMC23C10.




Revised Design With AMC23C10 Isolated Comparator

The AMC23C10 uses capacitive isolation to provide a working voltage of 1000 V. The voltage source for VDD1 is specified from 3 V to 27 V, controlled internally through an LDO. VDD2 is specified from 2.7 V to 5.5 V. The input voltage range under normal operation is $\pm 1 V$. The logic output on OUT1 is open drain which can be used with a pullup resistor to VDD1. OUT2 is a push-pull type output needing no external pullup resistors.


Design Simulations

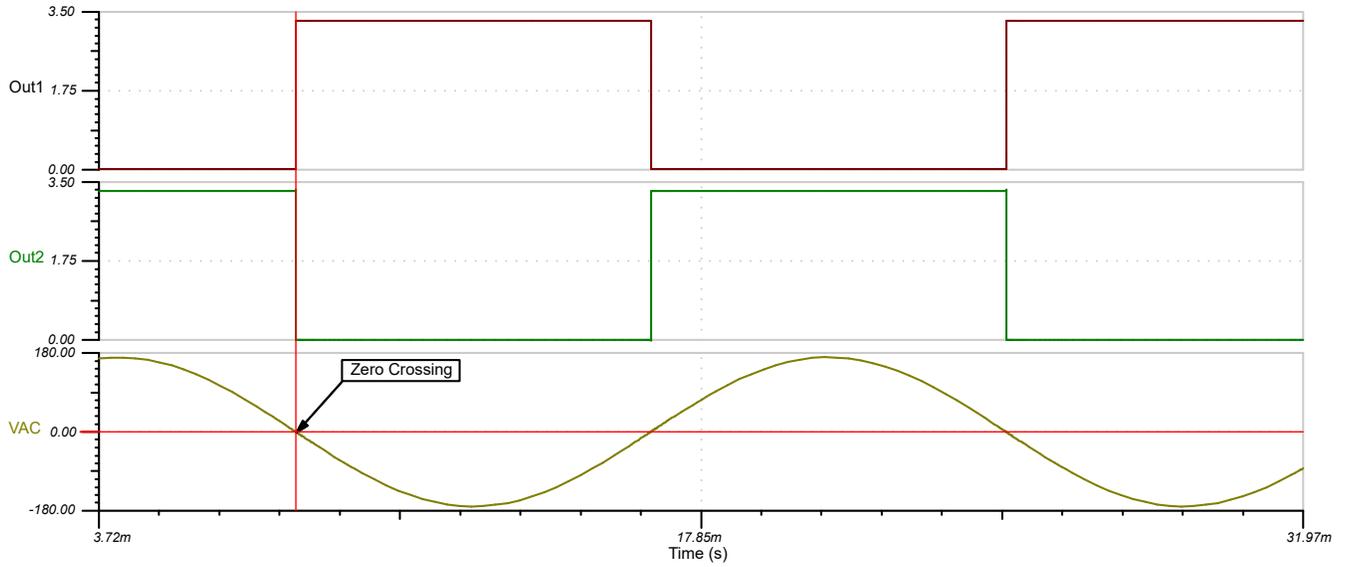

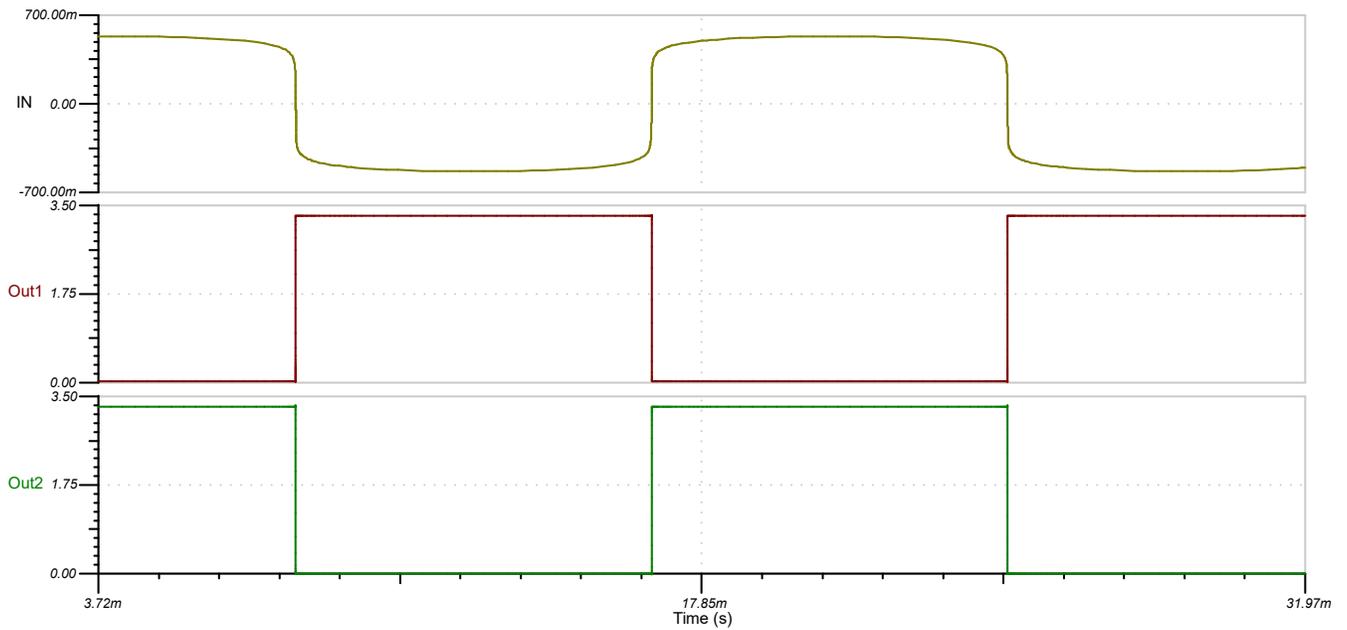Simulation of Zero-Crossing Detection With Sine Wave Input



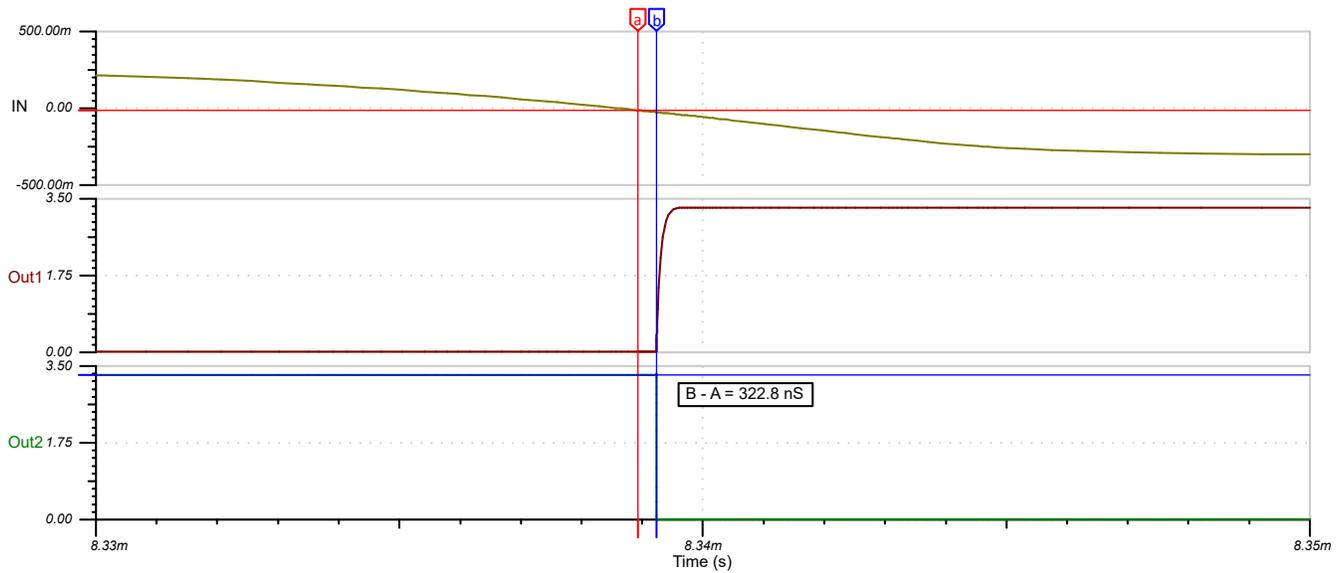
Simulation of Zero-Crossing Detection With Rectified Input




Simulation of Response Time for Zero-Crossing Detection

Measured Response

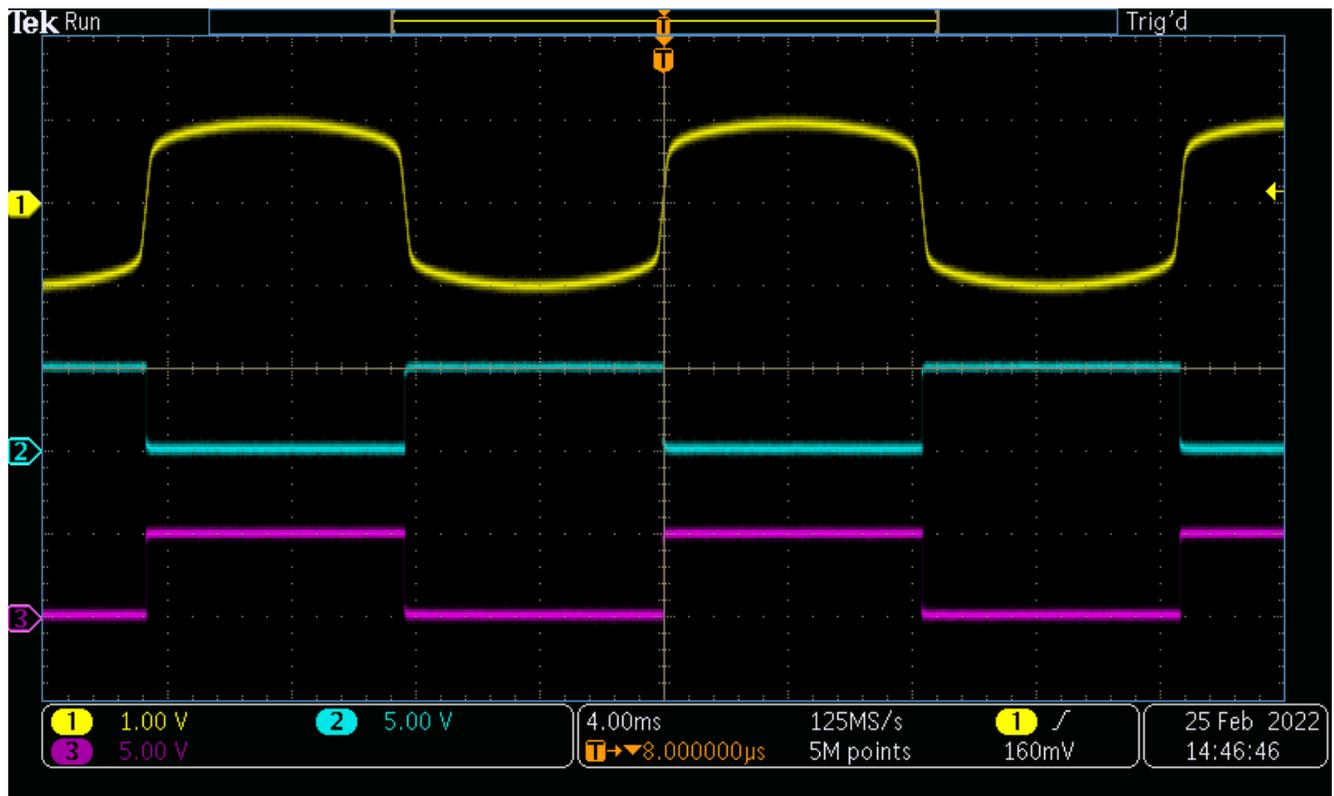
The following images show the measured response of the zero-crossing detection circuit using the AMC23C10 isolated comparator. The input is captured on trace 1, while OUT1 and OUT2 are shown on traces 2 and 3 respectively. When measured at both the rising and falling edges of the input, the delay between the zero-crossing of the input and the output transition does not exceed 220 ns.



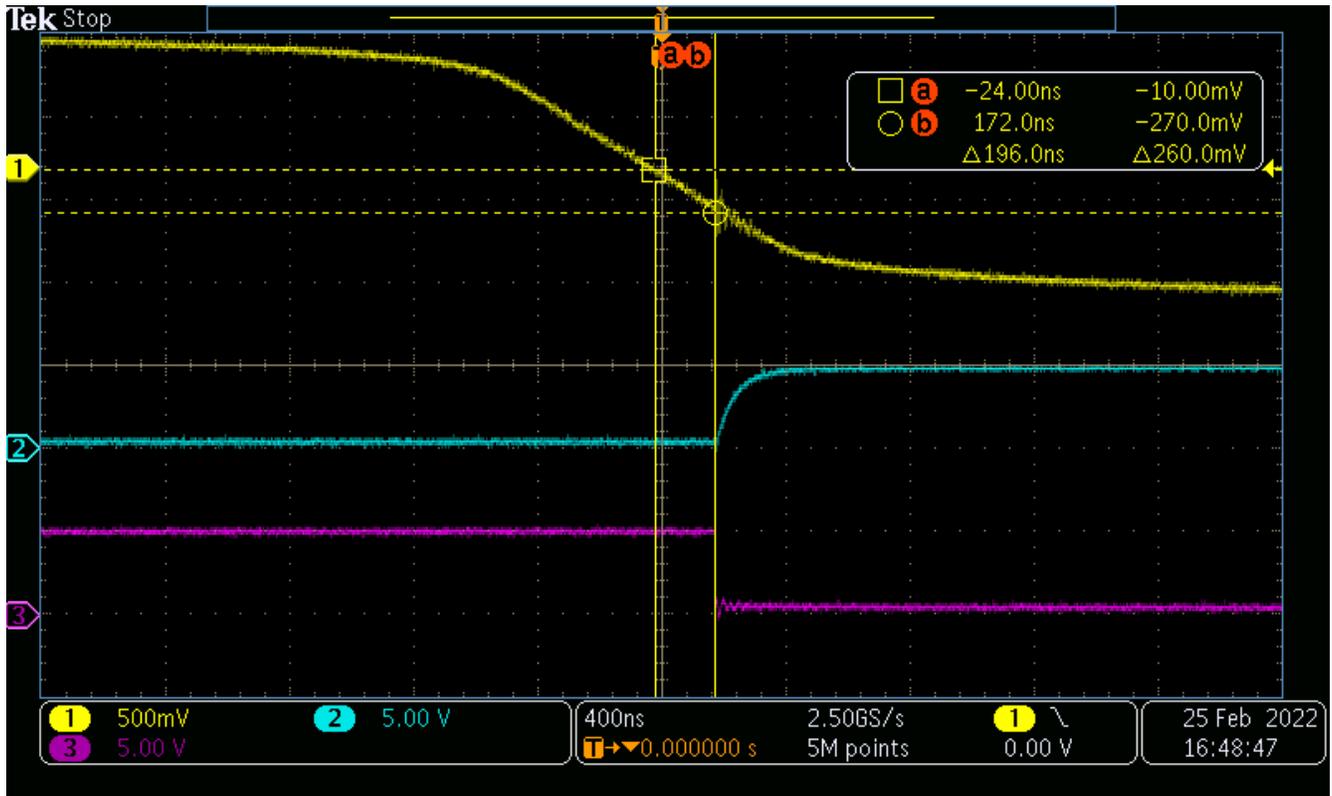Zero-Crossing Detection of Rectified Input



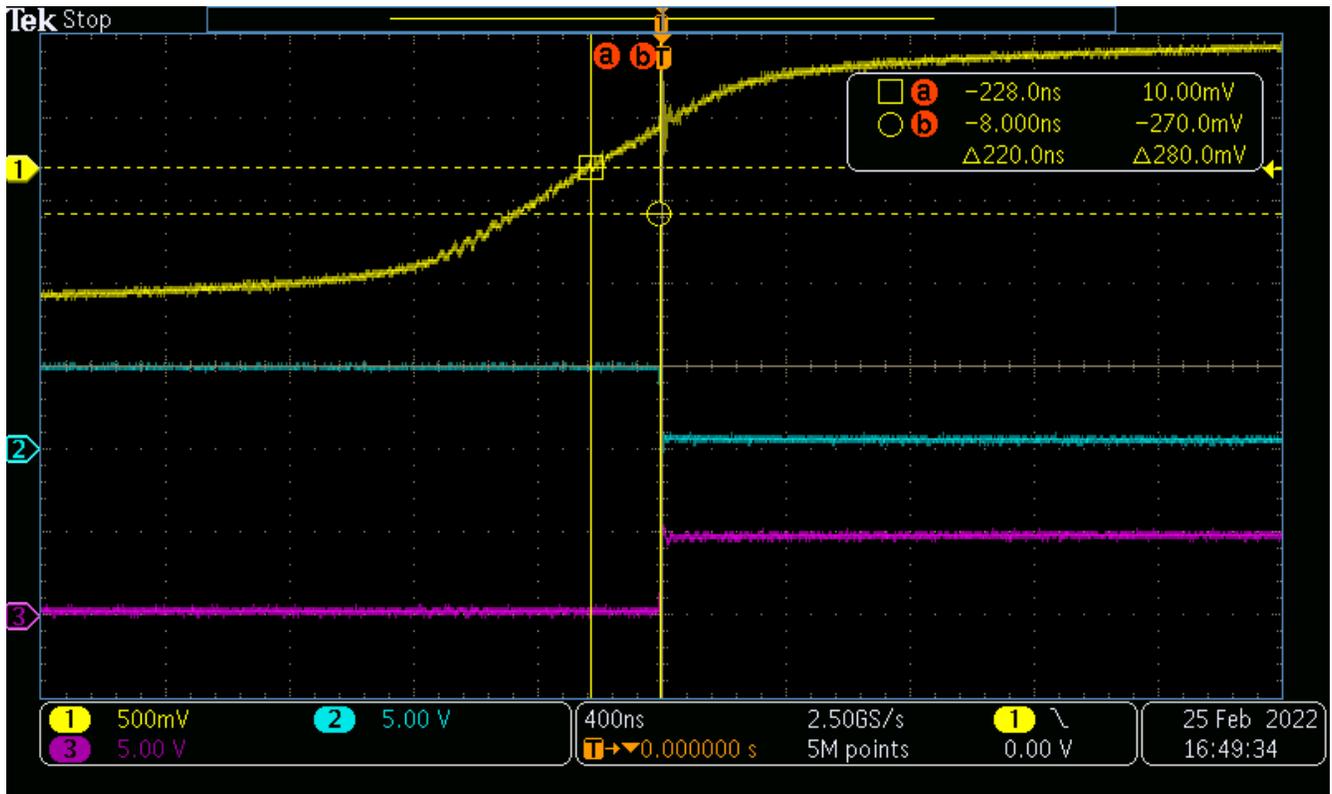Zero-Crossing Detection Output Latency – Falling Edge



Zero-Crossing Detection Output Latency – Rising Edge

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

Texas Instruments, [AMC23C10 Fast Response, Reinforced Isolated Comparator With Dual Output](#) data sheet

Design Featured Isolated Comparator

AMC23C10	
Working Voltage	1000 V _{RMS}
VDD1	3.0 V–27 V
VDD2	2.7 V–5.5 V
Input Voltage Range	±1000 mV
Output Options	OUT1 - Open Drain
	OUT2 - Push-Pull
AMC23C10	

Alternate Design for 230-VAC Input

AMC23C10	
Working Voltage	1000 V _{RMS}
AC Input	325 V _{pk}
R1 Ideal	3.25 MΩ
R1 E96 Standard	Three each 1.09 MΩ

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated