

High-Voltage Signal Conditioning for Low-Voltage ADCs

Pete Wilson, P.E.
High-Performance Linear Products/Analog Field Applications

ABSTRACT

Analog designers are frequently required to develop circuits that convert high-voltage signals to levels acceptable for low-voltage data converters. This paper describes several solutions for this common task using modern amplifiers and typical power supplies. Five examples of conditioning $\pm 10\text{V}$ bipolar signals for low-voltage, single-rail analog-to-digital converters (ADCs) are presented: a modular approach, a single-supply/single-part approach, and an instrumentation amplifier approach. Both single-ended, differential input versions are discussed.

Contents

1	Introduction	2
2	Circuit 1: The Modular Approach	2
3	Circuit 2: Single-Supply/Single-Port Approach.....	4
4	Circuit 3: Difference Amp Approach.....	5
5	Circuit 4: Differential Input with INA146.....	7
6	Circuit 5: Differential Input Modular	8
7	Voltage References and Ranges	8
8	References	9

List of Figures

1	Circuit 1: Modular Design.....	2
2	DC Sweep of Circuit 1	3
3	Circuit 2: Single-Supply/Single-Part	4
4	DC Sweep of Circuit 2	5
5	Circuit 3: INA146.....	5
6	DC Sweep of Circuit 3	6
7	Circuit 4 (Circuit 3 with Differential Input).....	7
8	Circuit 5 (Circuit 1 with Differential Input).....	8

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

Analog front-end designers are often confronted with the challenge of coupling high-voltage bipolar signals to ADCs that operate on low-voltage single supplies. Traditional single-part, high-voltage converters are becoming obsolete, although many applications continue to use high-voltage bipolar analog signals. Modern data converters are designed on small geometry processes because of advanced digital capabilities, higher yields, and overall lower costs. Op amps, on the other hand, are designed on large geometry processes to withstand higher internal voltages and allow precise control of internal elements. Modern op amps offer several outstanding features, such as rail-to-rail I/O, a wide input common-mode voltage range, linear transfer functions, low power consumption and low-voltage operation. By using discrete op amps and data converters, designers can optimize circuit performance by using the proper part and avoiding expensive, compromised, single-part solutions.

2 Circuit 1: The Modular Approach

The circuit shown in Figure 1 is a classic modular approach to circuit design. The first stage is attenuation. The second stage is level-shifting. This style is convenient because designers can compartmentalize adjustments. Input range can be adjusted by changing R1. Level-shift can be changed by adjusting REF1V50. These parameters are independent and can be tuned with minimal interactions. Furthermore, designers may want to include anti-alias filtering or other analog functions. These blocks can be neatly inserted at node N₂.

 


Figure 1. Circuit 1: Modular Design

On the front-end voltage divider, the equation for R1 is:

$$\frac{R1}{R2} = \frac{V_{OUT}}{(V_{IN} - V_{OUT})} \quad (1)$$

In Circuit 1, the following values are used:

- $V_{OUT} = 3V$
- $V_{IN} = 20(\pm 10)V = V_1$
- $R1 = 1.76k$ (1.78k is closest standard value)
- $R2 = 10k$
- REF1V50 = midpoint of ADC full-scale input range.

These component values can be altered to account for different input ranges or input impedance requirements. In this example, the value of R2 is held constant to simplify calculations and reduce trimming to one element.

The first stage op amp is an OPA277. The OPA277 was chosen for its low V_{IO} , low drift, and bipolar swing. This stage needs to have bipolar swing about ground because the input signal is bipolar. The OPA277 is also a great candidate for active-filter stages. TI's free FilterPro design tool (available for download at www.ti.com) can be used to design and model active filters. FilterPro presumes that the amplifiers under consideration are operating in a bipolar mode, making node N1 the appropriate place for filters. Another option for the first stage is the OPA725, which is suitable for bipolar stages with $\pm 5V$ rails.

The second stage op amp is the OPA364. This outstanding, low-voltage op amp offers many assets which are ideal at this stage: it is low-voltage and low-power, in addition to having a large input common-mode voltage range. It also has zero crossover distortion for linear, monotonic, large-signal output.

Resistor networks are used to bias the OPA364 and the reference because they are matched. This ratiometric design takes advantage of this property. Gain errors from mismatched components cannot be distinguished from genuine signals. For example, the gain error from discrete 1% components is equivalent to $-40dB$ of erroneous signal. This is inadequate for 12-bit, or higher, conversions, where the minimum detectable signal is below $-70dB$. Resistor networks with ratio 0.01% tolerances ($-80dB$) are readily available. High-quality metal foil networks with 0.005% tolerances ($-106dB$) may be necessary for extreme cases.

The DC sweep plot of Circuit 1 is shown in [Figure 2](#). Node N3 shows the input common-mode voltage swing of the second stage.

 


Figure 2. DC Sweep of Circuit 1

Designers may want to consider the INA132 or the INA152 for the second stage. These amps are considerably slower than the OPA364, but they come with precision-matched internal resistors to reduce gain errors. In general, DC precision is desirable for open-loop applications such as temperature sensors or calibrated transducers, where absolute accuracy, offset and drift are critical. This precision makes the INA132 a good choice for absolute measurements. In closed-loop applications such as servos loops or PID controllers, high-speed and monotonicity are desirable. In closed-loop systems, DC offsets and gain errors will be canceled by feedback and calibration. This makes the OPA364, or the OPA301, a good choice for servos and feedback signals.

3 Circuit 2: Single-Supply/Single-Port Approach

Figure 3 shows a circuit that is attractive to designers who are limited to a single low-voltage supply. The proper selection of biasing components enables both the attenuation and level-shifting functions to be accomplished in one stage.

 


Figure 3. Circuit 2: Single-Supply/Single-Port

The following series of formulas defines the relationship of the bias components:

$$R1 = R3 \quad (2)$$

$$R2 = R4 \quad (3)$$

$$\frac{R1}{R2} = \frac{V_{IN}}{V_{OUT}} \quad (4)$$

Circuit 2 uses the following values:

- $V_{OUT} = 3V$
- $V_{IN} = 20(\pm 10)V = V1$
- $R1 = R3 = 20.0k$ 1%
- $R2 = R4 = 3.01k$ 1%
- REF1V50 = midpoint of ADC full-scale input range.

This architecture is much more compact than the modular solution of Circuit 1; however, it does rely on tight component tolerances, and does not offer either simple adjustment or filter insertion options. The DC sweep plot of Circuit 2 is shown in Figure 4. Note the large common-mode voltage swing at node N1 and the rail-to-rail output range. These two requirements make the OPA364 the best choice. Also, note the output clamping action of the OPA364, which ensures that the ADC output is not overdriven. This design can be used with input voltages far outside the power-supply rails, though designers need to pay attention to the power dissipated in R3 and the input common-mode voltage limitations of the operational amplifier.

 


Figure 4. DC Sweep of Circuit 2

4 Circuit 3: Difference Amp Approach

Figure 5 shows a circuit designed with the INA146. This part has built-in biasing components for attenuation and a user-programmable gain stage. Additionally, the difference amp offers excellent common-mode rejection.

 


Figure 5. Circuit 3: INA146

The following equations relate the bias components:

$$\frac{V_{OUT}}{V_{IN}} = \left(\frac{10k}{100k} \right) \times \left(1 + \frac{RF}{RG} \right) \quad (5)$$

$$RF = RG \left(\frac{100k}{10k} \times \frac{V_{OUT}}{V_{IN}} - 1 \right) \quad (6)$$

$$RF = 10k \left(\frac{100k}{10k} \times \frac{5}{20} - 1 \right) = 15k \quad (7)$$

With $RG = 10k$.

Figure 6 shows the DC sweep of Circuit 3.

 


Figure 6. DC Sweep of Circuit 3

5 Circuit 4: Differential Input with INA146

Some systems have differential inputs. This is a popular technique to reduce common-mode noise. Audio engineers have used low-level, differential signals in harsh on-stage environments for decades. The INA146 is designed for these types of applications. Figure 7 shows Circuit 3 adapted for differential input. However, changing Circuit 3 from single-ended to differential is straightforward. Note the polarity reversal of the inputs.

 


Figure 7. Circuit 4 (Circuit 3 with Differential Input)

6 Circuit 5: Differential Input Modular

Circuit 1 can also be adapted for differential input. The changes require more effort, though; additionally, the attenuation stages are inverting, and the overall circuit looks more like a classic differential audio input. Note the use of matched components in this circuit. [Figure 8](#) shows Circuit 5.

 


Figure 8. Circuit 5 (Circuit 1 with Differential Input)

7 Voltage References and Ranges

The references shown in these examples are simple. They are for ratiometric applications where the ADC range is the rail. The references shown are $V_{CC}/2$, or at the mid-scale of the ADC range. This proportion is required for these circuits. 3.3V or 5V can be used in any of these designs; the references would be 1.65V or 2.5V, respectively. These designs will work with absolute references as well, as long as the V_{REF} is one-half of the ADC full-scale range.

The other requirement is a good buffer driving the reference signal. These designs put a wide range of loads on the reference, and a buffer is essential. For in-depth information on buffering references for precision and high-resolution designs, see Application Note *Voltage Reference Filters* ([SBVA002](#)).

8 References

1. Bishop, J., B. Trump, and R.M. Stitt. *MFB Low-Pass Filter Design Program*. Application note. (SBFA001)
2. Stitt, R.M. *Voltage Reference Filters*. Application note. (SBVA002)
3. Wilson, P. *High-Voltage Signal Conditioning*. Application note. (SBOA096)
4. *FilterPro™ MFB and Sallen-Key Design Program*. Executable program. (SLVC003.zip)

To obtain a copy of the referenced documents, visit the Texas Instruments web site at www.ti.com.

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from A Revision (June 2004) to B Revision	Page
• Changed format to current TI application report template.	1

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated