

Low Power Input and Reference Driver Circuit for ADS8318 and ADS8319

Hemant Ashok Deshmukh

Data Acquisition Products

ABSTRACT

The *one size fits all* approach to operational amplifiers (op amps) is not effective. Every application has its own specific requirements that must be fulfilled. Appropriate selection of the op amp that drives an analog-to-digital converter (ADC) in a low-power application is a critical step. Most available low-power op amps trade off low-power features with other parameters such as bandwidth, settling time, slew rate, or amplifier noise, and typically, these trade-off areas play a crucial role in data conversion applications. This report specifically addresses the matching of the [THS4281](#) (a very low power, high-speed op amp) with the [ADS8318](#) and the [ADS8319](#), two 16-bit, 500-kSPS, low-power, serial, successive approximation register (SAR) ADCs.

The discussion starts with a short introduction to the ADS8318, ADS8319, and THS4281, followed by the driver circuits for the ADS8318 (for both differential and single-ended input configurations) and the ADS8319. Then, circuit performance is demonstrated through test results and several recommendations are presented regarding op amp selection for both the ADS8318 and ADS8319.

Contents

1	Introduction	2
2	ADS8318 Driver Circuits	4
3	ADS8319 Driver Circuit	7
4	Performance Results	7
5	Step-Input Settling	12
6	Quick Op Amp Selection Guide	13

List of Figures

1	Open-Loop Gain vs Frequency (Generic Op Amp Response)	2
2	Reduced Feedback Factor Reduces Peaking	3
3	Noise Reduction Effect	3
4	ADS8318: Driver Configuration for Unipolar Differential Input	4
5	ADS8318: Driver Configuration for Unipolar Single-Ended Input	5
6	ADS8319: Driver Configuration	7
7	Power Spectrum Comparison	8
8	ADS8318: Typical Linearity Graphs (Differential Configuration)	9
9	ADS8318: Typical Linearity Graphs (Single-Ended Configuration)	9
10	ADS8319: Typical Linearity Graphs	10
11	Step-Input Response for Circuit Shown in Figure 6	12
12	THS4281 Operating Region and Power Dissipation Comparison	13

1 Introduction

The ADS8318 and ADS8319 are two 16-bit, 500-kSPS SAR ADCs available from Texas Instruments. The ADS8318 receives a unipolar differential input while the ADS8319 receives a unipolar single-ended input. Both devices are optimized for very low power operation (typically, 18 mW at a speed of 500 kSPS and 5-V supply voltage), and overall power consumption directly scales with speed. This feature makes it attractive for a wide range of low-power applications.

The low-power feature of the ADS8318 and ADS8319 becomes even more attractive if the ADC is matched with low-power op amps for driving its inputs and reference. The THS4281 meets these demands by offering a very low quiescent current (less than 1 mA) across supply voltage and temperature. It also has a high bandwidth (40 MHz, specified at gain of 2) and settles quickly.

Figure 1 illustrates the open-loop gain versus frequency response of a generic op amp. This response shows a dominant pole frequency (f_{P1}), a crossover frequency (f_x) and a higher-order pole (f_{P2}). The crossover frequency, f_x , is the point at which $a\beta = 1$; a is the open-loop gain of the op amp and β is the feedback factor.

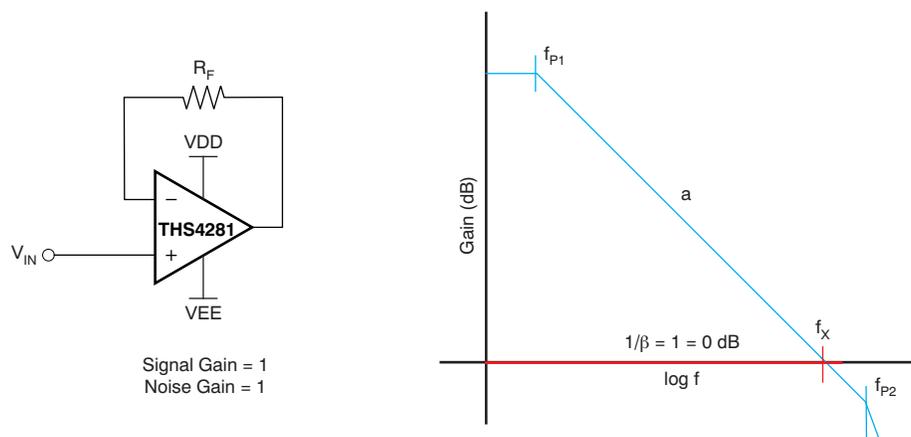


Figure 1. Open-Loop Gain vs Frequency (Generic Op Amp Response)

When f_x and any higher-order poles (f_{P2} , f_{P3} ... etc.) are far from each other (say, $f_{P2} > 10f_x$), then the closed-loop unity gain frequency response of the op amp is flat. But, when f_x and f_{P2} are very close, peaking is seen in the closed-loop unity gain response of the op amp because of the reduced phase margin, which may lead to oscillations. As expected, the THS4281 shows peaking in its closed-loop unity gain frequency response.

The closed-loop frequency response of the op amp can be improved by pushing the $a\beta = 1$ point (that is, the crossover frequency) towards the low frequency end, where phase margin is higher. This effect can be achieved by reducing β (or increasing $1/\beta$), as shown in Figure 2. However, reduction in β is usually achieved at a cost of increased noise gain ($1 + R_F/R_1$, in Figure 2). This trade-off causes signal-to-noise ratio (SNR) degradation of the ADC. Note that the circuit shown in Figure 2 maintains its unity gain configuration without loading the source or the op amp output.

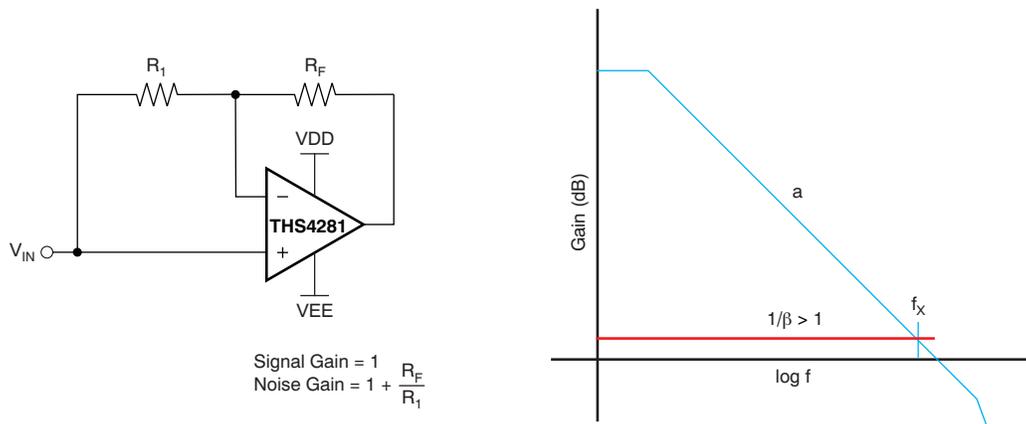


Figure 2. Reduced Feedback Factor Reduces Peaking

The feedback network can be made to be frequency-dependent. For example, at low frequencies where $1/f$ noise dominates and noise spectral density is high, the noise gain is maintained as unity. At a crossover frequency f_x (where $a\beta = 1$), $1/\beta$ is maintained sufficiently high to provide compensation for a peaked closed-loop response (as Figure 3 illustrates). For the THS4281, $\beta = R_1/(R_1 + R_F)$ of -3 dB to -6 dB is found to be sufficient to flatten the unity-gain frequency response.

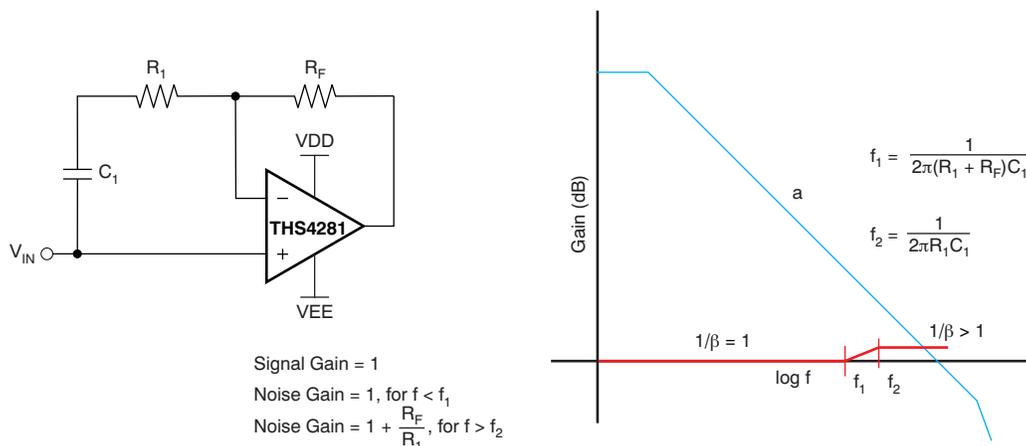


Figure 3. Noise Reduction Effect

2 ADS8318 Driver Circuits

Figure 4 and Figure 5 illustrate two driver circuits for the ADS8318, using the THS4281 as an input driver and reference buffer. Figure 4 illustrates the circuit configuration for a unipolar differential input, and Figure 5 shows the configuration for a unipolar single-ended input.

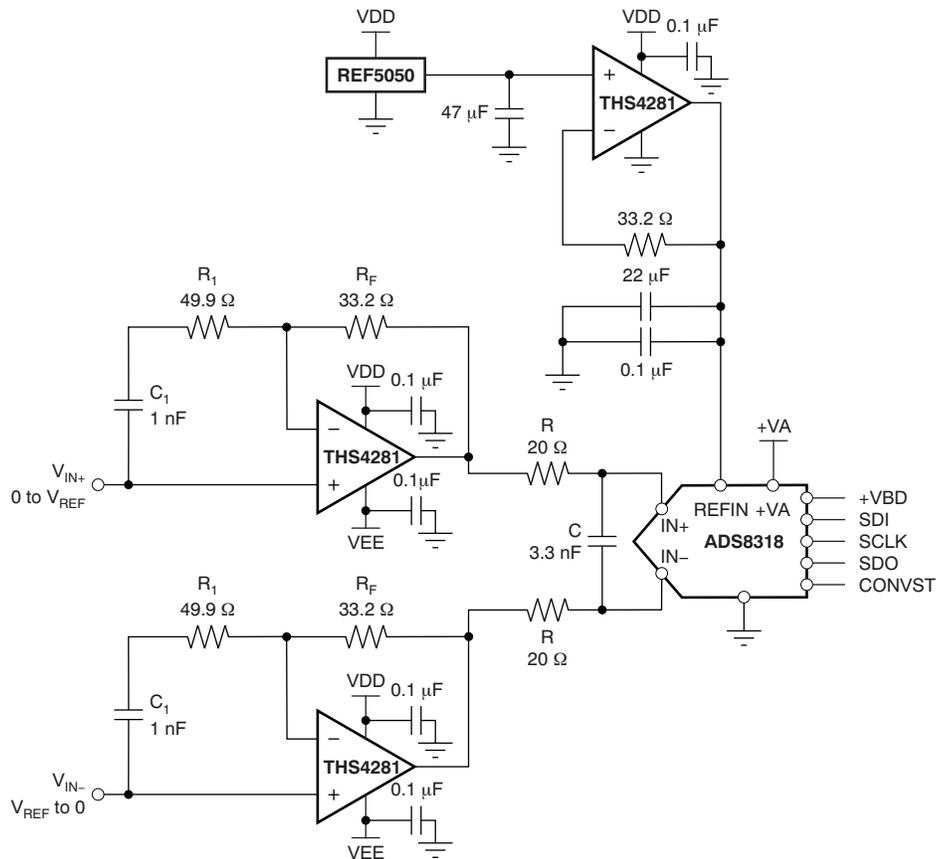


Figure 4. ADS8318: Driver Configuration for Unipolar Differential Input

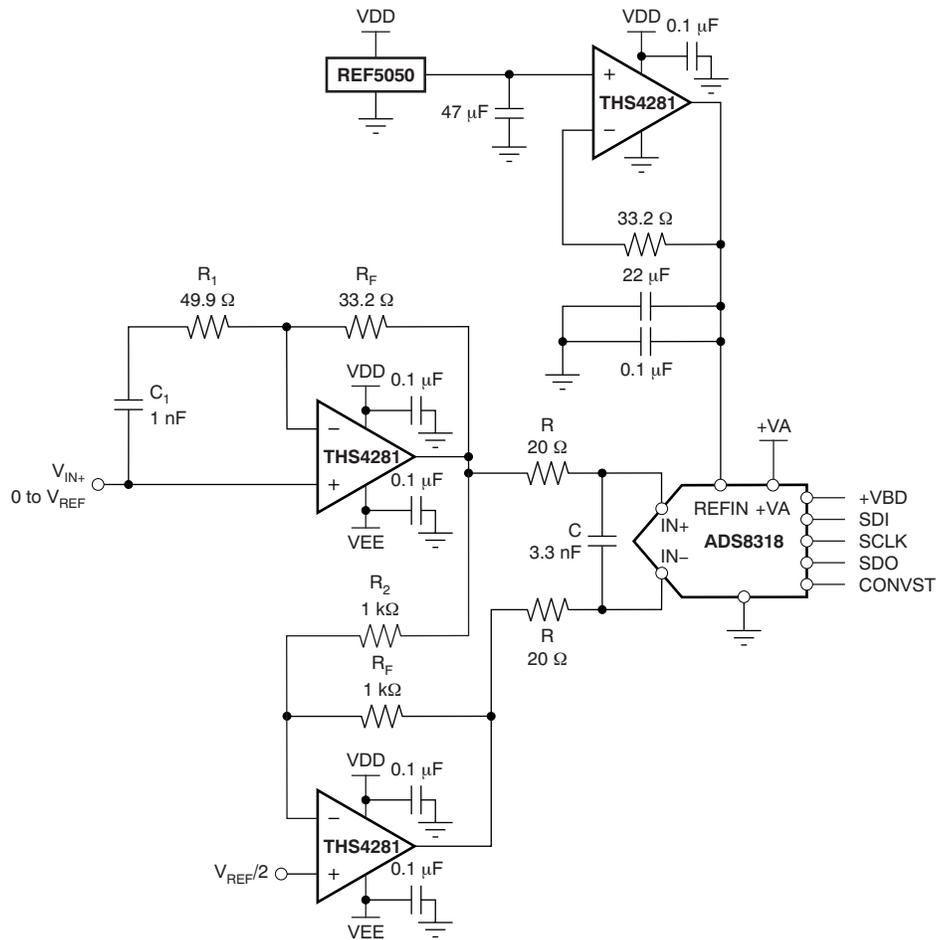


Figure 5. ADS8318: Driver Configuration for Unipolar Single-Ended Input

These circuits are configured with these design parameters:

- V_{REF} = Reference voltage applied to the ADC
- VDD = Positive analog power supply (VDD > 0)
- VEE = Negative power supply to the op amp (VEE < 0)
- VDD > $V_{REF} + 1.5$ V (to accommodate an input offset voltage shift with the common-mode input voltage for the THS4281)
- $(VDD - VEE) < 16.5$ V

None of the THS4281 input pins are left floating when it is powered.

From [Figure 4](#):

- $2RC$ time constant = $2 \times 20 \times 3.3 \text{ nF} = 132 \text{ ns}$
- Corresponding -3-dB frequency = 1.2 MHz
- THS4281 input voltage noise = $12.5 \text{ nV}/\sqrt{\text{Hz}}$
- Noise contribution from one THS4281 = $12.5 \text{ nV}/\sqrt{\text{Hz}} \times \sqrt{1.2 \text{ MHz}} = 13.7 \text{ }\mu\text{V}$
- $V_{\text{REF}} = 5.0 \text{ V}$
- RMS signal voltage = $5.0 \text{ V}/2\sqrt{2} = 1.767 \text{ V}$
- Quantization noise = $5.0 \text{ V}/(2^{16} \times \sqrt{12}) = 22.0 \text{ }\mu\text{V}$
- Total RMS noise (quantization noise and noise of two THS4281s):

$$\sqrt{13.7^2 + 13.7^2 + 22.0^2} = 29.13 \text{ }\mu\text{V}$$

- $\text{SNR} = 20\log(1.767 \text{ V} / 29.13 \text{ }\mu\text{V}) = 95.6 \text{ dB}$

The $2RC$ time constant applied in [Figure 4](#) is 132 ns . For a full-scale step input to settle to 18-bit accuracy at the ADC input, the $2RC$ time constant should be less than:

$$\frac{600 \text{ ns}}{[(N + 2) \times \ln 2]} = 48 \text{ ns}$$

where:

- 600 ns is the acquisition time
- $N = 16$ is the resolution of the ADC

Because the THS4281 is slightly noisy, a higher time constant is required to band-limit the noise within the acceptable specification range.

3 ADS8319 Driver Circuit

Figure 6 illustrates a driver circuit for the ADS8319, also using the THS4281 as an input driver and reference buffer.

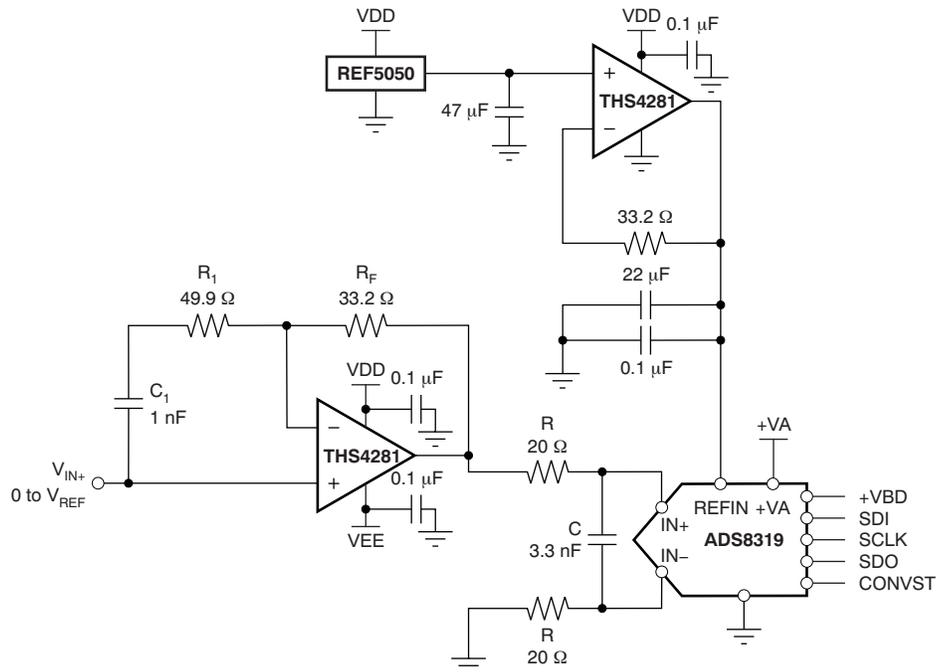


Figure 6. ADS8319: Driver Configuration

4 Performance Results

This section presents the performance results obtained on several devices for the driver configurations discussed earlier. The results are then compared with the benchmark results obtained for these circuits with the THS4031 as the driving op amp. The THS4031 is very high-performance op amp, but it has very high quiescent current.

Figure 7 illustrates a typical power spectrum for the circuits shown in Section 2 and Section 3. Figure 8, Figure 9, and Figure 10 show typical linearity plots for these same circuits. To compare these results with the graphs obtained using the THS4031 as the driving op amp, refer to the ADS8318 and ADS8319 product data sheets (available for download at www.ti.com).

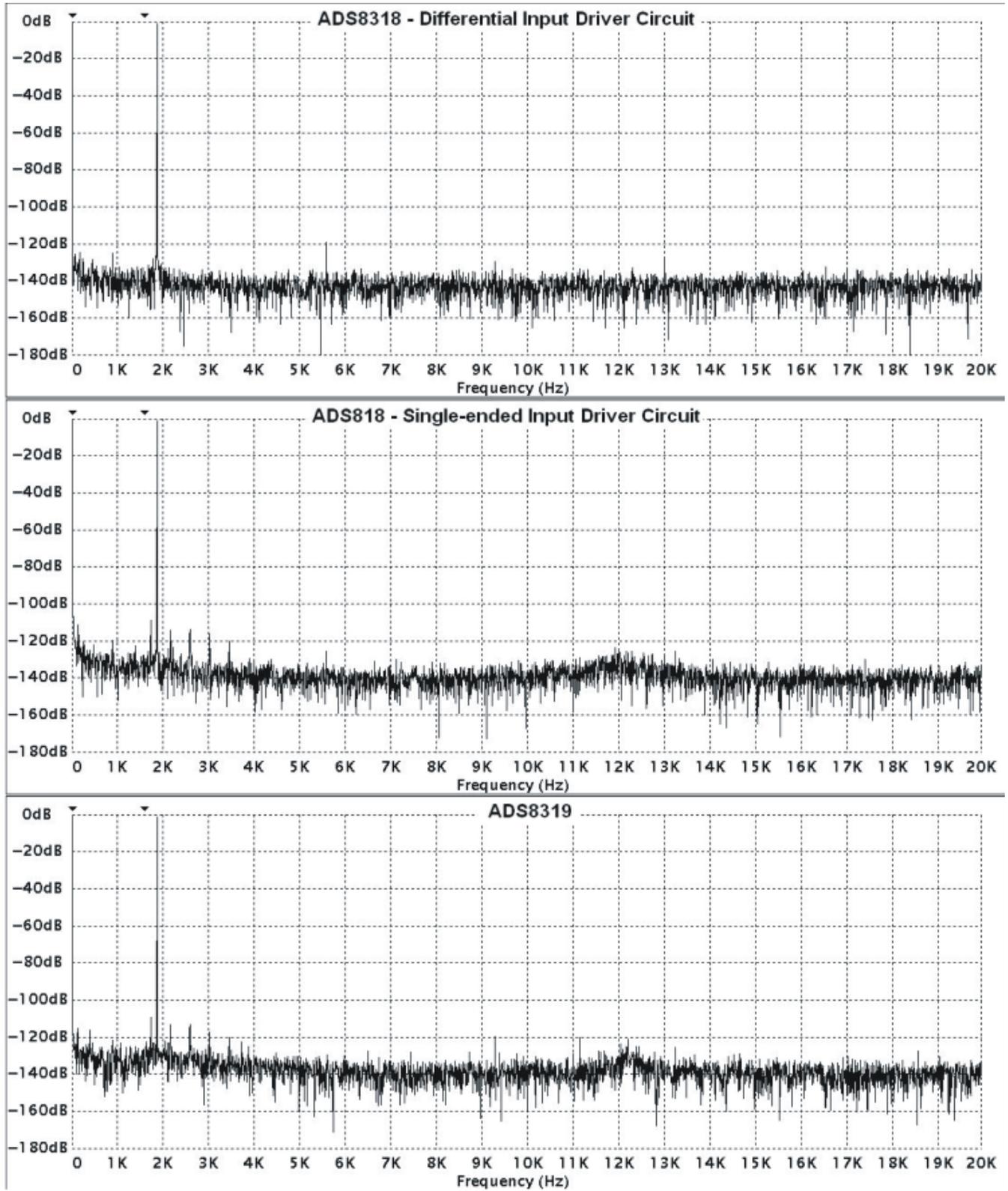


Figure 7. Power Spectrum Comparison

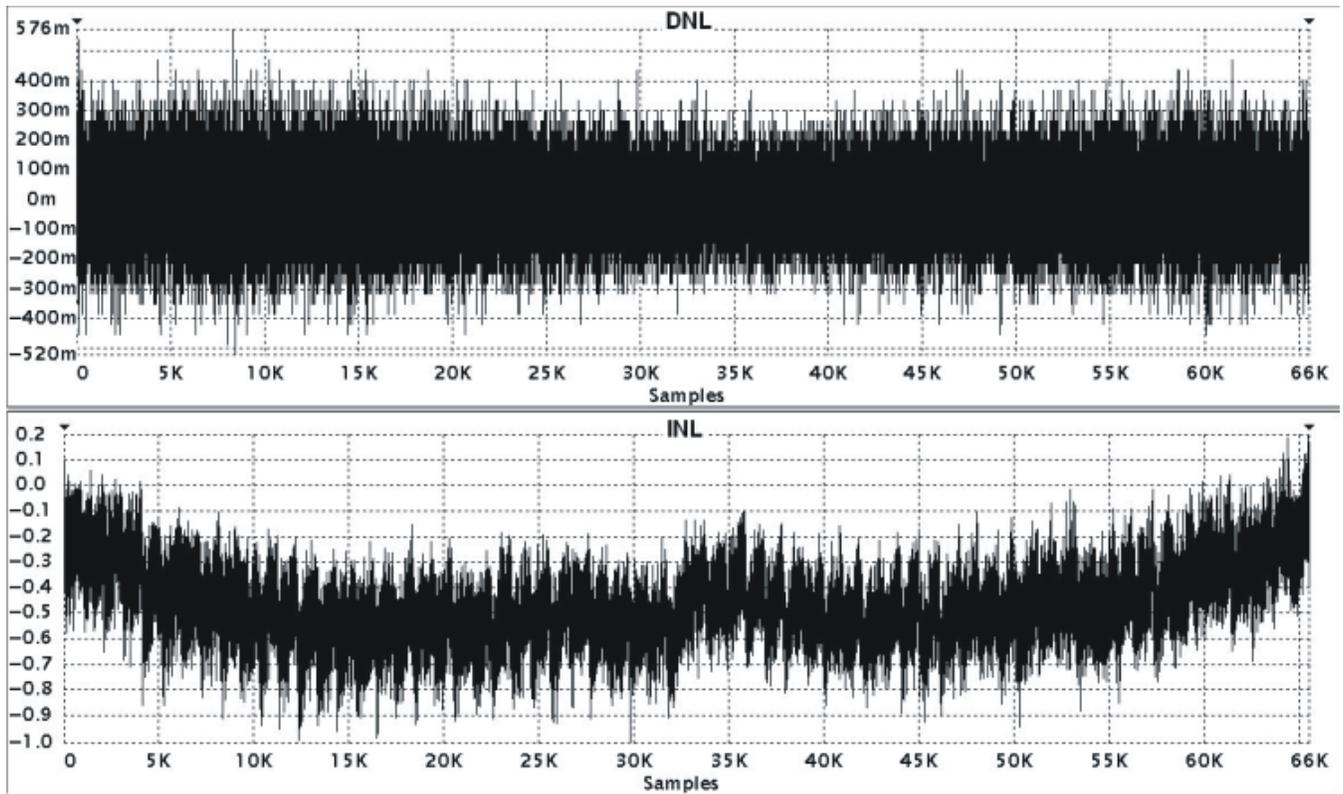


Figure 8. ADS8318: Typical Linearity Graphs (Differential Configuration)

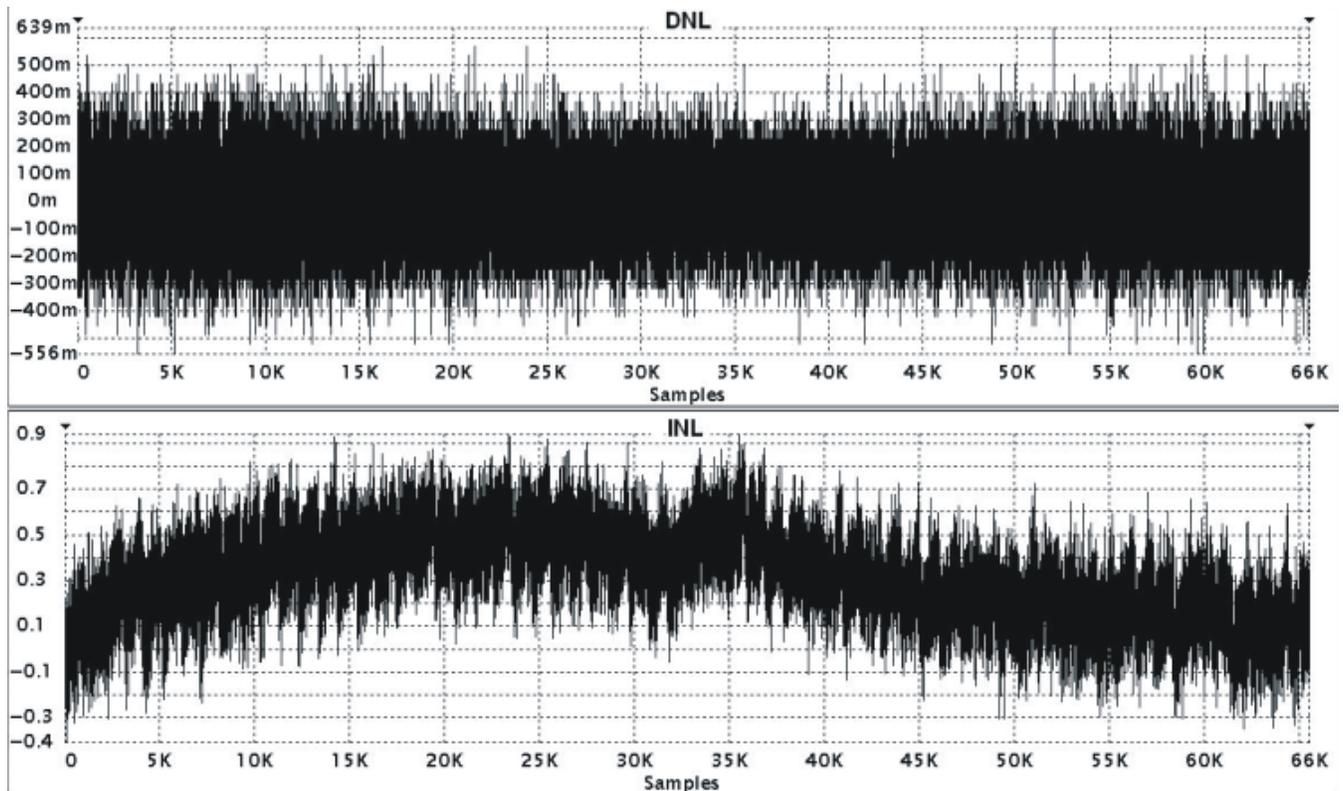


Figure 9. ADS8318: Typical Linearity Graphs (Single-Ended Configuration)

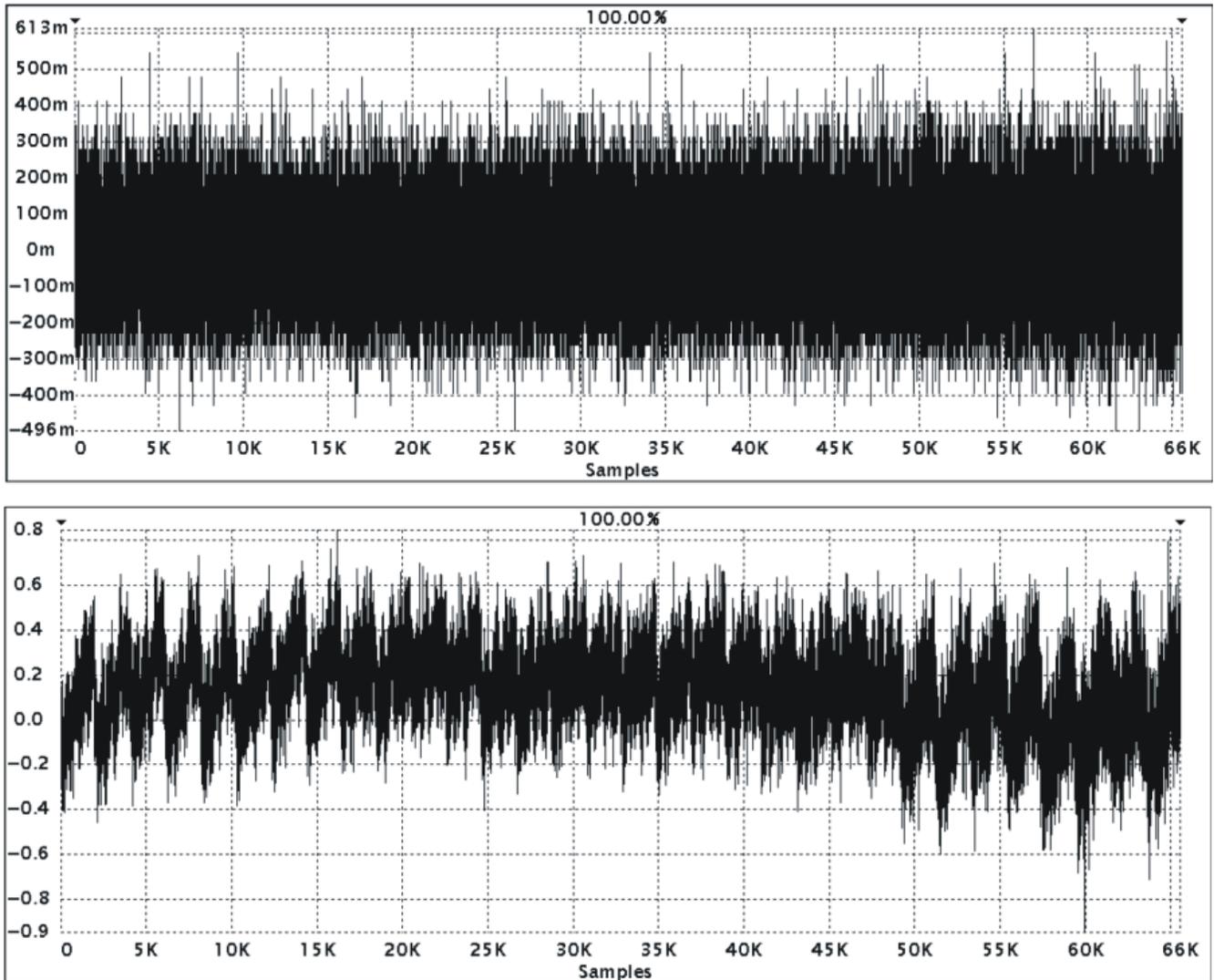


Figure 10. ADS8319: Typical Linearity Graphs

Table 1 describes the typical average power contribution from the various components used in the circuits shown in Figure 4 and Figure 6.

Table 1. Typical Average Power Numbers

Circuit	ADC	Input Driver Op Amps (THS4281)	REF5050	Reference Buffer (THS4281)	Total Power
ADS8318 Differential (Figure 4)	20 mW	$2 \times 0.8 \text{ mA} \times 7.3 \text{ V} = 11.68 \text{ mW}$	$0.8 \text{ mA} \times 7 \text{ V} = 5.6 \text{ mW}$	$1 \text{ mA} \times 7 \text{ V} = 7 \text{ mW}$	44.28 mW
ADS8319 (Figure 6)	20 mW	$0.8 \text{ mA} \times 7.3 \text{ V} = 5.84 \text{ mW}$	$0.8 \text{ mA} \times 7 \text{ V} = 5.6 \text{ mW}$	$1 \text{ mA} \times 7 \text{ V} = 7 \text{ mW}$	38.44 mW

Test Conditions: ADC: +VA = 5 V, +VBD = 5 V, V_{REF} = 5 V, Throughput = 500 kSPS, T = 300 kelvin, and input signal frequency = 1.9 kHz.

Op Amp: VDD = 7 V, VEE = -0.3 V

Table 2 summarizes the results obtained for a differential circuit configuration (see Figure 4), and Table 3 shows the results obtained for single-ended circuits (see Figure 5 and Figure 6).

Table 2. Performance Results for Differential Circuit Configuration (Figure 4)

Parameter	Datasheet Limits	ADS8318 with THS4031	ADS8318 with THS4281
DNL _{MAX}	< 1	0.33	0.47
DNL _{MIN}	> -1	-0.34	-0.52
INL _{MAX}	< 1.5	0.35	0.33
INL _{MIN}	> -1.5	-0.59	-0.68
SNR	> 95.5 dB	96.0 dB	95.5 dB
THD	-114 dB (typ)	-118 dB	-114 dB
SFDR	116 dB (typ)	121 dB	117 dB
SINAD	96 dB (typ)	96.0 dB	95.4 dB
Circuit power consumption	—	315.6 mW (for Figure 4)	44.28 mW (for Figure 4)

Table 3. Performance Results for Single-Ended Circuit Configuration (Figure 5 and Figure 6)

Parameter	Datasheet Limits	ADS8319 with THS4031	ADS8318 with THS4281	ADS8319 with THS4281
DNL _{MAX}	< 1.5	0.54	0.64	0.65
DNL _{MIN}	> -1	-0.5	-0.56	-0.53
INL _{MAX}	< 2.5	0.62	0.94	0.83
INL _{MIN}	> -2.5	-0.95	-0.4	-0.65
SNR	> 92 dB	93.9 dB	92.5 dB	92.5 dB
THD	-111 dB (typ)	-113 dB	-113 dB	-113 dB
SFDR	113 dB (typ)	115 dB	115 dB	115 dB
SINAD	93.8 dB (typ)	93.8 dB	92.4 dB	92.4 dB
Circuit power consumption	—	205.6 mW (for Figure 6)	55 mW (for Figure 5)	38.44 mW (for Figure 6)

5 Step-Input Settling

For applications where multiple signal channels must be sampled (such as those with a multiplexed input), the step response of the circuit is important. The response of the circuit shown in Figure 6 was studied for a 5-V step-input.

Simulation results are shown in Figure 11. Because of the presence of capacitance C1 (1 nF) in the feedback path, the THS4281 output shows an overshoot. The THS4281 output then settles to 18-bit accuracy (within 20 μ V, for a 5-V reference) within 0.54 μ s. The voltage at the IN+ pin of the ADS8319 settles to 18-bit accuracy within 1.57 μ s.

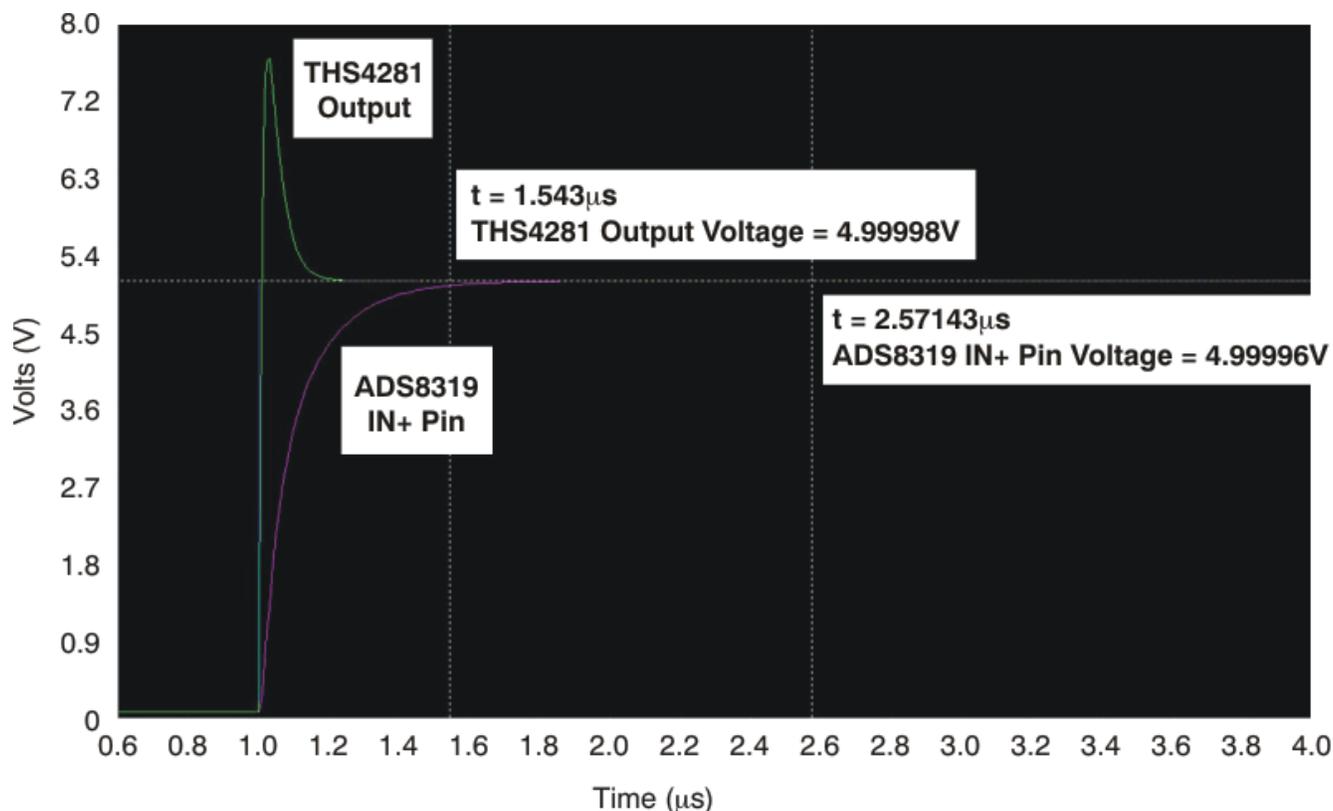


Figure 11. Step-Input Response for Circuit Shown in Figure 6

From the transfer function of the input drive circuit (see Figure 6):

- Natural frequency of oscillation (ω_n) = 47.55×10^6 rad/s
- Damping ratio (ζ) = 0.521
- Settling time (for 18-bit accuracy, output of THS4281) = 0.51 μ s
- Settling time required for voltage at IN+ pin of ADS8319 to 18-bit accuracy = $12.5 \times (2 \times 20\Omega) \times 3.3$ nF = 1.65 μ s

Thus, the numbers obtained from the simulation and the calculated numbers are reasonably consistent. The voltage at the IN+ pin of the ADS8319 should not take more than 1.65 μ s to settle to 18-bit accuracy. In a worst-case scenario, if the step-input changes at the end of conversion time (1.4 μ s), the total ADC cycle time will be 1.4 μ s + 1.65 μ s = 3.05 μ s. 3.05 μ s corresponds to a throughput of 333 kSPS. Thus, the circuit illustrated in Figure 6 (as well as those shown in Figure 4 and Figure 5) can operate with step-inputs only up to 333 kSPS speed.

6 Quick Op Amp Selection Guide

Figure 12 shows the operating region of the THS4281, where the op amp performs very well with ADS8318 and ADS8319. For operation of these ADCs at more than 300-kSPS throughput (with step-inputs), however, we must use an OPA365 or THS4031. This configuration comes with a penalty, though, in the form of the power dissipation required to achieve the desired performance. Figure 12 also illustrates the power dissipation of the OPA365 and THS4031 compared to the THS4281.

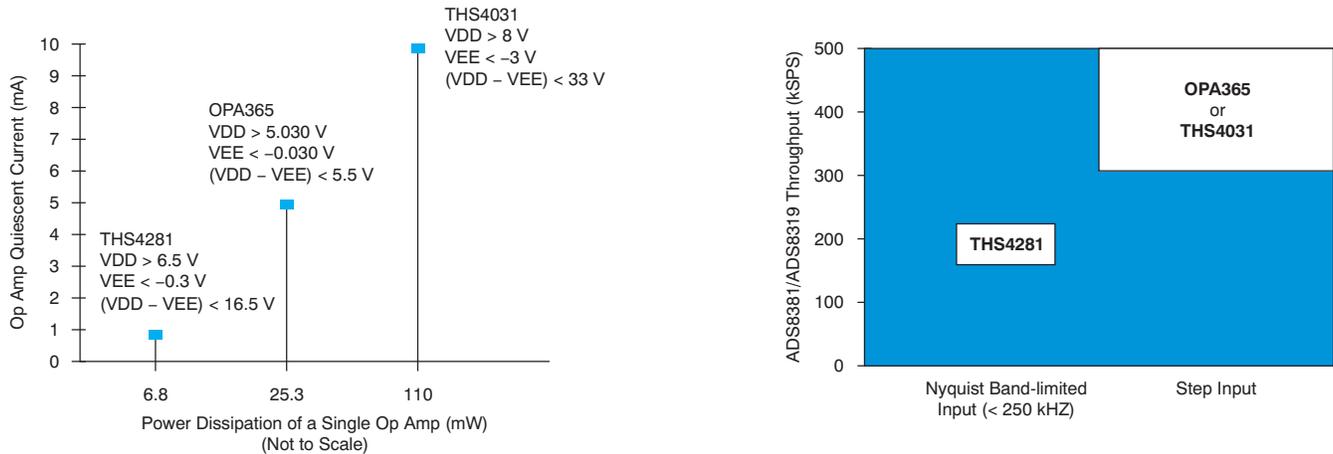


Figure 12. THS4281 Operating Region and Power Dissipation Comparison

When either the OPA365 or the THS4031 is used as an input driver in the circuits discussed earlier (see Figure 4, Figure 5, and Figure 6), some changes should be made to the component values used in the circuit. These changes are summarized in Table 4.

Table 4. Changes Required When THS4031 or OPA365 is Used as Input Driver

Component	THS4281	THS4031	OPA365
R ₁	49.9 Ω	Not installed	Not installed
C ₁	1 nF	Not installed	Not installed
C	3.3 nF	1 nF	1 nF
Minimum VDD	6.5 V	8 V	5.030 V
Maximum VEE	-0.3 V	-3 V	-0.030 V
Maximum allowed (VDD - VEE)	16.5 V	33 V	5.5 V

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated