

# Analog Engineer's Circuit

## Differentiator Circuit




### Design Goals

Input		Output		Supply		
$f_{\text{Min}}$	$f_{\text{Max}}$	$V_{\text{oMin}}$	$V_{\text{oMax}}$	$V_{\text{cc}}$	$V_{\text{ee}}$	$V_{\text{ref}}$
100Hz	2.5kHz	0.1V	4.9V	5V	0V	2.5V
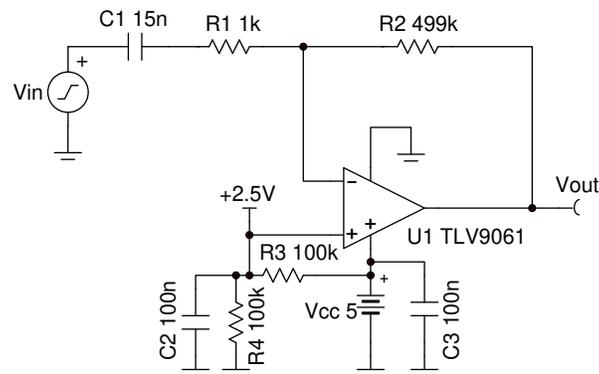
### Design Description

The differentiator circuit outputs the derivative of the input signal over a frequency range based on the circuit time constant and the bandwidth of the amplifier. The input signal is applied to the inverting input so the output is inverted relative to the polarity of the input signal. The ideal differentiator circuit is fundamentally unstable and requires the addition of an input resistor, a feedback capacitor, or both, to be stable. The components required for stability limit the bandwidth over which the differentiator function is performed.



Copyright © 2018, Texas Instruments Incorporated

### Design Notes

1. Select a large resistance for  $R_2$  to keep the value of  $C_1$  reasonable.
2. A capacitor can be added in parallel with  $R_2$  to filter the high-frequency noise of the circuit. The capacitor will limit the effectiveness of the differentiator function starting about half a decade (approximately 3.5 times) away from the filter cutoff frequency.
3. A reference voltage can be applied to the non-inverting input to set the DC output voltage which allows the circuit to work single-supply. The reference voltage can be derived from a voltage divider.
4. Operate within the linear output voltage swing (see Aol specification) to minimize non-linearity errors.

## Design Steps

The ideal circuit transfer function is given below.

$$V_{out} = -R_2 \times C_1 \times \frac{dV_{in}(t)}{dt}$$

1. Set  $R_2$  to a large standard value.

$$R_2 = 499k\Omega$$

2. Set the minimum differentiation frequency at least half a decade below the minimum operating frequency.

$$C_1 \geq \frac{3.5}{2 \times \pi \times R_2 \times f_{min}} \geq \frac{3.5}{2 \times \pi \times 499k\Omega \times 100Hz} \geq 11.1 \text{ nF} \approx 15\text{nF} \text{ (Standard Value)}$$

3. Set the upper cutoff frequency at least half a decade above the maximum operating frequency.

$$R_1 \leq \frac{1}{3.5 \times 2 \times \pi \times C_1 \times f_{Max}} \leq \frac{1}{7 \times \pi \times 15\text{nF} \times 2.5\text{kHz}} \leq 1.2k\Omega \approx 1 \text{ k}\Omega \text{ (Standard Value)}$$

4. Calculate the necessary op amp gain bandwidth product (GBP) for the circuit to be stable.

$$GBP > \frac{R_1 + R_2}{2 \times \pi \times R_1^2 \times C_1} > \frac{499k\Omega + 1 \text{ k}\Omega}{2 \times \pi \times 1 \text{ k}\Omega^2 \times 15\text{nF}} > 5.3\text{MHz}$$

- The bandwidth of the TLV9061 is 10MHz, therefore this requirement is met.

5. If a feedback capacitor,  $C_F$ , is added in parallel with  $R_2$ , the equation to calculate the cutoff frequency follows.

$$f_c = \frac{1}{2 \times \pi \times R_2 \times C_F}$$


6. Calculate the resistor divider values for a 2.5-V reference voltage.

$$R_3 = \frac{V_{cc} - V_{ref}}{V_{ref}} \times R_4 = \frac{5V - 2.5V}{2.5V} \times R_4 = R_4$$

$$R_3 = R_4 = 100k\Omega \text{ (Standard Values)}$$


## Design Simulations

### AC Simulation Results

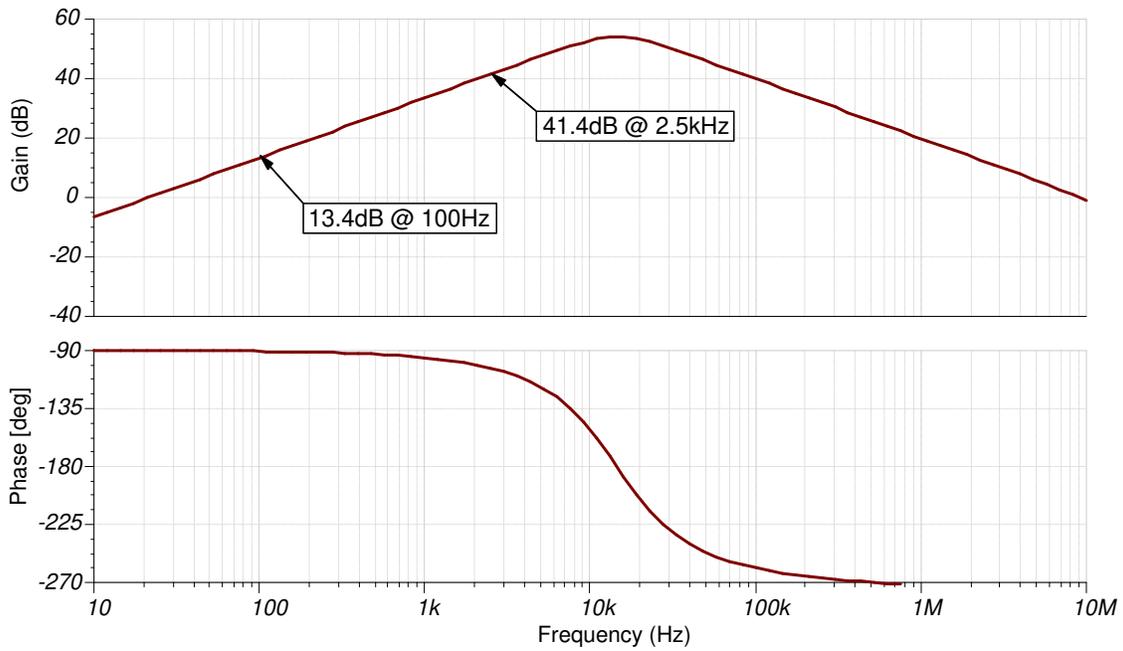

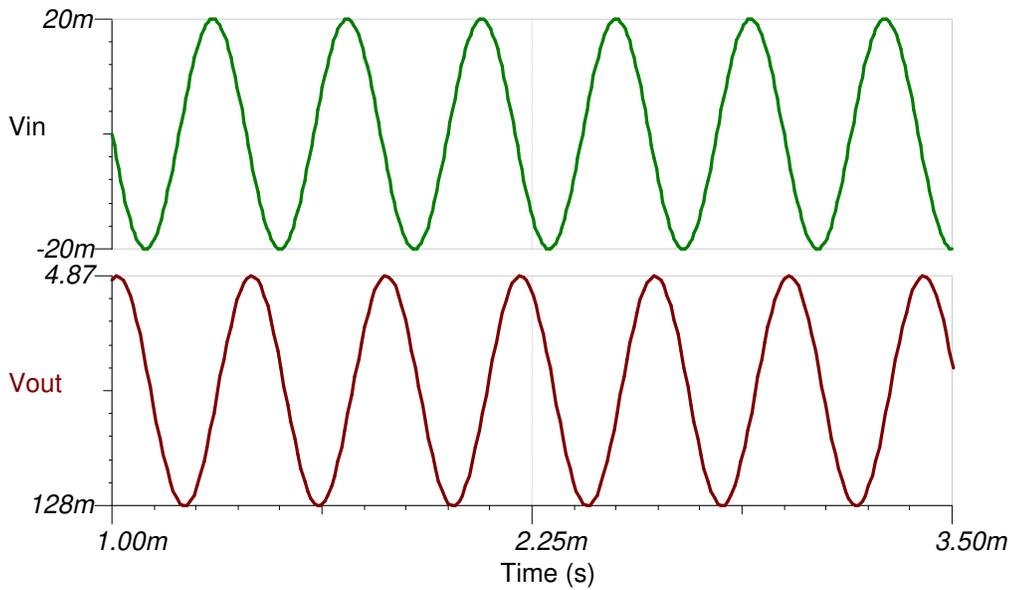
### Transient Simulation Results


A 2.5-kHz sine wave input yields a 2.5-kHz cosine output.



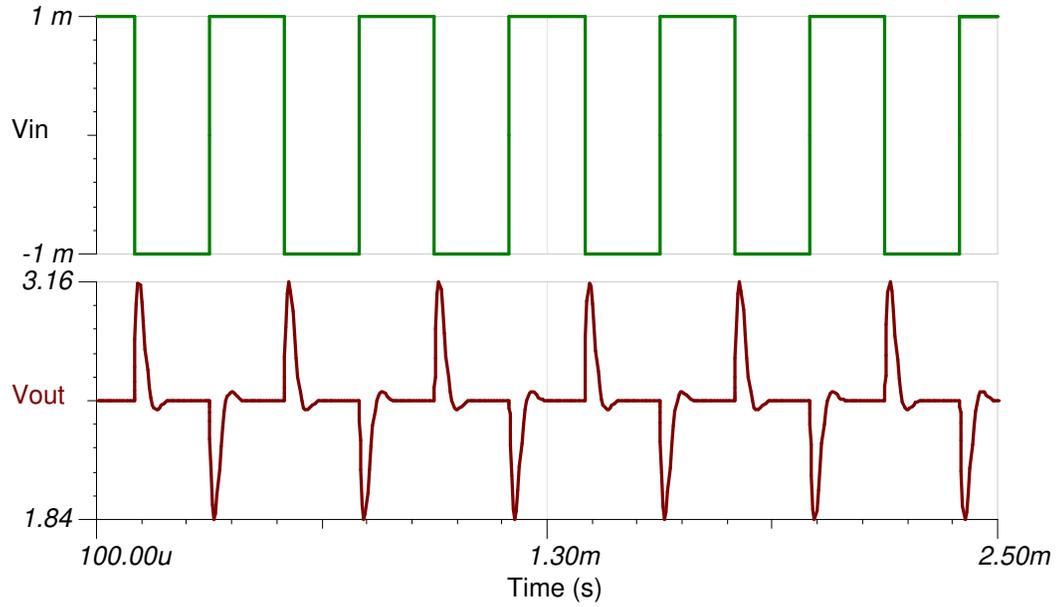A 2.5-kHz square wave input produces an impulse output.



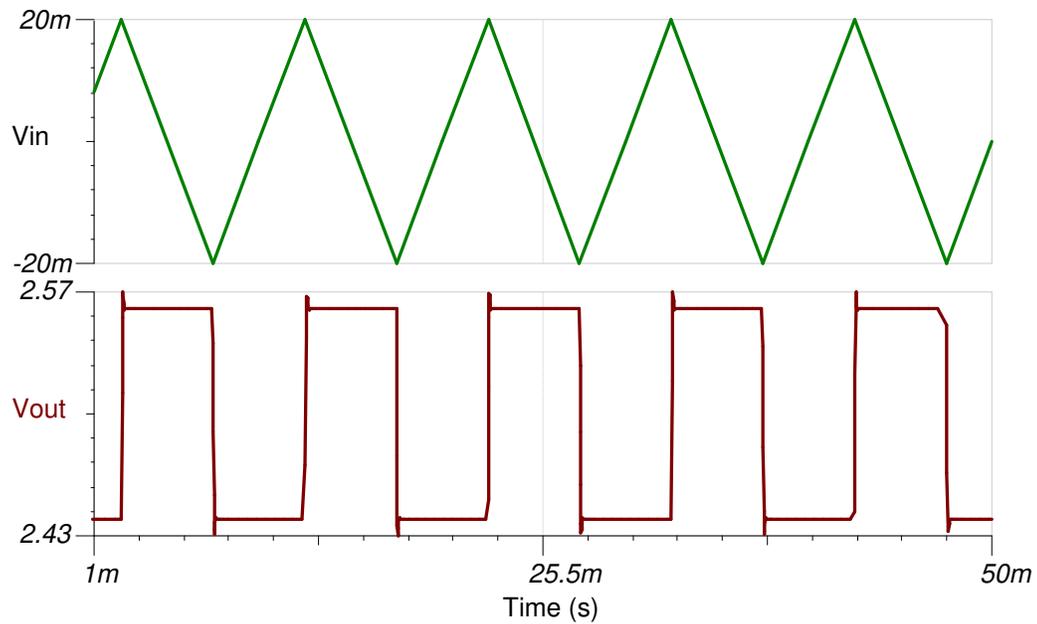A 100-Hz triangle wave input yields a square wave output.



## Design Featured Op Amp

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See circuit SPICE simulation file [SBOC497](#).

TLV9061	
$V_{CC}$	1.8V to 5.5V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	0.3mV
$I_q$	0.538mA
$I_b$	0.5pA
<b>UGBW</b>	10MHz
<b>SR</b>	6.5V/ $\mu$ s
<b>#Channels</b>	1, 2, 4
<a href="http://www.ti.com/product/tlv9061">www.ti.com/product/tlv9061</a>	

## Design Alternate Op Amp

OPA374	
$V_{CC}$	2.3V to 5V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	1mV
$I_q$	0.585mA
$I_b$	0.5pA
<b>UGBW</b>	6.5MHz
<b>SR</b>	0.4V/ $\mu$ s
<b>#Channels</b>	1, 2, 4
<a href="http://www.ti.com/product/opa374">www.ti.com/product/opa374</a>	

## Revision History

Revision	Date	Change
A	January 2019	Downscale the title and changed title role to 'Amplifiers'. Added link to circuit cookbook landing page.
B	April 2020	Changed $f_{MAX}$ in the Design Goals from 5kHz to 2.5kHz.
C	August 2021	Updated the numbering format for tables, figures and cross-references throughout the document.

## **IMPORTANT NOTICE AND DISCLAIMER**

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated