# Introduction to Current Sense Amplifiers



# Introduction

#### What are Current Sense Amplifiers?

Current sense amplifiers, also called current shunt monitors, are specialized differential amplifiers with a precisely matched resistive gain network with the following characteristics:

- Designed to monitor the current flow by measuring the voltage drop across a sense element, typically a shunt resistor.
- Tend to be easier to use, more precise, and less prone to noise.
- Support currents from 10s of µA to 100s of A.
- Natively-support common-mode voltages from –16 to +80 V and with additional circuitry up to 100s of volts.

#### System Benefits Addressed by Using Current Sense Amplifiers

- · Real-time overcurrent protection
- · Current and power monitoring for system optimization
- · Current measurement for closed-loop feedback

## **Key Parameters**

#### Common Mode Range

This specification defines the DC voltage range at the input of an amplifier with respect to ground. Current sense amplifiers are typically designed to support common-mode voltages well beyond the chip supply voltage. For example, the INA240 is capable of supporting a common-mode voltage between –4 V to +80 V while running on a supply as low as 2.7 V.

# Offset Voltage


This is a differential DC error at the input of the amplifier. Historically, to reduce the impact of amplifiers with high offsets, larger value shunt resistors were used to increase the measured voltage drop. Today, TI is able to offer current sense amplifiers with offsets as low as 10  $\mu$ V, enabling higher-precision measurements at low currents and allowing the use of smaller value shunt resistors for improved system efficiency.

#### Gain

Current sense amplifiers come with various gain options that have robust performance over temperature and process variations by integrating a precisely-matched resistive gain network. The gain options for fixed gain amplifiers vary from 0.125 V/V to 1000 V/V with gain errors as low as 0.01%.
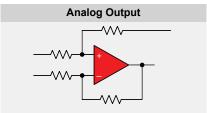
### Temperature Stability


Current sense amplifiers integrate the amplifier along with all the gain-setting resistors which enables small and unified temperature drift. This allows for robust current measurements across the whole specified temperature range. The achieved temperature stability is one of the key advantages current sense amplifiers have over discrete implementations.




Integrates the full analog signal processing and provides a voltage or current output.



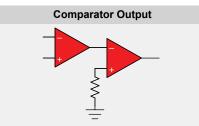Integrates the full signal conditioning path and utilizes a standard two-wire digital interface.



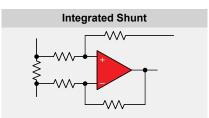Provides a simple ALERT signal when the load current exceeds a threshold.



Offers a low-drift, precision-integrated sense element.



# **Key Design Considerations**

# **High-Side Measurements**

Sensing between supply bus and load.

#### System Advantages:


- · Able to detect load short to ground
- · Current is monitored directly from the source
- · High immunity to ground disturbance

#### System Challenges:

· High bus voltage limits the availability of high input common-mode voltage devices
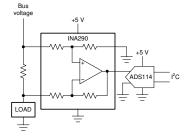
#### **Advantages Over Discrete Current Sense Circuit:**

- · Integrated gain resistors provide excellent matching to enable higher performance
- · Reduction in board space requirements
- Unique input architecture allows for the common-mode voltage to greatly exceed the device supply voltage



## **Low-Side Measurements**

Sensing between the load and ground.

## System Advantages:


- · Simple to implement and low-cost solution
- · Wide range of available options

#### System Challenges:

- · Difficult to detect load short to ground
- · System ground disturbance by the shunt resistor
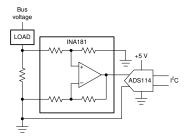
#### **Advantages Over Discrete Current Sense Circuit:**

- Integrated gain resistors provide excellent matching enable higher performance
- · Reduction in board space requirements
- · Sense a true differential measurement across the shunt resistor
- Lower V<sub>OFFSET</sub> saves system power by enabling the use of smaller value shunt resistors to achieve the same error level



## **In-line Measurements**

Sense current in-line to the load.

#### System Advantages:


- True phase current at all times reduces phase-to-phase errors
- · Best current feedback for greatest accuracy

#### **System Challenges:**

- · PWM common-mode voltage seen by amplifier
- High common-mode voltage combined with high dV/dT poses steep challenge to many amplifiers
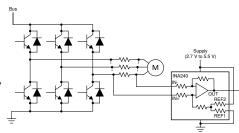
# INA240 Advantages Over Discrete Current-Sense Circuit:

 Enhanced PWM rejection provides high levels of suppression for large common-mode transients (dV/dT) in systems that use PWM signals



# IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2022, Texas Instruments Incorporated