

Output Overvoltage Protection Circuit for Voltage DACs With an External Feedback Pin



Precision DAC: Factory Automation and Control

Joseph Wu and Art Kay


Design Objective

Key Input Parameter	Key Output Signal	Recommended Devices
SPI or I ² C communication to control DAC voltage output	$\pm 10\text{V}$ output DAC signal with overvoltage protection	DAC8760, OPA206, TPS26611, TVS3301 (optional)

Objective: Protection of a $\pm 10\text{V}$ output signal from a sustained $\pm 32\text{V}$ overvoltage connection for a digital-to-analog converter (DAC) with an output buffer with a feedback sense pin.


Design Description

This circuit design describes an overvoltage protection circuit for a precision DAC output. This circuit protects the DAC output from a continuous overvoltage above the maximum and below the minimum supply voltages. In a device with a positive sense pin, the DAC output buffer is contained within the device, with a pin access to the positive sense feedback pin of the output buffer. The overvoltage protection circuit consists of an op amp with input protection set up in unity gain for the output buffer feedback sense pin, an eFuse to protect the output, and an optional transient-voltage-suppression (TVS) diode. For a DAC operating on $\pm 15\text{V}$, the output is protected to $\pm 32\text{V}$ or greater without damaging the DAC and the protection circuit. This type of protective circuit buffer can be used in many industrial factory automation and control applications. This circuit is particularly useful if the output experiences an overvoltage event from miswiring at an output terminal such as in a Programmable Logic Controller (PLC).

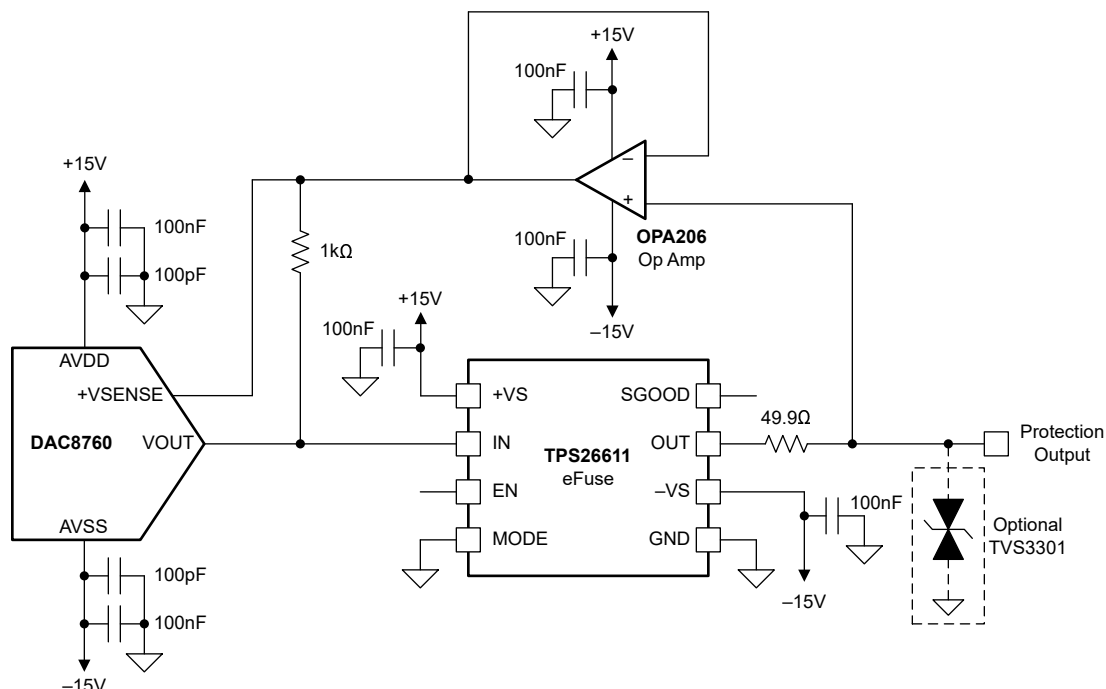

Design Notes

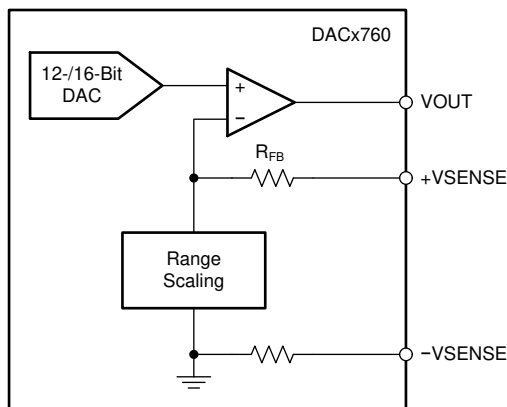
1. This design protects the output of a DAC with a positive sense pin as feedback from a sustained overvoltage event. The positive sense pin is the feedback to output buffer of the voltage DAC. The following figure shows the basic diagram.



This sense pin is used as a Kelvin connection to provide better accuracy where there are long traces or cables. There are many DACs that are configured with the positive sense pin, but this circuit uses the DAC8760 as an example. The DAC output is set to a range of $\pm 10\text{V}$.

2. If the DAC does not have a positive sense pin as feedback, the circuit in [Output Overvoltage Protection Circuit for Voltage DACs Without an External Feedback Pin](#) can be used to protect the DAC output.
3. The DAC8760 has three separate power supply inputs (AVDD, VDD, and AVSS). The [DAC8760](#) data sheet recommends using a decoupling capacitor for each power supply pin. In this circuit, parallel 100nF and 100pF capacitors are used as the decoupling capacitors for AVDD and AVSS. The DVDD pin uses a 100nF capacitor that is not shown in the circuit.
4. REFOUT is the output of the DAC8760 internal reference. Connect a 100nF capacitor from the REFOUT pin to ground if the internal reference is used. REFOUT is also not shown in the circuit.
5. The DAC is protected from overvoltage events using an op amp configured as a unity gain buffer to the feedback of the +VSENSE of the DAC output voltage. The output protection requires protecting the op amp input from a sustained overvoltage beyond the supply and from protecting the DAC output from sourcing or sinking excessive currents during these events.
6. An optional 1k Ω resistor is placed between VOUT and +VSENSE. This resistor prevents the output buffer feedback loop of the DAC from breaking in case the feedback sense signal is cut.

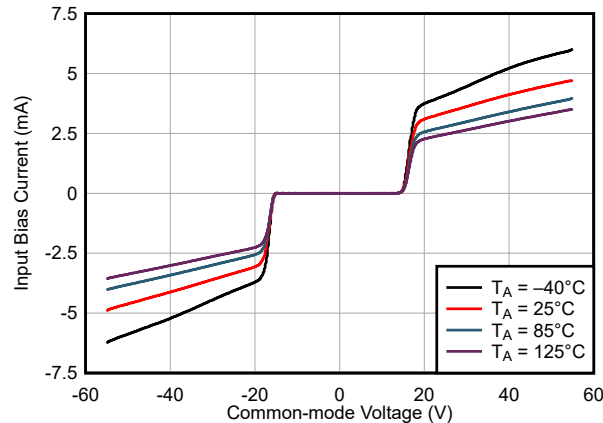
7. In this circuit, the [OPA206](#) is selected for the op-amp feedback buffer used for overvoltage protection. This op amp is selected for several characteristics:
- The offset voltage is very low and the buffer contributes little error to the DAC sense feedback. The OPA206 offset voltage is typically $\pm 4\mu\text{V}$ (at 25°C) and $\pm 55\mu\text{V}$ (from -40°C to 125°C).
 - The OPA206 has an integrated input overvoltage protection that extends up to $\pm 40\text{V}$ beyond the op-amp supply voltage. The input bias current relative to the input common-mode voltage for the OPA206 is shown in the following figure.



- If an alternate op amp without integrated input overvoltage protection is used, series resistance for the inputs can be used for protection to limit the input current. For more information about overvoltage and electrical overstress in op amps, see the TI Precision Labs – Op Amps video on [Electrical Overstress](#).
8. The [TPS26611](#) is a current loop protector that acts as an eFuse to limit the current of the DAC8760 voltage output at the VOUT pin. The TPS26611 has a fixed bipolar current limit of 32mA (I_{OL}).
- In normal operation, the TPS26611 passes the DAC8760 output current. Even if the short-circuit current limit of the DAC8760 is typically 30mA , the current through the ESD diodes to the output is not limited as the output voltage is forced beyond the DAC supply voltage.
 - The maximum series resistance of the TPS26611 is 12.5Ω . With an additional series resistance of 49.9Ω , the extra headroom needed at the supply output is 0.936V at an output of 15mA . With supplies of $\pm 15\text{V}$ and a DAC output range of $\pm 10\text{V}$, there is plenty of headroom for DAC operation.
 - The EN and $\overline{\text{SGOOD}}$ pins can be left floating.
 - The MODE pin is set to ground. In this setting, the device behavior depends on the I_{OUT} current through the TPS26611.
 - If $I_{OUT} < I_{OL}$, then the current I_{OUT} is passed through the TPS26611.
 - If $I_{OUT} > I_{OL}$, then I_{OUT} is quickly limited to I_{OL} through the TPS26611 for an expiry period of 100ms (t_{OL_Expiry}). If the current remains above I_{OL} , the device shuts off the output and the device retries the output after a period 800ms (t_{Retry1}).
 - Current protection in the TPS26611 is bidirectional, and negative current limits in a similar manner.
 - If the output voltage is forced beyond the positive or negative supply, the TPS26611 cuts off the output, preventing any damage.
 - For more information about using the TPS26611 as protection for an analog output module, see the [Protection for HART I/O in Analog Input and Output Modules with TPS2661x](#) application note.
9. An optional TVS diode is applied to the circuit for additional surge protection. If a TVS diode is used, the chosen breakdown voltage must be higher than any sustained overvoltage. If the breakdown voltage is less than the sustained overvoltage, then the overvoltage can damage the TVS diode. In this circuit, the expected sustained overvoltage is $\pm 32\text{V}$ and an optional [TVS3301](#) device with a bidirectional 33V breakdown is used for surge protection.


Simulation

The overvoltage protection feedback buffer is simulated with PSpice®. First, the transfer function of the buffer is simulated using a pulse voltage source as the DAC. The input of the feedback buffer is ramped from -10V to $+10\text{V}$, showing the full output range of the DAC. Another OPA206 is used as a model for the DAC output buffer. The OPA206 has a current limit of 25mA , which is an approximation for the DAC8760. The current limit is needed in a later simulation.

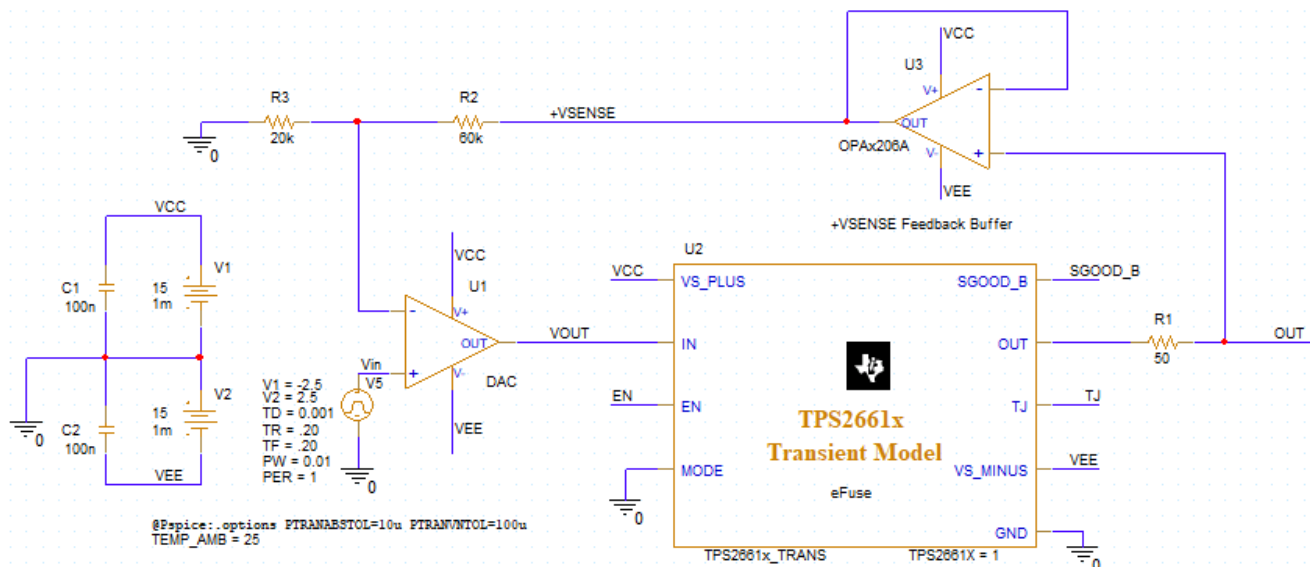


The op amp and resistor network on the left side of the figure represent the voltage DAC output and feedback. The nodes labeled +VSENSE and VOUT are pins for the DAC8760.

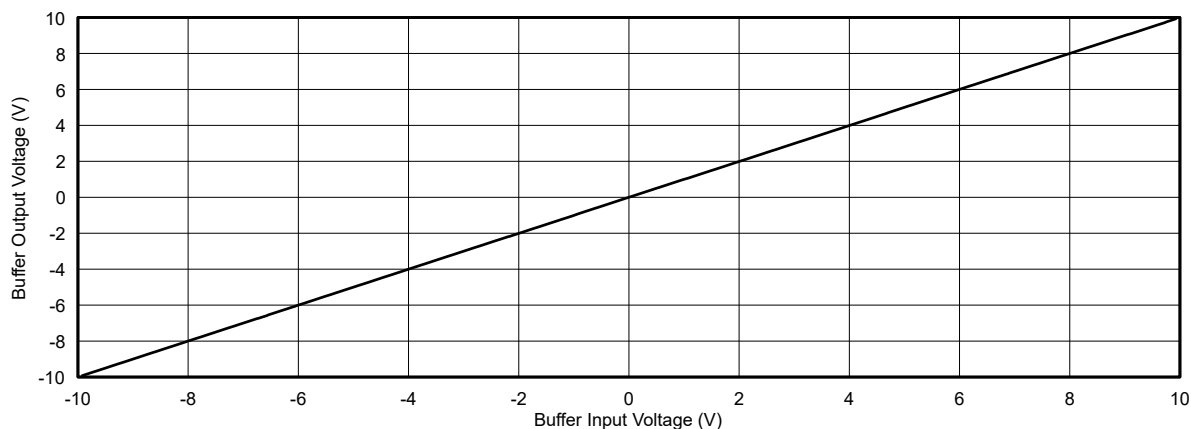The transfer function from input to output of the buffer is derived from the transient simulation.




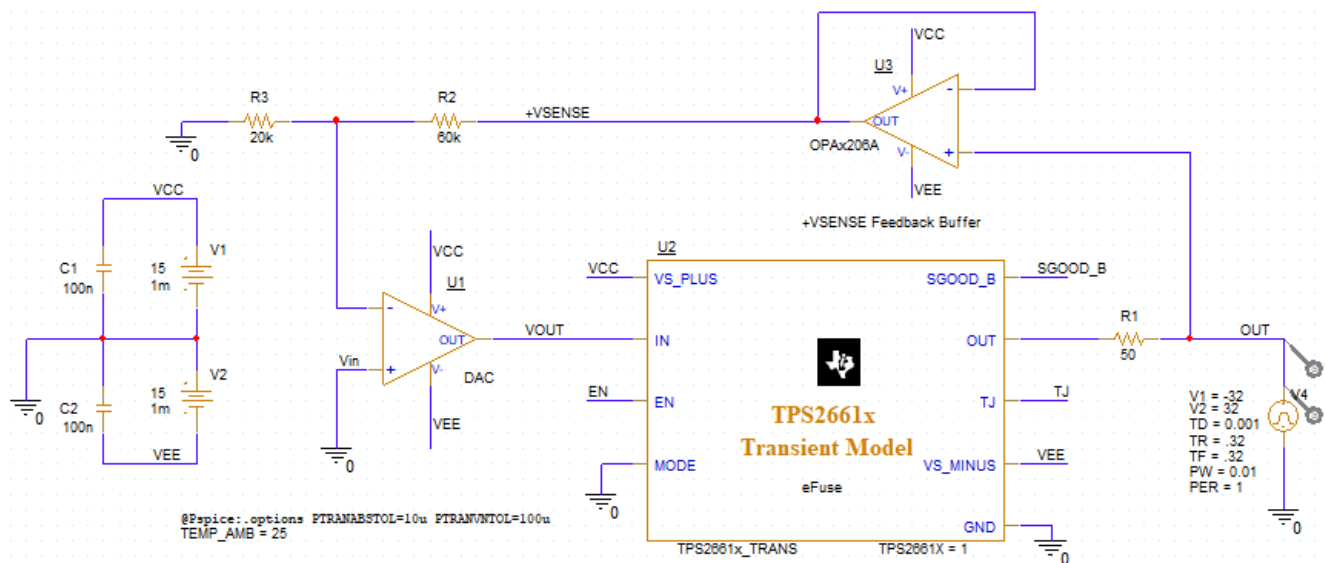A second transient simulation shows the current during an overvoltage event.



The DAC is set to 0V and a voltage supply is placed at the output of the buffer to simulate an overstress event caused by a wiring error. The supply ramp simulates the overvoltage transition from -32V to $+32\text{V}$.

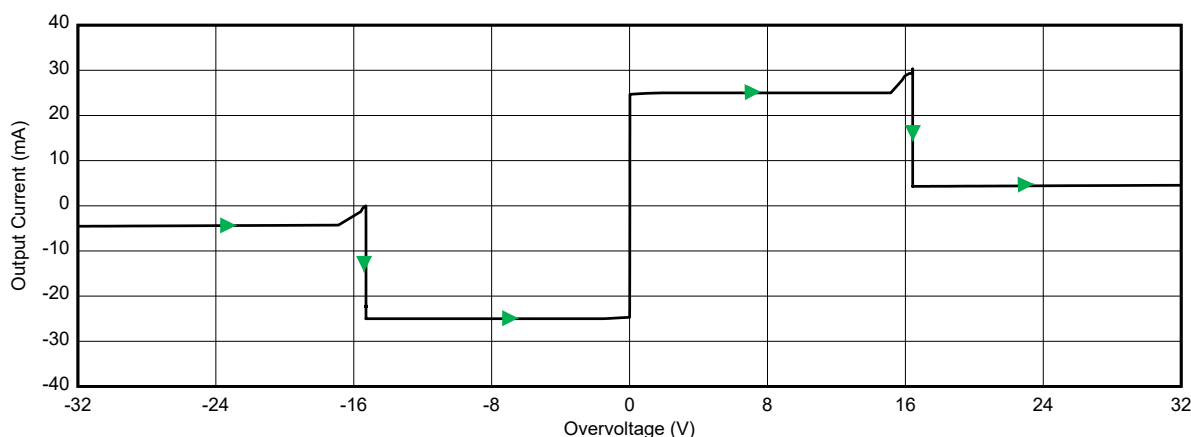The simulation begins with the output at -32V , the TPS26611 eFuse is open, preventing any current from being sourced from the output of the DAC8760. The residual current at the output comes from the input of the OPA206 which has an integrated input protection, limiting the current to about 5mA. The current seen at the output of the buffer remains at 5mA as the voltage is reduced.




As the voltage increases to near the lower supply voltage of -15V , the TPS26611 begins to conduct current from the DAC output. The DAC, driven by the ramping voltage, immediately reaches the device short-circuit current limit near 30mA. This current limit is lower than the 32mA current limit level of the TPS26611, which passes the conducted current. Sustained operation of the DAC8760 current limit is not destructive.

As the ramped voltage rises above 0V, the output of the DAC changes from sourcing current to sinking current. The DAC is forced into a current limit in the opposite direction.

Finally, the ramped voltage rises above the positive supply. Because of the added voltage from the series resistance and output current, the eFuse detects the output is beyond the supply after the ramped voltage rises above $+16\text{V}$. After the overvoltage is detected, the TPS26611 eFuse opens again and the DAC output stops sinking current. At the output, the only remaining output current comes from the OPA206 input overvoltage protection.

A similar simulation is run to show the voltage transition in the opposite direction. A supply ramp simulates the transition from +32V to -32V. When the simulation begins with the output at +32V, the TPS26611 eFuse is open, preventing any current from being sourced from the output of the DAC8760. Current at the output comes from the input of the OPA206. As the output voltage drops, the TPS26611 allows the short-circuit limited current of the DAC8760 to flow.

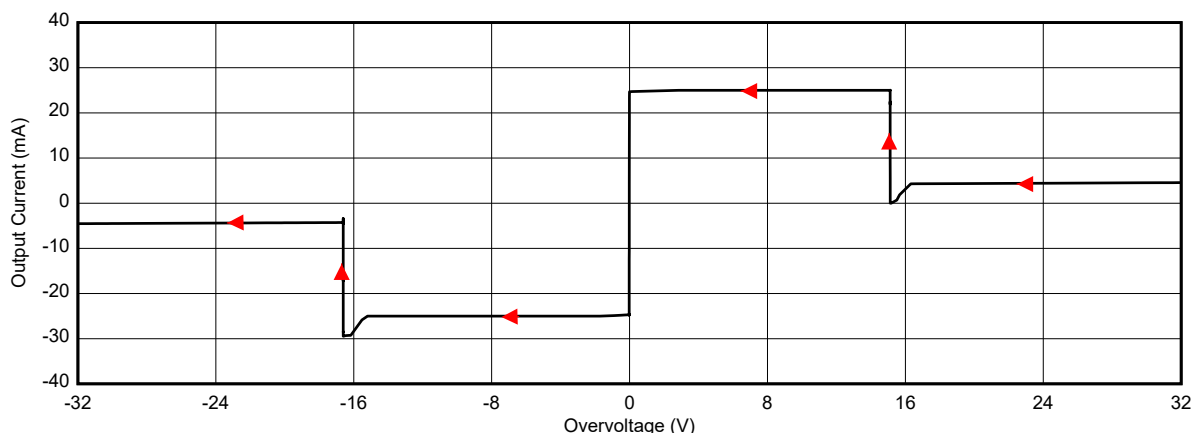
As the voltage drops below 0V, the current output of the DAC changes from sinking current to sourcing current. As the voltage continues to drop, the TPS26611 shuts off when the output voltage drops past -16V and the current sourced comes from the input of the OPA206.




In both simulations, the TVS3301 is not included. The output is not sent beyond the protection threshold of $\pm 33V$, which turns on TVS conduction. At the simulated level of 32V, the TVS3301 does not affect the operation of the protection buffer and output of the DAC.

Measured Results

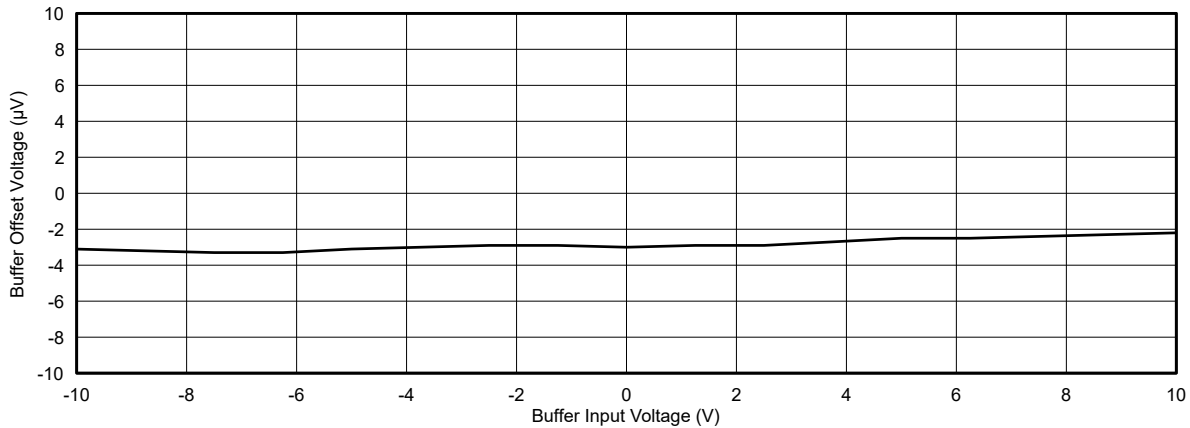The overvoltage protection buffer is constructed for testing and is attached to the output of the [DAC8760EVM](#). First, the output of the DAC is ramped from -10V to $+10\text{V}$ to drive the feedback buffer input. The offset seen from the buffer is measured to be less than $10\mu\text{V}$ over the full range.



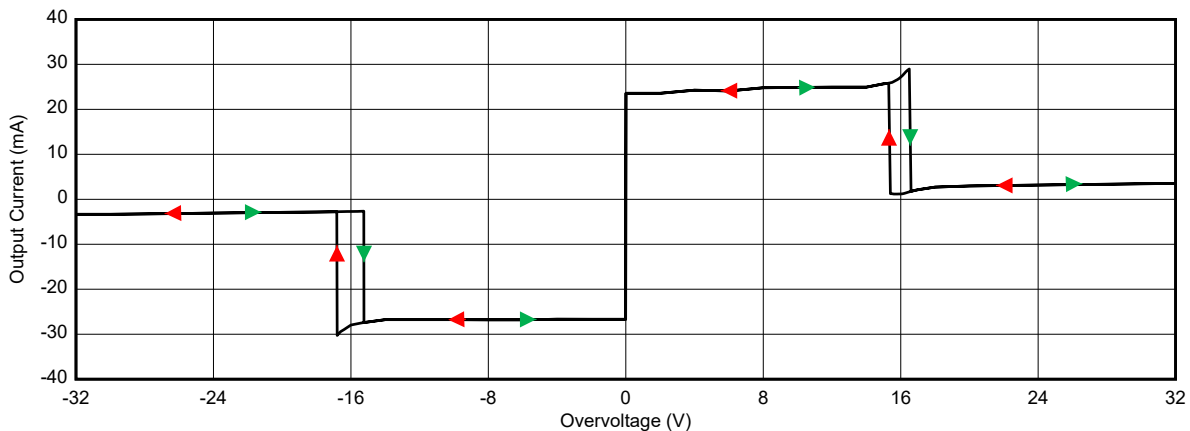The DAC is set to 0V and the output is then connected to a variable supply. As the output is driven, the current at the output is recorded. The measurement starts with the supply at -32V and the variable supply is raised to $+32\text{V}$. Then the output is changed from $+32\text{V}$ back down to -32V . This setup is similar to the schematic in the previously-described simulation.



In the test, the OPA206 short-circuit current and input protection current are slightly lower than simulation. There is a hysteresis in the closing and opening of the TPS26611 eFuse. This hysteresis is seen when superimposing the positive and negative overvoltage simulations and comes from the extra voltage across the series resistor at the output of the TPS26611. When starting with the TPS26611 eFuse closed and conducting current in normal operation, the eFuse opens when the output rises and is driven to about 1.5V to 2V beyond either supply. In the measurement, the TPS26611 shuts off when the output is forced up above 16.5V or below -16.8V . If the output is beyond the supply, the TPS26611 resumes operation when the voltage rises above $+15.3$ or drops below $+15.3$. This action is seen in the two overvoltage simulations, which combined have the same hysteresis behavior. This hysteresis comes from the extra voltage across the series resistor at the output of the TPS26611.

Register Settings

The following table shows an example register map for this application with the DAC8760. The values given here are for the design choices made in the [Design Notes](#) section.

Register Settings for DAC8760

Register Address	Register Name	Setting	Description
0x56	Reset	0x0001	[15:1] 0x0000: Writing to these bits does not cause any change
			[0] 0b1: Perform a software reset to all registers
0x55	Control	0x1003	[15] 0b0: VOUT clear sets to 0V upon reset
			[14] 0b0: DAC overrange not used
			[13] 0b0: External RSET resistor not used
			[12] 0b1: DAC output enabled
			[11:8] 0b0000: Slew rate clock control (not used)
			[7:5] 0b0: Slew rate step (not used)
			[4] 0b0: Slew rate is disabled
			[3] 0b0: Reserved, must be set to 0
0x01	DAC Data	0x8000	[2:0] 0b011: Voltage output set to $\pm 10V$ range
			[15:0] 0x8000: Set new value for DAC voltage output, 0V (default setting for DAC Data is 0x0000 which sets the VOUT to $-10V$ in this DAC range)

Pseudocode Example

The following shows a pseudocode sequence to initialize the setup for the DAC8760. This pseudocode sets up the device for one channel for an output of $\pm 10V$. The values given here are for the design choices made in the [Design Notes](#) section.

Pseudocode Example for DAC8760

```

1: //SYNTAX: WRITE <REGISTER NAME (Hex code)>, <MSB DATA>, <LSB DATA>
2: //Perform a software reset to the device registers
3: WRITE RESET(0x56), 0x00, 0x01
4: //Set DAC to  $\pm 10V$  range and enable output
5: WRITE CONTROL(0x55), 0x10, 0x03
6: //Default output setting is to  $-10V$ , set output to 0V
7: WRITE DAC DATA Register(0x01), 0x80, 0x00

```


Design Featured Devices

Find other possible devices using the [Parametric Search Tool](#).

Device	Key Features	Link
DAC8760	Single-channel, 16-bit programmable current and voltage output digital-to-analog converters for 4mA to 20mA current-loop applications	DAC8760
OPA206	Input-overvoltage-protected, 4 μ V, 0.08 μ V/ $^{\circ}$ C, low-power super beta, e-trim operational amplifiers	OPA206
TPS26611	50V, Universal 4–20mA, \pm 20mA current loop protector with input and output miswiring protection	TPS26611
TVS3301	33V Bidirectional flat-clamp surge protection device	TVS3301

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

Additional Resources

- Texas Instruments, [DACx760EVM and DACx750EVM User's Guide](#)
- Texas Instruments, [Output Overvoltage Protection Circuit for Voltage DACs Without an External Feedback Pin](#)
- Texas Instruments, [Protection for HART I/O in Analog Input and Output Modules with TPS2661x Application Report](#)
- Texas Instruments, [Precision labs series: Digital-to-analog converters \(DACs\)](#)
- Texas Instruments, [Precision labs series: Op Amps](#)
- Planet Analog, [Op-amp input protection can be noisy](#)

For direct support from TI Engineers, use the E2E community:

e2e.ti.com

Trademarks

PSpice® is a registered trademark of Cadence Design Systems, Inc..
All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2025, Texas Instruments Incorporated