

Product Overview

Multiplexers in Hearing Aids



In modern day hearing aids, multiplexers are used to select the audio signal either from omnidirectional or directional microphones to suppress ambient noise and provide a clear audio signal to the user. Since the audio signals need to be multiplexed before pre-amplification to provide the best noise filtering, select a multiplexer with minimal ON resistance and low total harmonic distortion (THD). Moreover, hearing aids are battery powered portable devices, so the design must be as compact and power efficient as possible.

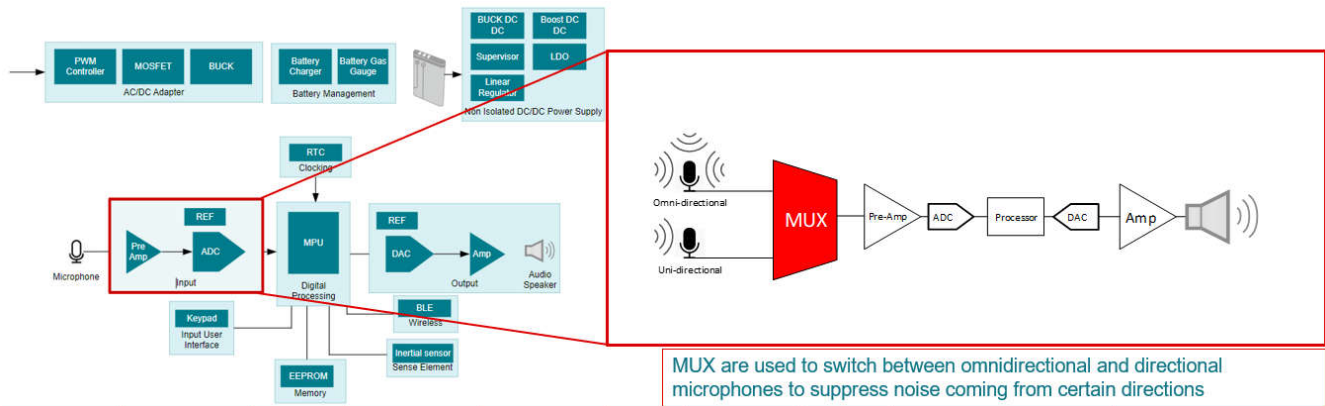


Figure 1. Hearing-Aid Block Diagram

Design Considerations

- RON: Low RON (<math><1\Omega</math>) is needed to maintain audio signal integrity
- Total harmonic distortion (THD) or RON flatness must be kept minimal to maintain audio signal integrity
- Supply Voltage Range: A low-voltage switch must be chosen to support the operating range.
- Package size: The smallest package must be chosen to keep the design compact
- Leakage: Low leakage current to maintain that the battery lasts long enough

Table 1. Recommended Parts

Device	Configuration	I/O Voltage	Supply Voltage	R-ON	C-ON/OFF	Leakage Current	THD
TMUX4827	2:1 x 2	-12V to +12V	1.8V to 5.5V	0.13 Ω	40/70pF	20nA	0.0008%
TMUX2889	2:1 x 2	-5.5V to +5.5V	1.8V to 5.5V	0.15 Ω	40/70pF	20nA	0.0008%
TS5A12301E	2:1 x 1	0V to 5.5V	2.25V to 5.5V	0.5 Ω	112/28pF	2nA	0.003%
TS5A3159	2:1 x 1	0V to 5.5V	1.65V to 5.5V	0.75 Ω	84/23pF	2.8nA	0.015%

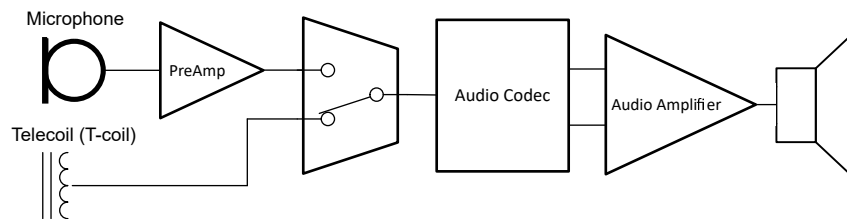


Figure 2. Typical Application

Additional Resources

- Learn about multiplexer parameters with this [TI precision lab video](#)
- Ask a question on our [TI E2E™ forum](#)
- Product Page: [Hearing Aid](#)

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, on-state resistance, and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated