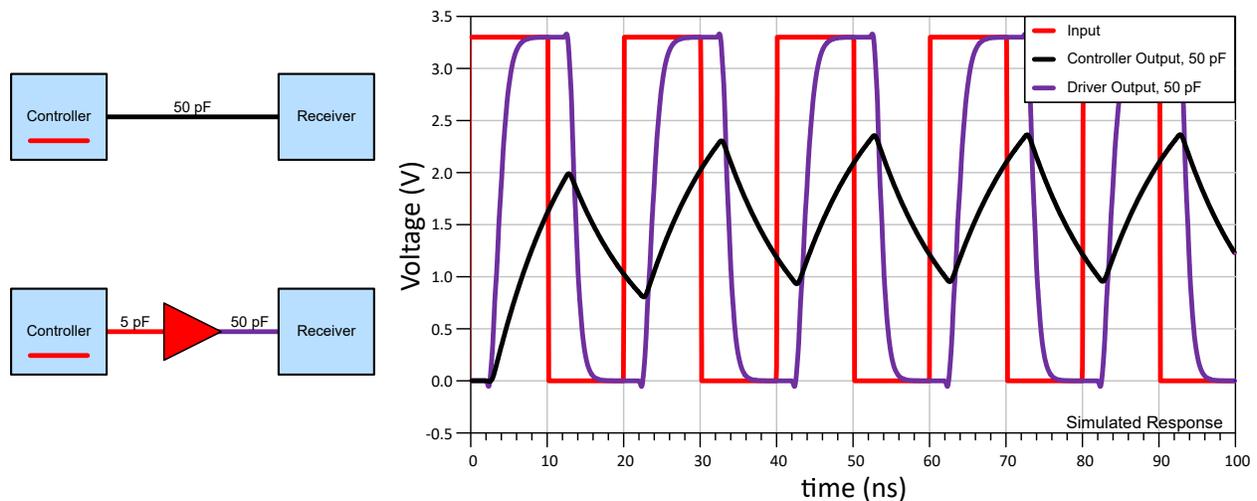


Product Overview

Redrive Digital Signals



System controllers can have weak output drive strength and thus cannot be used to directly transmit over relatively high capacitance signal lines. A logic buffer can be added to reduce loading and improve signal integrity. This can be done at intervals on a bus or trace to improve signal integrity and data rates in particularly large systems.



Left: block diagrams for signal redriving. Right: simulated input (red) and output signals with weak controller (black) and typical buffer driver from the LVC logic family (purple).

Figure 1-1. Signal Redriving Block Diagrams; Simulated Waveforms

Design Considerations

- Reducing load capacitance will decrease output transition time, allowing for faster operation
- Each buffer adds some delay; see the Switching Characteristics table in the device's data sheet
- For traces longer than 12 cm (4760 mil) see [Drive Transmission Lines With Logic](#)
- [\[FAQ\] How does a slow or floating input affect a CMOS device?](#)
- [\[FAQ\] Where do I find maximum power dissipation for a device?](#)
- Ask a question on our [Engineer-to-Engineer forum](#)

Recommended Parts

Part Number	AEC-Q100	V _{CC} Range	Channels	Features
SN74LVC1G34		1.65 V – 5.5 V	1	High Drive Strength – 32 mA Over-voltage tolerant inputs
SN74HCS125		2 V – 6 V	4	Schmitt-trigger inputs Input and output clamp diodes Three-state outputs
SN74HCS125-Q1	✓			
SN74AUC245		0.8 V – 2.7 V	8	Flow-through pinout Selectable direction Ultra high speed (t _{pd} < 5ns)

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated