

Optimizing Body Control Modules (BCMs) Using Logic and Translation



Albert Xu

Functional Block Diagram

For the purpose of this report, [Figure 1](#) is used to illustrate the logic and translation use cases. Each red block has an associated use-case document. Links are provided in [Table 1](#) and [Table 2](#). For a more complete block diagram, see the [Interactive Online End Equipment Reference Diagram for Body Control Modules](#).

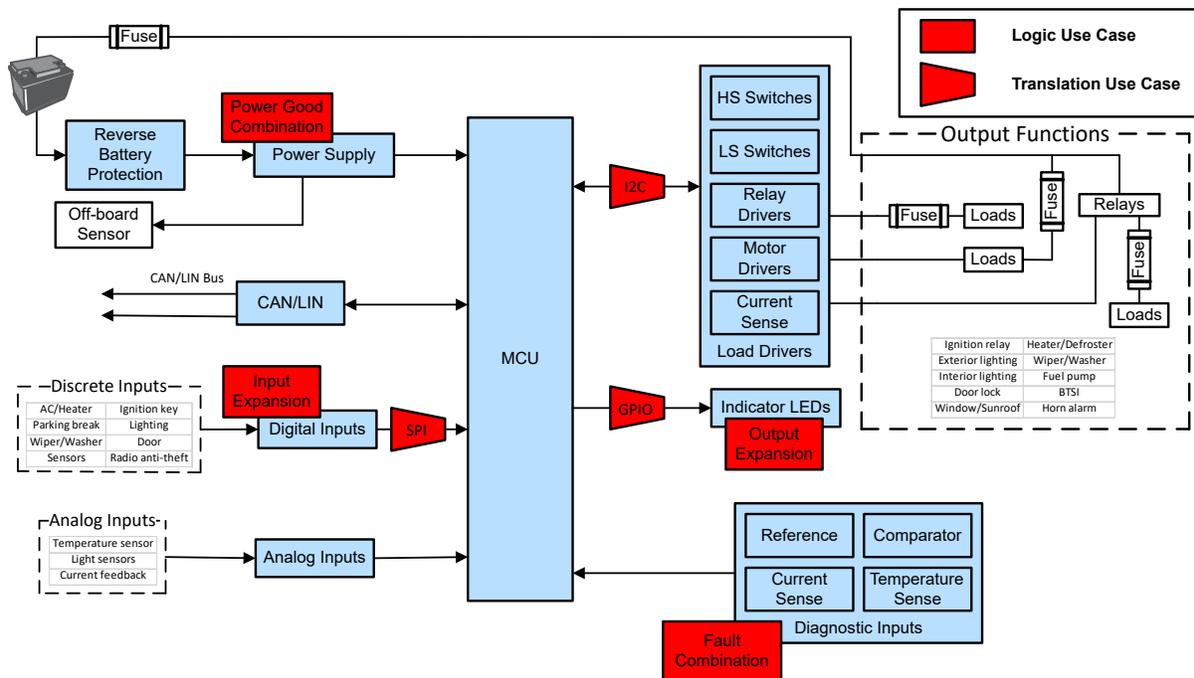


Figure 1. Simplified Body Control Module Block Diagram

Logic and Translation Use Cases

Each use case links to a separate document that provides additional details including a block diagram, design tips, and part recommendations. The nearest block and use-case identifiers are listed to match up exactly to the use cases shown in the provided [Figure 1](#).

Table 1. Logic Use Cases


Nearest Block	Use-Case Identifier	Use Case
Power Supply	Power Good Combination	Combine Power Good Signals
Digital Inputs	Input Expansion	Increase the Number of Inputs on a Microcontroller
LED Drivers	Output Expansion	Increase the Number of Outputs on a Microcontroller
Diagnostic Inputs	Fault Combination	Using Fewer Inputs to Monitor Error Signals

Table 2. Translation Use Cases

Nearest Block	Use-Case Identifier	Use Case
Load Drivers	I2C	Translate Voltages for I2C
LED Drivers	GPIO	Translate Voltages for GPIO
Digital Inputs	SPI	Translate Voltages for SPI

Increase the Number of Outputs on a Microcontroller

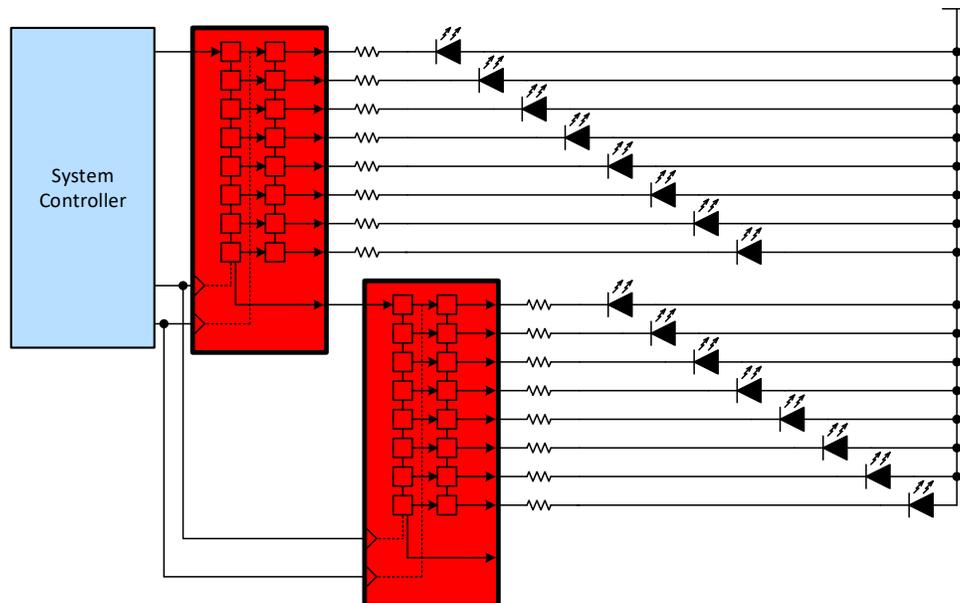Microcontrollers often have a very limited number of GPIO pins. Serial-in parallel-out shift registers can be used to output to a large number of devices while only using a few GPIO pins from the controller.



See more about this use case in the *Logic Minute* video [Increase the Number of Outputs on a Microcontroller](#).

- Serial input data (BR_{in}) must be faster than the desired output data rate (BR_{out}) based on the number of output bits (N) by this equation: $BR_{in} \text{ (Mbps)} = BR_{out} \text{ (Mbps)} \times N$
- The clock input controls the rate at which data is loaded into the shift register, $F_{clk} \text{ (MHz)} = BR_{in} \text{ (Mbps)}$
- For more outputs, shift registers can be daisy-chained together
- [\[FAQ\] What is the default output of a latched device? \(Flip-Flop, latch, register\)](#)
- Ask a question on our [TI Engineer-to-Engineer \(E2E™\) forum](#)

Recommended Parts

Part Number	V _{CC} Range	Bits	Output Register	Features
SN74HCS594-Q1	2 V to 6 V	8	✓	Schmitt-trigger inputs, Push-pull outputs
SN74HCS595-Q1	2 V to 6 V	8	✓	Schmitt-trigger inputs, 3-state outputs
SN74HCS164-Q1	2 V to 6 V	8		Schmitt-trigger inputs, Push-pull outputs
SN74HCT595-Q1	4.5 V to 5.5 V	8	✓	TTL-compatible CMOS inputs, 3-state outputs

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated