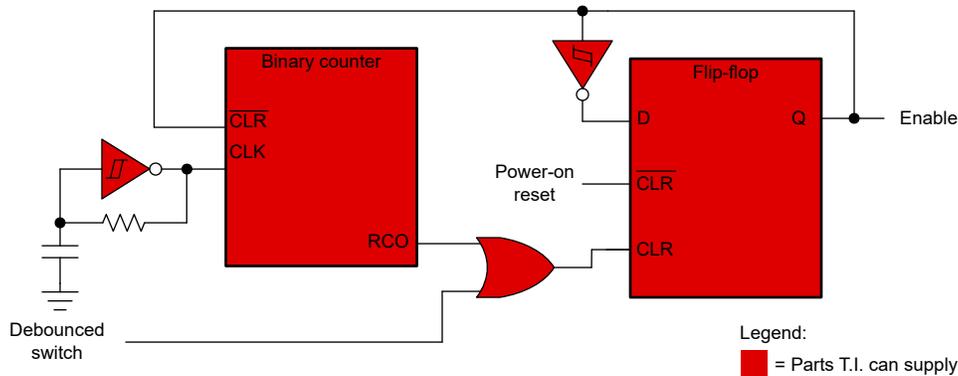


# Generate a Timed Pulse Using a Binary Counter



A binary counter paired with a resistor-capacitor (RC) oscillator generates a timed enable pulse, when triggered. Triggering a system that is not enabled enables the system for an amount of time determined by the RC, after which the system disables. Triggering an already-enabled system disables the system prematurely.



## Design Considerations

- A gate with Schmitt-trigger inputs connected to the debounced switch does not need a buffer to debounce the switch input
- The pulse width of the enable pulse when the switch is triggered is RC (number of bits)
  - Binary counters without an RCO output can use the highest bit output in the counter. Doing this reduces the effective number of bits of the counter by 1.
- When the device is first powered on, the flip-flop outputs an unknown state unless the device is reset with a power-on reset pulse
  - Systems which do not require starting in a specific state do not require asynchronous clear
- Ask a question on the [TI E2E™](#) forum

## Recommended Parts

Part Number	AEC-Q100	V <sub>CC</sub> Range	Function	Features
<a href="#">SN74LV163A</a>		2 V – 5.5 V	Binary counter	4 bit, RCO output, load function
<a href="#">SN74HC4060</a>		2 V – 6 V	Binary counter	14 bit, Integrated oscillator, Active high clear
<a href="#">SN74HC4060-Q1</a>	✓			
<a href="#">SN74LVC1G08</a>		1.65 V – 5.5 V	D-type flip-flop	1 channel
<a href="#">SN74LVC1G08-Q1</a>	✓			
<a href="#">SN74LVC1G175</a>		1.65 V – 5.5 V	D-type flip-flop	1 channel, Asynchronous clear
<a href="#">SN74LVC2G74</a>				
<a href="#">SN74LVC2G74-Q1</a>	✓	1.65 V – 5.5 V	D-type flip-flop	1 channel, Asynchronous clear, Inverted output, Preset
<a href="#">SN74LVC1G14</a>				
<a href="#">SN74LVC1G14-Q1</a>	✓	1.65 V – 5.5 V	Inverting buffer	1 channel, Schmitt-trigger inputs
<a href="#">SN74LVC1G32</a>				
<a href="#">SN74LVC1G32-Q1</a>	✓	1.65 – 5.5 V	OR gate	1 channel

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated