

Application Brief

Multiplexers in TI Programmable Logic Devices



Malcolm Lyn

Application Description

Multiplexing (also known as muxing) is a common logic application where a device known as a multiplexer selects between several digital or analog input signals and outputs the selected input on a single line. TPLD's customizable lookup tables (LUT) allow for easy implementation of digital muxing and demuxing of signals. In addition, some TPLD devices contain analog multiplexer modules, allowing TPLD to select between external analog signals such as sine and sawtooth waves. This document provides an overview of creating digital and analog muxes with TPLD.

2:1 Digital Multiplexer

A simple 2:1 digital multiplexer can be created by a single lookup table as shown in [Figure 1](#). The lookup table is configured with the equation $(A \& !C) \parallel (B \& C)$, where A and B are the signals to be multiplexed and C is the select signal. For more details on configuring lookup tables, see [Using Lookup-Tables in Programmable Logic](#).

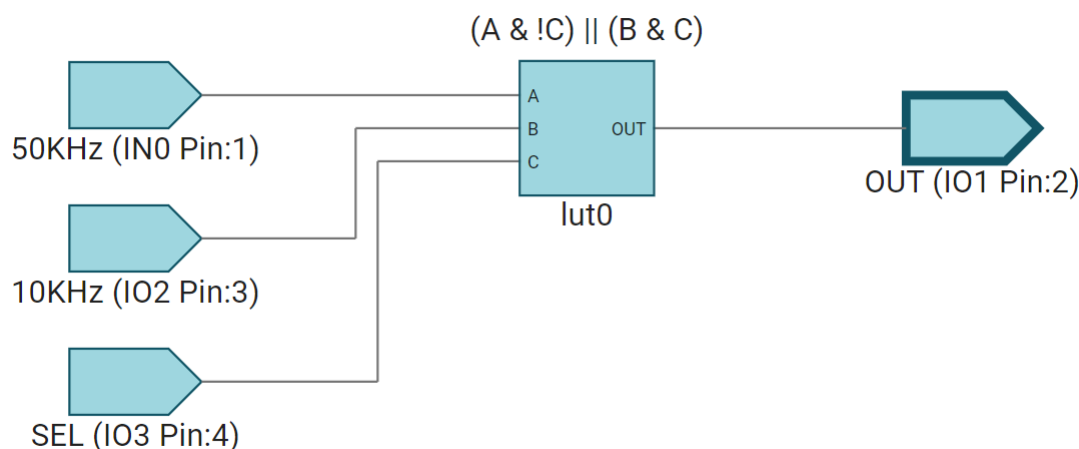


Figure 1. 2:1 Digital Multiplexer Using a Lookup Table

A simulation of the multiplexer is provided in [Figure 2](#), where the top two waveforms are the frequencies being multiplexed, the green waveform is the multiplexer output, and the red waveform is the select input.

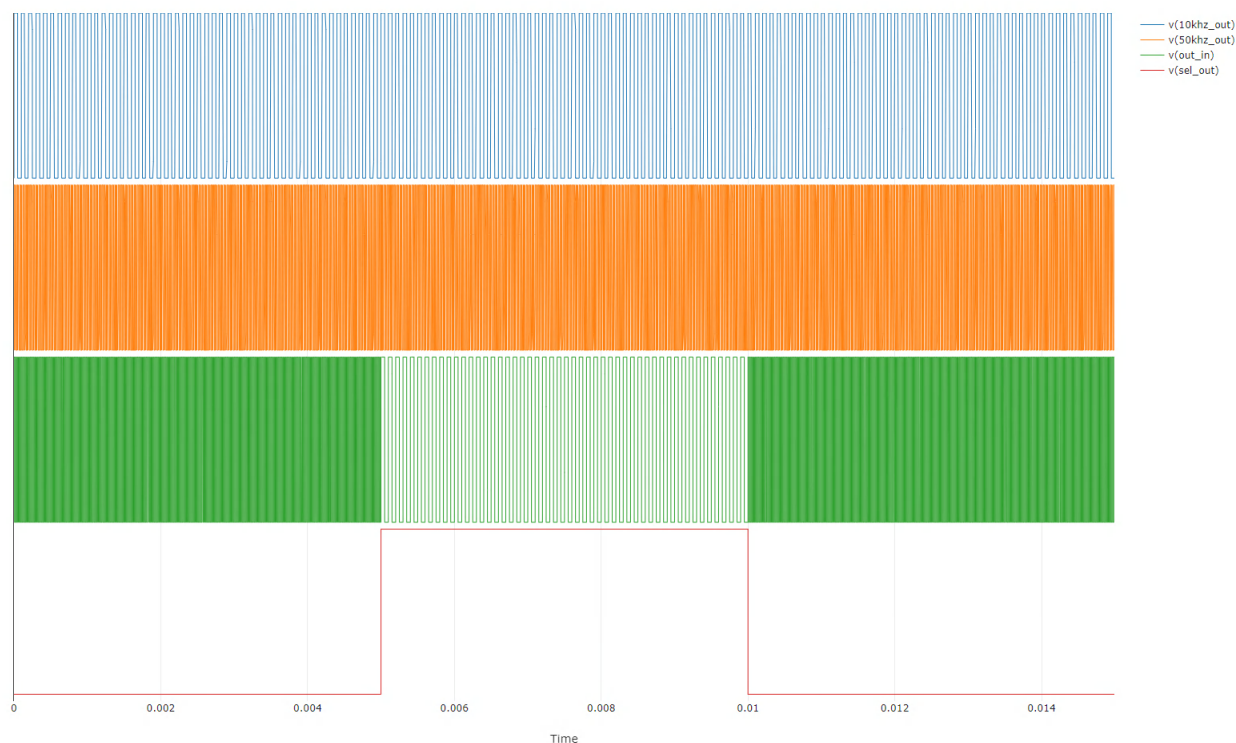


Figure 2. 2:1 Multiplexer Simulation

Chaining Multiplexers

4:1 or even 8:1 multiplexers or larger can be created by chaining three or more of the 2:1 multiplexer configuration from [Figure 1](#). [Figure 3](#) shows a 4:1 multiplexer configuration.

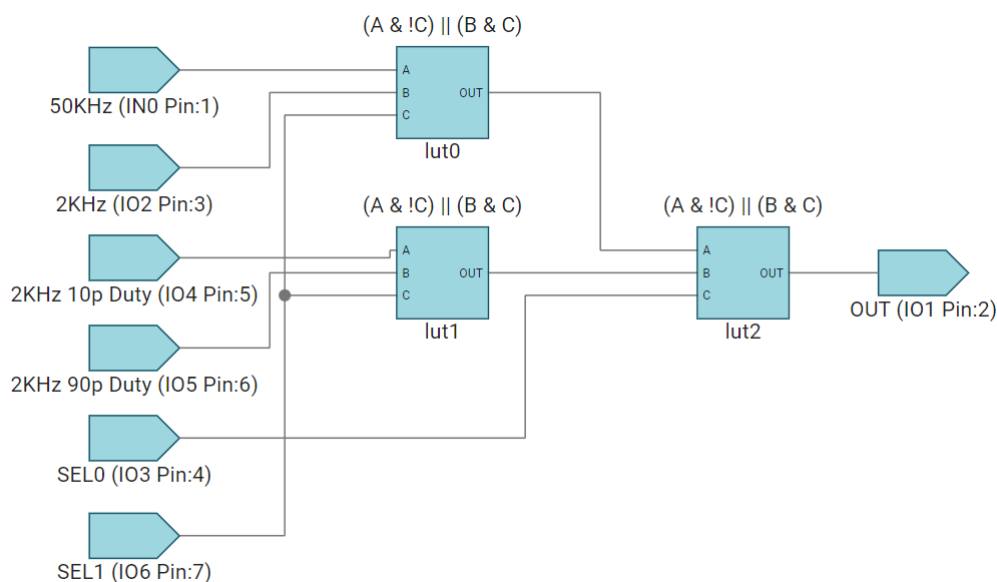


Figure 3. 4:1 Multiplexer From Three 2:1 Multiplexers

Figure 4 shows simulation results for this configuration. The top four signals are the inputs of varying frequencies being multiplexed, the purple signal is the multiplexer circuit output, and the bottom two signals are the multiplex select inputs.

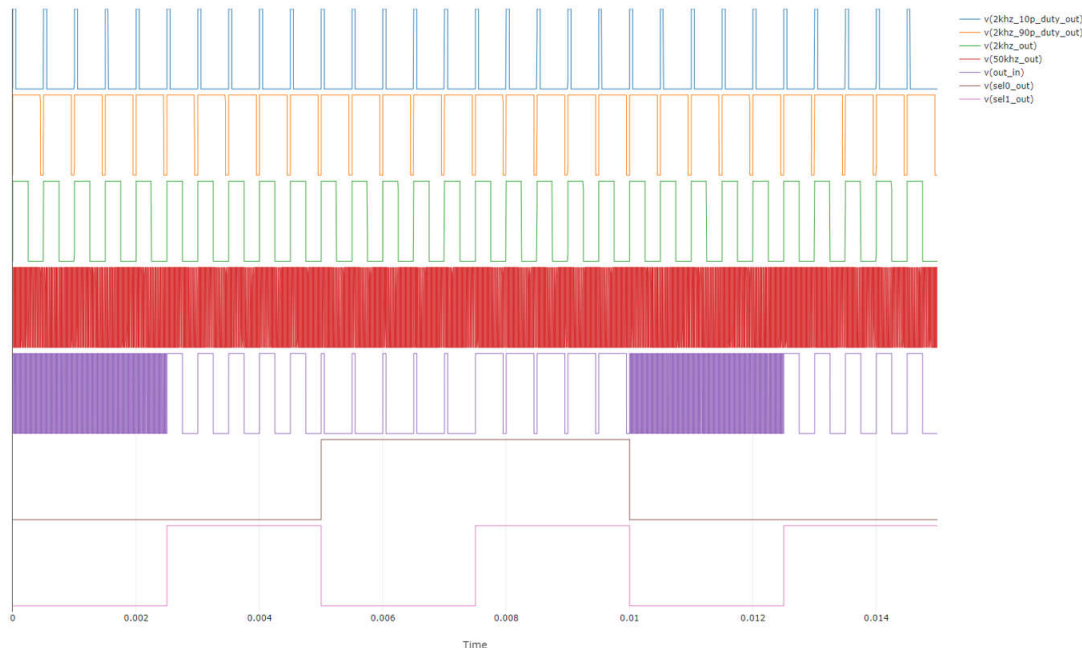


Figure 4. 4:1 Multiplexer Simulation

2:1 Analog Multiplexer

Some TPLD have analog multiplexers which can select between two analog signals. This module is shown in Figure 5.

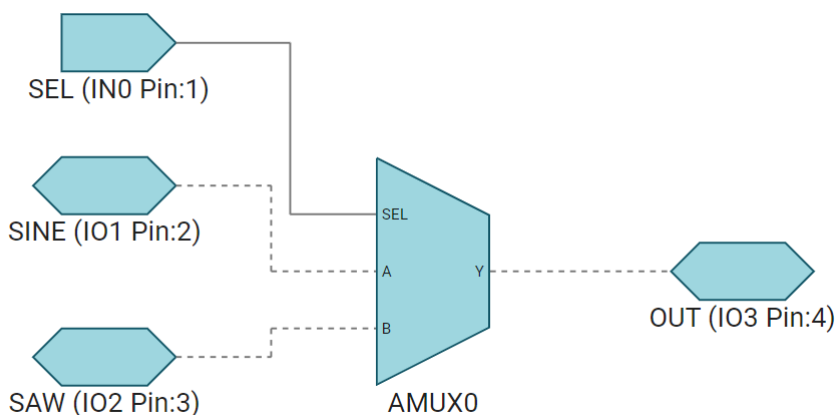


Figure 5. 2:1 Analog Multiplexer Module

Figure 6 shows a simulation where the module muxes between a sine wave and sawtooth wave.

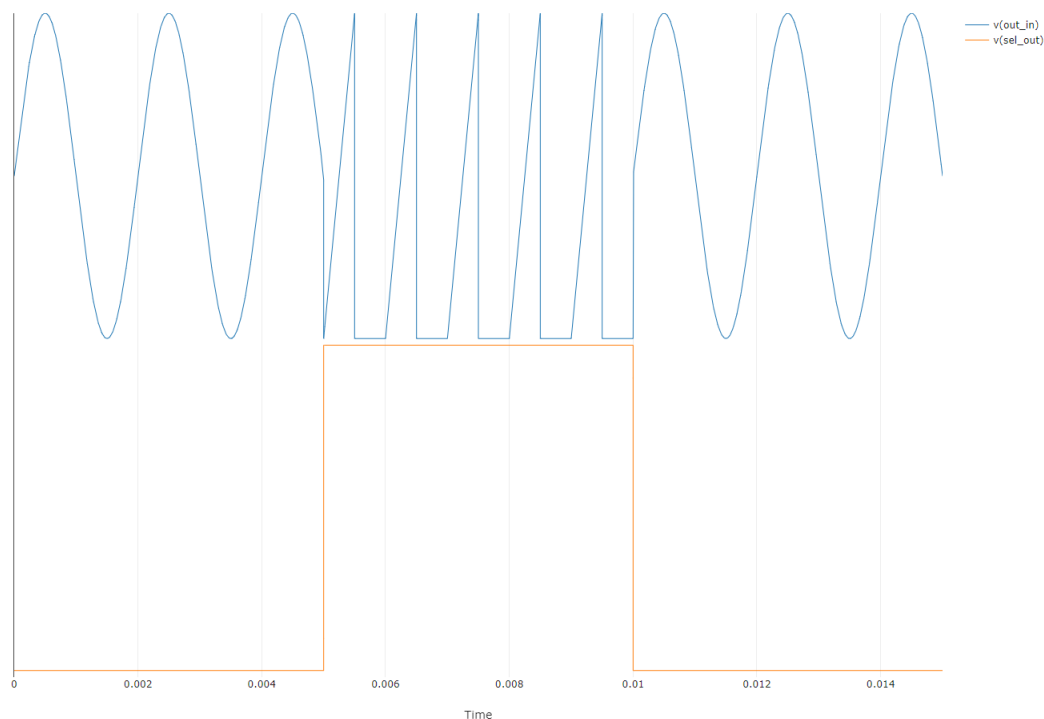


Figure 6. 2:1 Analog Multiplexer Simulation

Conclusion

TPLD's lookup tables allow for easy configuration of 2:1, 4:1, and even 8:1 digital muxes that can be used to select between both external and internal digital signals. Some TPLD also have 2:1 analog muxes which allow for the devices to control the selection of analog signals.

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2025, Texas Instruments Incorporated