

Improving Accuracy of Shunt-Less Short Circuit Protection in Wide Temperature Range Using LM74912-Q1



Shiven Dhir, Praveen GD, Abhijeet Godbole

Introduction

In automotive applications, robust reverse polarity protection is essential to safeguard downstream electronics from potential damage. Systems such as Advanced Driver Assistance Systems (ADAS), which are directly connected to the vehicle's battery bus, are particularly susceptible to such faults. To address this, ideal diode controllers are employed at the power input, emulating a low forward-voltage (V_F) diode by driving an external N-channel MOSFET.

As system power demands continue to rise, traditional Schottky diodes become thermally inefficient and inadequate, prompting the replacement with ideal diode designs that offer lower power dissipation and enhanced thermal performance. Furthermore, with increased load currents, it becomes critical to implement overcurrent and short-circuit protection mechanisms.

To meet these requirements, modern ideal diode controllers integrate precision current-sense amplifiers, enabling real-time current monitoring and fault protection. This integration reduces BOM count, PCB area, and design complexity by offering a compact, single-chip protection design.

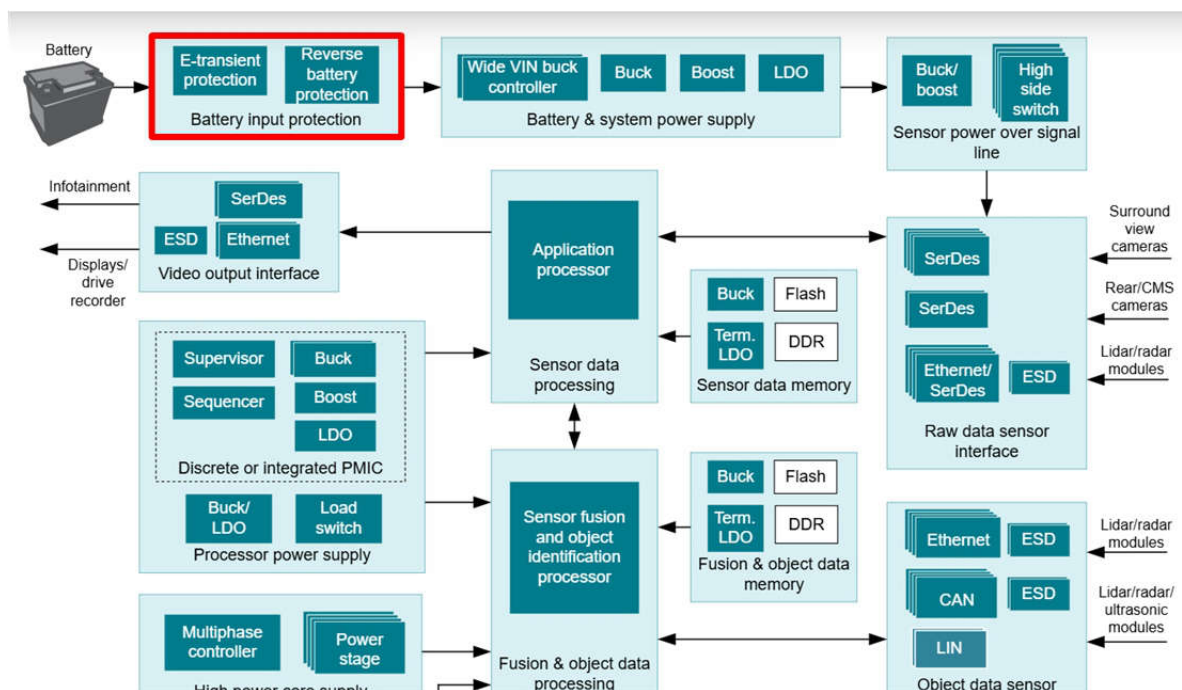


Figure 1. ADAS Domain Controller

LM749xx-Q1 Ideal Diode Controller Overview

The LM749xx-Q1 family of Ideal Diode controller drives back-to-back external N-Channel MOSFETs to realize low loss power path protection with circuit breaker, under and over voltage protection functionality. The wide input supply of 3V to 65V allows protection and control of 12V and 24-V automotive battery powered ECUs. The device can withstand and protect the loads from negative supply voltages down to -65 V . An integrated ideal diode controller (DGATE) drives the first MOSFET to replace a Schottky diode for reverse input protection and output voltage holdup. With a second MOSFET in the power path the device allows load disconnect (ON/OFF control) and overvoltage protection using HGATE control. The device features an adjustable overvoltage cut-off protection feature. With Common Drain configuration of the power MOSFETs, the mid-point can be used for OR-ing designs using another ideal diode. The LM749xx-Q1 has a maximum voltage rating of 65V. This family has two major devices, LM74900-Q1 and LM74912-Q1. The devices differ in how the devices protect from short circuit protection.

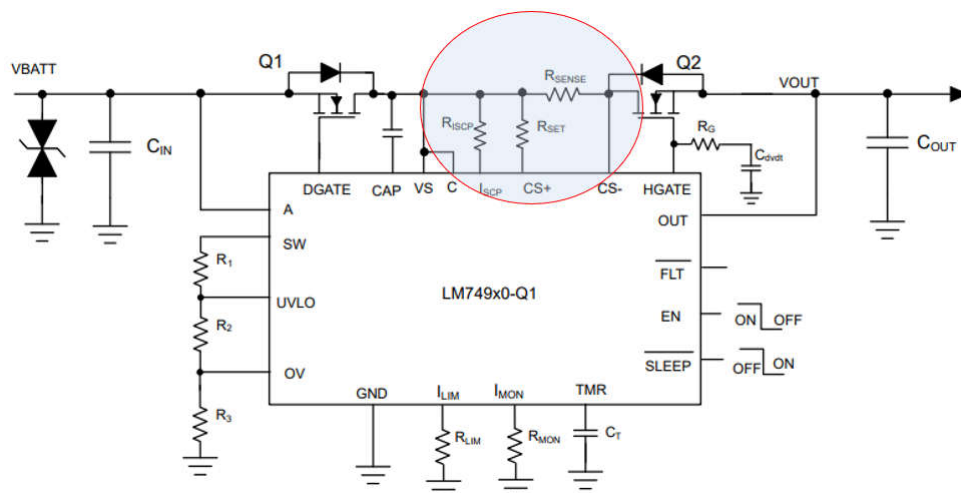


Figure 2. Typical Application Diagram of LM749x0-Q1

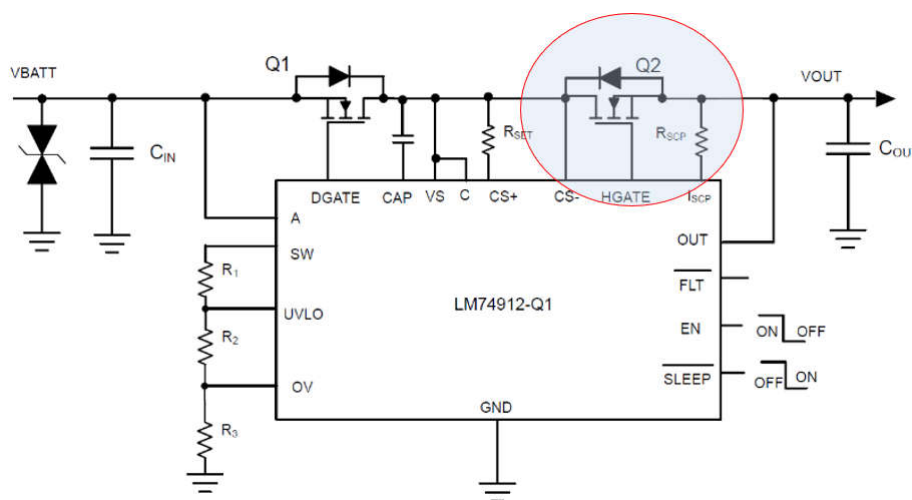


Figure 3. Typical Application Diagram of LM74912-Q1

As shown in [Figure 2](#) and [Figure 3](#) LM749x0-Q1 uses a shunt resistor to feed information to the internal current sense amplifier whereas LM74912-Q1 uses MOSFET V_{DS} for the same function.

Although the shunt provides high accuracy but also increases solution size and cost of the design whereas LM74912-Q1 resolves this but can have wide accuracy at different temperature due to the MOSFET.

Protection Against Short Circuit using LM74912-Q1

The LM74912-Q1 integrates a fast-acting short-circuit protection mechanism to safeguard the external high-side FET and the downstream loads. The internal short-circuit comparator is activated once the HGATE-OUT voltage exceeds 6.4V (typ), ensuring the FET is fully enhanced and avoiding false detection during power-up. Upon detecting a short-circuit event—defined by the differential voltage between CS+ and ISCP exceeding 50 mV (typ)—the device pulls HGATE to OUT within 2 μ s, quickly turning off the HFET to limit stress. Concurrently, the FLT pin asserts low to flag the fault condition. The device enters a latched-off state, keeping Q2 off until a low-to-high transition is applied to the EN, SLEEP, or VS pins.

Short circuit protection threshold can be increased or decreased from the default 50mV threshold by using an external series resistor R_{SET} from CS+ pin or R_{ISCP} from ISCP pin as shown in Figure 4. The R_{SET} resistor shifts the threshold in positive direction while R_{ISCP} resistor shifts the threshold in negative direction. The shift in the short circuit protection threshold can be calculated using Equation 1.

$$V_{DS_SNS} = 50\text{mV} + (11\mu\text{A} \times R_{SET}) - (11\mu\text{A} \times R_{ISCP}) \quad (1)$$

Here, once V_{DS_SNS} is decided, the short-circuit current threshold also depends on the R_{DSon} of the FET.

$$I_{SCP} = \frac{V_{DS_SNS}}{R_{DSon}} \quad (2)$$

Equation 2 states the short-circuit current threshold.

Since Equation 2 is dependent on the R_{DSon} of the FET, the MOSFET characteristics are important.

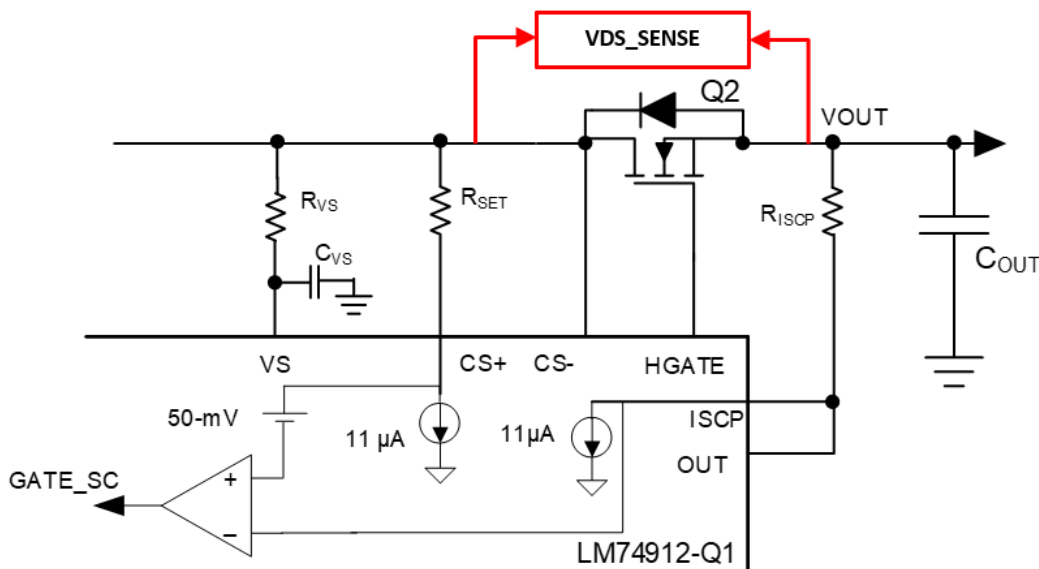


Figure 4. Short Circuit Protection Comparator

MOSFET Dependency

Power MOSFET datasheets have a specification called temperature coefficient 'α' that is used to describe the relationship between R_{DSon} and junction temperature T_J . The drain-source on-state resistance R_{DSon} of MOSFET mostly has a positive temperature coefficient in the normal operation condition, that contributes to the balanced current distribution over the complete area of the die. With a positive coefficient, the hottest spot at a die shows a higher resistance and would tend to conduct less currents, leading to lower temperature in that area. This mechanism creates an effective negative feedback and finally lead to the current balance of the MOSFET.

$$R_{DSon}(T_J) = R_{DSon}(25^\circ\text{C}) \times [1 + \alpha \times (T_J - 25^\circ\text{C})] \quad (3)$$

From the data sheet of BUK7Y4R8-60E, the temperature coefficient α has been given to describe the relationship between R_{DSon} and junction temperature T_J . It indicates the R_{DSon} temperature stability, i.e. the degree to which the R_{DSon} is affected by T_J . The greater the α, the greater the R_{DSon} is affected by temperature. The resistance of the MOSFET changes according to [Equation 3](#).

Resistance at different temperatures can be found out using [Equation 3](#) and information from data sheets for alpha. An example relation is shown in [Figure 5](#).

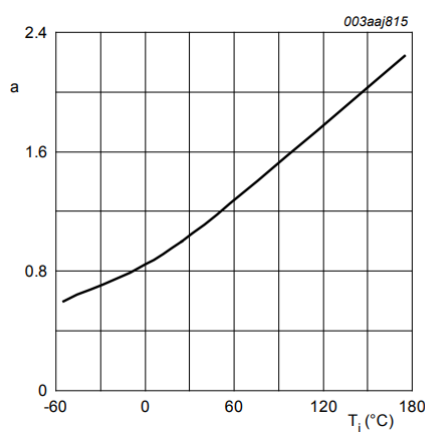


Figure 5. Temperature Coefficient Variation of BUK7Y4R8-60E MOSFET with Temperature

[Figure 5](#) shows that the FET R_{DSon} varies approximately by a factor of 2.5 from -40°C to 125°C, which affects the desired response of the controller when used in stringent conditions which is very likely in automotive use cases. With this, the short circuit protection can vary widely as listed in [Table 2](#). This leads to over-scaling the design in terms of connector sizes, denser copper boards and higher current capability layouts to accommodate the higher current flow and hence increasing the design cost and size.

Reducing Threshold Variability for Safer Short Circuit Protection

Since the temperature change causes high variation in R_{DSon} and causes deviation in short circuit current threshold, a negative temperature coefficient resistor is added close to the FET such that similar temperature variation is seen on NTC (negative temperature coefficient) and FET. This R_{NTC} must be connected parallel to the R_{ISCP} resistor as shown in [Figure 6](#) to create an offset voltage when paired with the internal current source of the controller to the varied R_{DSon} . Based on temperature of the MOSFET, variable offset voltage gets added to SCP comparator reference which linearizes the SCP threshold.

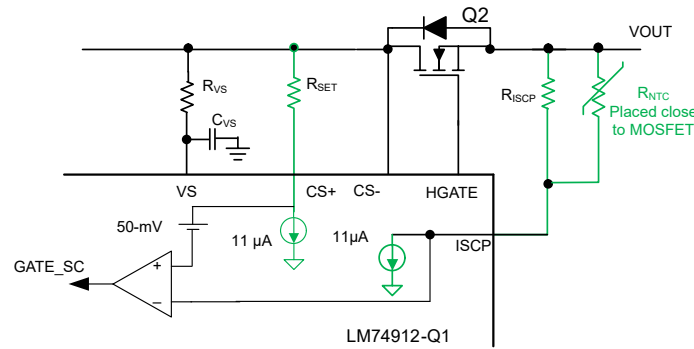


Figure 6. Typical Application Diagram with NTC Addition

Working Principle

The short-circuit current threshold is as shown in Equation 6.

$$\frac{V_{DS_{SNS}}}{R_{DSon}} = \frac{[50\text{mV} + (11\mu\text{A} \times R_{SET}) - (11\mu\text{A} \times R_{ISCP} || R_{NTC})]}{R_{DSon}} \quad (4)$$

At high temperature (125C), R_{NTC} is low impedance compared to R_{ISCP} and approximately shorts the R_{ISCP} resistor. Hence the current source does not create an offset. Only parameter to decide the short-circuit current threshold is R_{SET} .

$$ISCP@125C = 50\text{mV} + 11\mu\text{A} \times \frac{R_{SET}}{R_{DSon}@125C} \quad (5)$$

$$ISCP@-40C = 50\text{mV} + 11\mu\text{A} \times \frac{R_{SET} - R_{ISCP}}{R_{DSon}@-40C} \quad (6)$$

At low temperature (-40C), R_{NTC} is high impedance compared to R_{ISCP} and has very minor effect on the system thresholds and the offset is primarily decided by R_{SET} and R_{ISCP} .

Example Design

For a design which requires 15A short circuit protection threshold, the flow of components selection must be as follows.

Selected MOSFET: BUK7Y4R8-60E, R_{NTC} : NCU18XH103E60RB

Target short circuit protection threshold: 15A

Table 1 shows the variation of MOSFET and R_{NTC} with temperature which is important to calculate the desired values of the components.

Table 1. FET R_{DSon} and R_{NTC} Variation with Temperature

Temperature (C)	BUK7Y4R8-60E	NCU18XH103E60RB
	R_{DSon} (mΩ)	NTC Resistance, kΩ
-40	1.885	200
0	2.61	28
25	2.9	10
50	3.48	4
100	4.64	1
125	5.365	0.5

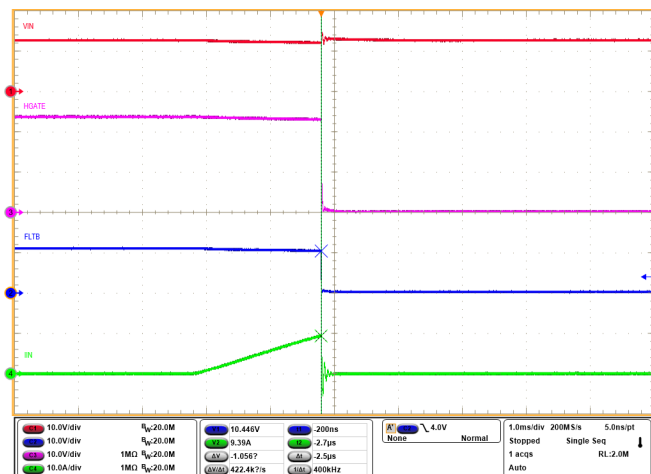


Figure 9. Overload Protection Without RNTC at 100°C

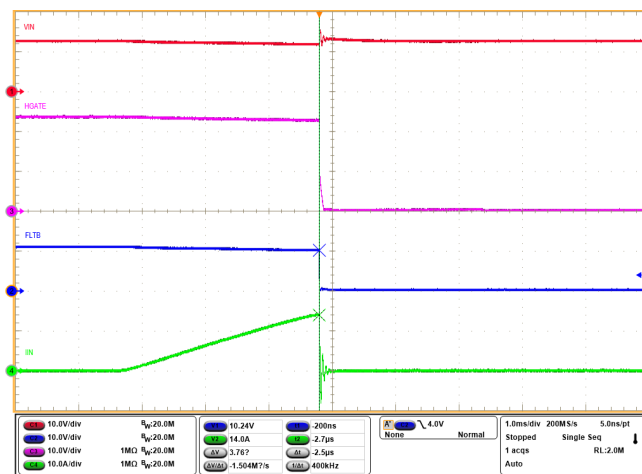


Figure 10. Overload Protection With RNTC at 100°C

Figure 11 shows the theoretical deviation in the thresholds with two different schemes.

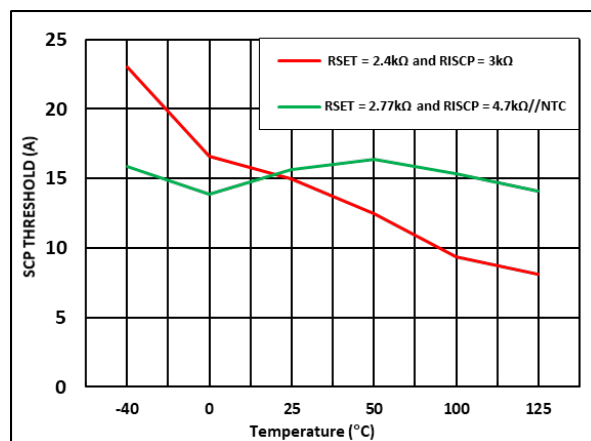


Figure 11. Comparison of SCP Threshold With and Without R_{NTC}

Summary

The R_{DSon} of a MOSFET increases with temperature due to the construction fundamental and impacts system protection when R_{DSon} is used for system level decisions. The positive temperature coefficient of the FET can be compensated with negative temperature coefficient resistor to maintain a stable short circuit current threshold. The proposed approach in this article helps to reduce the variation from approximately 184% to approximately 15.1%.

References

- Texas Instruments, [LM74912-Q1 data sheet, product information and support | TI.com](#), product folder.
- Texas Instruments, [LM74900-Q1 data sheet, product information and support | TI.com](#), product folder.
- Texas Instruments, [What's not in the power MOSFET data sheet, part 1: temperature dependency](#), technical article.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2025, Texas Instruments Incorporated