

Application Note

FAQs on UCC25661x



Sougata Nayak

ABSTRACT

This application note discusses the most frequently asked questions of the UCC25661x LLC resonant controller when used in different applications.

Table of Contents

1 UCC25661x Frequently Asked Questions	2
1.1 How to Connect External Gate Drivers to the UCC25661x for High Gate Driver Current Capability?.....	2
1.2 Up To What Switching Frequency Controller Can Operate?.....	2
1.3 While Operating UCC25661x, 1 Second Fault is Coming. How to Debug it?.....	2
1.4 How to Implement A Battery Charger with UCC25661x?.....	4
1.5 How to Set Up OVP/OTP Pin?.....	8
1.6 How to Set Up The TSET Pin in UCC25661x Family?.....	9
1.7 How to Avoid FB Pin Saturation? How to Detect it?.....	9
1.8 Can the Device Sustain Damage if the HV Pin Current Goes Beyond What is Mentioned in the Datasheet?.....	10
1.9 How does TON extension work in UCC25661?.....	10
1.10 How ZCS Protection Works in UCC25661x?.....	12
1.11 How does Adaptive Deadtime Work?.....	12
1.12 How is the Dead Time in UCC25661x Determined During ZCS Detection and in the Absence of Valid Slew Rate Detection?.....	13
1.13 How to Test UCC25661 Without Applying High DC Voltage in Input of the Converter?.....	13
1.14 How to Connect GaN With UCC25661x?.....	14
1.15 How Much Maximum LL, TSET and ISNS Pin Decoupling Capacitors Must Be Used?.....	14
1.16 How Can Burst Mode Programming Be Changed While Running the Controller?.....	14
1.17 Summary.....	15
1.18 References.....	15

Trademarks

All trademarks are the property of their respective owners.

1 UCC25661x Frequently Asked Questions

1.1 How to Connect External Gate Drivers to the UCC25661x for High Gate Driver Current Capability?

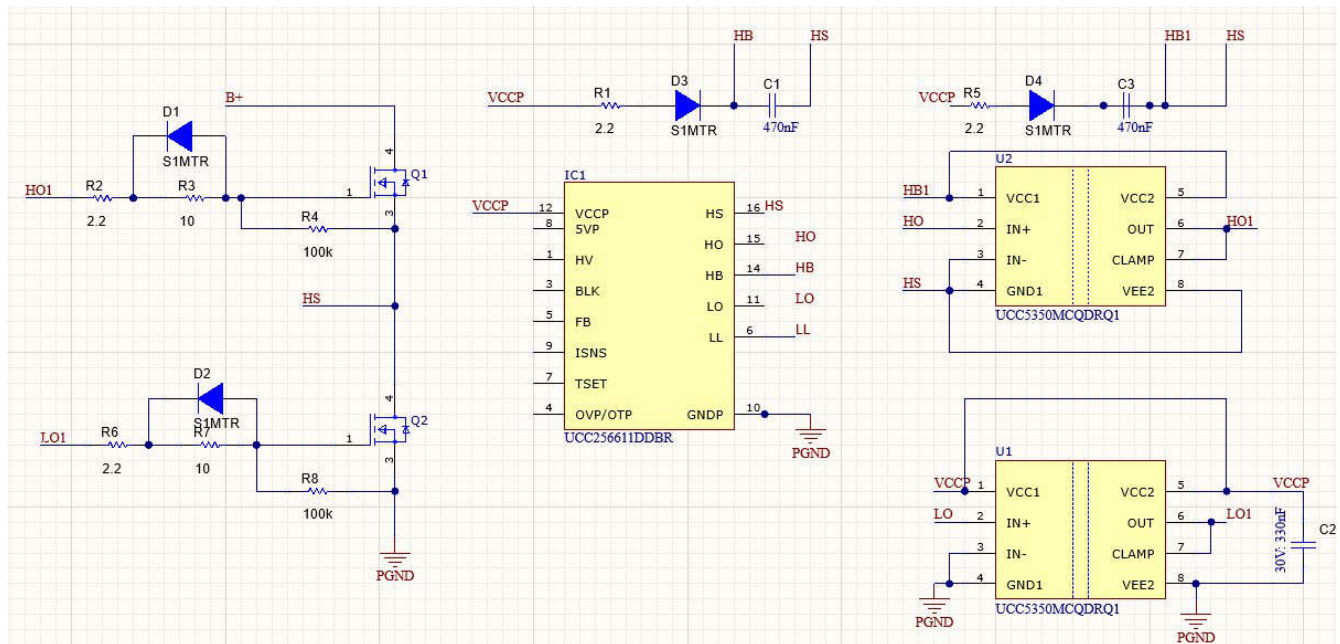


Figure 1-1. External Driver Interface with UCC25661x

Figure 1-1 shows a simpler way of connecting external gate drivers to the UCC25661x. Here two drivers such as UCC5350MCQDRQ1 are used which has a higher output current capability. Here the external high side driver is bootstrapped just like the internal driver of the UCC25661x.

1.2 Up To What Switching Frequency Controller Can Operate?

UCC25661x family can operate up to a 750kHz switching frequency.

1.3 While Operating UCC25661x, 1 Second Fault is Coming. How to Debug it?

If the controller is giving LO pulses and then there is no pulse from the controller side and the controller is retrying after 1 sec, this is due to either the OCP fault or OLP fault. For OCP fault detection, the voltage across the ISNS pin and PGND has to be probed. If the peak voltage at the ISNS pin touches the threshold of 3.5V, it is the OCP fault. To avoid OCP fault, R_{ISNS} must be reduced gradually, and TSET resistor divider must be adjusted accordingly by the design calculator to accommodate P_{in} vs VFBReplica graph within 2V-4V for no load to full load variation.

For OLP fault detection, FBReplica vs Pin graph has to be fitted one first prototype. The procedure to measure FBReplica in practical hardware is as follows:

1. Measure FBReplica voltage by inserting 5k resistor between feedback optocoupler emitter and ground as shown in Figure 1-2. The calculation can be done by Equation 1 .

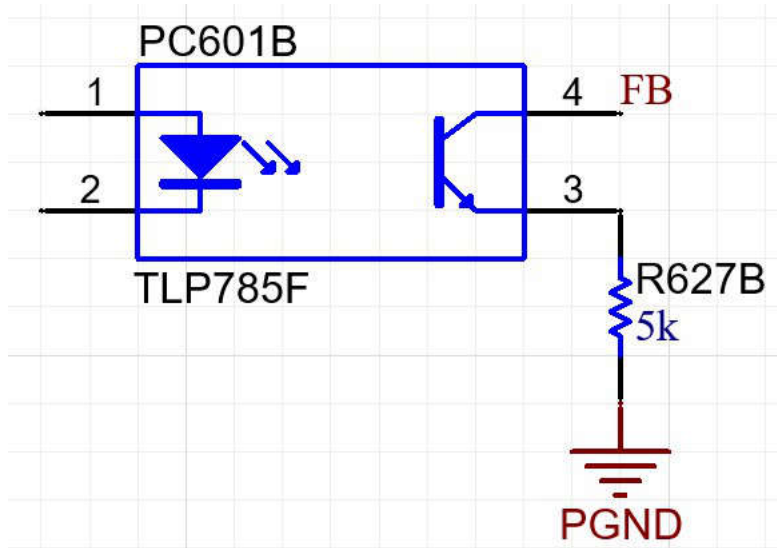


Figure 1-2. FB Replica Measurement Circuit

$$FB_{\text{Replica}} = \left(I_{FB} - \frac{V_{5k}}{5k} \right) \times R_{FB_{\text{Internal}}} \quad (1)$$

- Plot FB Replica voltage vs Pin graph at different input power up to considering peak output power, not just up to full load output power, as shown in Figure 1-3.

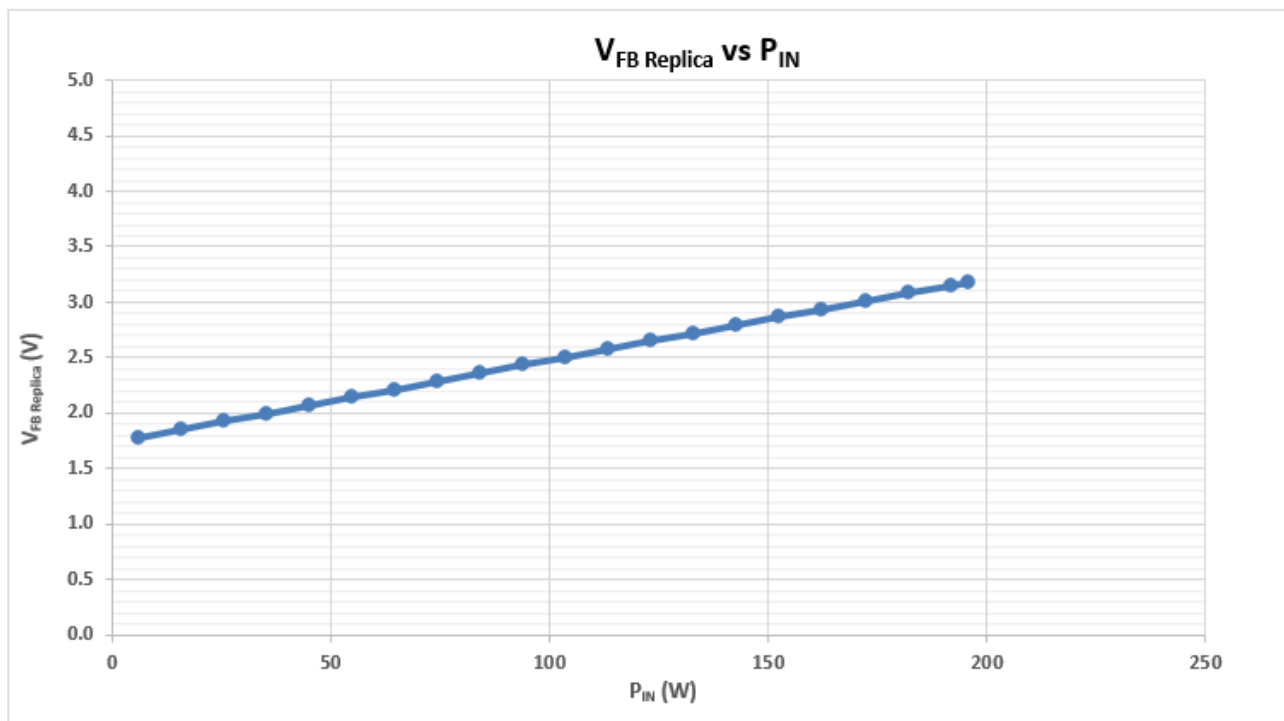


Figure 1-3. VFB Replica vs Pin Graph

If at any load, FB Replica touches 4.75V, then the fault at that load is OLP.

1.4 How to Implement A Battery Charger with UCC25661x?

The battery chargers exhibit different effective output resistance variation with the change in output voltages. In case of battery chargers, the effective output resistance increases with the output voltage whereas in case of LED drivers, the voltage can be reduced. When LLC is designed in these applications, we need to make sure required voltage gains are met.

The LLC tank parameters and the turns ratio are chosen based on the $V_{in_typ} = 390V$ (350V-410V) , $V_{out_typ} = 58.7V$ (V_{out_min} 46.2V- V_{out_max} 71.2V),

Battery charging current = 7A , $f_{res} = 100kHz$. Three Excel calculators must be made with typical, maximum, and minimum V_{out} with the same tank circuit. Make sure that $M_g(min)$, $M_g(max)$ lines meet with the LLC gain curve with a good margin (peak gain of LLC gain curve is at least 10-15% higher than $M_g(max)$ at V_{out_Max} . The minimum gain goes below 90% of $M_g(min)$) as shown in Figure 1-4, Figure 1-5, and Figure 1-6

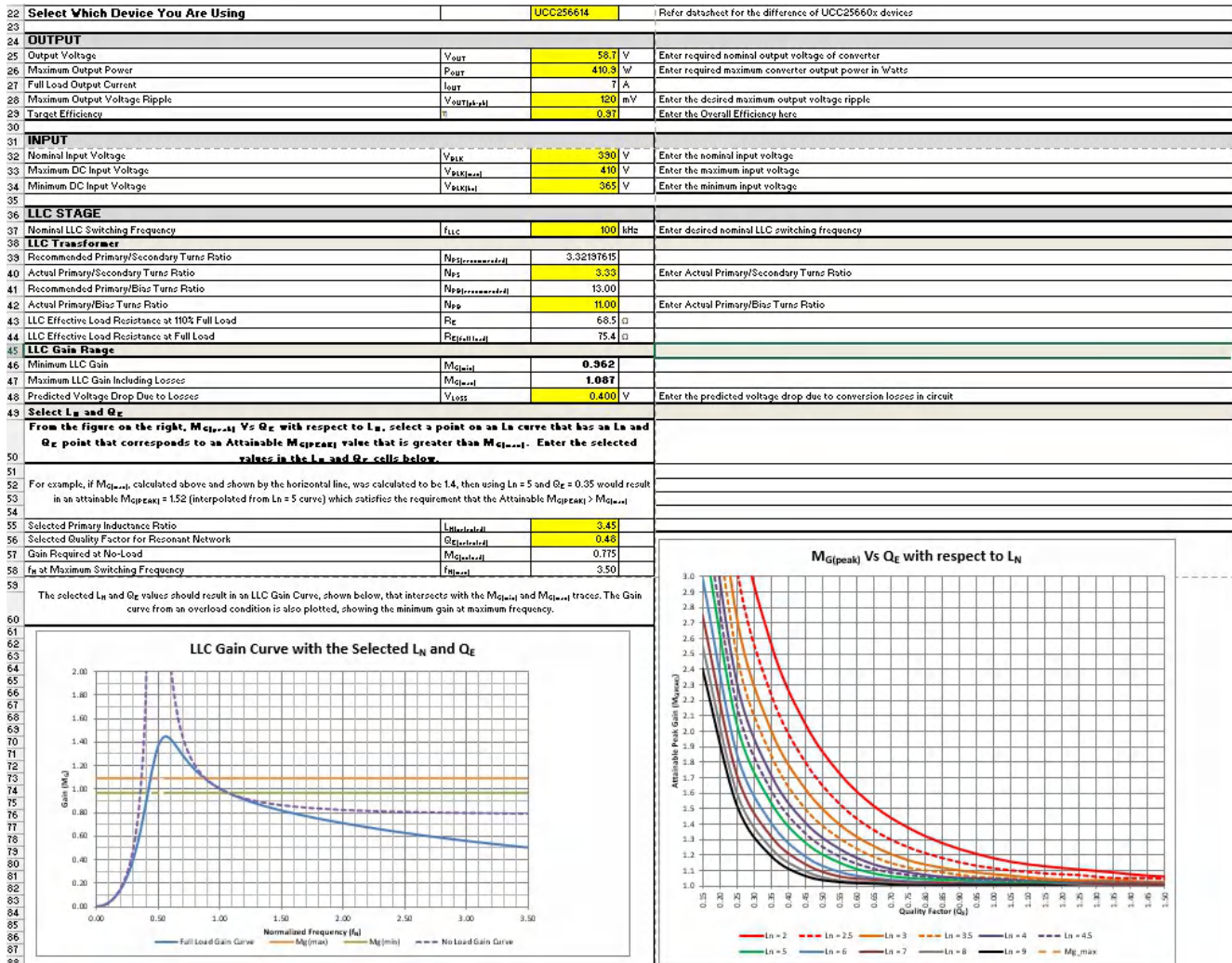


Figure 1-4. Design Calculator for Nominal Output Voltage

22	Select Which Device You Are Using	UCC256614	Refer datasheet for the difference of UCC25660x devices	
23	OUTPUT			
25	Output Voltage	V_{OUT}	71.2 V	Enter required nominal output voltage of converter
26	Maximum Output Power	P_{OUT}	436.4 W	Enter required maximum converter output power in Watts
27	Full Load Output Current	I_{OUT}	7 A	
28	Maximum Output Voltage Ripple	$V_{OUT(ripple)}$	120 mV	Enter the desired maximum output voltage ripple
29	Target Efficiency	η	0.91	Enter the Overall Efficiency here
30	INPUT			
32	Nominal Input Voltage	V_{IN}	390 V	Enter the nominal input voltage
33	Maximum DC Input Voltage	$V_{IN(max)}$	410 V	Enter the maximum input voltage
34	Minimum DC Input Voltage	$V_{IN(min)}$	365 V	Enter the minimum input voltage
35	LLC STAGE			
36	Nominal LLC Switching Frequency	f_{LLC}	100 kHz	Enter desired nominal LLC switching frequency
37	LLC Transformer			
38	Recommended Primary/Secondary Turns Ratio	$N_{PS(Recommended)}$	2.738764045	
40	Actual Primary/Secondary Turns Ratio	N_{PS}	3.33	Enter Actual Primary/Secondary Turns Ratio
41	Recommended Primary/Bias Turns Ratio	$N_{PB(Recommended)}$	13.00	
42	Actual Primary/Bias Turns Ratio	N_{PB}	11.00	Enter Actual Primary/Bias Turns Ratio
43	LLC Effective Load Resistance at 100% Full Load	R_E	83.1 <input type="checkbox"/>	
44	LLC Effective Load Resistance at Full Load	$R_E(FullLoad)$	31.4 <input type="checkbox"/>	
45	LLC Gain Range			
46	Minimum LLC Gain	$M_{G(min)}$	1.165	
47	Maximum LLC Gain Including Losses	$M_{G(max)}$	1.316	
48	Predicted Voltage Drop Due to Losses	V_{LOSS}	0.400 V	Enter the predicted voltage drop due to conversion losses in circuit
49	Select L_N and Q_E			
50	From the figure on the right, $M_{G(max)}$ Vs Q_E with respect to L_N , select a point on an L_N curve that has an L_N and Q_E point that corresponds to an Attainable $M_{G(peak)}$ value that is greater than $M_{G(max)}$. Enter the selected values in the L_N and Q_E cells below.			
51				
52	For example, if $M_{G(max)}$ calculated above and shown by the horizontal line, was calculated to be 1.4, then using $L_N = 5$ and $Q_E = 0.35$ would result in an attainable $M_{G(peak)}$ = 1.52 (interpolated from $L_N = 5$ curve) which satisfies the requirement that the Attainable $M_{G(peak)}$ > $M_{G(max)}$.			
53				
54				
55	Selected Primary Inductance Ratio	$L_{N(selected)}$	3.45	
56	Selected Quality Factor for Resonant Network	$Q_E(selected)$	0.40	
57	Gain Required at No-Load	$M_{G(no-load)}$	0.775	
58	f_R at Maximum Switching Frequency	$f_{R(max)}$	3.50	
59	The selected L_N and Q_E values should result in an LLC Gain Curve, shown below, that intersects with the $M_{G(max)}$ and $M_{G(no-load)}$ traces. The Gain curve from an overload condition is also plotted, showing the minimum gain at maximum frequency.			
60				
61				
62				
63				
64				
65				
66				
67				
68				
69				
70				
71				
72				
73				
74				
75				
76				
77				
78				
79				
80				
81				
82				
83				
84				
85				
86				
87				
88				
89				
90				

Figure 1-5. Design Calculator at Maximum Output Voltage

2 Select Which Device You Are Using		UCC256614	Refer datasheet for the difference of UCC25660x devices
3 OUTPUT			
4 Output Voltage	V_{OUT}	46.2 V	Enter required nominal output voltage of converter
5 Maximum Output Power	P_{OUT}	323.4 W	Enter required maximum converter output power in W/atts
6 Full Load Output Current	I_{OUT}	7 A	
7 Maximum Output Voltage Ripple	$V_{OUT(ripple)}$	120 mV	Enter the desired maximum output voltage ripple
8 Target Efficiency	η	0.37	Enter the Overall Efficiency here
9 INPUT			
1 Nominal Input Voltage	V_{IN}	390 V	Enter the nominal input voltage
2 Maximum DC Input Voltage	$V_{IN(max)}$	410 V	Enter the maximum input voltage
3 Minimum DC Input Voltage	$V_{IN(min)}$	365 V	Enter the minimum input voltage
4 LLC STAGE			
5 Nominal LLC Switching Frequency	f_{LLC}	100 kHz	Enter desired nominal LLC switching frequency
6 LLC Transformer			
7 Recommended Primary/Secondary Turns Ratio	$N_{PS(recommended)}$	4.220713221	
8 Actual Primary/Secondary Turns Ratio	N_{PS}	3.33	Enter Actual Primary/Secondary Turns Ratio
9 Recommended Primary/Bias Turns Ratio	$N_{PB(recommended)}$	13.00	
10 Actual Primary/Bias Turns Ratio	N_{PB}	11.00	Enter Actual Primary/Bias Turns Ratio
11 LLC Effective Load Resistance at 110% Full Load	R_L	53.3 Ω	
12 LLC Effective Load Resistance at Full Load	$R_L(full\ load)$	58.3 Ω	
13 LLC Gain Range			
14 Minimum LLC Gain	$M_{G(min)}$	0.753	
15 Maximum LLC Gain Including Losses	$M_{G(max)}$	0.853	
16 Predicted Voltage Drop Due to Losses	V_{LOSS}	0.400 V	Enter the predicted voltage drop due to conversion losses in circuit
17 Select L_N and Q_L			
18 From the figure on the right, $M_{G(peak)}$ Vs Q_L with respect to L_N , select a point on an L_N curve that has an L_N and Q_L point that corresponds to an Attainable $M_{G(peak)}$ value that is greater than $M_{G(max)}$. Enter the selected values in the L_N and Q_L cells below.			
19 For example, if $M_{G(max)}$ calculated above and shown by the horizontal line, was calculated to be 1.4, then using $L_N = 5$ and $Q_L = 0.35$ would result in an attainable $M_{G(peak)} = 1.52$ (interpolated from $L_N = 5$ curve) which satisfies the requirement that the Attainable $M_{G(peak)} > M_{G(max)}$.			
20			
21			
22			
100			

Figure 1-6. Design Calculator at Minimum Output Voltage

Battery chargers must operate in either constant current mode (CC) or constant voltage (CV), depending on the charging status of the battery and effective load resistance. Effective load resistance determines the operating point of the CC-CV controlled power supply.

Figure 1-7 shows an example of how CC-CV loop is implemented.

*

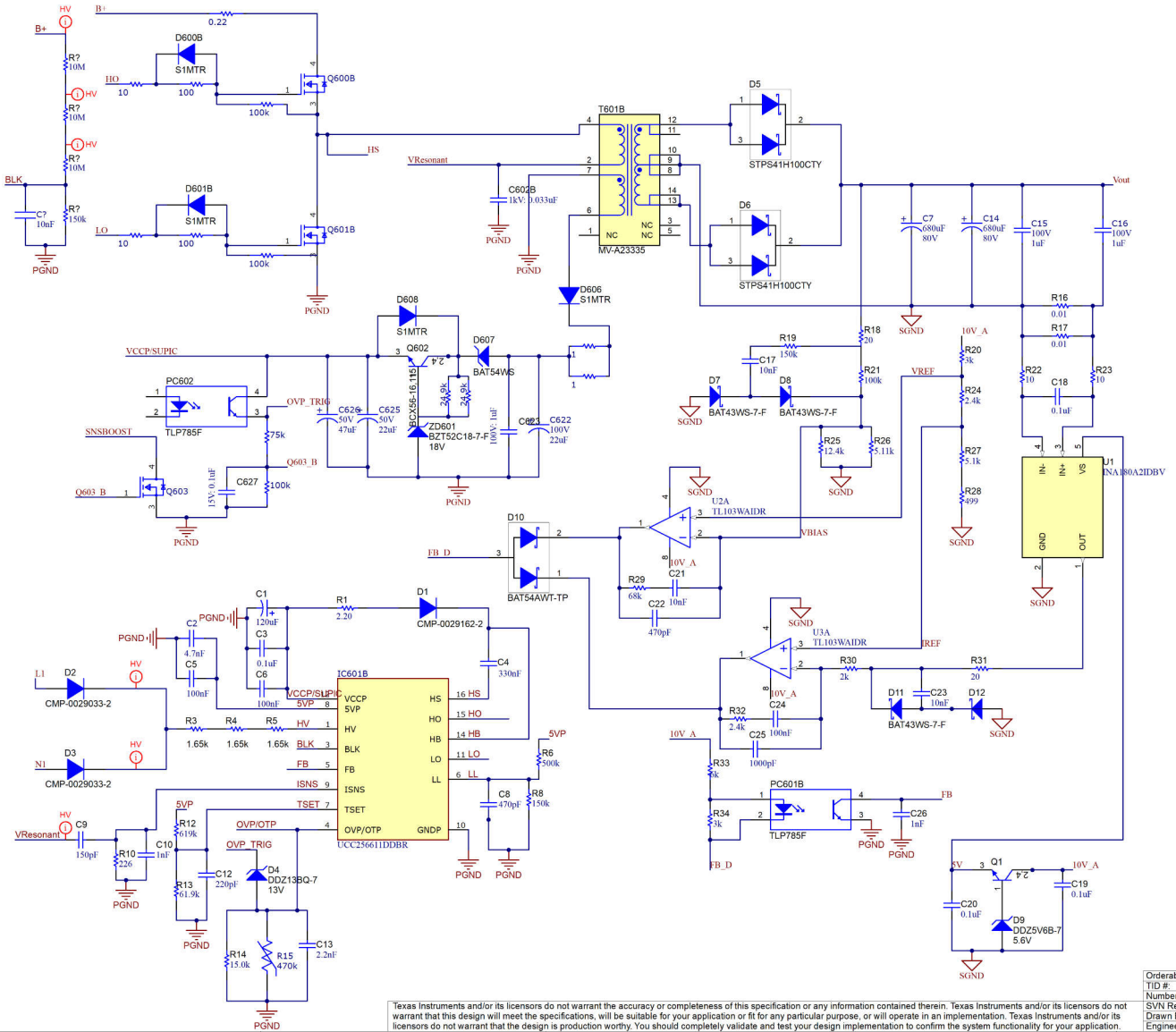


Figure 1-7. CC-CV Control Loop Circuit With UCC25661x

Orderable
 TID #:
 Number:
 SVN Rev:
 Drawn By:
 Engineer:

1.5 How to Set Up OVP/OTP Pin?

UCC25661x family uses a multi-function pin (OVP/OTP) that monitors for output overvoltage and external over-temperature conditions. To operate the controller in normal condition, the OVP/OTP pin voltage should be in between $VOVP_{Pos}$ and $VOTP_{Neg}$. Normally, The OVP/OTP pin voltage is $I_{OTP} * NTC$ resistance. If Temperature is very high, NTC resistance becomes very less. Thus, OVP/OTP pin voltage becomes less than $VOTP_{Neg}$, IC will give OTP Fault.

If the output voltage of the LLC converter becomes high enough that VCCP becomes high and Zener diode in OVP/OTP pin starts conducting, then total current through NTC resistors become (Zener diode current + I_{OTP}). Therefore, the voltage at the OVP/OTP pin starts rising. If the voltage is over $VOVP_{Pos}$, IC gives OVP fault.

While designing a circuit using $VOVP_{Pos}$ and $VOTP_{Neg}$, the OVP and OTP comparator hysteresis values must be considered.

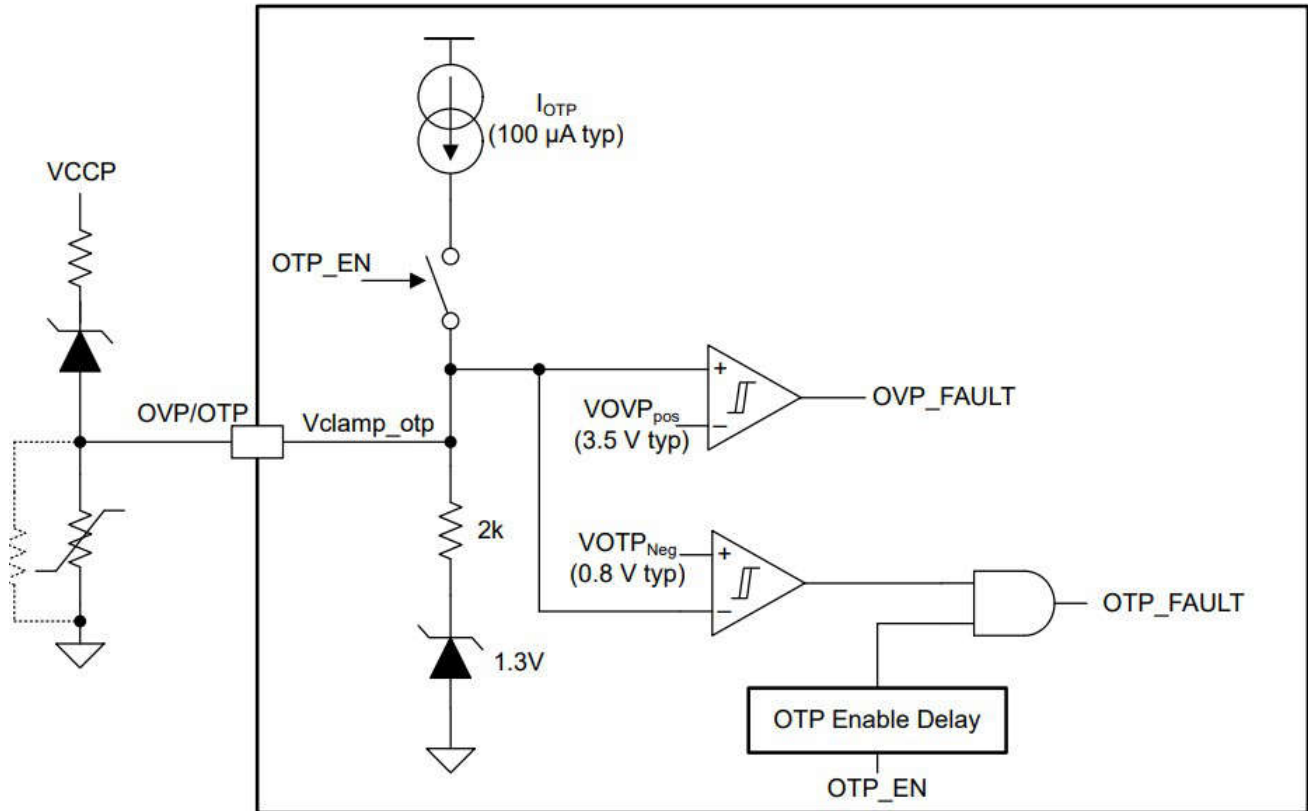


Figure 1-8. OVP/OTP Pin Architecture

1.6 How to Set Up The TSET Pin in UCC25661x Family?

At the startup of the controller, TSETA and TSETB voltages are programmed. V_{TSETB} voltage configures the minimum frequency for IPPC operation and the maximum dead time. Whereas, $(V_{TSETA} - V_{TSETB})$ configures the integrator time constants that help to set the FBReplica magnitude for a given power output. So, while selecting TSET, first check what is the minimum switching frequency of the converter at full load and select a TSET option from the TSET table so that the minimum switching frequency at that TSET option is less than the minimum switching frequency. After that, select another TSET option which sets the VCR synthesizer integrator time constants to make sure that Vfbreplica vs Pin graph remains in between 2 (At slight load) to 4V(at peak load). If Vfbreplica touches 4.5V, the controller hits overload protection (OLP) and conducts the overload current for 100ms and after that it goes to 1sec fault.

For example, suppose a converter has a minimum operating frequency of 350kHz, so a user can select any TSET option between one to 12 for TSETB. Then, suppose, upon checking Pin vs VfbReplica graph in the design calculator, the user can select any TSET option between seven to nine to make VfbReplica vs Pin graph within two to four . Then, for this case, the TSET option with higher integrator time constant is preferable (for example, TSET option seven). The reason is with the reduction in integrator time constant, the bandwidth of the system increases. Thus, with a large load transient, resonant current as well as ISNS voltage can rise more than OCP threshold level (3.5V) for some of the cycles momentarily and can reach a false OCP level. [Figure 1-9](#) shows a snapshot from the design calculator for TSET selection in the previous example.

 


Figure 1-9. TSET Option Selection in Design Calculator

1.7 How to Avoid FB Pin Saturation? How to Detect it?

The FB pin of UCC25661x is current source driven. Thus, the FB pin voltage is normally constant (3.5V typically). If we want to check if the FB pin voltage is saturated or not, FB pin voltage must be checked. If the FB pin voltage drops below 3V, it indicates that the opto-coupler associated to the FB pin got saturated. If FB pin saturates, the transient response of the converter suffers. Avoid this by using the following circuit, adding a 1.5V Zener (D100) and 2.22k resistor (R100) between the V5P pin and the FB pin, as shown in [Figure 1-10](#).

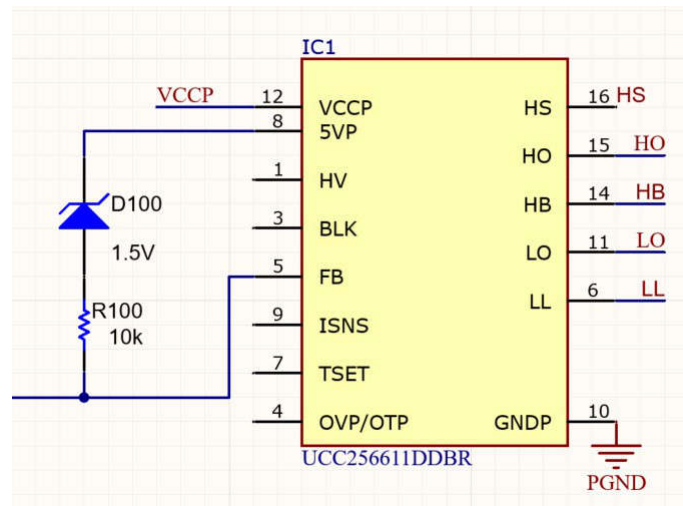


Figure 1-10. Circuit Implementation to Keep FB Pin Out of Saturation

1.8 Can the Device Sustain Damage if the HV Pin Current Goes Beyond What is Mentioned in the Datasheet?

The HV current is internally clamped to maximum 13.8mA. HV current cannot go beyond that. 1k-5k ohm HV resistors are recommended in the HV pin. If resistance in HV pin is increased too much, voltage drop across the resistor is higher and limits the minimum input voltage from where the IC can operate.

1.9 How does TON extension work in UCC25661?

During start-up and for the first few switching cycles, the MOSFET on the primary side can experience body diode reverse recovery and hard switching. The experience is mainly due to the fact that at start-up, the resonant capacitor can have DC bias voltage which is off from the steady state operating voltage of $V_{in}/2$ as shown in [Figure 1-11](#) or zero resonant current at tank at the time of startup, as shown in [Figure 1-12](#). These conditions lead to an asymmetry in the resonant tank current at start-up. In the first few cycles, asymmetry can be high enough that the current at the point of switch turn-off is in the wrong polarity. TON extension avoids the wrong polarity of current using UCC25661x device. [Figure 1-11](#) and [Figure 1-12](#) shows TON extension to fix the wrong polarity of current within early cycles.

 


Figure 1-11. Startup Switching Waveform of UCC25661x

 


Figure 1-12. TON Extension in UCC25661x

1.10 How ZCS Protection Works in UCC25661x?

ZCS typically happens when the LLC operates at heavy load condition and the switching frequency is too low. ZCS detection relies on the resonant current polarity detection (IPolarity). The IPolarity comparator detects the direction of the resonant current. The capacitive region detection is done by checking the resonant current polarity at HSON or LSON falling edge. If the resonant current is positive at LSON falling edge, or negative at HSON falling edge, the ZCS signal in the waveform generator is turned high. When a ZCS event is detected, the internal soft start ramp voltage is slowly reduced. When the internal soft start ramps down, the switching frequency is also forced to increase, forcing the converter out of capacitive region. In the event of a persistent ZCS condition for a period of 10ms, the UCC25661x family controller ceases switching and move to the fault state.

When operation nears the inductive/capacitive boundary, the resonant current decreases before the gate is turned off. If the ISNS waveform is less than the VISNS_ZCS threshold, the gate pulse HO is terminated early instead of waiting for the VCR waveform to cross the VTH boundary. This early gate termination scheme is capable of leaving enough resonant current at the gate turn-off edge to drive the ZVS transition during the dead-time. Similar explanation holds good for the LO gate pulse.

 


Figure 1-13. ZCS Avoidance Algorithm at ZCS Boundary

1.11 How does Adaptive Deadtime Work?

During the dead time, the HS node slews from one input rail to the other due to the inductive resonant current. To achieve zero voltage switching (ZVS) turn on, the dead time must be long enough for the resonant current to fully charge or discharge the HS node. After the body diode starts conducting, the MOSFET must be turned on quickly. Too long of a turn on delay can result in reverse resonant current and lead to the loss of ZVS. The voltage drop on the body diode is higher than that on the MOSFET channel. Optimized dead time can help to minimize the power loss. The resonant current flowing through the HS node during the dead time depends on the LLC resonant tank design and varies by operating frequency and output/input voltage ratio. Therefore, the optimized dead time varies widely with LLC operating conditions. UCC25661x includes an adaptive dead time control to automatically find the optimized dead time across the entire operating range. The device detects the change of slew rate of the HS node voltage. During a switching transition, the slew rate rises up first and then drops back to zero. A slew rate detector is used to detect the moment when the slew rate drops below a pre-defined threshold. A slew done event is only detected when the slew rate during dead time crosses the threshold and then drops back below the threshold. In burst mode, during a ZCS prevention operation or in power stages where the slew rate can be slow, the resonant tank current polarity signal (IPolarity comparator output) is used to augment the slew rate detector. Taking advantage of the natural symmetric operation of LLC,

the slew rate detector determines only the dead time between high-side switch turn off and low-side switch turn on. This dead time is copied and applied to the dead time between low-side MOSFET turn off and high-side MOSFET turn on.

There are a few exceptions where the dead time is not copied

1. Missing slew rate detector signal in the previous High to Low transition,
2. ZCS detection in the previous cycle

Under these conditions, the IPolarity comparator based on the ISNS signal is used to adjust the dead time during low to high transitions.

1.12 How is the Dead Time in UCC25661x Determined During ZCS Detection and in the Absence of Valid Slew Rate Detection?

Case 1: Valid Slew Rate Detection and No ZCS

As soon as the high side gate (HO) is turned off, the low side gate (LO) is turned on after the slew rate is detected. The same dead time is copied over during low side turn off to high side turn on.

Case 2: No Slew Rate Detection and No ZCS

If no valid slew rate detection occurs after the HO turn off, the dead time during both transitions (HO turn off to LO turn on) and (LO turn off to HO turn on) depends on the resonant current polarity. Furthermore, this dead time does not exceed 1us or 0.5us, depending upon TSET settings.

Case 3: ZCS During HO Turn Off and No ZCS during LO Turn Off

If the ZCS is detected during HO turn off, the dead time from HO off to LO on is determined by polarity of the resonant current (IPolarity signal). The maximum dead time here does not exceed 1.1us. The dead time during LO turn off to HO turn on depends on the resonant current polarity. Furthermore, this dead time does not exceed 1.1us.

Case 4: No ZCS During HO Turn Off and ZCS during LO Turn Off

The dead time during HO off to LO on depends on the slew rate detection similar to case1. However, if no valid slew rate detection occurs after the HO turn off, the dead time during HO turn off to LO turn on depends on the resonant current polarity. Furthermore, this dead time does not exceed 1us or 0.5us, depending upon the TSET option. If the ZCS is detected during LO turn off, the time from LO off to HO on is determined by the polarity of the resonant current (ISNS signal). The maximum dead time here will not exceed 1.1us.

Case 5: ZCS During Both HO Turn Off and LO Turn Off

If the ZCS is detected during HO turn off, the dead time from HO off to LO on is determined by the polarity of the resonant current (IPolarity signal). The maximum dead time here does not exceed 1.1 us. If the ZCS is detected during LO turn off, the dead time from LO off to HO on is determined by the polarity of the resonant current (IPolarity signal). The maximum dead time here does not exceed 1.1us.

1.13 How to Test UCC25661 Without Applying High DC Voltage in Input of the Converter?

15V has to be applied to Vcc pin from an external DC source. 1.5V has to be applied at the BLK pin. LO and HS pin must be probed to check low side FET gate-source voltage and switch node voltage. In this condition, some LO pulses should come. Then, slowly increase the DC input voltage to 20V and in steps to 50V and check LO pulses and switch node. If this is correct, the BLK pin of the UCC25661 can be powered by input voltage and BLK resistors and high voltage can be applied at the input side of the converter.

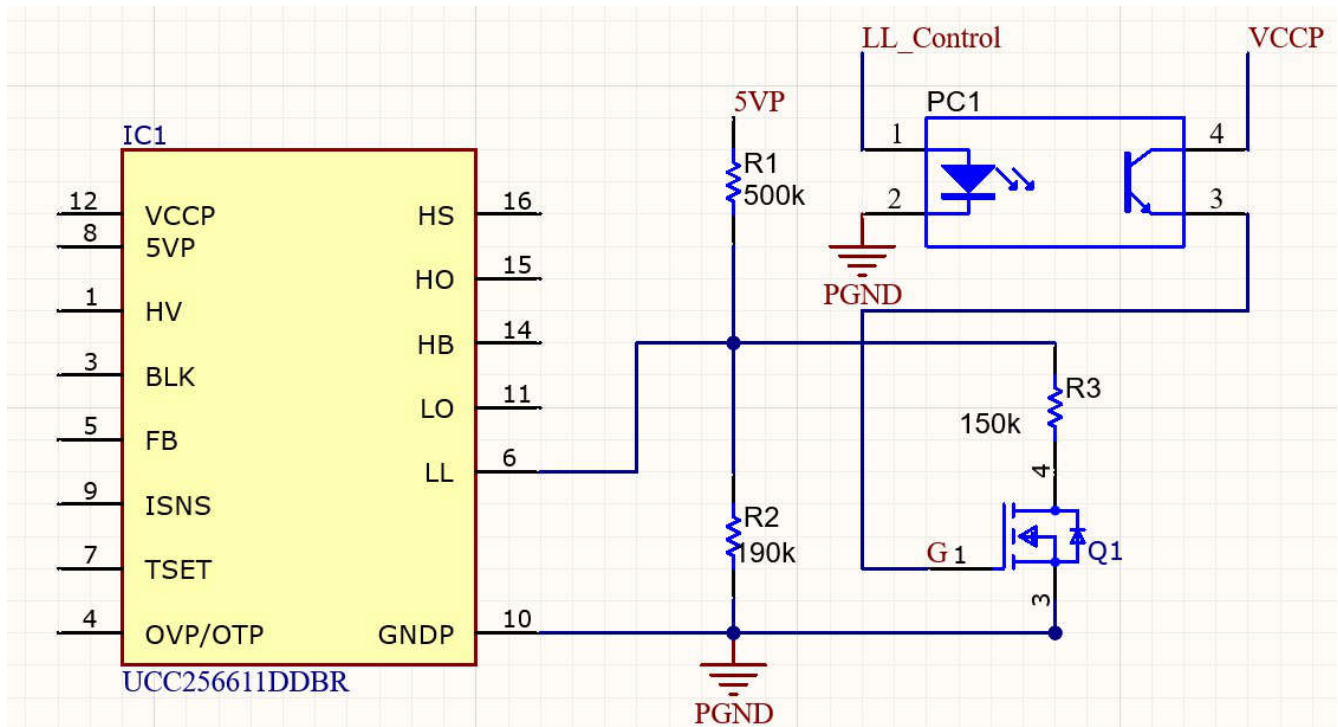


Figure 1-15. Dynamic LL Pin Circuit Diagram in UCC25661x

1.17 Summary

UCC25661x is an analog LLC controller that can switch up to 750kHz in normal conditions which allows it to integrate with GaN. The controller is configured according to the user. UCC256610 and UCC256614 variants within this family are capable of supporting wide input LLC applications.

1.18 References

1. Texas Instruments, [UCC25661](#), product page.
2. Texas Instruments, [UCC25661-Q1](#), product page.
3. Texas Instruments, [UCC25661x Design Calculator](#), design calculator.
4. Texas Instruments, [UCC25661EVM-128](#), EVM.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025