

Using References to Generate Offsets for the TLC55XX Family Data Converter

Robert McCarthy
Mixed Signal Products

ABSTRACT

This application report describes the process for using references to generate offsets for Texas Instrument's TLC55XX family data converters.

Contents

Description	1
High-Speed Converters	1
Biasing Techniques for a Split Supply	2
Biasing Techniques for a Single Supply	3
180 Degree Phase Shift	4
Power Supply and Layout Consideration	5

List of Figures

1 High-Speed Converter Basic Circuit	2
2 Example With Split Supply	3
3 Example With Single Supply	3
4 Circuit With a 180 Degree Phase Shift	4

Description

One common problem when interfacing to modern single supply A/D converters is biasing the analog input so that it is centered within the reference voltage range of the A/D. For the more common SAR type data converters it is often sufficient to set Vref top to V_{CC} and Vref bottom to GND. Then, biasing the midscale voltage of the input stage is simply a matter of generating $1/2V_{CC}$. This can be accomplished with a resistor divider network or, if more line/load stability is needed, by using the TLE2425 virtual ground or the TLE2426 rail splitter.

High-Speed Converters

Some high-speed converters such as the TLC5510, TLC5540, and TLV5580 have internal resistors that can be used to set internal reference voltages. On these devices, reference top (REFT) and reference bottom (REFB) pins are available. Normally, these pins would be used as reference inputs when an external reference is used. In this case we are relying on V_{DDA} and the internal divider to generate the reference voltages and take advantage of their availability. In Figure 1, the two 100 K Ω (R1, R2) resistors from REFT to REFB divide this voltage in half, generating a midpoint value between the top and bottom references. The small loading effect of these resistors only slightly moves the references and these can be taken into account in the DSP or other processor. The values shown for the internal reference divider resistors are the nominal values from the data sheet. Keep in mind that only the ratio of these internal resistors is accurate. The actual value of these internal resistors can vary by as much as 20%.

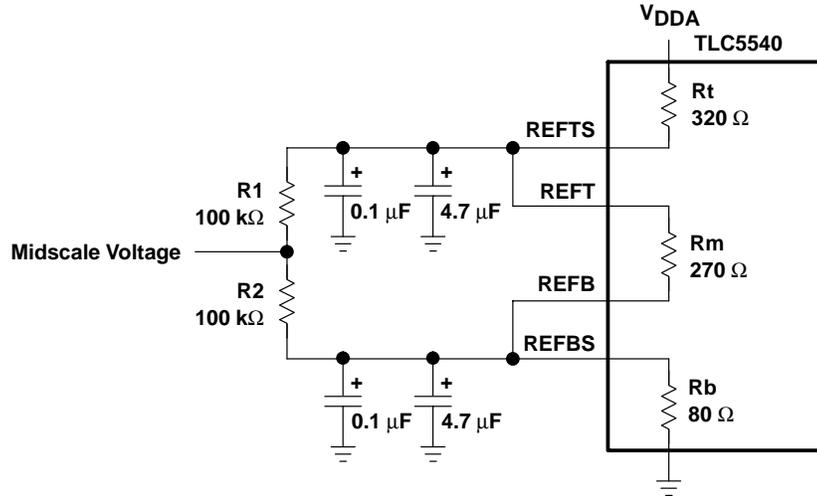


Figure 1. High-Speed Converter Basic Circuit

Figure 1 shows the high-speed converter basic circuit. One definite advantage to this technique is that the midpoint value will track ratiometrically to any variations in V_{DDA} .

$$\text{Midscale Voltage } (V_{\text{ref}}) = V_{\text{Bot}} + (V_{\text{Top}} - V_{\text{Bot}}) \times \frac{R_2}{R_1 + R_2} \quad (1)$$

Where

$$V_{\text{Top}} = V_{\text{DDA}} \times \frac{\left(\frac{R_M \times (R_1 + R_2)}{R_M + R_1 + R_2} \right) + R_B}{R_T + \left(\frac{R_M \times (R_1 + R_2)}{R_M + R_1 + R_2} \right) + R_B} \quad (2)$$

and

$$V_{\text{Bot}} = V_{\text{DDA}} \times \frac{R_B}{R_T + \left(\frac{R_M \times (R_1 + R_2)}{R_M + R_1 + R_2} \right) + R_B} \quad (3)$$

Biasing Techniques for a Split Supply

Armed with this midpoint value, the following biasing techniques can be used with bipolar, dc coupled or ac coupled inputs to prepare them for processing by a single supply converter. The first technique, shown in Figure 2, gives a noninverting gain set by the two resistors R1 and R2.

$$V_o = V_{\text{in}} \left(1 + \frac{R_1}{R_2} \right) + V_{\text{Midscale}} \left(\frac{R_1}{R_2} \right) \quad (4)$$

The midscale voltage is inverted by the op-amp marked TLE2227(B) and a negative version of it is used for the offset. One requirement with this technique is that the amplifiers have a split supply for a bipolar input.

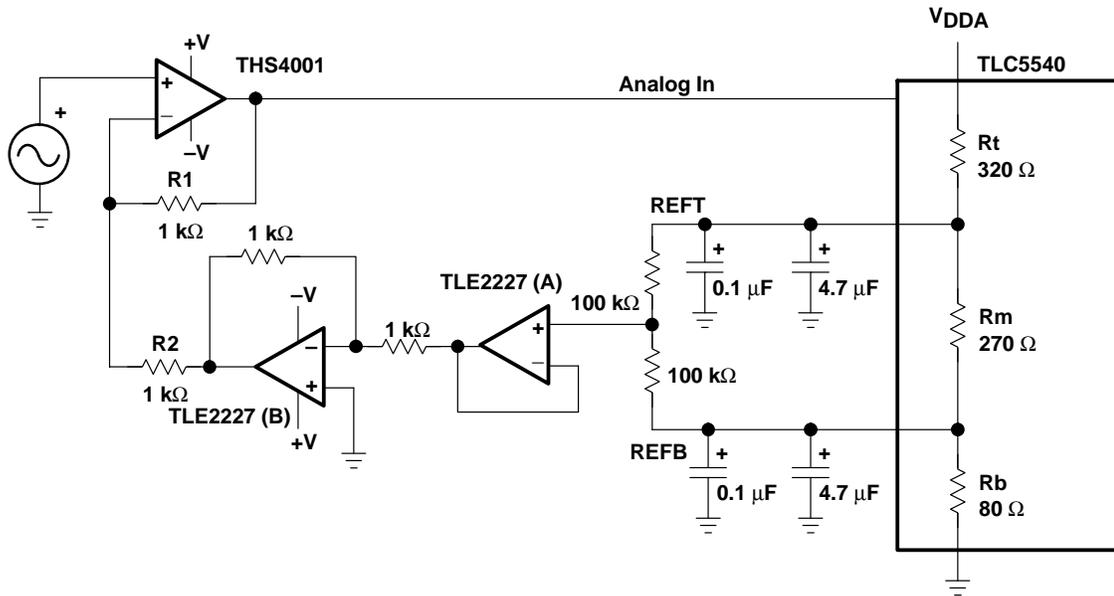


Figure 2. Example With Split Supply

Biasing Techniques for a Single Supply

If it is desired that the entire system operate on a single supply yet still be able to measure bipolar inputs, a slightly different technique is required. Figure 3 shows an example of this technique.

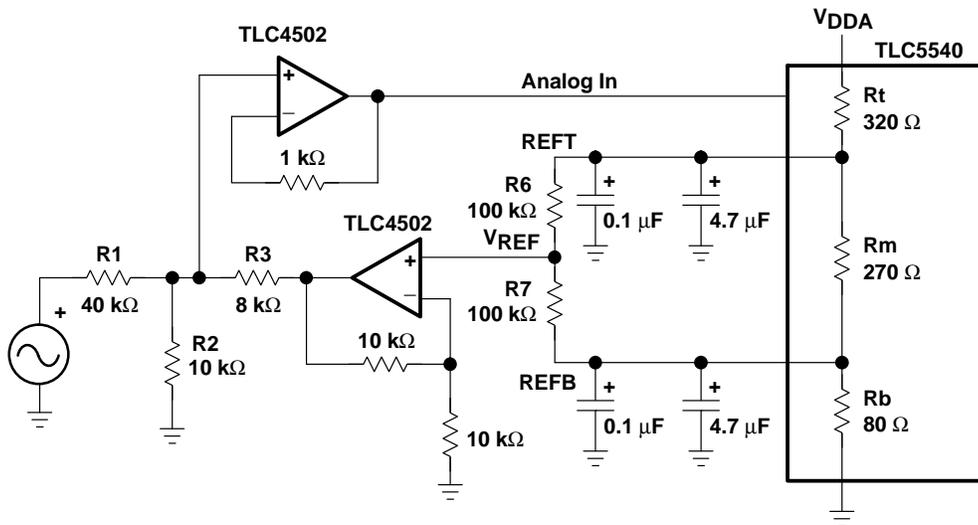


Figure 3. Example With Single Supply

To simplify the analysis of this circuit you can use the principle of superposition. In this case, consider that the incoming bipolar signal is larger than the span of the reference and therefore it needs to be attenuated. Also consider that the signal is centered at zero volts (other possibilities can be easily accounted for by adjusting the dividers). The resistance divider circuit made up of R1 and R2||R3 does the attenuating while the output of op-amp TLC4502 provides the offset needed through the divider network R3 and R1||R2.

As a real world example, consider that the input signal is a ± 10 V signal that needs to be measured. First figure the full-scale span of the data converter which is the voltage at REFT minus the voltage at REFB. Doing math for a 5 V V_{DDA} , the span comes to about 2.01 V with a midpoint half way between 2.61 V and 0.597 V or about 1.6 V.

Now consider 2 V as the span, a 10:1 reduction is needed on the input signal, which means that R1 needs to be nine times the value of $R2||R3$.

In order to supply the midpoint voltage through a buffered source, a gain of 2 is introduced. The gain of 2 is then removed by the resistor divider network R3 and $R1||R2$.

The values arrived at are shown in Figure 3.

$$V_{\text{out}}(\text{Analog in}) = V_{\text{in}} \times \frac{R2||R3}{R1 + R2||R3} + 2 \times V_{\text{ref}} \times \frac{R1||R2}{R3 + R1||R2} \quad (5)$$

Where

$$R2||R3 = \frac{R2 \times R3}{R2 + R3} \quad \text{And} \quad R1||R2 = \frac{R1 \times R2}{R1 + R2} \quad (6)$$

180 Degree Phase Shift

The circuit in Figure 4, introduces a 180 degree phase shift on the signal, but since far fewer resistors are required, it is much easier to meet the accuracy needs of the system. Note that resistors R6 and R7 are now different values. This is because of the amplifying effect of the inverting stage due to dc-coupling. If the calculations are done with these values, it is seen that a zero volt input is centered within the A/D's reference range. If the input is ac-coupled, R6 and R7 must be the same value (i.e., 100 k Ω).

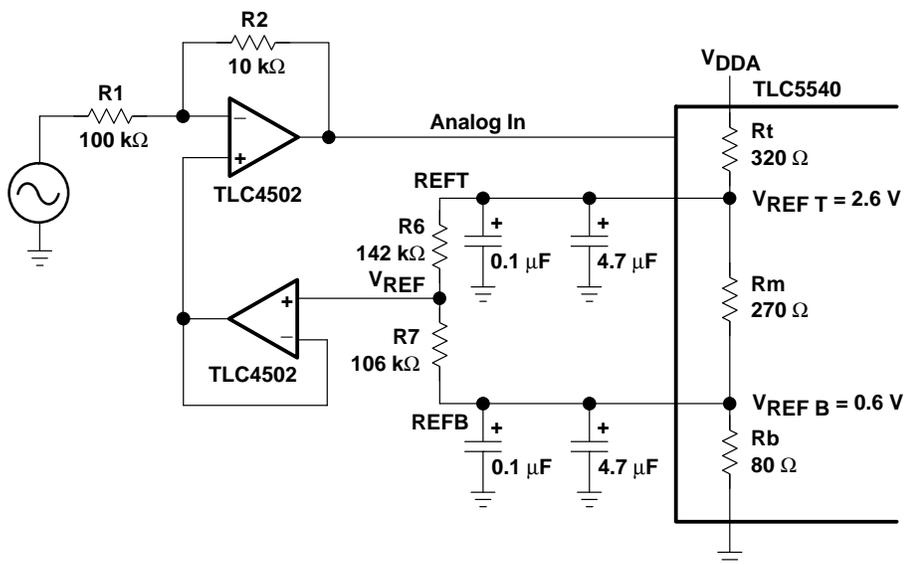


Figure 4. Circuit With a 180 Degree Phase Shift

$$V_{\text{out}} = V_{\text{in}} \left(-\frac{R2}{R1} \right) + V_{\text{ref}} \left(1 + \frac{R2}{R1} \right) \quad (7)$$

Where

$$V_{\text{ref}} = V_{\text{Bot}} + \left(V_{\text{Top}} - V_{\text{Bot}} \right) \times \frac{R7}{R6 + R7} \quad (8)$$

And, V_{Top} , V_{Bot} are derived as they were for Figure 1.

Power Supply and Layout Consideration

Power supply noise and circuit board layout are key to achieving desired performance for most high speed converters. Refer to application section of the data sheet of the converters you are using for power supply decoupling and layout recommendations. The evaluation module (EVM) for the TLC5510/5540 is also an example of proper layout and decoupling.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Mailing Address:

Texas Instruments
Post Office Box 655303
Dallas, Texas 75265