



Uttama Sahu, Sanjay Pithadia, Ivan Salazar

Medical alarm designs require expertise in hardware, software, acoustics and in-depth understanding of the regulatory requirements. The DAC53701 smart DAC provides a simple way to implement the alarm with configurable in-built waveforms triggered by a GPI.

Articles [1] and [2] discuss the medical alarm requirements and conventional implementation techniques in detail.

Introduction

Medical alarms are a critical part of most medical devices used in intensive care units (ICU), such as [multiparameter patient monitors](#), [neonatal warmers and incubators](#), [anesthesia delivery systems](#), [dialysis machines](#), [infusion pumps](#), [ventilators](#), and [surgical equipment](#). A patient's health and wellbeing often depend on the proper functionality of medical devices and medical alarms play an important role in alerting the caregiver when a failure event occurs. All medical devices need single-fault protection. A *single-fault condition* in medical equipment refers to the presence of a single independent abnormal condition. During a single-fault condition, a medical device must provide basic safety from physical hazards and minimum functionality, known as *essential performance*. While basic safety is usually obtained through isolation and leakage control, the alarm function is a key contributor to the essential performance for most therapeutic and all critical-care medical devices. The DAC53701 smart DAC provides integrated medical alarm functions compatible with the IEC60601-1-8 standard, such as different alarm priorities, *pulse frequency*, and *burst* patterns with configurable timings, thus simplifying the design and shortening the development time.

Smart DAC - DAC53701

The DAC53701 device is a 10-bit smart digital-to-analog converter (DAC) with nonvolatile memory (NVM), I²C interface, and general-purpose input (GPI). This device is available in a tiny, 2-mm x 2-mm package. This device supports medical alarm generation using pre-programmed waveforms. The waveforms can be triggered by both I²C and GPI interfaces. This DAC can be used for both auditory and visual alarm generation. It supports configurability

of the pulse frequency and the timings for the pulse envelope and the burst.

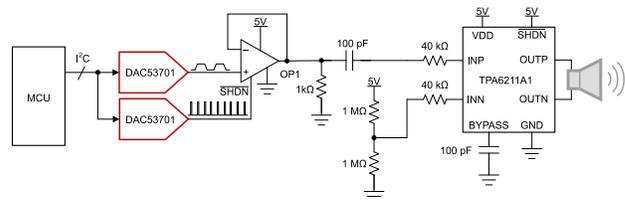


Figure 1. Primary Auditory Alarm

Primary Auditory Alarm

For the primary auditory alarm implementation, two DAC53701 devices are required: one device to generate the *pulse envelope* and the *burst*, and the second device to generate the *pulse frequency* as shown in Figure 1. The signals coming from both the DACs are combined together using the amplifier OP1 that has a shutdown pin, for example, the TLV9002S or OPA363 devices. The combined signal is then AC-coupled to an audio amplifier, such as the TPA6211A1, to drive the speaker. The TPA6211A1 is an integrated Class-AB amplifier which can drive up to 3 W of output power with very little distortion. The waveforms at different nodes of the circuit in Figure 1 are shown in Figure 2.

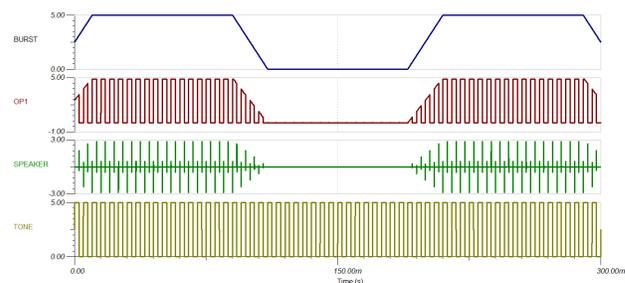


Figure 2. Auditory Alarm Waveforms

As per the IEC60601-1-8 medical alarm standard, the pulse frequency must be above 150 Hz and must have at least four harmonic components that are within ± 15 dB of each other. As a result of the square wave pulse frequency and the mixing done by OP1, the speaker output generates multiple harmonics of the fundamental pulse frequency. The DAC53701

provides a range of timing options for the pulse frequency and the pulse envelope.

Visual Alarm

The output of the DAC53701 can also be used to drive the visual alarm LEDs as shown in Figure 3. For redundancy, use another DAC53701 device and do not share the DAC from the auditory alarm. The force-sense output of the DAC53701 helps drive the gate and source of the MOSFET directly thus compensating for the drift of the gate-to-source voltage (V_{GS}). The circuit in Figure 3 provides linear control of the LED. In case high-power LEDs are used, a switching LED driver is preferred to linear control for power efficiency and the DAC output can drive the current control pin of the LED driver.

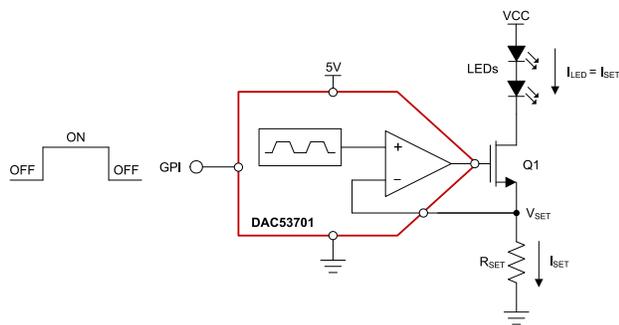


Figure 3. Visual Alarm

Secondary Alarm

The medical alarm is part of the essential performance for most medical devices. Hence, it is responsible to alert the caregiver in case of any failure event that does not have any redundant protection mechanisms. A power failure for mains-powered medical devices or battery discharge for battery-powered medical devices can be fatal to the patient. A similar risk may also occur in case of the failure of the primary alarm system. Hence, an independent alarm is used to indicate power failure or the failure of the primary alarm system. This secondary alarm is usually triggered by a secondary processor, a watchdog timer, or a power failure detection circuit. This alarm circuit is typically powered by a supercapacitor or a battery. Particular medical device standards specify a minimum ON-time for the power failure alarm. Simplistic implementations of secondary alarms often connect an internally driven buzzer to a supercapacitor directly. Such implementations generate a single tone alarm that is hard to modify. Figure 4 shows a circuit for creating a more effective alarm implementation where custom patterns can be generated using a single or two DAC53701 devices and inexpensive externally driven transducers. Custom alarm patterns help distinguish the alarm

more clearly in a crowded ICU setup as compared to a single tone. The DAC53701 operates at very low quiescent current thus increasing the duration of the power failure alarm running from a supercapacitor.

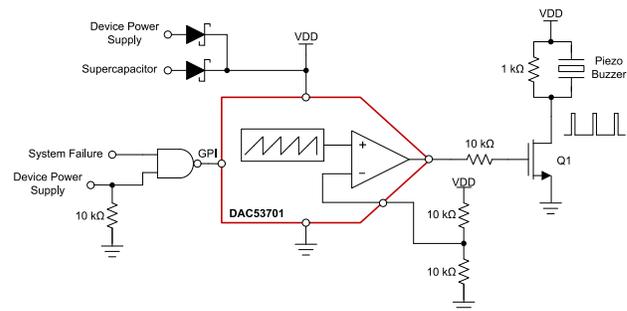


Figure 4. Secondary Alarm

Volume Control

Medical devices need volume control for the alarms. The DAC53701 provides 3 gain control settings that can be used for volume control. A more granular control can also be achieved by controlling the maximum level of the alarm waveforms through the margin-high register bits.

Conclusion

As discussed thoroughly in articles [1] and [2] and in this application brief, creating designs for medical alarms can be challenging due to complex regulatory requirements, multi-domain expertise requirement, tuning requirements during testing, portability of the design across multiple end equipment, and total time and cost of the development. Conventional techniques lack in providing a holistic solution as discussed in 2. The DAC53701 provides a simple way to create medical alarm designs by addressing all the technical and non-technical challenges. This device can be used for both primary and secondary or auditory and visual alarm implementations. The tiny package also makes the solution suitable for small form factor designs.

References

1. [Demystifying medical alarm designs, part 1: IEC60601-1-8 standard requirements](#)
2. [Demystifying medical alarm designs, part 2: Design inputs and existing techniques](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated