

# Isolated Loop Powered 4 to 20mA Field Transmitter Designs



Donna Xu, Preeti Udapudi, Juergen Schneider

## ABSTRACT

This application note describes three designs of isolated low power supplies for 2-wire loop powered 4 to 20mA field transmitters or sensors, which are all based on primary side half-bridge topology and secondary side Schottky rectification. The design 1 is using a switching frequency of 50kHz and providing the best in class efficiency, which is available on ti.com as [TIDA-00349](#). The design 2 focuses on optimizing the board space with operating switching frequency of 250kHz and using the customized low size transformer. Furthermore, the design 3 provides maximum of flexibility in terms of switching frequency up to 500kHz by using MSPM0 to generate two channels of PWM (Pulse Width Modulation) signals. This application note describes the design 3 in detail.

## Table of Contents

<b>1 Introduction</b> .....	<b>2</b>
1.1 System Description.....	2
1.2 Design 1: High Efficiency Design with 50kHz.....	2
1.3 Design 2: Space Optimized Design with 250kHz.....	3
1.4 Design 3: MCU Driven Design with Flexible Switching Frequency.....	3
<b>2 Design File</b> .....	<b>8</b>
2.1 Schematics.....	8
2.2 Bill of Materials.....	8
<b>3 Summary</b> .....	<b>10</b>
<b>4 References</b> .....	<b>10</b>

## Trademarks


FemtoFET™ is a trademark of Texas Instruments.  
All trademarks are the property of their respective owners.

# 1 Introduction

## 1.1 System Description

In the realm of industrial automation and control, 2-wire loop-powered 4 to 20mA field transmitters are very common for their reliable and accurate signal transmission over long distances. The current loop's ability to maintain signal integrity over several hundred meters, or even kilometers, is largely attributed to the current signal's robustness against the electrical noise that can be induced into long cable runs. The current-based signal, as opposed to voltage signal, is less susceptible to voltage drops and the interference from electromagnetic sources, making sure a stable and reliable communication pathway between sensors and control systems.

However, the very nature of industrial sites often requires sensors, such as thermocouples, to be in direct contact with grounded metallic structures, while the control systems they communicate with can reference a different ground potential. This disparity can result in ground loop currents, which, due to the extensive distances involved, can significantly degrade measurement accuracy by introducing unwanted noise and potential offsets into the signal. To mitigate these issues, electrical isolation becomes imperative.

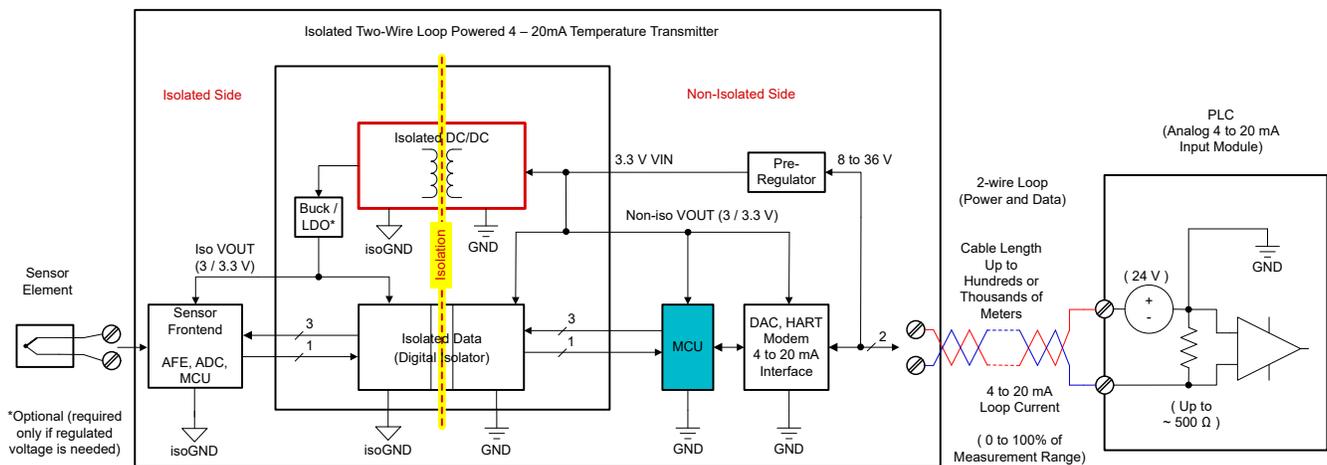

**Figure 1-1. Isolated Two-Wire Loop-Powered 4 to 20mA Temperature Transmitter Control System**

Figure 1-1 shows a typical block diagram of an isolated two-wire loop powered 4 to 20mA temperature transmitter system, including the current flow used for the communication bus and power for the system, which is designed to convert sensor measurements into a 4 to 20mA loop current signal. Under normal operating conditions, the total current consumption of the transmitter's transmitter must be less than the actual loop current. Power savings achieved from any individual sub-circuit, including the isolated DC/DC, can be redistributed to other circuit blocks of the system. It allows for optimization of other functionality, ultimately leading to a more efficient end product. Due to the limited supply current budget, it is crucial that a highly efficient power design is imperative. This application note will focus on the isolated DC/DC designs which are encased in the red box in Figure 1-1, and the design 3 is more suitable for situations where there is already an MCU on the non-isolated side of the system, which the location is shown in the blue box. Additionally, the flexibility of these designs also allows them to be customized for various applications that demand small size and highly efficient power conversion and isolated data transmission, especially when they must operate from power sources with restricted current availability.

## 1.2 Design 1: High Efficiency Design with 50kHz

Design 1 is characterized at  $-40^{\circ}\text{C}$ ,  $+25^{\circ}\text{C}$ , and  $+85^{\circ}\text{C}$ , accepts input voltages from 3V to 5.2V, and can deliver output currents up to 10mA. It uses a low power consumption charge pump to drive the transformer at 50kHz frequency. A low switching frequency helps to achieve a uniquely high efficiency even at much lower output power levels, ranging from some tens of milliwatts down into the sub-milliwatt range. This design is able to provide more than an 85% efficiency for a 5V input operation at 15mW to 50mW of output power and more than 80% efficiency for a 3.3V operation at a 3mW to 20mW power level.


### 1.3 Design 2: Space Optimized Design with 250kHz

Design 2 focuses on optimizing the board space by reducing the size of the transformer, [Table 1-1](#) outlines the comparison of two transformers on different features. Design 2 and design 3 (with high switching frequency) use a customized smaller size transformer with 9.60 x 5.51 x 4.83mm<sup>3</sup>.

**Table 1-1. Comparison of Transformer Specifications**

	Turns Ratio (NP:NS)	Magnetizing Inductance Lm (mH)	V-t Product (V- $\mu$ s)	Isolation (V <sub>AC</sub> , 1 Minute)	Dimensions (mm <sup>3</sup> )	Operating Temperature Range (°C)	Manufacturer
Design 1	1:1.25	> 3	100	1500	9.78 x 9.14 x 10.54	-40 to 100	WURTH ELEKTRONIK
Design 2, 3	1:1.5	>0.6	10	800	9.60 x 5.51 x 4.83	-40 to 100	WURTH ELEKTRONIK


[Figure 1-2](#) shows the detailed schematic of design 2, in order to use a smaller size transformer, the switching frequency has to be increased. This can be realized by using TPS60403 with a frequency of 250kHz. In this design, power consumption of charge pump is higher due to higher switching frequency. As a result, design 2 will be slightly less efficient than design 1. However, it can still achieve more than 80% efficiency with 3.6V input and nearly 70% efficiency with 1.8V input.

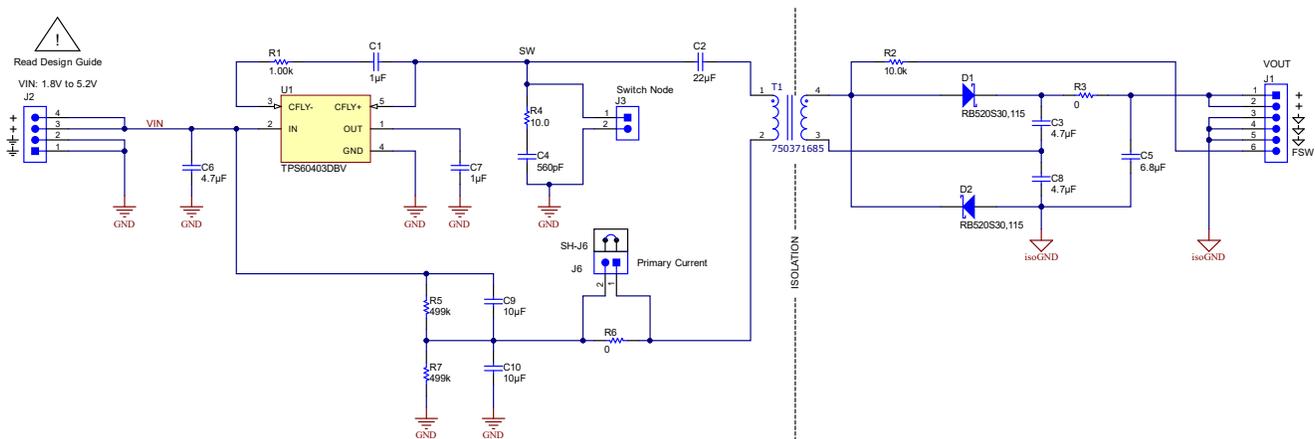

**Figure 1-2. Schematic of Design 2**

### 1.4 Design 3: MCU Driven Design with Flexible Switching Frequency

The design 3 is designed to operate with input voltages ranging from 1.62V to 3.6V, compatible with output currents up to 10mA. In terms of efficiency, design 3 can reach up to 83% with 3.6V input and 72% at 1.8V input when operating at 50kHz switching frequency. When the switching frequency is increased to 250kHz, efficiencies of up to 77% with 3.6V input and 62% with 1.8V input are attainable.

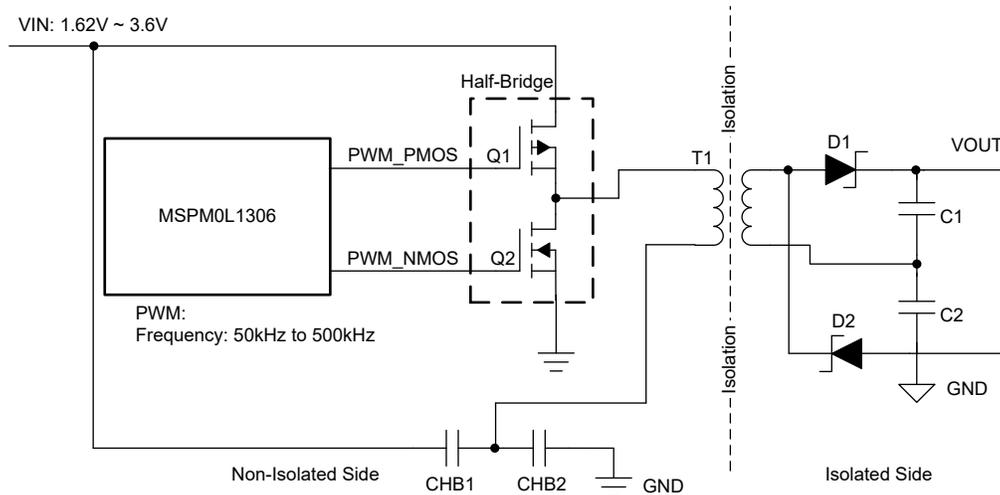

**Figure 1-3. Block Diagram of Design 3**

Figure 1-3 illustrates a block diagram of MCU driven design, it uses MSPM0L1306 to generate two-channel of PWM signals to control the half-bridge composed of a P-MOSFET and a N-MOSFET, which in turn drives the primary winding of the transformer on the non-isolated side and the double voltage circuit on the isolated side. The MSPM0 series MCU's versatility allows for accurate and programmable switching frequency up to 500kHz.

#### 1.4.1 Selection of MOSFETs

To make sure the half-bridge circuit depicted in Figure 1-3 operate within safe limits, maintain efficiency, and contribute to the circuit's longevity, selecting the appropriate MOSFETs involves several considerations:

1. Voltage Rating: The MOSFETs must have a drain-to-source voltage rating ( $V_{DS}$ ) that exceeds the maximum input voltage (3.6V) of the circuit to handle voltage spikes without breaking down.
2.  $R_{DS(on)}$  Value: A lower on-resistance ( $R_{DS(on)}$ ) is preferred for reduced conduction losses, which improves efficiency and minimizes heat generation.
3. Gate Charge: Lower gate charge ( $Q_g$ ) allows for faster switching and lower switching losses, which is critical for high switching frequency operation.

Besides the aforementioned characteristics, it is also crucial to factor in the threshold voltage ( $V_{GS(th)}$ ), switching speed, and package. Aiming for a more compact design, a comparison of various MOSFETs with ultra-small footprints is conducted, as detailed in Table 1-2 for N-MOSFETs and Table 1-3 for P-MOSFETs.

**Table 1-2. Comparison of Ultra-Small Footprint N-Channel FemtoFET™ MOSFETs**

	CSD13380F3	CSD13383F4	CSD13385F5	CSD15380F3	CSD17381F4
$V_{DS}$ (V)	12	12	12	20	30
$R_{DS(on)}$ (mΩ) at $V_{GS} = 2.5V$	73	53	18	2220	110
$Q_g$ (typ) (nC)	0.91	2.0	3.9	0.216	1.04
$V_{GS(th)}$ (typ) (V)	0.85	1.0	0.8	1.1	0.85

**Table 1-3. Comparison of Ultra-Small Footprint P-Channel FemtoFET™ MOSFETs**


	CSD23280F3	CSD23382F4	CSD23285F5	CSD25480F3	CSD25481F4
$V_{DS}$ (V)	-12	-12	-12	-20	-20
$R_{DS(on)}$ (mΩ) at $V_{GS} = -2.5V$	129	90	38	203	145
$Q_g$ (typ) (nC)	0.95	1.04	3.2	0.7	0.913
$V_{GS(th)}$ (typ) (V)	-0.65	-0.8	-0.65	-0.95	-0.95

After comparing the specifications in the tables, the CSD13380F3 for N-Channel and CSD23382F4 for P-Channel MOSFETs have been selected. This decision is based on their lower resistance when on ( $R_{DS(on)}$ ) and the lower charge required to switch them on and off ( $Q_g$ ), which means they will use less power and switch faster. Additionally, both of them the threshold voltages ( $V_{GS(th)}$ ) are very similar, which ensures a balanced switching and reduces the risk of short through during transitions, and overall leads to a more efficient circuit operation. These features make them well-suited for high-frequency, space-conscious applications.

## 1.4.2 Efficiency Test

### 1.4.2.1 Current Consumption of PWM ( $I_{pwm}$ ) Test


To accurately ascertain the efficiency of the MCU driven design, it is essential to know the current consumption of the MSPM0 when it generates dual-channel PWM signals. This test is conducted on the MSPM0L1306 Evaluation Module (EVM) board, with the test configuration depicted in Figure 1-4. Measuring the current consumption of the MCU when driving the half-bridge (connect the green wires), and then subtracting the current consumed by the MCU running an empty program (disconnect the green wires), yields the specific current used for generating dual-channel PWM signals.

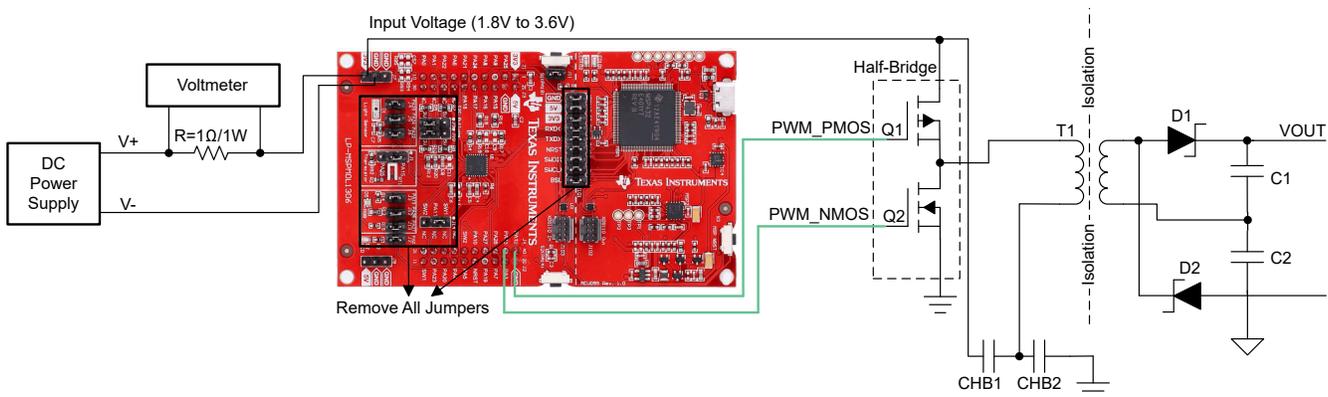

**Figure 1-4. Set Up of Current Consumption Test on MSPM0L1306 EVM Board**

As per the [MSPM0L1306 LaunchPad Development Kit User's Guide](#), in Section 2.6, an external power supply is utilized instead of USB power from a PC. The MSPM0L1306 is in "Free Run" mode and disconnect programming signals between the MSPM0L1306 and the debug portion of the board (header J101).

Current measurement is facilitated by a shunt resistor, placed between the power supply's positive terminal and the 3V3 pin on the MSPM0L1306 EVM board, by measuring the voltage drop across the resistor. To prevent any extraneous current consumption that can be caused by floating I/Os, all unused GPIOs are actively set to low. Additionally, to isolate the microcontroller from any parasitic loads, all other jumpers, especially those connected to indicator LEDs, are disconnected.

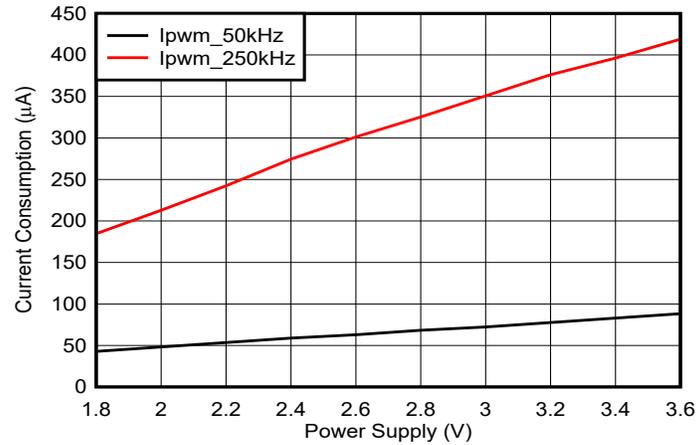

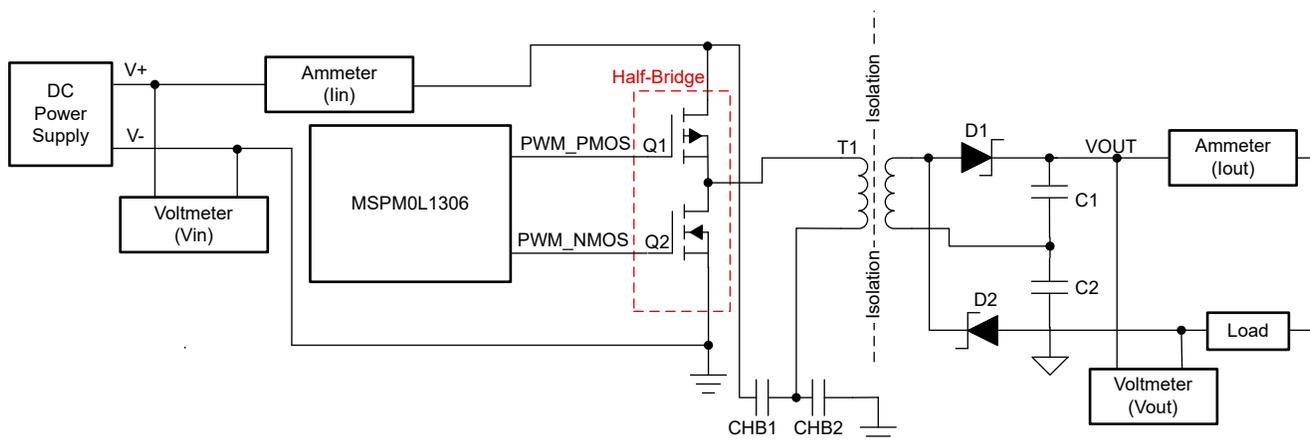
**Figure 1-5. Current Consumption versus Power Supply Voltage at Different PWM Frequency of MSPM0L1306**

Figure 1-5 displays the current consumption of generating PWM signals with different frequency at different power supply voltages from 1.8V to 3.6V. Red line shows the current consumption of 250kHz switching frequency with 45.3% duty cycle, black line shows the current consumption of 50kHz switching frequency with 49% duty cycle. As the power supply voltages increases, the current consumption also increases. Specifically, at a higher switching frequency of 250kHz, the current consumption is significantly greater across all power supply voltages compared to the lower frequency of 50kHz.

#### 1.4.2.2 Efficiency Test Set Up

Efficiency of isolated DC/DC is a critical parameter for two-wire loop-powered 4 to 20mA field transmitter system, influencing both the power consumption and the reliability of the loop power supply. Figure 1-6 illustrates the setup of the MCU driven design efficiency test. The setup includes precision instruments that are connected to record the input and output voltages ( $V_{in}$  and  $V_{out}$ ) and currents ( $I_{in}$  and  $I_{out}$ ). Using a rotating resistor box as the load, it operates over an output current range up to 10mA to test. Digital multimeters are in place to capture voltage and current readings with high accuracy, ensuring the collected data reflects the true performance of this design. The efficiency can be calculated by using Equation 1, where  $I_{pwm}$  is the test results in the previous section.

$$\text{Efficiency} = \frac{V_{out} \times I_{out}}{V_{in} \times (I_{in} + I_{pwm})} \quad (1)$$

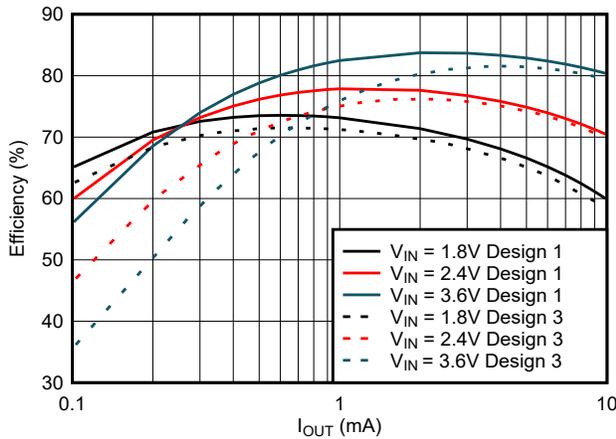


**Figure 1-6. Set Up of Efficiency Test**


### 1.4.2.3 Efficiency Test Results at 50kHz Switching Frequency

The efficiency test was conducted with input voltages set to 1.8V, 2.4V and 3.6V. Presented on [Figure 1-7](#) are the efficiency curves versus the output current for both design 1 in solid lines and design 3 in dashed lines. In this test, design 3 runs with 50kHz switching frequency using a same transformer as design 1. At an input voltage of 3.6V, it is observed that both designs attain an efficiency more than 80%.

[Figure 1-8](#) depicts the output voltage as a function of the output current for the two designs, where both demonstrating good linearity throughout the current range tested.



**Figure 1-7. Efficiency Test Results of Design 1 and Design 3 at 50kHz Switching Frequency**

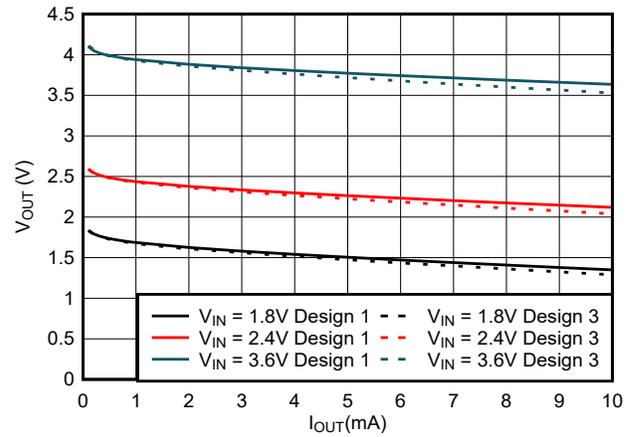


**Figure 1-8. VOUT vs IOU of Design 1 and Design 3 at 50kHz Switching Frequency**


### 1.4.2.4 Efficiency Test Results at 250kHz Switching Frequency

The efficiency test for a 250kHz switching frequency utilized the same arrangement as the 50kHz frequency test but incorporated a smaller newly designed transformer. Solid lines represent the results for design 2, while dashed lines correspond to the design 3. [Figure 1-9](#) shows the efficiency plotted against the output current for both designs, and [Figure 1-10](#) displays the output voltage as a function of the output current.

The tests were performed at input voltages of 1.8V, 2.4V, and 3.6V. The increasing in switching frequency to 250kHz resulted in a higher power dissipation for MSPM0L1306 generating PWM signals, as evidenced by a comparison of data from [Figure 1-5](#). This increase in power consumption contributed to a decrease in the efficiency of design 3 comparing with design 2. Nonetheless, at an input voltage of 3.6V, design 3 also can achieve an efficiency of up to 77%.

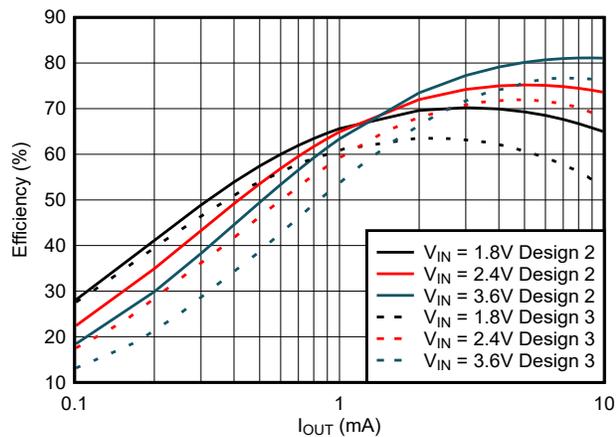

**Figure 1-9. Efficiency Test Results of Design 2 and Design 3 at 250kHz Switching Frequency**

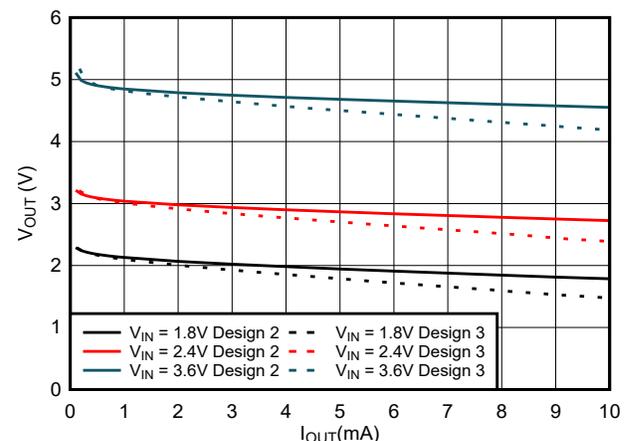

**Figure 1-10. VOUT vs IOU of Design 2 and Design 3 at 250kHz Switching Frequency**



**Table 2-1. Bill of Materials (continued)**

Item #	Designator	Quantity	Part Number	Manufacturer	Description	Package Reference
16	R2	1	CRCW08050000Z0EAHP	Vishay-Dale	RES, 0, 5%, 0.333 W, 0805	0805
17	R3, R5	2	CRCW0402499KFKED	Vishay-Dale	RES, 499k ohm, 1%, 0.063W, 0402	0402
18	SH-J6	1	969102-0000-DA	3M	Shunt, 100mil, Gold plated, Black	Shunt
19	T1	1	750371685	Würth Electronics	TRANSFORMER	SMT4
20	U1	1	MSPM0L1306SDYY	Texas Instruments	Mixed-Signal Microcontrollers SOT-23-THIN-16	SOT-23-THIN-6
21	FID1, FID2, FID3	0	N/A	N/A	Fiducial mark. There is nothing to buy or mount.	Fiducial
22	R4	0	CRCW08050000Z0EAHP	Vishay-Dale	RES, 0, 5%, 0.333 W, 0805	0805

### 3 Summary

This application note introduces three designs regarding to isolated power supply for two-wire loop-powered 4 to 20mA field transmitter system.

Design 1 runs at a fixed switching frequency of 50kHz offers the highest efficiency at 5V input voltage, reaching 86%, and maintains a higher efficiency at lower input voltages. However, it uses a larger transformer which may not be optimal for size-constrained applications.

Design 2 with 250kHz switching frequency shows a slightly reduced efficiency compared to design 1, with the best performance of 80% at 3.6V. It benefits from a smaller transformer size, which is advantageous for compact designs.

Design 3 is the most flexible with programmable frequency up to 500kHz, allowing a small transformer, and maintaining a compact form factor. [Table 3-1](#) gives an overview of these three designs.

**Table 3-1. Comparison of Three Designs**

Features	Design 1 (50kHz)	Design 2 (250kHz)	Design 3 (up to 500kHz)
<b>Switching Frequency</b>	Fixed 50kHz (- 40%, +40%)	Fixed 250kHz (-40%, +20%)	Programmable up 500kHz
<b>Efficiency</b>	<ul style="list-style-type: none"> <li>• 86%(5V)</li> <li>• 82%(3.3V)</li> </ul>	<ul style="list-style-type: none"> <li>• 80%(3.6V)</li> <li>• 67%(1.8V)</li> </ul>	<ul style="list-style-type: none"> <li>• 50kHz:               <ul style="list-style-type: none"> <li>– 83%(3.6V)</li> <li>– 72%(1.8V)</li> </ul> </li> <li>• 250kHz:               <ul style="list-style-type: none"> <li>– 77%(3.6V)</li> <li>– 62%(1.8V)</li> </ul> </li> </ul>
<b>Transformer Size (mm<sup>3</sup>)</b>	<b>Large</b> 9.78 x 9.50 x 10.54	<b>Small</b> 9.60 x 5.51 x 4.83	<b>Small</b> 9.60 x 5.51 x 4.83

In conclusion, the selection of an appropriate design should be based on specific application requirements, considering factors like overall board size and efficiency. The design 3 is particularly suitable for systems where an MCU is already present on the non-isolated side, offering a streamlined integration with programmable flexibility.

### 4 References

1. Texas Instruments, [Uniquely Efficient Isolated DC/DC Converter for Ultra-Low Power and Low-Power Applications](#), design guide.
2. Texas Instruments, [Isolated Loop Powered Thermocouple Transmitter](#), design guide.
3. Texas Instruments, [Isolated Power and Data Interface for Low-Power Applications](#), design guide.
4. Texas Instruments, [MSPM0L1306 LaunchPad Development Kit \(LP-MSPM0L1306\)](#), user's guide.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated