

Application Brief

Space-Grade, 30-krad, Isolated I²C Circuit



Alfred Chong


Design Goals

Parameter	Design Requirement
Supply voltage	3.3 V
Signaling Rate	1Mbps (fast Mode)
Maximum Total Ionizing Dose	30krad(Si)
Maximum SEL to LET	43MeV × cm ² /mg
Isolation voltage	3000 V _{RMS} per UL1577

Design Description

In spacecraft, I²C buses might be used for board-to-board communication, and the prevalence of using cold spares might require the addition isolation into the system. The I²C bus is a commonly-used bus for communication. The particular challenge in designing an isolated I²C interface by using standard digital isolators lies in the different operation modes between the two. The I²C bus operates in bidirectional, half-duplex mode, while standard digital isolators are unidirectional devices. To make efficient use of one technology supporting the other, external circuitry is required to separate the bidirectional bus into two unidirectional signal paths without introducing significant propagation delay.

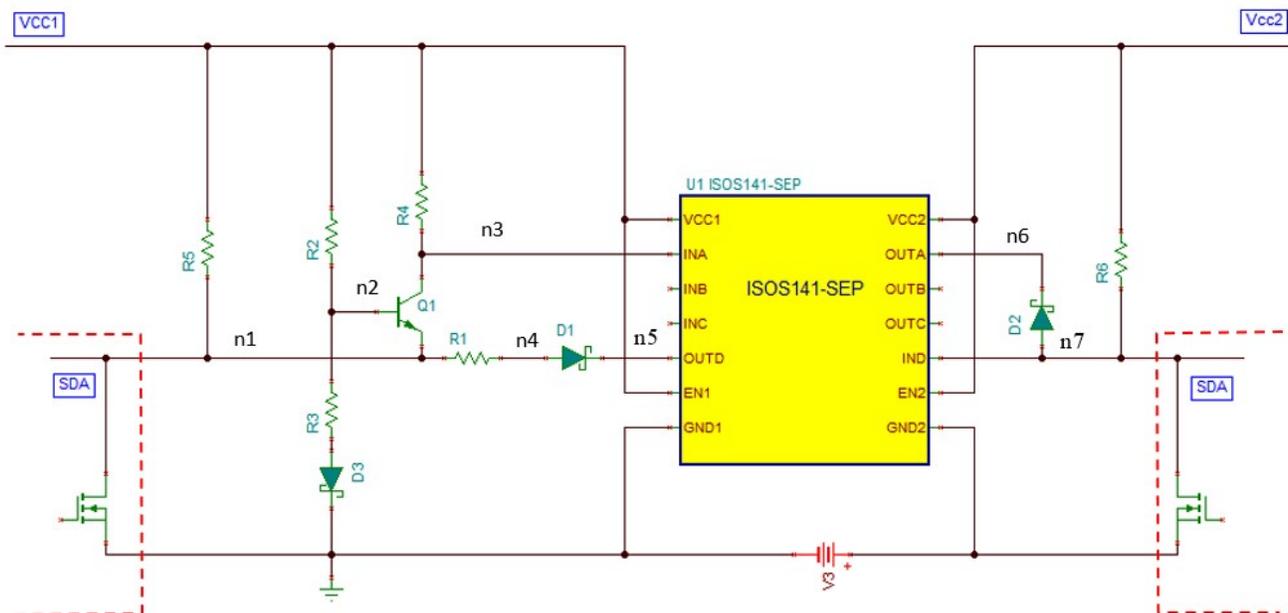
This circuit design uses an NPN transistor, 3 Schottky diodes, and 4 resistors to transform a digital isolator into an isolated I²C device.




Design Notes

Transistor Q1 and its surrounding resistor network provide the comparator function. Since the dominant switching level in I²C is logic low, the base of Q1 is so biased that a low level applied to n1 turns the transistor on, and a low level at n7 keeps Q1 at high impedance. While the R3, R2 voltage divider primarily determines the biasing, diode D3 provides temperature compensation. To prevent low level at n7 and thus n1 from turning Q1 on, the voltage level at n1 is raised by a voltage drop across R1 from n4, which raises the emitter potential of Q1, V_E, and decreases the base-emitter voltage below the minimum turn-on level. However, care must be taken to maintain V_E below the minimum input high-level threshold of SDA, which the I²C specification lists as V_{ILmax} = 0.3 × V_{CC}.

When the I²C bus at n7 is pulled to logic low state as illustrated in the dotted orange arrows in the next figure, the low state passing into IND and causes OUTD to go to low state. The voltage at n1 is pulled down to a low state illustrated by the blue arrows. The R1 introduces a voltage drop to n4 from n1, which raises the voltage at n1 high enough to turn off the Q1 but well below V_{ILmax}, thus presenting a valid low for an I²C input. At the same time, R4 provides a logic high at to the isolator input INA and causes OUTA to go high, preventing diode D2 from conducting.

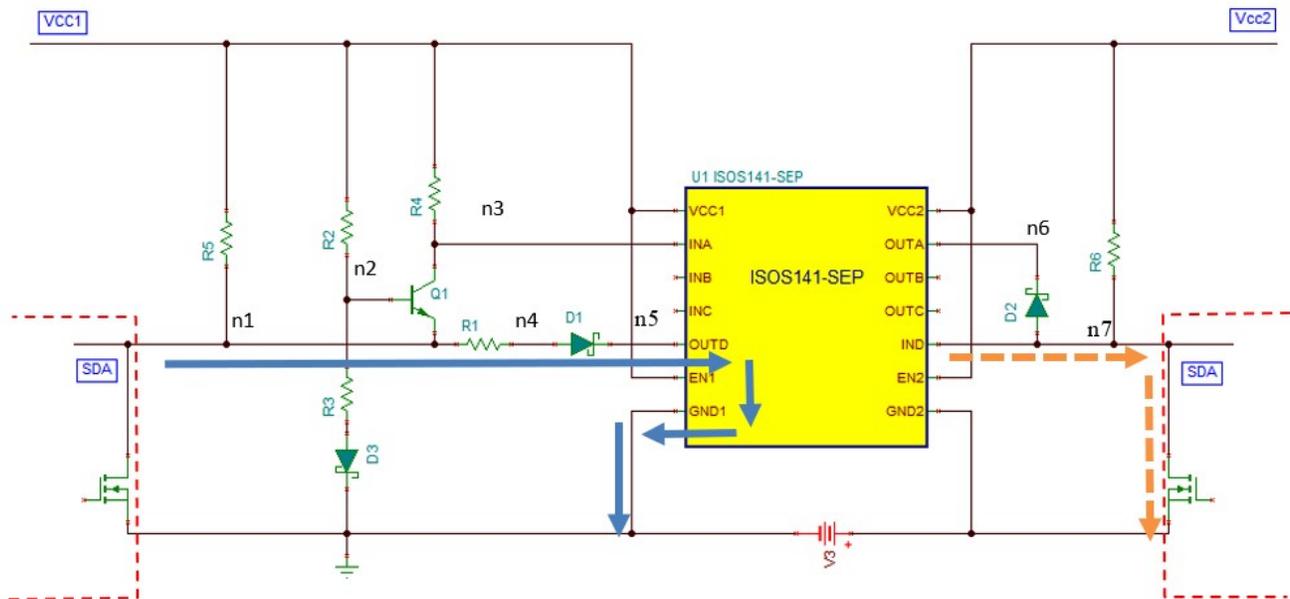

When n1 is pulled to a low state, the voltage across n2 and n1 is significantly lower than V_E and causes Q1 to conduct. This causes the INA to go to a logic low illustrated by the dotted orange arrows in the next figure. The low-state signal passing through the isolator and causes OUTA to go low. The voltage at n7 is pulled down through the forward bias of diode D2 illustrated by the blue arrows. However, when n1 goes high, its voltage cannot return to the level of V_{CC1} immediately due to the remaining low-level signal at n7 and n5 that causes D1 to forward bias. Instead, n1 rises to the necessary V_E potential that blocks Q1. It remains at this level until a high impedance across Q1 allows R4 to provide a logic high to the isolator input INA, thus releasing n6 and D3 and causing n7 to go high level. Only then will n1 be able to return to the level of V_{CC1}.

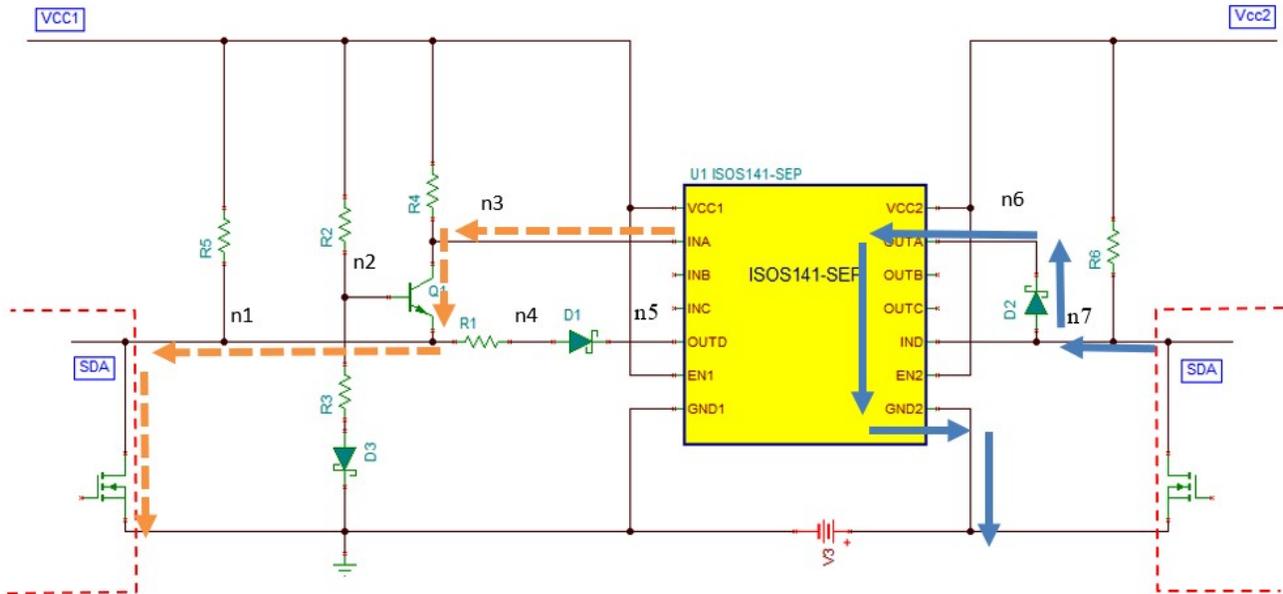

Design Steps

- Calculate pullup resistors

See the [I2C Bus Pullup Resistor Calculation](#) application report for the equation to calculate the pullup resistor for n1 and n7. In this design, the calculated pullup resistors for both n1 and n7 are 1.1kΩ. The pullup resistances vary from the selected I²C devices and bus capacitance.

Notes:

1. Include the capacitance of D1 and Q1 in the bus capacitance for n1 pullup resistor calculation
 2. Include the capacitance of D3 in the bus capacitance for n7 pullup resistor calculation
- Calculate R6 = pullup resistor for n7
R6 = 1.1kΩ
 - Calculate R5 and R4
R5 is parallel to R4. Assuming the transistor capacitance is 2.5 times smaller than the bus capacitance, we set R4 = 2.5 × R5 to make R5 have 2.5 times stronger pullup strength.

$$R_T = \frac{R_4 R_5}{R_4 + R_5} \rightarrow (1)$$

$$R_4 = 2.5 R_5 \rightarrow (2)$$

Using (2) in (1)

$$R_T = \frac{2.5 R_5}{3.5}$$

Let $R_T = 1.1\text{k}\Omega$ from n1 pullup resistor, $R_5 = 1.54\text{k}\Omega$ and $R_4 = 3.85\text{k}\Omega$

- Calculate R2 and R3
R2 and R3 is a voltage divider that sets the bias voltage for transistor Q1. The bias voltage should be higher than the turn-off voltage of the transistor Q1, 0.6V, but lower than the SDA $V_{ILmax} = 0.3 \times V_{CC}$. The constant current through R2 and R3 must be less than 1mA.

For $V_{CC} = 3.3V$, $0.6V < \text{bias voltage} < 0.99V$, let bias voltage = $0.65V$

$$0.001 = \frac{3.3}{R3 + R2} - (2)$$

$R3 = 650 \Omega$ and $R2 = 2.65k\Omega$

- Calculate R1

The purpose of R1 is to prevent transistor Q1 from turning on when n4 is pulled to 0V. The transistor Q1 turn-on voltage is 0.6 V, and the bias voltage is 0.65 V. Hence, the drop-out voltage across the R1 should be greater than the bias voltage minus the turn-on voltage but less than the V_{ILmax} . Also, the voltage drop across R1 is the voltage divider of R1 and R5

$$0.99V \leq \frac{R1}{R1 + R5} * 3.3 \geq 0.65V - 0.6V - (1)$$



Let the voltage-drop across R1 to be 0.17 V:

$$\frac{R1}{R1 + R5} * 3.3V = 0.17V$$



Using $R5 = 1.54k\Omega$ from the previous equation, $R1 = 84.5\Omega$.

Design Simulations


The following figure shows the final isolated I²C circuit whether the primary is isolated from a secondary bus. Only the SDA data line is bidirectional, and the SCL clock line is unidirectional. A pulse generator with 500kHz is set at the primary SDA to simulate the 1Mbps 0101 data pattern transmitted from n1 to n7. As shown in the lower figure, n1 is pulled down to logic low. This causes n3 to go to logic low and pass the value from the input INA to output OUTA. Hence n6 and n7 are pulled down to logic low. When SDA is released, n1 voltage only returns to logic high after the n7 voltage goes to logic high.

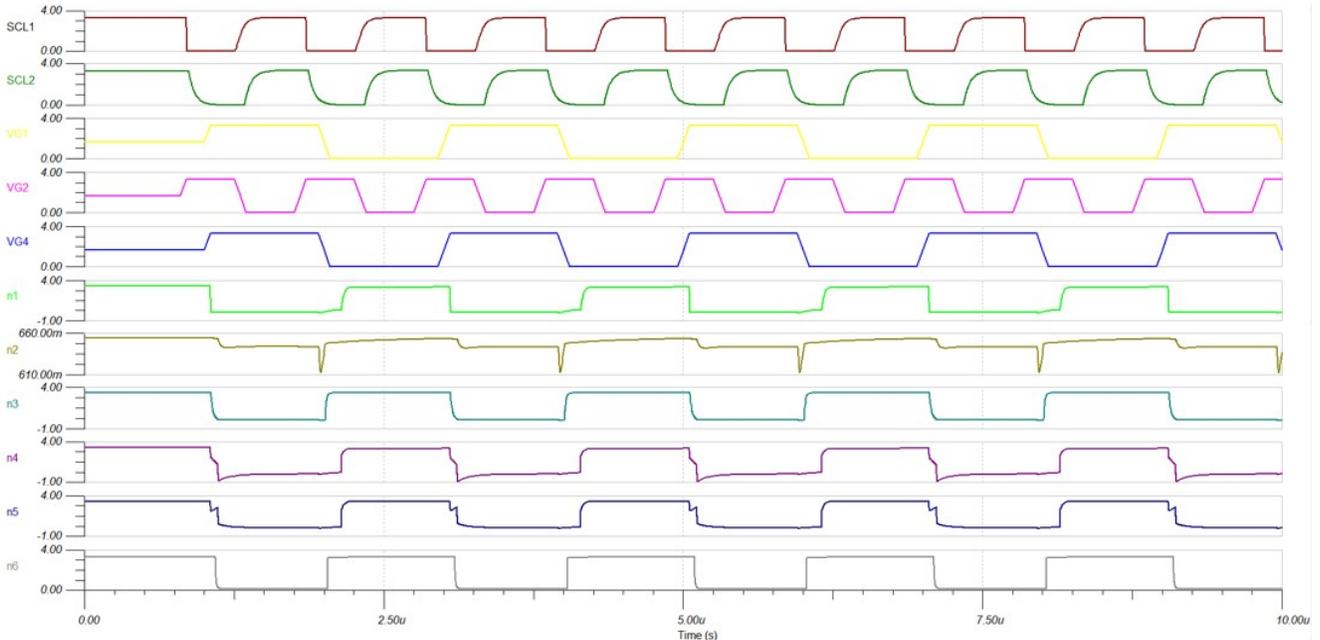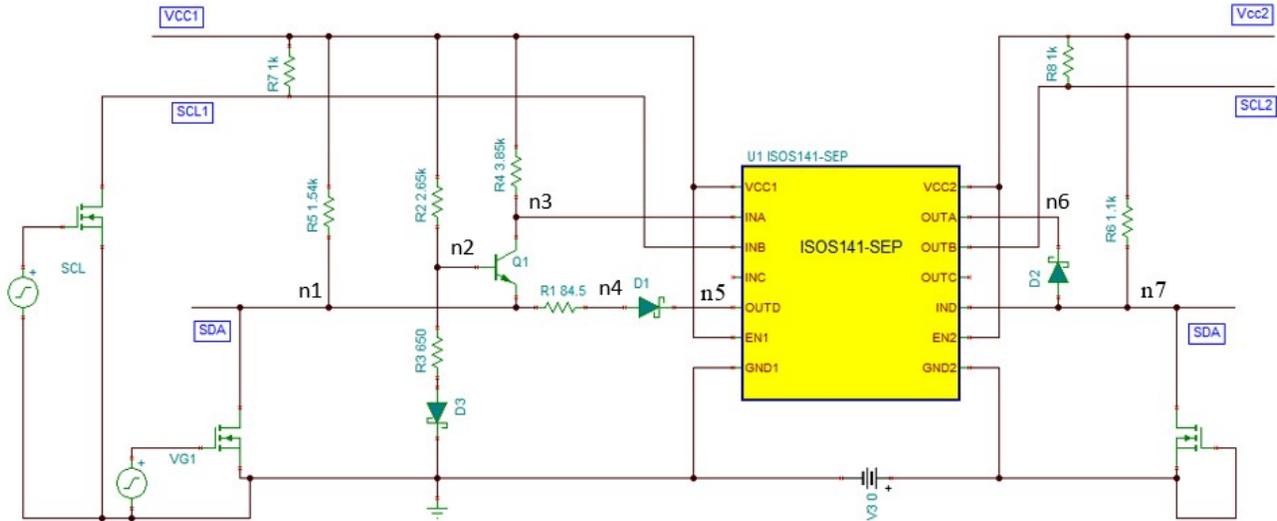

A pulse generator with 500kHz is set at the secondary SDA to simulate the 1Mbps 0101 data pattern transmitted from n7 to n1. As shown in the lower figure, n7 is pulled down to logic low and passing the value from the input IND to output OUTD. Hence n5 and n4 are pulled down to logic low. The n1 voltage is 0.17V higher than the n4 voltage due to the voltage drop across R1 but still well below VILmax.

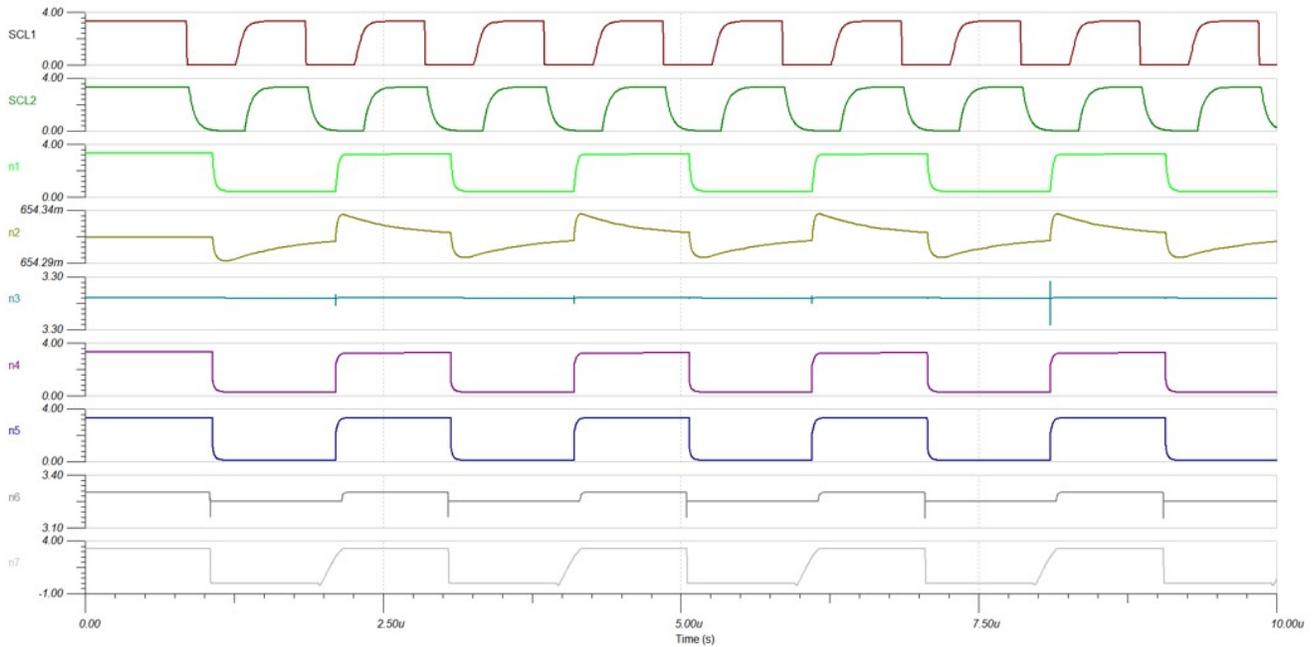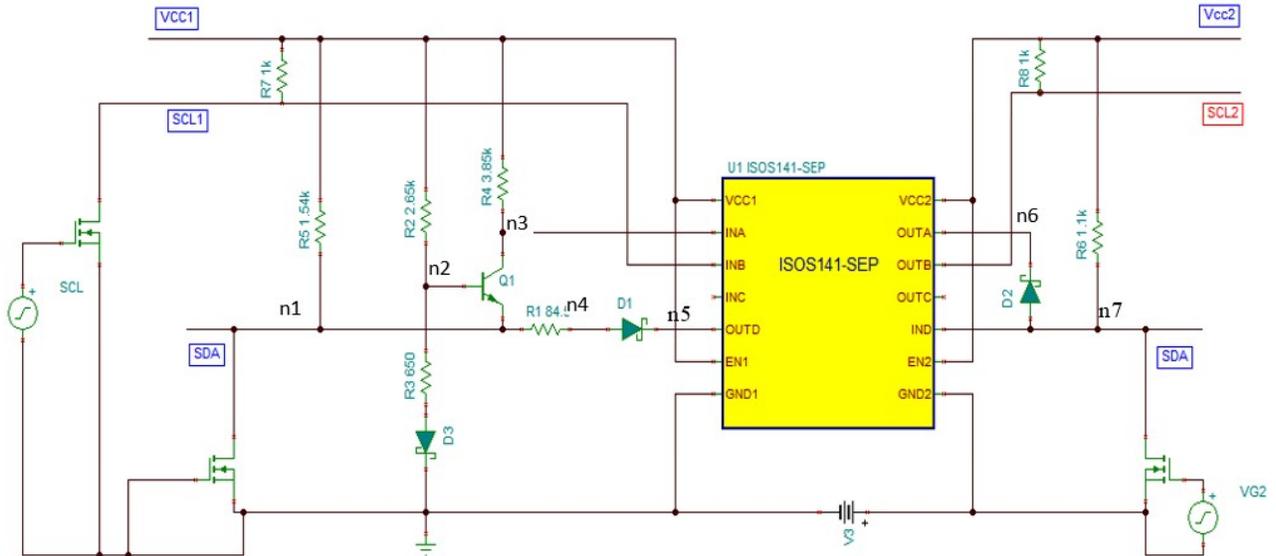

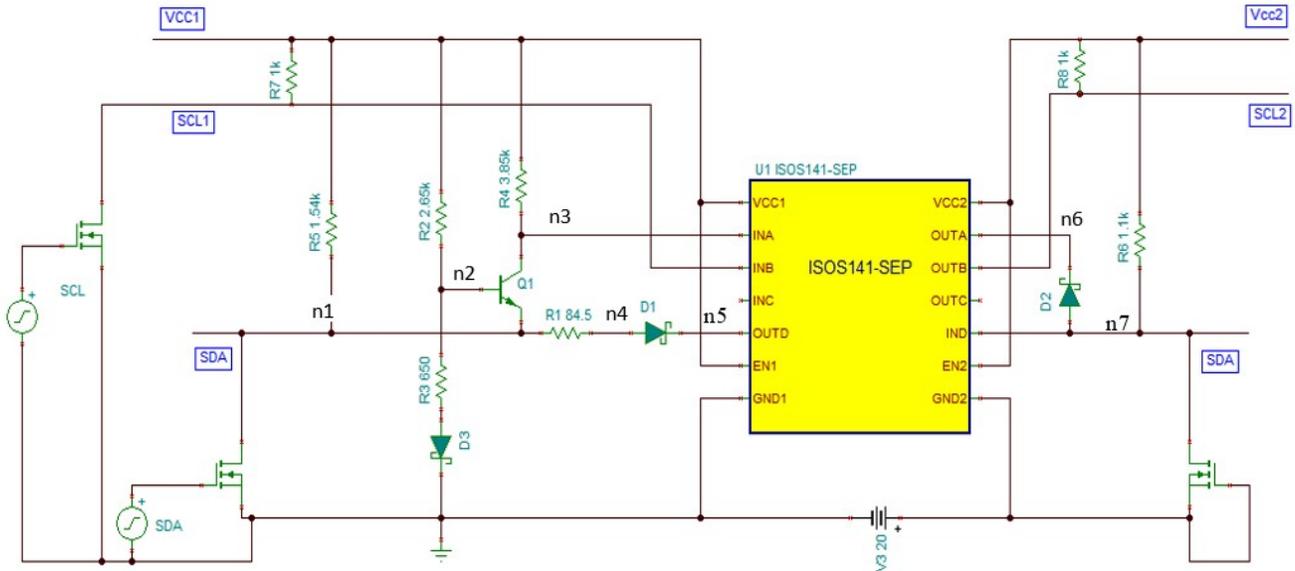A pulse generator with 500kHz is set at the primary SDA to simulate the 1Mbps 0101 data pattern transmitted from n1 to n7. The secondary side ground is raised by 20 V to simulate the performance of the isolated I²C. As shown in the following image, The primary side SDA (n1) operates from 0 V to 3.3 V, and the secondary side SCL and SDA (n7) operate from 20 V to 23.3 V due to ground bounds.



Reference

Design Featured Digital Isolator

ISOS141-SEP	
V _{CC1} , V _{CC2}	2.25 V to 5.5 V
Data-rate	100MHz
Propagation delay	10.7ns to 16ns
TID Characterized (ELDRS-Free)	30krad(Si)
TID RLAT, RHA	30krad(Si)
CMT1	±100kV/μs
V _{ISO}	3000 V _{RMS}
www.ti.com/product/ISOS141-SEP	

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated