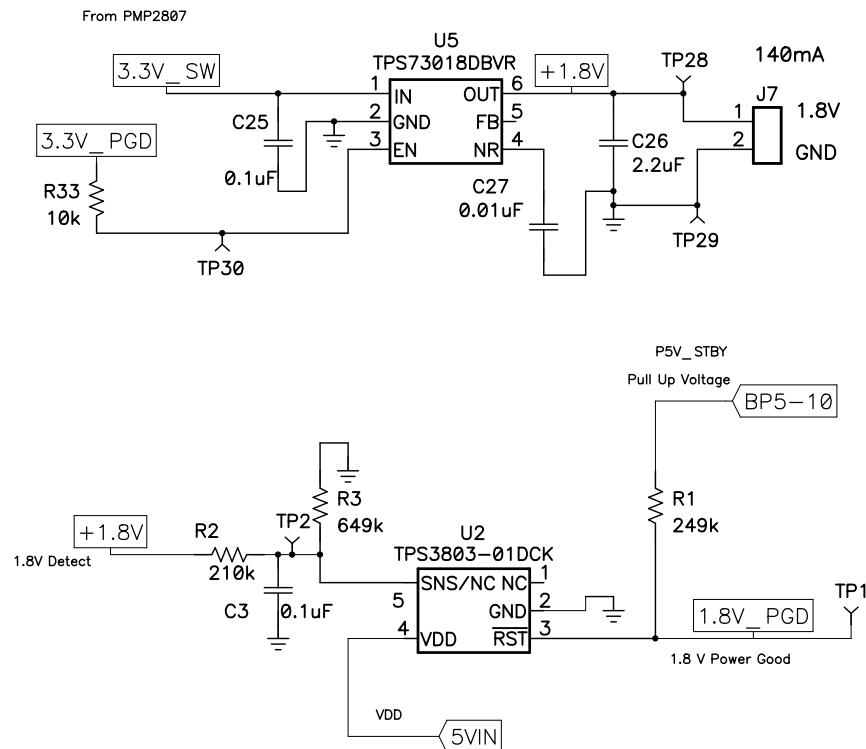


TEXAS INSTRUMENTS

Title		
	TPS40192 (x2), LDO	
Size	Number	Rev
B	PMP4025	A
Date	08-27-2008	Drawn by T. Olabumuyi
Filename	PMP4025REVA.SCH	Sheet 1 of 3


A                    B                    C                    D



TEXAS INSTRUMENTS

Title		
	TPS40192 (x2), LDO	
Size	Number	Rev
B	PMP4025	A
Date	08-27-2008	Drawn by Olabumuyi
Filename	PMP4025REVA.SCH	Sheet of

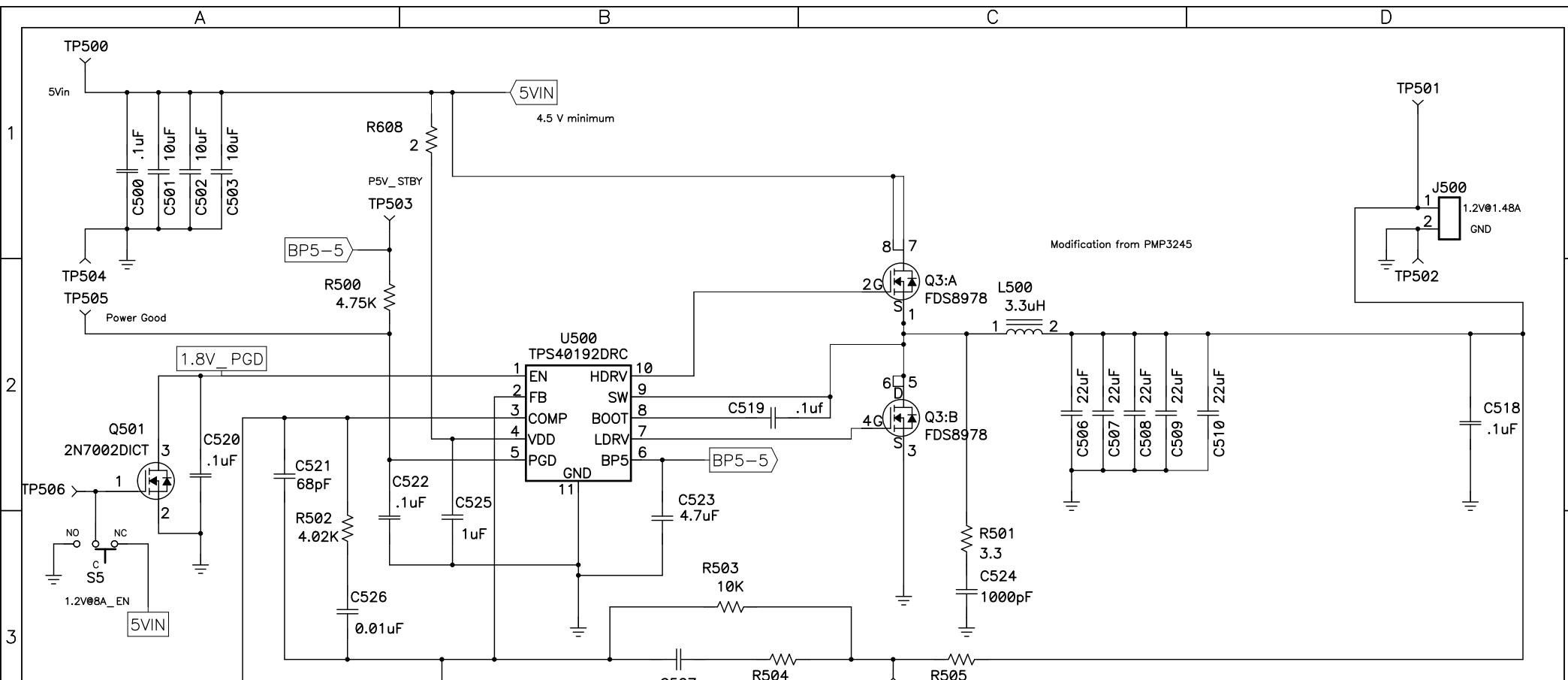A                    B                    C                    D



TEXAS INSTRUMENTS

Title TPS40192 (x2), LDO		
Size B	Number PMP4025	Rev A
Date 08-27-2008		Drawn by T. Olabumuyi
Filename PMP4025REVA.SCH		Sheet 3 of 3

**A****B****C****D**

**PMP4025REVA BOM**

COUNT	RefDes	Value	Description	Size	Part Number	Mfr
8	C1000, C1018, C1020, C1022, C1028, C518, C520, C522	.1uF	Capacitor, Ceramic, 16V, X7R, 10%	0402	C1005X7R1C104K	TDK
3	C1003, C1004, C1005	10uF	Capacitor, Ceramic, 16V, X5R, 10%	0805	GRM21BR61C106KE15L	Murata
8	C1006, C1007, C1008, C506, C507, C508, C509, C510	22uF	Capacitor, Ceramic, 6.3V, X5R, 10%	0805	C2012X5R0J226K	TDK
2	C1019, C519	.1uf	Capacitor, Ceramic, 25V, X7R, 10%	0603	C1608X7R1E104K	TDK
1	C1021	22pF	Capacitor, Ceramic, 50V, COG, 5%	0603	C1608COG1H100D	TDK
2	C1023, C523	4.7uF	Capacitor, Ceramic, 10V, X5R, 10%	0805	C2012X5R1A475K	TDK
2	C1024, C524	1000pF	Capacitor, Ceramic, 50V, X7R, 10%	0603	C1608X7R1H102K	TDK
2	C1025, C525	1uF	Capacitor, Ceramic, 50V, X7R, 10%	0603	C1608X7R1H105K	TDK
1	C1026	0.01uF	Capacitor, Ceramic, 50V, X7R, 10%	0603	C1608X7R1H332K	TDK
1	C1027	3300pF	Capacitor, Ceramic, 50V, X7R, 10%	0603	C1608X7R1H102K	TDK
1	C25	0.1uF	Capacitor, Ceramic, 0.1-uF, 50-V, X7R, 15%	0603	Std	TDK
1	C26	2.2uF	Capacitor, Ceramic, 16V, X7R	0805	std	std
1	C27	0.01uF	Capacitor, Ceramic, 0.01uF, 50-V, X7R, 15%	0603	Std	TDK
1	C3	0.1uF	Capacitor, Ceramic, 25V, X5R, 10%	0603	C1608X5R1E104KC	TDK
1	C500	.1uF	Capacitor, 0.1uF, 6.3V, Ceramic, +/-15%	201	C0603X5R0J104K	TDK
3	C501, C502, C503	10uF	Capacitor, Ceramic, 6.3V, X5R, 10%	0805	GRM21BR60J106KE15L	Murata
1	C521	68pF	Capacitor, Ceramic, 68p, 50V, COG, 5%	0603	std	std
1	C526	0.01uF	Capacitor, Ceramic, 0.01u, 50V, X7R, 10%	0603	std	std
1	C527	3900pF	Capacitor, Ceramic, 3900p, 50V, X7R, 10%	0603	std	std
2	J1000, J500	ED555/2DS	Terminal Block, 2-pin, 15-A, 5.1mm	0.40 x 0.35 inch	D120/2DS	OST
1	J7	ED1609-ND	Terminal Block, 2-pin, 15-A, 5.1mm	0.40 x 0.35	ED1609	
1	L1000	47uH	Inductor, SMT, 1.15A, 216milliohm	0.300 sq"	DR74-470-R	Coiltronics
1	L1001	OPEN	Inductor, SMT, yyA, zzmilliohm	0.255 x 0.270 inch	IHLP2525CZ-01	Vishay
1	L500	3.3uH	Inductor, SMT, 3.39A, 18.3milliohm	0.300 sq"	DR74-3R3-R	Coiltronics
2	Q1001, Q501	2N7002DICT	MOSFET, N-ch, 60-V, 115-mA, 1.2-Ohms	SOT23	2N7002DICT	Vishay-Liteon
2	Q2, Q3	FDS8978	MOSFET, NCh 30V, 7.5A , 18 milliOhm	S08	FDS8978	Fairchild
1	R1	249k	Resistor, Chip, 1/16-W, 1%	0603	Std	Std
2	R1000, R500	4.75K	Resistor, Chip, 1/16W, 1%	0402	Std	Std
2	R1001, R501	3.3	Resistor, Chip, 1/10W, 1%	0805	Std	Std
1	R1002	11.8K	Resistor, Chip, 1/16W, 1%	0603	Std	Std
	R1003	10K	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R1004	95.3	Resistor, Chip, 1/16W, 1%	0603	Std	Std
2	R1005, R505	49.9	Resistor, Chip, 1/16W, 1%	0603	Std	Std
2	R1006, R506	OPEN	Resistor, Chip, 1/16W, yy%	0603	Std	Std
1	R1007	2.15K	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R2	210k	Resistor, Chip, 1/16-W, 1%	0603	Std	Std
1	R3	649k	Resistor, Chip, 1/16-W, 1%	0603	Std	Std
2	R33	10k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R502	4.02K	Resistor, Chip, 4.02k, 1/16W, 1%	0603	Std	Std
1	R503	10K	Resistor, Chip, 10k, 1/16W, 1%	0603	Std	Std
1	R504	66.5	Resistor, Chip, 66.5ohms, 1/16W, 1%	0603	Std	Std
1	R507	9.53K	Resistor, Chip, 9.53K, 1/16W, 1%	0603	Std	Std
1	R608	2	Resistor, Chip, 1/16W, 1%	0402	Std	Std
2	S5, S10	EG1218	Switch, SPDT, Slide, PC-mount,	0.457 x 0.157 inch	EG1218	E_Switch
2	TP1, TP2	5011	Test Point, Black, Thru Hole	0.125 x 0.125 inch	5011	Keystone
14	TP28, TP30, TP1000, TP1001, TP1003, TP1005, TP1006, TP1007, TP500, TP501, TP503, TP505, TP506, TP507	5000	Test Point, Red, Thru Hole Color Keyed	0.100 x 0.100 inch	5000	Keystone
5	TP29, TP1002, TP1004, TP502, TP504	5001	Test Point, Black, Thru Hole Color Keyed	0.100 x 0.100 inch	5001	Keystone
2	U1000, U500	TPS40192DRC	IC, Cost Optimized Mid Vin High Freq. Sync. Buck controller	DRC10	TPS40192DRC	TI
1	U2	TPS3803-01DCK	IC, Voltage Detector	SOP-5 (DCK)	TPS3803-01DCK	TI
1	U5	TPS73018DBVR	IC, UltraLow-Noise, High PSRR, Fast RF 200 mA, LDO Regulator	SOT23-6	TPS73018DBVR	TI

9/17/2008

## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

**DM643x – TPS40192 & TPS73018 - (PMP4025-RevA)**  
**9/17/08**

The following test report includes measurements for the following output voltage rails for 5V input:

A. **Start Up Waveform for all outputs**  
**1.2V @ 1.48A Using the TPS40192 Device**

1. Output Voltage Ripple (Measured Full Load)
2. Load Transient (50% to 100%, Load Step)
3. Load Regulation
4. Efficiency
5. Switch Node
6. Frequency Response

C. **3.3V @ 0.18A Using the TPS40192 Device**

1. Output Voltage Ripple (Measured Full Load)
2. Load Transient (25% to 100% Load Step)
3. Load Regulation
4. Efficiency
5. Switch Node
6. Frequency Response


D. **1.8V @ 0.14A Using the TPS73018 Device - LDO**  
**1. Output Voltage Ripple (Measured Full Load)**  
**2. Load Transient (50% to 100% Load Step, & 25% to 100% Load Step)**

9/17/2008

## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

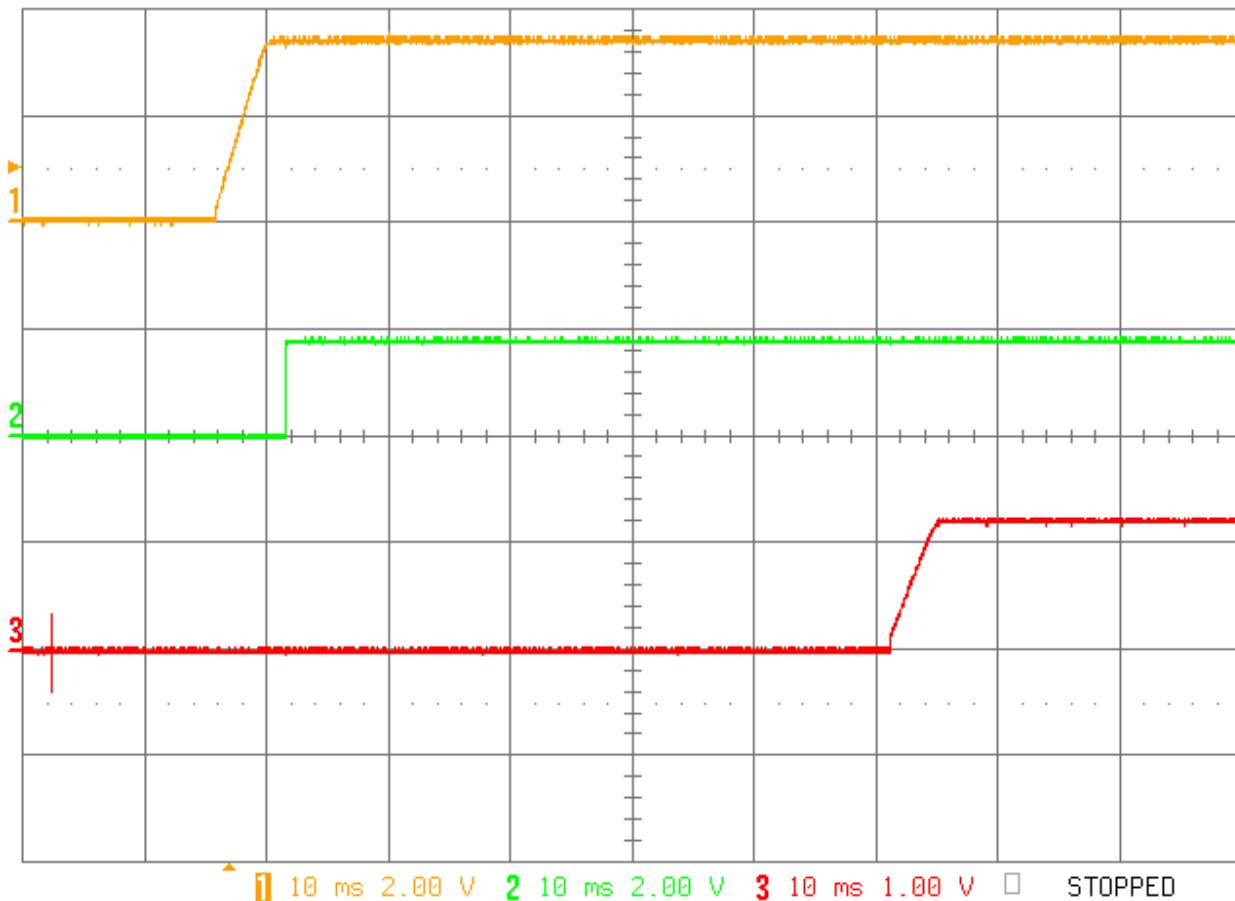**A Start Up Waveform All Outputs – TPS 40192 (x2) & TPS 73018**

Sequence is 3.3V, 1.8V and 1.2V, with 5V input



9/17/2008

## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report


**A 1.2V @ 1.48A – TPS 40192 – DCDC****1 Output Ripple Voltage**

The photo below shows the output voltage ripple. The input voltage is 5V.

Channel 1: 1.2V Output - Orange (20mV/Division; AC Coupled)

Channel 2: 1.2V Output – Green (2V/Division, DC Coupled)

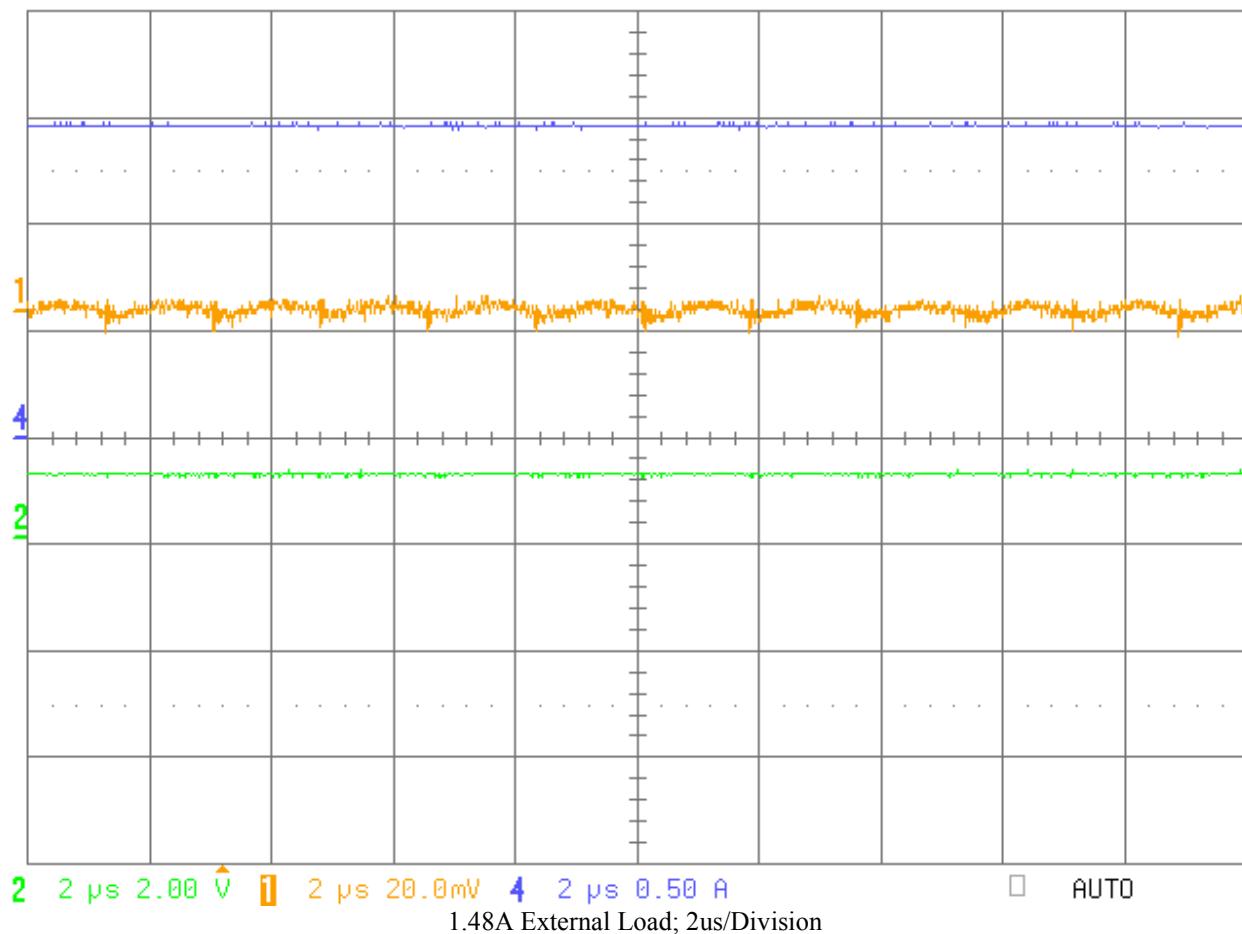Channel 4: Output Current – Blue (0.5A/Division. DC Coupled)



9/17/2008

# DM643x – TPS40192 (x 2) & TPS73018 Test Report


## 2 Load Transients – TPS 40192 – DCDC 1.2V@1.48A

The photo below shows the transient response. The current is pulsed from 0.75A to 1.48A. The input voltage is 5V. The time-base is set to 500us/Division.

Channel 1: 1.2V Output - Orange (20mV/Division; AC Coupled)

Channel2: 1.2V Output – Green (2V/Division, DC Coupled)

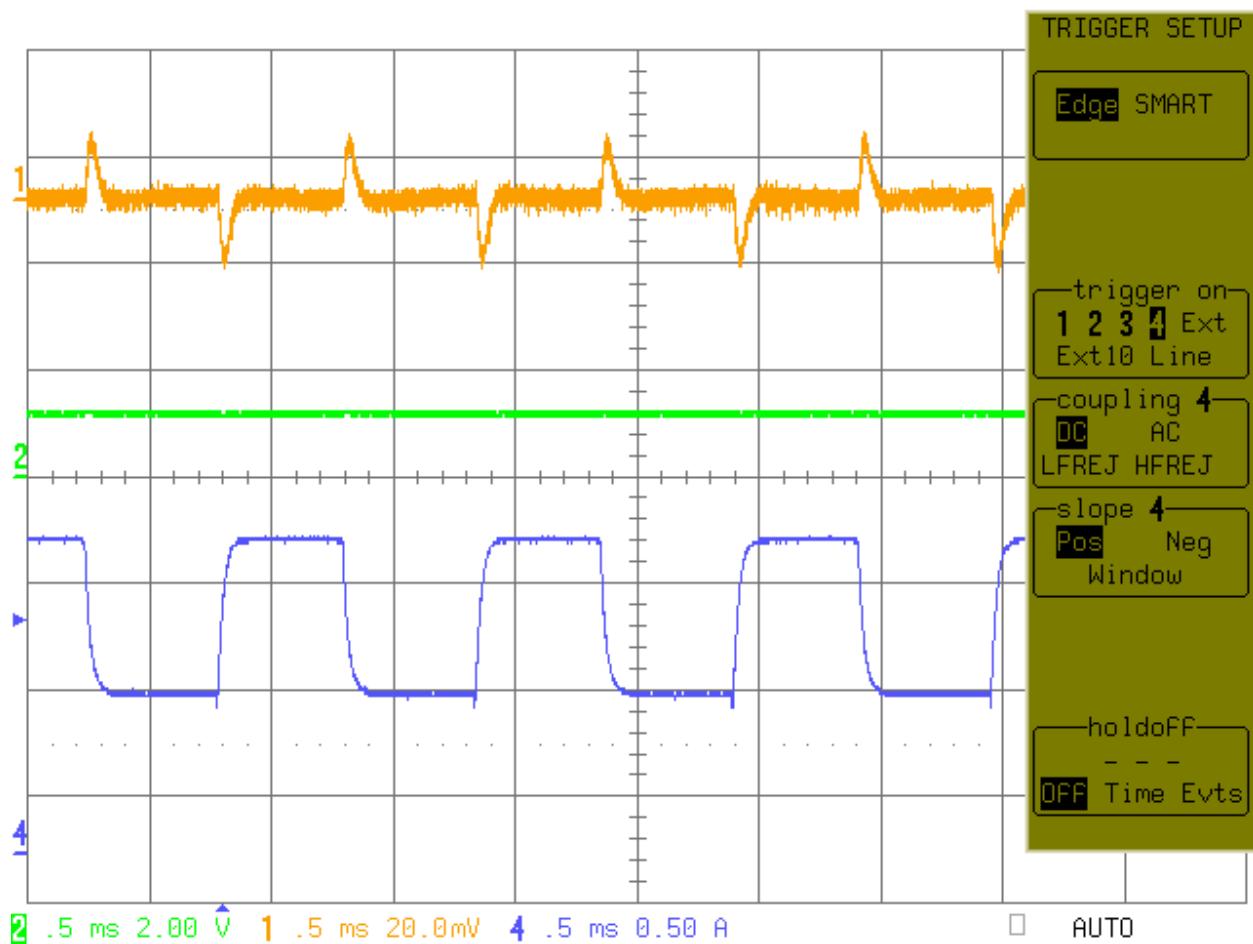Channel 4: Output Current - Blue (0.5A/Division)




9/17/2008

## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

### 3 Load Regulation – TPS 40192 - DCDC

The load regulation is shown in the figure below. The input voltage is 5V.
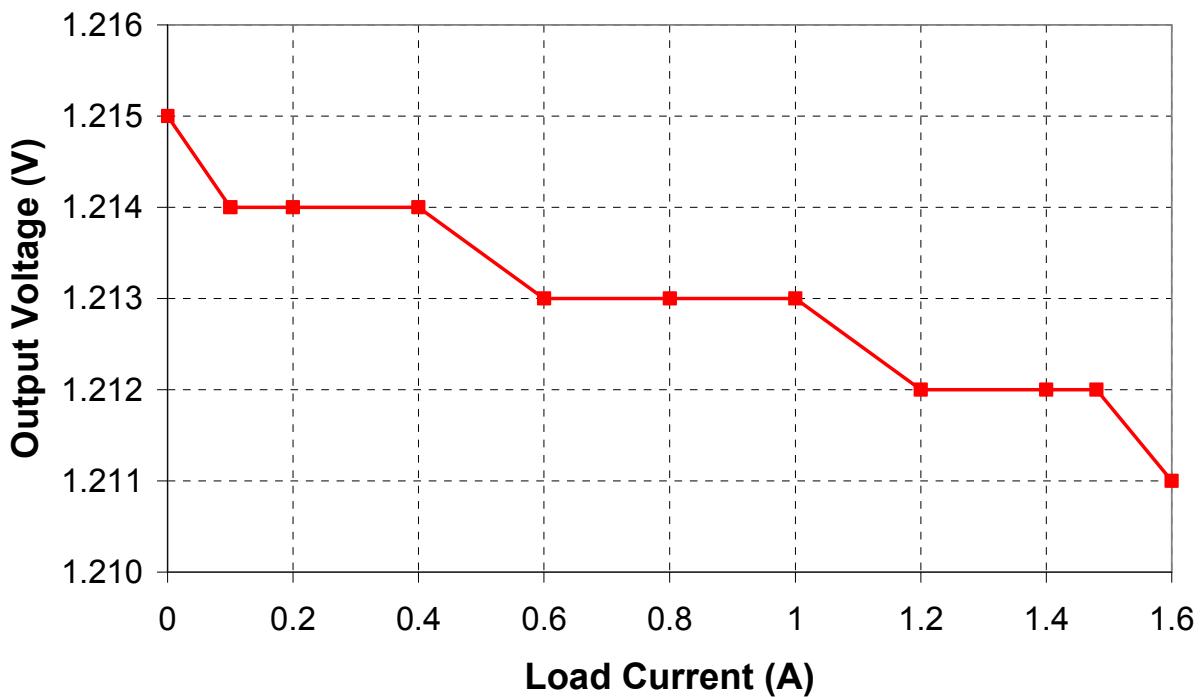
#### 1.2V@1.48A Output Voltage vs. Load Current




9/17/2008

## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

**4 Efficiency – TPS 40192 - DCDC**

The efficiency is shown in the figure below. The input voltage is 5V.

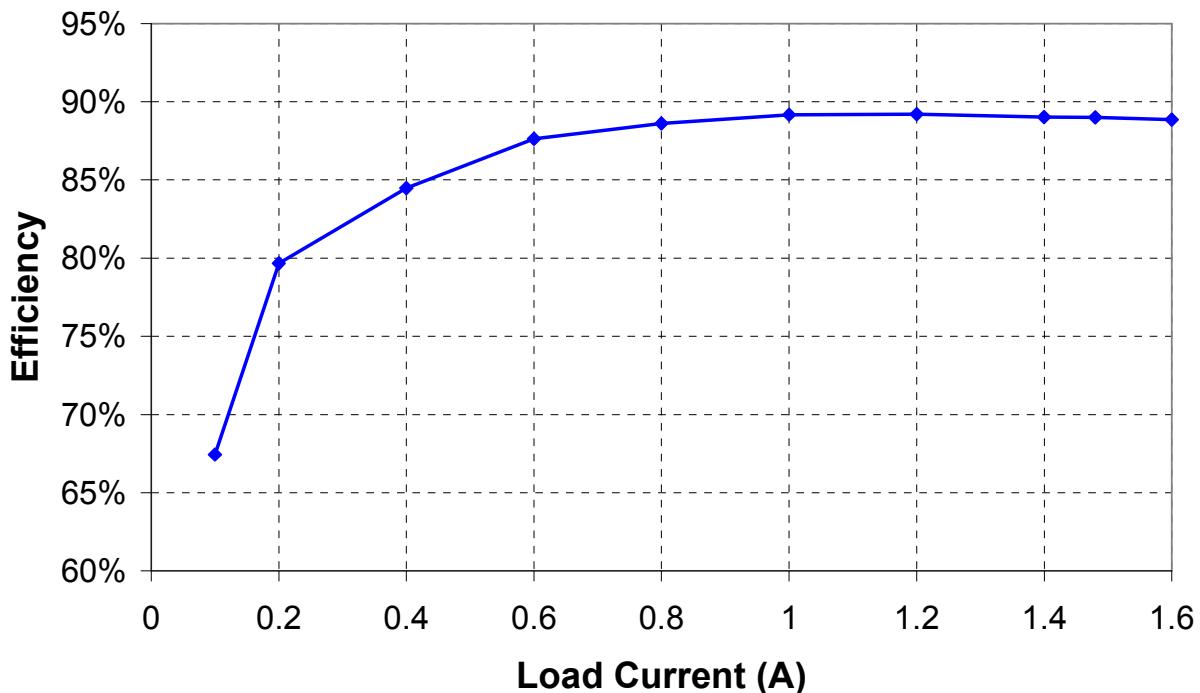**1.2V@1.48A Efficiency vs. Load Current**

9/17/2008


## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

**5 Switch Node Waveforms – TPS40192 – 1.2V@1.48A**

The plot below shows the switching waveforms for the converter. The input is 5V.

Channel 2: Switch Node - Green (2V/Division)

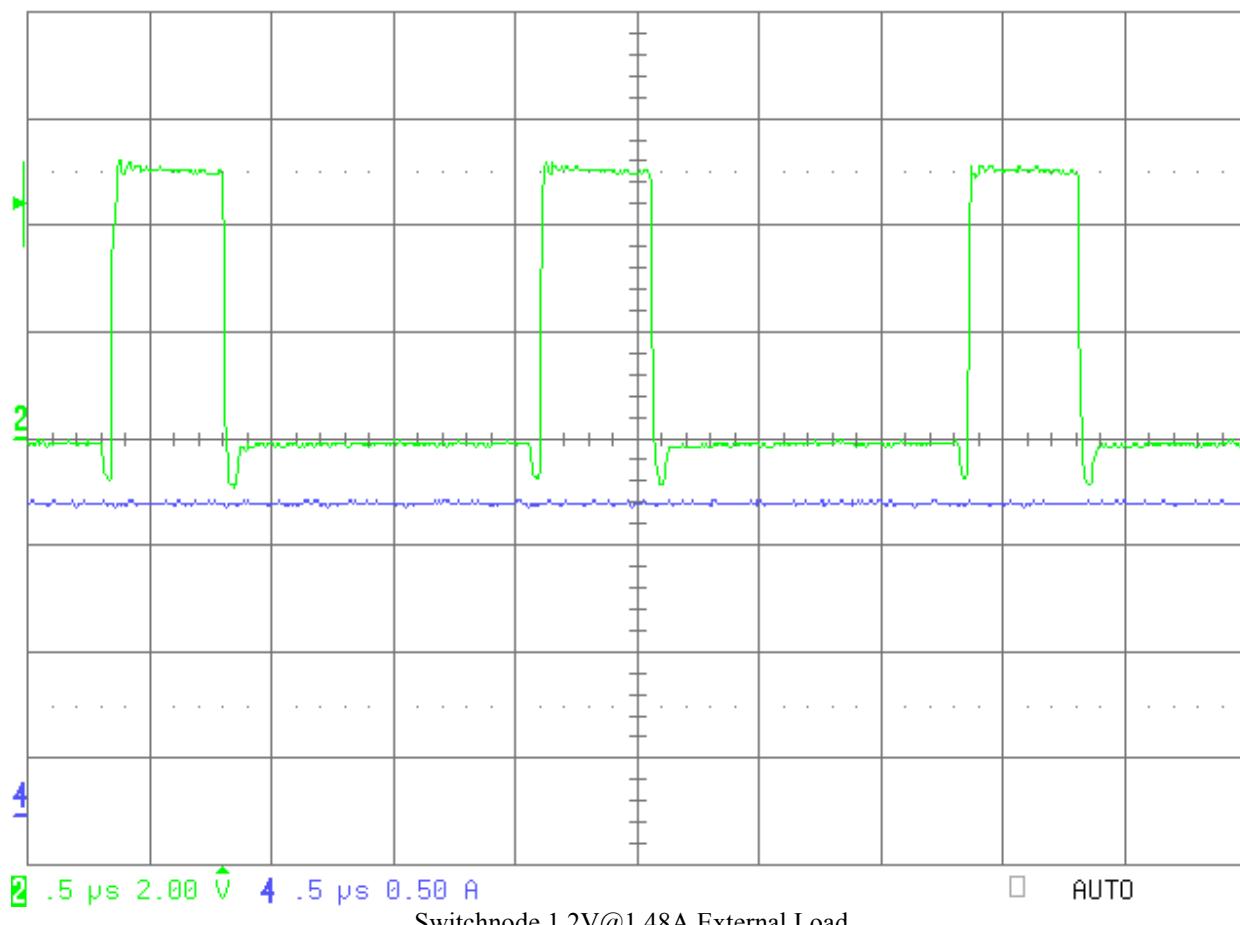Channel 4: Load Current – Blue (0.5A/Division)



9/17/2008


# DM643x – TPS40192 (x 2) & TPS73018 Test Report

## 6 Frequency Response – TPS 40192 – 1.2V@1.48A

The input voltage is 5V.

Cross over frequency : 53kHz

Phase Margin: 73.4deg

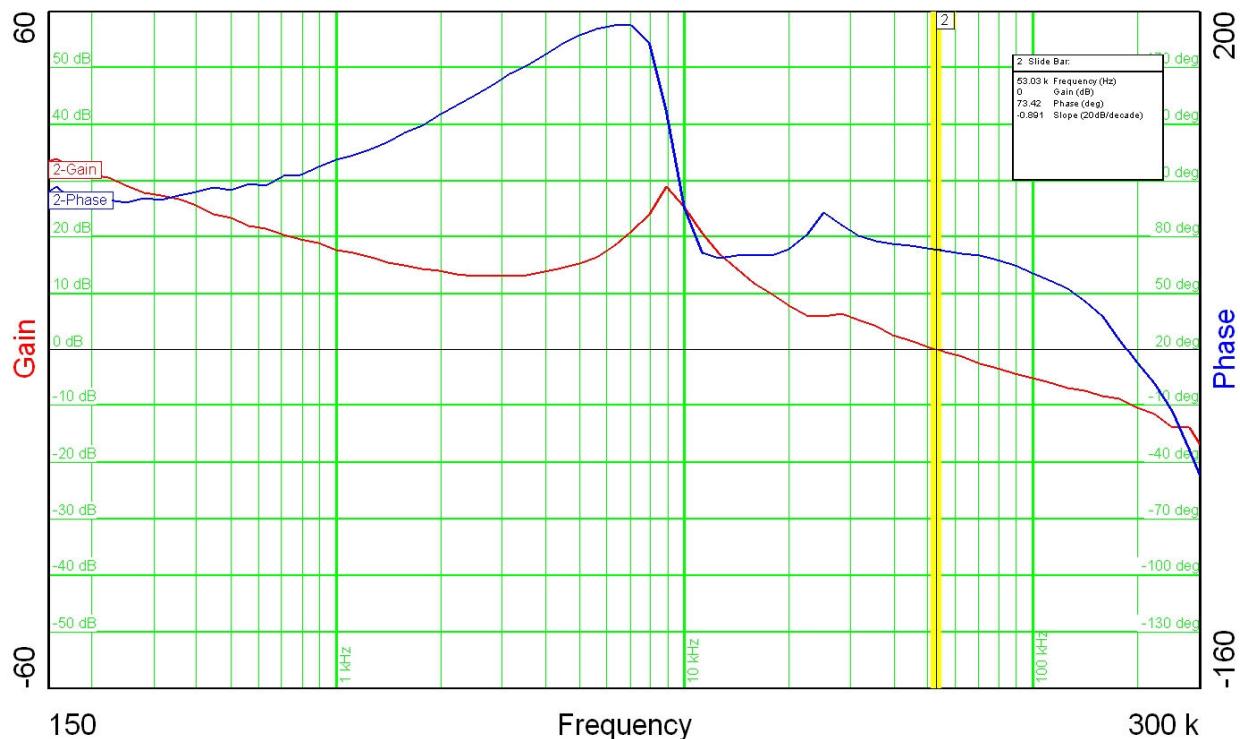


9/17/2008

## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

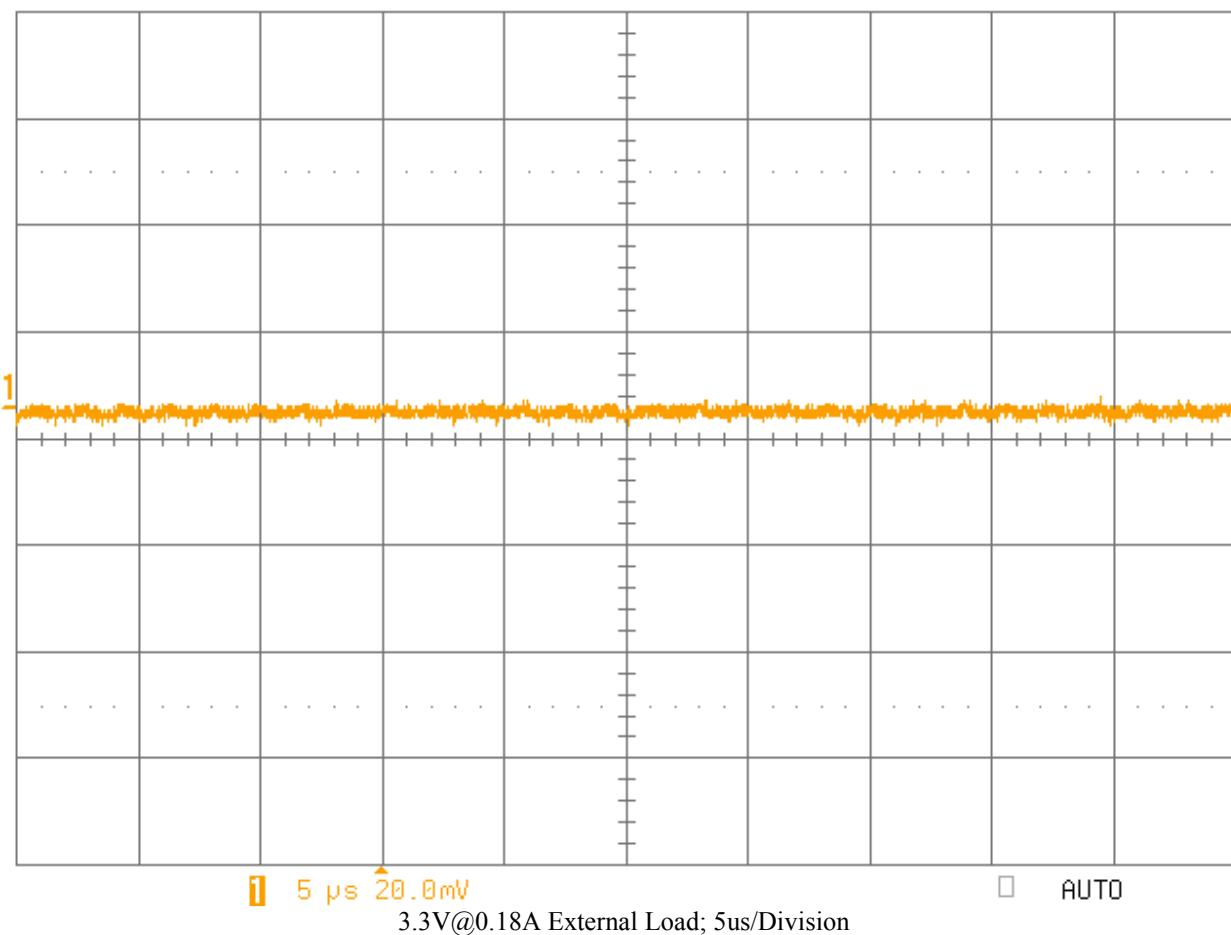**B 3.3V @ 0.18A – TPS 40192 – DCDC****1. Output Ripple Voltage – TPS 40192 – 3.3V@ 0.18A**

The photo below shows the output voltage ripple. The input voltage is 5V.

Channel 1: 3.3V Output - Orange (20mV/Division; AC Coupled)



9/17/2008


## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

**2. Load Transients –TPS 40192 – 3.3V@0.18A**

The photo below shows the transient response. The current is pulsed from 0.045A to 0.18A. The input voltage is 5V. The time-base is set to 200us/Division.

Channel 1: 3.3V Output - Orange (20mV/Division; AC Coupled)

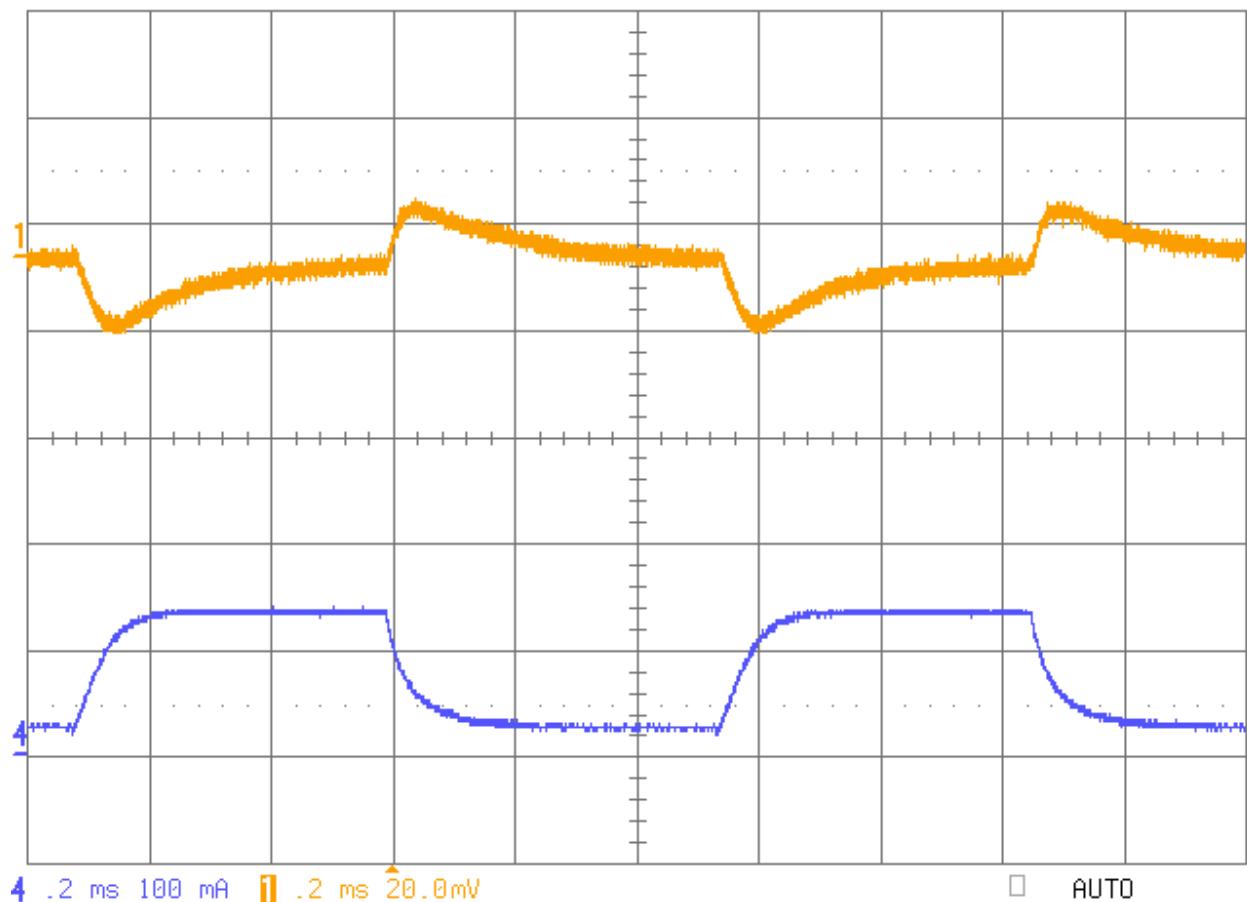Channel 4: Output Current - Blue (100mA/Division)




9/17/2008

## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

**3. Load Regulation – TPS 40192 – 3.3V@0.18A**

The load regulation is shown in the figure below. The input voltage is 5V.

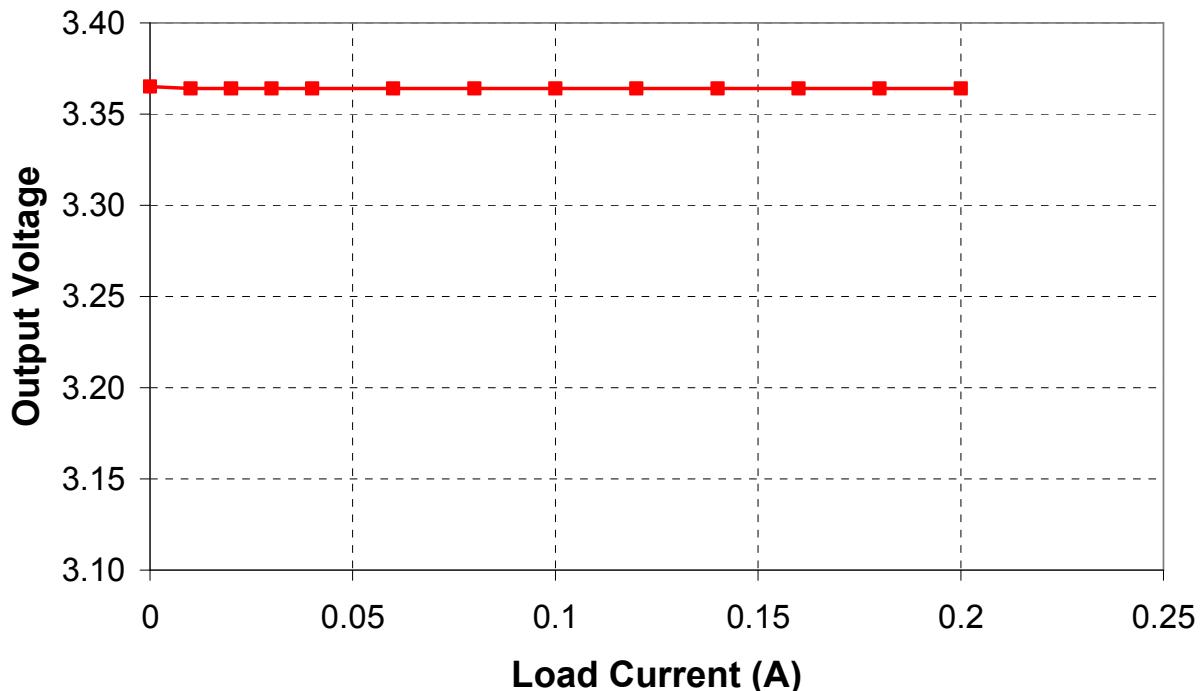
**3.3V @ 0.18A Output Voltage vs. Load Current**

9/17/2008

## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

**4. Efficiency – TPS 40192 – 3.3V@0.18A**

The efficiency is shown in the figure below. The input voltage is 5V.

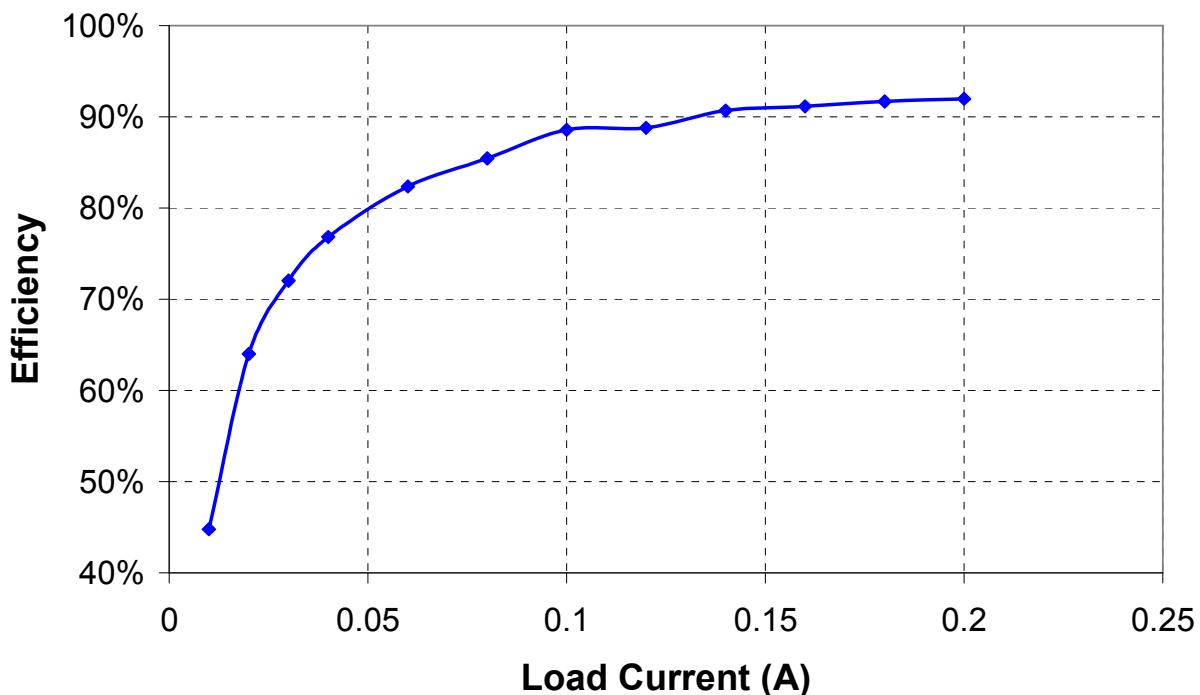**3.3V @ 0.18A Efficiency vs. Load Current**


9/17/2008

# DM643x – TPS40192 (x 2) & TPS73018 Test Report
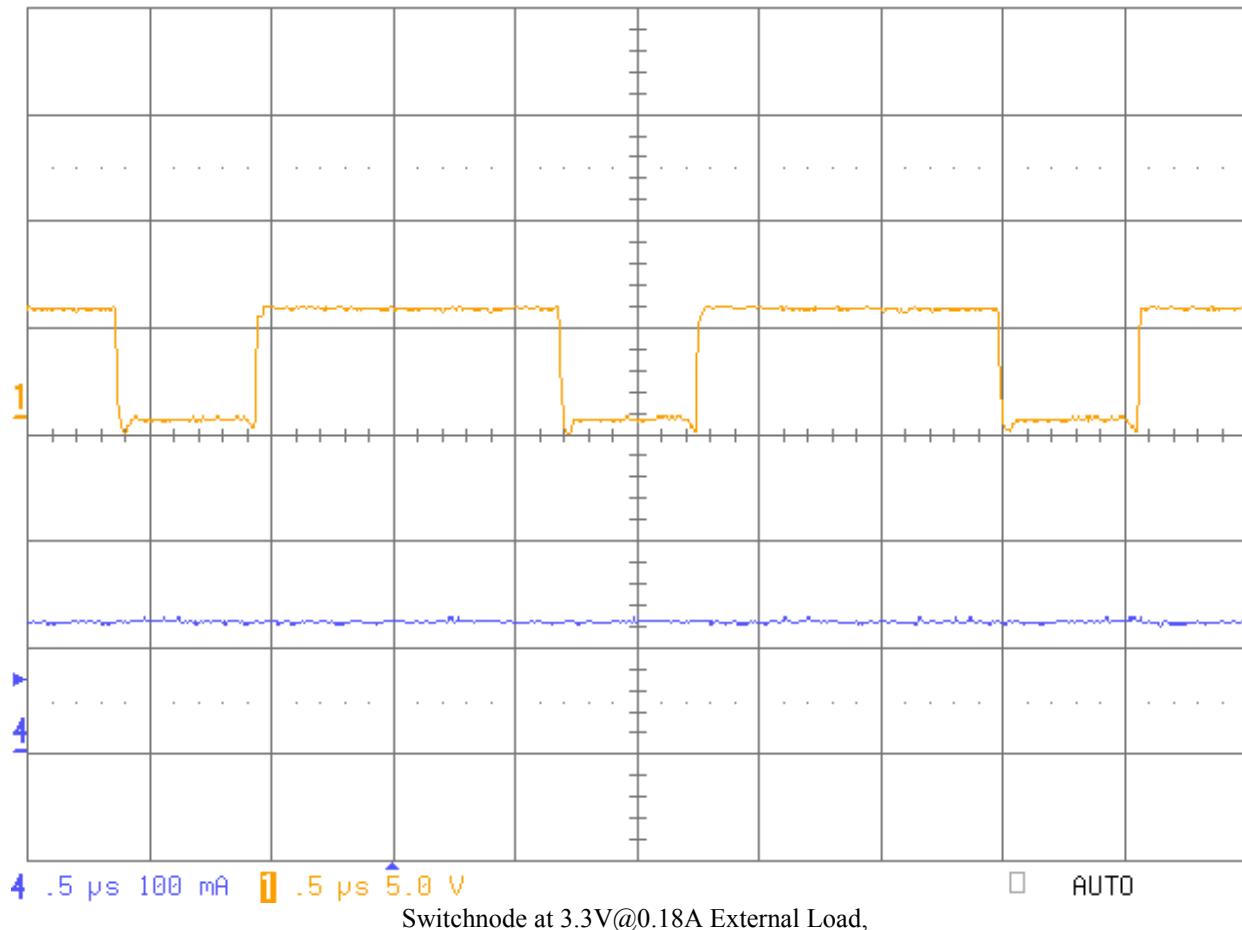
## 5. Switch Node Waveforms – TPS 40192 – 3.3V@0.18A

The plot below shows the switching waveforms for the converter. The input is 5V.

Channel 2: Switch Node - Orange (2V/Division)




9/17/2008

# DM643x – TPS40192 (x 2) & TPS73018 Test Report
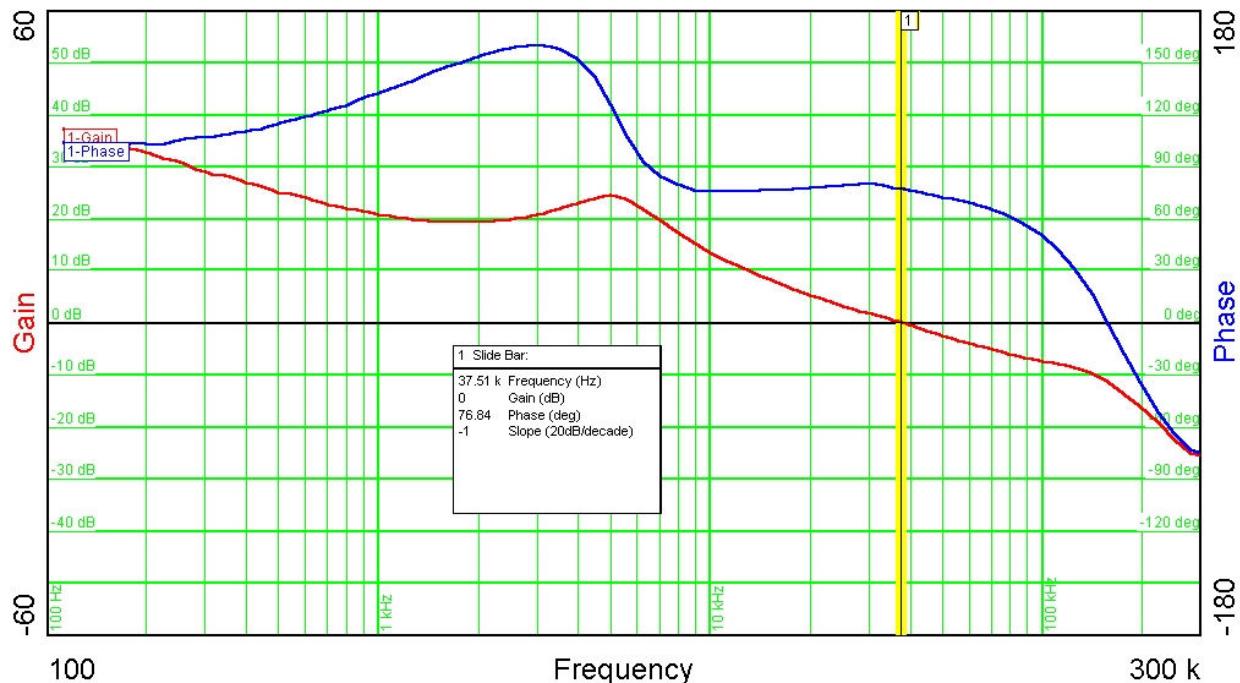
## 6. Frequency Response – TPS 40192 – 3.3V @ 0.18A

The input voltage is 5V.  
 Cross over frequency : 37.5kHz  
 Phase Margin: 76.8deg



9/17/2008


# DM643x – TPS40192 (x 2) & TPS73018 Test Report

## C 1.8V @ 0.14A – TPS 73018 – LDO
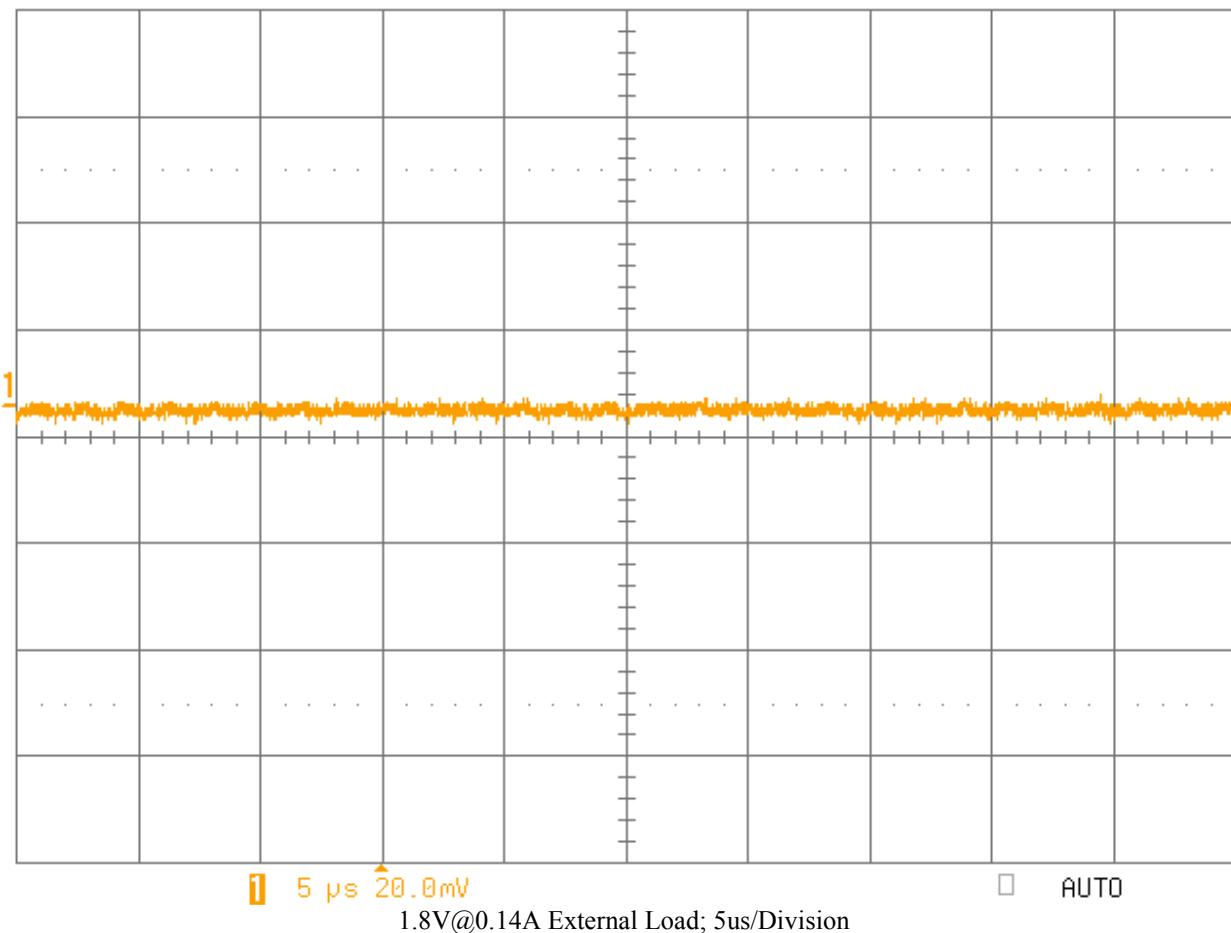
### 1. Output Ripple Voltage – TPS 73018 – LDO, 1.8V@0.14A

The photo below shows the output voltage ripple. The input voltage is 5V.

Channel 1: 3.3V Output - Orange (20mV/Division; AC Coupled)



9/17/2008

## DM643x – TPS40192 (x 2) &amp; TPS73018 Test Report

**2. Load Transients – TPS 73018 – LDO, 1.8V@0.14A**

The photo below shows the transient response. The current is pulsed from 0.02A to 0.04A. The input voltage is 5V. The time-base is set to 100us/Division.

Channel 1: 3.3V Output - Orange (20mV/Division; AC Coupled)  
Channel 4: Output Current - Blue (100mA/Division)

