

Using the bq24650 to Charge LiFePO₄ Battery

Jeff Falin PMP - Portable Power

ABSTRACT

This application report gives an example of using the bq24650 charge management device to provide a high-efficiency, switching-mode charging solution for the LiFePO₄ battery.

The bq24650 integrated circuit was designed to charge single-, two- or three-cell Li-ion and Li-polymer battery packs. Its regulation voltage set point can be easily adjusted by two resistors, which allows the bq24650 to support the newly developed lithium iron phosphate (LiFePO $_4$) battery. This application report gives an example of using the bq24650 to provide a high-efficiency, switching-mode charging solution for LiFePO $_4$ batteries.

The LiFePO₄ battery has many unique features such as very high thermal runaway temperatures, very high discharge current capability, and high charge current. These special features make it more and more attractive in many applications, such as power tools. Figure 1 shows a typical open-circuit voltage (OCV) curve versus depth of discharge (DOD) of an ANR26650M1 LiFePO₄ battery from A123Systems.

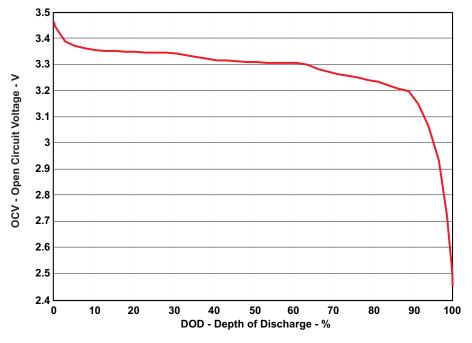


Figure 1. LiFePO₄ Battery OCV Curve

Figure 2 shows the typical discharge characteristics at 25°C. It is able to support a very high discharge rate. The recommended charge voltage is 3.6 V, the charge current is 2 A and the termination current is 200mA.



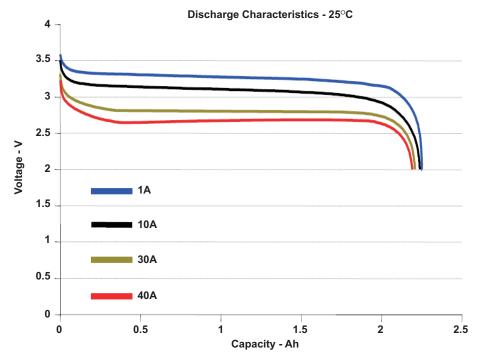


Figure 2. 2 LiFePO₄ Battery Discharge Characteristic at 25°C

One bq24650EVM evaluation module was modified to evaluate the performance for charging LiFePO₄ battery. The design changes are straightforward. The schematic is shown in Figure 3.

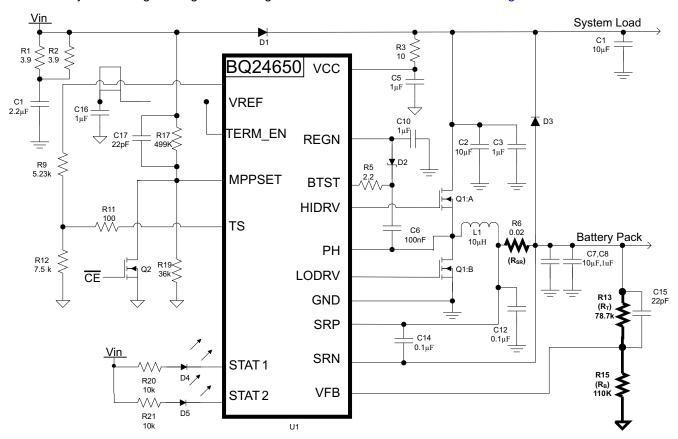


Figure 3. Modified EVM Schematic for LiFePO₄ Battery



The internal reference voltage of the bq24650 is set to 2.1 V for voltage regulation. The resistor value for R13 and R15 can be easily calculated by the following equations:

$$R_{13} = \frac{\left(V_{\text{CHARGE}} - V_{\text{REFCHARGE}}\right)}{V_{\text{REFCHARGE}}} \times R_{15} = \frac{\left(3.6 - 2.1\right) \times R_{15}}{2.1} = 0.714R_{15}$$

Set R15 = 110k then R13 = 78.6k, so select R13 = 78.7k standard value.

All the other components on the EVM are not changed. The recharge threshold is 50mV below the charger's 2.1-V feedback voltage reference, 2.05V. After the 4.2-V regulation voltage set point is changed to 3.6 V, the recharge voltage threshold changes from 4.1 V to the level that can be calculated by the following equation:

$$V_{RECHARGE} = \frac{V_{REFRECHARGE} \times (R_{13} + R_{15})}{V_{15}} = \frac{2.05 \times (78.7k + 110k)}{110k} = 3.515V$$

This leaves only a 85-mV difference between the regulation set point and the rechargeable threshold, making the IC frequently enter into recharge mode when a small load current is applied. This frequent recharging can be prevented by lowering the recharge voltage threshold by 200 mV, for example, to discharge more energy from the battery before it enters the recharge mode again. The modified schematic is shown in Figure 4.

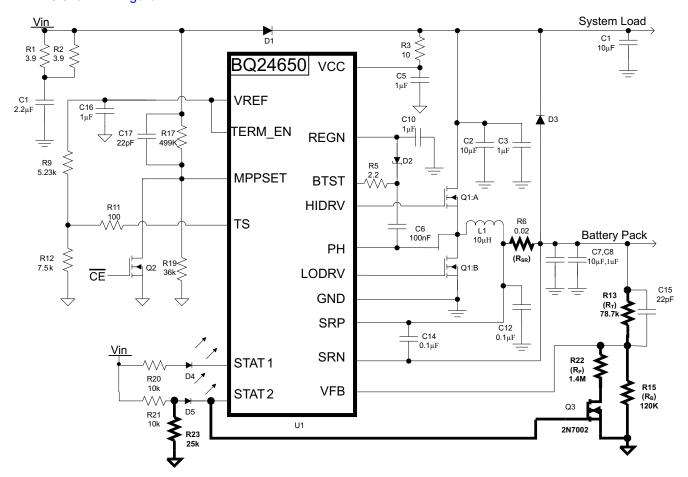


Figure 4. Modified EVM Schematic to Lower Recharge Voltage Threshold for LiFePO₄

In constant current phase, the STAT2 pin is turned off with a high-impedance output. As a result, V_{IN} turns on Q3 through R21 and D5. So, R22 is parallel with R15 to set the voltage regulation to 3.6 V. When the termination current is detected, the STAT2 pin goes low and pulls down the Q3 gate to ground to turn off Q3, R15, and R13 to set the recharge voltage threshold to 3.4 V.



$$R_{15} = \frac{V_{REFRECHARGE} \times R_{13}}{V_{REFCHARGE} - V_{REFRECHARGE}} = \frac{2.05 \times R_{13}}{3.4 - 2.05} = 1.519R_{13}$$

Keep R13 = 78.7k, R15 = 119.5k, so select R15 = 120k standard value.

As a check,

$$R_{\rm 15equ} = \frac{V_{REFCHARGE} \times R_{13}}{V_{CHARGE} - V_{REFCHARGE}} = \frac{2.1 \times R_{13}}{3.6 - 2.1} = 1.4 R_{13}, \, R15 equ = 110.2 k$$
 where R15 equ is the equivalent resistance of R15 parallel with R22.

$$R_{22} = \frac{R_{15} \times R_{15 equ}}{R_{15} - R_{15 equ}} = \frac{120k \times 110.2k}{120k - 110.2k} = 1.35M, \, \text{select R22} = 1.4M \, \text{standard value}.$$

Figure 5 shows a ANR26650M1 LiFePO₄ battery being charged by the circuit in Figure 4.

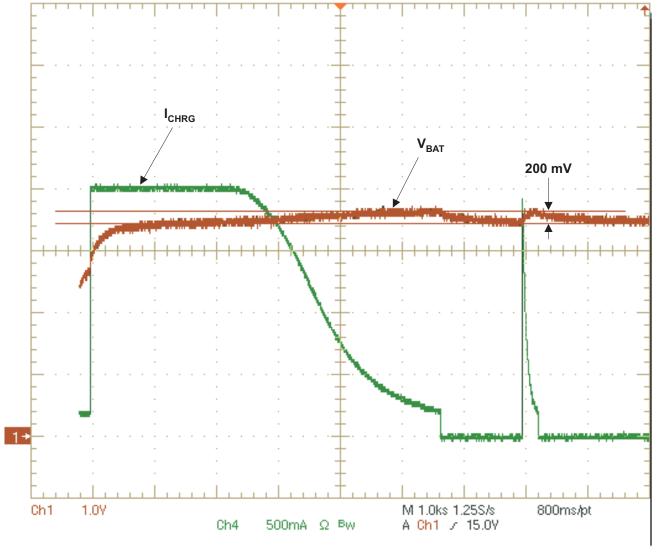


Figure 5. Charging ANR26650M1 LiFePO₄ Battery



www.ti.com

The measured regulation voltage and recharge voltage thresholds are 3.63 V and 3.42 V, respectively. A small load was applied to the battery after the inital charging in order to quickly discharge the battery and initiate a recharge. The voltage difference is increased from 85 mV to 200 mV.

This application report shows how to modify the bq24650EVM Lilon battery charger to be a LiFePO₄ battery charger. The only required changed is to the feedback resistors that set the battery charger regulation voltage. However, only changing the regulation voltage results in the charger beginning to recharge the battery when the battery voltage is only 85mV below the regulation voltage. If the battery is seeing a 1-A discharge rate, the charger begins recharging after only a few seconds. In order to lower the battery recharge threshold, one resistor and one small MOSFET are added, with the MOSFET being controlled by the status output. In this example, a 3.4-V recharge threshold was selected, increasing the difference between the battery regulation and recharge thresholds from 85 mV to 200 mV. In this example, the charger began recharging the battery after a 1 minute and 6 seconds discharge time by 1-A discharge current. The recharge threshold must be selected based on real application conditions, such as system load and battery impedance.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	<u>dsp.ti.com</u>	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps