

Minimizing Switch Ringing on TPS53318 and TPS53319 Family of Devices

Benyam Gebru

ABSTRACT

The system reliability of a high-efficiency DC/DC converter with a fast slew rate is improved when switch node ringing is reduced. This document describes switching ringing reduction methods and lab bench test results with the 14-A TPS53319 and also applies to the pin compatible 8-A TPS53318. Both devices are well-suited for rack-server, single-board-computer, and hardware-accelerator applications that benefit from the fast transient response time of D-CAP™ control, or when multi-layer ceramic capacitors are undesirable for the output filter.

Contents

1	Introduction	2
2	Proper Measurement Method of Switch Ringing	2
3	Minimizing Switch Ringing by Adding RC Snubber and Bootstrap Circuit	5
4	Practical Design	8
5	Adding Bootstrap Resistor	10
6	Affects of Snubber on Efficiency Performance	11
7	Summary	12
8	References	12

List of Figures

1	Single-Ended Probing	2
2	1-GHz Differential Probing.....	3
3	Typical Switch Ringing Waveform of TPS53319 Device	4
4	RC Snubber Added Circuit With Parasitic Components	5
5	TPS53319EVM-136 RC Snubber Placements.....	6
6	Switch Ringing Waveform Rising and Falling Edges	6
7	Switch Node Ringing Waveform Without Snubber	8
8	Switch Ringing Waveforms With Snubber.....	8
9	Switch Node Ringing Waveforms at 14-A Load	9
10	Affect of Boot Resistors on Ringing Voltage When Rbst = 0 Ω, 1.54 Ω, and 3 Ω	10
11	Boot Resistor Effects on Efficiency	11
12	Efficiency Comparison When Snubber Capacitance-Cs Changes	12

List of Tables

1	TPS53319 and TPS53318 Devices: Comparing Ringing Voltage of Three Snubbers.....	10
2	TPS53319 and TPS53318: Comparing Ringing Voltage of three Bootstrap Resistors	10

Trademarks

D-CAP, SWIFT are trademarks of Texas Instruments.
All other trademarks are the property of their respective owners.

1 Introduction

Due to high-voltage changes (dv/dt) and current changes (di/dt) at the high-speed switching MOSFETs, a significant amount of ringing and overshoot voltage can be observed at the switch node of the synchronous buck converter while the high-side MOSFET is turned on. Even though fast-switching speeds help reduce the switching loss, buck converter efficiency still suffers. This application note focuses on minimizing switch ringing on the TPS53k family of devices of SWIFT™ synchronous step-down converters. First, this document describes switching ringing measurement methods. Next the application report describes how to minimize switching ringing by adding an RC snubber circuit and bootstrap resistor. Lastly, the application report describes the effect of the snubber on efficiency performance of the synchronous buck converter.

2 Proper Measurement Method of Switch Ringing

How and where to measure fast switching ringing at buck regulators is crucial. TI highly recommends using a 1-GHz differential probe and it must be probed as close as possible to the switching node and thermal pad-GND. The voltage probe must have a bandwidth of 500 MHz or more. [Figure 1](#) and [Figure 2](#) show two different probing methods used on TPS53k family devices. [Figure 1](#) shows the single-ended, P6139B device, with a 500-MHz passive probe.

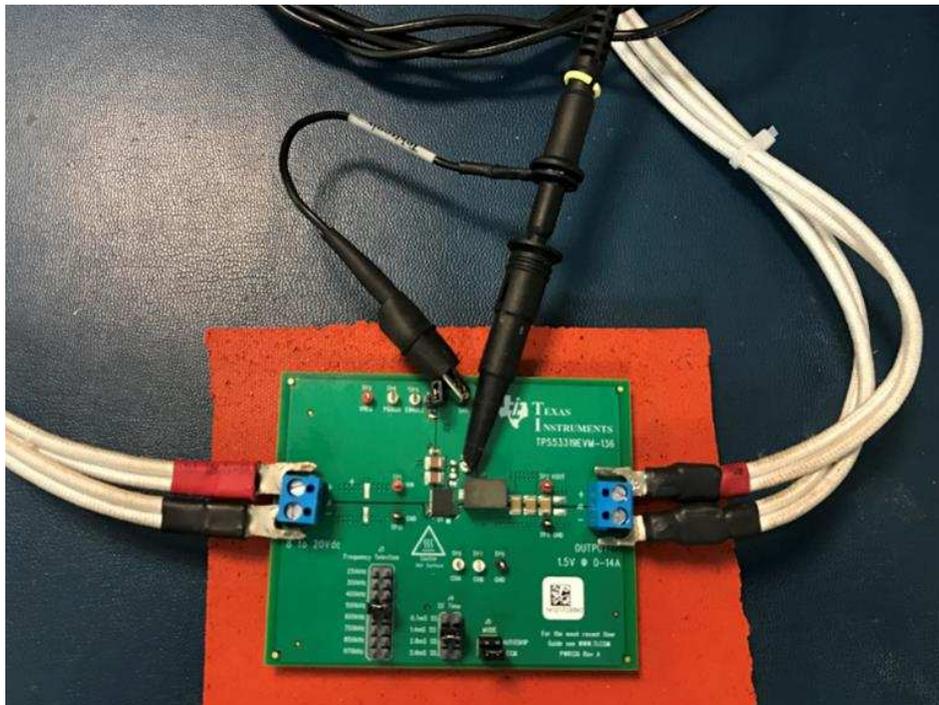


Figure 1. Single-Ended Probing

Figure 2 shows the TDP1000 device, with a 1-GHz differential probe.

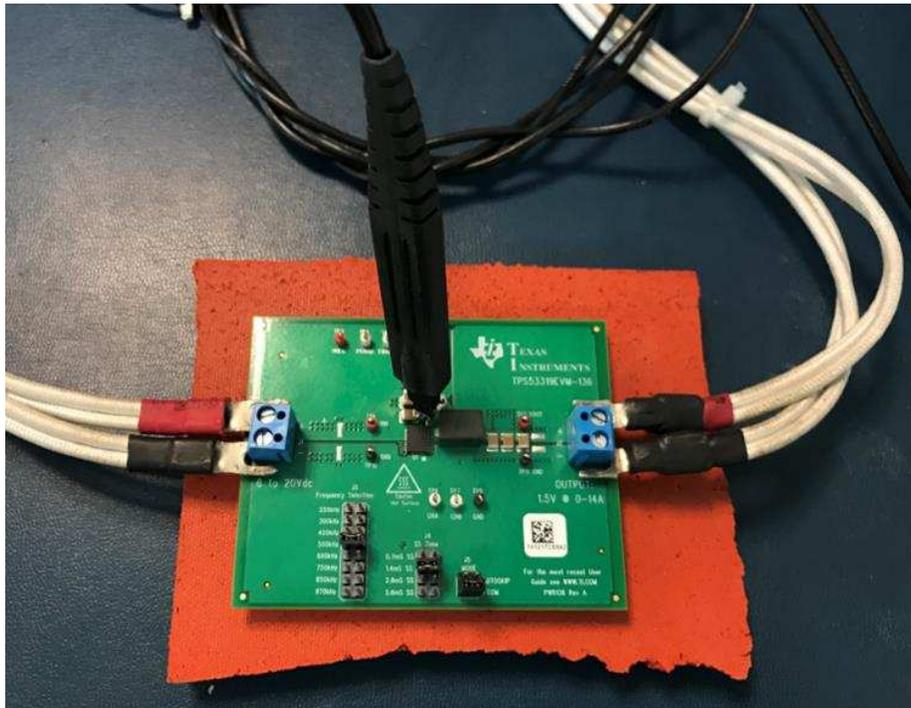


Figure 2. 1-GHz Differential Probing

These probing techniques result in different ringing peak voltages. Because the single-ended probe has 6.5-inch ground wire loop, the probe can pick noises generated from neighboring devices of the system board, which can couple to the switch node voltage. By placing the differential probe close to the IC with two short leads reduces the measurement loop results with less noise coupling to the switch node. Optimal switch ringing can be obtained using this measurement method.

Figure 3 shows a typical switch ringing waveform of the TPS53319 device using a single-ended, 6.5-inch, ground wire loop. The waveform was taken using a single-ended probe at the TPS53319EVM-136 evaluation module (EVM) with 12-V input voltage, 1.5-V output voltage, 14-A load, and 500-kHz switching frequency. The switching peak voltage is 21.76 V; whereas, at the same test condition, using differential probes, the peak switching voltage is 18.4 V. Therefore, improper measurement can result in inaccurate ringing voltage.


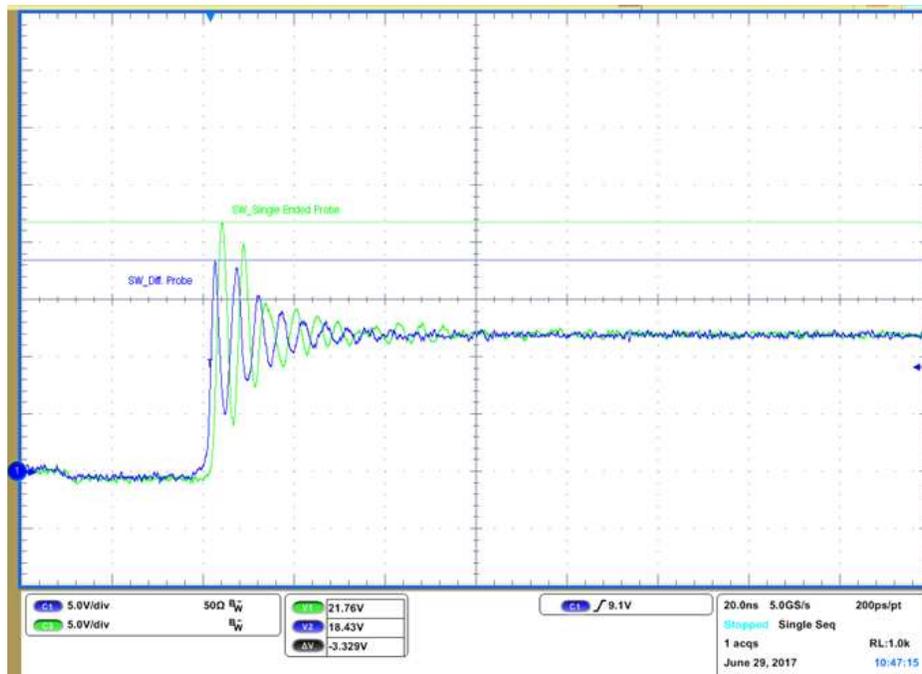


Figure 3. Typical Switch Ringing Waveform of TPS53319 Device

3 Minimizing Switch Ringing by Adding RC Snubber and Bootstrap Circuit

The addition of the RC snubber reduces the switch ringing voltage with a small impact on overall efficiency. This RC snubber is needed to avoid excessive ringing which can cause damage to the devices and high-frequency EMI radiation. The RC snubber must be placed as close as possible to the switch-to-ground pins. Figure 4 and Figure 5 shows the placement of the RC snubber with the parasitic components.

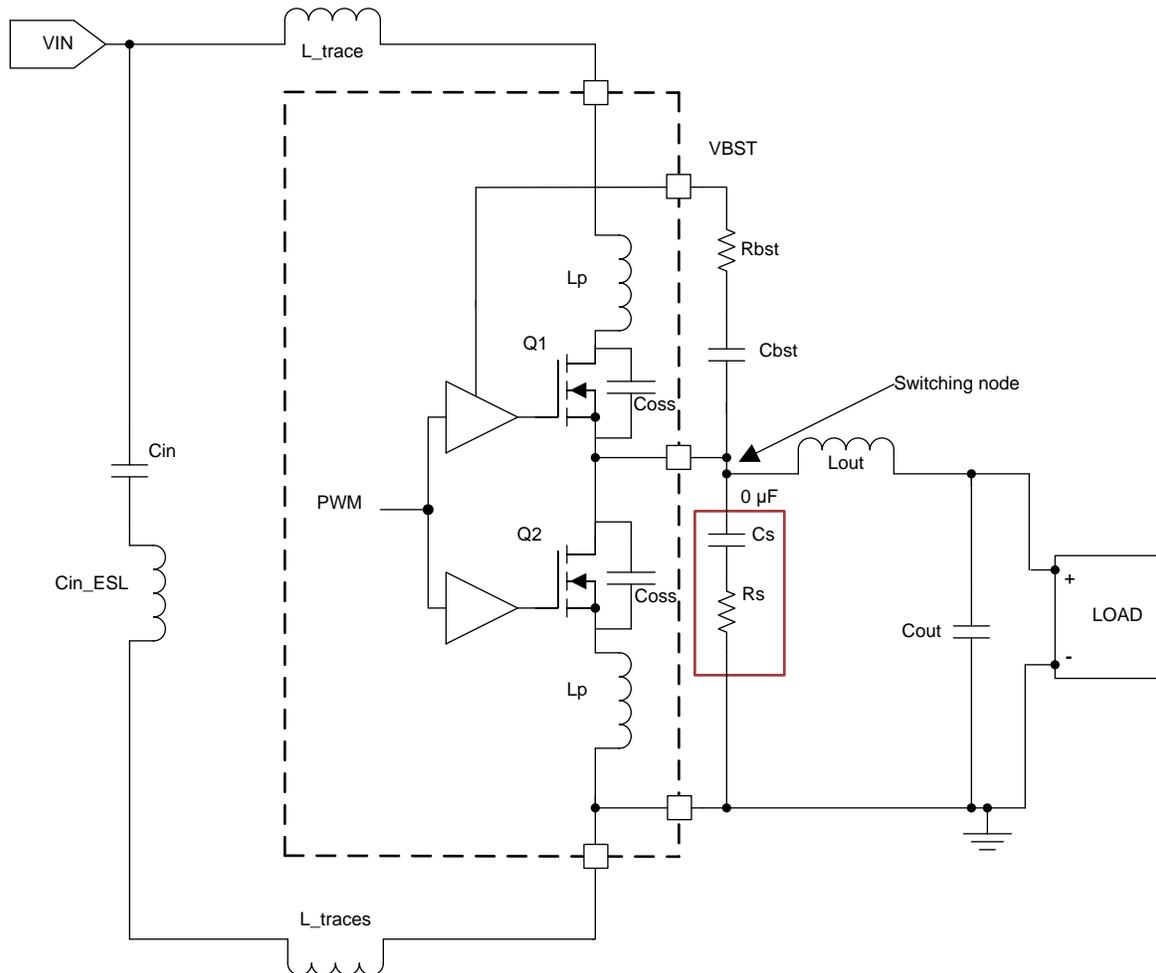

Copyright © 2017, Texas Instruments Incorporated

Figure 4. RC Snubber Added Circuit With Parasitic Components

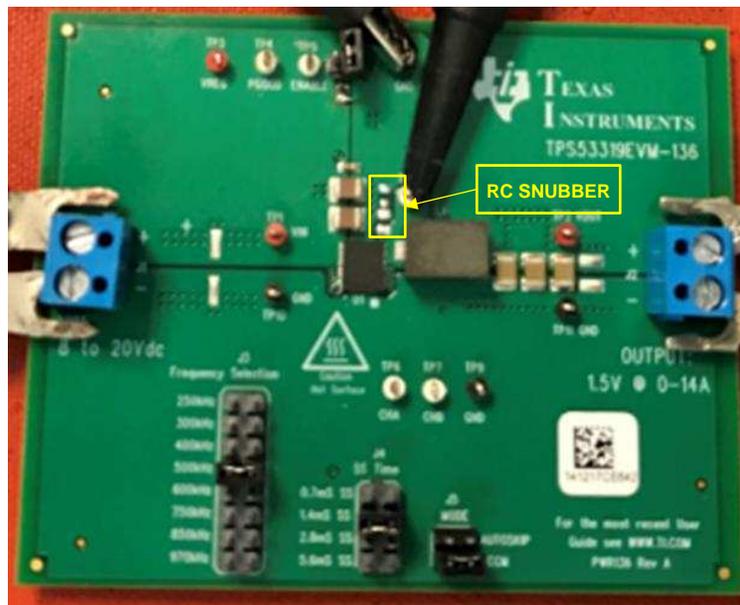


Figure 5. TPS53319EVM-136 RC Snubber Placements

Switch ringing occurs when the high-side MOSFET is on, the low-side MOSFET is off, and with parasitic capacitance and inductance of the internal MOSFETs, which creates a resonance circuit, result in high-frequency switch ringing. Figure 6 shows the rising edge of the switch-on ringing, which is mostly determined by the COSS of the low-side FET and the total parasitic inductance of both FETs switching loop (L_p on both MOSFETs, L_{traces} , and C_{in_ESL}).

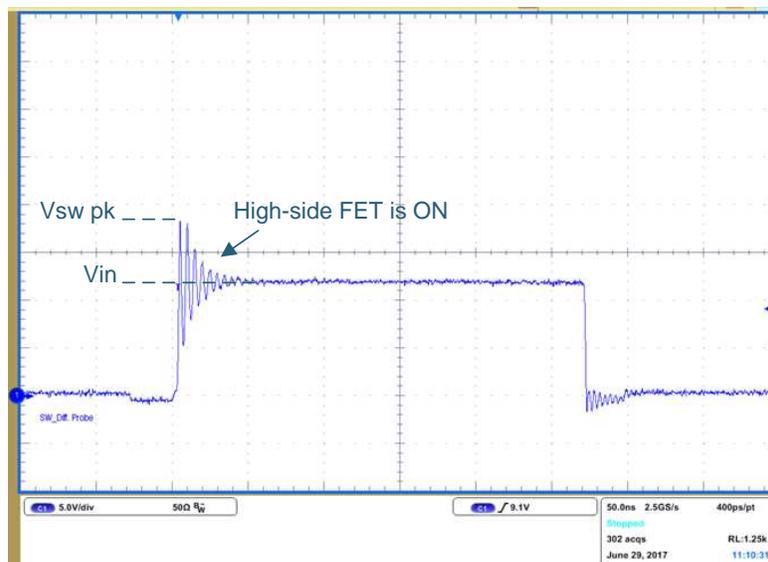


Figure 6. Switch Ringing Waveform Rising and Falling Edges

The parasitic inductance, capacitance, and R_s -snubber values depend on the parasitic inductance and parasitic capacitance, C_p , components of the network. Because of the parasitic value for integrated MOSFETs, the layout parasitic and packaging parasitic, such as wire bond, are unknown. A quick and easy way to determine snubber component values is to measure the ringing frequency (F_{ring}) at the lab bench, then characterize the impedance of the circuit.

3.1 Method of RC Snubber Designing

The following method is used to estimate the RC snubber components.

1. Measure the switch node ringing frequency (F_{ring}) of original circuit without the snubber. Reduce the original ringing frequency in half by adding a small capacitor from the switch to GND.

NOTE: Usually, the added capacitance, which is snubber capacitor, C_s , is chosen to be approximately three times larger than the total parasitic capacitance, C_p . Therefore, the total resonance parasitic capacitor is approximately 1/3 of the added capacitance.

2. Estimate parasitic inductance, L_p , using the original ringing frequency and the ringing frequency after adding the snubber capacitor and two capacitances (C_p and $C_p + C_s$).
3. Estimate the parasitic switch node capacitance, C_p .
4. Finally, determine the snubber resistor, R_s , that is required for optimal damping.

To estimate L_p , the parasitic inductance of the circuit, first measure the switch ringing frequency, $Fring_1$ (T_1), of the original circuit without the snubber. Next, add the external snubber capacitor, C_s , in the circuit (from the switch to GND) and increase the value of the capacitor until the frequency of the ringing to be damped has been reduced by half ($Fring_2$). This means the change of the period (T_2) doubled when changing the original parasitic capacitance, C_p , to $C_p + C_s$.

Estimate parasitic capacitance, C_p , and parasitic inductance, L_p , to calculate the snubber resistor, R_s , that is required for optimal damping. The damping factor, ξ , for the damping response of the LC circuit usually ranges from $\xi < 1$ (under damped) to $\xi = 1$ (critically damped). The value of the snubber resistor is equal to the characteristic impedance of the parasitic resonant circuit and that provides damping near $\xi = 1$.

The characteristics of impedances of the LC circuit can be expressed as follows. Equation 1 shows the natural resonate of the LC frequency.

$$\omega_n = \frac{1}{\sqrt{L_p C_p}} \quad (1)$$

Equation 2 shows the resonate ringing frequency or period without adding an external capacitor.

$$F_{ring_1} = \frac{1}{2\pi\sqrt{L_p C_p}} \quad T_1 = 2\pi\sqrt{L_p C_p} \rightarrow T_1^2 = 4\pi^2 L_p C_p \quad (2)$$

Equation 3 shows the reduced ringing frequency by half (the period doubled) after adding a small capacitor, C_s .

$$F_{ring_2} = \frac{1}{2\pi\sqrt{L_p (C_p + C_s)}} \quad T_2 = 2\pi\sqrt{L_p (C_p + C_s)} \rightarrow T_2^2 = 4\pi^2 L_p (C_p + C_s) \quad (3)$$

Subtract Equation 2 from Equation 3, then manipulate the two equations to find L_p then C_p (see Equation 4 and Equation 5).

$$L_p = \frac{T_2^2 - T_1^2}{4\pi^2 C_s} \quad \text{or} \quad L_p = \frac{1}{4\pi^2 (Fring_2 - Fring_1)^2 C_s} \quad (4)$$

$$C_p \approx \frac{1}{4\pi^2 (Fring_1)^2 L_p} \quad (5)$$

After calculating L_p and C_p , determine the snubber resistor, R_s , that is required for optimal damping. By setting $\xi = 1$, the value of the snubber resistor can be calculated as follows in Equation 6.

$$\xi = \frac{1}{2R_s} \sqrt{\frac{L_p}{C_p}} \quad \text{Damping Factor} \quad R_s = \frac{1}{2\xi} \sqrt{\frac{L_p}{C_p}} \quad (6)$$

4 Practical Design

Figure 7 shows an example of a typical, unsnubbed, $R_{bst} = 0 \Omega$, switch ringing waveform of the TPS53319 D-CAP™ mode, with a 14-A synchronous buck converter that provides a fixed 1.5-V output at up to 14 A from a 12-V input bus. The board is operated at 500-kHz switching frequency, 12 V_{in} and 1.5 V/14 A load. This design example uses the *High Efficiency 14A Synchronous Buck Converter with Eco-Mode™* user's guide.


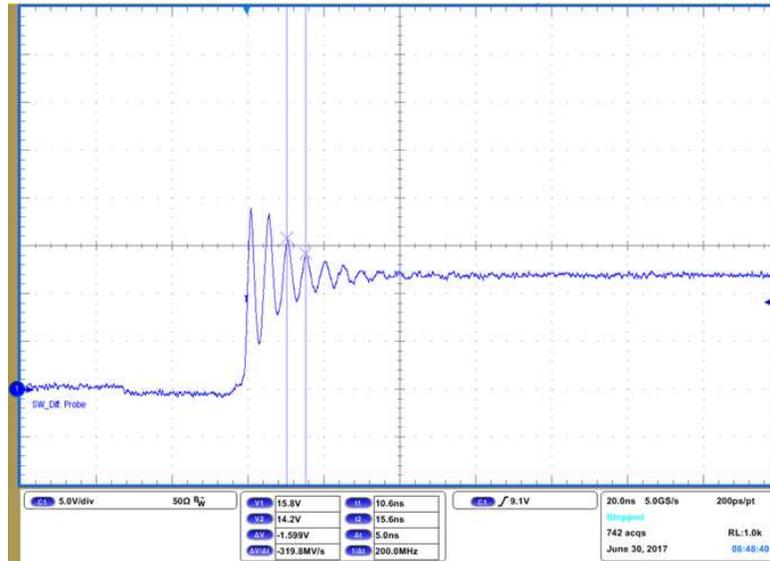


Figure 7. Switch Node Ringing Waveform Without Snubber

Figure 8 shows the unsnubbed switch node with a peak voltage of 19.9 V and a ringing frequency (F_{ring_1}) of 200 MHz.

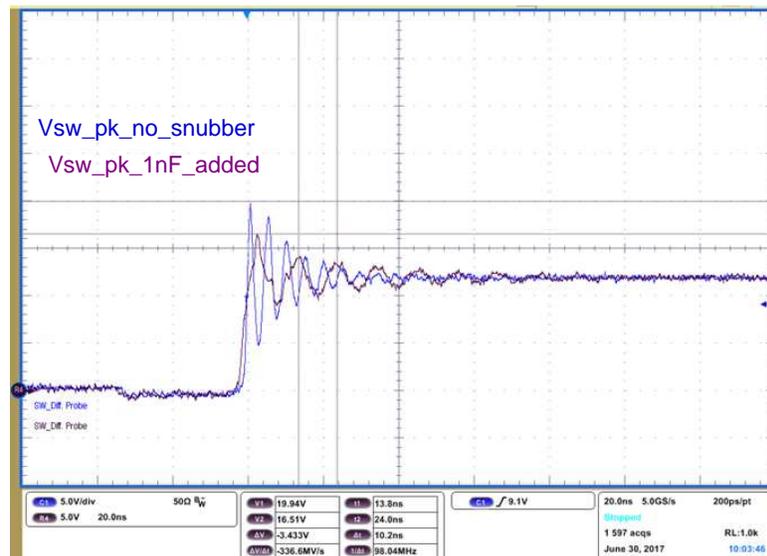

- (1) Purple: 1-nF capacitor added
- (2) Blue: no snubber added

Figure 8. Switch Ringing Waveforms With Snubber

To reduce this original ringing frequency, a small capacitor was added. The goal is to reduce the original ringing frequency in half, by increasing the value of the capacitor. The 1-nF capacitor was chosen and placed from the switch to GND, which reduced the original frequency to 98 MHz (F_{ring_2}) and reduced peak voltage to 16.5 V. Now estimate L_p using the original ringing frequency, F_{ring_1} , and the ringing frequency after adding C_s , F_{ring_2} .

Using Equation 4, the parasitic inductance, L_p , is calculated as 2.43 nH (see Equation 7) and the parasitic capacitance, C_p , is approximately 261 pF (see Equation 8).


$$L_p = \frac{1}{4\pi^2 (98 \text{ MHz} - 200 \text{ MHz})^2 1 \text{ nF}} = 2.43 \text{ nH} \tag{7}$$

$$C_p \approx \frac{1}{4\pi^2 (200 \text{ MHz})^2 2.43 \text{ nH}} = 261 \text{ pF} \tag{8}$$

When L_p and C_p are determined, the snubber resistor, R_s , which is required for optimal damping, is 1.53 Ω , and because 1.53 Ω is not available, an $R_s = 1.54 \Omega$, 0805 chip resistor is used for this example.

$$C_p \approx \frac{1}{4\pi^2 (200 \text{ MHz})^2 2.43 \text{ nH}} = 261 \text{ pF} \tag{9}$$

With the previously calculated RC value, the RC snubber network (1.54 Ω + 1 nF) was placed at the switch to ground and optimum switch node ringing was measured at different load conditions. For instance, at the 14-A load condition, the snubber circuit reduced the switch ringing peak voltage to 17.04 V from 25.4 V. Figure 9 shows the ringing waveforms at a 14-A load with the snubber = 1 nF + 1.54 Ω , and without the snubber.

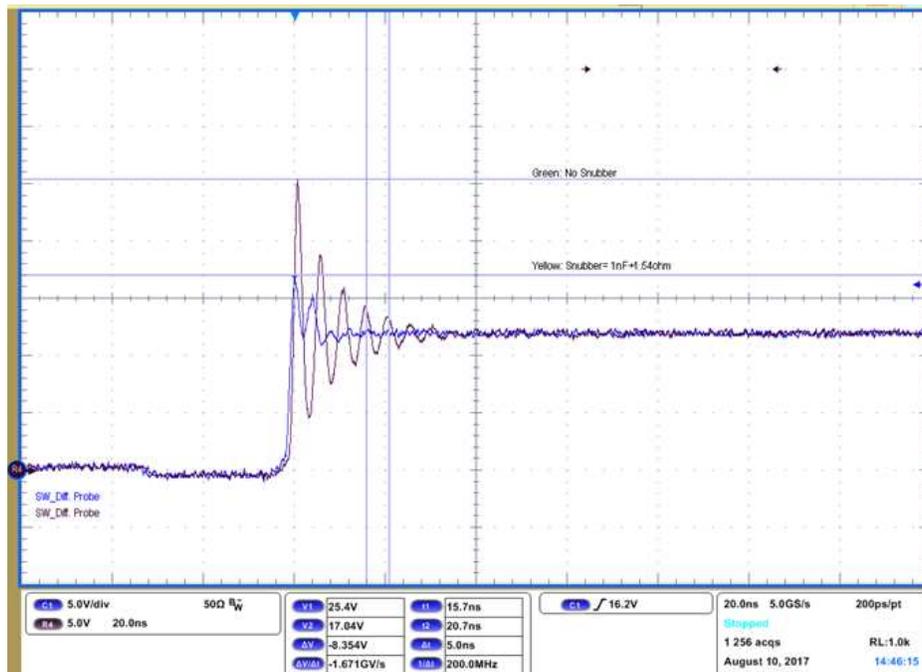

- (1) Blue: With Snubber 1nF+1.54Ω;
- (2) Purple: no snubber

Figure 9. Switch Node Ringing Waveforms at 14-A Load

Table 1 lists different RC snubber configurations test data.

Table 1. TPS53319 and TPS53318 Devices: Comparing Ringing Voltage of Three Snubbers

Test Condition	No Snubber Rbst = 0 Ω + 0.1 μF		Snubber = 1.54 Ω + 1000 pF Rbst = 0 Ω + 0.1 μF		Snubber = 1.54 Ω + 560 pF Rbst = 0 Ω + 0.1 μF	
	Vsw_pk	dV/dt (V/nsec)	Vsw_pk	dV/dt (V/nsec)	Vsw_pk	dV/dt (V/nsec)
V _{IN} = 12 V V _{OUT} = 1.5 V Temperature = 25°C F _{sw} = 500 kHz						
Load = 4 A	18	7.6	14.7	5.05	14.7	5.7
Load = 8 A	22	12.4	15.4	6.2	16	7.0
Load = 14 A	26	16.3	17.5	10.1	18.4	10.35

5 Adding Bootstrap Resistor

Another way to reduce switch ringing is to add a boot resistor, Rbst, in series with the boot capacitor, Cbst, as shown in Figure 4, to slow down the turn-on of the high-side MOSFET. To control the rising rate of the switch node and reduce the V_{sw} ring, add the Rbst = 0 Ω resistor and increase the Rbst resistance until the desired switch node ringing voltage is met. Figure 10 and Table 2 show the switch node ring comparison with the boot resistor = 0 Ω, 1.54 Ω, and 3.01 Ω at the same load conditions. For example, with Rbst = 0 Ω, the peak voltage of the switch node is 24.5 V and 14 V/nsec, and when Rbst = 3.01 Ω, the peak voltage of the switch node is reduced to 18 V and the rising edge is reduced to 10.4 V/nsec.

Table 2. TPS53319 and TPS53318: Comparing Ringing Voltage of three Bootstrap Resistors

Test Condition	Rbst = 0 Ω + 0.1 μF No snubber		Rbst = 0 Ω + 0.1 μF No Snubber		Rbst = 0 Ω + 0.1 μF No Snubber	
	Vsw_pk	dV/dt (V/nsec)	Vsw_pk	dV/dt (V/nsec)	Vsw_pk	dV/dt (V/nsec)
V _{IN} = 12 V V _{OUT} = 1.5 V Temperature = 25°C F _{sw} = 500 kHz						
Load = 14 A	24.5	14	20	11.7	18	10.4

So, increasing the boot resistor affects the turn-on of the high-side MOSFET and the related rising edge of the switch node voltage; however, as shown in Figure 10 adding a higher boot resistor does not affect the ringing frequency.


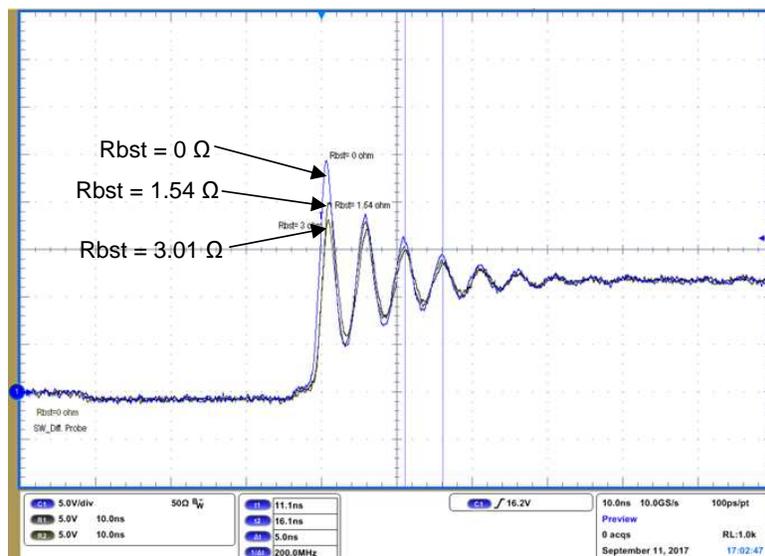


Figure 10. Affect of Boot Resistors on Ringing Voltage When Rbst = 0 Ω, 1.54 Ω, and 3 Ω

Adding a 3.01-Ω boost resistor has little efficiency impact on the converter. As shown in Figure 11, the 3.01-Ω boot resistor does not affect the efficiency at the light load current (< 5 A). Even at a load greater than 5 A, the boot resistor still has little effect on efficiency. With R_{bst} = 3.01 Ω, the efficiency at 14-A load current is 90.37%; however, with R_{bst} = 0 Ω, efficiency at the 14-A load current is 90.67%. Therefore, because increasing the boot resistor slows the MOSFET switch-on timing and increases switching power loss, the efficiency suffers as a result.

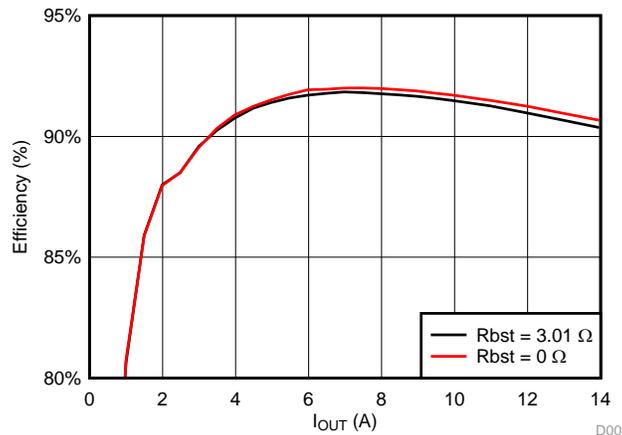

- (1) Black: RBST = 3.01 Ω with 12 V_{IN}, 1.5 V_{OUT}, at 500 MHz and 25°C (no snubber)
- (2) Red: RBST = 0 Ω with 12 V_{IN}, 1.5 V_{OUT}, at 500 MHz and 25°C (no snubber)

Figure 11. Boot Resistor Effects on Efficiency

6 Affects of Snubber on Efficiency Performance

Using Philip Todd's classic paper [2], the power dissipated in R_s can be estimated from the peak energy stored in C_s (see Equation 10).

$$P_{Cs} = \frac{1}{2} C_s V^2_{sw} \tag{10}$$

This is the amount of energy dissipated in R_s when C_s is charged and discharged in each switching cycle. By the principle of conservation of charge, an amount of energy equal to that stored is dissipated. This amount of power dissipation is independent of the snubber resistor; therefore, the average power dissipation at a given switching frequency (F_{sw}), C_s, and charging voltage, V_{sw}, can be estimated as follows (see Equation 11).

$$P_{diss} \approx 2 \left(\frac{1}{2} C_s V^2_{sw} \right) F_{sw} = F_{sw} C_s V^2_{sw} \tag{11}$$

Therefore, the main factor of power loss in the snubber circuit is C_s. It is essential to keep the snubber capacitor as small as possible for less power loss. Increasing C_s increases the power loss. For example, at an 8-A load current using C_s = 1000 pF, the efficiency is 91.62%, and at the same test condition with load current = 8 A with C_s = 330 pF, the efficiency is 91.81%. It is noticeable that using a small snubber capacitor improves the efficiency of the buck converter.

The following data in [Figure 12](#) shows the efficiency performance of the TPS53319 converter using three different snubber capacitance configurations:

- Snubber = 1.54 Ω +1000 pF and Rbst = 0 Ω + 0.1 μ F
- Snubber = 1.54 Ω + 560 pF and Rbst = 0 Ω + 0.1 μ F
- Snubber = 1.54 Ω + 330 pF and Rbst = 0 Ω + 0.1 μ F

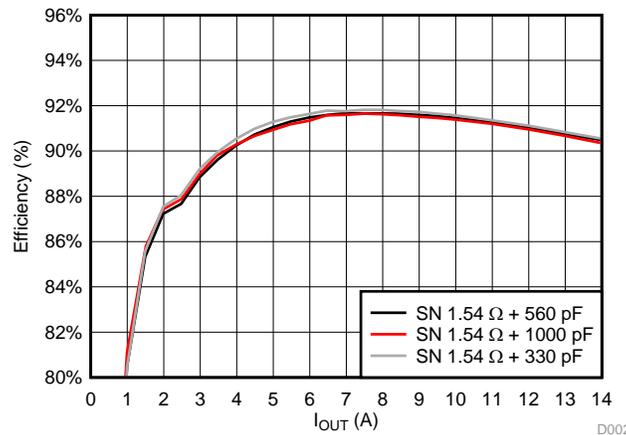


Figure 12. Efficiency Comparison When Snubber Capacitance-Cs Changes

7 Summary

In this application note, the proper measurement of switch node ringing is discussed, which showed that improper measurement can lead to a switch node ringing voltage that is higher than desired. The RC snubber design methods were introduced and examined, to reduce both the amplitude and the ringing frequency of the switch node voltage to acceptable levels. Moreover, this application note showed that the result of adding a boot resistor slows down the turn-on of the high-side MOSFET and reduces the associated rising edge of the SW node voltage. However, the boot resistor does not affect the ringing frequency. Finally, this document has shown the affects on efficiency performance of the synchronous buck converter by using different snubber component values.

8 References

1. Texas Instruments, [High Efficiency 14A Synchronous Buck Converter with Eco-Mode™](#), User's Guide
2. Philip C. Todd, Snubber Circuits: Theory, Design and Practice, Unitrode Power Seminar 900 Topic 2, May 1993.
3. Rudy Severns, [Design of Circuits for Power Circuits](#), Application Note from Cornell Dubilier Electronics, Inc.

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Original (December 2017) to A Revision	Page
• Rewrite the abstract to include end equipment applications.....	1

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated