

High Density Auxiliary Power Supply Using a SiC MOSFET for 800-V Traction Inverters



Eric Reicher
Pei-Hsin Liu

ABSTRACT

A high-voltage to low-voltage backup auxiliary power supply has become prevalent in automotive powertrain applications. This application report discusses key considerations and design guidelines for the backup power supply such as the operating voltage of the switching device, startup circuitry, noise coupling, and high-voltage isolation.

Table of Contents

1 Introduction.....	2
2 Operating Voltage of the Switching Device.....	4
3 Start-Up Circuitry and Comparisons.....	5
4 Current Filtering, Leading-Edge Blanking, and Slope Compensation.....	12
5 High Voltage Isolation.....	14
6 Summary.....	15
7 Related Documentation.....	15

List of Figures

Figure 1-1. Traction Inverter Block Diagram.....	3
Figure 3-1. Typical 1.2-kV NPN-based Active Start-up Circuit.....	5
Figure 3-2. Miniature Active Startup Circuit Using Stacked 600-V Depletion Mode MOSFETs.....	6
Figure 3-3. Solving for the Output Current, I_o	7
Figure 3-4. Simulation of the Depletion Mode Startup Circuit, $V_{IN} = 800\text{ V}$	8
Figure 3-5. Simulation of the Depletion Mode Startup Circuit, $V_{IN} = 800\text{ V}$	9
Figure 3-6. NPN Active Startup at 50 V, 1.3 A Load.....	10
Figure 3-7. NPN Active Startup at 800 V, 2.7 A Load.....	10
Figure 3-8. Depletion Mode Active Startup at 50-V, 1.3-A Load.....	10
Figure 3-9. Depletion Mode Active Startup at 800-V, 2.7-A Load.....	10
Figure 3-10. 2D View Comparing the Area of the Startup Circuits.....	11
Figure 3-11. 3D View Comparing the Heights of the Startup Circuits.....	11
Figure 4-1. Current Filtering, Leading-Edge Blanking, and Slope Compensation.....	12
Figure 4-2. 800 V, 0.25 A Load, $R_{23}=1\text{ k}\Omega$, $C_{21}=10\text{ nF}$	13
Figure 4-3. 800 V, 0.25 A load, $R_{23}=1\text{ k}\Omega$, $C_{21}=10\text{ nF}$	13
Figure 4-4. 800V, 0.25 A Load, $R_{23}=15\text{ k}\Omega$, $C_{21}=2.2\text{ }\mu\text{F}$	13
Figure 4-5. 800V, 0.25 A Load, $R_{23}=15\text{ k}\Omega$, $C_{21}=2.2\text{ }\mu\text{F}$	13
Figure 4-6. Comparison of Light Load Regulation for Two Combinations of R_{23} and C_{21}	14

List of Tables

Table 1-1. Summary of UCC28C5x Variants Supporting SiC MOSFETs.....	2
Table 1-2. Key Parameter Comparisons Between UCC28C4x-Q1 and UCC28C5x-Q1.....	2
Table 2-1. MOSFET Comparisons and Efficiency Improvements from SiC.....	4
Table 3-1. Cost Comparisons Between the Two HV Startup Circuits.....	11

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

The traction inverter efficiently converts DC power from a high-voltage battery to alternating phases of power needed to drive multi-phase motors. Galvanic isolation is required to protect people, as well as the low-voltage components on the cold side of the system, from the high-voltage traction inverter on the hot side of the system. As automotive applications continue to trend in the direction of increased safety, it has become more common to include a high-voltage to low-voltage backup supply in the traction inverter system. The backup power supply powers the low-voltage components if the 12-V battery fails. [Figure 1-1](#) displays an example block diagram featuring the high-voltage to low-voltage redundant power supply.

Also, Silicon Carbide (SiC) MOSFETs are becoming more and more prevalent in the industry too. For an 800V_{TYP} EV/HEV battery system, the primary-side switching device of the isolated bias supply once required two silicon MOSFETs in a cascode configuration. The cascode configuration is employed in TI's [PMP41009](#) reference design. Those two MOSFETs can now be replaced by a single 1700V SiC MOSFET saving component cost, condensing PCB area, and reducing losses to produce higher efficiency.

To operate efficiently with their lowest R_{DS,ON}, SiC MOSFETs require higher gate drive voltages than silicon MOSFETs. To drive SiC MOSFETs reliably and efficiently, Texas Instruments has introduced the new auto-grade UCC28C5x current-mode PWM controllers with higher ABS MAX voltage of the VDD pin (30V) and additional/increased options for the UVLO Start/Stop thresholds, VDD_{ON} and VDD_{OFF} in the data sheet. With 30 V VDD rating, the gate drive voltage at the OUT pin can easily be adjusted to support a variety of SiC MOSFETs with different optimal gate voltage levels, such as 20 V, 18 V, or 15 V. A proper VDD_{OFF} level is also a very critical consideration to avoid the risk of thermal runaway issue of SiC MOSFETs. Compared to the [UCC28C4x](#) family, other improvements include reduced startup and operating currents, and improved accuracy of the reference voltage.

[Table 1-1](#) and [Table 1-2](#) are summaries of the new UCC28C5x-Q1 controllers dedicated to SiC MOSFET applications and their enhancements over the preceding UCC28C4x-Q1 family.

Table 1-1. Summary of UCC28C5x Variants Supporting SiC MOSFETs

UVLO			Maximum Duty Cycle	Temperature (T _J)
Turn On at 18.8 V Turn Off at 15.5 V Suitable for 20-V _{GS} SiC MOSFETs	Turn On at 18.8 V Turn Off at 14.5V Suitable for 18-V _{GS} SiC MOSFETs	Turn On at 16 V Turn Off at 12.5V Suitable for 15-V _{GS} SiC MOSFETs		
UCC28C56H-Q1	UCC28C56L-Q1	UCC28C58-Q1	100%	-40°C to 150°C
UCC28C57H-Q1	UCC28C57L-Q1	UCC28C59-Q1	50%	

Table 1-2. Key Parameter Comparisons Between UCC28C4x-Q1 and UCC28C5x-Q1

Parameter	UCC28C4x-Q1	UCC28C5x-Q1
Supply current at 52 kHz	2.3 mA	1.3 mA
Start-up current	100 μA	75 μA
V _{DD} absolute maximum	20 V	30 V
Reference voltage accuracy	± 2%	± 1%
UVLO and D _{MAX} for Si MOSFET	6 options	6 options
UVLO and D _{MAX} for SiC MOSFET	no options	6 options

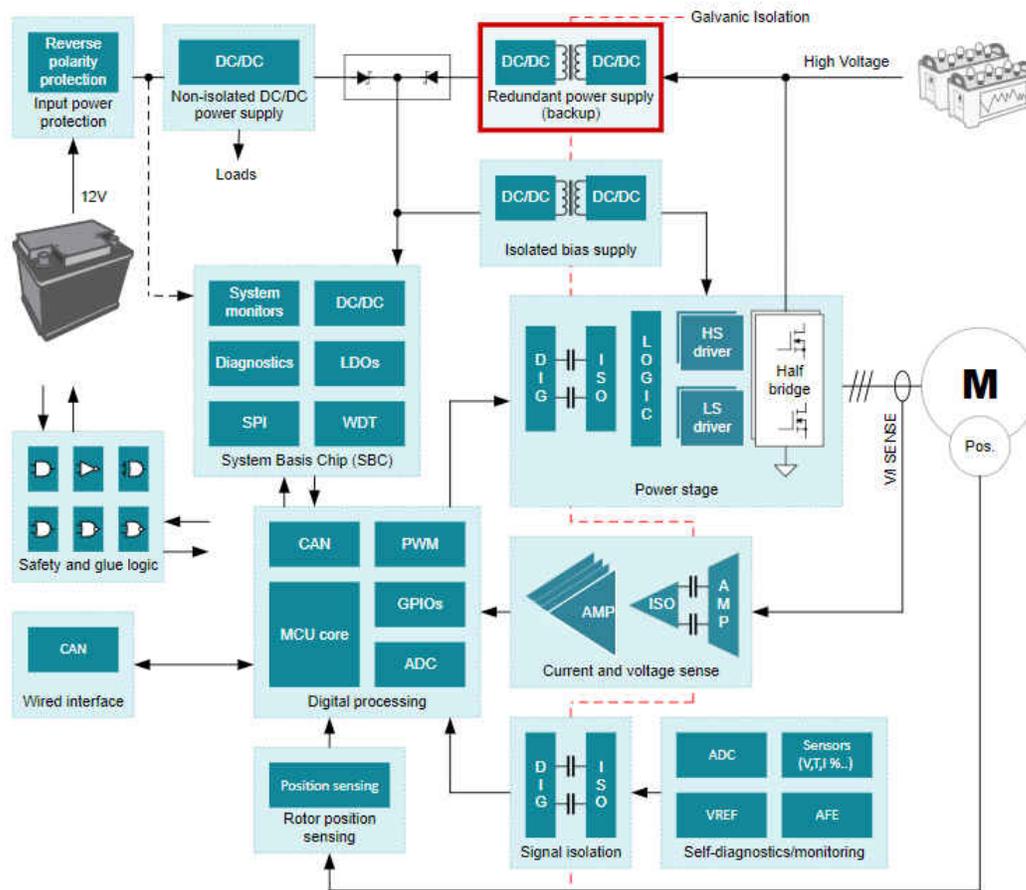


Figure 1-1. Traction Inverter Block Diagram

The high-voltage to low-voltage backup supply presents new challenges compared to the low-input voltage flyback converters tapped from the 12-V battery that currently dominate HEV and EV powertrains. The high-voltage input flyback converter needs to support ultra-wide input voltages. The backup supply needs to operate down to 40 V to support functional safety tests during regenerative braking of the traction motor. This enables engineers and mechanics to work safely. The second safety critical scenario is when the car is towed or pushed (maybe during an accident). In this case the motor becomes a generator and charges up the high voltage input bus capacitor of the traction inverter. In both cases, the backup supply needs to start operation relatively fast to provide the bias power to the isolated gate driver such that the drivers can short the motor windings and prevent the bus capacitor from charging above 60 V. These considerations require the total startup time of the backup supply to be hundreds of milli-seconds, across the range of input voltages.

A 1000 V maximum input-voltage is usually required in 800-V battery systems, considering the battery charged voltage, the AC ripple through the harness, and design margin. Additional challenges, which arise from operating off the high-voltage battery, are selecting a high-voltage power device, minimizing start-up losses, minimizing noise coupling, and ensuring the system meets safety standards.

The flyback topology is the most popular redundant power supply solution due to a low cost, and the ability to support a wide input-voltage range. A controller from the recently expanded and improved UCC28C5x-Q1 family is well suited for this application. When designing a redundant, flyback power supply, all of these design requirements must be addressed.

2 Operating Voltage of the Switching Device

The maximum input voltage must be considered when selecting the power device, since the maximum switch node voltage of the flyback converter is the summation of the input voltage, the reflected output voltage, and the voltage spike. For 800-V battery systems, Silicon Carbide (SiC) MOSFETS are becoming more popular due to their improved figure of merit (FOM) and their high voltage rating, typically 1700 V. Even though there are 1500-V or 1700-V rated silicon MOSFETs on the market, their poor FOM, non-availability of auto-grade, high unit cost, and limited suppliers makes 1.7-kV SiC MOSFETs the more preferable option. [Table 2-1](#) compares the critical parameters between a Si MOSFET and two SiC MOSFETs and quantifies the efficiency gains achieved by the SiC MOSFETs.

Careful consideration must be given to the UVLO turn-off threshold of the SiC-based flyback controller, because it is not only the minimum operating voltage of the controller, but also the gate drive voltage for the SiC MOSFET. For example, a UVLO turn-off greater than 15 V for a 20-V_{GS} SiC MOSFET is recommended to provide increased reliability of the device. Gate drive voltages less than 15 V can cause the power device to operate in the negative temperature coefficient region of turn-on resistance and lose the current balance nature among the clustered cells. This usually results in a thermal runaway issue. Similarly, for 18-V_{GS} or 15-V_{GS} SiC MOSFETs it is highly recommended to maintain the gate drive voltage higher than 14 V and 12 V, respectively.

Table 2-1. MOSFET Comparisons and Efficiency Improvements from SiC

Parameter	1.7-kV Si MOSFET (STW12N170K5)	1.7-kV SiC MOSFET (G2R1000MT17D)	Efficiency Gain Due To SiC MOSFET
R_{DS,ON} at T _J =125°C	2.2 Ω at 10 V _{GS}	1.2 Ω at 20 V _{GS}	45% lower conduction loss
Gate Charge QG	37 nC at 10 V _{GS}	11.0 nC at 20 V _{GS}	40% lower gate drive loss
C_{OSS(ER)} at V _{DS} = 1 kV	26 pF	19 pF	>23% lower turn-on loss

3 Start-Up Circuitry and Comparisons

To satisfy functional safety during the regenerative braking test and to limit the bus voltage from charging above an unsafe level when the vehicle is towed or pushed, the auxiliary supply must have a total startup time on the order of hundreds of milliseconds. If the controller uses a simple high voltage resistor string to bias VDD during startup, low resistance is needed to charge the VDD capacitor above the controller UVLO threshold. The resistor string will continue to consume power during normal operation, which reduces efficiency and increases standby power. Standby power is a critical requirement in battery-operated systems since it affects the range of an electric vehicle. Therefore, an external, active start-up circuit is recommended.

Figure 3-1 shows a well-known active start-up circuit using a high-voltage BJT (or enhancement-mode MOSFET) with 1.2-kV voltage rating or above. Figure 3-2 shows a novel, alternative startup circuit with two 600-V depletion mode MOSFETs in series. The following discussion will briefly discuss the design and operation of each circuit and then provide comparisons.

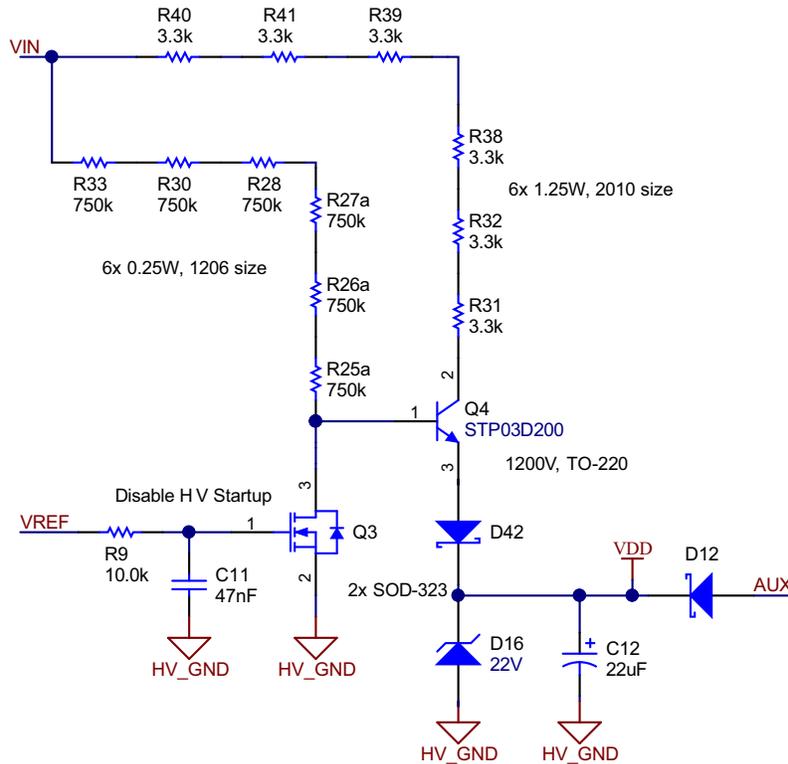


Figure 3-1. Typical 1.2-kV NPN-based Active Start-up Circuit

To power up at low V_{IN} (40 V) within the maximum startup time ($t_{SS, MAX}$), the NPN-based active startup circuit must provide high enough startup current to charge the VDD capacitor (C_{12}) above V_{DDON} and also deliver the startup current of the PWM controller, $I_{START-UP(Contoller)}$. This startup requirement sets the maximum value of the total current limiting resistance ($R_{C, MAX}$) connected from V_{IN} to the collector of the NPN. The trade-off is the resistor size and cost to handle the pulsed current, especially at high V_{IN} (1000V).

$$R_{C, MAX} = \frac{(V_{IN, MIN} - V_{CE, SAT} - V_{DDON})}{\frac{C_{VDD} \times V_{DDON}}{t_{SS, MAX}} + I_{START-UP(Contoller)}} \quad (1)$$

During component selection, surge rated resistors with relatively high power handling capability are needed, such as the CRGP Series from TE Connectivity. The 2010 size resistor (typically 1.25 W) from this series is rated for 20-30 W for 100 ms. The collector resistors must be chosen to withstand the power dissipated at the highest V_{IN} (1000 V). Also, multiple resistors in series are required to distribute the maximum input voltage without exceeding the individual voltage rating of each resistor (200 V per resistor).

Lastly, the NPN transistor must receive adequate base current and have a high enough current gain to deliver the previously mentioned current to the VDD capacitor at low V_{IN} . The base current, derived from a second resistor string, increases the standby power and the total power loss of the circuit shown in [Figure 3-1](#) at 1 kV is $(1 \text{ kV})^2 / (6 \times 750 \text{ k}\Omega) = 220 \text{ mW}$. To guarantee high current gain for lowering power consumption from base current at high V_{IN} and for providing sufficient collector current at low V_{IN} a Darlington transistor was selected, rated for 1.2 kV. Due to the special component selection, the smallest package size option is TO-220, which is over-sized for high voltage startup function. Besides, the component cost and footprint are compromised as well.

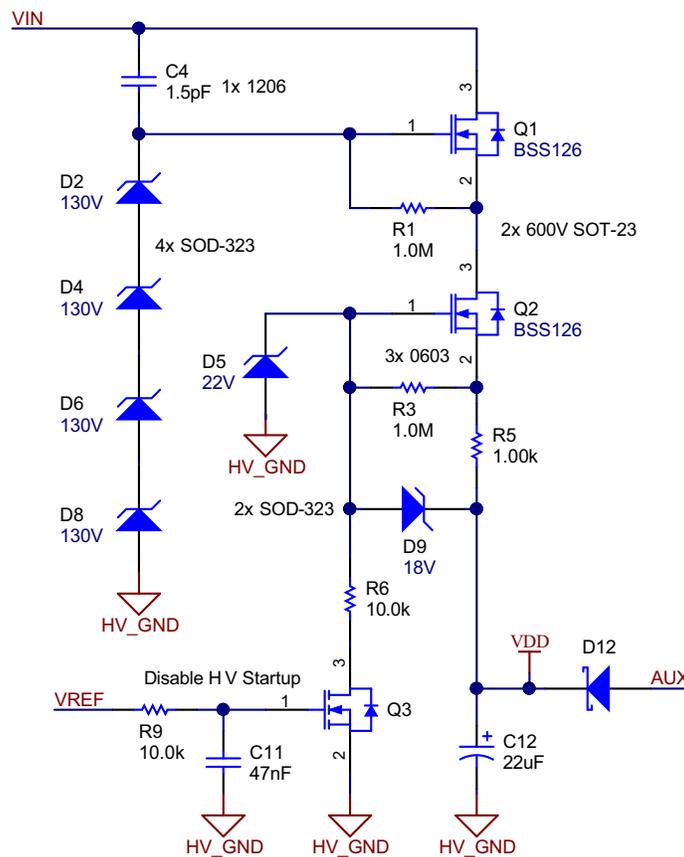


Figure 3-2. Miniature Active Startup Circuit Using Stacked 600-V Depletion Mode MOSFETs

The circuit in [Figure 3-2](#) utilizes two 600V depletion mode MOSFETs (2x BSS126). The depletion mode MOSFET conducts when no gate voltage is applied and begins to turn off as the VGS voltage becomes more and more negative. It is completely off when VGS is below the turn-off threshold. The characteristics of the depletion mode FET make it well suited to implementing a current source for high-voltage startup. It is difficult to find a low-cost and small-size depletion MOSFET with 1.2-kV rating, but there are wide variety of selection

in 600V to 800V domain. Therefore, the new stacked depletion MOSFET configuration with the proposed gate clamp circuit will evenly distribute the voltage stress from the 1 kV input voltage.

First, let's look at the operation of Q1. Notice the four 130-V Zener diodes; D2, D4, D6 and D8. Their combined Zener voltage is 520 V. Next, think of R1 as a pull-up resistor to VIN that provides current to the Zener diodes. With that in mind, it's obvious that these diodes will be off if VIN < 520V. Now, as VIN rises above 520 V, the voltage at the source of Q1 will be clamped slightly above 520 V, let's say 521 V. In effect Q1 is biased such that the maximum voltage presented to Q2 is 521 V. The V_{DS} voltage of Q1 is VIN – 520 V. At 1000 VIN the V_{DS} of Q2 will be 521 V and V_{DS} of Q1 will be 479 V.

Next, let's look at the operation of Q2. For now, let's say D5 is a 22-V redundant (safety) clamp to limit the maximum value of VDD in case Q3 were in a single fault situation and could not shut down Q2. So, for normal operation it's practical to assume D5 is off. When VDD < V_{DD,ON}, Q3 is also off because the controller has not been powered up and VREF = 0V. R3 is a pull-up resistor (similar to R1 for Q1) that biases D9 on in the forward direction during HV startup. As shown in Figure 3-3, the majority of current flows from the source of Q2 through R5 and charges the 22 μF capacitor on VDD. We can draw the following diagram and use KVL around the loop formed by R3, D9, and R5. Then, the soft start time requirement sets the maximum value of R5, the current limiting resistor.

$$R_{5,MAX} = \frac{(V_{TH(Q2)} + V_{F(D9)})}{\frac{C_{VDD} \times V_{DD,ON}}{t_{SS,MAX}} + I_{START-UP}(Controller)} \quad (2)$$

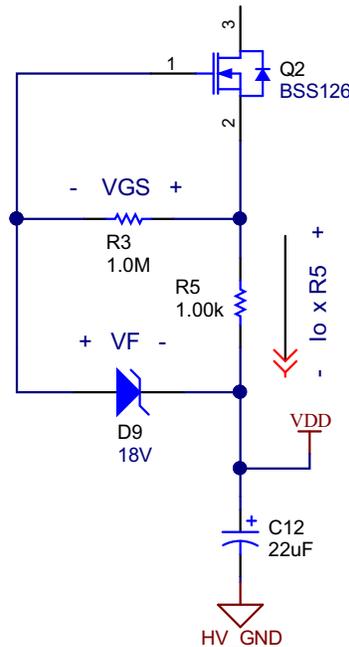


Figure 3-3. Solving for the Output Current, I_o

Typical values for V_{F(D9)} and V_{TH(Q2)} are 0.3 V and 1.0 V, respectively. With this information we can solve for I_o: (0.3 V + 1.0 V) / 1 kΩ = 1.3 mA. Notice this current does not depend on VIN so it will be constant over the entire range of VIN. The power dissipated by the current limit resistor, (1.3 mA)² x 1 kΩ = 1.7 mW, is very low for the entire VIN range so the resistor can be quite small, 0603 size.

In both the NPN and Depletion Mode circuits, Q3 functions as a simple switch controlled by VREF from the controller to shut down the HV startup circuit. When Q3 turns on Zener diode D9 is reverse biased and clamps the V_{GS} voltage of Q2 to about –18 V. In all cases, shutting down the HV startup circuit reduces power and improves efficiency. Biasing the zener string only requires few μA. The power consumption of Figure 3-2 can be derived as [V_{TH(Q1)} / R1 + V_{TH(Q2)} / R3] x VIN. For 1-V V_{TH} and a 1 MΩ resistors, the power loss at 1 kV is only 1 mW. Compared to the 220 mW consumption of the NPN startup circuit, the standby power is greatly reduced.

C4 is a feedforward capacitor from VIN to the (520-V) zener string. This capacitor speeds up the zener string response in the event VIN changes very quickly ($dV_{IN}/dt < 10 \text{ V/ns}$) to maintain even distribution of the voltage stress between the two depletion mode MOSFETs. This capacitor typically should be 1-2 pF, but should be rated for at least 630 V.

Figure 3-4 is a simulation of the depletion mode startup circuitry with VIN ramping up to 800 V in 100 ms. Notice the V_{DS} of Q1 is limited to 280 V and V_{DS} of Q2 is limited to 520 V (the total Zener voltage). Also, the output current is 1.34 mA, as predicted. The VDD voltage rises linearly for 300 ms to 18.27 V.

Note

Q3 turns on at 300 ms.

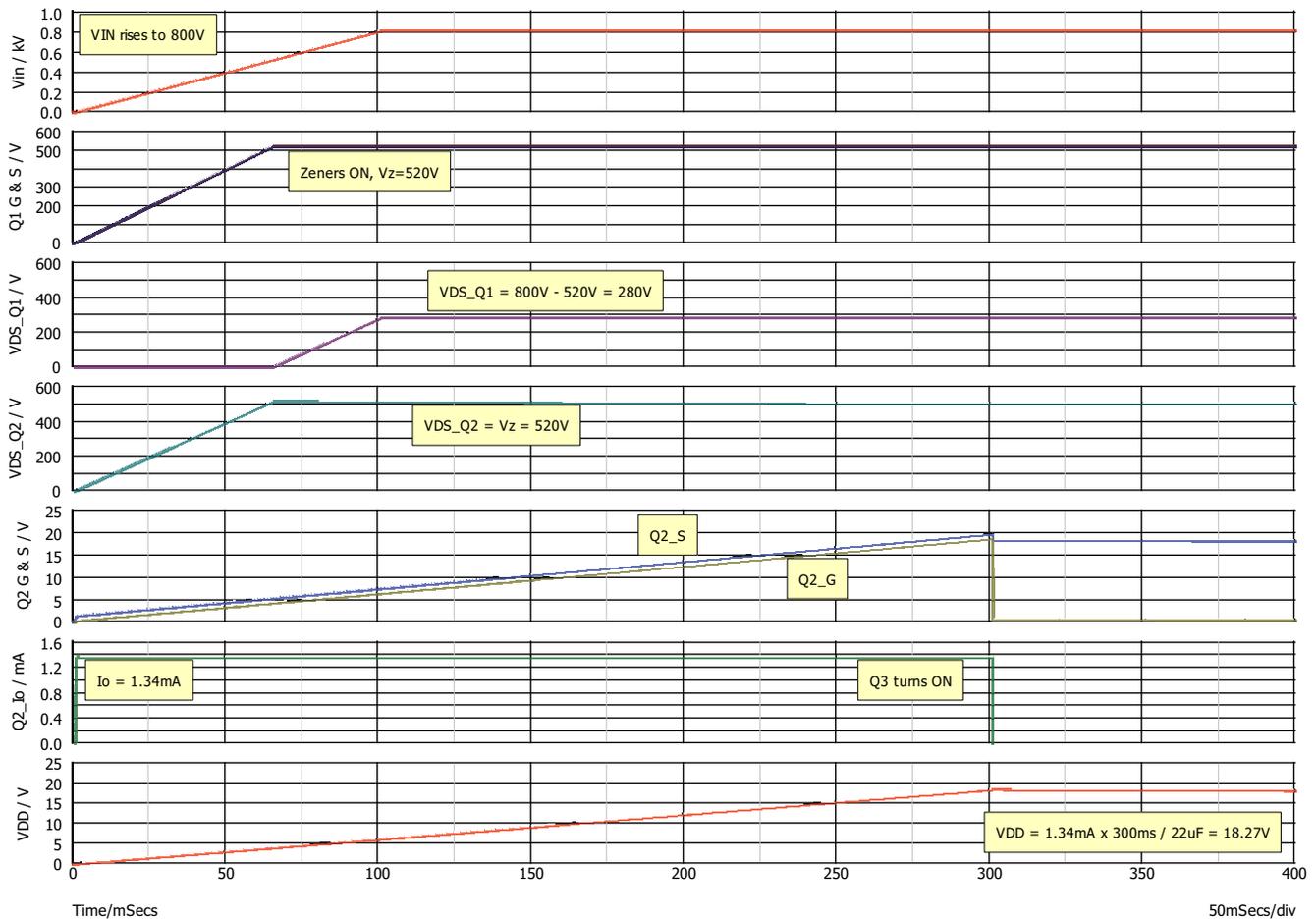


Figure 3-4. Simulation of the Depletion Mode Startup Circuit, VIN = 800 V

Figure 3-5 is a simulation when Q3 does not turn on due to single fault event. VDD and V_{SG_Q2} rise until the 22-V Zener (D5) turns on. At this instant VDD is limited to 22.7 V, a benign value. Without D5 the VDD voltage would rise to a destructive voltage.

Note

Q3 does not turn on but VDD is clamped at 22.7 V, a safe value.

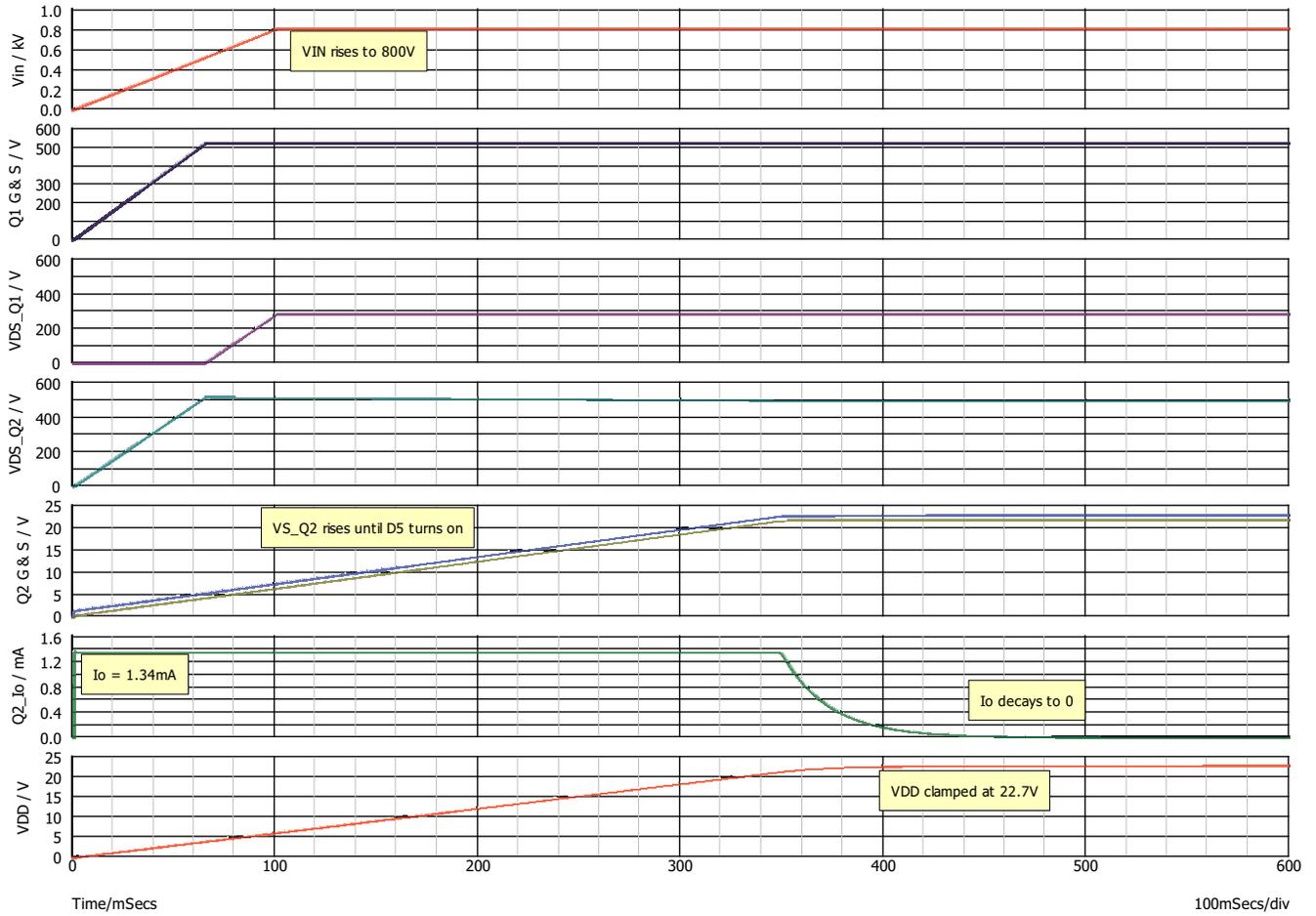


Figure 3-5. Simulation of the Depletion Mode Startup Circuit, VIN = 800 V

The waveforms in Figure 3-6 to Figure 3-9 are plots measured for both the NPN and Depletion Mode active startup circuits at 50 VIN, 1.3-A load and 800 VIN, 2.7-A load. The total startup time of the NPN based circuit varies from 254 ms at 50 VIN to only 44ms at 800 VIN, a change of 210 ms. The startup time of the Depletion Mode circuit varies from 254 ms to 243 ms, a change of only 11 ms (4.3%)! The performance of the Depletion Mode circuit correlates very well to the simulations.



Total soft start time is 254 ms.



Total soft start time is 44ms, $\Delta = -210$ ms.

Figure 3-6. NPN Active Startup at 50 V, 1.3 A Load Figure 3-7. NPN Active Startup at 800 V, 2.7 A Load



Total soft start time is 254 ms.



Total soft start time is 243 ms, $\Delta = -11$ ms.

Figure 3-8. Depletion Mode Active Startup at 50-V, 1.3-A Load Figure 3-9. Depletion Mode Active Startup at 800-V, 2.7-A Load

Figure 3-10 and Figure 3-11 are physical comparisons of components required for the NPN and Depletion Mode HV startup circuits. The NPN active startup components require 0.64 in². The depletion mode active startup components require only 0.19 in². The NPN based circuitry requires at least 3.4x the PCB area, probably more after placing and routing the higher current traces associated with the NPN circuit. Note: the shutdown FET (Q3) and its associated components are common to both solutions so it was omitted from the comparisons.

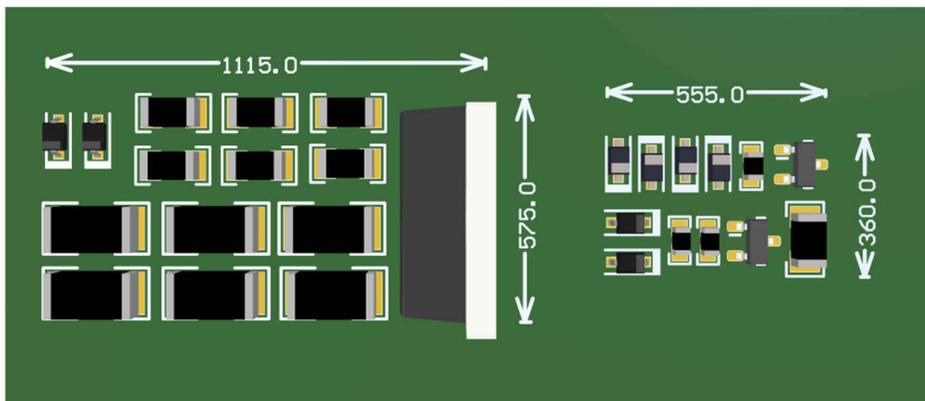


Figure 3-10. 2D View Comparing the Area of the Startup Circuits

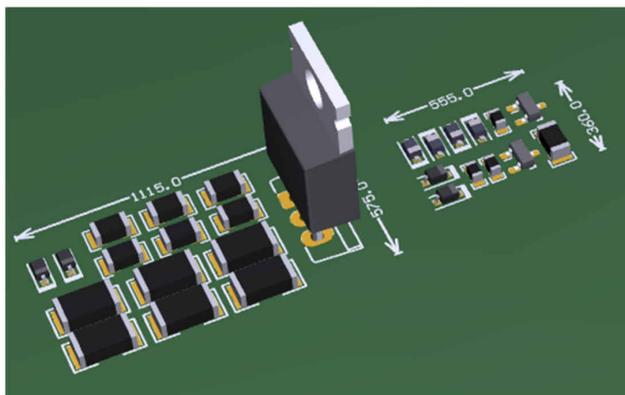


Figure 3-11. 3D View Comparing the Heights of the Startup Circuits

Table 3-1 is a cost comparison between the NPN and Depletion Mode HV startup circuits.

Table 3-1. Cost Comparisons Between the Two HV Startup Circuits

COMPONENT	UNIT COST	NPN-BASED CIRCUIT	DEPLETION MODE CIRCUIT
1.2-kV NPN in TO-220	\$1.10	1	
600-V depletion mode MOSFETs in SOT-23	\$0.12		2
2010-size surge-rated resistors	\$0.05	6	
1206-size resistors	\$0.015	6	
0603-size resistors	\$0.005		3
Zener/Schottky diode in SOD-223	\$0.04	2	6
1206-size 630-V capacitor	\$0.04		1
	Total Cost:	\$1.57	\$0.54

In the second pair of waveforms, R23 is increased to 15 kΩ and C21 to 2.2 μF. When the MOSFET turns on the CS signal starts from ~0V, has almost the same slope as Rsense, and peaks at 140 mV when Rsense is at 240 mV (58%). The regulator consistently produces pulse width of 358 ns and the light load regulation is much better. Pulse skipping does not occur until the load is less than 200 mA.



Inconsistent gate pulse widths

Figure 4-2. 800 V, 0.25 A Load, R23=1 kΩ, C21=10 nF



CS signal starts below 0 V, slope of CS does not follow Rsense

Figure 4-3. 800 V, 0.25 A load, R23=1 kΩ, C21=10 nF



Consistent gate pulse widths

Figure 4-4. 800V, 0.25 A Load, R23=15 kΩ, C21=2.2 μF



CS signal starts at 0 V, slope of the CS follows Rsense

Figure 4-5. 800V, 0.25 A Load, R23=15 kΩ, C21=2.2 μF

Figure 4-6 shows load regulation for two sets of R23 and C21 values discussed. The light load regulation with 15 kΩ / 2.2 μF is significantly improved below 1-A load.

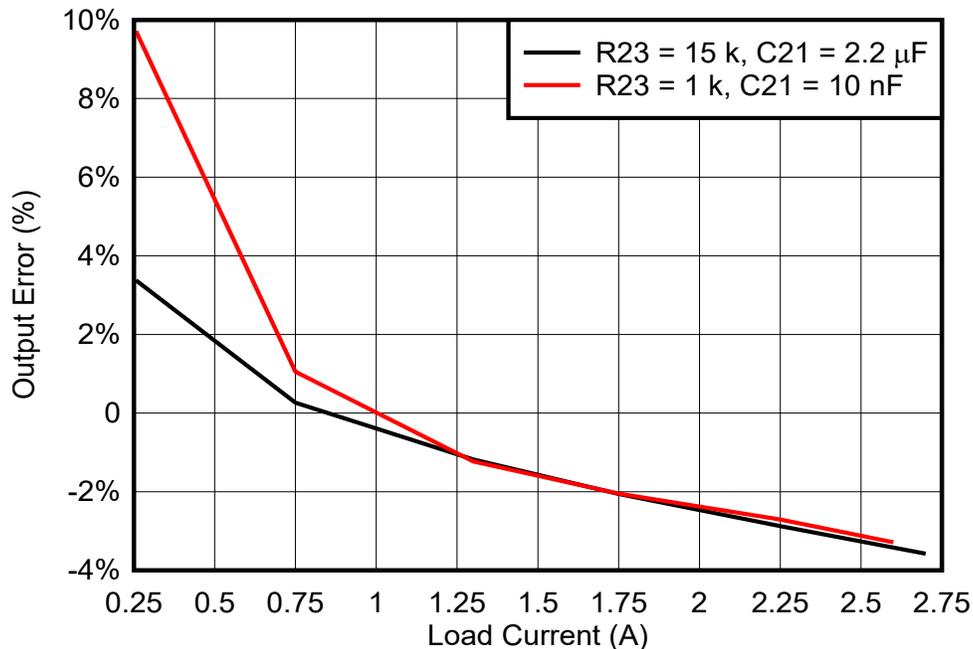


Figure 4-6. Comparison of Light Load Regulation for Two Combinations of R23 and C21

5 High Voltage Isolation

The distance between the high-voltage area at the primary side, and low-voltage area at the secondary side, must have enough creepage and clearance to comply with standards such as IEC 60664-1. For creepage design criteria as example, with 800 Vrms working voltage and pollution degree 2, the working voltage for material group I is 4 mm for basic isolation, and 8 mm for reinforce isolation. Therefore, the PCB layout between primary and secondary side and the transformer pin-out needs to follow the guideline.

The ground of the low-voltage side can be connected to a 12-V battery or vehicle chassis, which a user can come in contact with. Therefore, a transformer with reinforced isolation and AEC-Q200 Grade 1 compliance is recommended for this application.

With internal error amplifier and reference, the UCC28C5x family can be configured as a primary-side regulated solution by using an auxiliary winding for feedback, so that it can avoid the need to use optocoupler across isolation and eliminate the CTR degradation from the optocoupler life time issue

6 Summary

When designing a backup power supply for a traction inverter to achieve high converter efficiency, fast startup time, and target thermal de-rating careful consideration must be given to selecting a high voltage power device and topology. The new, ultra-small, low-cost active high voltage depletion mode startup circuit introduced in this document helps achieve fast startup, reduces both PCB area, and component cost. The total startup time with the new startup circuit is very consistent over the entire VIN operating range. The new UVLO options and 30-V rating to reliably drive SiC MOSFET with UC28C5x family enable higher thermal de-rating power and optimal switching performance of the backup power supply in the increasingly popular 800-V battery system of EV traction inverters.

For high voltage power device selection of a flyback converter, silicon MOSFETs are typically acceptable for 400-V battery systems. However, Silicon Carbide MOSFETs must be used in 800-V battery systems due to their higher voltage rating (typically 1700 V) and improved FOM. Also, primary-side regulation (PSR) does not require an optocoupler which increases system reliability, eliminates a component crossing the isolation barrier, and further reduces cost.

7 Related Documentation

- Texas Instruments, [UCC28C4x-Q1 Automotive BiCMOS Low-Power Current-Mode PWM Controllers](#) data sheet.
- Texas Instruments, [UCC28C5x-Q1 BiCMOS Low-Power Current-Mode PWM Controllers for Si and SiC MOSFETs](#) data sheet.
- Texas Instruments, [Using the UCC28C56EVM-066 High-Density Auxiliary Power Supply for 800-V Traction Inverters](#) EVM user's guide.
- Texas Instruments, [Why is High UVLO Important for Safe IGBT and SiC MOSFET Power Switch Operation?](#) application brief.
- Texas Instruments, [PMP41009 350-V to 1000-V DC Input, 56-W Flyback Isolated Power Supply Reference Design](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated