



Justin Kim

ABSTRACT

This application note describes the optimized layout guide for the BQ257XX family of buck-boost charger solutions. BQ257XX family includes BQ2570X, BQ2571X, BQ2572X, BQ2573X. These products are synchronous NVDC buck-boost battery charge controller, offering a low component counts, high efficiency solution for space constrained, 1s~4s battery charging applications. In order for the chargers to perform optimally, certain layout rules should be followed. The rule of utilizing a good layout is to minimize the PCB trace inductance in the high di/dt current paths, to limit capacitive coupling from high dv/dt nodes onto other traces, and to ensure proper GND connections. By following the rules, designer will be able to achieve the best charger operation including low EMI, high accuracy, high efficiency, low temperature operation.

Table of Contents

1 Introduction	2
1.1 BQ25710 EVM Circuit.....	3
2 Layout Guidelines	4
2.1 PCB Stack-Up (4 Layers).....	4
2.2 Identifying Critical Circuit Paths.....	5
2.3 Input and Output Loop Placements Considering Noise, Efficiency, and Thermal Performance.....	6
2.4 Kelvin Sensing Circuit for Current Sense to Achieve High Accuracy.....	7
2.5 Small Capacitors Placements Considering Noise.....	8
2.6 Separating AGND and PGND.....	9
3 References	10

List of Figures

Figure 1-1. BQ25710 EVM Circuit.....	3
Figure 2-1. Layout Example for PCB Stack-Up and Top Side Components Placement.....	4
Figure 2-2. Power Stage Component Placement and Ground Layer.....	4
Figure 2-3. BQ25710 Application Diagram Identifying High di/dt Loops, High dv/dt Nodes and Sensitive Traces.....	5
Figure 2-4. Power Components Placement on Top Layer.....	6
Figure 2-5. Kelvin Sensing Connections for R_{SR} Resistor.....	7
Figure 2-6. Capacitors Placement for VBUS, VDDA, REGN.....	8
Figure 2-7. Capacitors for BTST1/2 pins.....	8
Figure 2-8. Separating AGND and PGND With Net-Tie.....	9

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

Buck-boost charger has 5 switches and one inductor. The proper layout design is the key to achieve the stable operation, good thermal and low EMI performance. But there are many layout challenges for circuit designers. A poor layout can result in low efficiency, reduced charging capability, reduced measurement accuracy, or even unstable operation due to noise interference. To overcome the challenges, TI BQ257XX EVM is a good starting point for a custom layout. There can be alternative methods however, this layout is proven and most likely provides the best operation of the device due to the optimization of PCB trace inductance and the suggested grounding method. [Figure 1-1](#) shows the BQ25710 EVM circuit as an example for the layout guide in this application note.

1.1 BQ25710 EVM Circuit

 


Figure 1-1. BQ25710 EVM Circuit

2 Layout Guidelines

Proper layout of the components to minimize high frequency current path loop is important to prevent electrical and magnetic field radiation and high frequency resonant problems. Here is a PCB layout guide based on priority for proper layout.

2.1 PCB Stack-Up (4 Layers)

For proper layout design, multi-layer PCB is suggested. The BQ257XX EVM uses a 4-layer PCB as shown in [Figure 2-1](#). The top layer contains power traces and most signal lines. Any remaining area on top layer must be filled with ground and be connected to bottom and internal grounds by strong via connection through all layers. The internal layer 2 is ground only and layer 3 contains signal lines and ground. The bottom layer is used for additional non-critical signals and ground.

As shown in [Figure 2-2](#), put ground near power components layer (Top layer) since that can be an effective shield to reduce inductive and capacitive coupling noise. If the ground layer is the next layer following the power stage layer, the ground layer copper gets the lowest thermal resistance, smallest high-frequency loop area and shield most of the rest circuit from the high-noise power stage. Also, if all high-current loop components are put on the same layer, the magnetic field lines are vertical to the board. So, the ground copper layer can provide the best shielding performance between the power stage circuit and other small signal circuits on the board.

 


Figure 2-1. Layout Example for PCB Stack-Up and Top Side Components Placement

 


Figure 2-2. Power Stage Component Placement and Ground Layer

2.3 Input and Output Loop Placements Considering Noise, Efficiency, and Thermal Performance

Once the critical parts of layout are identified, the next task is to minimize any sources of noise and unwanted parasitic. The input-switching current loop and output-switching current loop are the dominant high current loops. Minimize the area of these loops to suppress generated switching noise and optimize switching performance. Therefore, it's highly recommended to put the power components on same layer. Also Allow enough copper area for thermal dissipation. Multiple thermal vias can be used to connect more copper layers together and dissipate more heat. [Figure 2-4](#) shows the power components placement on top layer as a good example with BQ25710 EVM matching with the schematic shown in [Figure 1-1](#).

 


Figure 2-4. Power Components Placement on Top Layer

VBUS capacitors, R_{AC} , Q1 and Q2 form a small loop1. VSYS capacitors, Q3 and Q4 form a small loop 2. As shown in [Figure 2-1](#), the most important loop areas to minimize on loop 1 and loop 2 are the path from the input capacitors through the buck high-side and low-side MOSFETs, and back to the ground connection of the input capacitor and the path from the output capacitors through the boost high-side and low-side MOSFETs, and back to the ground connection of the output capacitor. Connect the negative terminal of the capacitor close to the source of the low-side MOSFETs (at ground). Similarly, connect the positive terminal of the capacitor or capacitors close to the drain of the high-side MOSFETs of both loops. Especially 10nF + 1nF (0402 size) decoupling capacitors must be placed after R_{AC} as close as possible to FETs for decoupling switching loop high frequency noise.

Connect the power components with large copper to reduce the parasitic resistance. Since the current path from VBUS to VSYS and VBAT to VSYS has low impedance, pay attention to via resistance if not on the same layer. The number of vias can be estimated as 1 to 2A/via for a 10mil via with 1oz copper thickness. If high density design is required, you can move part of CBUS or CSYS to the other side of PCB. Lastly, we recommend to place QBAT and R_{SR} near the battery terminal since the device detects the battery voltage through SRN pin near battery terminal.

2.4 Kelvin Sensing Circuit for Current Sense to Achieve High Accuracy

Use Kelvin-sensing connections for R_{AC} and R_{SR} current sense resistors. [Figure 2-5](#) shows an example of Kelvin-sensing technique for R_{SR} resistor. Put enough copper on high current path going through sensing resistor since the thin trace can cause an unexpected voltage drop on the board. Also keep in mind that non-kelvin connection can cause the different voltage across SRP and SRN compared to the voltage across sensing resistor. So, connect the current sense traces to the center of the pads and run current sense traces as differential pairs. To avoid noise getting picked up, put signal lines far away from noisy paths into inner layers.

 


Figure 2-5. Kelvin Sensing Connections for R_{SR} Resistor

2.5 Small Capacitors Placements Considering Noise

Place REGN capacitor(C30), VBUS capacitor(C25), VDDA capacitor(C29) close to IC as shown in [Figure 2-6](#). Use AGND for VBUS, VDDA capacitors and use PGND for REGN capacitor since REGN pin out is for power stage gate drive. Since REGN capacitor provides a low impedance path for the driver circuits in BQ25710, put REGN capacitor close to the IC to maintain the lowest impedance source for the fast di/dt required for IC's FET drivers.

Place high-side FET bootstrap circuit capacitors close to IC and on the same layer of PCB. As shown in [Figure 2-7](#), capacitors on SW1/2 nodes are recommended to use wide copper polygon to connect to power stage and capacitors on BTST1/2 nodes are recommended to use at least 8mil trace to connected to BTST1/2 pins to reduce line parasitic inductance. Another R/C for signal pins must be placed close to the IC far away from high frequency noise. Add ground vias close to R/C to connect the ground of signal to ground plane.

 


Figure 2-6. Capacitors Placement for VBUS, VDDA, REGN

 


Figure 2-7. Capacitors for BTST1/2 pins

2.6 Separating AGND and PGND

Separate PGND and AGND first to avoid small signal ground coupling high current (high di/dt) ground noise. In power supply layout, separating the signal system is important, such as the feedback path which is susceptible to noise and the switching nodes that switch large current.

- AGND: a quiet ground reference for control signals (analog ground)
- PGND: a noisy ground reference for power signals (power ground)

AGND is used for all sensing, compensation, and control network ground for example: ACP/ACN/COMP1/COMP2/CMPIN/CMPOUT/IADPT/IBAT/PSYS. PGND is used as return path for power stage related large current signals.

Though the DC ground potential is the same, measure must be taken to separate these AGND and PGND planes to make sure noise arising from digital or high-power signals is not conducted between them to interfere with analog signals. As shown in [Figure 1-1](#), we recommend to have two ground signs in the schematic already as difficulties arise when visualizing sensitive and noisy potentials on the layout if the same GND sign is used on the schematic. Therefore, we recommend starting with split GND in the schematic level and connect them with a net tie (NT1).

[Figure 2-8](#) shows the connection between PGND and AGND with a net tie in PCB layout highlighting top layer (Red) and layer3 (Blue). AGND is used for control signals and must be closer to the IC and own a polygon. Connect all AGND to a dedicated low-impedance copper lane to make sure AGND and PGND are on the same potential and ultimately must be connected together at one point near the IC as shown in [Figure 2-8](#) (like exposed power pad underneath the IC).

 


Figure 2-8. Separating AGND and PGND With Net-Tie

3 References

- Texas Instruments, [BQ25710 SMBus Narrow VDC Buck-Boost Battery Charge Controller With System Power Monitor and Processor Hot Monitor](#) data sheet.
- Texas Instruments, [bq2571x Evaluation Module](#) user's guide.
- Texas Instruments, [Layout Optimization of 4-Switch Buck-Boost Converters](#) application note.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated