

Nancy Hidalgo, Ethan Galloway

## ABSTRACT

This application notes aims to aid engineers in the selection of the switching MOSFETs for the BQ2575x family of devices and understand the origin of power losses from MOSFETs. The MOSFETs in use can play a large role in the overall efficiency of the system. MOSFET selection depend heavily on the system parameters, such as the switching frequency, output current, output voltage, and input voltage.

---

## Table of Contents

<b>1 Introduction.....</b>	<b>2</b>
<b>2 MOSFET Power Losses in Buck and Boost Chargers.....</b>	<b>3</b>
2.1 Buck Mode Losses.....	3
2.2 Boost Mode Losses.....	5
2.3 Closing Thoughts for FET Losses.....	6
<b>3 Evaluating MOSFETs Using the Design Calculator.....</b>	<b>6</b>
3.1 Correlating MOSFET Data Sheet Parameters With the Design Calculator Parameters.....	7
3.2 Design Calculator MOSFET Comparison Example.....	8
<b>4 BOM Evaluation.....</b>	<b>9</b>
<b>5 Summary.....</b>	<b>12</b>
<b>6 References.....</b>	<b>13</b>

## Trademarks

All trademarks are the property of their respective owners.



## 2 MOSFET Power Losses in Buck and Boost Chargers

In a switch-mode converter, the total losses come from the MOSFET losses and the parasitic resistances of the reactive and inductive components. For the energy storage elements, the losses come from the equivalent series resistance of each component. This application note focuses on the MOSFET losses and which parameters contribute to these losses. For ease of reference, [Figure 2-1](#) is a MOSFET parasitic model.

 


Figure 2-1. MOSFET Parasitic Model

### 2.1 Buck Mode Losses

For buck mode, the top FET is the synchronous FET and the bottom FET is the asynchronous FET. The power loss for the top FET can be split into the switching losses and conduction losses and is expressed in [Equation 1](#).

$$P_{top} = P_{con\_top} + P_{sw\_top} \quad (1)$$

The conduction losses come from the MOSFET being statically-on.

$$P_{con\_top} = D \times I_{L\_RMS}^2 \times R_{DS(on)\_top} \quad (2)$$

$$I_{L\_RMS}^2 = I_{L\_DC}^2 + \frac{I_{ripple}^2}{12} \quad (3)$$

The switching losses come from the current and voltage overlap during the FET turn-on and turn-off; the parasitic gate capacitance; and gate drive losses into the FET.

$$P_{sw\_top} = P_{IV\_top} + P_{Qoss\_top} + P_{gate\_top} \quad (4)$$

Where  $P_{IV\_top}$  is the loss in the top MOSFET loss due to the current and voltage overlap,  $P_{Qoss\_top}$  is the loss due to the MOSFET parasitic output capacitance, and  $P_{gate\_top}$  is the gate drive loss.  $P_{IV\_top}$  is given by the following equations:

$$P_{IV\_top} = 0.5V_{IN} \times I_{valley} \times t_{on} \times f_{sw} + 0.5V_{IN} \times I_{peak} \times t_{off} \times f_{sw} \quad (5)$$

$$I_{valley} = I_{L\_DC} - 0.5I_{ripple} \quad (6)$$

$$I_{peak} = I_{L\_DC} + 0.5I_{ripple} \quad (7)$$

Where  $I_{L\_DC}$  is the DC inductor current and  $I_{ripple}$  is the peak-to-peak ripple current of the inductor. The MOSFET turn-on and turn-off times,  $t_{on}$  and  $t_{off}$ , are defined with the following equations:

$$t_{on} = \frac{Q_{sw\_top}}{I_{on}} \quad (8)$$

$$t_{off} = \frac{Q_{sw\_top}}{I_{off}} \quad (9)$$

Here,  $Q_{sw\_top}$  is the switching charge of the top side FET which can be approximated by [Equation 10](#).

$$Q_{sw\_top} = Q_{GD\_top} + Q_{GS\_top} \quad (10)$$

And  $I_{on}$  and  $I_{off}$  are defined with the following equations:

$$I_{on} = \frac{V_{DRV\_SUP} - V_{plt}}{R_{on}} \quad (11)$$

$$I_{off} = \frac{V_{plt}}{R_{off}} \quad (12)$$

Where  $V_{plt}$  is the Miller plateau voltage,  $V_{DRV\_SUP}$  is the gate drive voltage on the MOSFETs,  $R_{on}$  is the total turn-on gate resistance, and  $R_{off}$  is the total turn-off gate resistance of the gate drive. The next term in the total loss calculation,  $P_{Qoss\_top}$ , can be calculated with [Equation 13](#).

$$P_{Qoss\_top} = 0.5V_{IN} \times Q_{oss\_total} \times f_{sw} \quad (13)$$

Where  $Q_{oss\_total}$  is the total parasitic output charge.

$$Q_{oss\_total} = Q_{gd\_top} + Q_{ds\_top} + Q_{gd\_bot} + Q_{ds\_bot} \quad (14)$$

The last term in the loss equation can be calculated with [Equation 15](#).

$$P_{gate\_top} = V_{IN} \times Q_{gate\_top} \times f_{sw} \quad (15)$$

Where  $Q_{gate\_top}$  is the gate charge of the top MOSFET and  $V_{IN}$  is the input voltage, not the gate drive voltage of the MOSFET. This is to include the losses generated by the internal LDO of the charge controller. If an external gate drive voltage is provided, the LDO losses can be avoided and [Equation 16](#) can be used instead:

$$P_{gate\_top} = V_{DRV\_SUP} \times Q_{gate\_top} \times f_{sw} \quad (16)$$

The losses for the bottom MOSFET are comprised of conduction losses and switching losses:

$$P_{bottom} = P_{con\_bottom} + P_{sw\_bottom} \quad (17)$$

As for the conduction loss, the loss can be defined for buck mode similar to the top FET with [Equation 18](#).

$$P_{con\_bottom} = (1 - D) \times I_{L\_RMS}^2 \times R_{DS\_ON\_bottom} \quad (18)$$

Where  $D$  is the duty cycle and  $I_{L\_RMS}$  is the RMS current through the inductor. To minimize the conduction loss, the  $R_{DS\_ON}$  need to be low. The next and final term in the loss calculation, the switching loss, can be calculated with [Equation 19](#).

$$P_{sw\_bottom} = P_{RR\_bottom} + P_{dead\_bottom} + P_{gate\_bottom} \quad (19)$$

Where the  $P_{RR\_bottom}$  term is the loss due to the reverse recovery charge of the MOSFET,  $P_{dead\_bottom}$  is the loss due to the conduction loss of the body diode during dead time, and  $P_{gate\_bottom}$  is the gate drive loss. Each term can be derived with the following equations:

$$P_{RR\_bottom} = V_{IN} \times Q_{rr} \times f_{sw} \quad (20)$$

$$P_{dead\_bottom} = V_{SD} \times I_{valley} \times f_{sw} \times t_{dead\_rise} + V_{SD} \times I_{peak} \times f_{sw} \times t_{dead\_fall} \quad (21)$$

$$P_{gate\_bottom} = V_{IN} \times Q_{gate\_bottom} \times f_{sw} \quad (22)$$

$Q_{gate\_bottom}$  is the gate charge of the bottom MOSFET,  $V_{SD}$  is the forward voltage of the body diode, and  $V_{IN}$  is the input voltage, not the gate drive voltage of the MOSFET. This is to include the losses generated by the internal LDO of the device. If an external gate drive voltage is provided, Equation 23 can be used instead:

$$P_{gate\_bottom} = V_{DRV\_SUP} \times Q_{gate\_bottom} \times f_{sw} \quad (23)$$

## 2.2 Boost Mode Losses

For boost mode, the top FET is asynchronous and the bottom FET is synchronous. The total power losses for the top and bottom FET can be determined in the same way as in buck mode with the following equations:

$$P_{top} = P_{con\_top} + P_{sw\_top} \quad (24)$$

$$P_{bottom} = P_{con\_bottom} + P_{sw\_bottom} \quad (25)$$

The conduction losses for the top FET are similar the buck mode losses:

$$P_{con\_top} = (1 - D) \times I_{L\_RMS}^2 \times R_{DS(on)\_top} \quad (26)$$

$$I_{L\_RMS}^2 = I_{L\_DC}^2 + \frac{I_{ripple}^2}{12} \quad (27)$$

In boost mode, the top FET has losses from the reverse recovery charge, dead time, and gate capacitance.

$$P_{sw\_top} = P_{RR\_top} + P_{dead\_top} + P_{gate\_top} \quad (28)$$

The gate losses, dead time losses, and reverse recovery losses are:

$$P_{RR\_top} = V_{IN} \times Q_{rr} \times f_{sw} \quad (29)$$

$$P_{dead\_top} = V_{SD} \times I_{valley} \times f_{sw} \times t_{dead\_rise} + V_{SD} \times I_{peak} \times f_{sw} \times t_{dead\_fall} \quad (30)$$

$$P_{gate\_top} = V_{IN} \times Q_{gate\_top} \times f_{sw} \quad (31)$$

As before, if an external gate drive voltage is provided, the following equation can be used instead:

$$P_{gate\_top} = V_{DRV\_SUP} \times Q_{gate\_top} \times f_{sw} \quad (32)$$

The losses for the bottom FET can be calculated is much the same way as the synchronous buck FET.

$$P_{con\_bottom} = D \times I_{L\_RMS}^2 \times R_{DS(on)\_bottom} \quad (33)$$

$$I_{L\_RMS}^2 = I_{L\_DC}^2 + \frac{I_{ripple}^2}{12} \quad (34)$$

The switching losses come from the current and voltage overlap during the FET turn-on and turn-off; the parasitic gate capacitance; and gate drive losses into the FET.

$$P_{sw\_bottom} = P_{IV\_bottom} + P_{Qoss\_bottom} + P_{gate\_bottom} \quad (35)$$

Where  $P_{IV\_top}$  is the loss in the top MOSFET loss due to the current and voltage overlap,  $P_{Qoss\_top}$  is the loss due to the MOSFET parasitic output capacitance, and  $P_{gate\_top}$  is the gate drive loss.  $P_{IV\_top}$  is given by the following equations:

$$P_{IV\_bottom} = 0.5V_{IN} \times I_{valley} \times t_{on} \times f_{sw} + 0.5V_{IN} \times I_{peak} \times t_{off} \times f_{sw} \quad (36)$$

The calculations for  $I_{valley}$ ,  $I_{peak}$ ,  $t_{on}$ , and  $t_{off}$  are the same as in buck mode.

## 2.3 Closing Thoughts for FET Losses

As can be inferred by the equations, switching losses are dominant when the charge current is low. As the current increases, the conduction losses increase as well and the conduction losses become the dominant loss term in the equation. Selecting an efficient FET can depend on the switching frequency of the charger and the average charge current.

Also, the recommendation is to limit the switch node capacitance such that the following is true:

$$C_{sw}(nF) < \frac{160}{V_{in}} \quad (37)$$

If  $V_{in}$  is 60V, the recommendation is to keep the total switch node capacitance ( $C_{sw}$ ) under 2.67nF. This can mitigate the switching loss and is a requirement for proper device functionality.

For ease of reference, BQ2575X's gate driver resistance of  $R_{on}$  and  $R_{off}$  and the dead time ( $t_{dead\_time}$ ) are listed in [Table 2-1](#). The dead time can be adjust to be 45ns, 75ns, 105ns, or 135ns.

**Table 2-1. BQ2575X IC's Gate Driver Characteristics**

Parameter	Typical Value
$R_{on}$	3.4Ω
$R_{off}$	1.0Ω
$t_{dead\_time}$ (Both sides)	45ns


## 3 Evaluating MOSFETs Using the Design Calculator

The [BQ25756 Design Calculator](#) can be used for all of the BQ2575X family of devices. This calculator can help with resistor programming, IC set-up, and the BOM selection process. The calculator can also take user inputs about the operating conditions, BOM, and system requirements to estimate the power loss and efficiency. Note that the calculator does not take into account power losses from other sources, like magnetic core losses, or copper trace losses. The efficiency calculator is best used to compare one FET to another FET.

This calculator also includes a thermistor qualification tab to estimate the minimum/typical/maximum temperature falling and rising thresholds for the various temperature charging windows. This tab can be used to select a thermistor for the application of interest, but this section focuses on the power loss/efficiency tab of the calculator.

To use this calculator, ignore the warning about circular references and fill in the yellow cells. The cells with red tabs contain additional information about the adjacent cell. Red cells highlight the cells that can have an issue. After filling out all of the yellow cells in the design calculator, the efficiency/power loss analyzer section can be used to plot the efficiency, sense resistor loss, and power losses of the two MOSFETs.

[Figure 3-1](#) shows the input voltage max is outside of the operating range. As a result, the text is red. When the cursor hovers over the red tab, the description text appears.

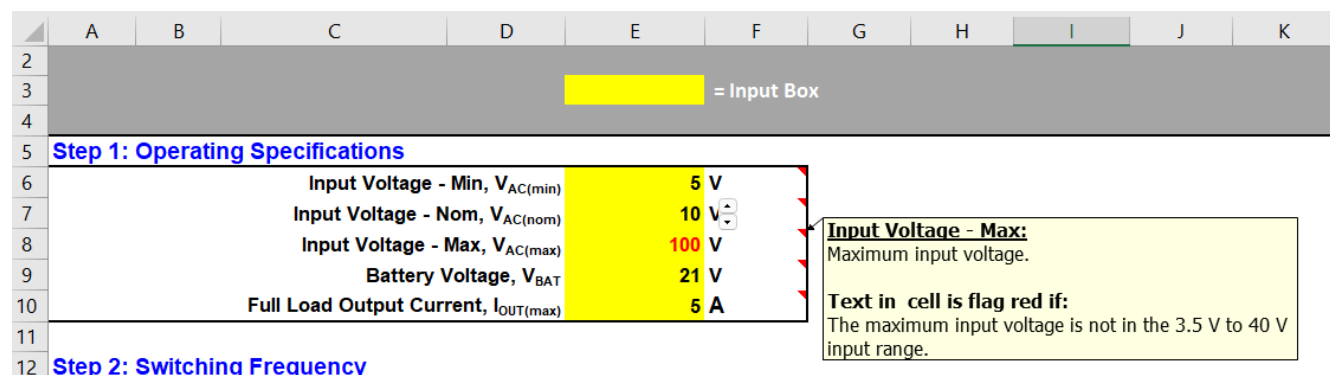

**Figure 3-1. BQ2575x Design Calculator Example**

### 3.1 Correlating MOSFET Data Sheet Parameters With the Design Calculator Parameters

This section aims to correlate device parameters typically given on a MOSFET data sheet to the parameters included in the design calculator. If a parameter is not on the data sheet, reach out to the device manufacturer.

These parameters here are the inputs required to use the design calculator. The parameters are the same for the buck-phase and the boost-phase switching MOSFETs.

Custom Power MOSFETs			
Custom MOSFET			
Buck-Leg Power MOSFETs (Q <sub>1</sub> , Q <sub>2</sub> )			
	Hi-side	Low-side	
On-State Resistance V <sub>gs</sub> = 4.5 V, R <sub>DS(on)</sub>	8.6	8.6	mΩ
On-State Resistance V <sub>gs</sub> = 10 V, R <sub>DS(on)</sub>	5.7	5.7	mΩ
On-State Resistance V <sub>gs</sub> = Custom Voltage, R <sub>DS(on)</sub>	4.9	4.9	mΩ
Total Gate Charge V <sub>gs</sub> = 4.5 V, Q <sub>G</sub>	7.3	7.3	nC
Total Gate Charge V <sub>gs</sub> = 10 V, Q <sub>G</sub>	15	15	nC
Total Gate Charge V <sub>gs</sub> = Custom Voltage, Q <sub>G</sub>	17	17	nC
Gate-Drain Charge, Q <sub>GD</sub>	2.9	2.9	nC
Gate-Source Charge, Q <sub>GS</sub>	3.3	3.3	nC
Output Charge, Q <sub>OSS</sub>	36	36	nC
Gate Resistance, R <sub>G</sub>	1.5	1.5	Ω
Transconductance, g <sub>FS</sub>	100	100	S
Gate-Source Threshold Voltage, V <sub>TH</sub>	4	4	V
Diode Forward Voltage, V <sub>SD</sub>	0.8	0.8	V
Reverse Recovery Charge, Q <sub>RR</sub>		63	nC
Thermal Resistance, θ <sub>JA</sub>	50	50	°C/W

Figure 3-2. MOSFET Parameter Inputs for the BQ2575x Design Calculator

The first parameter in the design calculator is the on-state resistance (R<sub>DS(on)</sub>). This is the resistance across the drain and source terminals when the MOSFET is turned-on. The calculator asks for R<sub>DS(on)</sub> at 4.5V and 10V. R<sub>DS(on)</sub> is typically given in the data sheet either in the electrical characteristics section or in a graph that plots the V<sub>gs</sub> versus R<sub>DS(on)</sub>.

The total gate charge (Q<sub>G</sub>) refers to the charge (in Coulombs) necessary to charge the gate capacitance to turn on the MOSFET so that the actual gate voltage of the MOSFET matches the driving voltage. This is different from the switching charge. Q<sub>G</sub> is typically given in the MOSFET data sheet. The gate-drain charge (Q<sub>GD</sub>) and gate-source charge (Q<sub>GS</sub>) are also usually provided. The output charge, Q<sub>OSS</sub>, is defined in Equation 38.

$$Q_{OSS} = \int_0^{V_{DS}} C_{OSS}(v) dv \quad (38)$$

The internal gate resistance R<sub>G</sub> can be modeled by a resistor in series with the MOSFET gate, as depicted in Figure 2-1.

The transconductance (g<sub>fs</sub>) refers to the small signal gain of the MOSFET. The threshold voltage (V<sub>TH</sub>) is the voltage at which the MOSFET enters the active region and conducts current across the drain and the source terminals. Both of these parameters are typically included in the MOSFET data sheet.

The diode forward voltage (V<sub>SD</sub>) is the voltage drop across the drain and source terminals when the body diode of the MOSFET is forward biased.

The reverse recovery charge (Q<sub>RR</sub>) is the charge that is stored in the body diode that must be depleted before the body diode can block the flow of current in the reverse biased direction.

The thermal resistance is a measure of the thermal performance of the MOSFET. The higher the thermal resistance, the higher the temperature change of the MOSFET for a given power dissipation.

## 3.2 Design Calculator MOSFET Comparison Example

As an example, the design calculator is used here to compare the TI recommended MOSFET, the SiR680LDP, and the SiR880BDP as the custom MOSFET. For this example, the following operating conditions are used for both.


All other input parameters are left as the default.

**Table 3-1. Operating Conditions for Design Calculator Example**

Parameter	Value
$V_{IN}$ (minimum)	5V
$V_{IN}$ (nominal)	10V
$V_{IN}$ (maximum)	50V
$V_{BAT}$	21V
$V_{ext\_drv}$	10V
$I_{out}$	8A
$f_{sw}$	200kHz
$R_{fsw}$	200k $\Omega$
$I_{SAT}$	19A
Selected Inductance, L	10 $\mu$ H
Selected Inductor DCR	12m $\Omega$

These operating conditions then result in the following efficiency and power loss graphs.

After the yellow cells are filled in, the calculator can plot these graphs. Plot 1 is the recommendation, SiR680LDP, and plot 2 is SiR880BDP.

 

**Figure 3-3. Design Calculator Efficiency and Loss Graphs for MOSFET Comparison**

In this example, the SiR880BDP MOSFET (depicted in Plot 2) has a higher efficiency for a lighter load because of the lower gate capacitance and output capacitance. The lower capacitance reduces the switching losses. At higher loads, the conduction losses become greater than the switching losses and the SiR680LDP is more efficient because of the lower  $R_{DS(ON)}$ .



## 4 BOM Evaluation

Several BOMs have been evaluated for efficiencies and losses. Each found that efficient systems can be designed using the BQ2575x family of devices. A summary of the highest efficiencies for each BOM is included in [Table 4-1](#).

The operating condition shows the output current, the bus voltage, switching frequency, input voltage, and external gate drive voltage.

**Table 4-1. BOM Summary**


BOM Number	MOSFET Key Properties ( $R_{DS(ON)}$ , voltage rating)	Switching Frequency	Inductor Properties
1	SiR880BDP MOSFET ( $BV_{dss}=80V$ , $R_{DS(ON)}=5.3m\Omega$ for $V_{gs}=10$ , $I_d=10$ )	450kHz	CMLB135T-100MS Inductor ( $L=10\mu H$ , $DCR=22m\Omega$ )
2	AON6380 MOSFET ( $BV_{dss}=30V$ , $R_{DS(ON)}$ ( $V_{gs}=10V$ , $I_d=20A$ )=5.6mohm)	600kHz	HCM1103-2R2-R Inductor ( $L=2.2\mu H$ , $DCR=8.4m\Omega$ )
3	SiR680LDP MOSFET ( $BV_{dss}=80V$ , $R_{DS(ON)}=2.33mohm$ )	250kHz	SRP1050Wa-100M inductor ( $L=10\mu H$ , $DCR=23m\Omega$ )
4	SiR188LDP MOSFET ( $BV_{dss}=60V$ , $R_{DS(ON)}=3.1mohm$ )	350kHz	CMLB135T-6RBMS inductor ( $L=6.8\mu H$ , $DCR=15m\Omega$ )
5	SiR880BDP MOSFET ( $BV_{dss}=80V$ , $R_{DS(ON)}=5.3mohm$ for $V_{gs}=10$ , $I_d=10$ )	450kHz	IHLP6767GZER150M01 inductor ( $L=15\mu H$ , 18.8m $\Omega$ )

The following graphs show the efficiency and losses for each of these BOMs.


In [Figure 4-1](#) and [Figure 4-2](#), the efficiency is highest when  $V_{IN}$  is approximately equal to  $V_{OUT}$ . Big differences from  $V_{IN}$  to  $V_{OUT}$  reduce the duty cycle and make the charger work harder. Buck-Boost mode is the most efficient mode because the buck-phase and the boost-phase operate in a low duty cycle and the switching losses are minimized.

In [Figure 4-2](#), BOM1 is the same as the BQ25758BOM and BOM1 can cover the full range of USB-EPR voltages.


In [Figure 4-3](#), BOM2 is designed to work with the 100W USB-PD and fit the components into a small area.

 

**Figure 4-1. BOM1 Efficiency and Loss With  $V_{IN}=48V$**

 

**Figure 4-2. BOM1 Efficiency and Loss With  $V_{IN}=20V$**

 


**Figure 4-3. BOM2 With  $V_{IN}=20V$**


In **Figure 4-4**, BOM3 is designed for automotive applications to work with 12V LiFePO<sub>4</sub> batteries.

In **Figure 4-5**, BOM4 was designed to work with 140W USB-PD charging. In the graph, BOM4 is using a external gate drive supply of 7V.


In **Figure 4-6**, BOM5 is designed for automotive applications with a 48V LiFePO<sub>4</sub> battery.

 

**Figure 4-4. BOM3 Efficiency Graph With  $V_{IN}=12V$**

 


**Figure 4-5. BOM4 Efficiency Graph With  $V_{IN}=20V$**

 

**Figure 4-6. BOM5 Efficiency With  $V_{IN}=48V$**

The key takeaway here is that the end application can inform the operating conditions and BOM selection. Efficiency is highest when  $V_{IN}$  is close to  $V_{OUT}$ . These decisions can largely determine the overall efficiency of the system.


Next, a closer examination of different gate drive voltages can be performed. Now, compare cases with the same input voltage, output voltage, and BOM but with different gate drive voltages:

 

**Figure 4-7. BOM2 With  $V_{IN}=20V$  and  $V_{OUT}=15V$**


Note, the device has an internal LDO that provides the gate drive voltage for the switching converter. Having an external drive omits the losses caused by the internal LDO, REGN. The higher the input voltage, the higher the LDO losses. This effect can be observed in the above figure.

To make the graph easier to read, [Figure 4-8](#) is the gate drive supplies compared at only 5A.

 

**Figure 4-8. BOM2 With  $V_{IN}=20V$ ,  $V_{OUT}=15V$ , and  $I_{CHG}=5A$**

In this case, 7V was found to be the voltage at which the switching losses and conduction losses are lower. For 10V, the switching losses increase to offset the reduced FET conduction gained. [Figure 4-9](#) shows the increased efficiency with a 7V external gate drive.

 

**Figure 4-9. BOM2 With  $V_{IN}=20V$  and  $V_{DRV\_SUP}=7$**

## 5 Summary

The BQ2575x family of devices can be used to create efficient charger systems for a myriad of applications. The efficiency of these systems can vary based on the operating conditions of the system and BOM selection, especially the MOSFET selection. The data sheet parameters of the MOSFET need to be reviewed and considered carefully, especially the gate charge parameters and the  $R_{DS(ON)}$ . How the MOSFET is used can impact these parameters so the operating conditions like the switching frequency, the gate drive voltage, and the output load need to be considered as well.

## 6 References

1. Texas Instruments, [GaN to the rescue! Part 1: Body-diode reverse recovery](#), Technical Article
2. Texas Instruments, [BQ25756: Standalone/I<sup>2</sup>C Controlled, 1- to 14-Cell Bidirectional Buck-Boost Battery Charge Controller](#), data sheet
3. Texas Instruments, [BQ25750: Standalone/I<sup>2</sup>C Controlled, 1- to 14-Cell Bidirectional Buck-Boost Battery Charge Controller with Direct Power Path Control](#), data sheet
4. Texas Instruments, [BQ25758: I<sup>2</sup>C Controlled, Bidirectional Buck-Boost Controller with Wide Voltage Range](#), data sheet
5. Texas Instruments, [BQ25756-Design-Calc](#), design calculator
6. Vishay, [Measuring Power MOSFET Characteristics](#), application note

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2025, Texas Instruments Incorporated